

### Karnaugh map

- Karnaugh map (K-map) allows viewing the function in a picture form
- Containing the same information as a truth table
- But terms are arranged such that two neighbors differ in only one variable
- It is easy to identify which terms can be combined

• Example:

A map with 3 variables

|   |    |    |    |    |    |
|---|----|----|----|----|----|
|   | AB | 00 | 01 | 11 | 10 |
| C | 0  | 1  | 0  | 1  | 1  |
|   | 1  | 1  | 1  | 1  | 0  |

|   |   |   |   |
|---|---|---|---|
| A | B | C | F |
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

1

### Location of Min-terms in K-maps

|       |       |       |       |
|-------|-------|-------|-------|
| $x_1$ | $x_2$ | $x_3$ |       |
| 0     | 0     | 0     | $m_0$ |
| 0     | 0     | 1     | $m_1$ |
| 0     | 1     | 0     | $m_2$ |
| 0     | 1     | 1     | $m_3$ |
| 1     | 0     | 0     | $m_4$ |
| 1     | 0     | 1     | $m_5$ |
| 1     | 1     | 0     | $m_6$ |
| 1     | 1     | 1     | $m_7$ |

|       |          |       |       |       |       |
|-------|----------|-------|-------|-------|-------|
|       | $x_1x_2$ | 00    | 01    | 11    | 10    |
| $x_3$ | 0        | $m_0$ | $m_2$ | $m_6$ | $m_4$ |
|       | 1        | $m_1$ | $m_3$ | $m_7$ | $m_5$ |

(b) Karnaugh map

$$m_2 + m_6 = x_1' x_2 x_3' + x_1 x_2 x_3' = x_2 x_3'$$

(a) Truth table

2

### Simplification using K-map

- Groups of '1's of size 1x1, 2x1, 1x2, 2x2, 4x1, 1x4, 4x2, 2x4, or 4x4 are called prime implicants (p.159 in textbook).

|   |    |    |    |    |    |
|---|----|----|----|----|----|
|   | AB | 00 | 01 | 11 | 10 |
| C | 0  | 1  | 0  | 1  | 1  |
|   | 1  | 1  | 1  | 1  | 0  |

|   |    |    |    |    |    |
|---|----|----|----|----|----|
|   | AB | 00 | 01 | 11 | 10 |
| C | 0  | 1  | 0  | 1  | 1  |
|   | 1  | 1  | 1  | 1  | 0  |

- A '1' in the K-map can be used by more than one group
- Some rule-of-thumb in selecting groups:
  - Try to use as few group as possible to cover all '1's.
  - For each group, try to make it as large as you can (i.e., if you can use a 2x2, don't use a 2x1 even if that is enough).

3

### Examples of 3-Variable K-map

|       |          |    |    |    |    |
|-------|----------|----|----|----|----|
|       | $x_1x_2$ | 00 | 01 | 11 | 10 |
| $x_3$ | 0        | 0  | 0  | 1  | 1  |
|       | 1        | 1  | 0  | 0  | 1  |

$f = x_1 x_3 + \bar{x}_2 x_3$

|       |          |    |    |    |    |
|-------|----------|----|----|----|----|
|       | $x_1x_2$ | 00 | 01 | 11 | 10 |
| $x_3$ | 0        | 1  | 1  | 1  | 1  |
|       | 1        | 0  | 0  | 0  | 1  |

$f = \bar{x}_3 + x_1 \bar{x}_2$

4

### Karnaugh maps with up to 4 variables

- Example: 1, 2, 3, and 4 variables maps are shown below

|   |   |   |
|---|---|---|
| A | 0 | 1 |
| 0 | 0 | 1 |
| 1 | 1 | 1 |

|   |   |   |   |
|---|---|---|---|
|   | A | 0 | 1 |
| B | 0 | 1 | 0 |
|   | 1 | 0 | 1 |

|   |    |    |    |    |    |
|---|----|----|----|----|----|
|   | AB | 00 | 01 | 11 | 10 |
| C | 0  | 1  | 1  | 1  | 1  |
|   | 1  | 1  | 0  | 1  | 0  |

|    |    |    |    |    |    |
|----|----|----|----|----|----|
|    | AB | 00 | 01 | 11 | 10 |
| CD | 00 | 1  | 1  | 1  | 1  |
|    | 01 | 1  | 0  | 1  | 0  |
|    | 11 | 0  | 1  | 1  | 0  |
|    | 10 | 0  | 1  | 1  | 0  |

- What if a function has 5 variables?

5

### Farmer's example and truth tables

6

### Farmer's example truth tables and K-maps

- With three variables, we do not want W and G or G and C to be equal (both 0 or both 1) at the same time
- With four variables, it is not a problem if F is also the same

| W | G | C | A1 | WG | GC | CF | A2 |
|---|---|---|----|----|----|----|----|
| 0 | 0 | 0 | 1  | 00 | 00 | 00 | 0  |
| 0 | 0 | 1 | 1  | 00 | 01 | 01 | 1  |
| 0 | 1 | 0 | 0  | 01 | 00 | 00 | 0  |
| 0 | 1 | 1 | 1  | 01 | 01 | 01 | 1  |
| 1 | 0 | 0 | 1  | 10 | 00 | 00 | 0  |
| 1 | 0 | 1 | 0  | 10 | 01 | 01 | 1  |
| 1 | 1 | 0 | 1  | 11 | 00 | 00 | 0  |
| 1 | 1 | 1 | 1  | 11 | 01 | 01 | 1  |

A1

A2

A1 =  $\bar{W}\bar{G} + \bar{W}G + W\bar{G} + WG$   
A2 =  $\bar{W}\bar{C} + \bar{W}C + W\bar{C} + WC$

### K-map for 5-variables functions

$f_1 = \bar{x}_1x_3 + x_1\bar{x}_3x_4 + x_1\bar{x}_2\bar{x}_3x_5$

### K-map for 5-variables functions

$F(A,B,C,D,E) = \sum m(2,5,7,8,10,13,15,17,19,21,23,24,29,31)$   
 $F(A,B,C,D,E) = CE + AB'E + BC'D'E' + A'C'DE'$

### K-map for 6-variable functions

$G(A,B,C,D,E,F) = \sum m(2,8,10,18,24,26,34,37,42,45,50,53,58,61)$

$G(A,B,C,D,E,F) = D'E'F' + ADE'F + A'CD'F'$

### K-map Example for Adder functions

| A | B | C | S | Count |
|---|---|---|---|-------|
| 0 | 0 | 0 | 0 | 0     |
| 0 | 0 | 1 | 1 | 0     |
| 0 | 1 | 0 | 1 | 0     |
| 0 | 1 | 1 | 0 | 1     |
| 1 | 0 | 0 | 1 | 0     |
| 1 | 0 | 1 | 0 | 1     |
| 1 | 1 | 0 | 0 | 1     |
| 1 | 1 | 1 | 1 | 1     |

$S(A,B,C) = \sum m(1,2,4,7)$   
 $Count(A,B,C) = \sum m(3,5,6,7)$

S


Count

$S = A'B'C + A'BC' + AB'C' + ABC$   
 $Count = BC + AC + AB$

### Minimization of POS Forms

POS minimization of  $f = \Pi M(4, 5, 6)$
 
### Minimization of 4-Var. Function in POS Form



POS minimization of  $f = \Pi M(0, 1, 4, 8, 9, 12, 15)$


13

### 7-segment display

14

 
### Simplification of 'g' in 7-segment display

$$g = Z'YX'W' + ZY'X'W' + Z'YX'W + ZYX'W + ZY'X'W + Z'Y'XW + ZYXW + ZY'XW + Z'Y'XW' + Z'YXW' + ZYXW' + ZY'XW'$$




15
 
### Minimization of Product-of-Sums Forms



$$g = ZY' + XW' + ZW + Y'X + Z'YX'$$

 Cost = 22  
(5 AND gates,  
1 OR gates  
16 inputs)




$$g = (Z+Y+X) \cdot (Z+Y'+X'+W') \cdot (Z'+Y'+X+W)$$

Cost = 18  
(3 OR gates,  
1 AND gates  
14 inputs)

16
 
### Simplification of 'a' in 7-segment display


$$a = Z'Y'X'W' + ZYX'W' + ZY'X'W' + Z'YX'W + Z'YX'W + ZY'X'W + Z'Y'XW + Z'YXW + ZYXW + Z'Y'XW' + Z'YXW' + ZYXW' + ZY'XW'$$



$$a = Y'W' + ZW' + Z'X + YX + Z'YW + ZY'X'$$

17

### Simplification of 'a' in POS Form

 

SOP:  $a = Y'W' + ZW' + Z'X + YX + Z'YW + ZY'X'$

Cost = ( 4 AND gates, 1 OR gates inputs)


POS:

Cost = ( 3 AND gates, 1 OR gates inputs)

18
 
### K-map with Don't Care Conditions

- *Don't care condition* is input combination that will never occur.
- So the corresponding output can either be 0 or 1.
- This can be used to help simplifying logic functions.
- Example:  $F(A,B,C,D) = \sum m(1,3,7,11,15) + \sum D(0,2,5)$



$$F = CD + A'B'$$


$$F = CD + A'D$$

d: Don't Care Condition

19
 
### Examples

- Simplify the following function considering:
  - the sum-of-products form
  - the product-of-sums form




20

### 1-bit building blocks to make n-bit circuit

- Design a 1-bit circuit with proper "glue logic" to use it for n-bits
  - It is called a bit slice
  - The basic idea of bit slicing is to design a 1-bit circuit and then piece together n of these to get an n-bit component

 • Example:

- A half-adder adds two 1-bit inputs
- Two half adders can be used to add 3 bits
- A 3-bit adder is a full adder
- A full adder can be a bit slice to construct an n-bit adder




| A | B | S | C |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

21
 
### Full adder & multi-bit ripple-carry adder


- Two half adders can be used to add 3 bits
- n-bit adder can be built by full adders
- n can be arbitrary large



22
 
### Multiple Function Unit Design


- Design a unit that can do more than one function
- In that case, we can design a function unit for each operation like ADD, SUB, AND, OR, ...
- And then select the desired output
- For example, if we want to be able to perform ADD and SUB on two given operands A and B, and select any one
- Then the following set up will work



23
 
### Design of a SUB Unit

- An n-bit subtract unit can be designed in the same way as an n-bit adder
- One bit subtract unit: It has two inputs A and B (B is subtracted from A) and a borrow (w)
- Outputs: R (primary), W borrow (cascading)
- Borrow from one stage is fed to the next stage
- Truth table is shown
- An n-bit subtract circuit is shown



| A | B | w (in) | R | w(out) |
|---|---|--------|---|--------|
| 0 | 0 | 0      | 0 | 0      |
| 0 | 0 | 1      | 0 | 1      |
| 0 | 1 | 0      | 1 | 0      |
| 0 | 1 | 1      | 1 | 0      |
| 1 | 0 | 0      | 1 | 0      |
| 1 | 0 | 1      | 1 | 0      |
| 1 | 1 | 0      | 1 | 1      |
| 1 | 1 | 1      | 1 | 1      |

24


### ADD/SUB unit design – First Idea

- Separate ADD and SUB units are expensive
- We can simplify the design
- $A - B$  is the same as adding negation of B to A
- How to negate?
  - 2's complement (i.e., take 1's complement and add 1)
  - Adding 1 is also expensive
  - It needs an n-bit adder in general
  - However, we only need to add two bits in each stage
    - In the first stage, we need to add 1's complement of LSB and 1
    - In other stages, we need to add carry output of previous bit to 1's complement of current bit
- We select B or negation of B depending on the requirement
- We add A to the selected input to obtain the result

25
 
### ADD/SUB unit design – Better Idea

- 2's complement generation of B is expensive
- We can take 1's complement of B and add it to A
- Then we need to add 1 to the result
- This can be done by setting input carry=1 to n-bit adder
- For add, we simply add B to A with input carry = 0
- Selection signal ADD/SUB = 0 for ADD and 1 for SUB
- The block diagram is shown below
- MUX and inverter can be replaced by XOR (B, ADD/SUB)



26

### ADD/SUB unit design – Better Idea Example


Example: Find A-B  
A=0101, B=0110

1's comp. of B  
(i.e., neg (B))  
= 1001  
2's comp. of B  
= 1010

First Idea:  
 $A + (\text{comp}(B) + 1)$

$$\begin{array}{r} 0101 \\ + \quad \leftarrow 2\text{'s} \\ \hline \end{array}$$

Better Idea:  
 $A + \text{comp}(B) + 1$
 
$$\begin{array}{r} \phantom{0}1 \\ 0101 \\ + \quad \leftarrow 1\text{'s} \\ \hline \end{array}$$


27

### ADD/SUB unit design – Better Idea Operation


Example: Find A-B  
A=0101, B=0110

1's comp. of B  
(i.e., neg (B))  
= 1001  
2's comp. of B  
= 1001 + 1 = 1010

First Idea:  
 $A + (\text{neg}(B) + 1)$

$$\begin{array}{r} 0000 \\ 0101 \\ + 1010 \leftarrow 2\text{'s} \\ \hline 1111 \end{array}$$


Better Idea:  
 $A + \text{neg}(B) + 1$
 
$$\begin{array}{r} 00011 \\ 0101 \\ + 1001 \leftarrow 1\text{'s} \\ \hline 1111 \end{array}$$


28
 
### One-Bit Adder

- Takes three input bits and generates two output bits
- Multiple bits can be cascaded



29

### Adder Boolean Algebra

- A B C<sub>i</sub> C<sub>o</sub> S
  - 0 0 0 0 0
  - 0 0 1 0 1
  - 0 1 0 0 1
  - 0 1 1 1 0
  - 1 0 0 0 1
  - 1 0 1 1 0
  - 1 1 0 1 0
  - 1 1 1 1 1
- $$C = A.B + A.C_i + B.C_i$$
- $$S = A.B.C_i + A'.B'.C_i + A'.b.C_i + a.B'.C_i$$

30

### Detecting Overflow

- No overflow when adding a positive and a negative number
- No overflow when signs are the same for subtraction
- Overflow occurs when the value affects the sign:
  - overflow when adding two positives yields a negative
  - or, adding two negatives gives a positive
  - or, subtract a negative from a positive and get a negative
  - or, subtract a positive from a negative and get a positive
- Consider the operations  $A + B$ , and  $A - B$ 
  - Can overflow occur if  $B$  is 0 ?
  - Can overflow occur if  $A$  is 0 ?

31

### Problem: ripple carry adder is slow

- Is a 32-bit ALU as fast as a 1-bit ALU?
- Is there more than one way to do addition?
  - two extremes: ripple carry and sum-of-products

Can you see the ripple? How could you get rid of it?

$$c_1 = b_0c_0 + a_0c_0 + a_0b_0$$

$$c_2 = b_1c_1 + a_1c_1 + a_1b_1 \quad c_2 =$$

$$c_3 = b_2c_2 + a_2c_2 + a_2b_2 \quad c_3 =$$

$$c_4 = b_3c_3 + a_3c_3 + a_3b_3 \quad c_4 =$$

Not feasible! Why?

32

### Carry-look-ahead adder

- An approach in-between our two extremes
- Motivation:
  - If we didn't know the value of carry-in, what could we do?
  - When would we always generate a carry?  $g_i = a_i b_i$
  - When would we propagate the carry?  $p_i = a_i + b_i$
- Did we get rid of the ripple?

$$c_1 = g_0 + P_0c_0$$

$$c_2 = g_1 + P_1c_1 \quad c_2 = g_1 + P_1g_0 + P_1P_0c_0$$


$$c_3 = g_2 + P_2c_2 \quad c_3 = g_2 + P_2g_1 + P_2P_1g_0 + P_2P_1P_0c_0$$

$$c_4 = g_3 + P_3c_3 \quad c_4 = g_3 + P_3g_2 + P_3P_2g_1 + P_3P_2P_1g_0 + P_3P_2P_1P_0c_0$$

Feasible! Why?

33


### A 4-bit carry look-ahead adder

 

- Generate  $g$  and  $p$  term for each bit
- Use  $g$ 's,  $p$ 's and carry in to generate all  $C$ 's
- Also use them to generate block  $G$  and  $P$
- CLA principle can be used recursively

34

### Use principle to build bigger adders

 

- A 16 bit adder uses four 4-bit adders
- It takes block  $g$  and  $p$  terms and  $c_{in}$  to generate block carry bits out
- Block carries are used to generate bit carries
  - could use ripple carry of 4-bit CLA adders
  - Better: use the CLA principle again!

35

### Delays in carry look-ahead adders

- 4-Bit case
  - Generation of  $g$  and  $p$ : 1 gate delay
  - Generation of carries (and  $G$  and  $P$ ): 2 more gate delay
  - Generation of sum: 1 more gate delay
- 16-Bit case
  - Generation of  $g$  and  $p$ : 1 gate delay
  - Generation of block  $G$  and  $P$ : 2 more gate delay
  - Generation of block carries: 2 more gate delay
  - Generation of bit carries: 2 more gate delay
  - Generation of sum: 1 more gate delay
- 64-Bit case
  - 12 gate delays

36