


Sequential Circuit and State Machine

- Combinational circuits
 - output is simply dependent on the current input
- Sequential circuits
 - output may depend on the input sequence
- The effect of the input sequence can be memorized as a state of the system
- So a sequential circuit is also called a State Machine
- Memory elements (usually D flop-flips) are used to store the state
- System state changes with input
- A different input sequence produces different final state and different output sequence

1

State Transition Diagram (or State Diagram)

 - Example:
 - A very simple machine to remember which building I am at
 - The only input is the clock signal
 - The state machine is represented as a state transition diagram (or called state diagram) below
 - One step (i.e., transition) can be taken whenever there is a clock signal



2

State Transition Table (State Table)

- States can be coded as binary combinations of variables
- Let N be total number of states, each state can be represented by $n = \log_2 N$ bits
- n bits can represent up to 2^n states
- This is called the state assignment
- A truth table will then give the next state
- This is called a state transition table (or called state table)
- x_n and y_n can be specified in terms x_o and y_o


	X	Y
S0	0	0
S1	0	1
S2	1	0
S3	1	1

Current State $x_o y_o$	Next State $x_n y_n$
0 0	0 1
0 1	1 0
1 0	1 1
1 1	0 0

$x_n = x_o \oplus y_o$
 $y_n = y_o'$

3

 The Resulting Sequential Circuit / State Machine



4

Counter state machine

- A counter counts
- Number of elements in counter determines how many different states we need
- For example, an eight-state counter can count eight steps

Current X Y Z	Next X Y Z	
000	001	X=
001	010	
010	011	Y=
011	100	
100	101	Z=
101	110	
110	111	
111	000	

5

Another counter

- Counter need not have number of states that is equal to a power of 2
- Here is a five state counter
- Is it simpler?


Current X Y Z	Next X Y Z	
000	001	X=
001	010	
010	011	Y=
011	100	
100	000	Z=

6

State Machine with Explicit Inputs

- In a state transition diagram, state may change with time
- A clock signal represents passage of time
- Each time a clock arrives, state changes to next state
- Clock is an implicit input
- There may or may not be other explicit inputs

 - For the previous example, let say we also have an explicit input i
- For the state transition diagram shown, i can be 0 or 1
- Next state depends on current state and the value of input i
- When the next state depends upon the inputs, the inputs are examined at the clock edges



State Transition Table with Explicit Inputs

- State transition table will have two sets of inputs
- Current state variable and explicit input variables
- Total number of row in table is $2^{(n+m)}$
 - n is number of variables representing states
 - m is number of input variables

State Assignment

	X	Y
S0	0	0
S1	0	1
S2	1	0
S3	1	1

Current		Input	Next State	
x_0	y_0	i	x_n	y_n
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	1	1
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	0	1

$$x_n = x_0' y_0' i + x_0' y_0 i' + x_0 y_0' i + x_0 y_0 i'$$

$$= x_0' i + x_0' y_0 + x_0 y_0' i'$$

$$y_n = x_0' y_0' i' + x_0' y_0 i + x_0 y_0' i' + x_0 y_0 i$$



$$= y_0' i' + y_0 i$$

Output of state machine

- Output of a state machine may depend on state, or state & input:
 - Mealy machine: Output depends on both current state and current input (i.e., depends on transition)
 - Moore machine: Output depends on current state
- Thus we have two different circuits to implement
 - 1. Decides what is the next state
 - 2. Decides what is the output
- Both circuits are combinational
- States are remembered by memory elements
 - Usually D flips-flops are used to remember states


State Transition Diagram with Outputs

  - Moore Machine: (For example, output 1 whenever in Coover)
- Mealy Machine: (For example, output 1 whenever walking between Coover and Durham)




Overall structure of a State machine

 Moore machine (outputs depend on current state, but not current inputs)



 Mealy machine (outputs depend on both current state and current inputs)



Steps in designing a state machine

- Start writing a state transition diagram
 - It has an initial state
 - It has other states to keep track of various activities
 - It has some transitions
- Generate a state transition table and an output table
- Write state transition table and output table in binary
 - Needs state assignment, i.e., the code used for each state
 - State assignment is a complex process
 - For the time being assume straightforward combinations
- Derive canonical sum-of-product expressions
 - You can simplify the expressions

Determining number of states

- Identify how many different things we need to keep track of
- This is critical to know
- Otherwise the number of states (and their meaning) may get out of hand very quickly
- This is different from what is the output of interest (in each state we may have some outputs)
- For example, if we are to process a sequence of input bits, depending on interest, the number of states may be different
 - If we need to know how many 1's there are, we need states corresponding to the count
 - If we need to know if we have even or odd number of 1's, we may need only two states

13


Example

- Design a state machine that will repeatedly display in binary values 1, 3, 5, and 7
- Solutions:
 - How many states we need?
 - What is the state transition diagram?
 - What is the output in each state?
 - What is the next state logic?
 - Construct the truth tables with state variables
 - Derive the next state logic and output logic
 - Draw the circuits

14

Example (contd.)

- We need four states: S0, S1, S2, S3

 

State transition table		Implementation level state transition table		Output table		Implementation level output tables						
Current State	Next State	Current X	Next Y	Current X	Next Y	Current State	Output	Current X	Current Y	Output L2	Output L1	Output L0
S0	S1	0	0	0	1	S0	1	0	0	0	0	1
S1	S2	0	1	1	0	S1	3	0	1	0	1	1
S2	S3	1	0	1	1	S2	5	1	0	1	0	1
S3	S0	1	1	0	0	S3	7	1	1	1	1	1

$$\begin{aligned}
 X &= X'Y + XY' & L2 &= XY' + XY = X \\
 Y &= X'Y' + XY' = Y' & L1 &= X'Y + XY = Y \\
 & & L0 &= X'Y' + X'Y + XY' + XY = X' + X = 1
 \end{aligned}$$


15

Another Example for State Machine

- Design a state machine to display the characters in the string HELLO using a seven segment display
- How many states do we need?
 - Five, one for each character
 - In state S0 (000) we display H
 - In state S1 (001) we display E
 - In state S2 (010) we display L
 - In state S3 (011) we display L
 - In state S4 (100) we display O
- State transitions are
 - S0 -> S1
 - S1 -> S2
 - S2 -> S3
 - S3 -> S4
 - S4 -> S0

16

Example (contd.)

 


- Next State and Output logic tables are

Cur State Xc Yc Zc	Next State Xn Yn Zn	State Xc Yc Zc	Output a b c d e f g
0 0 0	0 0 1	0 0 0	0 1 1 0 1 1 1
0 0 1	0 1 0	0 0 1	1 0 0 1 1 1 1
0 1 0	0 1 1	0 1 0	0 0 0 1 1 1 0
0 1 1	1 0 0	0 1 1	0 0 0 1 1 1 0
1 0 0	0 0 0	1 0 0	1 1 1 1 1 1 0

17

To Detect if # of 1's in Input is Divisible by 3

- Design a state machine with 1 bit of input and 1 bit of output
- The output bit will be 1 whenever the number of bits in input sequence is divisible by 3
- How many states do we need?
- What are the meaning of the states?
 - In state S0 (00), remainder = 0 (i.e., divisible by 3)
 - In state S1 (01), remainder = 1
 - In state S2 (10), remainder = 2
- Choose to design a Moore machine
 - Output is 1 whenever in state S0

 

18

State machines as sequence detector

- State machine by nature are ideally suited to track state and detect specific sequence of events
- For example, we may design specific machines to track certain pattern in an input sequence
- Examples:
 - to count 1's in a sequence and produce an output if a specific situation occurs like 3rd one, or every 2nd one, or nth one
 - to generate an output or stop if a specific pattern in the sequence (such as 011 or 0101 or 1111) is observed
- In each of these cases, it is to create a relationship between input and output sequence
- We will review input and output relations for such operations

19

Example input/output sequences

- n-th one detector, n=2
 - Input: 0 0 1 0 0 1 1 1 0 1 1 0 0 1 0 1 0 1 0 1 1 1 0 0 0 1
 - Output: 0 0 0 0 0 1 0 1 0 0 1 0 0 0 0 1 0 0 0 1 0 1 0 0 0 0
- n-th one detector, n=3
 - Input: 0 0 1 0 0 1 1 1 0 1 1 0 0 1 0 1 0 1 0 1 1 1 0 0 0 1
 - Output: 0 0 0 0 0 0 1 0 0 0 1 0 0 0 0 0 0 0 1 0 0 0 1 0 0 0 0
- 011 pattern detector
 - Input: 0 0 1 0 0 1 1 1 0 1 1 0 0 1 0 1 0 1 0 1 1 1 0 0 0 1
 - Output: 0 0 0 0 0 0 1 0 0 0 1 0 0 0 0 0 0 0 0 0 0 1 0 0 0 0 0
- 1010 pattern detector
 - Input: 0 0 1 0 0 1 1 1 0 1 1 0 0 1 0 1 0 1 0 1 1 1 0 0 0 1
 - Output: 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 1 0 1 0 0 0 0 0 0

20


How to design sequence detector

- Our goal is to be able to identify minimum number of states
- It is very easy to miss that goal (in terms of number of states)
- Sometimes CAD tools may identify redundant states
- We first discuss the number of possible states to track
- For example in sequence detection, for 011,
 - we need states representing we have not seen the first zero, we have seen only the first 0, we have seen 01, and finally we have seen 011
 - So a four state system will work
- 1010 has a pattern that also repeats part of the sequence
 - So we need states that represent starting state, received first 1, first 10, first 101, and finally 1010 (a total of five state)
 - However after we see 1010, we have already seen 10 pattern for the next output (i.e., if we have 101010 repeating)

21

3-rd One Detector

 - Use a Mealy machine design
- 3 states are enough
- Have a similar structure to the Moore machine to detect if # of 1's in Input is Divisible by 3



- If Moore machine design is used, 4 states is needed

22

Design of a sequence detector for 011

- Four states and state transitions are shown in the figure
- Output: 1 for State S3, 0 for all others




Current State	Input	Next State	State Assignment		Output of states	
Current State	Input	Next State	Current State	Binary	Current State	Out put
S0	0	S1				
S0	1	S0	S0	00	S0	0
S1	0	S1	S1	01	S1	0
S1	1	S2	S2	10	S2	0
S2	0	S1	S3	11	S3	1
S2	1	S3				
S3	0	S1				
S3	1	S0				

23

Design of a sequence detector for 1010

 - Four states and state transitions are shown in the figure
- Output: 1 for State S4, 0 for all others



Current State	Input	Next State	State Assignment		Output of states	
Current State	Input	Next State	Current State	Binary	Current State	Out put
S0	0	S0				
S0	1	S1	S0	000	S0	0
S1	0	S2	S1	001	S1	0
S1	1	S1	S2	010	S2	0
S2	0	S0	S3	011	S3	0
S2	1	S3	S4	100	S4	1
S3	0	S4				
S3	1	S3				
S4	0	S0				
S4	1	S3				

24

Another example: a complex vending machine

- Vending Machine
 - Collect money, deliver product and change
- Vending machine may get three inputs, n, d, q
 - Inputs are nickel (5c), dime (10c), and quarter (25c)
 - Only one coin input at a time
 - Product cost is 40c
 - Does not accept more than 50c (blocks the coin slot)
 - Returns 5c or 10c back
 - Exact change appreciated
- How many states?
- What are the output signals?


25

Design of Complex Vending Machine

- We are designing a Mealy state machine (i.e., output depends on both current state and inputs).
- Suppose we ask the machine to directly return the coin if it cannot accept an input coin.
- The following two-bit code is used:
 - 00 -- no coin, 01 -- nickel, 10 -- dime, and 11 -- quarter
- Inputs: I_1, I_2 which represent the coin inserted
- Outputs: C_1, C_2, P where C_1, C_2 represent the coin returned and P indicates whether to deliver product
- States: S00, S05, S10, S15, S20, S25, S30, S35
 - 3 bits are enough to encode the states
 - Notice the names (they need not be S0, S1...)
- State assignment: S00 - 000, S05 - 001, S10 - 010, S15 - 011, S20 - 100, S25 - 101, S30 - 110, S35 - 111

26


State Diagram for Vending Machine

 

27


Algorithmic State Machine (ASM) Charts

 - Another way to represent a state machine
- State diagrams are useful when the machine has only a few inputs and outputs
- ASM charts may be more convenient for larger machines




28

Example: Moore Machine

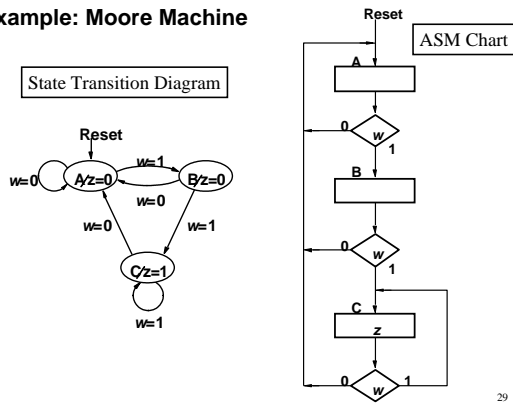

29

Example: Mealy Machine

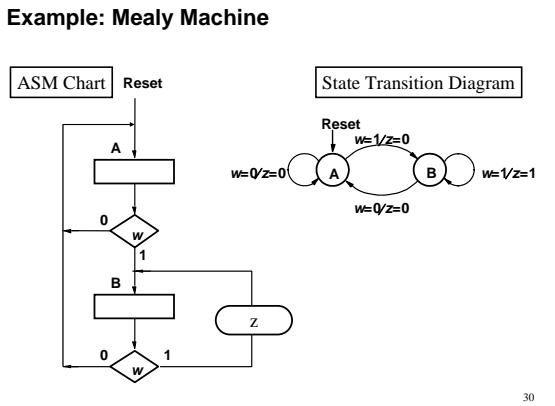

30