

### Timing Consideration


- Circuit timing is a very important consideration in the design of any electronic systems
- The following timing issues are considered:
  - For Flip-flops:
    - Set-up time
    - Hold time
    - Propagation delay
  - For Combinational circuits:
    - Contamination delay
    - Propagation delay
  - For Sequential circuits: (this lecture)
    - Clock frequency / Clock cycle time

### Speed of Sequential circuit and Clock frequency

- Clock frequency
    - is the number of rising clock edges (clock ticks) in a fixed period of time
    - determines the speed of a sequential circuit
  - Clock cycle time (or clock period) is the time between two rising clock edges
  - If circuit runs at clock frequency of  $f$ , corresponding clock cycle time is
    - $T = 1/f$ , or
    - $f = 1/T$
  - A frequency of 1 MHz gives a clock period of 1 micro second
  - A frequency of 500 MHz gives a clock period of 2 nano second
  - A frequency of 2 GHz gives a clock period of 0.5 nano second
  - A frequency of 1 GHz gives a clock period of 1 nano second
- (1 micro second =  $1e-6$  second, 1 nano second =  $1e-9$  second)

 
### Timing in a Sequential Circuit (State machine)

- From a rising clock edge, we should allow enough time for:
  - D FFs to generate stable output for the state
  - next state logic to generate the next state
  - D FFs to set up after the next state is available
- Then we can have the next rising clock edge
- Thus, D Flip-Flop propagation delay + Next state logic propagation delay + D FF set-up time sets a lower bound to the clock cycle time


 
### Review: Timing Issues of Combinational Circuits

- Contamination delay:
  - Minimum delay before any output starts to change once input changes
- Propagation delay:
  - Maximum delay after which all outputs are stable once input changes



- Contamination delay = 2
- Propagation delay = 3
- (Assume that delay of all gates = 1)

### Propagation delay for next-state logic

- The propagation delay for next-state logic is also called the compute time
- Consider a four states system  $S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3$
- State transition table and implementation level state transition table are given below



Current State	Next State	Current X	Current Y	Next X	Next Y
S0	S1	0	0	0	1
S1	S2	0	1	1	0
S2	S3	1	0	1	1
S3	S0	1	1	0	0

- Using the logic expressions below, combination logic for next state takes up to two gate delay (if both X and X' are available)

$$X := X'Y + XY'$$

$$Y := X'Y' + XY' = Y'$$


### Review: Timing Issues of FFs

  

- For this design:
- Set-up time = 5
- Hold time = 1
- Prop. delay = 3
- (Assume that delay of all gates = 1)
 
### Timing Constraints for a Sequential Circuit

- Clock cycle time  $\geq$  FF Prop delay + Compute time + FF set-up time
- Clock low time  $\geq$  FF set-up time
- Clock high time  $\geq$  FF Prop delay
- Contamination time of next state circuit  $\geq$  FF hold time




### Some Relationships in Sequential Circuit timing

- Let
  - $T$  be the clock period
  - $t_{pd}$  be the propagation time of next-state logic circuit
  - $t_{cd}$  be the contamination time of next-state logic circuit
  - $t_{rd}$  be the propagation time of FF (register) circuit
  - $t_{st}$  be the set-up time of FF (register) circuit
  - $t_{ht}$  be the hold time of FF (register) circuit
- What is the minimum clock period?  $T = t_{pd} + t_{rd} + t_{st}$
- By how long must any change in external inputs precede the next clock edge?  $\geq t_{pd} + t_{st}$
- How long after the clock edge must the external inputs be held valid?  $\geq t_{ht} - t_{cd}$
- What is the smallest time after the clock edge that outputs of state machine can be expected to be valid?  $t_{rd} + \text{propagation delay of output logic}$
 
### n-bit Equality Comparator


- First, we build a circuit to compare two n-bit numbers for equality



- We want to build the n-bit circuit using 1-bit building blocks
- Start with MSB and compare one bit at a time
  - If the two bits are different, then the numbers are different. This becomes the solution.
  - Else, i.e., if the two bits are equal, then compare the next bit.
 
### Basic building block for n-bit Equality Comparator


- 1-bit comparator forms the building block for comparing two n-bit numbers.
- E is the cascading signal
- $E_{i+1}$  is the Cascading input,  $E_i$  is the cascading output
- $E_{i+1} = 0$  implies that the two numbers are not equal so far
- $E_{i+1} = 1$  implies that the two numbers are equal so far
- If  $E_{i+1} = 0$ , then  $E_i = 0$
- else if  $E_{i+1} = 1$ , then  $E_i = A_i \text{ XOR } B_i$
- In other words,  $E_i = E_{i+1} \cdot (A_i \text{ XOR } B_i)$



$A_i$	$B_i$	$E_{i+1}$	$E_i$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1
 
### Building an n-bit Equality Comparator

- Using the building block, we can build an n-bit comparator circuit
- The final result is, if  $E_0 = 1$ , then  $A = B$  and if  $E_0 = 0$ , then  $A \neq B$
- What is the value of input  $E_n$  ?




### Another View of the n-bit Equality Comparator

- $E_{n-1} = E_n \cdot (A_{n-1} \text{ XOR } B_{n-1}) = (A_{n-1} \text{ XOR } B_{n-1})$
- $E_{n-2} = E_{n-1} \cdot (A_{n-2} \text{ XOR } B_{n-2})$
- .....
- $E_1 = E_2 \cdot (A_1 \text{ XOR } B_1)$
- $E_0 = E_1 \cdot (A_0 \text{ XOR } B_0)$
- Therefore,
  - $E_0 = (A_{n-1} \text{ XOR } B_{n-1}) \cdot (A_{n-2} \text{ XOR } B_{n-2}) \cdot \dots \cdot (A_1 \text{ XOR } B_1) \cdot (A_0 \text{ XOR } B_0)$
- We don't need to build a chain. We can use n XOR gates to compare the n bit pairs first. Then we can use a n-bit AND gate to combine the n results together.
 
## n-bit Complex Comparator

- Next, we compare the two numbers for  $A > B$ ,  $A = B$ , or  $A < B$




If  $A > B$ ,  $(A > B)_{out} = 1$ ,  $(A = B)_{out} = 0$ ,  $(A < B)_{out} = 0$   
 If  $A = B$ ,  $(A > B)_{out} = 0$ ,  $(A = B)_{out} = 1$ ,  $(A < B)_{out} = 0$   
 If  $A < B$ ,  $(A > B)_{out} = 0$ ,  $(A = B)_{out} = 0$ ,  $(A < B)_{out} = 1$

- Again, we want to build the n-bit circuit using 1-bit building blocks
- Similarly, we start with MSB and compare one bit at a time
 
## 1-bit Complex Comparator


- The basic building block for the purpose is as shown
  - The primary inputs are  $A_i$  and  $B_i$
  - Cascading inputs are  $(A > B)_{in}$ ,  $(A = B)_{in}$ , and  $(A < B)_{in}$
  - Cascading outputs are  $(A > B)_{out}$ ,  $(A = B)_{out}$ , and  $(A < B)_{out}$

- The equations can be directly written as
- $(A > B)_{out} = (A > B)_{in} + (A = B)_{in} \cdot (A_i \cdot B_i')$
- $(A < B)_{out} = (A < B)_{in} + (A = B)_{in} \cdot (A_i' \cdot B_i)$
- $(A = B)_{out} = (A = B)_{in} \cdot (A_i \cdot B_i + A_i' \cdot B_i')$



 
## Building an n-bit Complex Comparator

- Using the building block, we can build an n-bit comparator circuit
- The final result:
  - If  $A > B$ ,  $(A > B)_{out} = 1$ ,  $(A = B)_{out} = 0$ ,  $(A < B)_{out} = 0$
  - If  $A = B$ ,  $(A > B)_{out} = 0$ ,  $(A = B)_{out} = 1$ ,  $(A < B)_{out} = 0$
  - If  $A < B$ ,  $(A > B)_{out} = 0$ ,  $(A = B)_{out} = 0$ ,  $(A < B)_{out} = 1$
- What are the values of the inputs  $(A > B)_{in}$ ,  $(A = B)_{in}$ ,  $(A < B)_{in}$ ?


 
## 1-bit Simplified complex comparator

- The 1-bit complex comparator block is modified to have fewer cascading signals
- It has two primary inputs, two cascading inputs, and two cascading outputs
- The equations for the outputs are
- $(A > B)_{out} = (A > B)_{in} + (A < B)_{in}' \cdot (A_i \cdot B_i')$
- $(A < B)_{out} = (A < B)_{in} + (A > B)_{in}' \cdot (A_i' \cdot B_i)$
- If both  $(A > B)_{out}$  and  $(A < B)_{out}$  are 0, then the two numbers are equal so far



## 1-bit maximizer building block

- The 1-bit maximizer block is similar to the simplified complex comparator
- Primary inputs:  $A_i$ ,  $B_i$       Cascading inputs:  $(A > B)_{in}$ ,  $(A < B)_{in}$   
 Primary output:  $M_i$       Cascading outputs:  $(A > B)_{out}$ ,  $(A < B)_{out}$
- $M_i$  is either  $A_i$  or  $B_i$  depending on whether  $A$  or  $B$  is greater (not just depending on the current bits  $A_i$  and  $B_i$ )
- The equations for the outputs are
  - $(A > B)_{out} = (A > B)_{in} + (A < B)_{in}' \cdot (A_i \cdot B_i')$
  - $(A < B)_{out} = (A < B)_{in} + (A > B)_{in}' \cdot (A_i' \cdot B_i)$
  - $M_i = (A > B)_{in} \cdot A_i + (A < B)_{in} \cdot B_i + (A > B)_{in}' \cdot (A < B)_{in}' \cdot (A_i + B_i)$

