 


## A 32 bit ALU

- A Ripple carry ALU
- Two bits decide operation
  - Add/Sub
  - AND
  - OR
  - LESS
- 1 bit decide add/sub operation
- A carry in bit
- Bit 31 generates overflow and set bit



1

## Problem: ripple carry adder is slow

- Is a 32-bit ALU as fast as a 1-bit ALU?
- Is there more than one way to do addition?
  - two extremes: ripple carry and sum-of-products

Can you see the ripple? How could you get rid of it?

$$\begin{aligned}
 c_1 &= b_0c_0 + a_0c_0 + a_0b_0 \\
 c_2 &= b_1c_1 + a_1c_1 + a_1b_1 \quad c_2 = \\
 c_3 &= b_2c_2 + a_2c_2 + a_2b_2 \quad c_3 = \\
 c_4 &= b_3c_3 + a_3c_3 + a_3b_3 \quad c_4 =
 \end{aligned}$$

Not feasible! Why?

2

## Carry look ahead adder


- An approach in-between our two extremes
- Motivation:
  - If we didn't know the value of carry-in, what could we do?
  - When would we always generate a carry?  $g_i = a_i b_i$
  - When would we propagate the carry?  $p_i = a_i + b_i$
- Did we get rid of the ripple?

$$\begin{aligned}
 c_1 &= g_0 + p_0c_0 & c_2 &= g_1 + p_1g_0 + p_1p_0c_0 \\
 c_3 &= g_2 + p_2c_2 & c_3 &= g_2 + p_2g_1 + p_2p_1g_0 + p_2p_1p_0c_0 \\
 c_4 &= g_3 + p_3c_3 & c_4 &= g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0 + p_3p_2p_1p_0c_0
 \end{aligned}$$

Feasible! Why?

3


## A 4 bit carry look ahead adder

 

- Generate g and p term for each bit
- Use g's, p's and carry in to generate all C's
- Also use them to generate block G and P
- CLA principle can be used recursively

4

## Use principle to build bigger adders

 

- A 16 bit adder uses four 4-bit adders
- It takes block g and p terms and cin to generate block carry bits out
- Block carries are used to generate bit carries
  - could use ripple carry of 4-bit CLA adders
  - Better: use the CLA principle again!

5

## Delays in carry look ahead adders

- 4-Bit case
  - Generation of g and p: 1 gate delay
  - Generation of carries (and G and P): 2 more gate delay
  - Generation of sum: 1 more gate delay
- 16-Bit case
  - Generation of g and p: 1 gate delay
  - Generation of block G and P: 2 more gate delay
  - Generation of block carries: 2 more gate delay
  - Generation of bit carries: 2 more gate delay
  - Generation of sum: 1 more gate delay
- 64-Bit case
  - 12 gate delays

6

## Multiplication

- More complicated than addition
  - accomplished via shifting and addition
- More time and more area
- Let's look at 3 versions based on grade school algorithm

```

01010010 (multiplicand)
x01101101 (multiplier)
    
```

- Negative numbers: convert and multiply
- Use other better techniques like Booth's encoding

7


## Multiplication

```

01010010 (multiplicand)      01010010 (multiplicand)
x01101101 (multiplier)      x01101101 (multiplier)
-----                      -----
00000000 x1                  00000000
01010010 x1                  01010010 x1
00000000 x0                  01010010 x0
00000000 x0                  00000000 x0
001010010 x1                 001010010 x1
0101001000 x1                0101001000 x1
0110011010                   0110011010
01010010000 x1              01010010000 x1
10000101010                  10000101010
000000000000 x0             000000000000 x0
010000101010                010000101010
0101001000000 x1            0101001000000 x1
0111001101010               0111001101010
01010010000000 x1           01010010000000 x1
1000101101010               1000101101010
00000000000000 x0           00000000000000 x0
0010001011101010           0010001011101010
    
```


8

## Multiplication: Implementation

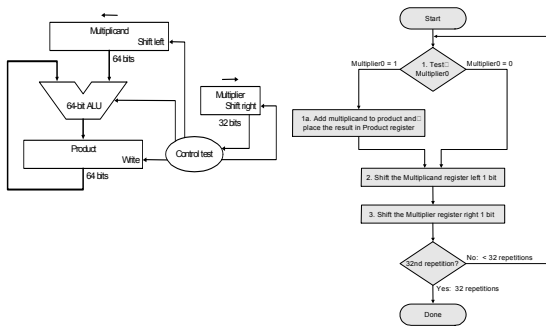


9

## Second Version

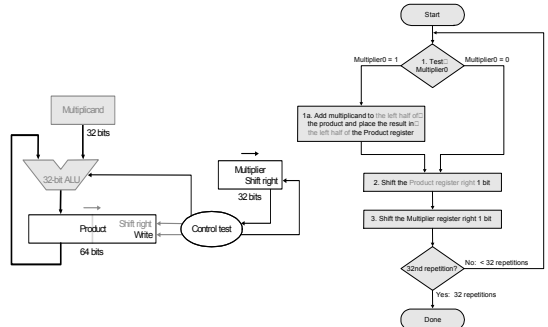

10

## Final Version

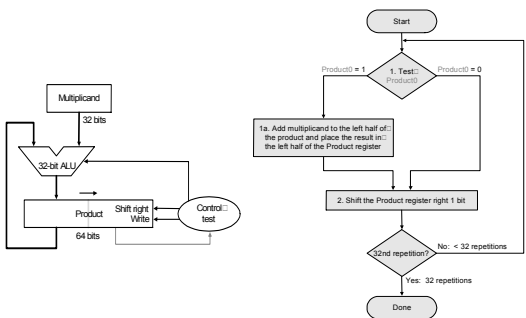

11

## Multiplication Example

Iteration	multi- plicand	Original algorithm	
		Step	Product
0	0010	Initial values	0000 0110
1	0010	1:0 ⇒ no operation	0000 0110
	0010	2: Shift right Product	0000 0011
2	0010	1a:1 ⇒ prod = Prod + Mcand	0010 0011
	0010	2: Shift right Product	0001 0001
3	0010	1a:1 ⇒ prod = Prod + Mcand	0011 0001
	0010	2: Shift right Product	0001 1000
4	0010	1:0 ⇒ no operation	0001 1000
	0010	2: Shift right Product	0000 1100

12

## Signed Multiplication

- Let Multiplier be  $Q[n-1:0]$ , multiplicand be  $M[n-1:0]$
- Let  $F = 0$  (shift flag)
- Let result  $A[n-1:0] = 0\dots00$
- For  $n-1$  steps do
  - $A[n-1:0] = A[n-1:0] + M[n-1:0] \times Q[0]$  /\* add partial product \*/
  - $F \leftarrow F \text{ or } (M[n-1] \text{ and } Q[0])$  /\* determine shift bit \*/
  - Shift A and Q with F, i.e.,
  - $A[n-2:0] = A[n-1:1]$ ;  $A[n-1]=F$ ;  $Q[n-1]=A[0]$ ;  $Q[n-2:0]=Q[n-1:1]$
- Do the correction step
  - $A[n-1:0] = A[n-1:0] - M[n-1:0] \times Q[0]$  /\* subtract partial product \*/
  - Shift A and Q while retaining  $A[n-1]$
  - This works in all cases excepts when both operands are 10...00

13

## Booth's Encoding

- Numbers can be represented using three symbols, 1, 0, and -1
- Let us consider -1 in 8 bits
  - One representation is 1 1 1 1 1 1 1 1
  - Another possible one 0 0 0 0 0 0 -1
- Another example +14
  - One representation is 0 0 0 0 1 1 1 0
  - Another possible one 0 0 0 1 0 0 -1 0
- We do not explicitly store the sequence
- Look for transition from previous bit to next bit
  - 0 to 0 is 0; 0 to 1 is -1; 1 to 1 is 0; and 1 to 0 is 1
- Multiplication by 1, 0, and -1 can be easily done
- Add all partial results to get the final answer

14

## Using Booth's Encoding for Multiplication

- Convert a binary string in Booth's encoded string
  - Multiply by two bits at a time
  - For  $n$  bit by  $n$ -bit multiplication,  $n/2$  partial product
  - Partial products are signed and obtained by multiplying the multiplicand by 0, +1, -1, +2, and -2 (all achieved by shift)
  - Add partial products to obtain the final result
  - Example, multiply 0111 (+7) by 1010 (-6)
  - Booths encoding of 1010 is -1 +1 -1 0
  - With 2-bit groupings, multiplication needs to be carried by -1 and -2
- ```

1 1 1 1 0 0 1 0 (multiplication by -2)
1 1 1 0 0 1 0 0 (multiplication by -1 and shift by 2 positions)
    
```
- Add the two partial products to get 11010110 (-42) as result

15

## Booth's algorithm (Neg. multiplier)

| Iteration | multi-<br>plicand | Booth's algorithm                        |             |
|-----------|-------------------|------------------------------------------|-------------|
|           |                   | Step                                     | Product     |
| 0         | 0010              | Initial values                           | 0000 1101 0 |
| 1         | 0010              | 1c: 10 $\Rightarrow$ prod = Prod - Mcand | 1110 1101 0 |
|           | 0010              | 2: Shift right Product                   | 1111 0110 1 |
| 2         | 0010              | 1b: 01 $\Rightarrow$ prod = Prod + Mcand | 0001 0110 1 |
|           | 0010              | 2: Shift right Product                   | 0000 1011 0 |
| 3         | 0010              | 1c: 10 $\Rightarrow$ prod = Prod - Mcand | 1110 1011 0 |
|           | 0010              | 2: Shift right Product                   | 1111 0101 1 |
| 4         | 0010              | 1d: 11 $\Rightarrow$ no operation        | 1111 0101 1 |
|           | 0010              | 2: Shift right Product                   | 1111 1010 1 |

16

## Carry Save Addition

- Consider adding six set of numbers (4 bits each in the example)
- The numbers are 1001, 0110, 1111, 0111, 1010, 0110 (all positive)
- One way is to add them pair wise, getting three results, and then adding them again

```

1001  1111  1010  → 01111  → 100101
0110  0111  0110  → 10110  → 10000
01111  10110  10000  100101  110101
    
```

- Other method is add them three at a time by saving carry

```

1001  0111  00000  010101  001101
0110  1010  11110  010100  101000
1111  0110  01011  001100  110101
00000  01011  010101  001101  ——— SUM
11110  01100  010100  101000  ——— CARRY
    
```

17

## Carry Save Addition for Multiplication

- $n$ -bit carry-save adder take 1FA time for any  $n$
- For  $n \times n$  bit multiplication,  $n$  or  $n/2$  (for 2 bit at time Booth's encoding) partial products can be generated
- For  $n$  partial products  $n/3$   $n$ -bit carry save adders can be used
- This yields  $2n/3$  partial results
- Repeat this operation until only two partial results are remaining
- Add them using an appropriate size adder to obtain  $2n$  bit result
- For  $n=32$ , you need 30 carry save adders in eight stages taking  $8T$  time where  $T$  is time for one-bit full adder
- Then you need one carry-propagate or carry-look-ahead adder

18

## Division


- Even more complicated
  - can be accomplished via shifting and addition/subtraction
- More time and more area
- We will look at 3 versions based on grade school algorithm

0011 | 0010 0010 (Dividend)

- Negative numbers: Even more difficult
- There are better techniques, we won't look at them


19

## Division, First Version

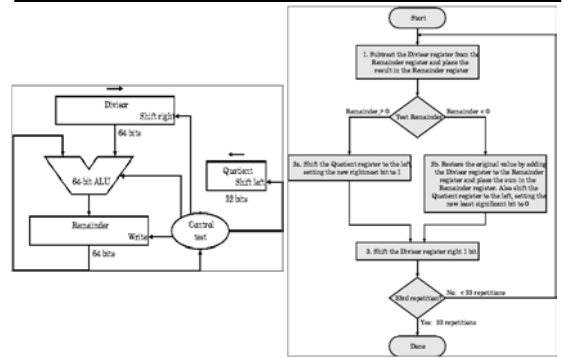


20

## Division, Second Version

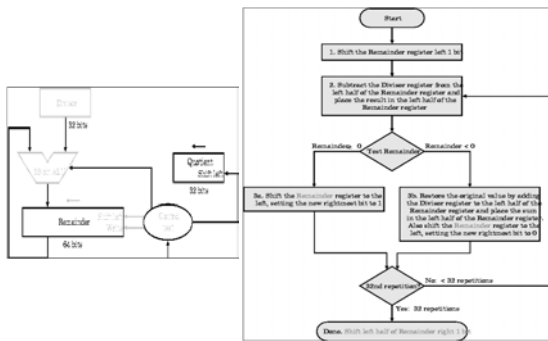

21

## Division, Final Version

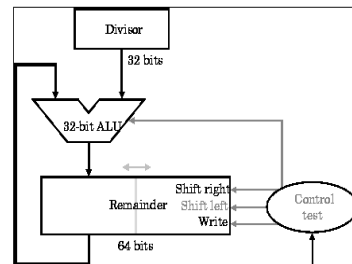

22

## Restoring Division

| Iteration | Divisor | Divide algorithm                    |           |
|-----------|---------|-------------------------------------|-----------|
|           |         | Step                                | Remainder |
| 0         | 0010    | Initial values                      | 0000 0111 |
|           | 0010    | Shift Rem left 1                    | 0000 1110 |
| 1         | 0010    | 2: Rem = Rem - Div                  | 1110 1110 |
|           | 0010    | 3b: Rem < 0 => + Div, sll R, R0 = 0 | 0001 1100 |
| 2         | 0010    | 2: Rem = Rem - Div                  | 1111 1100 |
|           | 0010    | 3b: Rem < 0 => + Div, sll R, R0 = 0 | 0011 1000 |
| 3         | 0010    | 2: Rem = Rem - Div                  | 0001 1000 |
|           | 0010    | 3a: Rem >= 0 => sll R, R0 = 1       | 0011 0001 |
| 4         | 0010    | 2: Rem = Rem - Div                  | 0001 0001 |
|           | 0010    | 3a: Rem >= 0 => sll R, R0 = 1       | 0010 0011 |
| Done      | 0010    | shift left half of Rem right 1      | 0001 0011 |

23

## Non Restoring Division

| Iteration | Divisor | Divide algorithm               |           |
|-----------|---------|--------------------------------|-----------|
|           |         | Step                           | Remainder |
| 0         | 0010    | Initial values                 | 0000 1110 |
| 1         | 0010    | 1: Rem = Rem - Div             | 1110 1110 |
|           | 0010    | 2b: Rem < 0 => sll R, R0 = 0   | 1101 1100 |
|           | 0010    | 3b: Rem = Rem + Div            | 1111 1100 |
| 2         | 0010    | 2b: Rem < 0 => sll R, R0 = 0   | 1111 1000 |
|           | 0010    | 3b: Rem = Rem + Div            | 0001 1000 |
| 3         | 0010    | 2a: Rem > 0 => sll R, R0 = 1   | 0011 0001 |
|           | 0010    | 3a: Rem = Rem - Div            | 0001 0001 |
| 4         | 0010    | 2a: Rem > 0 => sll R, R0 = 1   | 0010 0011 |
| Done      | 0010    | shift left half of Rem right 1 | 0001 0011 |

24

## Floating Point (a brief look)

---

- We need a way to represent
  - numbers with fractions, e.g., 3.1416
  - very small numbers, e.g., .00000001
  - very large numbers, e.g.,  $3.15576 \times 10^9$
- Representation:
  - sign, exponent, significand:  $(-1)^{\text{sign}} \times \text{significand} \times 2^{\text{exponent}}$
  - more bits for significand gives more accuracy
  - more bits for exponent increases range
- IEEE 754 floating point standard:
  - single precision: 8 bit exponent, 23 bit significand
  - double precision: 11 bit exponent, 52 bit significand

25

## IEEE 754 floating point standard

---

- Leading "1" bit of significand is implicit
- Exponent is "biased" to make sorting easier
  - all 0s is smallest exponent all 1s is largest
  - bias of 127 for single precision and 1023 for double precision
  - summary:  $(-1)^{\text{sign}} \times (1+\text{significand}) \times 2^{\text{exponent} - \text{bias}}$
- Example:
  - decimal:  $-.75 = -3/4 = -3/2^2$
  - binary:  $-.11 = -1.1 \times 2^{-1}$
  - floating point: exponent = 126 = 01111110
  - IEEE single precision: 10111111010000000000000000000000

26

## Floating Point Complexities

---

- Operations are somewhat more complicated (see text)
- In addition to overflow we can have "underflow"
- Accuracy can be a big problem
  - IEEE 754 keeps two extra bits, guard and round
  - four rounding modes
  - positive divided by zero yields "infinity"
  - zero divide by zero yields "not a number"
  - other complexities
- Implementing the standard can be tricky
- Not using the standard can be even worse
  - see text for description of 80x86 and Pentium bug!

27

## Floating Point Add/Sub

---

- To add/sub two numbers
  - We first compare the two exponents
  - Select the higher of the two as the exponent of result
  - Select the significand part of lower exponent number and shift it right by the amount equal to the difference of two exponent
  - Remember to keep two shifted out bit and a guard bit
  - add/sub the significand as required according to operation and signs of operands
  - Normalize significand of result adjusting exponent
  - Round the result (add one to the least significant bit to be retained if the first bit being thrown away is a 1
  - Re-normalize the result

28

## Floating Point Multiply

---

- To multiply two numbers
  - Add the two exponent (remember access 127 notation)
  - Produce the result sign as xor of two signs
  - Multiple significand portions
  - Results will be 1x.xxxxx... or 01.xxxx....
  - In the first case shift result right and adjust exponent
  - Round off the result
  - This may require another normalization step

29

## Floating Point Divide

---

- To divide two numbers
  - Subtract divisor's exponent from the dividend's exponent (remember access 127 notation)
  - Produce the result sign as xor of two signs
  - Divide dividend's significand by divisor's significand portions
  - Results will be 1.xxxxx... or 0.1xxxx....
  - In the second case shift result left and adjust exponent
  - Round off the result
  - This may require another normalization step

30