

Datapath & Control Design

- We will design a simplified MIPS processor
- The instructions supported are
 - memory-reference instructions: `lw`, `sw`
 - arithmetic-logical instructions: `add`, `sub`, `and`, `or`, `sllt`
 - control flow instructions: `beq`, `j`
- Generic Implementation:
 - use the program counter (PC) to supply instruction address
 - get the instruction from memory
 - read registers
 - use the instruction to decide exactly what to do
- All instructions use the ALU after reading the registers
 - Why? memory-reference? arithmetic? control flow?

1


What blocks we need

- We need an ALU
 - We have already designed that
- We need memory to store inst and data
 - Instruction memory takes address and supplies inst
 - Data memory takes address and supply data for `lw`
 - Data memory takes address and data and write into memory
- We need to manage a PC and its update mechanism
- We need a register file to include 32 registers
 - We read two operands and write a result back in register file
- Some times part of the operand comes from instruction
- We may add support of immediate class of instructions
- We may add support for `J`, `JR`, `JAL`

2

Simple Implementation

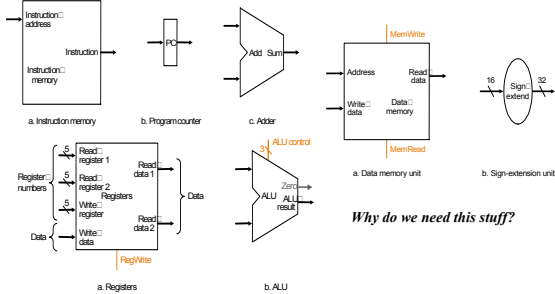
- Include the functional units we need for each instruction



3

More Implementation Details

- Abstract / Simplified View:

 


- Two types of functional units:
 - elements that operate on data values (combinational)
 - Example: ALU
 - elements that contain state (sequential)
 - Examples: Program and Data memory, Register File

4

Managing State Elements

 
- Unclocked vs. Clocked
- Clocks used in synchronous logic
 - when should an element that contains state be updated?



5

Building the Datapath

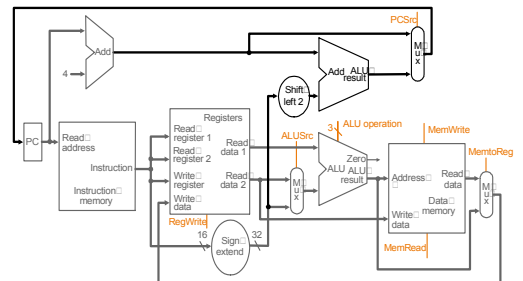- Use multiplexors to stitch them together



6

Latches and Flip flops


- Output is equal to the stored value inside the element (don't need to ask for permission to look at the value)
 - "logically true" could mean electrically low
- Change of state (value) is based on the clock
- Latches: whenever the inputs change, and the clock is asserted
- Flip-flop: state changes only on a clock edge (edge-triggered methodology)

A clocking methodology defines when signals can be read and written
 — wouldn't want to read a signal at the same time it was being written

7

An unlocked state element


 
- The set-reset latch
 - output depends on present inputs
 - If present inputs are 00, then it depends on the past inputs
 - What happens if R=1, S=1?



8

D latch

 
 
- Two inputs:
 - the data value to be stored (D)
 - the clock signal (C) indicating when to read & store D
- Two outputs:
 - the value of the internal state (Q) and its complement



9

D flip flop


- Output changes only on the clock edge

  

10

Our Implementation

 
- An edge triggered methodology
- Typical execution:
 - read contents of some state elements,
 - send values through some combinational logic
 - write results to one or more state elements



11

Register File

- Built using D flip-flops

 

12