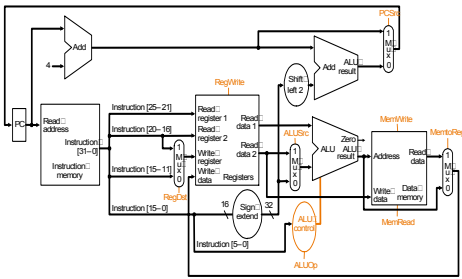


## A Complete Datapath for R Type Instructions

- Lw, Sw, Add, Sub, And, Or, Slt can be performed
- For j (jump) we need an additional multiplexor



1

## What Else is Needed in Data Path

- Support for j and jr
  - For both of them PC value need to come from somewhere else
  - For J, PC is created by 4 bits (31:28) from old PC, 26 bits from IR (27:2) and 2 bits are zero (1:0)
  - For JR, PC value comes from a register
- Support for JAL
  - Address is same as for J inst
  - OLD PC needs to be saved in register 31
- And what about immediate operand instructions
  - Second operand from instruction, but without shifting
- Support for other instructions like lw and immediate inst write

2

## Control


- For each instruction
  - Select the registers to be read (always read two)
  - Select the 2nd ALU input
  - Select the operation to be performed by ALU
  - Select if data memory is to be read or written
  - Select what is written and where in the register file
  - Select what goes in PC
- Information comes from the 32 bits of the instruction
- Example:

add \$8, \$17, \$18 Instruction Format:

|        |       |       |       |       |        |
|--------|-------|-------|-------|-------|--------|
| 000000 | 10001 | 10010 | 01000 | 00000 | 100000 |
| op     | rs    | rt    | rd    | shamt | funct  |

3

## Adding Control to DataPath

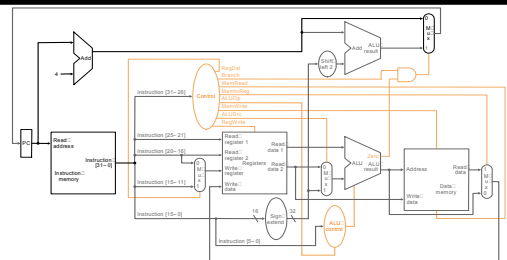


| Instruction | RegDst | ALUSrc | Memto-Reg | Reg Write | Mem Read | Mem Write | Branch | ALUOp1 | ALUOp0 |
|-------------|--------|--------|-----------|-----------|----------|-----------|--------|--------|--------|
| R-format    | 1      | 0      | 0         | 1         | 0        | 0         | 0      | 1      | 0      |
| lw          | 0      | 1      | 1         | 1         | 1        | 0         | 0      | 0      | 0      |
| sw          | X      | 1      | X         | 0         | 0        | 1         | 0      | 0      | 0      |
| beq         | X      | 0      | X         | 0         | 0        | 0         | 1      | 0      | 1      |

4
 
## Our Simple Control Structure

- All of the logic is combinational
- We wait for everything to settle down, and the right thing to be done
  - ALU might not produce "right answer" right away
  - we use write signals along with clock to determine when to write
- Cycle time determined by length of the longest path



We are ignoring some details like setup and hold times

5

## ALU Control

- ALU's operation based on instruction type and function code
  - e.g., what should the ALU do with any instruction
- Example: lw \$1, 100(\$2)

|    |   |   |     |
|----|---|---|-----|
| 35 | 2 | 1 | 100 |
|----|---|---|-----|

|    |    |    |               |
|----|----|----|---------------|
| op | rs | rt | 16 bit offset |
|----|----|----|---------------|

- ALU control input

|     |                  |
|-----|------------------|
| 000 | AND              |
| 001 | OR               |
| 010 | add              |
| 110 | subtract         |
| 111 | set-on-less-than |

- Why is the code for subtract 110 and not 011?

6

## Other Control Information


- Must describe hardware to compute 3-bit ALU control input
  - given instruction type
    - 00 = lw, sw
    - 01 = beq, 10 = arithmetic
    - 11 = Jump
- Control can be described using a truth table:

| ALUOp  | Funct field | Operation         |     |
|--------|-------------|-------------------|-----|
| ALUOp1 | ALUOp0      | F5 F4 F3 F2 F1 F0 |     |
| 0      | 0           | X X X X X X X     | 010 |
| X      | 1           | X X X X X X X     | 110 |
| 1      | X           | X X 0 0 0 0       | 010 |
| 1      | X           | X X 0 0 1 0       | 110 |
| 1      | X           | X X 0 1 0 0       | 000 |
| 1      | X           | X X 0 1 0 1       | 001 |
| 1      | X           | X X 1 0 1 0       | 111 |

7

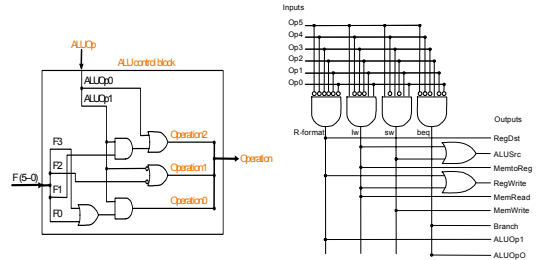
## Implementation of Control

- Simple combinational logic to realize the truth tables




8

## A Complete Datapath with Control

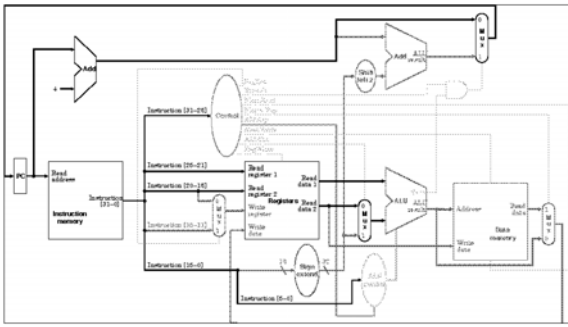

9

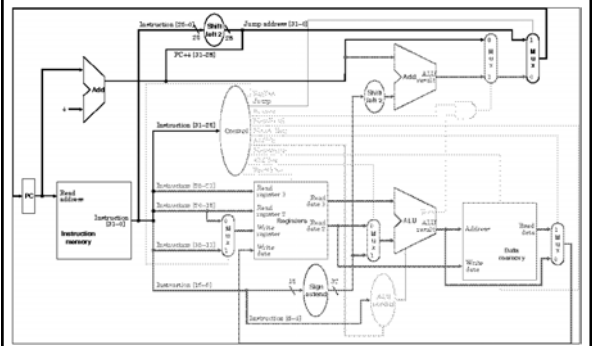
## Datapath with Control and Jump Instruction



10
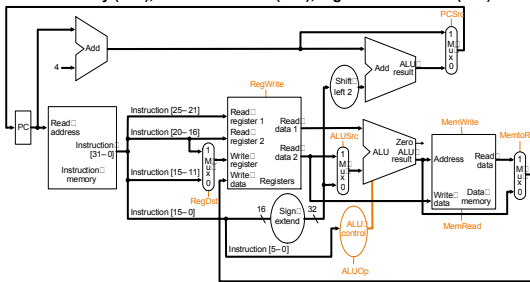
## Timing: Single Cycle Implementation


- Calculate cycle time assuming negligible delays except:
  - memory (2ns), ALU and adders (2ns), register file access (1ns)



11

 
## Where we are headed

- Single Cycle Problems:
  - what if we had a more complicated instruction like floating point?
  - wasteful of area
- One Solution:
  - use a "smaller" cycle time
  - have different instructions take different numbers of cycles
  - a "multicycle" datapath:



12

## Instruction Format

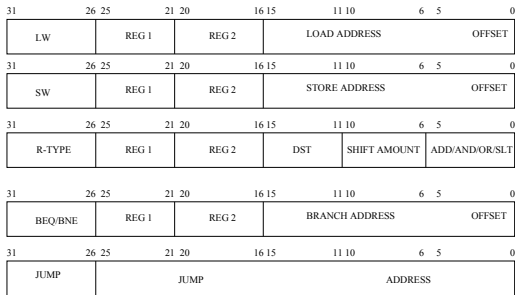

13

## Operation for Each Instruction

| LW:                                | SW:                                | R-Type:                            | BR-Type:                           | JMP-Type:    |
|------------------------------------|------------------------------------|------------------------------------|------------------------------------|--------------|
| 1. READ INST                       | 1. READ INST                       | 1. READ INST                       | 1. READ INST                       | 1. READ INST |
| 2. READ REG 1<br><i>READ REG 2</i> | 2. READ REG 1<br><i>READ REG 2</i> | 2. READ REG 1<br><i>READ REG 2</i> | 2. READ REG 1<br><i>READ REG 2</i> | 2.           |
| 3. ADD REG 1 + OFFSET              | 3. ADD REG 1 + OFFSET              | 3. OPERATE on REG 1 / REG 2        | 3. SUB REG 2 from REG 1            | 3.           |
| 4. READ MEM                        | 4. WRITE MEM                       | 4.                                 | 4.                                 | 4.           |
| 5. WRITE REG2                      | 5.                                 | 5. WRITE DST                       | 5.                                 | 5.           |

14


## Multicycle Approach

- We will be reusing functional units
  - Break up the instruction execution in smaller steps
  - Each functional unit is used for a specific purpose in one cycle
  - Balance the work load
  - ALU used to compute address and to increment PC
  - Memory used for instruction and data
- At the end of cycle, store results to be used again
  - Need additional registers
- Our control signals will not be determined solely by instruction
  - e.g., what should the ALU do for a "subtract" instruction?
- We'll use a finite state machine for control

15
 
## Review: finite state machines


- Finite state machines:
  - a set of states and
  - next state function (determined by current state and the input)
  - output function (determined by current state and possibly input)



- We'll use a Moore machine (output based only on current state)

16

## Multi-Cycle DataPath Operation

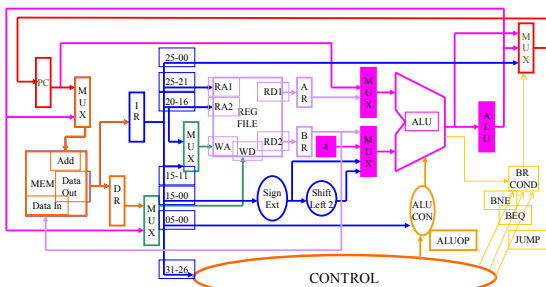

17

## Five Execution Steps

- Instruction Fetch
- Instruction Decode and Register Fetch
- Execution, Memory Address Computation, or Branch Completion
- Memory Access or R-type instruction completion
- Write-back step

*INSTRUCTIONS TAKE FROM 3 - 5 CYCLES!*

18

## Step 1: Instruction Fetch

- Use PC to get instruction and put it in the Instruction Register.
- Increment the PC by 4 and put the result back in the PC.
- Can be described succinctly using RTL "Register-Transfer Language"

```
IR = Memory[PC];
PC = PC + 4;
```

Can we figure out the values of the control signals?

What is the advantage of updating the PC now?

19

## Step 2: Instruction Decode and Register Fetch

- Read registers rs and rt in case we need them
- Compute the branch address in case the instruction is a branch
- RTL:

```
A = Reg[IR[25-21]];
B = Reg[IR[20-16]];
ALUOut = PC + (sign-extend(IR[15-0]) << 2);
```

- We aren't setting any control lines based on the instruction type (we are busy "decoding" it in our control logic)

20

## Step 3 (instruction dependent)

- ALU is performing one of three functions, based on instruction type
- Memory Reference:

```
ALUOut = A + sign-extend(IR[15-0]);
```

- R-type:

```
ALUOut = A op B;
```

- Branch:

```
if (A==B) PC = ALUOut;
```

21

## Step 4 (R type or memory access)

- Loads and stores access memory

```
MDR = Memory[ALUOut];
or
Memory[ALUOut] = B;
```

- R-type instructions finish

```
Reg[IR[15-11]] = ALUOut;
```

The write actually takes place at the end of the cycle on the edge

22

## Write back step

- Reg[IR[20-16]] = MDR;

What about all the other instructions?

23

## Summary:

| Step name   | Action for R-type instructions   | Action for memory-reference instructions                      | Action for branches          | Action for jumps                  |
|---|--|---|------------------------------|-----------------------------------|
| Instruction fetch                                       | IR = Memory[PC]<br>PC = PC + 4   |   |                              |                                   |
| Instruction decode/register fetch                       | A = Reg[IR[25-21]]<br>B = Reg[IR[20-16]]<br>ALUOut = PC + (sign-extend(IR[15-0]) << 2) |   |                              |                                   |
| Execution, address computation, branch/ jump completion | ALUOut = A op B  | ALUOut = A + sign-extend(IR[15-0])                            | if (A == B) then PC = ALUOut | PC = PC[31-28]    (IR[25-0] << 2) |
| Memory access or R-type completion                      | Reg[IR[15-11]] = ALUOut  | Load: MDR = Memory[ALUOut]<br>or<br>Store: Memory[ALUOut] = B |                              |                                   |
| Memory read completion                                  |  | Load: Reg[IR[20-16]] = MDR                                    |                              |                                   |

24