


## Multicycle Approach

- **Single Cycle Problems:**
  - what if we had a more complicated instruction?
  - wasteful of area
- **One Solution:**
  - use a “smaller” cycle time and use different numbers of cycles for each instruction using a “multicycle” datapath:
- **We will be reusing functional units**
  - Break up the instruction execution in smaller steps
  - Each functional unit is used for a specific purpose in one cycle
  - Balance the work load
    - ALU used to compute address and to increment PC
    - Memory used for instruction and data
- **At the end of cycle, store results to be used again**
  - Need additional registers
- **Our control signals will not be determined solely by instruction**
  - e.g., what should the ALU do for a “subtract” instruction?
- **We'll use a finite state machine for control**

1
 
## Review: finite state machines


- **Finite state machines:**
  - a set of states and
  - next state function (determined by current state and the input)
  - output function (determined by current state and possibly input)



- We'll use a Moore machine (output based only on current state)

2

## Instruction Format

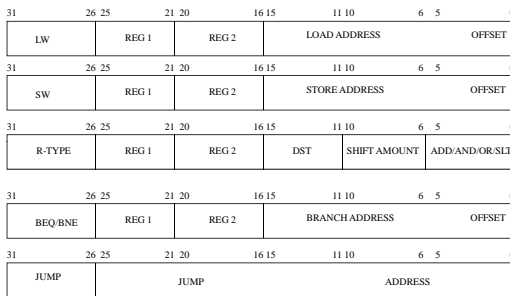


3

## Operation for Each Instruction

LW:	SW:	R-Type:	BR-Type:	JMP-Type:
1. READ INST	1. READ INST	1. READ INST	1. READ INST	1. READ INST
2. READ REG 1 READ REG 2	2. READ REG 1 READ REG 2	2. READ REG 1 READ REG 2	2. READ REG 1 READ REG 2	2.
3. ADD REG 1 + OFFSET	3. ADD REG 1 + OFFSET	3. OPERATE on REG 1 / REG 2	3. SUB REG 2 from REG 1	3.
4. READ MEM	4. WRITE MEM	4.	4.	4.
5. WRITE REG2	5.	5. WRITE DST	5.	5.

4

## Multi-Cycle DataPath Operation

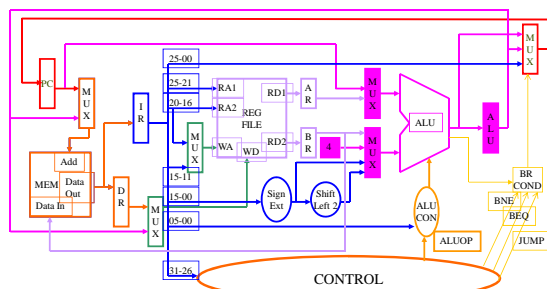

5

## Five Execution Steps

- Instruction Fetch
- Instruction Decode and Register Fetch
- Execution, Memory Address Computation, or Branch Completion
- Memory Access or R-type instruction completion
- Write-back step

*INSTRUCTIONS TAKE FROM 3 - 5 CYCLES!*

6

## Step 1: Instruction Fetch

- Use PC to get instruction and put it in the Instruction Register.
- Increment the PC by 4 and put the result back in the PC.
- Can be described succinctly using RTL "Register-Transfer Language"

```
IR = Memory[PC];
PC = PC + 4;
```

Can we figure out the values of the control signals?

What is the advantage of updating the PC now?

7

## Step 2: Instruction Decode and Register Fetch

- Read registers rs and rt in case we need them
- Compute the branch address in case the instruction is a branch
- RTL:

```
A = Reg[IR[25-21]];
B = Reg[IR[20-16]];
ALUOut = PC + (sign-extend(IR[15-0]) << 2);
```

- We aren't setting any control lines based on the instruction type (we are busy "decoding" it in our control logic)

8

## Step 3 (instruction dependent)

- ALU is performing one of three functions, based on instruction type

- Memory Reference:

```
ALUOut = A + sign-extend(IR[15-0]);
```

- R-type:

```
ALUOut = A op B;
```

- Branch:

```
if (A==B) PC = ALUOut;
```

9

## Step 4 (R-type or memory-access)

- Loads and stores access memory

```
MDR = Memory[ALUOut];
or
Memory[ALUOut] = B;
```

- R-type instructions finish

```
Reg[IR[15-11]] = ALUOut;
```

*The write actually takes place at the end of the cycle on the edge*

10

## Write-back step

- Reg[IR[20-16]] = MDR;

What about all the other instructions?


11

## Summary:

Step name	Action for R-type instructions	Action for memory-reference instructions	Action for branches	Action for jumps
Instruction fetch	IR = Memory[PC] PC = PC + 4			
Instruction decode/register fetch	A = Reg[IR[25-21]] B = Reg[IR[20-16]] ALUOut = PC + (sign-extend(IR[15-0]) << 2)			
Execution, address computation, branch/ jump completion	ALUOut = A op B	ALUOut = A + sign-extend(IR[15-0])	if (A==B) then PC = ALUOut	PC = PC[31-28]    (IR[25-0] << 2)
Memory access or R-type completion	Reg[IR[15-11]] = ALUOut	Load: MDR = Memory[ALUOut] or Store: Memory[ALUOut] = B		
Memory read completion		Load: Reg[IR[20-16]] = MDR		


12

### Multi-Cycle DataPath Operation

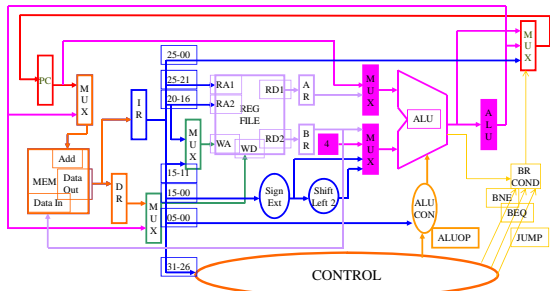


13
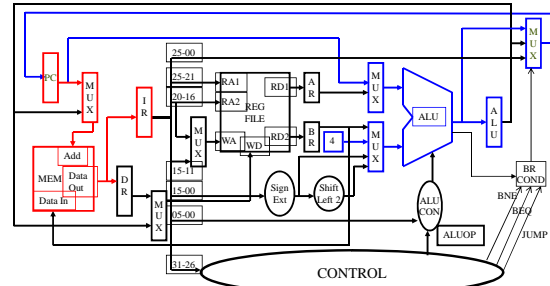
### LW Operation on Multi-Cycle Data Path: C1




14
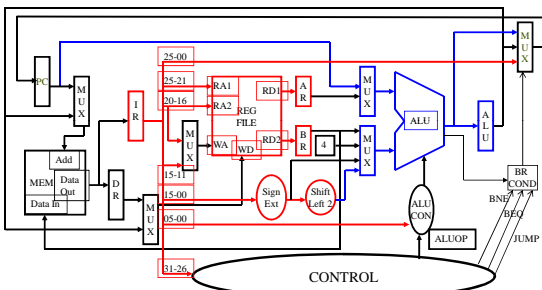
### LW Operation on Multi-Cycle Data Path: C2




15
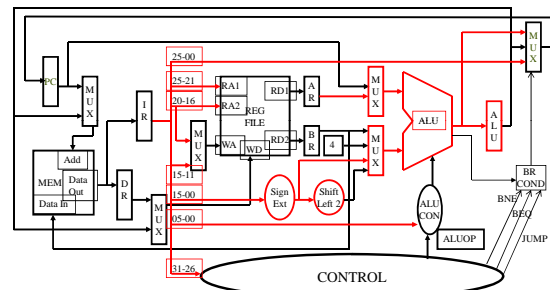
### LW Operation on Multi-Cycle Data Path: C3




16
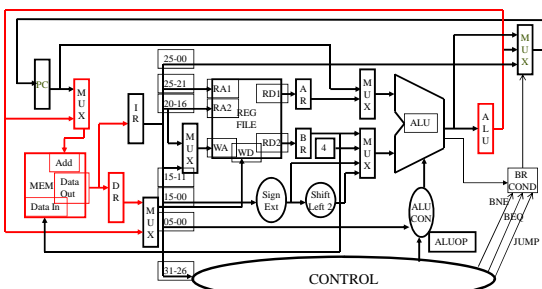
### LW Operation on Multi-Cycle Data Path: C4




17
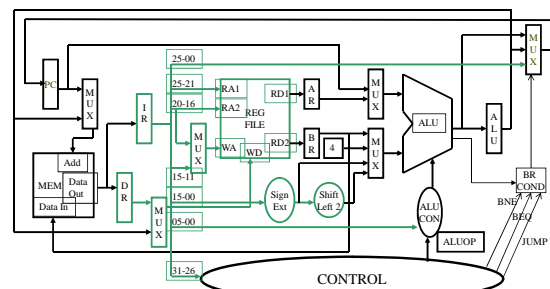
### LW Operation on Multi-Cycle Data Path: C5




18
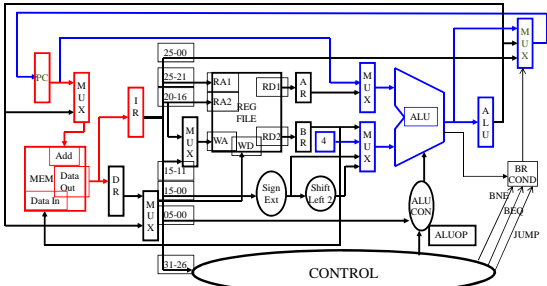
### SW Operation on Multi-Cycle Data Path: C1




19
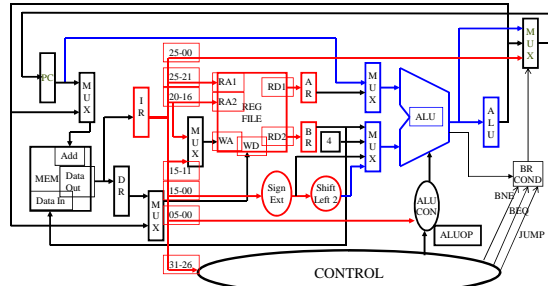
### SW Operation on Multi-Cycle Data Path: C2




20
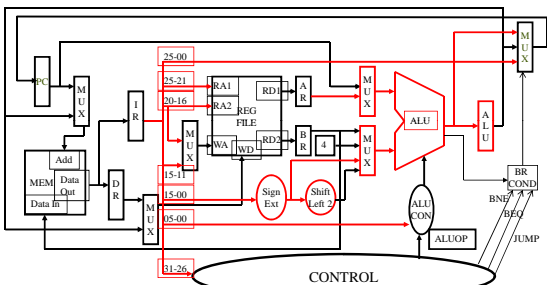
### SW Operation on Multi-Cycle Data Path: C3




21
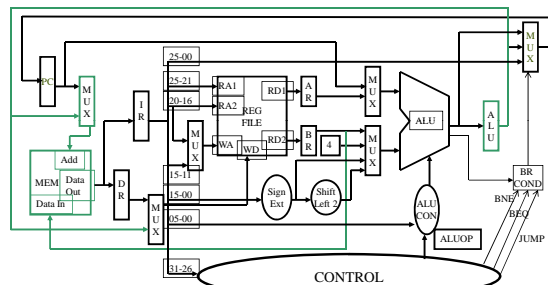
### SW Operation on Multi-Cycle Data Path: C4




22
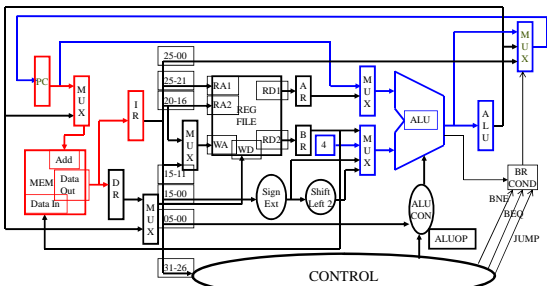
### R-TYPE Operation on Multi-Cycle Data Path: C1




23
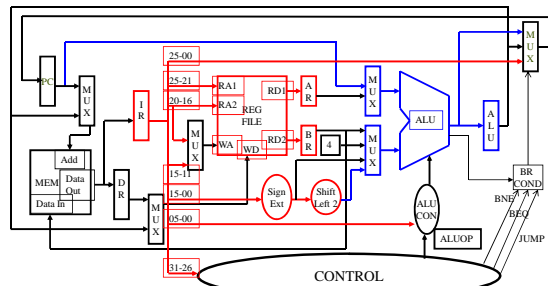
### R-TYPE Operation on Multi-Cycle Data Path: C2




24
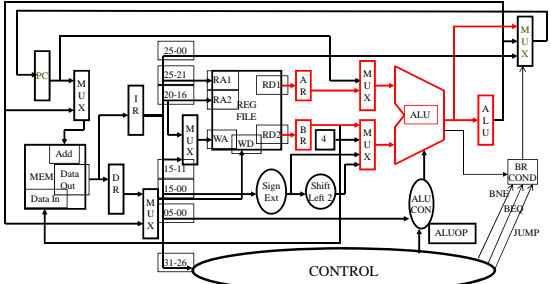
### R-TYPE Operation on Multi-Cycle Data Path: C3




25
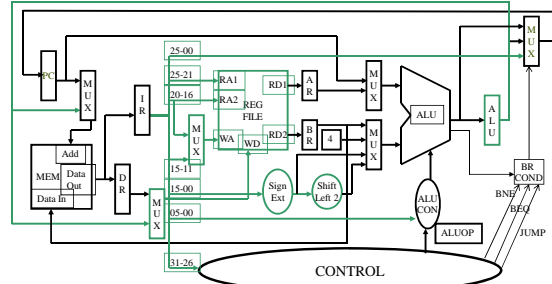
### R-TYPE Operation on Multi-Cycle Data Path: C4




26
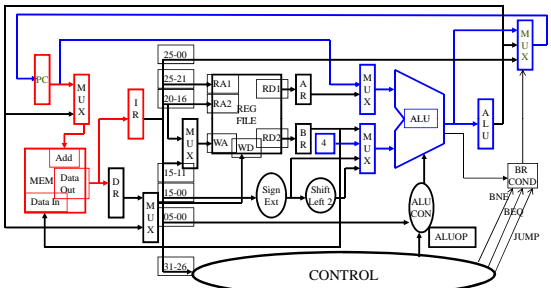
### BR Operation on Multi-Cycle Data Path: C1




27
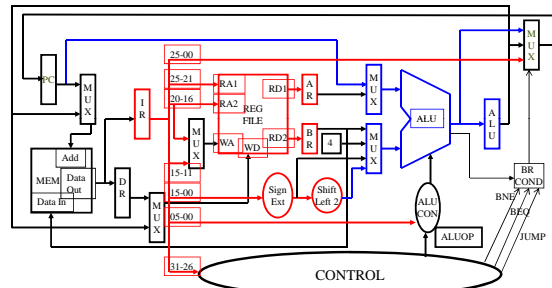
### BR Operation on Multi-Cycle Data Path: C2




28
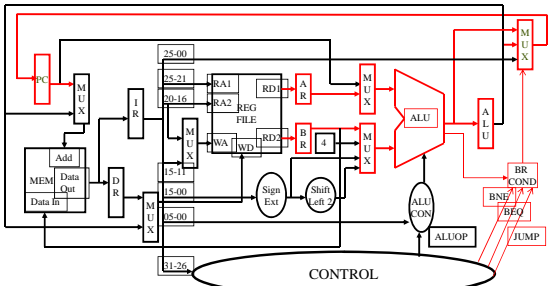
### BR Operation on Multi-Cycle Data Path: C3




29
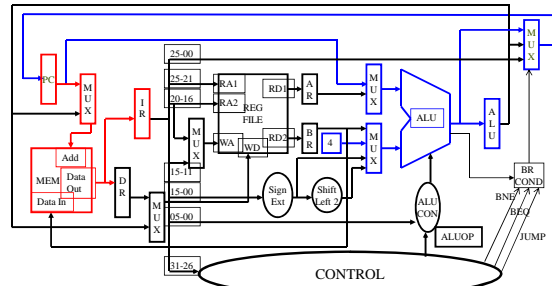
### JUMP Operation on Multi-Cycle Data Path: C1



30
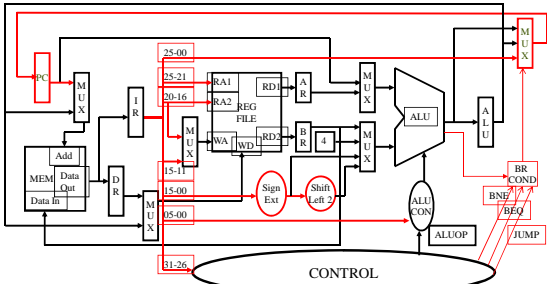
## JUMP Operation on Multi-Cycle Data Path: C2



31

## Simple Questions

- How many cycles will it take to execute this code?

```
lw $t2, 0($t3)
lw $t3, 4($t3)
beq $t2, $t3, Label #assume not
add $t5, $t2, $t3
sw $t5, 8($t3)
```

Label: ...

- What is going on during the 8th cycle of execution?
- In what cycle does the actual addition of \$t2 and \$t3 take place?



32

## Implementing the Control

- Value of control signals is dependent upon:
  - what instruction is being executed
  - which step is being performed
- Use the information we've accumulated to specify a finite state machine
  - specify the finite state machine graphically, or
  - use micro-programming
- Implementation can be derived from specification

33

## Deciding the Control

- In each clock cycle, decide all the action that needs to be taken
- The control signal can be 0 and 1 or x (don't care)
- Make a signal an x if you can to reduce control
- An action that may destroy any useful value be not allowed
- Control Signal required
  - ALU: SRC1 (1 bit), SRC2(2 bits), operation (Add, Sub, or from FC)
  - Memory: address (I or D), read, write, data in IR or MDR
  - Register File: address r/rd, data (MDR/ALUOUT), read, write
  - PC: PCwrite, PCwrite-conditional, Data (PC+4, branch, jump)
- Control signal can be implied (register file read are values in A and B registers (actually A and B need not be registers at all))
- Explicit control vs indirect control (derived based on input like instruction being executed, or function code field) bits


34

## Graphical Specification of FSM

- How many state bits will we need?


- 4 bits.

- Why?

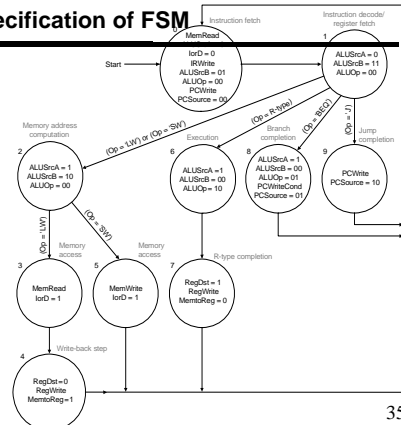

35
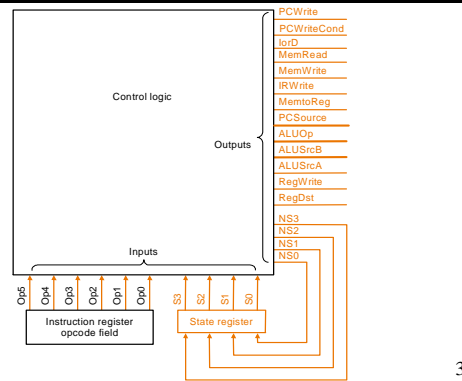
## Finite State Machine: Control Implementation



36

### PLA Implementation

- If I picked a horizontal or vertical line could you explain it?

37

### ROM Implementation

- ROM = "Read Only Memory"
  - values of memory locations are fixed ahead of time
- A ROM can be used to implement a truth table
  - if the address is m-bits, we can address  $2^m$  entries in the ROM.
  - our outputs are the bits of data that the address points to.

0	0	0	0	0	1	1	1
0	0	1	1	1	0	0	0
0	1	0	1	1	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	0	0	0	0	1
1	1	0	0	1	1	0	0
1	1	1	0	1	1	1	1

m is the "height", and n is the "width"

38

### ROM Implementation

- How many inputs are there?
  - 6 bits for opcode, 4 bits for state = 10-bit (i.e.,  $2^{10} = 1024$  different addresses)
- How many outputs are there?
  - 16 datapath-control outputs, 4 state bits = 20 bits
- ROM is  $2^{10} \times 20 = 20K$  bits (an unusual size)
- Rather wasteful, since for lots of the entries, the outputs are the same
  - i.e., opcode is often ignored

39

### ROM vs PLA

- Break up the table into two parts
  - 4 state bits tell you the 16 outputs,  $2^4 \times 16$  bits of ROM
  - 10 bits tell you the 4 next state bits,  $2^{10} \times 4$  bits of ROM
  - Total: 4.3K bits of ROM
- PLA is much smaller
  - can share product terms
  - only need entries that produce an active output
  - can take into account don't cares
- Size is  $(\#inputs \times \#product\text{-terms}) + (\#outputs \times \#product\text{-terms})$ 
  - For this example =  $(10 \times 17) + (20 \times 17) = 460$  PLA cells
- PLA cells usually about the size of a ROM cell (slightly bigger)

40

### Another Implementation Style

- Complex instruction: the "next state" is often current state + 1

41


### Details-1

Dispatch ROM1			Dispatch ROM2		
Op	Opcode name	Value	Op	Opcode name	Value
00000	Rformat	0110	10011	lw	0011
00010	jmp	1001			
00010	beq	1000			
10011	lw	0010			
10101	sw	0010			

State number	Address-control action	Value of AddrCtl
0	Use incremented state	3
1	Use dispatch ROM 1	1
2	Use dispatch ROM 2	2
3	Use incremented state	3
4	Replace state number by 0	0
5	Replace state number by 0	0
6	Use incremented state	3
7	Replace state number by 0	0
8	Replace state number by 0	0
9	Replace state number by 0	0


42

## Details-2

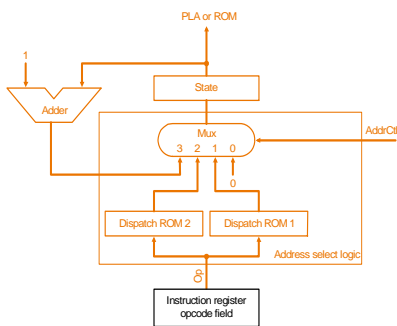

43
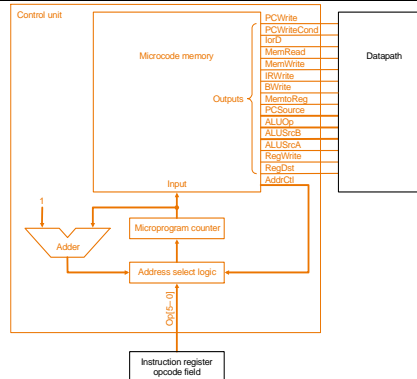
## Microprogramming: What is a "microinstruction"



44

## Microprogramming

- A specification methodology
  - appropriate if hundreds of opcodes, modes, cycles, etc.
  - signals specified symbolically using microinstructions

Label	ALU control	SRC1	SRC2	Register control	Memory	PCWrite control	Sequencing
Fetch	Add	PC	4		Read PC	ALU	Seq
Mem1	Add	PC	Extend	Read			Dispatch 1
LW2		A			Read ALU		Dispatch 2
SW2				Write MDR			Fetch
Rformat1	Func code	A	B		Write ALU		Seq
BEQ1	Subst	A	B	Write ALU			Fetch
JUMP1						ALUOut-cond	Fetch
						Jump address	Fetch

- Will two implementations of the same architecture have the same microcode?
- What would a micro-assembler do?

45

## Microinstruction format

Field name	Value	Signals active	Comment
ALU control	Add	ALUOp = 00	Cause the ALU to add
	Subt	ALUOp = 01	Cause the ALU to subtract; this implements the compare for branches
Func code	PC	ALUSrcA = 0	Use the PC as the first ALU input
	A	ALUSrcA = 1	Register A is the first ALU input
SRC2	B	ALUSrcB = 00	Register B is the second ALU input
	4	ALUSrcB = 01	Use 4 bits the second ALU input
Extend	Extend	ALUSrcB = 10	Use output of the sign-extension unit as the second ALU input
	Exshft	ALUSrcB = 11	Use the output of the shift-by-two unit as the second ALU input
Register control	Read	RegWrite = 0, RegDst = 1, MemtoReg = 0	Read two registers using the rs and rt fields of the IR as the register numbers and output the data into registers A and B
	Write ALU	RegWrite = 1, RegDst = 0, MemtoReg = 1	Write a register using the rd field of the IR as the register number and the contents of the ALUOut as the data
	Write MDR	RegWrite = 1, RegDst = 0, MemtoReg = 1	Write a register using the rd field of the IR as the register number and the contents of the MDR as the data
Memory	Read PC	MemRead, lrd = 0	Read memory using the PC as address; write result into IR (and the MDR)
	Read ALU	MemRead, lrd = 1	Read memory using the ALUOut as address; write result into MDR
PC write control	Write ALU	MemWrite, lrd = 1	Write memory using the ALUOut as address; contents of B as the data
	ALU	PCSource = 00	Write the output of the ALU into the PC
Sequencing	ALUOut-cond	PCSource = 01, PCWriteCond	If the Zero output of the ALU is active, write the PC with the contents of the register ALUOut
	Jump address	PCSource = 10, PCWrite	Write the PC with the jump address from the instruction
Sequencing	Seq	AddrCtl = 11	Choose the next microinstruction sequentially
	Fetch	AddrCtl = 00	Go to the first microinstruction to begin a new instruction
	Dispatch 1	AddrCtl = 01	Dispatch using the ROM 1
	Dispatch 2	AddrCtl = 10	Dispatch using the ROM 2

46

## Maximally vs. Minimally Encoded

- No encoding:
  - 1 bit for each datapath operation
  - faster, requires more memory (logic)
  - used for Vax 780 — an astonishing 400K of memory!
- Lots of encoding:
  - send the microinstructions through logic to get control signals
  - uses less memory, slower
- Historical context of CISC:
  - Too much logic to put on a single chip with everything else
  - Use a ROM (or even RAM) to hold the microcode
  - It's easy to add new instructions

47


## Microcode: Trade-offs

- Distinction between specification and implementation is blurred
- Specification Advantages:
  - Easy to design and write
  - Design architecture and microcode in parallel
- Implementation (off-chip ROM) Advantages
  - Easy to change since values are in memory
  - Can emulate other architectures
  - Can make use of internal registers
- Implementation Disadvantages, SLOWER now that:
  - Control is implemented on same chip as processor
  - ROM is no longer faster than RAM
  - No need to go back and make changes

48



## The Big Picture

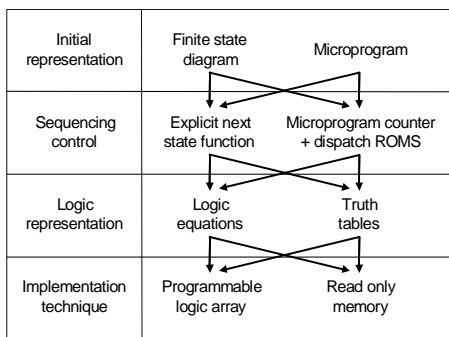

49

## Exceptions

- What should the machine do if there is a problem
- Exceptions are just that
  - Changes in the normal execution of a program
- Two types of exceptions
  - External Condition: I/O interrupt, power failure, user termination signal (Ctrl-C)
  - Internal Condition: Bad memory read address (not a multiple of 4), illegal instructions, overflow/underflow.
- Interrupts – external
- Exceptions – internal
- Usually we refer to both by the general term “Exception”
- In either case, we need some mechanism by which we can handle the exception generated.
- Control is transferred to an exception handling mechanism, stored at a pre-specified location
- Address of instruction is saved in a register called EPC


50

## How Exceptions are Handled

- We need two special registers
  - EPC: 32 bit register to hold address of current instruction
  - Cause: 32 bit register to hold information about the type of exception that has occurred.
- Simple Exception Types
  - Undefined Instruction
  - Arithmetic Overflow
- Another type is Vectored Interrupts
  - Do not need cause register
  - Appropriate exception handler jumped to from a vector table

51
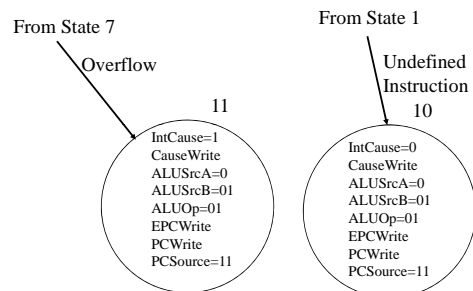
## Two new states for the Multi-cycle CPU



52

## Vectored Interrupts/Exceptions

- Address of exception handler depends on the problem
  - Undefined Instruction C0 00 00 00
  - Arithmetic Overflow C0 00 00 20
  - Addresses are separated by a fixed amount, 32 bytes in MIPS
- PC is transferred to a register called EPC
- If interrupts are not vectored, then we need another register to store the cause of problem
- In what state what exception can occur?

53

## Final Words on Single and Multi-Cycle Systems

- Single cycle implementation
  - Simpler but slowest
  - Require more hardware
- Multi-cycle
  - Faster clock
  - Amount of time it takes depends on instruction mix
  - Control more complicated
- Exceptions and Other conditions add a lot of complexity
- Other techniques to make it faster

54