

Datapath & Control Design

- We will design a simplified MIPS processor
- The instructions supported are
 - memory-reference instructions: `lw`, `sw`
 - arithmetic-logical instructions: `add`, `sub`, `and`, `or`, `sllt`
 - control flow instructions: `beq`, `j`
- Generic Implementation:
 - use the program counter (PC) to supply instruction address
 - get the instruction from memory
 - read registers
 - use the instruction to decide exactly what to do
- All instructions use the ALU after reading the registers
 - Why? memory-reference? arithmetic? control flow?

1


What blocks we need

- We need an ALU
 - We have already designed that
- We need memory to store inst and data
 - Instruction memory takes address and supplies inst
 - Data memory takes address and supply data for `lw`
 - Data memory takes address and data and write into memory
- We need to manage a PC and its update mechanism
- We need a register file to include 32 registers
 - We read two operands and write a result back in register file
- Some times part of the operand comes from instruction
- We may add support of immediate class of instructions
- We may add support for `J`, `JR`, `JAL`

2

Simple Implementation

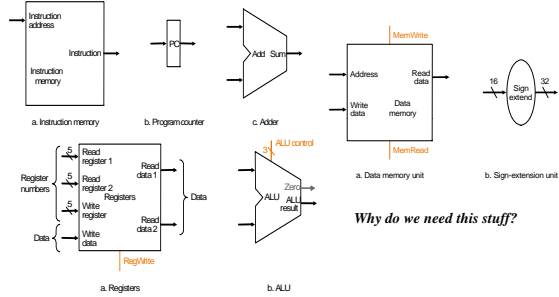
- Include the functional units we need for each instruction



3

More Implementation Details

- Abstract / Simplified View:

 


- Two types of functional units:
 - elements that operate on data values (combinational)
 - Example: ALU
 - elements that contain state (sequential)
 - Examples: Program and Data memory, Register File

4

Managing State Elements

 - Unclocked vs. Clocked
- Clocks used in synchronous logic
 - when should an element that contains state be updated?



5


MIPS Instruction Format

31	26	25	21	20	16	15	11	10	6	5	0	
LW		REG 1			REG 2			LOAD ADDRESS		OFFSET		
31	26	25	21	20	16	15	11	10	6	5	0	
SW		REG 1			REG 2			STORE ADDRESS		OFFSET		
31	26	25	21	20	16	15	11	10	6	5	0	
BEQ/BNE/J		REG 1			REG 2			BRANCH ADDRESS		OFFSET		
31	26	25	21	20	16	15	11	10	6	5	0	
R-TYPE		REG 1			REG 2			DST	SHIFT AMOUNT		ADD/AND/OR/SLT	
31	26	25	21	20	16	15	11	10	6	5	0	
I-TYPE		REG 1			REG 2			IMMEDIATE DATA				
31	26	25	21	20	16	15	11	10	6	5	0	
JUMP		JUMP					ADDRESS					

6

Building the Datapath

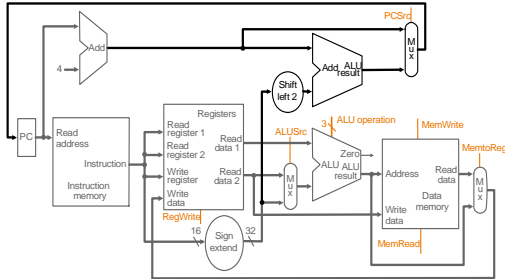
- Use multiplexers to stitch them together



7

A Complete Datapath for R-Type Instructions

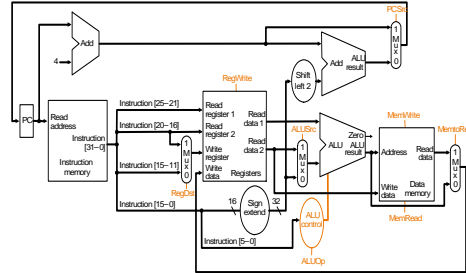- Lw, Sw, Add, Sub, And, Or, Slt can be performed
- For j (jump) we need an additional multiplexer



8

What Else is Needed in Data Path

- Support for j and jr
 - For both of them PC value need to come from somewhere else
 - For J, PC is created by 4 bits (31:28) from old PC, 26 bits from IR (27:2) and 2 bits are zero (1:0)
 - For JR, PC value comes from a register
- Support for JAL
 - Address is same as for J inst
 - OLD PC needs to be saved in register 31
- And what about immediate operand instructions
 - Second operand from instruction, but without shifting
- Support for other instructions like lw and immediate inst write


9

Operation for Each Instruction

LW:	SW:	R/I/S-Type:	BR-Type:	JMP-Type:
1. READ INST	1. READ INST	1. READ INST	1. READ INST	1. READ INST
2. READ REG 1 READ REG 2	2. READ REG 1 READ REG 2	2. READ REG 1 READ REG 2	2. READ REG 1 READ REG 2	2.
3. ADD REG 1 + OFFSET	3. ADD REG 1 + OFFSET	3. OPERATE on REG 1 / REG 2	3. SUB REG 2 from REG 1	3.
4. READ MEM	4. WRITE MEM	4.	4.	4.
5. WRITE REG2	5.	5. WRITE DST	5.	5.

10


Data Path Operation

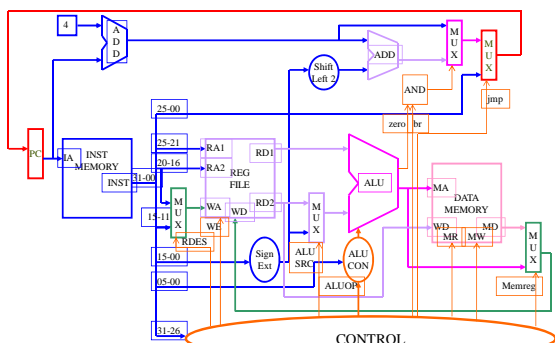

11

Our Simple Control Structure

 - All of the logic is combinational
- We wait for everything to settle down, and the right thing to be done
 - ALU might not produce "right answer" right away
 - we use write signals along with clock to determine when to write
- Cycle time determined by length of the longest path



We are ignoring some details like setup and hold times

12

Control

- For each instruction
 - Select the registers to be read (always read two)
 - Select the 2nd ALU input
 - Select the operation to be performed by ALU
 - Select if data memory is to be read or written
 - Select what is written and where in the register file
 - Select what goes in PC

- Information comes from the 32 bits of the instruction


- Example:

add \$8, \$17, \$18 Instruction Format:

000000	10001	10010	01000	00000	100000
op	rs	rt	rd	shamt	funct

19

Adding Control to DataPath

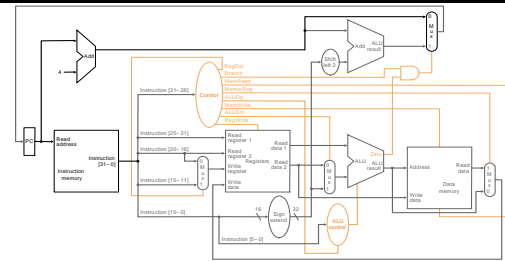

Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUOp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

20

ALU Control

- ALU's operation based on instruction type and function code
 - e.g., what should the ALU do with any instruction

- Example: lw \$1, 100(\$2)

35	2	1	100
op	rs	rt	16 bit offset

- ALU control input

000	AND
001	OR
010	add
110	subtract
111	set-on-less-than

- Why is the code for subtract 110 and not 011?

21

Other Control Information

- Must describe hardware to compute 3-bit ALU control input
 - given instruction type

00 = lw, sw
 01 = beq,
 10 = arithmetic
 11 = Jump

ALUOp computed from instruction type

- function code for arithmetic


- Control can be described using a truth table:

ALUOp		Funct field					Operation	
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	010
X	1	X	X	X	X	X	X	110
1	X	X	X	0	0	0	0	010
1	X	X	X	0	0	1	0	110
1	X	X	X	0	1	0	0	000
1	X	X	X	0	1	0	1	001
1	X	X	X	1	0	1	0	111

22


Implementation of Control

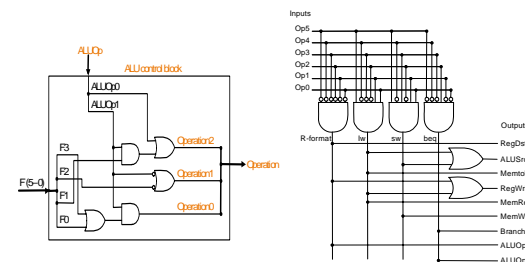- Simple combinational logic to realize the truth tables




23

A Complete Datapath with Control

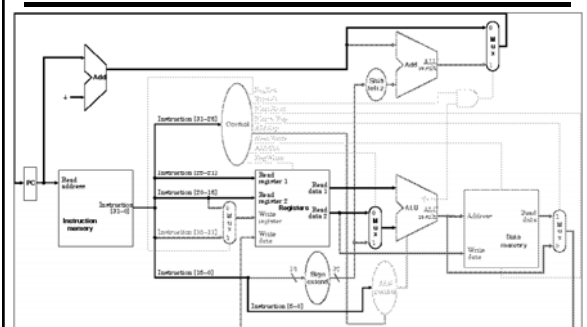

24

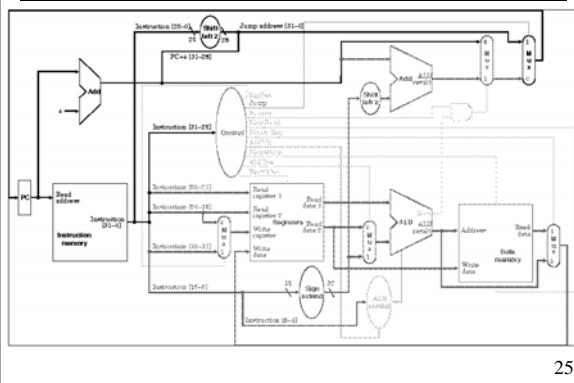
Datapath with Control and Jump Instruction



25

Timing: Single Cycle Implementation

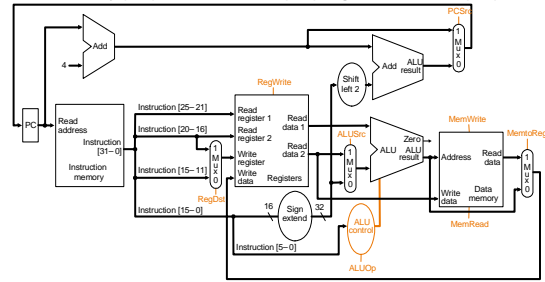
- Calculate cycle time assuming negligible delays except:
 - memory (2ns), ALU and adders (2ns), register file access (1ns)



26

Where we are headed

 - Design a data path for our machine specified in the next 3 slides
- Single Cycle Problems:
 - what if we had a more complicated instruction like floating point?
 - wasteful of area
- One Solution:
 - use a "smaller" cycle time and use different numbers of cycles for each instruction using a "multicycle" datapath:



27

Machine Specification

- 16-bit data path (can be 4, 8, 12, 16, 24, 32)
- 16-bit instruction (can be any number of them)
- 16-bit PC (can be 16, 24, 32 bits)
- 16 registers (can be 1, 4, 8, 16, 32)
- With m register, $\log m$ bits for each register
- Offset depends on expected offset from registers
- Branch offset depends on expected jump address
- Many compromise are made based on number of bits in instruction

28

Instruction

- LW R2, #v(R1); Load memory from address (R1) + v
- SW R2, #v(R1); Store memory to address (R1) + v
- R-Type – OPER R3, R2, R1; Perform $R3 \leftarrow R2 \text{ OP } R1$
 - Five operations ADD, AND, OR, SLT, SUB
- I-Type – OPER R2, R1, V; Perform $R2 \leftarrow R1 \text{ OP } V$
 - Four operation ADDI, ANDI, ORI, SLTI
- B-Type – BC R2, R1, V; Branch if condition met to address PC+V
 - Two operation BNE, BEQ
- Shift class – SHIFT TYPE R2, R1; Shift R1 of type and result to R2
 - One operation
- Jump Class -- JAL and JR (JAL can be used for Jump)
 - What are the implications of J vs JAL
 - Two instructions

29

Instruction bits needed

- LW/SW/BC – Requires opcode, R2, R1, and V values
- R-Type – Requires opcode, R3, R2, and R1 values
- I-Type – Requires opcode, R2, R1, and V values
- Shift class – Requires opcode, R2, R1, and shift type value
- JAL requires opcode and jump address
- JR requires opcode and register address
- Opcode – can be fixed number or variable number of bits
- Register address – 4 bits if 16 registers
- How many bits in V?
- How many bits in shift type?
 - 4 for 16 types, assume one bit shift at a time
- How many bits in jump address?

30