 


Three Representations of Logic Functions

	AND		OR		NOT																																		
1. Logic Expression	$X \cdot Y$	$X + Y$	X'	X	$\sim X$	$!X$																																	
2. Truth Table	<table border="1"> <thead> <tr><th>X</th><th>Y</th><th>$X \cdot Y$</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	X	Y	$X \cdot Y$	0	0	0	0	1	0	1	0	0	1	1	1	<table border="1"> <thead> <tr><th>X</th><th>Y</th><th>$X + Y$</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	X	Y	$X + Y$	0	0	0	0	1	1	1	0	1	1	1	1	<table border="1"> <thead> <tr><th>X</th><th>X'</th></tr> </thead> <tbody> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </tbody> </table>	X	X'	0	1	1	0
X	Y	$X \cdot Y$																																					
0	0	0																																					
0	1	0																																					
1	0	0																																					
1	1	1																																					
X	Y	$X + Y$																																					
0	0	0																																					
0	1	1																																					
1	0	1																																					
1	1	1																																					
X	X'																																						
0	1																																						
1	0																																						

3. Circuit Diagram / Schematic



1

Logic Functions of 2 Variables

XY	F0	F1	F2	F3	F4	F5	F6	F7
00	0	0	0	0	0	0	0	0
01	0	0	0	0	1	1	1	1
10	0	0	1	1	0	0	1	1
11	0	1	0	1	0	1	0	1

XY	F8	F9	F10	F11	F12	F13	F14	F15
00	1	1	1	1	1	1	1	1
01	0	0	0	0	1	1	1	1
10	0	0	1	1	0	0	1	1
11	0	1	0	1	0	1	0	1

- F1 is called a logical AND, denoted by $X \cdot Y$
- F6 is called an XOR (Exclusive-OR), denoted by $X \oplus Y$
- F7 is called OR, denoted by $X + Y$
- F8 is NOR, denoted by $\overline{X + Y}$
- F9 is called an XNOR (Exclusive-NOR), denoted by $\overline{X \oplus Y}$
- F14 is NAND, denoted by $\overline{X \cdot Y}$

2

Truth Tables for 2 Variable Functions

X	Y	AND	X	Y	OR	X	Y	XOR
0	0	0	0	0	0	0	0	0
0	1	0	0	1	1	0	1	1
1	0	0	1	0	1	1	0	1
1	1	1	1	1	1	1	1	0

X	Y	NAND	X	Y	NOR	X	Y	XNOR
0	0	1	0	0	1	0	0	1
0	1	1	0	1	0	0	1	0
1	0	1	1	0	0	1	0	0
1	1	0	1	1	0	1	1	1

3

Which Truth Tables Are the Same?

1)

B	A	F
0	0	0
0	1	0
1	0	1
1	1	0

2)

A	B	F
0	0	0
0	1	0
1	0	1
1	1	0

3)

B	A	F
1	1	0
1	0	1
0	1	0
0	0	0

4

Logic Gate Symbols

- AND denoted by $X \cdot Y$
- OR denoted by $X + Y$
- XOR denoted by $X \oplus Y$
- NOT denoted by X' or \overline{X}
- NAND denoted by $\overline{X \cdot Y}$
- NOR denoted by $\overline{X + Y}$
- XNOR denoted by $\overline{X \oplus Y}$

5

Half and Full Adder Truth Tables

1)

B	A	S
0	0	0
0	1	1
1	0	1
1	1	0

2)

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

C	B	A	S	C	B	A	C
0	0	0	0	0	0	0	0
0	0	1	1	0	0	1	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	1	1
1	0	0	1	1	0	0	0
1	0	1	0	1	0	1	1
1	1	0	0	1	1	0	1
1	1	1	1	1	1	1	1

6

Truth Table with Three Inputs

- Three inputs X, Y, and Z; Output is F
- Logic Function:
F = 1 if and only if there is a 0 to the left of a 1 in the input

• Truth Table:

X	Y	Z	F	Min term
0	0	0	0	
0	0	1	1	
0	1	0	1	
0	1	1	1	
1	0	0	0	
1	0	1	1	
1	1	0	0	
1	1	1	0	

- Logic Expression:
F =

7

Truth Table with Four Inputs

- Four inputs X, Y, Z, and W; Output is F
- Logic Function:
F = 1 if and only if number of variables with value 1 is more than the number of variables with value 0

• Truth Table:

XYZW	F
0000	0
0001	0
0010	0
0011	0
0100	0
0101	0
0110	0
0111	1
1000	0
1001	0
1010	0
1011	1
1100	0
1101	1
1110	1
1111	1

- Logic Expression:
F =

8

The Idea of Min Term / Product Term

X	Y	F	A	B	X	Y	Min Term
0	0	1	1	0	0	0	X' Y'
0	1	0	0	0	0	1	X' Y
1	0	0	0	0	1	0	X Y'
1	1	1	0	1	1	1	X Y

- Each row in a truth table represents a unique combination of variables
- Each row can be expressed as a logic combination specifying when that row combination is equal to a 1
- The term is called a MIN TERM or a PRODUCT TERM
- Thus $F = A + B = X'Y' + XY$

9

Truth Table with Two Inputs

- Two inputs X and Y; Output is F
- Logic Function:
F = 1 if and only if X = Y

• Truth Table:

X	Y	F	Min Term
0	0	1	X'Y'
0	1	0	X'Y
1	0	0	XY'
1	1	1	XY

- Logic Expression:
 $F = X'Y'.1 + X'Y.0 + XY'.0 + XY.1$
 $= X'Y' + XY$

10

Min / Product terms for more variables

XYZ	Min Term	XYZW	Min Term
000	X' Y' Z'	0000	X' Y' Z' W'
001	X' Y' Z	0001	X' Y' Z' W
010	X' Y Z'	0010	X' Y' Z W'
011	X' Y Z	0011	X' Y' Z W
100	X Y' Z'	0100	X' Y Z' W'
101	X Y' Z	0101	X' Y Z' W
110	X Y Z'	0110	X' Y Z W'
111	X Y Z	0111	X' Y Z W
		1000	X Y' Z' W'
		1001	X Y' Z' W
		1010	X Y' Z W'
		1011	X Y' Z W
		1100	X Y Z' W'
		1101	X Y Z' W
		1110	X Y Z W'
		1111	X Y Z W

11

Multiplexer Circuit

s, x_1, x_2	$f(s, x_1, x_2)$
000	0
001	0
010	1
011	1
100	0
101	1
110	0
111	1

More compact truth-table representation

s	$f(s, x_1, x_2)$
0	x_1
1	x_2

$f = s'.x_1 + s.x_2$

Truth Table

Circuit

Graphical symbol

12

Canonical Sum-of-Product Expression

- A product (min) term is a unique combination of variables:
 - It has a value of 1 for only one input combination
 - It is 0 for all the other combinations of variables
- To write an expression, we need not write the entire truth table
- We only need those combinations for which function output is 1
- For example, for the function below: $f = x'yz' + xy'z' + xyz$

x	y	z	f	Min term
0	0	0	0	
0	0	1	0	
0	1	0	1	$x'yz'$
0	1	1	0	
1	0	0	1	$xy'z'$
1	0	1	0	
1	1	0	0	
1	1	1	1	xyz

- This is called the Canonical Sum-of-Product (SOP) Expression

13

Shorthand Notation for Canonical SOP

- We can also assign an integer to represent each input combination
- Thus the function produces a 1 for input combinations 2, 4, 7
- Therefore, the function can be written as $f(x,y,z) = \sum m(2,4,7)$

x	y	z	f	Index for shorthand notation
0	0	0	0	0
0	0	1	0	1
0	1	0	1	2
0	1	1	0	3
1	0	0	1	4
1	0	1	0	5
1	1	0	0	6
1	1	1	1	7

14

Max / Sum Terms

- A max (sum) term is also a unique combination of variables
 - However, it is opposite of a min term
 - It has a value of 0 for only one input combination
 - It is 1 for all the other combinations of variables
 - That is why it is called a max (sum) term
 - Each row in truth table has a max term corresponding to it
- Example, a max term $(x+y+z)$ is 0 for combination $xyz=000$ only

X	Y	Max Term
0	0	$X+Y$
0	1	$X+Y'$
1	0	$X'+Y$
1	1	$X'+Y'$

15

Canonical Product-of-Sum Expression

- A function can also be written in terms of max terms
- The function is product of all max terms for which function is 0
- For example, the same function of three variable x, y, and z produces 0 for $xyz=000, 011, 101$, then
 - $F = (x+y+z).(x+y'+z').(x'+y+z')$
- This is called the Canonical Product-of-Sum (POS) Expression
- The function can also be written as $F(x,y,z) = \prod M(0,3,5)$

X	Y	Z	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	0

$F = (F')$
 $= (x'y'z' + x'y'z + xy'z')$
 $= (x+y+z).(x+y'+z').(x'+y+z')$

16

Truth Tables and Logic Expression for Adder

A	B	C	X	Y
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$X(A,B,C) = \sum m(1,2,4,7)$
 $Y(A,B,C) = \sum m(3,5,6,7)$
 $X(A,B,C) = \prod M(0,3,5,6)$
 $Y(A,B,C) = \prod M(0,1,2,4,7)$

$$X = A'B'C + A'BC' + AB'C' + ABC$$

$$Y = A'BC + AB'C + ABC' + ABC$$

17

Multiple Forms and Equivalence

- Canonical Sum-of-Product form
- Canonical Product-of-sum form
- How to convert one from other?
- Minterm expansion of X to minterm expansion of X'
 - Just take the terms that are missing
- Maxterm expansion of X to maxterm expansion of X'
 - Just take the terms that are missing

$$X(A,B,C) = \sum m(1,2,4,7) \quad X'(A,B,C) = \sum m(0,3,5,6)$$

$$X(A,B,C) = \prod M(0,3,5,6) \quad X'(A,B,C) = \prod M(1,2,4,7)$$

18

Boolean Algebra



George Boole
1815-1864

- An algebraic structure consists of
 - a set of elements {0, 1}
 - binary operators {+, .}
 - and a unary operator { ' }
- Introduced by George Boole in 1854
- An effective means of describing circuits built with switches
- A powerful tool that can be used for designing and analyzing logic circuits

19

Axioms of Boolean Algebra

- 1a: $0 \cdot 0 = 0$
1b: $1 + 1 = 1$
- 2a: $1 \cdot 1 = 1$
2b: $0 + 0 = 0$
- 3a: $0 \cdot 1 = 1 \cdot 0 = 0$
3b: $1 + 0 = 0 + 1 = 1$
- 4a: If $x=0$, then $x' = 1$
4b: If $x=1$, then $x' = 0$

20

Single-Variable Theorems

- 5a: $x \cdot 0 = 0$ Null
5b: $x + 1 = 1$
- 6a: $x \cdot 1 = x$ Identity
6b: $x + 0 = x$
- 7a: $x \cdot x = x$ Idempotency
7b: $x + x = x$
- 8a: $x \cdot x' = 0$ Complementarity
8b: $x + x' = 1$
- 9: $(x')' = x$ Involution

21

Two- and Three-Variable Properties

- 10a: $x \cdot y = y \cdot x$ Commutative
10b: $x + y = y + x$
- 11a: $x \cdot (y \cdot z) = (x \cdot y) \cdot z$ Associative
11b: $x + (y + z) = (x + y) + z$
- 12a: $x \cdot (y + z) = x \cdot y + x \cdot z$ Distributive
12b: $x + y \cdot z = (x + y) \cdot (x + z)$
- 13a: $x + x \cdot y = x$ Absorption
13b: $x \cdot (x + y) = x$

22

Other Properties


- Combining
14a: $x \cdot y + x \cdot y' = x$
14b: $(x + y) \cdot (x + y') = x$
- DeMorgan's Theorem
15a: $(x \cdot y)' = x' + y'$
15b: $(x + y)' = x' \cdot y'$
- Another form of Absorption
16a: $x + x' \cdot y = x + y$
16b: $x \cdot (x' + y) = x \cdot y$

23

Simplify Logic Function by Algebraic Manipulation

$$\begin{aligned}
 F &= X'YZ + X'YZ' + XZ \\
 &= X'Y(Z+Z') + XZ && \text{by Distributive} \\
 &= X'Y(1) + XZ && \text{by Complementarity} \\
 &= X'Y + XZ && \text{by Identity}
 \end{aligned}$$

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 



24

Principle of Duality

- **Dual:**
 - A dual of a Boolean expression is derived by replacing $.$ by $+$, $+$ by $.$, 0 by 1, and 1 by 0 and leaving variables unchanged
 - In general duality: $f^D(x_1, x_2, \dots, x_n, 0, 1, +, \cdot) = f(x_1, x_2, \dots, x_n, 1, 0, \cdot, +)$
- **Principle of Duality:**
 - If any theorem can be proven, the dual theorem can also be proven.
 - A meta-theorem (a theorem about theorems)
- **Examples:**
 - **Multiplication and factoring:**
 - $(x+y) \cdot (x'+z) = x \cdot z + x' \cdot y$ and $x \cdot y + x' \cdot z = (x+z) \cdot (x'+y)$
 - **Consensus:**
 - $(x \cdot y) + (y \cdot z) + (x' \cdot z) = x \cdot y + x' \cdot z$ and


25

  DeMorgan's Theorem in Terms of Logic Gates




26

Using NAND to Implement SOP

 

27

Using NOR to Implement POS

 

28

Order of Precedence of Logic Operators

- From highest precedence to lowest: NOT, AND, OR
- We can use parenthesis to change the order


- **Examples:**

$$f = X' + X \cdot Y \text{ is the same as } f = ((X') + (X \cdot Y))$$

$$f = X \cdot (Y + Z) \text{ is NOT the same as } f = X \cdot Y + Z$$

29

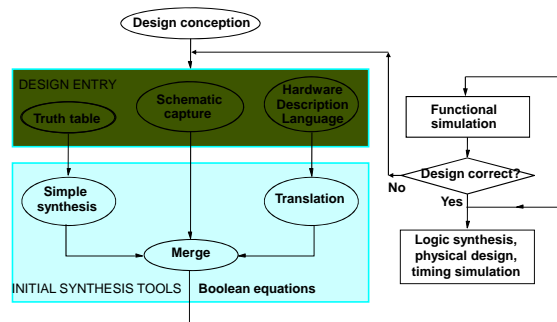A Typical CAD (Computer-Aided Design) System



30

Karnaugh map

- Karnaugh map (K-map) allows viewing the function in a picture form
- Containing the same information as a truth table
- But terms are arranged such that two neighbors differ in only one variable
- It is easy to identify which terms can be combined
- Example:

A map with 3 variables

	AB	00	01	11	10
C	0	1	0	1	1
	1	1	1	1	0

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

31

Location of Min-terms in K-maps

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

	$x_1 x_2$	00	01	11	10
x_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

(b) Karnaugh map

$$m_2 + m_6 = x_1' x_2 x_3' + x_1 x_2 x_3' = x_2 x_3'$$

(a) Truth table

32

Simplification using K-map

- Groups of '1's of size 1x1, 2x1, 1x2, 2x2, 4x1, 1x4, 4x2, 2x4, or 4x4 are called prime implicants (p.159 in textbook).

	AB	00	01	11	10
C	0	1	0	1	1
	1	1	1	1	0

	AB	00	01	11	10
C	0	1	0	1	1
	1	1	1	1	0

- A '1' in the K-map can be used by more than one group.
- Some rule-of-thumb in selecting groups:
 - Try to use as few group as possible to cover all '1's.
 - For each group, try to make it as large as you can (i.e., if you can use a 2x2, don't use a 2x1 even if that is enough).

33

Examples of 3-Variable K-map

	$x_1 x_2$	00	01	11	10
x_3	0	0	0	1	1
	1	1	0	0	1

$$f = x_1 x_3 + x_2 x_3$$

	$x_1 x_2$	00	01	11	10
x_3	0	1	1	1	1
	1	0	0	0	1

$$f = x_3 + x_1 x_2$$

34

Karnaugh maps with up to 4 variables

- Example: 1, 2, 3, and 4 variables maps are shown below

A	B	C	D
0	0	1	
0	1	0	
1	0	1	

- What if a function has 5 variables?

35

K-map Example for Adder functions

A	B	C	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S(A, B, C) = \sum m(1, 2, 4, 7)$$

$$Cout(A, B, C) = \sum m(3, 5, 6, 7)$$

S

	AB	00	01	11	10
C	0	0	1	0	1
	1	1	0	1	0

Cout

	AB	00	01	11	10
C	0	0	0	1	0
	1	0	1	1	1


$$S = A'B'C + A'BC' + AB'C' + ABC$$

$$Cout = BC + AC + AB$$

36

K-map with Don't Care Conditions

 - **Don't care condition** is input combination that will never occur.
- So the corresponding output can either be 0 or 1.
- This can be used to help simplifying logic functions.
- Example: $F(A,B,C,D) = \sum m(1,3,7,11,15) + \sum D(0,2,5)$



$$F = CD + A'B'$$


$$F = CD + A'D$$

d: Don't Care Condition

37

 Examples

- Simplify the following function considering:
 - the sum-of-products form
 - the product-of-sums form




38

1-bit building blocks to make n-bit circuit

- Design a 1-bit circuit with proper "glue logic" to use it for n-bits
 - It is called a bit slice
 - The basic idea of bit slicing is to design a 1-bit circuit and then piece together n of these to get an n-bit component

 • Example:

- A half-adder adds two 1-bit inputs
- Two half adders can be used to add 3 bits
- A 3-bit adder is a full adder
- A full adder can be a bit slice to construct an n-bit adder




Half Adder

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

39

Full adder & multi-bit ripple-carry adder

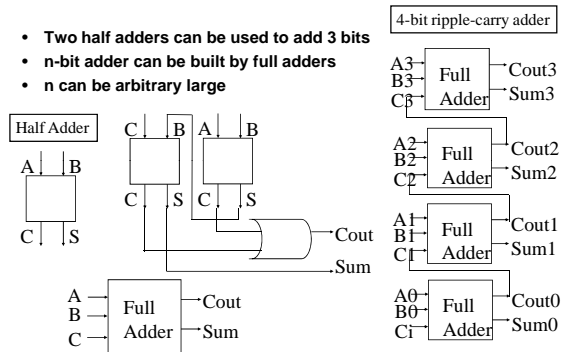
- Two half adders can be used to add 3 bits
- n-bit adder can be built by full adders
- n can be arbitrary large



40

Multiple Function Unit Design

 - Design a unit that can do more than one function
- In that case, we can design a function unit for each operation like ADD, SUB, AND, OR,
- And then select the desired output
- For example, if we want to be able to perform ADD and SUB on two given operands A and B, and select any one
- Then the following set up will work



41


ADD/SUB unit design

- Separate ADD and SUB units are expensive
- We can simplify the design
- $A - B$ is the same as adding negation of B to A
- How to negate?
 - 2's complement (i.e., take 1's complement and add 1)
 - Adding 1 is also expensive
 - It needs an n-bit adder in general
 - However, we only need to add two bits in each stage
 - In the first stage, we need to add 1's complement of LSB and 1
 - In other stages, we need to add carry output of previous bit to 1's complement of current bit
- We select B or negation of B depending on the requirement
- We add A to the selected input to obtain the result

42

Multiplexing and Multiplexer

- Multiplexers are circuits which select one of many inputs
- In here, we assume that we have one-bit inputs (in general, each input may have more than one bit)
- Suppose we have eight inputs: I0, I1, I2, I3, I4, I5, I6, I7
- We want one of them to be output based on selection signals
- 3 bits of selection signals to decide which input goes to output
- Note the order of selection signals
 - X is MSB and Z is LSB

 


43

Multiplexer Implementation


- We can write a logic expression for output F as follows
 
$$F = X' Y' Z' I_0 + X' Y' Z I_1 + X' Y Z' I_2 + X' Y Z I_3 + X Y' Z' I_4 + X Y' Z I_5 + X Y Z' I_6 + X Y Z I_7$$
- This circuit can be implemented using
 - eight 4-input AND gates and one 8-input OR gates



44

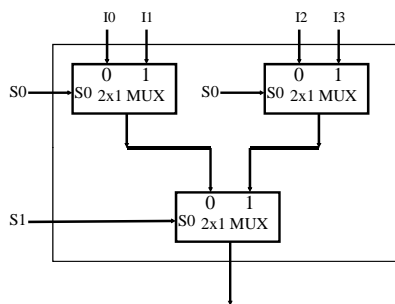Implementing 4-to-1 MUX using 2-to-1 MUXs




45

Making a 2-bit 4-to-1 Multiplexer

- Four 2-bit inputs A, B, C, D
- One 2-bit output F
- Two bits of selection signal X Y


X	Y	F
0	0	A
0	1	B
1	0	C
1	1	D

 

46

Synthesis of Logic Functions using Multiplexers

- Multiplexers can be directly used to implement a function
- Easiest way is to use function inputs as selection signals
- Input to multiplexer is a set of 1s and 0s depending on the function to be implemented
- We use a 8-to-1 multiplexer to implement function F
- Three select signals are X, Y, and Z, and output is F
- Eight inputs to multiplexer are 1 0 1 0 1 1 0 0
- Depending on the input signals
 - multiplexer will select proper output

 


47

Implementing 3-variable functions with 4x1 MUX

- Divide the outputs into 4 groups based on X and Y.
- Write the outputs as a function of Z
- There are only 4 possibilities: F=Z, F=Z', F=0, F=1


X	Y	Z	F
0	0	0	F=Z
0	0	1	F=Z
0	1	0	F=Z'
0	1	1	F=Z'
1	0	0	F=0
1	0	1	F=0
1	1	0	F=1
1	1	1	F=1

 

48

Implementing 4-variable functions with 8x1 MUX


A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

 

49

Implementing 4-variable functions with 4x1 MUX


A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

 

50

Implementing 4-variable functions with 4x1 MUX

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

 

51


Definition of Decoder

- Suppose we have n input bits (which can represent up to 2^n distinct elements of coded information).
- We need a device that allows us to select which of the 2^n elements, devices, memory locations, etc. is being selected.
- In general:
 - A decoder has n input bits
 - A decoder has 2^n (or less) output bits
 - As a rule, all but one of the outputs is zero (deselected) at any time (called *one-hot encoded*)

52

2-to-4 Decoder

 - The 2-to-4 decoder is a block which decodes the 2-bit binary inputs and produces four outputs
- One output corresponding to the input combination is a one
- Two inputs and four outputs are shown in the figure
- The equations are



- $y_0 = x_1' \cdot x_0'$
- $y_1 = x_1' \cdot x_0$
- $y_2 = x_1 \cdot x_0'$
- $y_3 = x_1 \cdot x_0$

- The truth table:

x1	x0	y3	y2	y1	y0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

53

Definition of Encoder

- Encoders perform the inverse function of Decoders.
- An encoder has 2^n (or less) input bits and n output bits
- The output bits generate the binary code corresponding to the input value
- Assuming only one input has a value of 1 at any given time
- Example: An 8-to-3 Encoder

Inputs								Outputs		
D7	D6	D5	D4	D3	D2	D1	D0	A2	A1	A0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1



$$A_2 = D_4 + D_5 + D_6 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_0 = D_1 + D_3 + D_5 + D_7$$

54

  What are the outputs of the following circuits?



55

Priority Encoders

- Each input signal has a priority level associated with it
- May have more than one 1's in the input signals
- Outputs indicate the active input that has the highest priority
- Example: 4-to-2 priority encoder
 - Assume w_3 has the highest priority and w_0 the lowest
 - $y_1 y_0$ indicate the active input with highest priority
 - z indicates none of the inputs is equal to 1

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1


Let $i_0 = w_0 w_1' w_2' w_3'$
 $i_1 = w_1 w_2' w_3'$
 $i_2 = w_2 w_3'$
 $i_3 = w_3$
 Then $y_0 = i_1 + i_3$
 $y_1 = i_2 + i_3$

x: both 0 and 1 (irrelevant)

56

Decoder with Enable

 - A 2-to-4 decoder can be designed with an enable signal
- If enable is zero, all outputs are zero
- If enable is 1, then an output corresponding to two inputs is a one, all others are still zero
- The equations are
 - $y_0 = x_1' \cdot x_0' \cdot E$
 - $y_1 = x_1' \cdot x_0 \cdot E$
 - $y_2 = x_1 \cdot x_0' \cdot E$
 - $y_3 = x_1 \cdot x_0 \cdot E$



57


Truth Table for 2-to-4 Decoder with Enable

x_1	x_0	E	y_3	y_2	y_1	y_0
0	0	0	0	0	0	0
0	0	1	0	0	0	1
0	1	0	0	0	0	0
0	1	1	0	0	1	0
1	0	0	0	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	0	0
1	1	1	1	0	0	0

58

Demultiplexers

 
- Perform the opposite function of multiplexers
- Placing the value of a single data input onto one of the multiple data outputs
- Same implementation as decoder with enable
- Enable input of decoder serves as the data input for the demultiplexer



59

3-to-8 decoder using a 2-to-4 decoder with Enable

 - The 3-to-8 decoder can be implemented using two 2-to-4 decoders with enable and one NOT gate
- The implementation is as shown



60

Verilog HDL

Popular Hardware Description Languages (HDLs):

- Verilog HDL
 - More popular with US companies
 - Similar to C / Pascal programming language in syntax
- VHDL
 - More popular with European companies
 - Similar to Ada programming language in syntax
 - More “verbose” than Verilog

Uses of Verilog:

- Synthesis
- Simulation
- Verification

61

Verilog Syntax

- Module / Signal names:
 - Start with a letter
 - Follow by any sequence of letter, number, _ and \$
 - Case sensitive
- Comment by // or /* */
- White spaces (SPACE, TAB, blank line) are ignored.


```
// An example
module example1 (x1, x2, x3, f);
    input x1, x2, x3;
    output f;

    and (g, x1, x2);
    not (k, x2);
    and (h, k, x3);
    or (f, g, h);
endmodule
```

```
// An example
module example1 (x1, x2, x3,
f);input x1, x2, x3; output
f;and (g, x1, x2); not (k, x2
);and (h, k, x3); or (f, g,
h);endmodule
```

62

 Structural Specification of Logic Circuit




```
module example1 (x1, x2, x3, f);
    input x1, x2, x3;
    output f;

    and (g, x1, x2);
    not (k, x2);
    and (h, k, x3);
    or (f, g, h);
endmodule
```

63

 Another Example of Structural Specification




```
module example2 (x1, x2, x3, x4, f, g, h);
    input x1, x2, x3, x4;
    output f, g, h;

    and (z1, x1, x3);
    and (z2, x2, x4);
    or (g, z1, z2);
    or (z3, x1, ~x3);
    or (z4, ~x2, x4);
    and (h, z3, z4);
    or (f, g, h);
endmodule
```

64

 Behavioral Specification Continuous Assignment



```
// Structural Specification
module example1 (x1, x2, x3, f);
    input x1, x2, x3;
    output f;

    and (g, x1, x2);
    not (k, x2);
    and (h, k, x3);
    or (f, g, h);
endmodule
```


```
// Behavioral Specification
module example3 (x1, x2, x3, f);
    input x1, x2, x3;
    output f;

    assign f = (x1 & x2) | (~x2 & x3);
endmodule
```

Concurrent statement

65

 Behavioral Specification Procedural (Sequential) Statement



```
module example5 (x1, x2, x3, f);
    input x1, x2, x3;
    output f;
    reg f; // Declared as variable (register) if assigned
           // a value in a procedural statement

    always @(x1 or x2 or x3) // Sensitivity list
    begin // always block
        if (x2 == 1)
            f = x1;
        else
            f = x3;
    end
endmodule
```

66