 


### Sequential Circuit and State Machine

- Combinational circuits
  - output is simply dependent on the current input
- Sequential circuits
  - output may depend on the input sequence
- The effect of the input sequence can be memorized as a state of the system
- So a sequential circuit is also called a State Machine
- Memory elements (usually D flop-flips) are used to store the state
- System state changes with input
- A different input sequence produces different final state and different output sequence

### State Transition Diagram (or State Diagram)

- Example:
  - A very simple machine to remember which building I am at
  - The only input is the clock signal
  - The state machine is represented as a state transition diagram (or called state diagram) below
  - One step (i.e., transition) can be taken whenever there is a clock signal



### State Transition Table (State Table)


- States can be coded as binary combinations of variables
- Let N be total number of states, each state can be represented by  $n = \log_2 N$  bits
- n bits can represent up to  $2^n$  states
- This is called the state assignment
- A truth table will then give the next state
- This is called a state transition table (or called state table)
- $x_n$  and  $y_n$  can be specified in terms  $x_o$  and  $y_o$

	X	Y
S0	0	0
S1	0	1
S2	1	0
S3	1	1

Current State $x_o y_o$	Next State $x_n y_n$
0 0	0 1
0 1	1 0
1 0	1 1
1 1	0 0

$x_n = x_o \oplus y_o$   
 $y_n = y_o'$
 
### The Resulting Sequential Circuit / State Machine



Current State $x_o y_o$	Next State $x_n y_n$
0 0	0 1
0 1	1 0
1 0	1 1
1 1	0 0

$x_n = x_o \oplus y_o$   
 $y_n = y_o'$

### Counter state machine

- A counter counts
- Number of elements in counter determines how many different states we need
- For example, an eight-state counter can count eight steps

Current X Y Z	Next X Y Z	
0 0 0	0 0 1	X=
0 0 1	0 1 0	
0 1 0	0 1 1	Y=
0 1 1	1 0 0	
1 0 0	1 0 1	Z=
1 0 1	1 1 0	
1 1 0	1 1 1	
1 1 1	0 0 0	


### Another counter

- Counter need not have number of states that is equal to a power of 2
- Here is a five state counter
- Is it simpler?

Current X Y Z	Next X Y Z	
0 0 0	0 0 1	X=
0 0 1	0 1 0	
0 1 0	0 1 1	Y=
0 1 1	1 0 0	
1 0 0	0 0 0	Z=
 
### State Machine with Explicit Inputs

- In a state transition diagram, state may change with time
  - A clock signal represents passage of time
  - Each time a clock arrives, state changes to next state
  - Clock is an implicit input
  - There may or may not be other explicit inputs
- For the previous example, let say we also have an explicit input  $i$
  - For the state transition diagram shown,  $i$  can be 0 or 1
  - Next state depends on current state and the value of input  $i$
  - When the next state depends upon the inputs, the inputs are examined at the clock edges



### State Transition Table with Explicit Inputs

- State transition table will have two sets of inputs
- Current state variable and explicit input variables
- Total number of row in table is  $2^{(n+m)}$ 
  - $n$  is number of variables representing states
  - $m$  is number of input variables

State Assignment

	X	Y
S0	0	0
S1	0	1
S2	1	0
S3	1	1

Current	Input	Next State
$x_0 y_0$	$i$	$x_n y_n$
0 0	0	0 1
0 0	1	1 0
0 1	0	1 0
0 1	1	1 1
1 0	0	1 1
1 0	1	0 0
1 1	0	0 0
1 1	1	0 1

$$x_n = x_0' y_0' i + x_0' y_0 i' + x_0 y_0' i + x_0 y_0 i'$$

$$= x_0' i + x_0' y_0 + x_0 y_0' i'$$

$$y_n = x_0' y_0' i' + x_0' y_0 i + x_0 y_0' i' + x_0 y_0 i$$


$$= y_0' i' + y_0 i$$

### Output of state machine

- Output of a state machine may depend on state, or state & input:
  - Mealy machine: Output depends on both current state and current input (i.e., depends on transition)
  - Moore machine: Output depends on current state
- Thus we have two different circuits to implement
  - 1. Decides what is the next state
  - 2. Decides what is the output
- Both circuits are combinational
- States are remembered by memory elements
  - Usually D flips-flops are used to remember states

 
### State Transition Diagram with Outputs

- Moore Machine: (For example, output 1 whenever in Coover)
  - Output is 1 for states S0 and S1.
- Mealy Machine: (For example, output 1 whenever walking between Coover and Durham)
  - Output is 1 for transitions from S0 to S1 and S1 to S2.



 
### Overall structure of a State machine

**Moore machine** (outputs depend on current state, but not current inputs)



 **Mealy machine** (outputs depend on both current state and current inputs)



### Steps in designing a state machine

- Start writing a state transition diagram
  - It has an initial state
  - It has other states to keep track of various activities
  - It has some transitions
- Generate a state transition table and an output table
- Write state transition table and output table in binary
  - Needs state assignment, i.e., the code used for each state
  - State assignment is a complex process
  - For the time being assume straightforward combinations
- Derive canonical sum-of-product expressions
  - You can simplify the expressions

### Determining number of states

- Identify how many different things we need to keep track of
- This is critical to know
- Otherwise the number of states (and their meaning) may get out of hand very quickly
- This is different from what is the output of interest (in each state we may have some outputs)
- For example, if we are to process a sequence of input bits, depending on interest, the number of states may be different
  - If we need to know how many 1's there are, we need states corresponding to the count
  - If we need to know if we have even or odd number of 1's, we may need only two states

13


### Example

- Design a state machine that will repeatedly display in binary values 1, 3, 5, and 7
- Solutions:
  - How many states we need?
  - What is the state transition diagram?
  - What is the output in each state?
  - What is the next state logic?
  - Construct the truth tables with state variables
  - Derive the next state logic and output logic
  - Draw the circuits

14

### Example (contd.)

- We need four states: S0, S1, S2, S3

 

State transition table		Implementation level state transition table		Output table		Implementation level output tables						
Current State	Next State	X	Y	X	Y	Current State	Output	X	Y	L2	L1	L0
S0	S1	0	0	0	1	S0	1	0	0	0	0	1
S1	S2	0	1	1	0	S1	3	0	1	0	1	1
S2	S3	1	0	1	1	S2	5	1	0	1	0	1
S3	S0	1	1	0	0	S3	7	1	1	1	1	1

$$\begin{aligned}
 X &= X'Y + XY' & L2 &= XY' + XY = X \\
 Y &= X'Y' + XY' = Y' & L1 &= X'Y + XY = Y \\
 & & L0 &= X'Y' + X'Y + XY' + XY = X' + X = 1
 \end{aligned}$$


15

### Another Example for State Machine

- Design a state machine to display the characters in the string HELLO using a seven segment display
- How many states do we need?
  - Five, one for each character
  - In state S0 (000) we display H
  - In state S1 (001) we display E
  - In state S2 (010) we display L
  - In state S3 (011) we display L
  - In state S4 (100) we display O
- State transitions are
  - S0 -> S1
  - S1 -> S2
  - S2 -> S3
  - S3 -> S4
  - S4 -> S0

16

### Example (contd.)

 


- Next State and Output logic tables are

Cur State	Next State	State	Output
Xc Yc Zc	Xn Yn Zn	Xc Yc Zc	a b c d e f g
0 0 0	0 0 1	0 0 0	0 1 1 0 1 1 1
0 0 1	0 1 0	0 0 1	1 0 0 1 1 1 1
0 1 0	0 1 1	0 1 0	0 0 0 1 1 1 0
0 1 1	1 0 0	0 1 1	0 0 0 1 1 1 0
1 0 0	0 0 0	1 0 0	1 1 1 1 1 1 0

17
 
### To Detect if # of 1's in Input is Divisible by 3

- Design a state machine with 1 bit of input and 1 bit of output
- The output bit will be 1 whenever the number of bits in input sequence is divisible by 3
- How many states do we need?
- What are the meaning of the states?
  - In state S0 (00), remainder = 0 (i.e., divisible by 3)
  - In state S1 (01), remainder = 1
  - In state S2 (10), remainder = 2
- Choose to design a Moore machine
  - Output is 1 whenever in state S0



18

### State machines as sequence detector

- State machine by nature are ideally suited to track state and detect specific sequence of events
- For example, we may design specific machines to track certain pattern in an input sequence
- Examples:
  - to count 1's in a sequence and produce an output if a specific situation occurs like 3rd one, or every 2nd one, or nth one
  - to generate an output or stop if a specific pattern in the sequence (such as 011 or 0101 or 1111) is observed
- In each of these cases, it is to create a relationship between input and output sequence
- We will review input and output relations for such operations

19

### Example input/output sequences

- n-th one detector, n=2
  - Input: 00100111011001010101110001
  - Output: 00000101001000010001010000
- n-th one detector, n=3
  - Input: 00100111011001010101110001
  - Output: 00000010001000000100010000
- 011 pattern detector
  - Input: 00100111011001010101110001
  - Output: 0000001000100000000000100000
- 1010 pattern detector
  - Input: 00100111011001010101110001
  - Output: 00000000000000000101000000

20


### How to design sequence detector

- Our goal is to be able to identify minimum number of states
- It is very easy to miss that goal (in terms of number of states)
- Sometimes CAD tools may identify redundant states
- We first discuss the number of possible states to track
- For example in sequence detection, for 011,
  - we need states representing we have not seen the first zero, we have seen only the first 0, we have seen 01, and finally we have seen 011
  - So a four state system will work
- 1010 has a pattern that also repeats part of the sequence
  - So we need states that represent starting state, received first 1, first 10, first 101, and finally 1010 (a total of five state)
  - However after we see 1010, we have already seen 10 pattern for the next output (i.e., if we have 101010 repeating)

21
 
### 3-rd One Detector

- Use a Mealy machine design
- 3 states are enough
- Have a similar structure to the Moore machine to detect if # of 1's in Input is Divisible by 3




- If Moore machine design is used, 4 states is needed

22
 
### Design of a sequence detector for 011

- Four states and state transitions are shown in the figure
- Output: 1 for State S3, 0 for all others




Current State	Input	Next State	State Assignment		Output of states	
			Current State	Binary	Current State	Output
S0	0	S0	S0	00	S0	0
S0	1	S1	S1	01	S1	0
S1	0	S1	S2	10	S2	0
S1	1	S2	S3	11	S3	1
S2	0	S2				
S2	1	S3				
S3	0	S0				
S3	1	S0				

23
 
### Design of a sequence detector for 1010

- Four states and state transitions are shown in the figure
- Output: 1 for State S4, 0 for all others



Current State	Input	Next State	State Assignment		Output of states	
			Current State	Binary	Current State	Output
S0	0	S0	S0	000	S0	0
S0	1	S1	S1	001	S1	0
S1	0	S2	S2	010	S2	0
S1	1	S3	S3	011	S3	0
S2	0	S2	S4	100	S4	1
S2	1	S3				
S3	0	S4				
S3	1	S0				
S4	0	S0				
S4	1	S0				

24

### Another example: a complex vending machine

- Vending Machine
  - Collect money, deliver product and change
- Vending machine may get three inputs, n, d, q
  - Inputs are nickel (5c), dime (10c), and quarter (25c)
  - Only one coin input at a time
  - Product cost is 40c
  - Does not accept more than 50c (blocks the coin slot)
  - Returns 5c or 10c back
  - Exact change appreciated
- How many states?
- What are the output signals?


25

### Design of Complex Vending Machine

- We are designing a Mealy state machine (i.e., output depends on both current state and inputs).
- Suppose we ask the machine to directly return the coin if it cannot accept an input coin.
- The following two-bit code is used:
  - 00 – no coin, 01 – nickel, 10 – dime, and 11 – quarter
- Inputs:  $I_1, I_2$  which represent the coin inserted
- Outputs:  $C_1, C_2, P$  where  $C_1, C_2$  represent the coin returned and  $P$  indicates whether to deliver product
- States: S00, S05, S10, S15, S20, S25, S30, S35
  - 3 bits are enough to encode the states
  - Notice the names (they need not be S0, S1....)
- State assignment: S00 – 000, S05 – 001, S10 – 010, S15 – 011, S20 – 100, S25 – 101, S30 – 110, S35 – 111

26


### State Diagram for Vending Machine

 

27

 
### Algorithmic State Machine (ASM) Charts

- Another way to represent a state machine
- State diagrams are useful when the machine has only a few inputs and outputs
- ASM charts may be more convenient for larger machines




28

### Example: Moore Machine

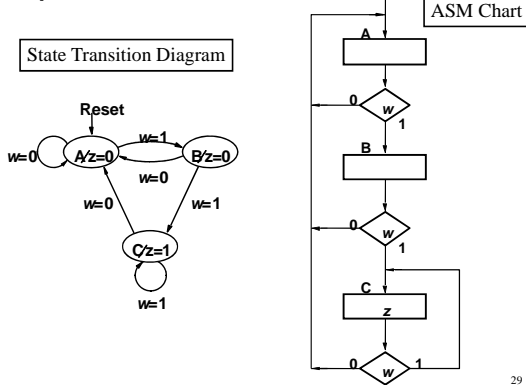

29

### Example: Mealy Machine

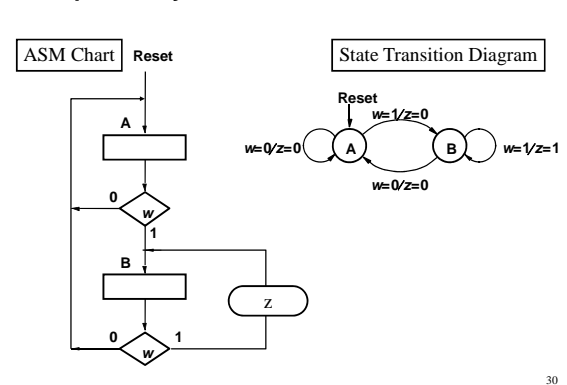

30


### Speed of Sequential circuit and Clock frequency

- **Clock frequency**
  - is the number of rising clock edges (clock ticks) in a fixed period of time
  - determines the speed of a sequential circuit
- **Clock cycle time (or clock period)** is the time between two rising clock edges
- If circuit runs at clock frequency of  $f$ , corresponding clock cycle time is
  - $T = 1/f$ , or
  - $f = 1/T$
- A frequency of 1 MHz gives a clock period of 1 micro second
- A frequency of 500 MHz gives a clock period of 2 nano second
- A frequency of 2 GHz gives a clock period of 0.5 nano second
- A frequency of 1 GHz gives a clock period of 1 nano second

(1 micro second =  $1e-6$  second, 1 nano second =  $1e-9$  second)

 
### Timing in a Sequential Circuit (State machine)

- From a rising clock edge, we should allow enough time for:
  - D FFs to generate stable output for the state
  - next state logic to generate the next state
  - D FFs to set up after the next state is available
- Then we can have the next rising clock edge
- Thus, D Flip-Flop propagation delay + Next state logic propagation delay + D FF set-up time sets a lower bound to the clock cycle time


 
### Review: Timing Issues of Combinational Circuits


- **Contamination delay:**
  - Minimum delay before any output starts to change once input changes
- **Propagation delay:**
  - Maximum delay after which all outputs are stable once input changes



- Contamination delay = 2
- Propagation delay = 3
- (Assume that delay of all gates = 1)
 
### Propagation delay for next-state logic

- The propagation delay for next-state logic is also called the compute time
- Consider a four states system
- State transition table and implementation level state transition table are given below





Current State	Next State	Current X	Next Y	Current X	Next Y
S0	S1	0	0	0	1
S1	S2	0	1	1	0
S2	S3	1	0	1	1
S3	S0	1	1	0	0

- Using the logic expressions below, combination logic for next state takes up to two gate delay (if both X and X' are available)

$$X := X'Y + XY'$$

$$Y := X'Y' + XY' = Y'$$

### Review: Timing Issues of FFs

  

- For this design:
- Set-up time = 5
  - Hold time = 1
  - Prop. delay = 3
  - (Assume that delay of all gates = 1)

### Timing Constraints for a Sequential Circuit

- **Clock cycle time**  $\geq$  FF Prop delay + Compute time + FF set-up time
- **Clock low time**  $\geq$  FF set-up time
- **Clock high time**  $\geq$  FF Prop delay
- **Contamination time of next state circuit**  $\geq$  FF hold time

