

Numbers

- **Bits are just bits (no inherent meaning)**
 - **conventions define relationship between bits and numbers**
- **Binary numbers (base 2)**
 - 0000 0001 0010 0011 0100 0101 0110 0111 1000 1001...**
 - decimal: $0 \dots 2^n - 1$**
- **Of course it gets more complicated:**
 - numbers are finite (overflow)**
 - fractions and real numbers**
 - negative numbers**
 - e.g., no MIPS subi instruction; addi can add a negative number)**
- **How do we represent negative numbers?**
 - i.e., which bit patterns will represent which numbers?**

Possible Representations

- | Sign Magnitude: | One's Complement | Two's Complement |
|-----------------|------------------|------------------|
| 000 = +0 | 000 = +0 | 000 = +0 |
| 001 = +1 | 001 = +1 | 001 = +1 |
| 010 = +2 | 010 = +2 | 010 = +2 |
| 011 = +3 | 011 = +3 | 011 = +3 |
| 100 = -0 | 100 = -3 | 100 = -4 |
| 101 = -1 | 101 = -2 | 101 = -3 |
| 110 = -2 | 110 = -1 | 110 = -2 |
| 111 = -3 | 111 = -0 | 111 = -1 |
- Issues: balance, number of zeros, ease of operations
- Which one is best? Why?

MIPS

- 32 bit signed numbers:

0000	0000	0000	0000	0000	0000	0000	0000	$_{\text{two}}$	=	0_{ten}	
0000	0000	0000	0000	0000	0000	0000	0001	$_{\text{two}}$	=	$+ 1_{\text{ten}}$	
0000	0000	0000	0000	0000	0000	0000	0010	$_{\text{two}}$	=	$+ 2_{\text{ten}}$	
...											
0111	1111	1111	1111	1111	1111	1111	1110	$_{\text{two}}$	=	$+ 2,147,483,646_{\text{ten}}$	/ <i>maxint</i>
0111	1111	1111	1111	1111	1111	1111	1111	$_{\text{two}}$	=	$+ 2,147,483,647_{\text{ten}}$	
1000	0000	0000	0000	0000	0000	0000	0000	$_{\text{two}}$	=	$- 2,147,483,648_{\text{ten}}$	/ <i>minint</i>
1000	0000	0000	0000	0000	0000	0000	0001	$_{\text{two}}$	=	$- 2,147,483,647_{\text{ten}}$	
1000	0000	0000	0000	0000	0000	0000	0010	$_{\text{two}}$	=	$- 2,147,483,646_{\text{ten}}$	
...											
1111	1111	1111	1111	1111	1111	1111	1101	$_{\text{two}}$	=	$- 3_{\text{ten}}$	
1111	1111	1111	1111	1111	1111	1111	1110	$_{\text{two}}$	=	$- 2_{\text{ten}}$	
1111	1111	1111	1111	1111	1111	1111	1111	$_{\text{two}}$	=	$- 1_{\text{ten}}$	

Two's Complement Operations

- **Negating a two's complement number: invert all bits and add 1**
 - remember: “negate” and “invert” are quite different!
- **Converting n bit numbers into numbers with more than n bits:**
 - MIPS 16 bit immediate gets converted to 32 bits for arithmetic
 - copy the most significant bit (the sign bit) into the other bits

0010 -> 0000 0010

1010 -> 1111 1010

 - "sign extension" (lbu vs. lb)

Addition & Subtraction

- Just like in grade school (carry/borrow 1s)

$$\begin{array}{r} 0111 \\ + 0110 \\ \hline \end{array} \qquad \begin{array}{r} 0111 \\ - 0110 \\ \hline \end{array} \qquad \begin{array}{r} 0110 \\ - 0101 \\ \hline \end{array}$$

- Two's complement operations easy
 - subtraction using addition of negative numbers




$$\begin{array}{r} 0111 \\ + 1010 \\ \hline \end{array}$$

- Overflow (result too large for finite computer word):
 - e.g., adding two n-bit numbers does not yield an n-bit number

$$\begin{array}{r} 0111 \\ + 0001 \\ \hline _ 1000 \end{array} \quad \textit{note that overflow term is somewhat misleading, it does not mean a carry "overflowed"}$$

One-Bit Adder

  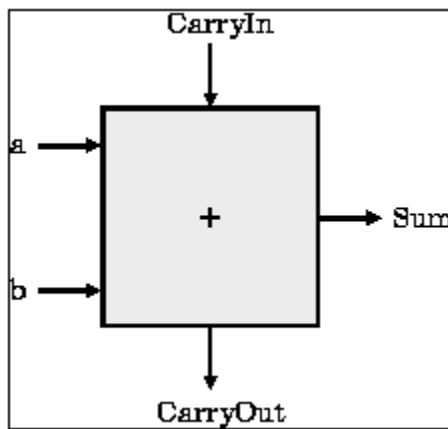- Takes three input bits and generates two output bits
- Multiple bits can be cascaded



Adder Boolean Algebra

•	A	B	CI	CO	S
•	0	0	0	0	0
•	0	0	1	0	1
•	0	1	0	0	1
•	0	1	1	1	0
•	1	0	0	0	1
•	1	0	1	1	0
•	1	1	0	1	0
•	1	1	1	1	1

$$C = A.B + A.CI + B.CI$$

$$S = A.B.CI + A'.B'.CI + A'.B.CI' + A.B'.CI'$$

Detecting Overflow

- **No overflow when adding a positive and a negative number**
- **No overflow when signs are the same for subtraction**
- **Overflow occurs when the value affects the sign:**
 - **overflow when adding two positives yields a negative**
 - **or, adding two negatives gives a positive**
 - **or, subtract a negative from a positive and get a negative**
 - **or, subtract a positive from a negative and get a positive**
- **Consider the operations $A + B$, and $A - B$**
 - **Can overflow occur if B is 0 ?**
 - **Can overflow occur if A is 0 ?**

Effects of Overflow

- An exception (interrupt) occurs
 - Control jumps to predefined address for exception
 - Interrupted address is saved for possible resumption
- Details based on software system / language
 - example: flight control vs. homework assignment
- Don't always want to detect overflow
 - new MIPS instructions: `addu`, `addiu`, `subu`

note: addiu still sign-extends!

note: sltu, sltiu for unsigned comparisons

Real Design

•	A	B	C	D	E	F
•	0	0	0	0	0	0
•	0	0	1	1	0	0
•	0	1	0	1	0	0
•	0	1	1	1	1	0
•	1	0	0	1	0	0
•	1	0	1	1	1	0
•	1	1	0	1	1	0
•	1	1	1	1	0	1



$$D = A + B + C$$

$$E = A'.B.C + A.B'.C + A.B.C'$$


$$F = A.B.C$$

An ALU (arithmetic logic unit)

  - Let's build an ALU to support the `andi` and `ori` instructions
 - we'll just build a 1 bit ALU, and use 32 of them




 - Possible Implementation (sum-of-products):



Different Implementations


 
- Not easy to decide the “best” way to build something
 - Don't want too many inputs to a single gate
 - Don't want to have to go through too many gates
 - for our purposes, ease of comprehension is important
- Let's look at a 1-bit ALU for addition:



$$c_{out} = a b + a c_{in} + b c_{in}$$
$$sum = a \text{ xor } b \text{ xor } c_{in}$$

- How could we build a 1-bit ALU for add, and, and or?
- How could we build a 32-bit ALU?


Building a 32 bit ALU

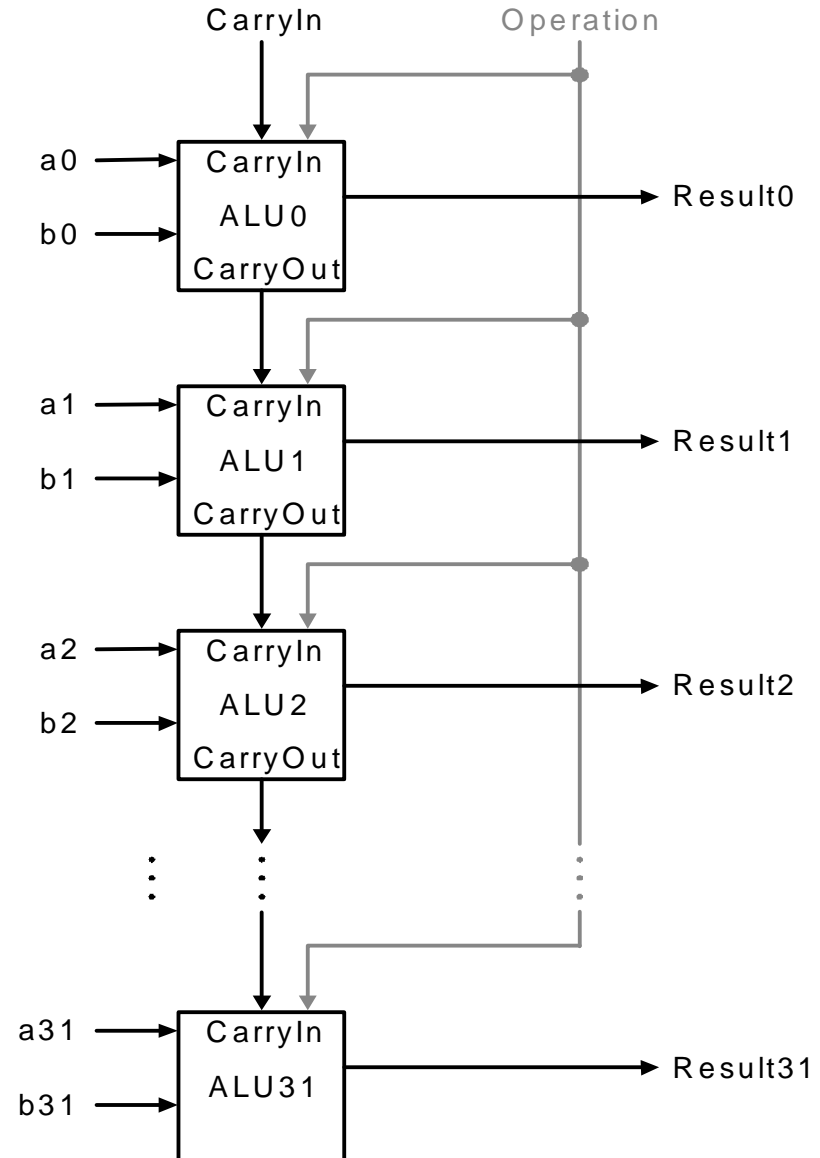 

What about subtraction (a - b) ?

- Two's complement approach: just negate b and add.
- How do we negate?

- A very clever solution:

 


Tailoring the ALU to the MIPS


- **Need to support the set-on-less-than instruction (slt)**
 - remember: **slt is an arithmetic instruction**
 - produces a 1 if $rs < rt$ and 0 otherwise
 - use subtraction: $(a-b) < 0$ implies $a < b$
- **Need to support test for equality (beq \$t5, \$t6, \$t7)**
 - use subtraction: $(a-b) = 0$ implies $a = b$

Supporting slt

- Can we figure out the idea?

 


a.

 

b.

A 32-bit ALU

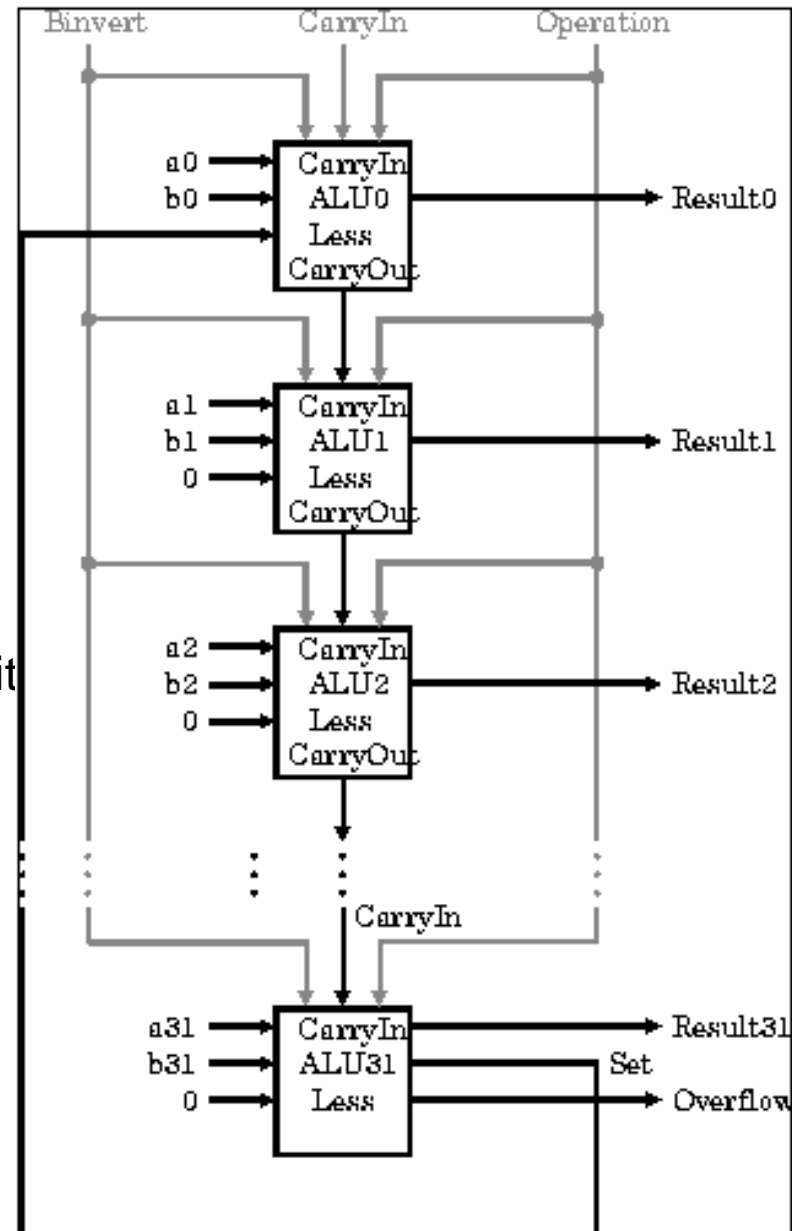- A Ripple carry ALU
- Two bits decide operation
 - Add/Sub
 - AND
 - OR
 - LESS
- 1 bit decide add/sub operation
- A carry in bit
- Bit 31 generates overflow and set bit




Test for equality

- Notice control lines:

000 = and
001 = or
010 = add
110 = subtract
111 = slt

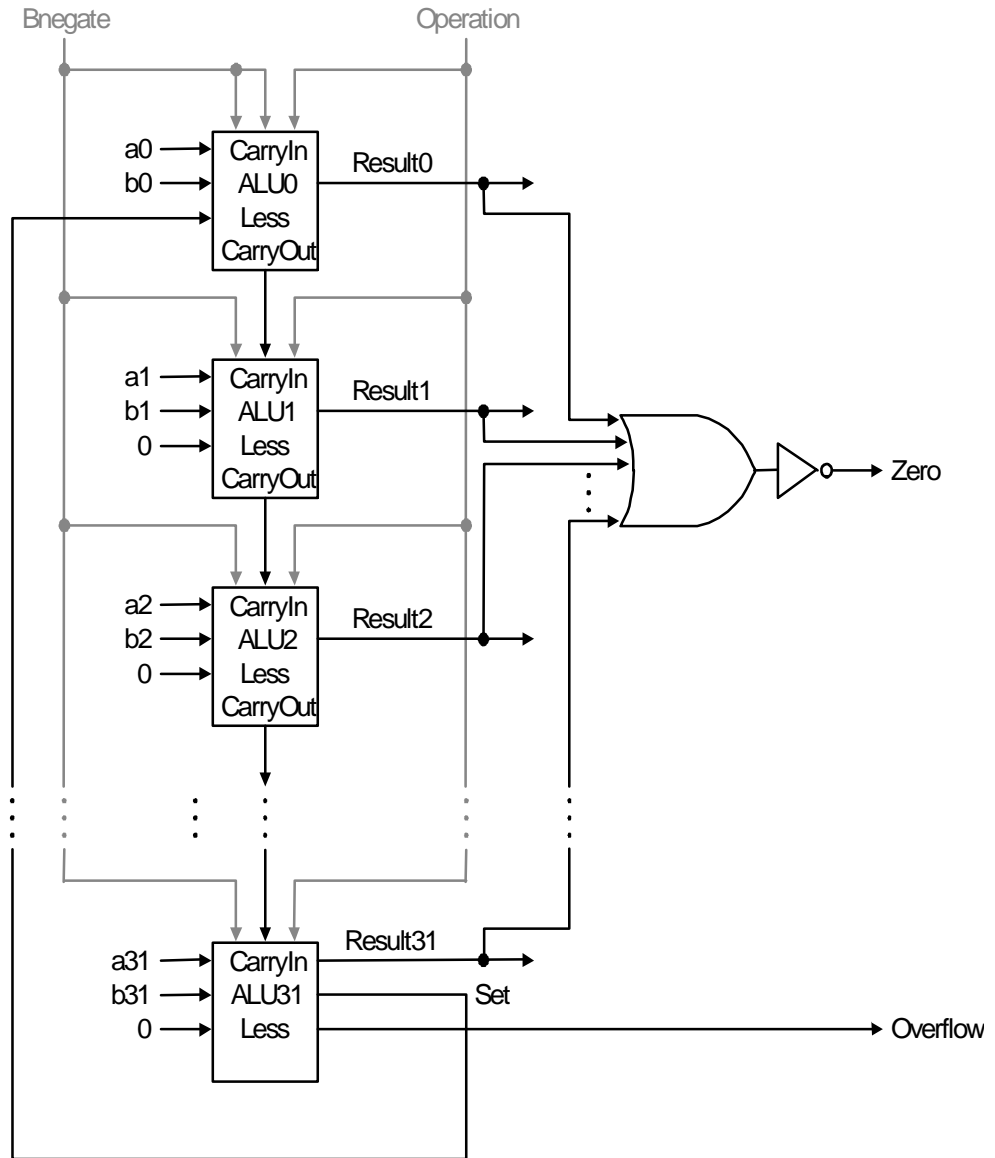•Note: zero is a 1 when the result is zero!



Problem: ripple carry adder is slow

- Is a 32-bit ALU as fast as a 1-bit ALU?
- Is there more than one way to do addition?
 - two extremes: ripple carry and sum-of-products

Can you see the ripple? How could you get rid of it?

$$\begin{aligned}c_1 &= b_0c_0 + a_0c_0 + a_0b_0 \\c_2 &= b_1c_1 + a_1c_1 + a_1b_1 \quad c_2 = \\c_3 &= b_2c_2 + a_2c_2 + a_2b_2 \quad c_3 = \\c_4 &= b_3c_3 + a_3c_3 + a_3b_3 \quad c_4 =\end{aligned}$$

Not feasible! Why?

Carry-look-ahead adder

- An approach in-between our two extremes
- Motivation:
 - If we didn't know the value of carry-in, what could we do?
 - When would we always generate a carry? $g_i = a_i b_i$
 - When would we propagate the carry? $p_i = a_i + b_i$
- Did we get rid of the ripple?

$$c_1 = g_0 + p_0 c_0$$


$$c_2 = g_1 + p_1 c_1 \quad c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 c_2 \quad c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

$$c_4 = g_3 + p_3 c_3 \quad c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$$


Feasible! Why?

A 4-bit carry look-ahead adder

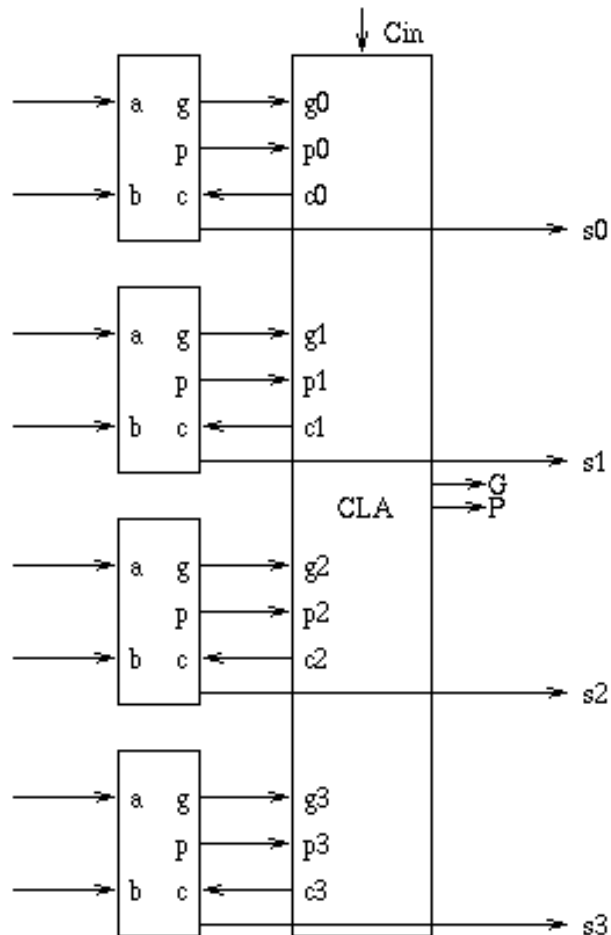

- **Generate g and p term for each bit**
- **Use g 's, p 's and carry in to generate all C 's**
- **Also use them to generate block G and P**
- **CLA principle can be used recursively**

Use principle to build bigger adders

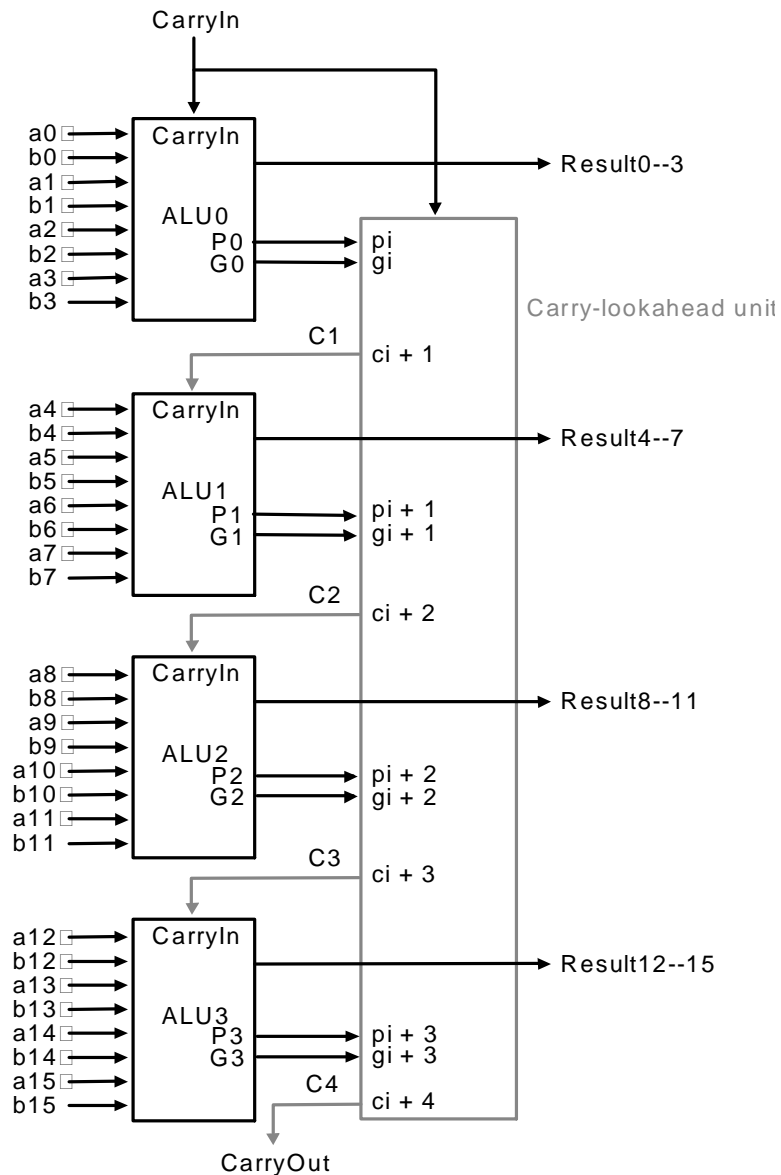

- A 16 bit adder uses four 4-bit adders
- It takes block g and p terms and cin to generate block carry bits out
- Block carries are used to generate bit carries
 - could use ripple carry of 4-bit CLA adders
 - Better: use the CLA principle again!

Delays in carry look-ahead adders

- **4-Bit case**
 - Generation of g and p: 1 gate delay
 - Generation of carries (and G and P): 2 more gate delay
 - Generation of sum: 1 more gate delay
- **16-Bit case**
 - Generation of g and p: 1 gate delay
 - Generation of block G and P: 2 more gate delay
 - Generation of block carries: 2 more gate delay
 - Generation of bit carries: 2 more gate delay
 - Generation of sum: 1 more gate delay
- **64-Bit case**
 - 12 gate delays

Multiplication

- **More complicated than addition**
 - accomplished via shifting and addition
- **More time and more area**
- **Let's look at 3 versions based on grade school algorithm**

```
      01010010 (multiplicand)
 x01101101 (multiplier)
```



- **Negative numbers: convert and multiply**
- **Use other better techniques like Booth's encoding**

Multiplication

01010010 (multiplicand)	
<u>x01101101 (multiplier)</u>	
00000000	
01010010	x1
01010010	
00000000	x0
001010010	
0101001000	x1
0110011010	
01010010000	x1
10000101010	
000000000000	x0
010000101010	
0101001000000	x1
0111001101010	
01010010000000	x1
10001011101010	
00000000000000	x0
0010001011101010	

01010010 (multiplicand)	
<u>x01101101 (multiplier)</u>	
00000000	
01010010	x1
01010010	
00000000	x0
001010010	
0101001000	x1
0110011010	
01010010000	x1
10000101010	
000000000000	x0
010000101010	
0101001000000	x1
0111001101010	
01010010000000	x1
10001011101010	
00000000000000	x0
0010001011101010	

Multiplication: Implementation

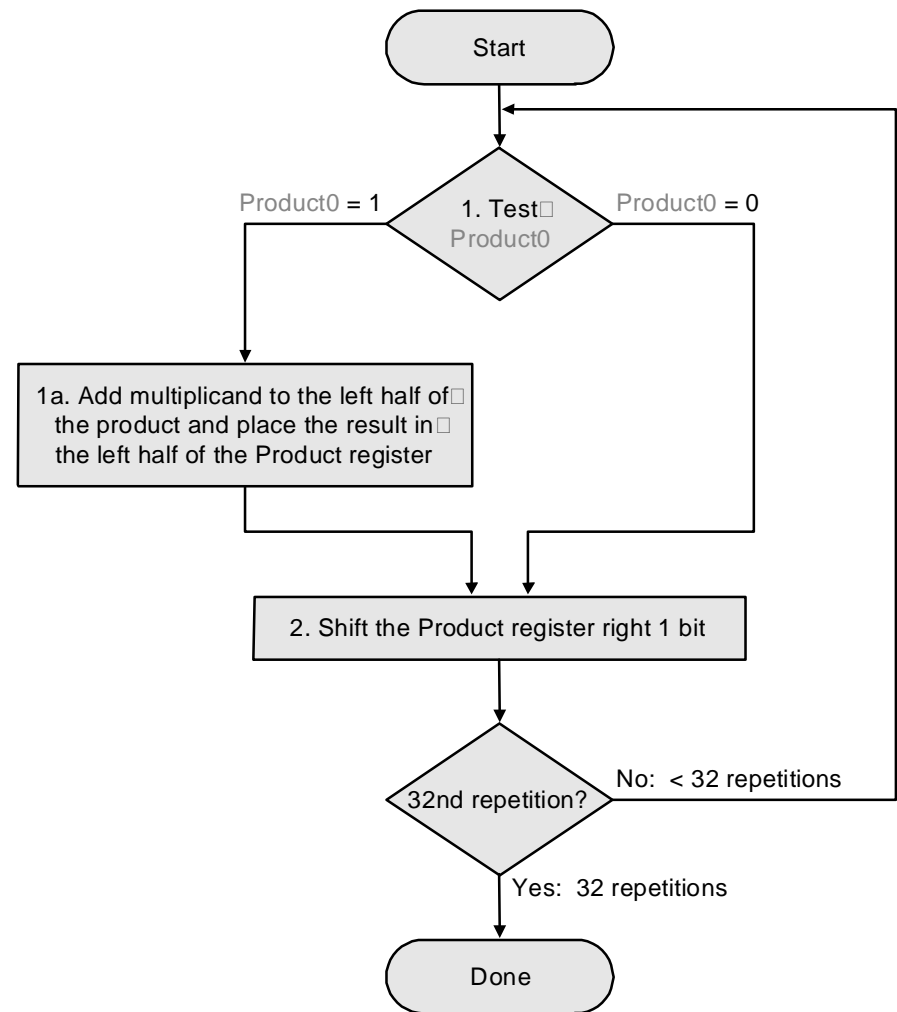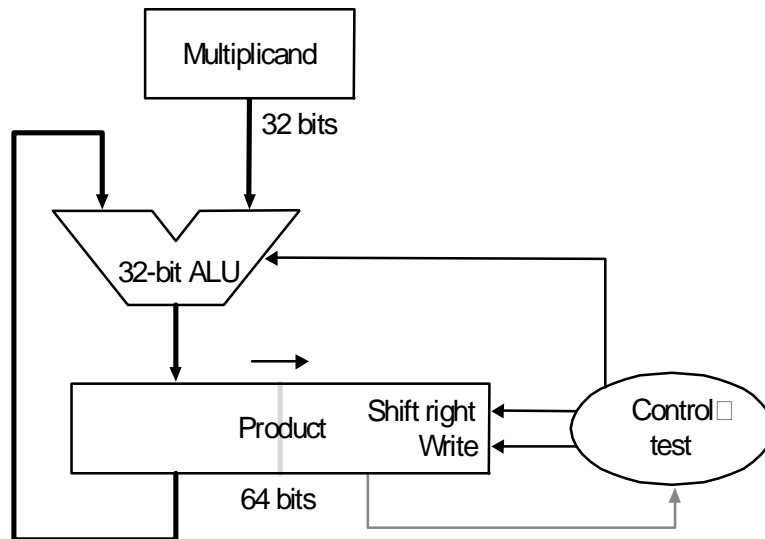

Multiplication Example

Iteration	multi- plicand	Original algorithm	
		Step	Product
0	0010	Initial values	0000 0110
1	0010	1:0 \Rightarrow no operation	0000 0110
	0010	2: Shift right Product	0000 0011
2	0010	1a:1 \Rightarrow prod = Prod + Mcand	0010 0011
	0010	2: Shift right Product	0001 0001
3	0010	1a:1 \Rightarrow prod = Prod + Mcand	0011 0001
	0010	2: Shift right Product	0001 1000
4	0010	1:0 \Rightarrow no operation	0001 1000
	0010	2: Shift right Product	0000 1100

Signed Multiplication

- Let Multiplier be $Q[n-1:0]$, multiplicand be $M[n-1:0]$
- Let $F = 0$ (shift flag)
- Let result $A[n-1:0] = 0\dots 00$
- For $n-1$ steps do
 - $A[n-1:0] = A[n-1:0] + M[n-1:0] \times Q[0]$ /* add partial product */
 - $F \leftarrow F \text{ .or. } (M[n-1] \text{ .and. } Q[0])$ /* determine shift bit */
 - Shift A and Q with F, i.e.,
 - $A[n-2:0] = A[n-1:1]$; $A[n-1]=F$; $Q[n-1]=A[0]$; $Q[n-2:0]=Q[n-1:1]$
- Do the correction step
 - $A[n-1:0] = A[n-1:0] - M[n-1:0] \times Q[0]$ /* subtract partial product */
 - Shift A and Q while retaining $A[n-1]$
 - This works in all cases excepts when both operands are $10..00$

Booth's Encoding

- Numbers can be represented using three symbols, 1, 0, and -1
- Let us consider -1 in 8 bits
 - One representation is 1 1 1 1 1 1 1 1
 - Another possible one 0 0 0 0 0 0 0 -1
- Another example +14
 - One representation is 0 0 0 0 1 1 1 0
 - Another possible one 0 0 0 1 0 0 -1 0
- We do not explicitly store the sequence
- Look for transition from previous bit to next bit
 - 0 to 0 is 0; 0 to 1 is -1; 1 to 1 is 0; and 1 to 0 is 1
- Multiplication by 1, 0, and -1 can be easily done
- Add all partial results to get the final answer

Using Booth's Encoding for Multiplication

- Convert a binary string in Booth's encoded string
- Multiply by two bits at a time
- For n bit by n-bit multiplication, n/2 partial product
- Partial products are signed and obtained by multiplying the multiplicand by 0, +1, -1, +2, and -2 (all achieved by shift)
- Add partial products to obtain the final result
- Example, multiply 0111 (+7) by 1010 (-6)
- Booths encoding of 1010 is -1 +1 -1 0
- With 2-bit groupings, multiplication needs to be carried by -1 and -2
-

$$\begin{array}{r} 1\ 1\ 1\ 1\ 0\ 0\ 1\ 0 \quad (\text{multiplication by } -2) \\ 1\ 1\ 1\ 0\ 0\ 1\ 0\ 0 \quad (\text{multiplication by } -1 \text{ and shift by 2 positions}) \end{array}$$


- Add the two partial products to get 11010110 (-42) as result

Booth's algorithm (Neg. multiplier)


Iteration	multiplier	Booth's algorithm	
		Step	Product
0	0010	Initial values	0000 1101 0
1	0010	1c: 10 \Rightarrow prod = Prod - Mcand	1110 1101 0
	0010	2: Shift right Product	1111 0110 1
2	0010	1b: 01 \Rightarrow prod = Prod + Mcand	0001 0110 1
	0010	2: Shift right Product	0000 1011 0
3	0010	1c: 10 \Rightarrow prod = Prod - Mcand	1110 1011 0
	0010	2: Shift right Product	1111 0101 1
4	0010	1d: 11 \Rightarrow no operation	1111 0101 1
	0010	2: Shift right Product	1111 1010 1

Carry-Save Addition

 - Consider adding six set of numbers (4 bits each in the example)
- The numbers are 1001, 0110, 1111, 0111, 1010, 0110 (all positive)
- One way is to add them pair wise, getting three results, and then adding them again



 - Other method is add them three at a time by saving carry




Division

- **Even more complicated**
 - can be accomplished via shifting and addition/subtraction
- **More time and more area**
- **We will look at 3 versions based on grade school algorithm**

$$\begin{array}{r|l} 0011 & 0010 \ 0010 \text{ (Dividend)} \end{array}$$

- **Negative numbers: Even more difficult**
- **There are better techniques, we won't look at them**

Division

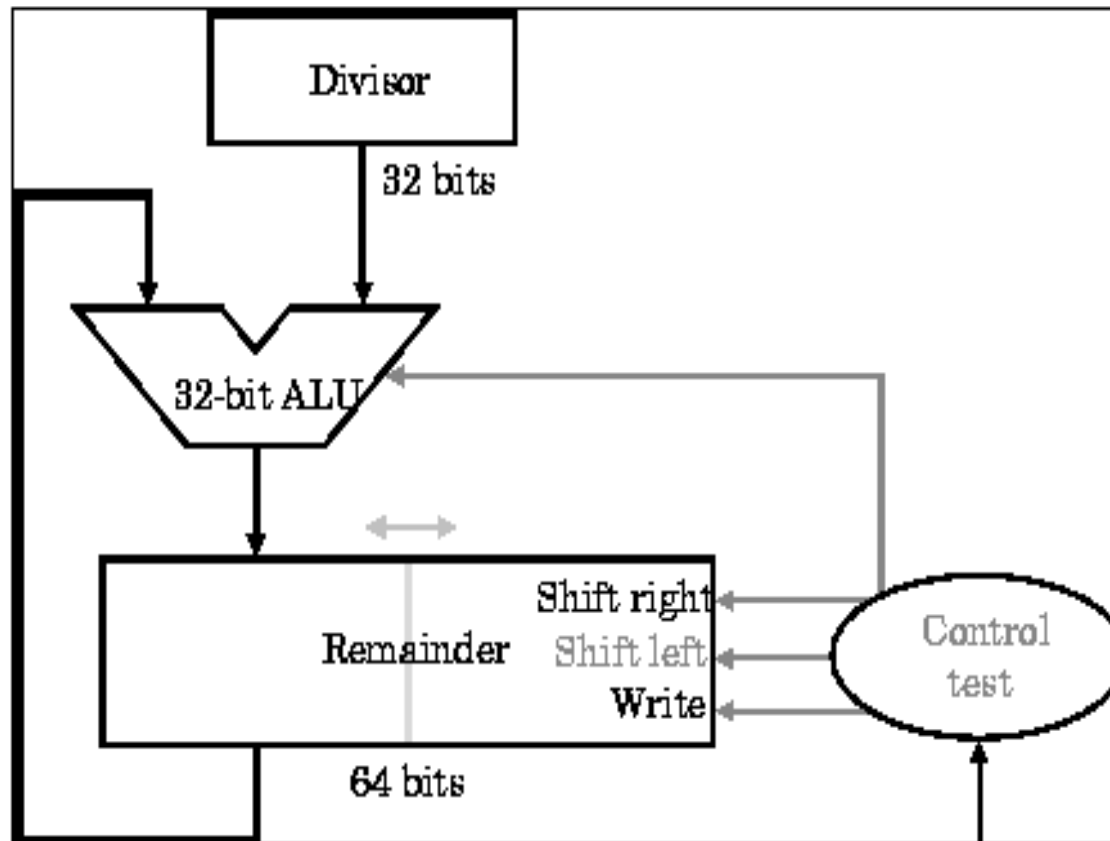

Restoring Division

Iteration	Divisor	Divide algorithm	
		Step	Remainder
0	0010	Initial values	0000 0111
	0010	Shift Rem left 1	0000 1110
1	0010	2: Rem = Rem - Div	1110 1110
	0010	3b: Rem < 0 \Rightarrow + Div, sll R, R0 = 0	0001 1100
2	0010	2: Rem = Rem - Div	1111 1100
	0010	3b: Rem < 0 \Rightarrow + Div, sll R, R0 = 0	0011 1000
3	0010	2: Rem = Rem - Div	0001 1000
	0010	3a: Rem \geq 0 \Rightarrow sll R, R0 = 1	0011 0001
4	0010	2: Rem = Rem - Div	0001 0001
	0010	3a: Rem \geq 0 \Rightarrow sll R, R0 = 1	0010 0011
Done	0010	shift left half of Rem right 1	0001 0011

Non-Restoring Division

Iteration	Divisor	Divide algorithm	
		Step	Remainder
0	0010	Initial values	0000 1110
1	0010	1: Rem = Rem - Div	1110 1110
	0010	2b: Rem < 0 \Rightarrow sll R, R0 = 0	1101 1100
	0010	3b: Rem = Rem + Div	1111 1100
2	0010	2b: Rem < 0 \Rightarrow sll R, R0 = 0	1111 1000
	0010	3b: Rem = Rem + Div	0001 1000
3	0010	2a: Rem > 0 \Rightarrow sll R, R0 = 1	0011 0001
	0010	3a: Rem = Rem - Div	0001 0001
4	0010	2a: Rem > 0 \Rightarrow sll R, R0 = 1	0010 0011
Done	0010	shift left half of Rem right 1	0001 0011