

CPRE 488

Embedded System Design

(VHDL Overview)

Instructor: Dr. Phillip Jones
(phjones@iastate.edu)

Reconfigurable Computing Laboratory
Iowa State University
Ames, Iowa, USA

<http://class.ece.iastate.edu/cpre488/>

VHDL basics

- VHDL: (V)HSIC (H)ardware (D)escription (L)anguage
 - VHSIC: (V)ery (H)igh (S)peed (I)ntegrated (C)ircuit

VHDL basics

- VHDL: (V)HSIC (H)ardware (D)escription (L)anguage
 - VHSIC: (V)ery (H)igh (S)peed (I)ntegrated (C)ircuit

- Golden Rules of Hardware Design (VHDL or Verilog)

1. VHDL is a Hardware Description Language (HDL)

- VHDL is NOT a programming language
- VHDL is conceptually VERY different than C/C++!

2. Draw your Hardware Circuit before writing ANY VHDL

- Easier for you, and others to check for bugs at the circuit diagram.
- A drawing gives a base from which you and other can check if the VHDL is reflecting the architecture envisioned.
- The tools are not magic! If you cannot sketch your circuit using basic building blocks (e.g., MUXs, counters, state diagrams, etc.), then it is not reasonable to expect the tools to figure it out. Having no sketch is just asking for weird hardware behaviors to occur.

VHDL basics

- VHDL: (V)HSIC (H)ardware (D)escription (L)anguage
 - VHSIC: (V)ery (H)igh (S)peed (I)ntegrated (C)ircuit
- Golden Rules of Hardware Design (VHDL or Verilog)
 1. VHDL is a Hardware **Description** Language (HDL)
 - VHDL is NOT a programming language
 - VHDL is conceptually **VERY** different than C/C++!
 2. Draw your Hardware Circuit before writing ANY VHDL
 - Easier for you, and others to check for bugs at the circuit diagram.
 - A drawing gives a base from which you and other can check if the VHDL is reflecting the architecture envisioned.
 - The tools are not magic! If you cannot sketch your circuit using basic building blocks (e.g., MUXs, counters, state diagrams, etc.), then it is not reasonable to expect the tools to figure it out. Having no sketch is just asking for weird hardware behaviors to occur.

VHDL basics

- VHDL: (V)HSIC (H)ardware (D)escription (L)anguage
 - VHSIC: (V)ery (H)igh (S)peed (I)ntegrated (C)ircuit
- Golden Rules of Hardware Design (VHDL or Verilog)
 1. VHDL is a Hardware **Description** Language (HDL)
 - VHDL is NOT a programming language
 - VHDL is conceptually VERY different than C/C++!
 2. Draw your Hardware Circuit before writing ANY VHDL
 - Easier for you, and others to check for bugs at the circuit diagram.
 - A drawing gives a base from which you and other can check if the VHDL is reflecting the architecture envisioned.
 - The tools are not magic! If you cannot sketch your circuit using basic building blocks (e.g., MUXs, counters, state diagrams, etc.), then it is not reasonable to expect the tools to figure it out. Having no sketch is just asking for weird hardware behaviors to occur.

VHDL basics

- VHDL: (V)HSIC (H)ardware (D)escription (L)anguage
 - VHSIC: (V)ery (H)igh (S)peed (I)ntegrated (C)ircuit
- Golden Rules of Hardware Design (VHDL or Verilog)
 1. VHDL is a Hardware **Description** Language (HDL)
 - VHDL is NOT a programming language
 - VHDL is conceptually **VERY** different than C/C++!
 2. Draw your Hardware Circuit before writing ANY VHDL
 - Easier for you, and others to check for bugs at the circuit diagram.
 - A drawing gives a base from which you and other can check if the VHDL is reflecting the architecture envisioned.
 - The tools are not magic! If you cannot sketch your circuit using basic building blocks (e.g., MUXs, counters, state diagrams, etc.), then it is not reasonable to expect the tools to figure it out. Having no sketch is just asking for weird hardware behaviors to occur.

Some Key Differences from C

- C is inherently sequential (serial), one statement executed at a time
- VHDL is inherently concurrent (parallel), many statements “execute” at a time

Some Key Differences from C

C example

Initially: A,B,C,D,Ans =1

$$C = A + D$$

$$D = A + B$$

$$Ans = C + D$$

VHDL example

$$C = A + D$$

$$D = A + B$$

$$Ans = C + D$$

Current Values:

$$A = 1$$

$$B = 1$$

$$C = 1$$

$$D = 1$$

$$Ans = 1$$

Some Key Differences from C

C example

Initially: A,B,C,D,Ans =1

$$C = A + D$$

$$D = A + B$$

$$Ans = C + D$$

VHDL example

$$C = A + D$$

$$D = A + B$$

$$Ans = C + D$$

Current Values:

$$A = 1$$

$$B = 1$$

$$C = 1$$

$$D = 1$$

$$Ans = 1$$

Some Key Differences from C

C example

Initially: A,B,C,D,Ans =1

→ $C = A + D$

$D = A + B$

$Ans = C + D$

VHDL example

$C = A + D$

$D = A + B$

$Ans = C + D$

Current Values:

$A = 1$

$B = 1$

$C = 2$

$D = 1$

$Ans = 1$

Some Key Differences from C

C example

Initially: A,B,C,D,Ans =1

$$C = A + D$$

→ $D = A + B$

$$\text{Ans} = C + D$$

VHDL example

$$C = A + D$$

$$D = A + B$$

$$\text{Ans} = C + D$$

Current Values:

$$A = 1$$

$$B = 1$$

$$C = 2$$

$$D = 2$$

$$\text{Ans} = 1$$

Some Key Differences from C

C example

Initially: A,B,C,D,Ans =1

$$C = A + D$$

$$D = A + B$$

→ Ans = C + D

VHDL example

$$C = A + D$$

$$D = A + B$$

$$\text{Ans} = C + D$$

Current Values:

$$A = 1$$

$$B = 1$$

$$C = 2$$

$$D = 2$$

$$\text{Ans} = 4$$

Some Key Differences from C

C example

Initially: A,B,C,D,Ans =1

$$C = A + D$$

$$D = A + B$$

$$Ans = C + D$$

VHDL example

$$C = A + D$$

$$D = A + B$$

$$Ans = C + D$$

Current Values:

$$A = 1$$

$$B = 1$$

$$C = 2$$

$$D = 2$$

$$Ans = 4$$

Some Key Differences from C

C example

Initially: A,B,C,D,Ans =1

$$C = A + D$$

$$D = A + B$$

$$\text{Ans} = C + D$$

Each statement
is a circuit

VHDL example

$$C = A + D$$

$$D = A + B$$

$$\text{Ans} = C + D$$



Current Values:

$$A = 1$$

$$B = 1$$

$$C = 2$$

$$D = 2$$

$$\text{Ans} = 4$$

Some Key Differences from C

C example

Initially: A,B,C,D,Ans = 1

$$C = A + D$$

$$D = A + B$$

$$\text{Ans} = C + D$$

Each statement
is a circuit

Current Values:

$$A = 1$$

$$B = 1$$


$$C = 2$$

$$D = 2$$

$$\text{Ans} = 4$$

VHDL example
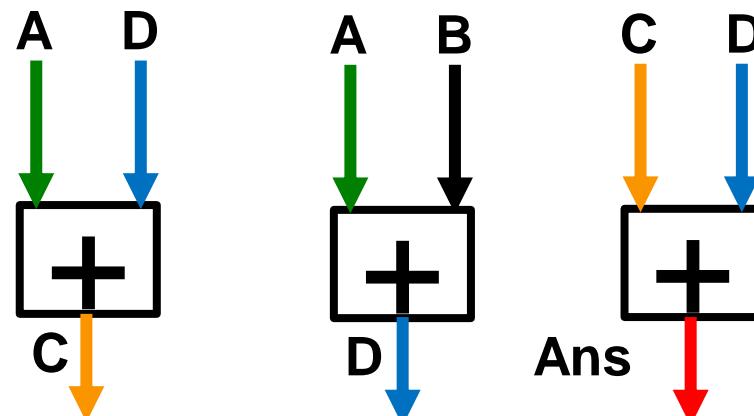
$$\begin{aligned}C &= A + D \\D &= A + B \\ \text{Ans} &= C + D\end{aligned}$$



Some Key Differences from C

C example

Initially: A,B,C,D,Ans = 1

$$C = A + D$$

$$D = A + B$$

$$\text{Ans} = C + D$$

Each statement
is a circuit

VHDL example

$$C = A + D$$

$$D = A + B$$

$$\text{Ans} = C + D$$

Current Values:


$$A = 1$$

$$B = 1$$

$$C = 2$$

$$D = 2$$

$$\text{Ans} = 4$$

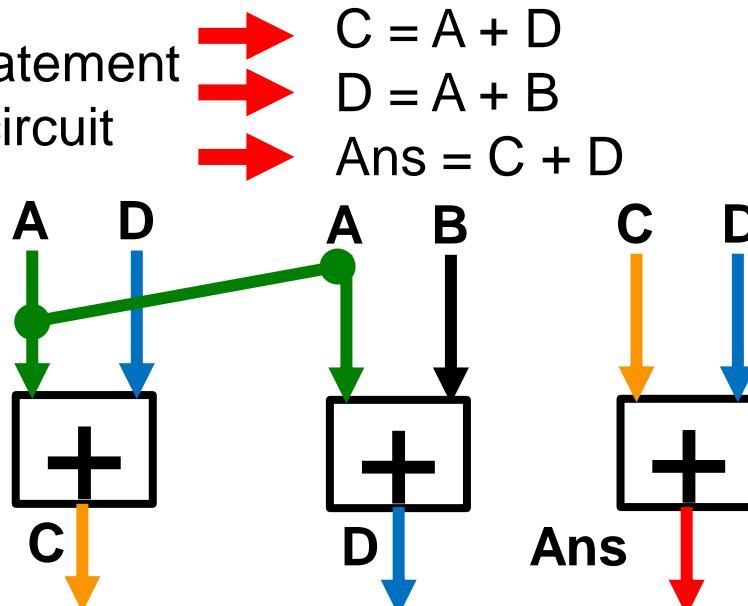

Some Key Differences from C

C example

Initially: A,B,C,D,Ans = 1

$$C = A + D$$

$$D = A + B$$

$$\text{Ans} = C + D$$

Each statement
is a circuit

VHDL example

$$C = A + D$$

$$D = A + B$$

$$\text{Ans} = C + D$$

Current Values:


$$A = 1$$

$$B = 1$$

$$C = 2$$

$$D = 2$$

$$\text{Ans} = 4$$

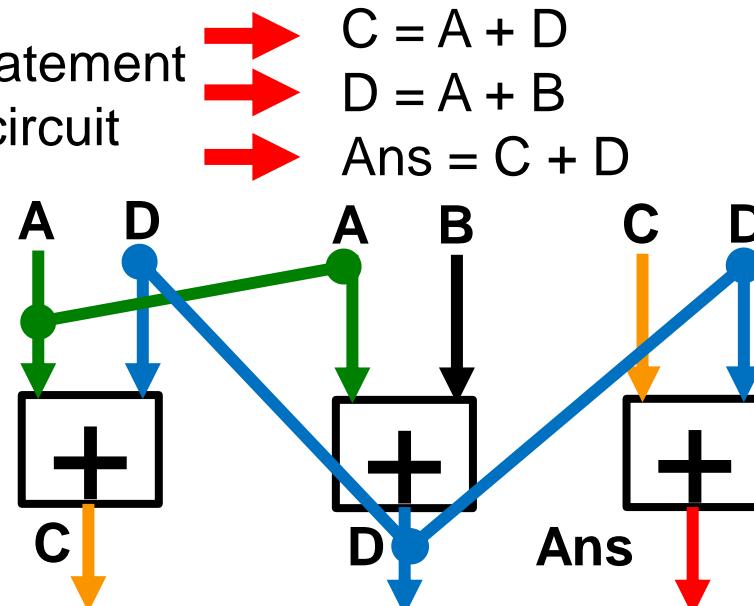

Some Key Differences from C

C example

Initially: A,B,C,D,Ans = 1

$$C = A + D$$

$$D = A + B$$

$$\text{Ans} = C + D$$

Current Values:

$$A = 1$$

$$B = 1$$

$$C = 2$$


$$D = 2$$

$$\text{Ans} = 4$$

VHDL example

Each statement
is a circuit
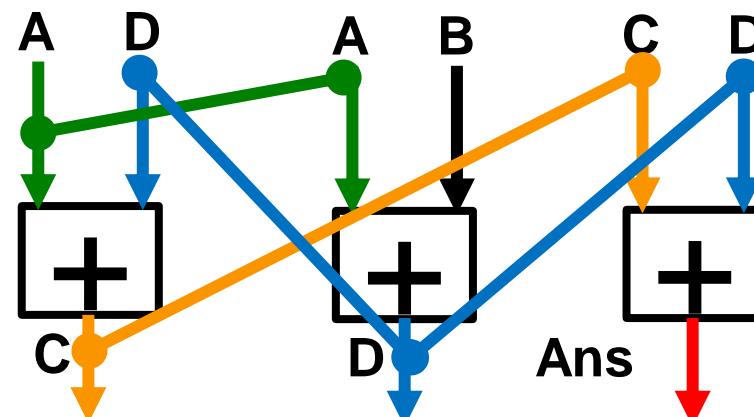
$$\begin{aligned} C &= A + D \\ D &= A + B \\ \text{Ans} &= C + D \end{aligned}$$



Some Key Differences from C

C example

Initially: A,B,C,D,Ans = 1

$$\begin{aligned}C &= A + D \\D &= A + B \\Ans &= C + D\end{aligned}$$


Current Values:

$$\begin{aligned}A &= 1 \\B &= 1 \\C &= 2 \\D &= 2 \\Ans &= 4\end{aligned}$$

VHDL example

Each statement
is a circuit
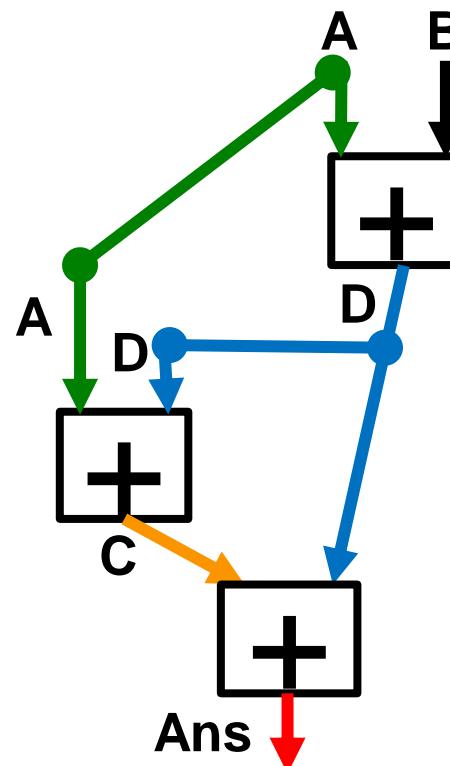
$$\begin{aligned}\rightarrow & C = A + D \\ \rightarrow & D = A + B \\ \rightarrow & Ans = C + D\end{aligned}$$



Some Key Differences from C

C example

Initially: A,B,C,D,Ans = 1

$$\begin{aligned}C &= A + D \\D &= A + B \\Ans &= C + D\end{aligned}$$


Current Values:

$$\begin{aligned}A &= 1 \\B &= 1 \\C &= 2 \\D &= 2 \\Ans &= 4\end{aligned}$$

VHDL example

Each statement
is a circuit
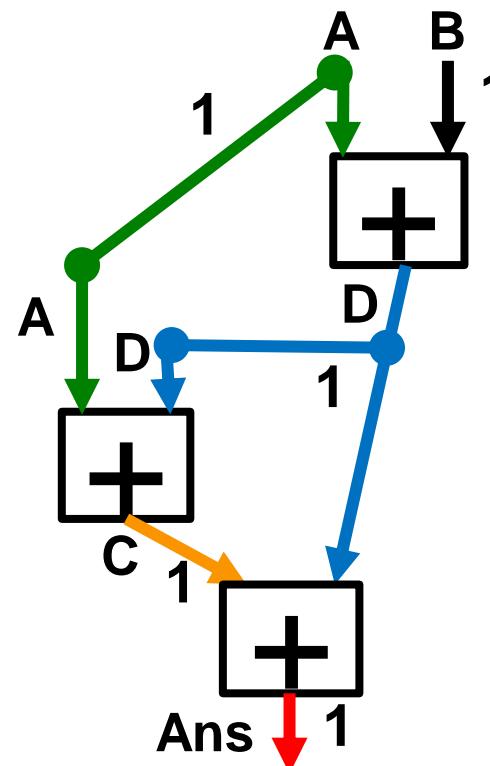
$$\begin{aligned}\rightarrow & C = A + D \\ \rightarrow & D = A + B \\ \rightarrow & Ans = C + D\end{aligned}$$



Some Key Differences from C

C example

Initially: A,B,C,D,Ans = 1

$$C = A + D$$

$$D = A + B$$

$$\text{Ans} = C + D$$

Each statement
is a circuit

VHDL example

$$C = A + D$$

$$D = A + B$$

$$\text{Ans} = C + D$$

Current Values:


$$A = 1$$

$$B = 1$$

$$C = 2$$

$$D = 2$$

$$\text{Ans} = 4$$

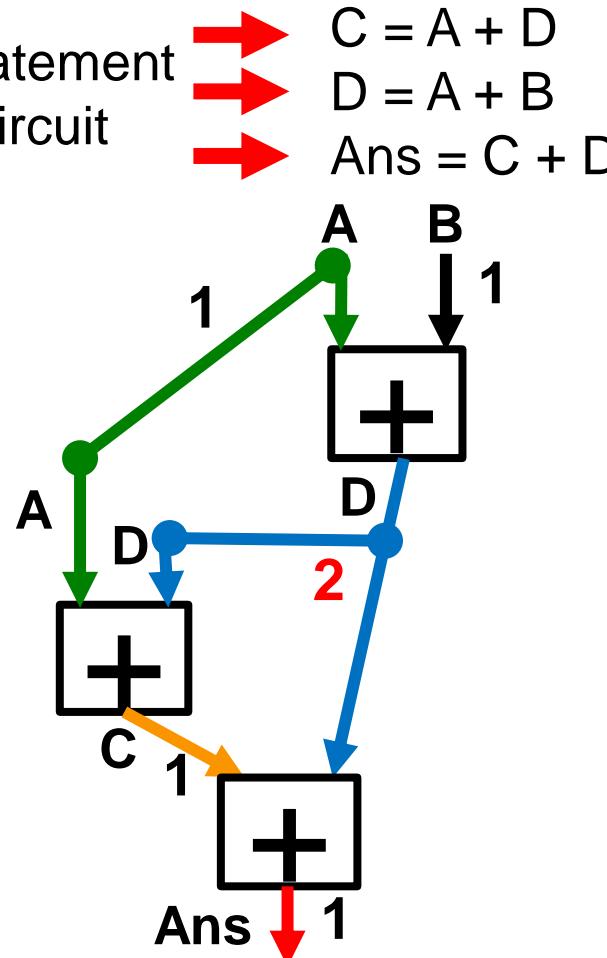

Some Key Differences from C

C example

Initially: A,B,C,D,Ans = 1

$$\begin{aligned}C &= A + D \\D &= A + B \\Ans &= C + D\end{aligned}$$


Current Values:

$$\begin{aligned}A &= 1 \\B &= 1 \\C &= 2 \\D &= 2 \\Ans &= 4\end{aligned}$$

VHDL example

Each statement
is a circuit
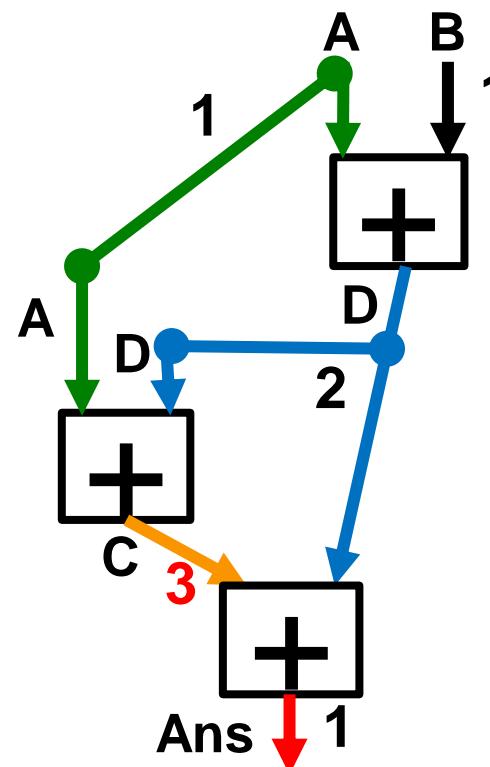
$$\begin{aligned}C &= A + D \\D &= A + B \\Ans &= C + D\end{aligned}$$



Some Key Differences from C

C example

Initially: A,B,C,D,Ans = 1

$$\begin{aligned}C &= A + D \\D &= A + B \\Ans &= C + D\end{aligned}$$


Current Values:

$$\begin{aligned}A &= 1 \\B &= 1 \\C &= 2 \\D &= 2 \\Ans &= 4\end{aligned}$$

VHDL example

Each statement
is a circuit
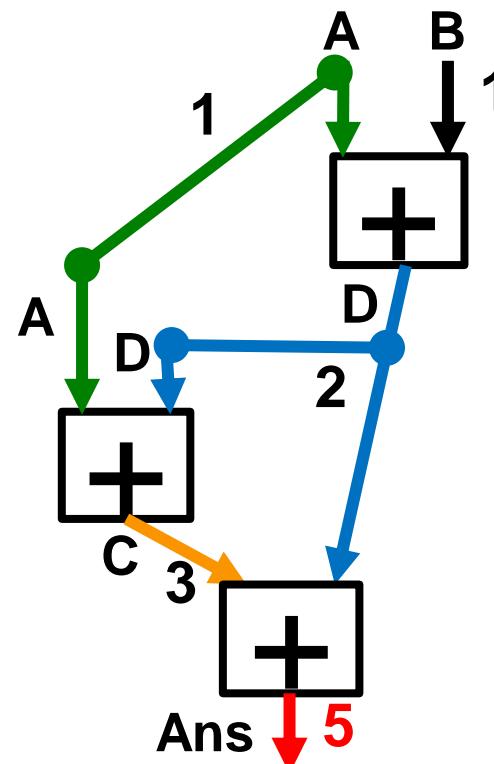
$$\begin{aligned}\rightarrow C &= A + D \\ \rightarrow D &= A + B \\ \rightarrow Ans &= C + D\end{aligned}$$



Typical Structure of a VHDL File

```
LIBRARY ieee;           ← Include Libraries

ENTITY test_circuit IS
    PORT(B,C,Y,Z,Ans);
END test_circuit;

ARCHITECTURE structure OF test_circuit IS
    signal A      : std_logic_vector(7 downto 0);
    signal X      : std_logic_vector(7 downto 0);

    BEGIN
        A <= B + C;
        X <= Y + Z;
        Ans <= A + X;
    END
}
```

Declare internal signals, components → {

Define component name and Input/output ports ← }

Implement components functionality ← }

Process

- Process provide a level serialization in VHDL (e.g. variables, clocked processes)
- Help separate and add structure to VHDL design

Process Example

BEGIN

```
My_process_1 : process (A,B,C,X,Y,Z)
```

```
Begin
```

```
    A <= B + C;
```

```
    X <= Y + Z;
```

```
    Ans <= A + X;
```

```
End My_process_1;
```

Sensitivity list: specify inputs to the process. Process is updated when a specified input changes

```
My_process_2 : process (B,X,Y,Ans1)
```

```
Begin
```

```
    A <= B + 1;
```

```
    X <= B + Y;
```

```
    Ans2 <= Ans1 + X;
```

```
End My_process_2;
```

END;

Process Example (Multiple Drivers)

BEGIN

```
My_process_1 : process (A,B,C,X,Y,Z)
```

```
Begin
```

```
  A <= B + C;
```

```
  X <= Y + Z;
```

```
  Ans <= A + X;
```

```
End My_process_1;
```

```
My_process_2 : process (B,X,Y,Ans1)
```

```
Begin
```


```
  A <= B + 1;
```

```
  X <= B + Y;
```

```
  Ans2 <= Ans1 + X;
```

```
End My_process_2;
```

END;

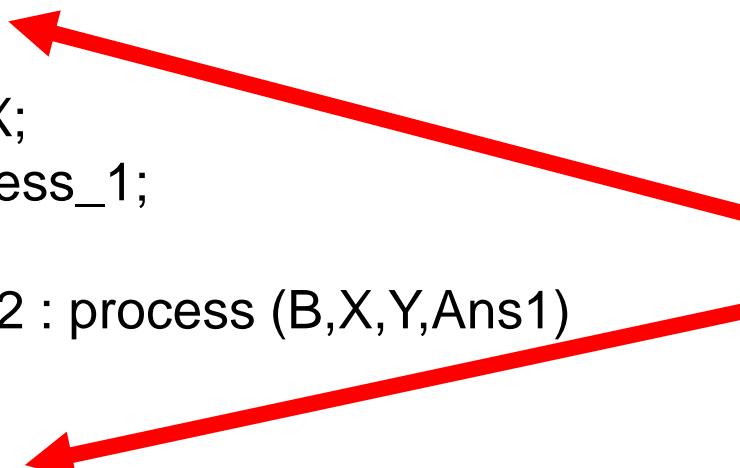

A signal can only be Driven (written) by one process. But can be read by many

Compile or simulator may give a “multiple driver” Error or Warning message

Process Example (Multiple Drivers)

BEGIN

```
My_process_1 : process (A,B,C,X,Y,Z)
```

```
Begin
```

```
    A <= B + C;
```

```
    X <= Y + Z;
```

```
    Ans <= A + X;
```

```
End My_process_1;
```

```
My_process_2 : process (B,X,Y,Ans1)
```

```
Begin
```

```
    A1 <= B + 1;
```

```
    X1 <= B + Y;
```

```
    Ans2 <= Ans1 + X;
```

```
End My_process_2;
```

Maybe A,X were suppose to be A1,X1. Cut and paste error. Or may need to rethink Hardware structure to remove multiple driver issue.

END;

Process Example (if-statement)

BEGIN

```
My_process_1 : process (A,B,C,X,Y,Z)
Begin
```

```
if (B = 0) then
  C <= A + B;
  Z <= X + Y;
  Ans1 <= A + X;
else
  C <= 1;
  Z <= 0;
  Ans1 <= 1;
end if;
```

Draw circuit

```
End My_process_1;
END;
```

Process Example (if-statement)

BEGIN


My_process_1 : process (A,B,C,X,Y,Z)

Begin

```
if (B = 0) then
  C <= A + B;
  Z <= X + Y;
  Ans1 <= A + X;
else
  C <= 1;
  Z <= 0;
  Ans1 <= 1;
end if;
```

```
End My_process_1;
END;
```

Circuit for My_process_1

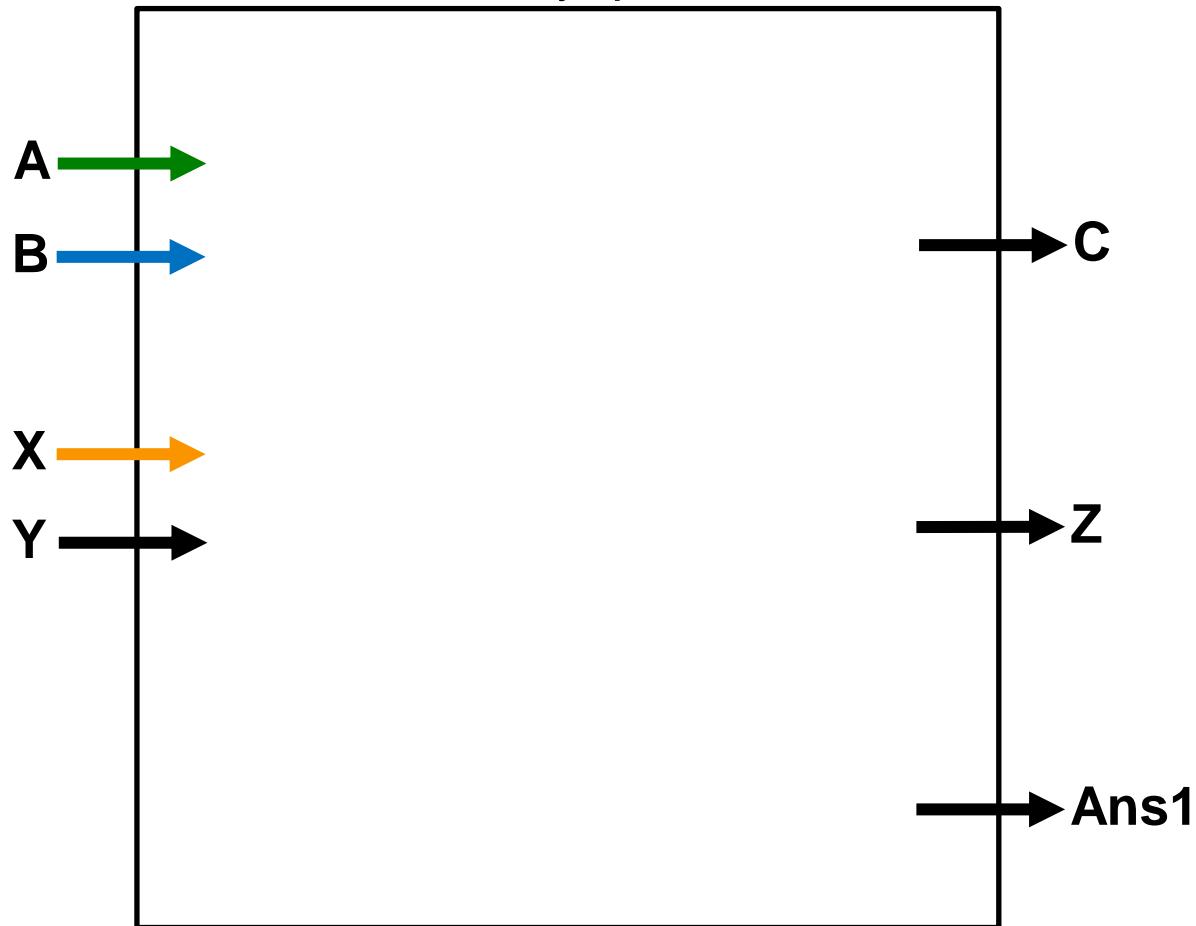

Process Example (if-statement)

BEGIN


My_process_1 : process (A,B,C,X,Y,Z)

Begin

```
if (B = 0) then
    C <= A + B;
    Z <= X + Y;
    Ans1 <= A + X;
else
    C <= 1;
    Z <= 0;
    Ans1 <= 1;
end if;
```

End My_process_1;
END;

Circuit for My_process_1

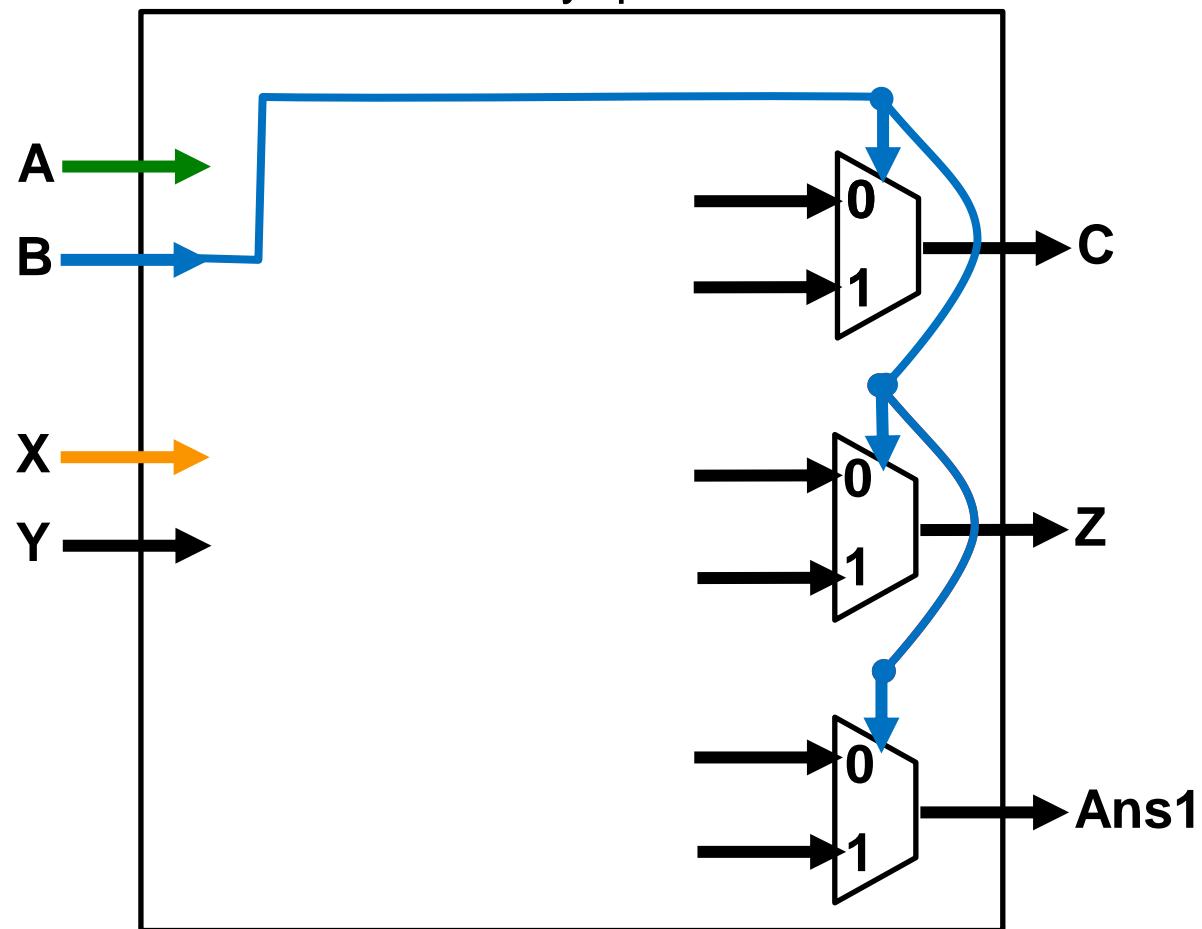

Process Example (if-statement)

BEGIN


My_process_1 : process (A,B,C,X,Y,Z)

Begin

```
if (B = 0) then
  C <= A + B;
  Z <= X + Y;
  Ans1 <= A + X;
else
  C <= 1;
  Z <= 0;
  Ans1 <= 1;
end if;
```

End My_process_1;
END;

Circuit for My_process_1

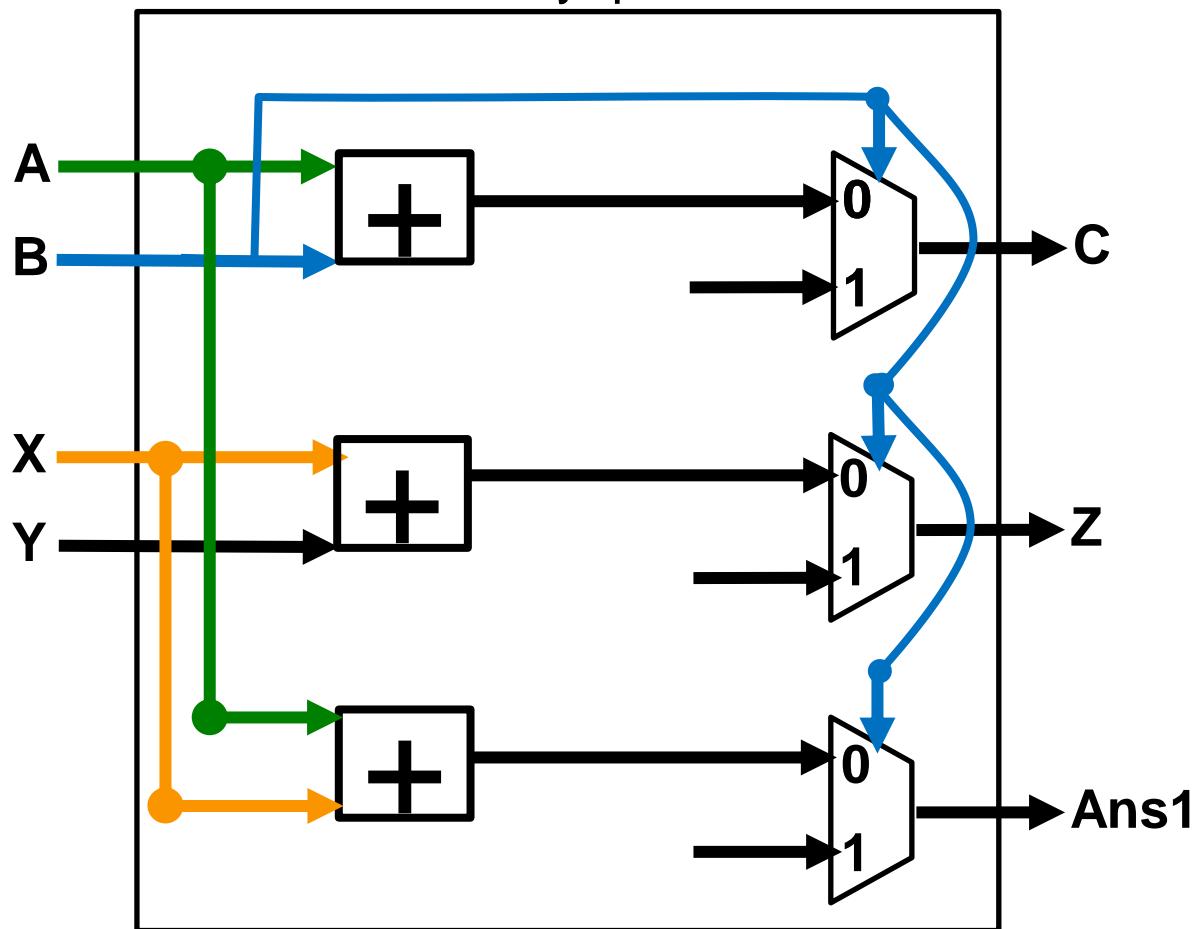

Process Example (if-statement)

BEGIN


My_process_1 : process (A,B,C,X,Y,Z)

Begin

```
if (B = 0) then
    C <= A + B;
    Z <= X + Y;
    Ans1 <= A + X;
else
    C <= 1;
    Z <= 0;
    Ans1 <= 1;
end if;
```

End My_process_1;
END;

Circuit for My_process_1

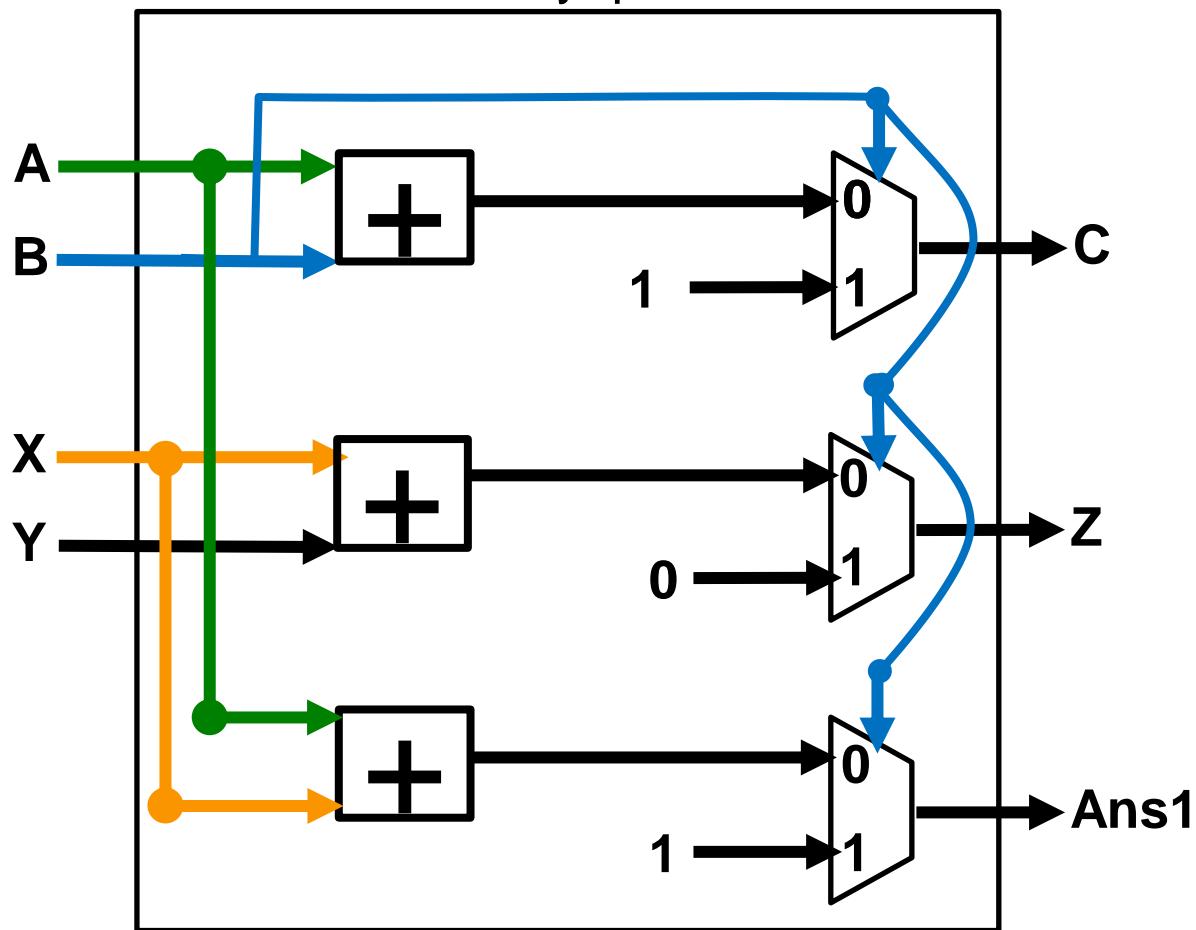

Process Example (if-statement)

BEGIN


My_process_1 : process (A,B,~~C~~,X,Y,~~Z~~)

Begin

```
if (B = 0) then
    C <= A + B;
    Z <= X + Y;
    Ans1 <= A + X;
else
    C <= 1;
    Z <= 0;
    Ans1 <= 1;
end if;
```

End My_process_1;
END;

Circuit for My_process_1

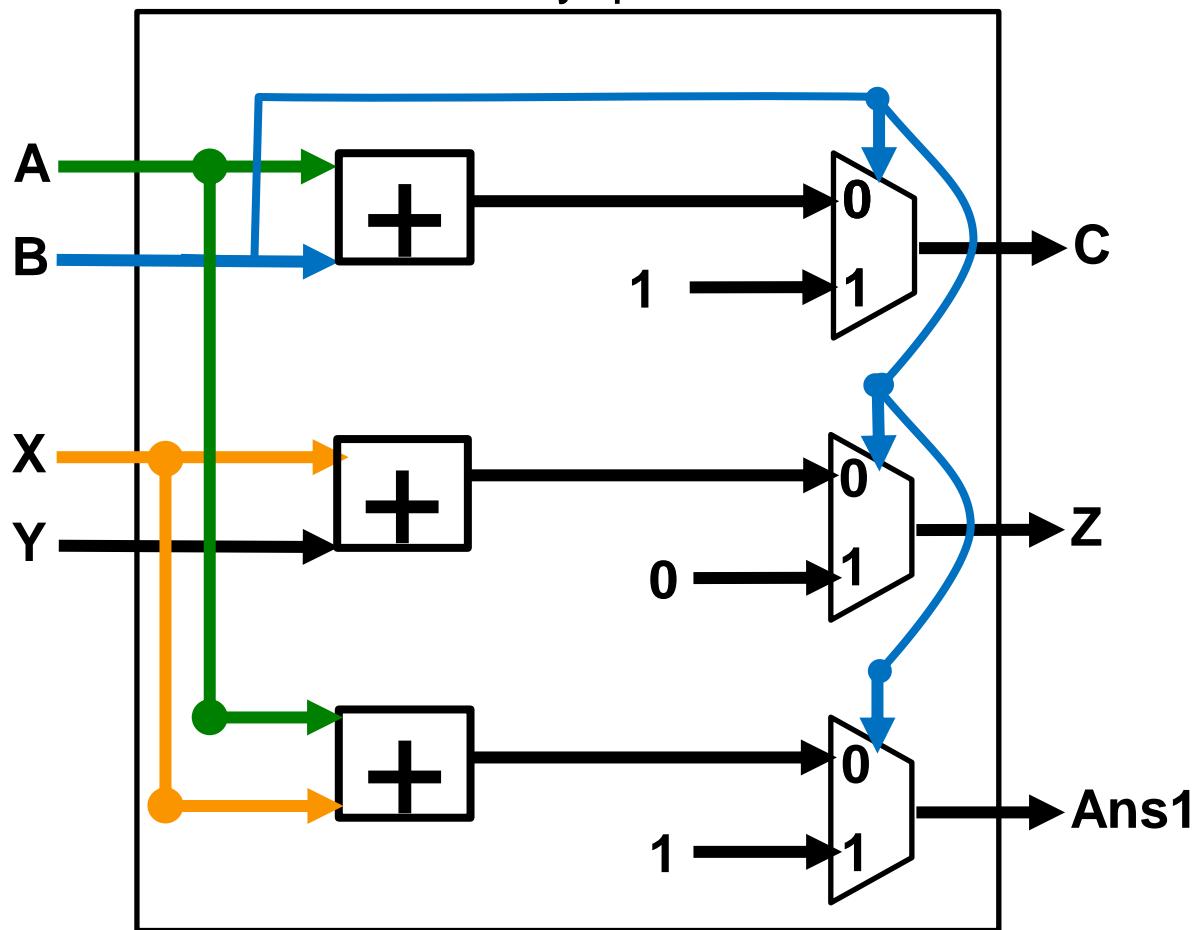

Process Example (if-statement)

BEGIN


My_process_1 : process (A,B,X,Y)

Begin

```
if (B = 0) then
    C <= A + B;
    Z <= X + Y;
    Ans1 <= A + X;
else
    C <= 1;
    Z <= 0;
    Ans1 <= 1;
end if;
```

```
End My_process_1;
END;
```

Circuit for My_process_1

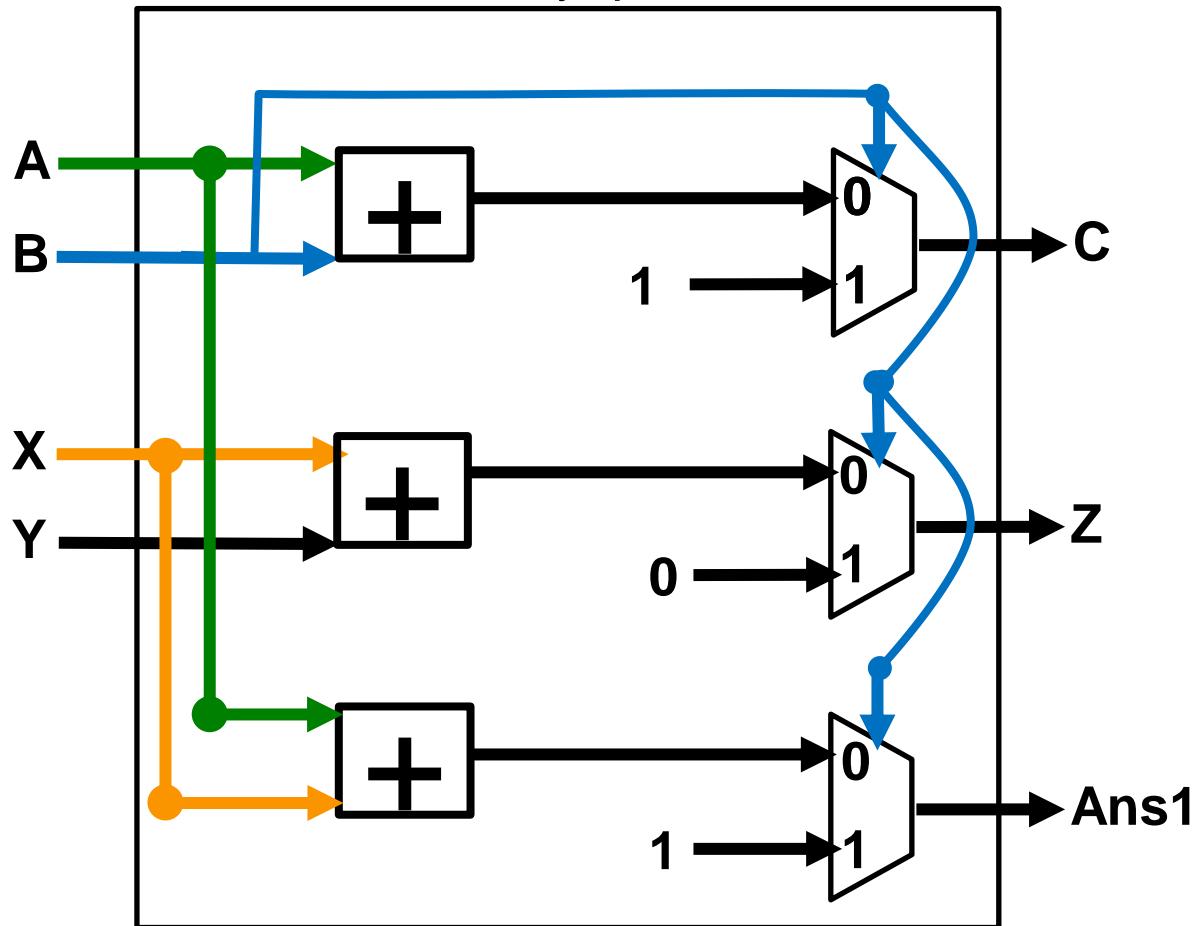

Process Example (if-statement)

BEGIN

My_process_1 : process (A,B,X,Y)

Begin


```
if (B = 0) then
    C <= A + B;
else
    C <= 1;
end if;

if (B = 0) then
    Z <= X + Y;
else
    Z <= 0;
end if;

if (B = 0) then
    Ans1 <= A + X;
else
    Ans1 <= 1;
end if;
```

End My_process_1;
END;

Circuit for My_process_1

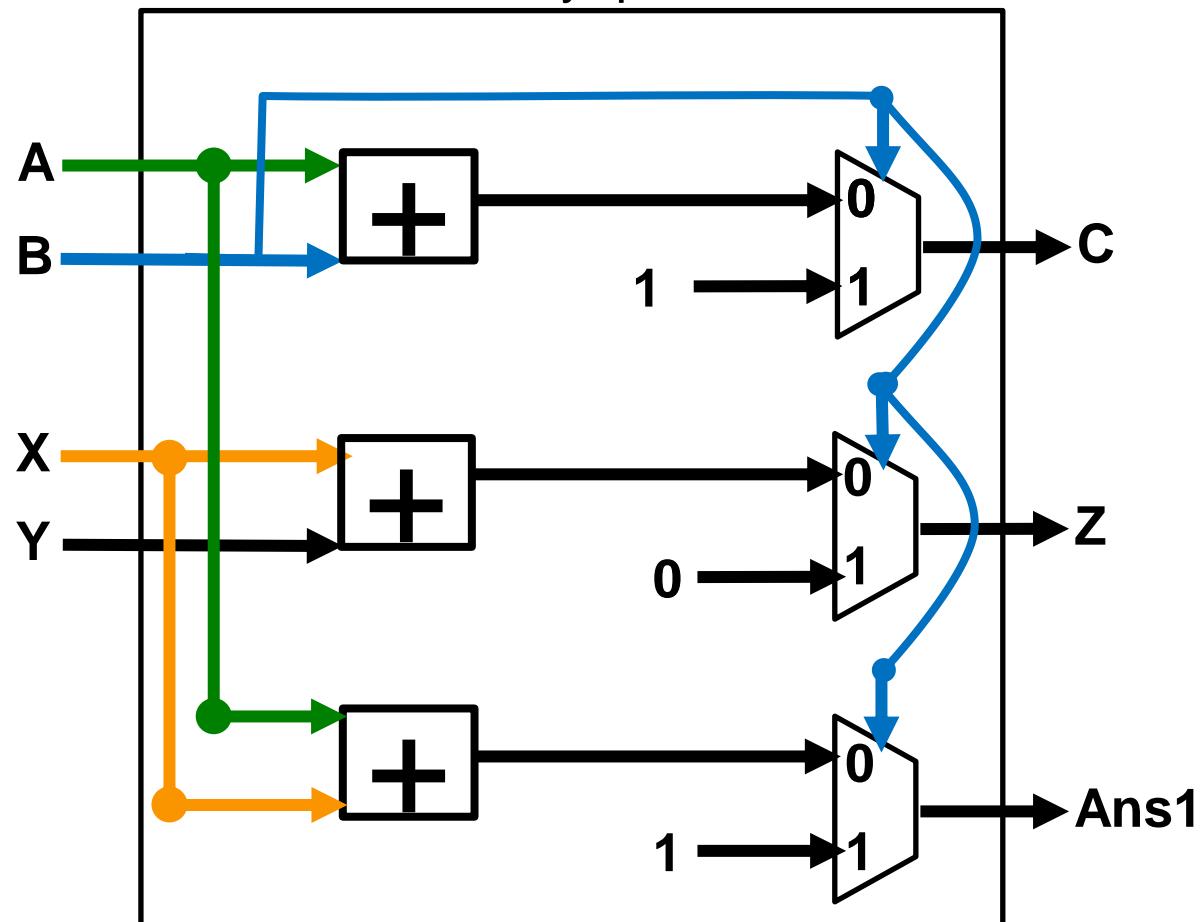


Clock Process Example

BEGIN

```
My_process_1 : process (clk)
Begin
  IF (clk'event and clk = '1') THEN
    C <= A or B;
    Z <= X or Y;
    Ans <= C and Z;
  END IF;
End My_process_1;
```

END;

circuit not clocked

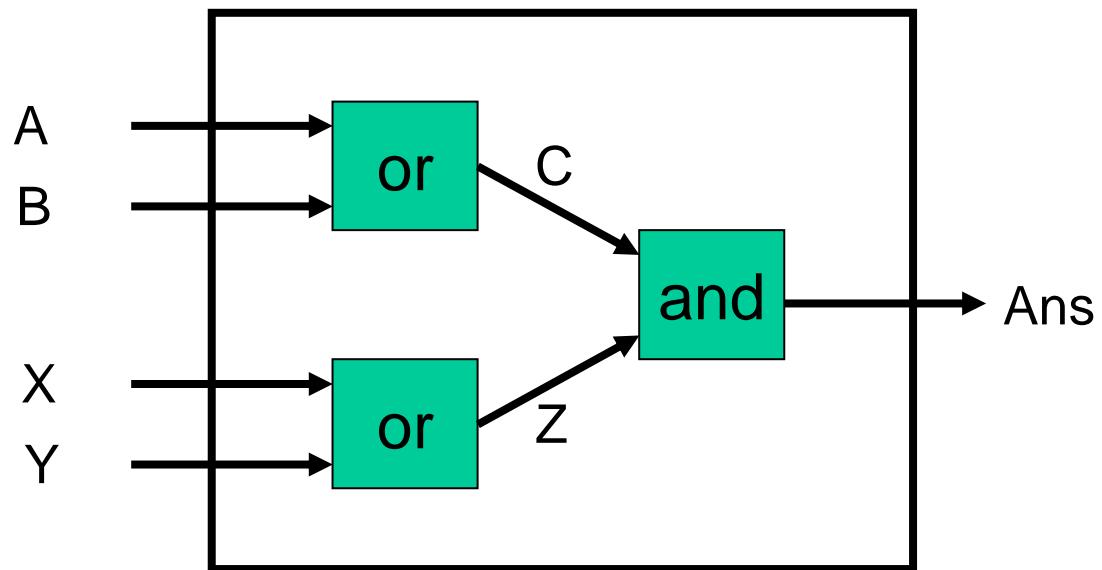

Clock Process Example


BEGIN

```
My_process_1 : process (clk)
Begin
  IF (clk'event and clk = '1') THEN
    C <= A or B;
    Z <= X or Y;
    Ans <= C and Z;
  END IF;
End My_process_1;
```

END;

D Flip-Flop
DFF
Register

circuit with clock

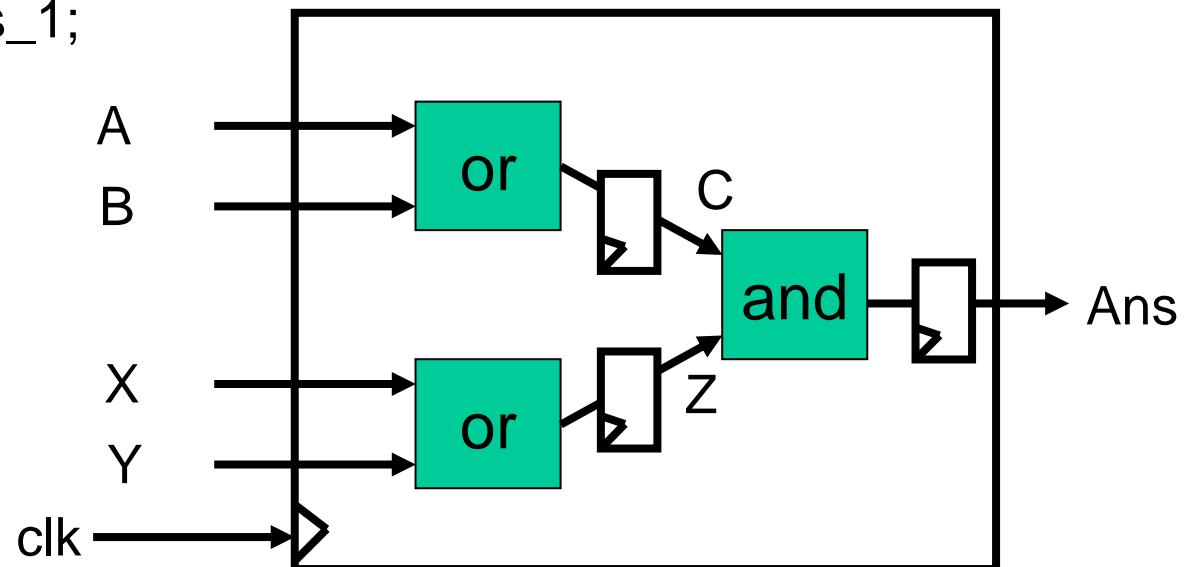

Clock Process Example

BEGIN

My_process_1 : process (clk)

Begin

IF (clk'event and clk = '1') THEN

C <= A or B;

Z <= X or Y;


Ans <= C and Z;

END IF;


End My_process_1;

END;

Current Simulation
Time: 7 us

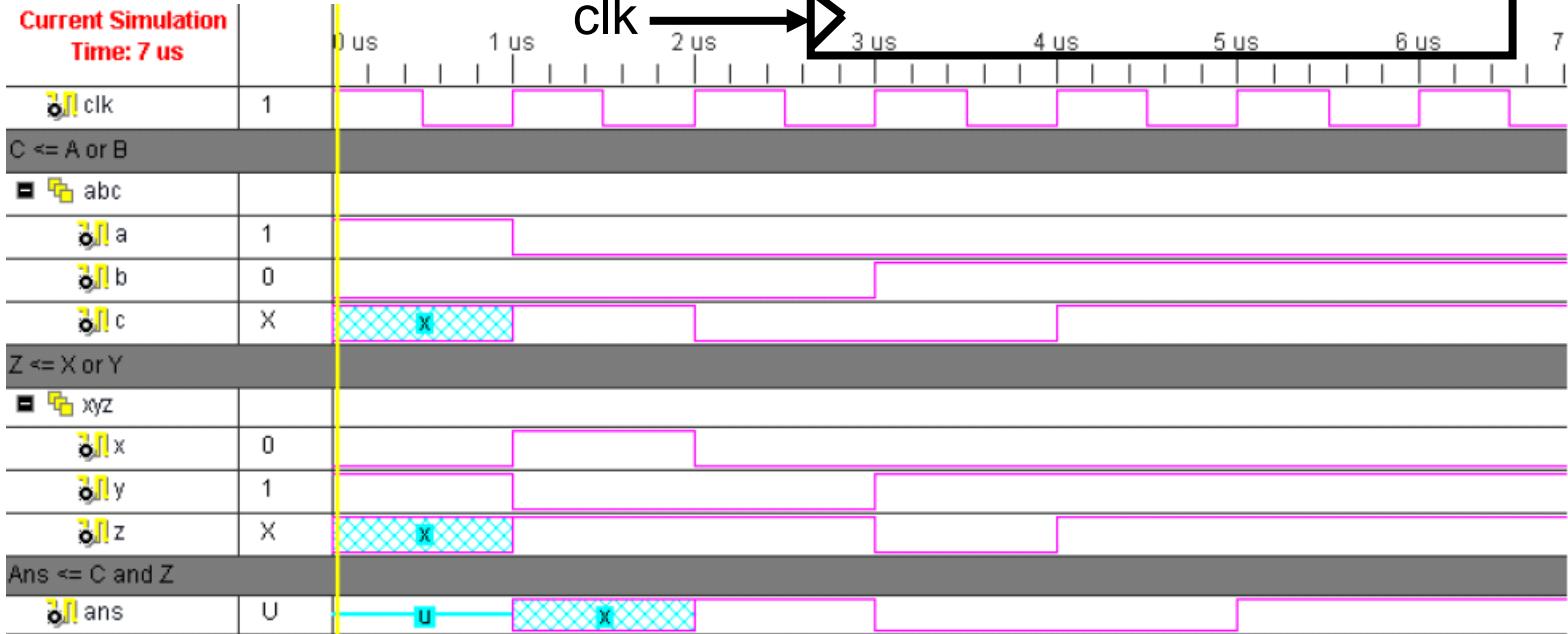

circuit with clock

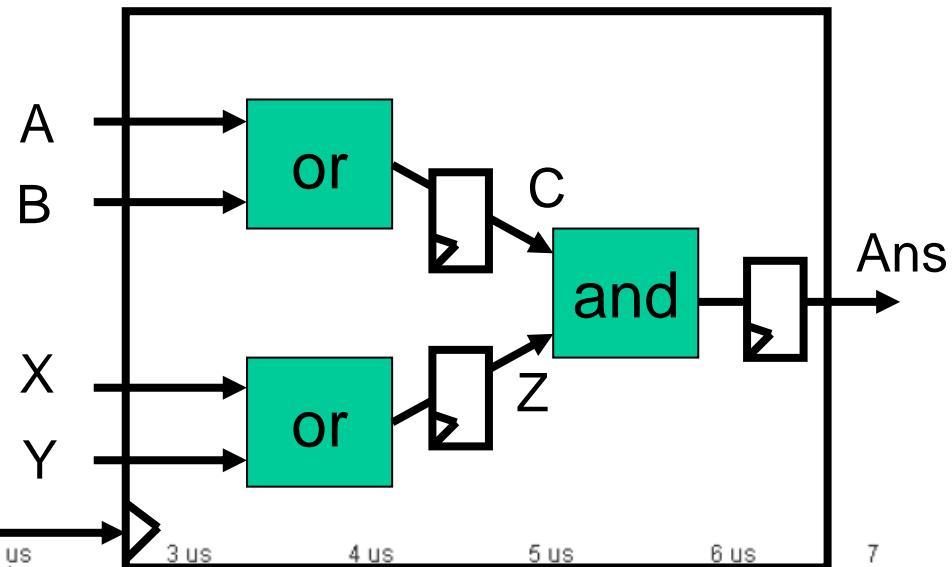

VHDL Constructs

- Entity
- Process
- Signal, Variable, Constants, Integers
- Array, Record

VHDL on-line tutorials:

http://www.seas.upenn.edu/~ese201/vhdl/vhdl_primer.html
<http://www.vhdl-online.de/tutorial/>

Signals and Variables

- Signals
 - Updated at the end of a process
 - Have file scope
- Variables
 - Updated instantaneously
 - Have process scope

VHDL on-line tutorials:

http://www.seas.upenn.edu/~ese201/vhdl/vhdl_primer.html
<http://www.vhdl-online.de/tutorial/>

std_logic, std_logic_vector

- Very common data types
- std_logic
 - Single bit value
 - Values: U, X, 0, 1, Z, W, H, L, -
 - Example: **signal A : std_logic;**
 - **A <= '1';**
- Std_logic_vector: is an array of std_logic
 - Example: **signal A : std_logic_vector (4 downto 0);**
 - **A <= "0Z001"**


VHDL on-line tutorials:

http://www.seas.upenn.edu/~ese201/vhdl/vhdl_primer.html
<http://www.vhdl-online.de/tutorial/>

Std_logic values

- Std_logic values

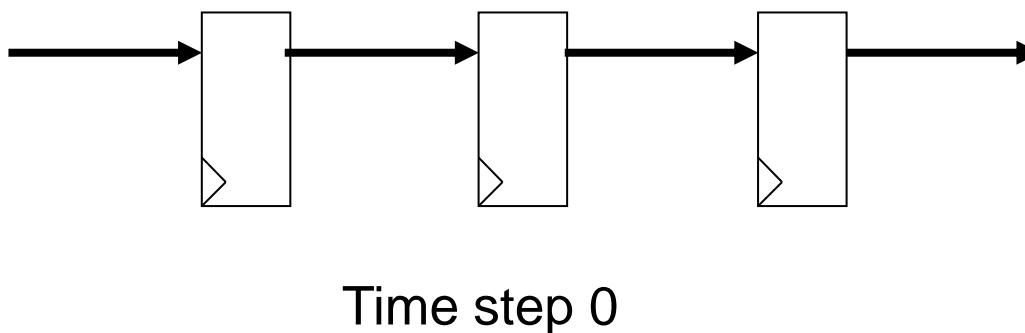
- U : Uninitialized (signal has not been assigned a value yet)
- X : Unknown (2 drivers one '0' one '1')
- H : weak '1' (example: model pull-up resister)
 - I have never used this value
- L : weak '0'



Std_logic values

- Std_logic values

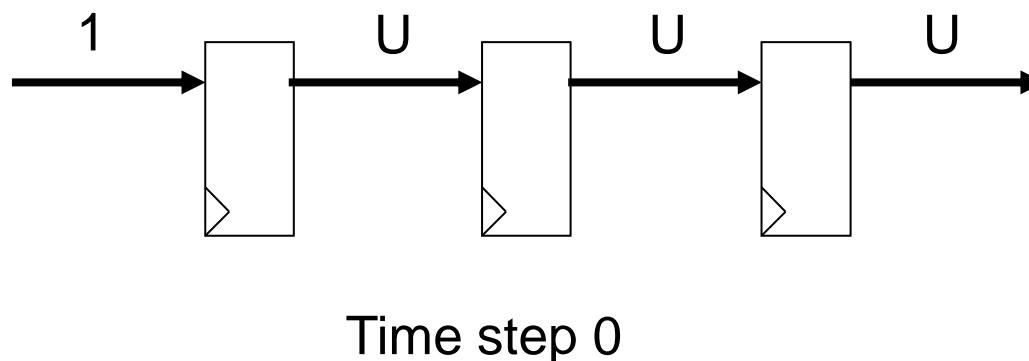
- U : Uninitialized (signal has not been assigned a value yet)
- X : Unknown (2 drivers one '0' one '1')
- H : weak '1' (example: model pull-up resistor)
 - I have never used this value
- L : weak '0'



Std_logic values

- Std_logic values

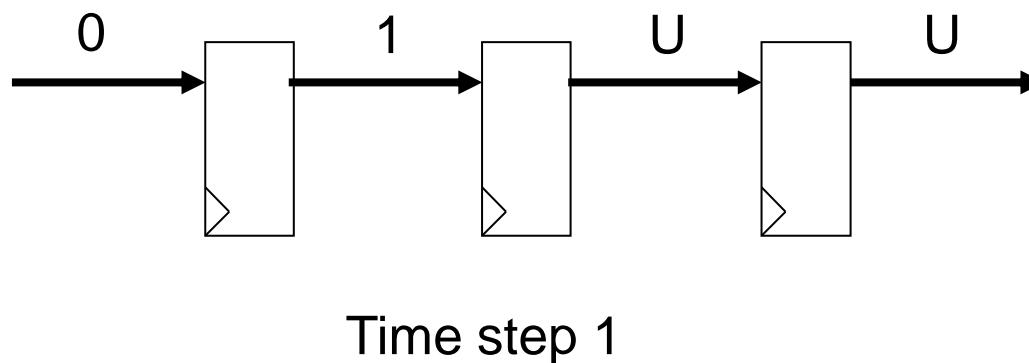
- U : Uninitialized (signal has not been assigned a value yet)
- X : Unknown (2 drivers one '0' one '1')
- H : weak '1' (example: model pull-up resistor)
 - I have never used this value
- L : weak '0'



Std_logic values

- Std_logic values

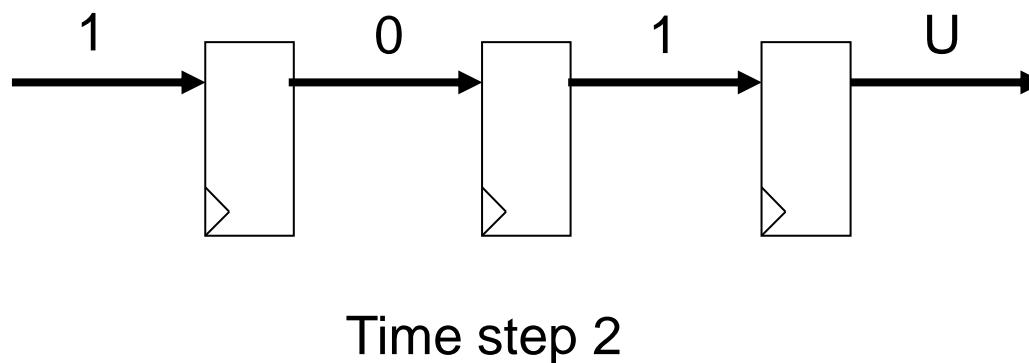
- U : Uninitialized (signal has not been assigned a value yet)
- X : Unknown (2 drivers one '0' one '1')
- H : weak '1' (example: model pull-up resistor)
 - I have never used this value
- L : weak '0'



Std_logic values

- Std_logic values

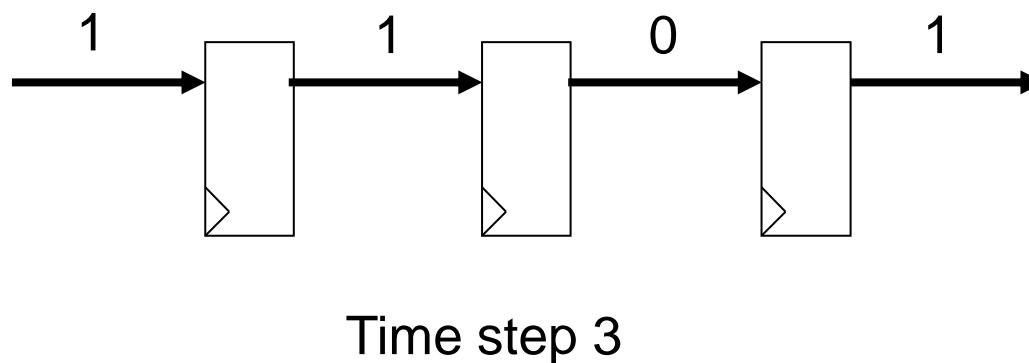
- U : Uninitialized (signal has not been assigned a value yet)
- X : Unknown (2 drivers one '0' one '1')
- H : weak '1' (example: model pull-up resistor)
 - I have never used this value
- L : weak '0'



Std_logic values

- Std_logic values

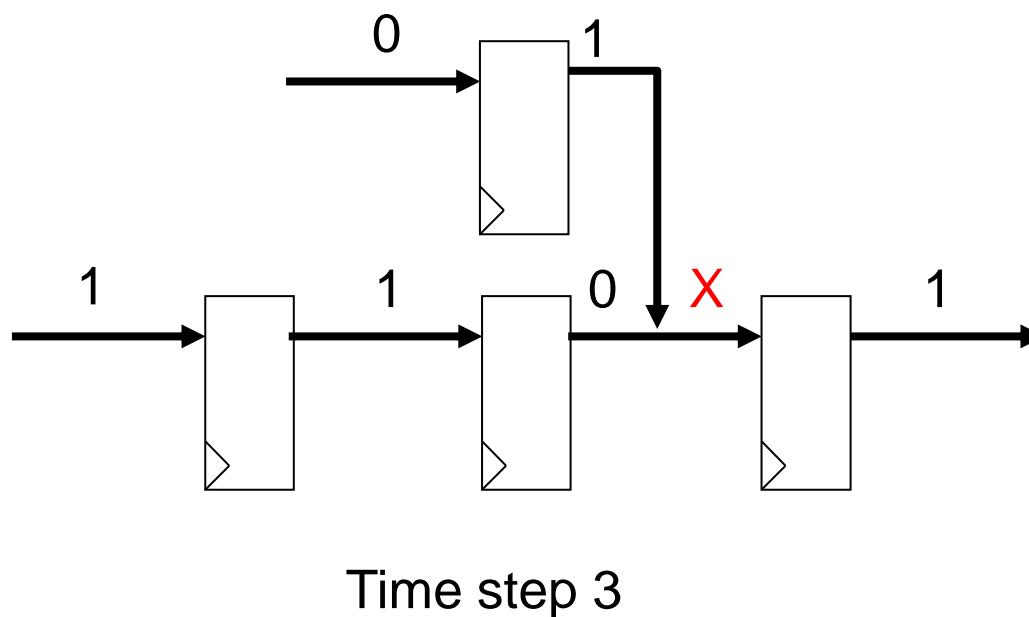
- U : Uninitialized (signal has not been assigned a value yet)
- X : Unknown (2 drivers one '0' one '1')
- H : weak '1' (example: model pull-up resistor)
 - I have never used this value
- L : weak '0'



Std_logic values

- Std_logic values

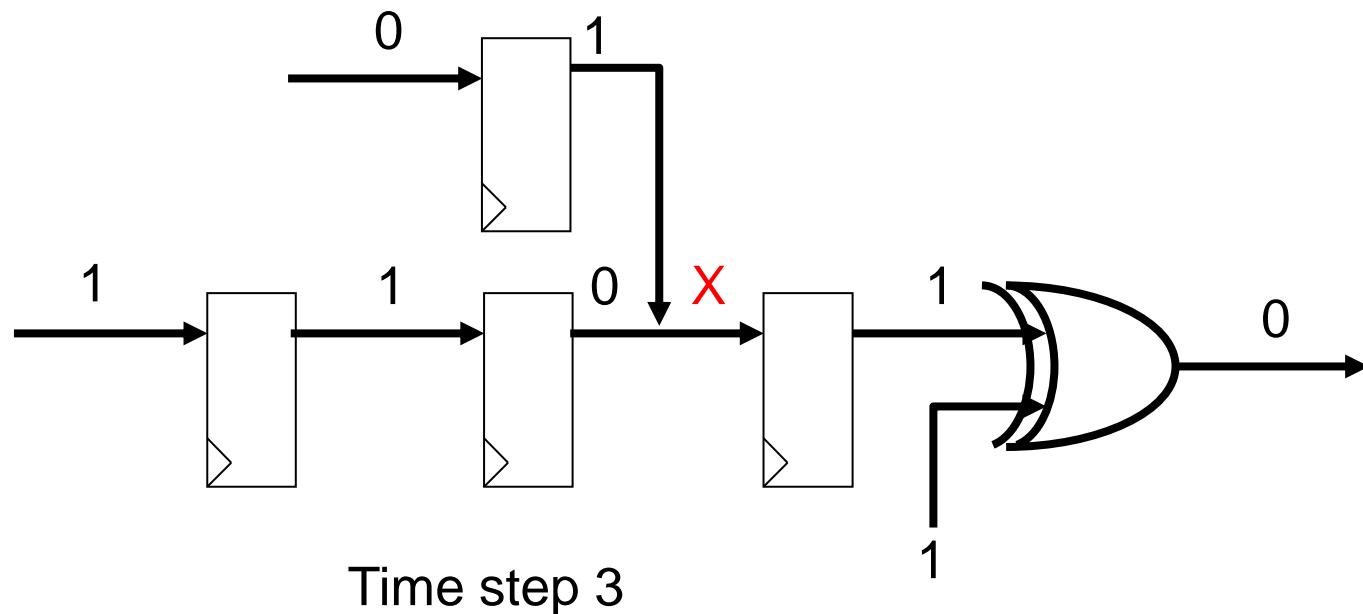
- U : Uninitialized (signal has not been assigned a value yet)
- X : Unknown (2 drivers one '0' one '1')
- H : weak '1' (example: model pull-up resistor)
 - I have never used this value
- L : weak '0'



Std_logic values

- Std_logic values

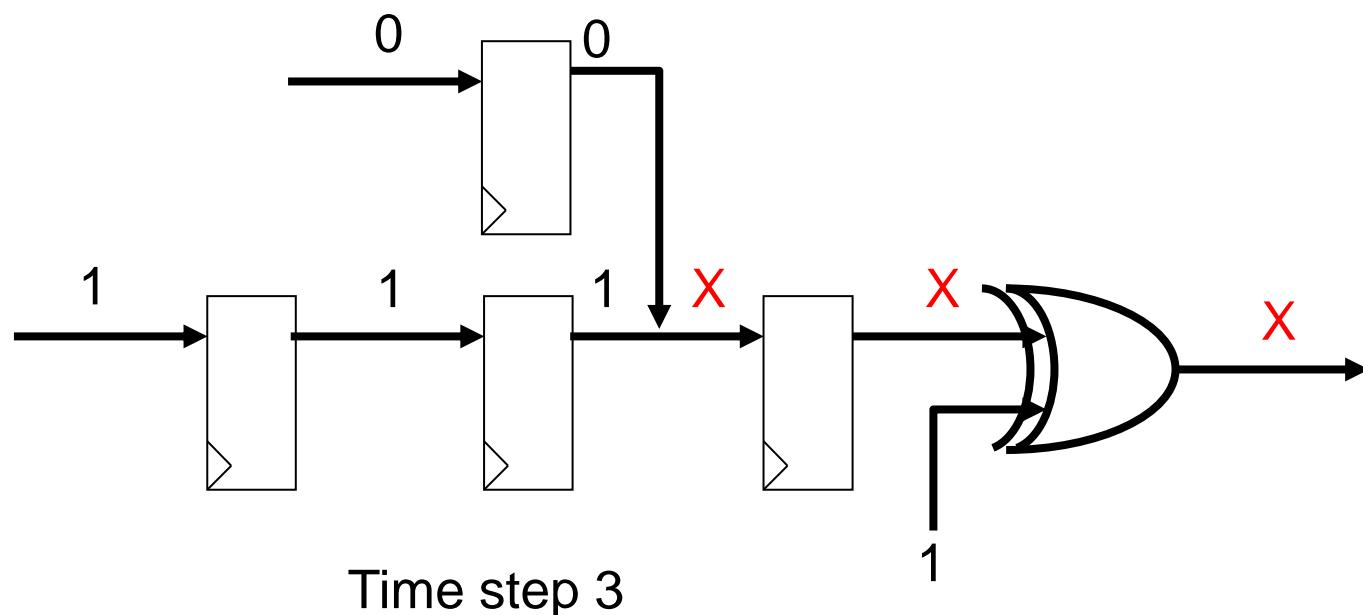
- U : Uninitialized (signal has not been assigned a value yet)
- X : Unknown (2 drivers one '0' one '1')
- H : weak '1' (example: model pull-up resistor)
 - I have never used this value
- L : weak '0'



Std_logic values

- Std_logic values

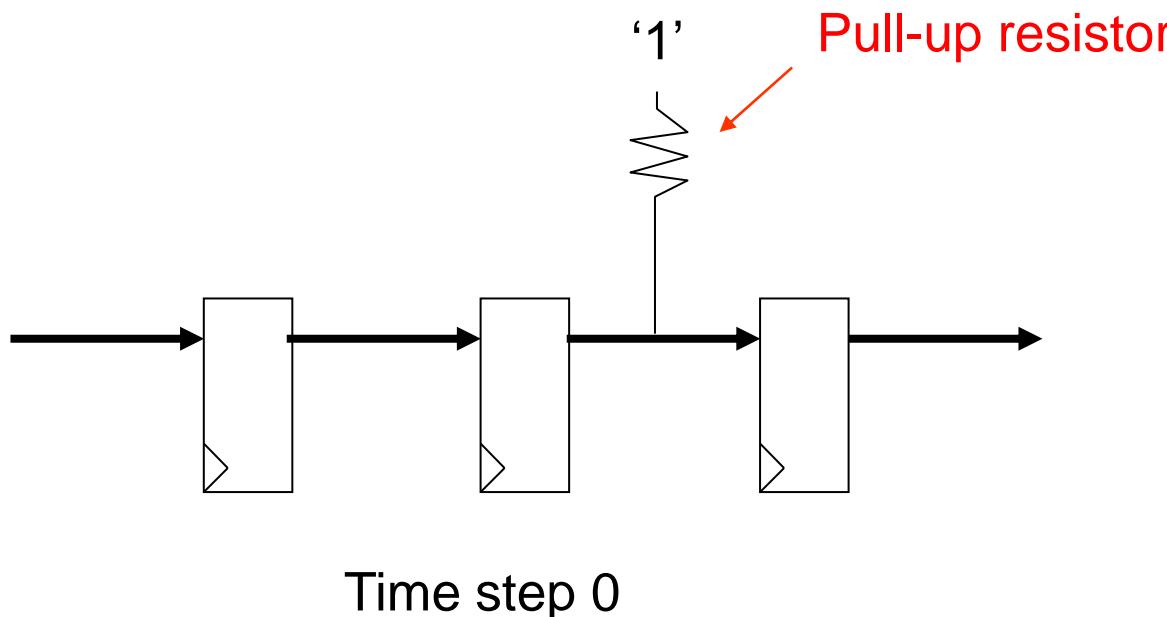
- U : Uninitialized (signal has not been assigned a value yet)
- X : Unknown (2 drivers one '0' one '1')
- H : weak '1' (example: model pull-up resistor)
 - I have never used this value
- L : weak '0'



Std_logic values

- Std_logic values

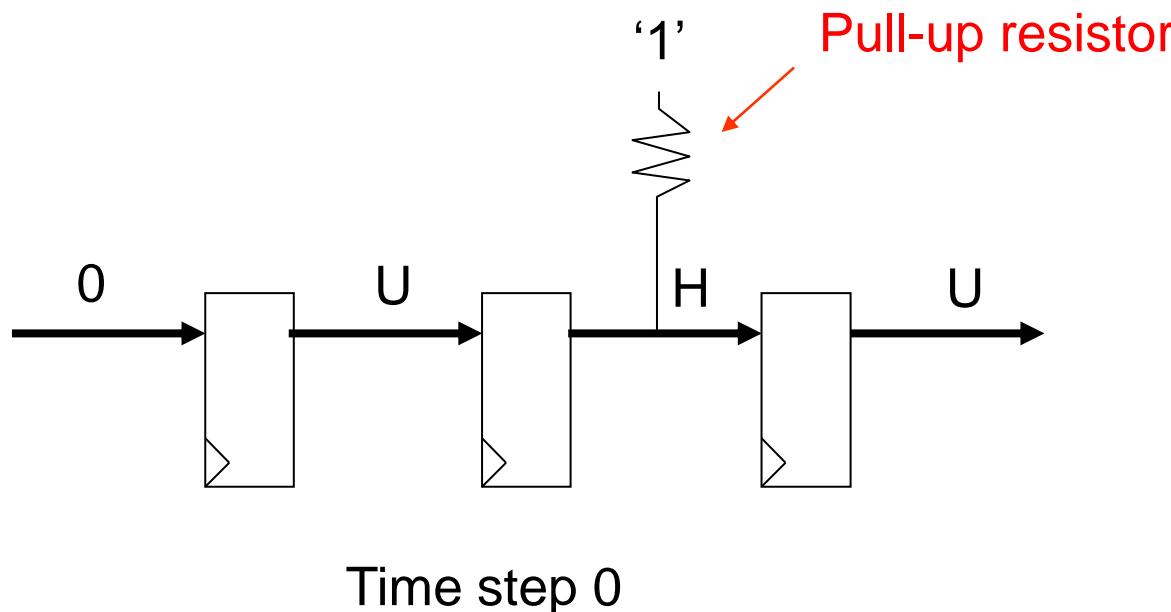
- U : Uninitialized (signal has not been assigned a value yet)
- X : Unknown (2 drivers one '0' one '1')
- H : weak '1' (example: model pull-up resistor)
 - I have never used this value
- L : weak '0'



Std_logic values

- Std_logic values

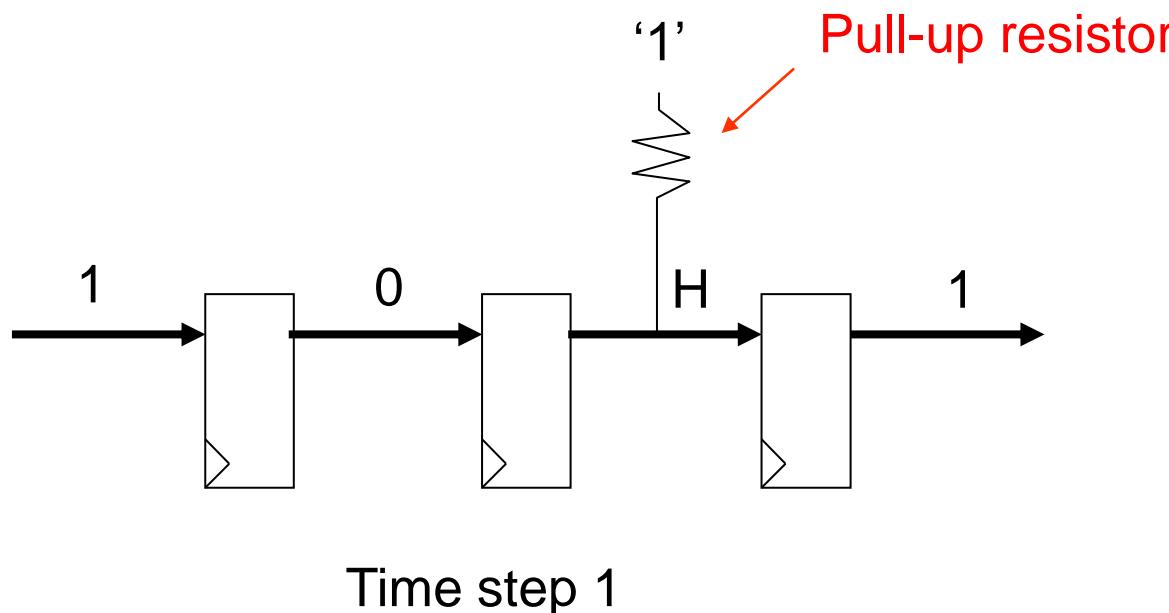
- U : Uninitialized (signal has not been assigned a value yet)
- X : Unknown (2 drivers one '0' one '1')
- H : weak '1' (example: model pull-up resistor)
 - I have never used this value
- L : weak '0'



Std_logic values

- Std_logic values

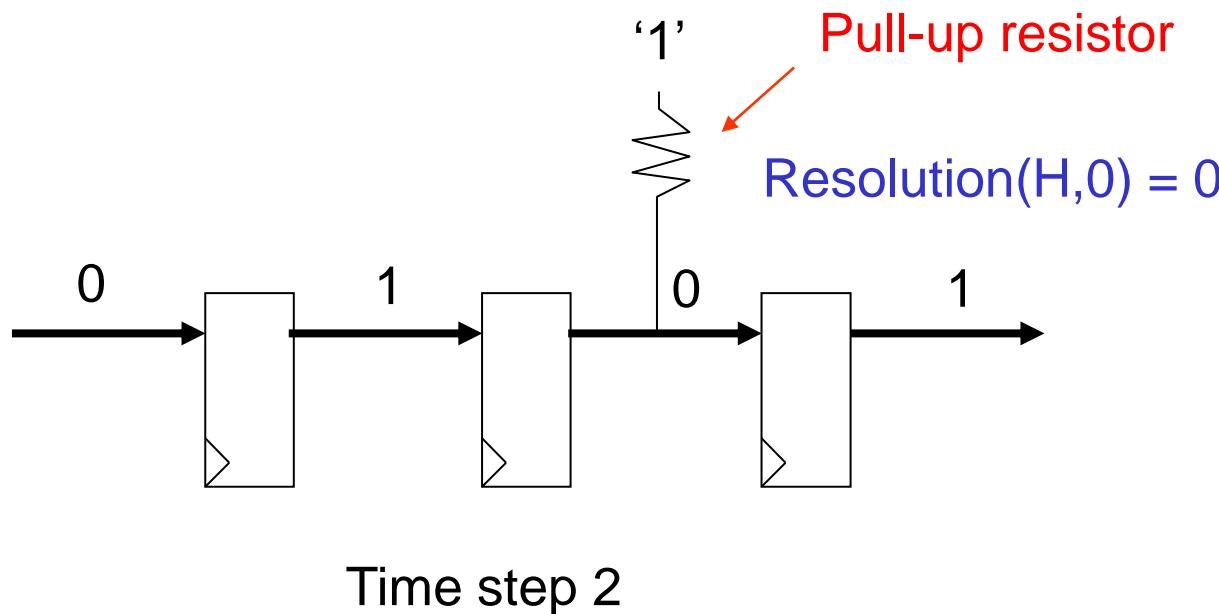- U : Uninitialized (signal has not been assigned a value yet)
- X : Unknown (2 drivers one '0' one '1')
- H : weak '1' (example: model pull-up resistor)
 - I have never used this value
- L : weak '0'



Pre-defined VHDL attributes

- `mysignal'event` (`mysignal` changed value)
- `mysignal'high` (highest value of `mysignal`'s type)
- `mysignal'low`
- Many other attributes
 - <http://www.cs.umbc.edu/help/VHDL/summary.html>

Singal vs Variable scope

- Signal: global to file
- Variable: local to process

```
My_process_1 : process (B,C,Y)
```

```
Begin
```

```
    A <= B + C;
```

```
    Z <= Y + C;
```

```
End My_process_1;
```

```
My_process_2 : process (B,X,Y,Ans1)
```

```
Begin
```

```
    X <= Z + 1;
```

```
    Ans <= B + Y;
```

```
End My_process_2;
```

VHDL on-line tutorials:

http://www.seas.upenn.edu/~ese201/vhdl/vhdl_primer.html

<http://www.cs.umbc.edu/help/VHDL/summary.html>

<http://www.vhdl-online.de/tutorial/>

Singal vs Variable scope

- Signal: global to file
- Variable: local to process

```
My_process_1 : process (B,C,Y)
```

```
Begin
```

```
    A <= B + C;
```

```
    varZ <= Y + C;
```

```
End My_process_1;
```

Each varZ are local
to their process.

Completely independent

```
My_process_2 : process (B,X,Y,Ans1)
```

```
Begin
```

```
    X <= varZ + 1;
```

```
    Ans <= B + Y;
```

```
End My_process_2;
```

VHDL on-line tutorials:

http://www.seas.upenn.edu/~ese201/vhdl/vhdl_primer.html

<http://www.cs.umbc.edu/help/VHDL/summary.html>

<http://www.vhdl-online.de/tutorial/>


Arrays and Records

- Arrays: Group signals of the **same** type together
- Records: Group signal of **different** types together

VHDL on-line tutorials:

http://www.seas.upenn.edu/~ese201/vhdl/vhdl_primer.html
<http://www.vhdl-online.de/tutorial/>

Array Example (Delay Shift Register)

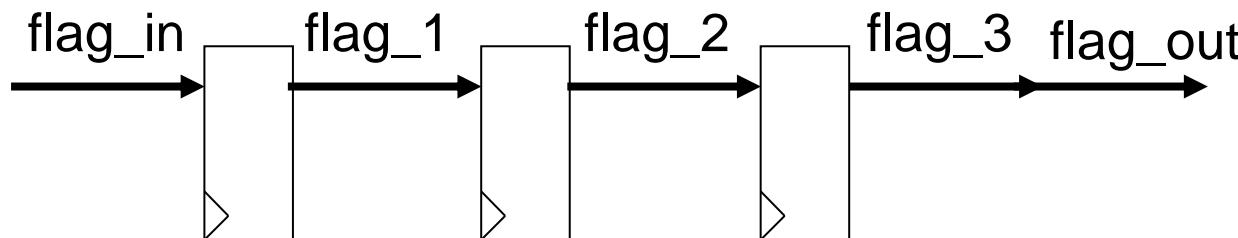


BEGIN

```
My_process_1 : process (clk)
Begin
  IF (clk'event and clk = '1') THEN
    flag_1 <= flag_in;
    flag_2 <= flag_1;
    flag_3 <= flag_2;
  END IF;
End My_process_1;
flag_out <= flag_3
END;
```

VHDL on-line tutorials:

http://www.seas.upenn.edu/~ese201/vhdl/vhdl_primer.html
<http://www.vhdl-online.de/tutorial/>

Array Example (Delay Shift Register)

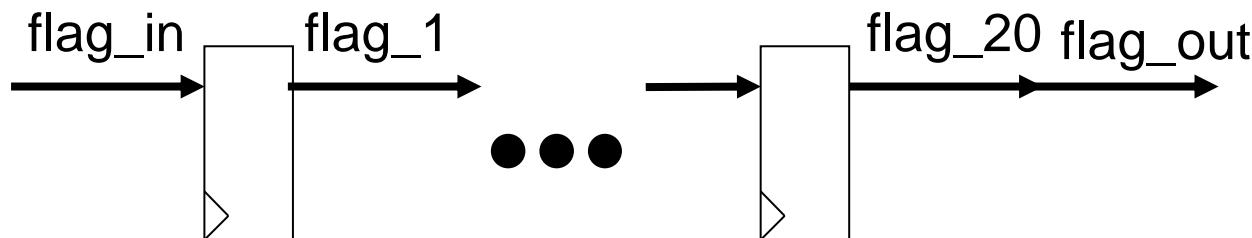

```
type flag_reg_array is array (DELAY-1 downto 0) of std_logic;  
signal flag_reg : flag_reg_array;
```

BEGIN

My_process_1 : process (clk)

Begin

IF (clk'event and clk = '1') THEN

flag_reg(flag_reg'high downto 0) <=

flag_reg(flag_reg'high-1 downto 0) & flag_in;


END IF;

End My_process_1;

flag_out <= flag_reg(flag_reg'high);

END;

Array Example (Delay Shift Register)

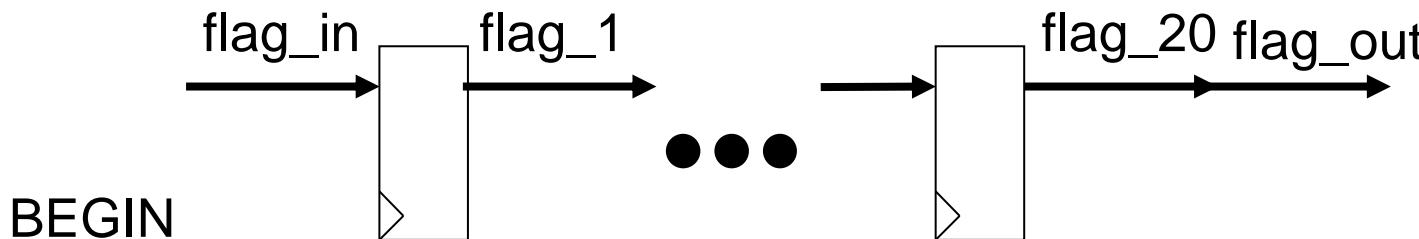

BEGIN


```
My_process_1 : process (clk)
Begin
  IF (clk'event and clk = '1') THEN
    flag_1 <= flag_in;
    flag_2 <= flag_1;
    ●●●
    flag_20 <= flag_19;
  END IF;
End My_process_1;
flag_out <= flag_20
END;
```

VHDL on-line tutorials:


http://www.seas.upenn.edu/~ese201/vhdl/vhdl_primer.html
<http://www.vhdl-online.de/tutorial/>

Array Example (Delay Shift Register)
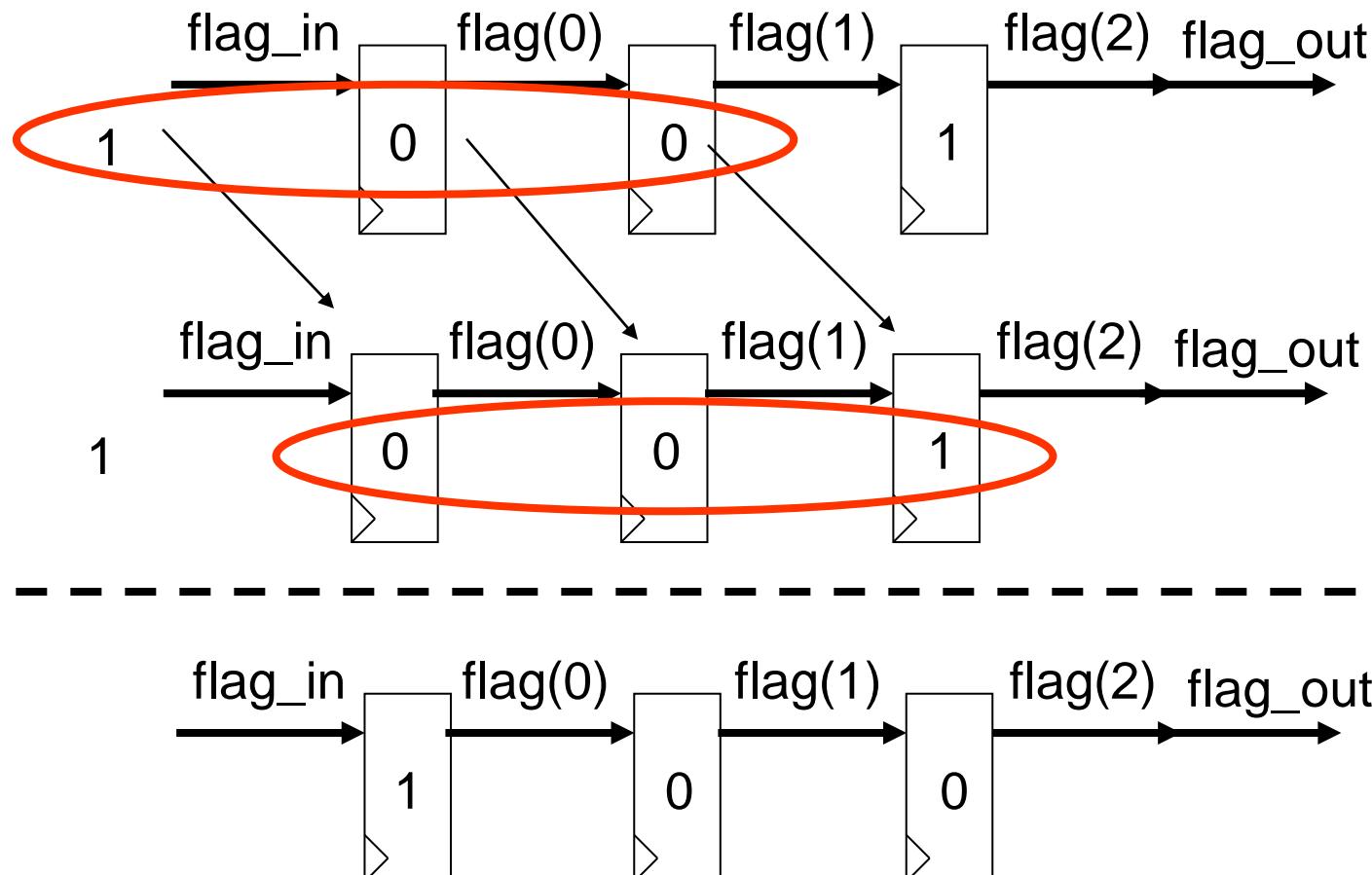
```
flag_reg(flag_reg'high downto 0) <= flag_reg(flag_reg'high-1 downto 0) & flag_in;
```



Array Example (Delay Shift Register)

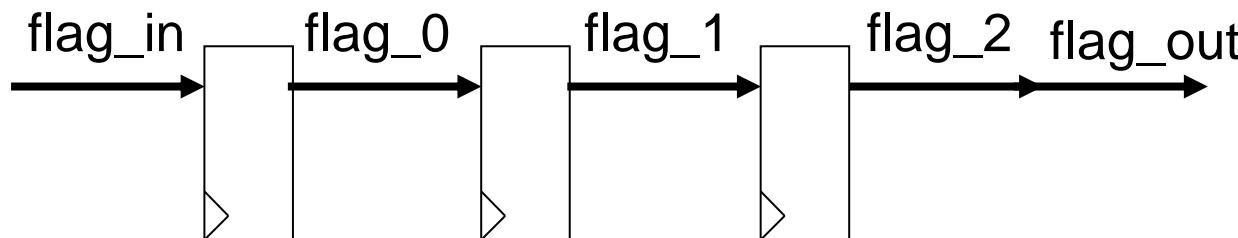

BEGIN

```
My_process_1 : process (clk)
Begin
  IF (clk'event and clk = '1') THEN
    flag_0 <= flag_in;
    flag_1 <= flag_0;
    flag_2 <= flag_1;
  END IF;
End My_process_1;
flag_out <= flag_2
END;
```

VHDL on-line tutorials:

http://www.seas.upenn.edu/~ese201/vhdl/vhdl_primer.html
<http://www.vhdl-online.de/tutorial/>

Finite State Machine (FSM) Design


- Model of computation
- High level application example (Networking)
- Two major types
 - Moore
 - Mealy
- Detailed view of application example

Finite State Machines

- What types of applications are they well suited
 - Streaming pattern recognition
 - Sequential event based control logic
- Allow hardware designer to reason about things in small pieces


Streaming Network application (MP1)

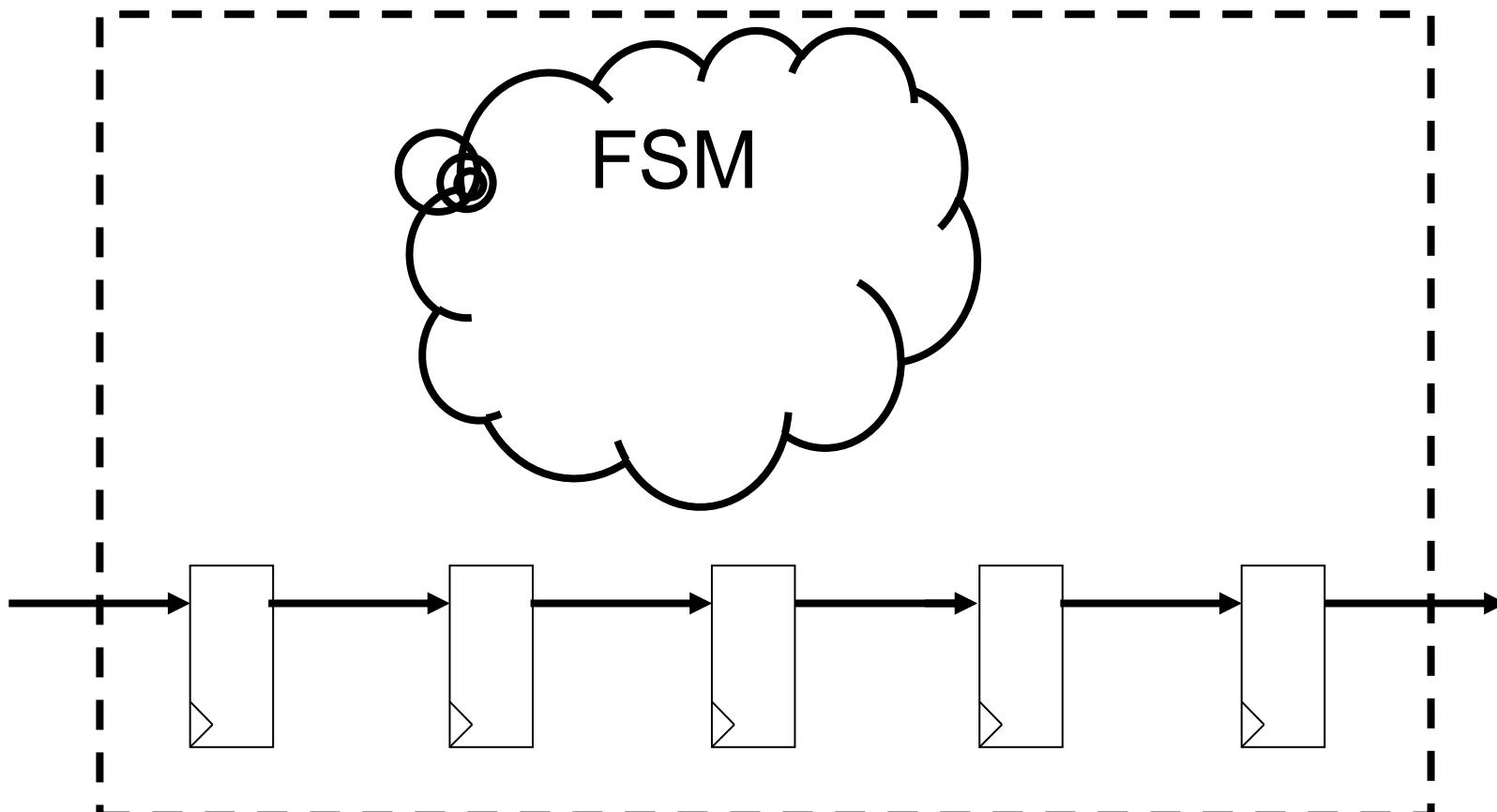- Process UDP packet headers (event driven)
- Detect patterns in payload (e.g. “Corn”)
- Modify payload based on header information




Streaming Network application (MP1)

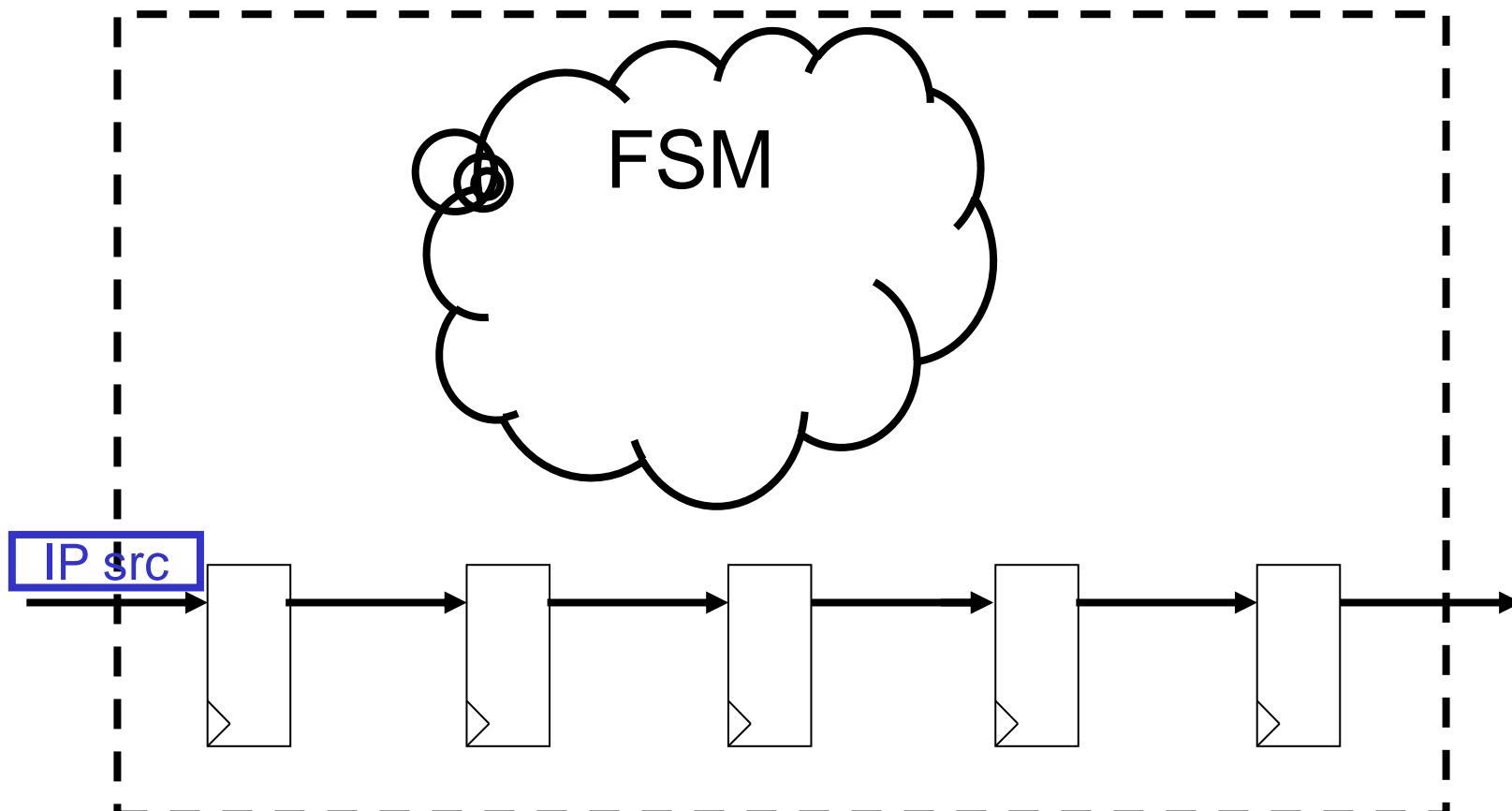- Process UDP packet headers (event driven)
- Detect patterns in payload (e.g. “Corn”)
- Modify payload based on header information




Streaming Network application (MP1)

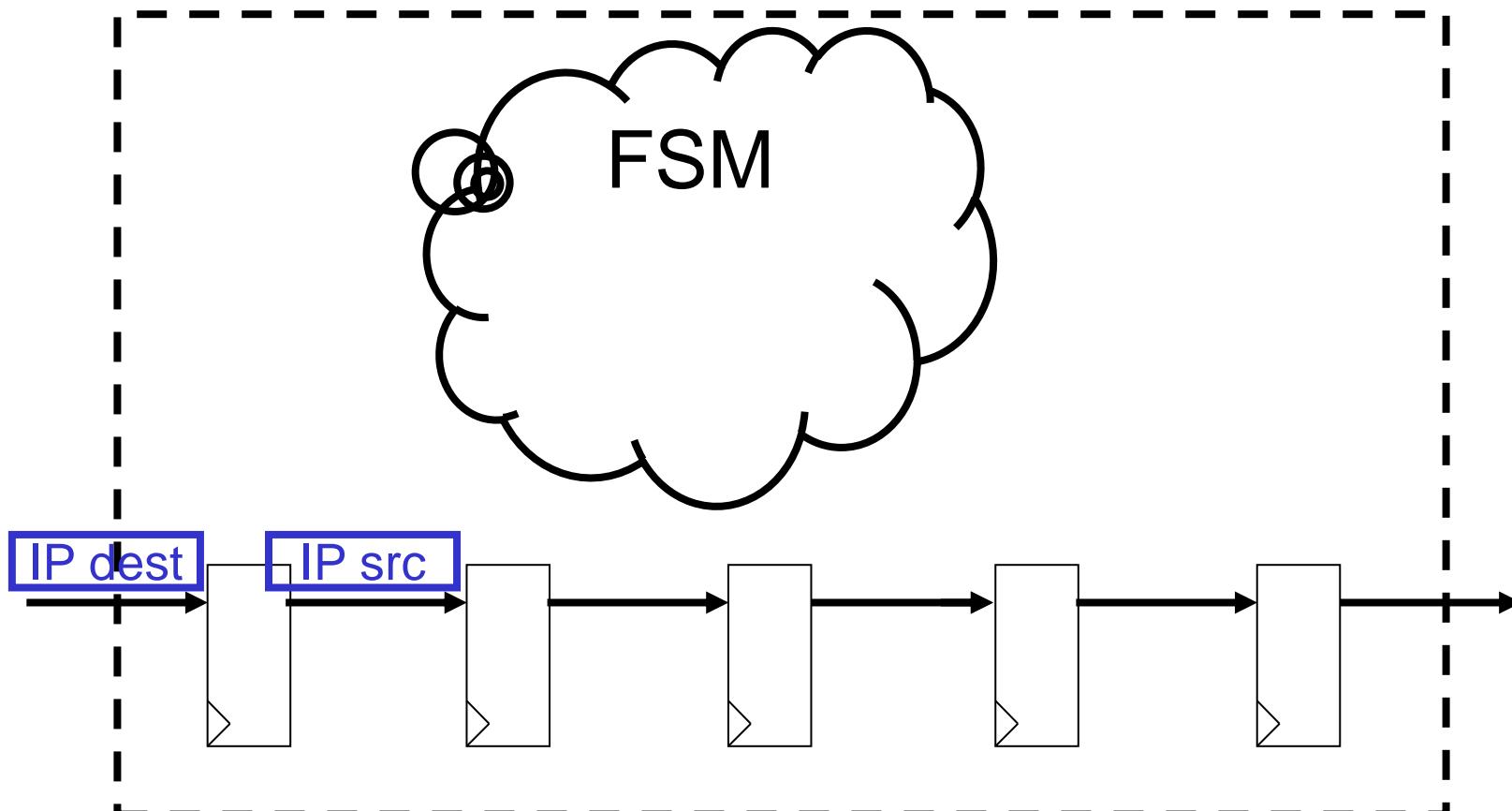- Process UDP packet headers (event driven)
- Detect patterns in payload (e.g. “Corn”)
- Modify payload based on header information




Streaming Network application (MP1)

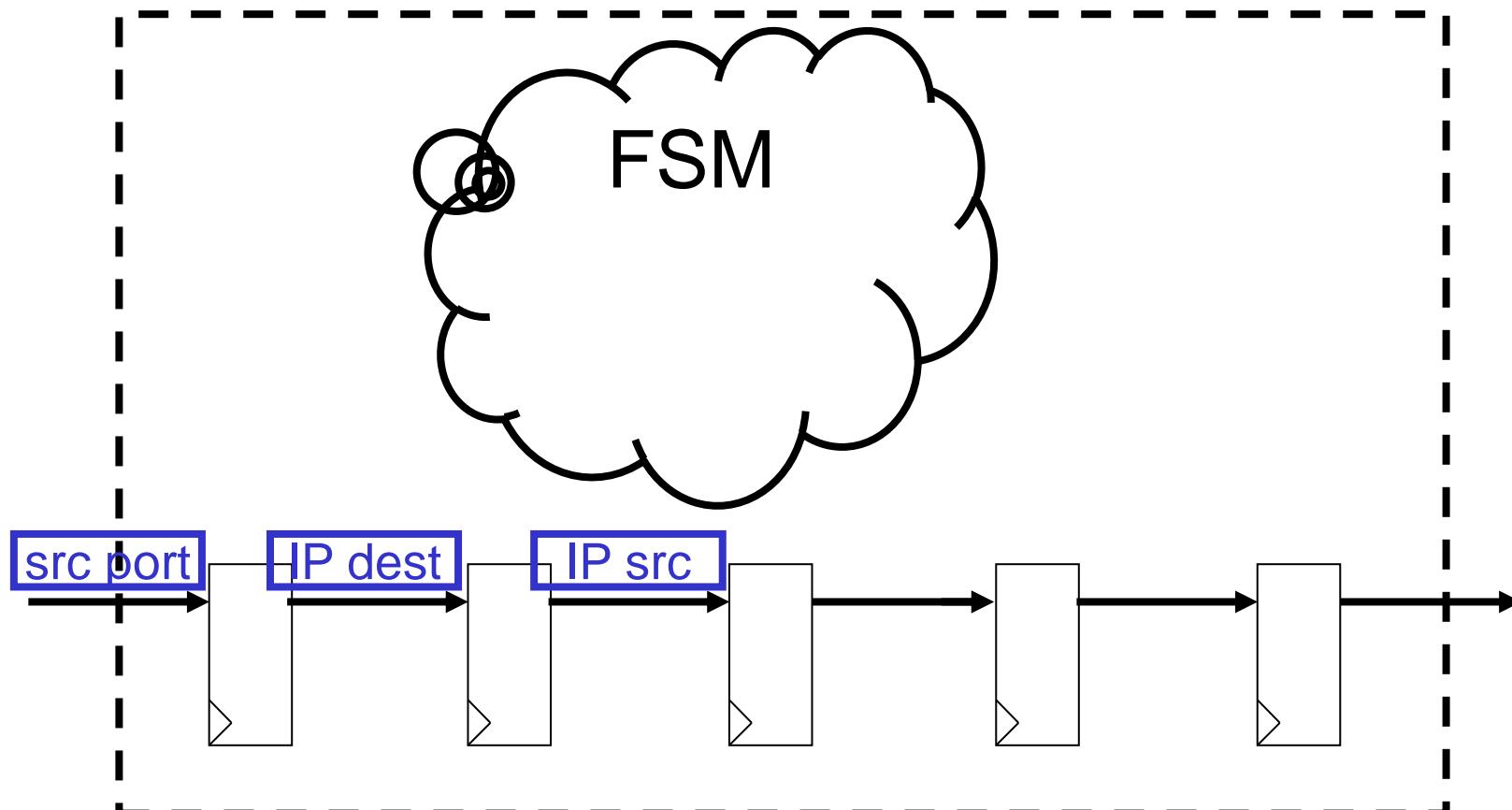- Process UDP packet headers (event driven)
- Detect patterns in payload (e.g. “Corn”)
- Modify payload based on header information




Streaming Network application (MP1)

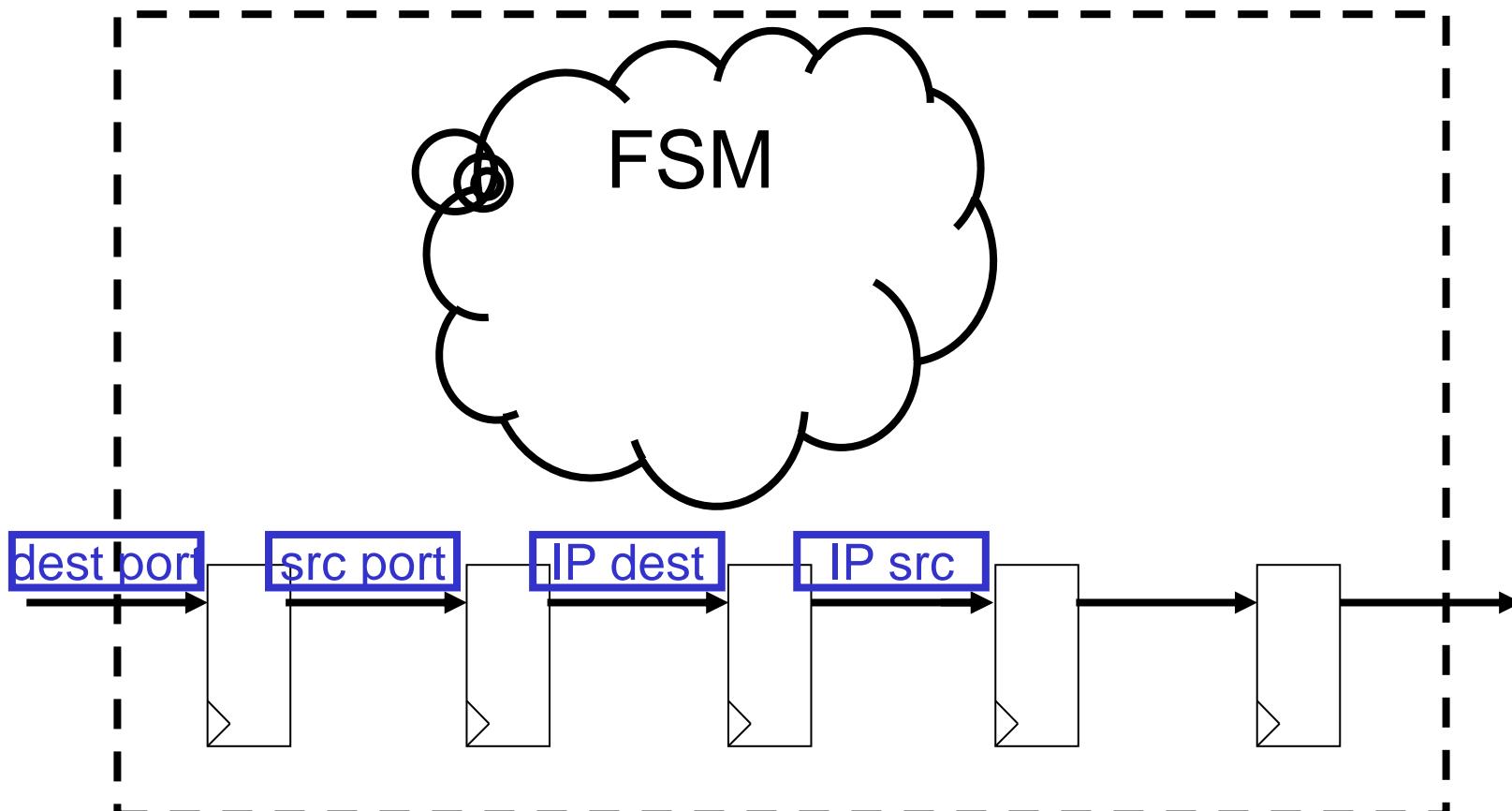- Process UDP packet headers (event driven)
- Detect patterns in payload (e.g. “Corn”)
- Modify payload based on header information




Streaming Network application (MP1)

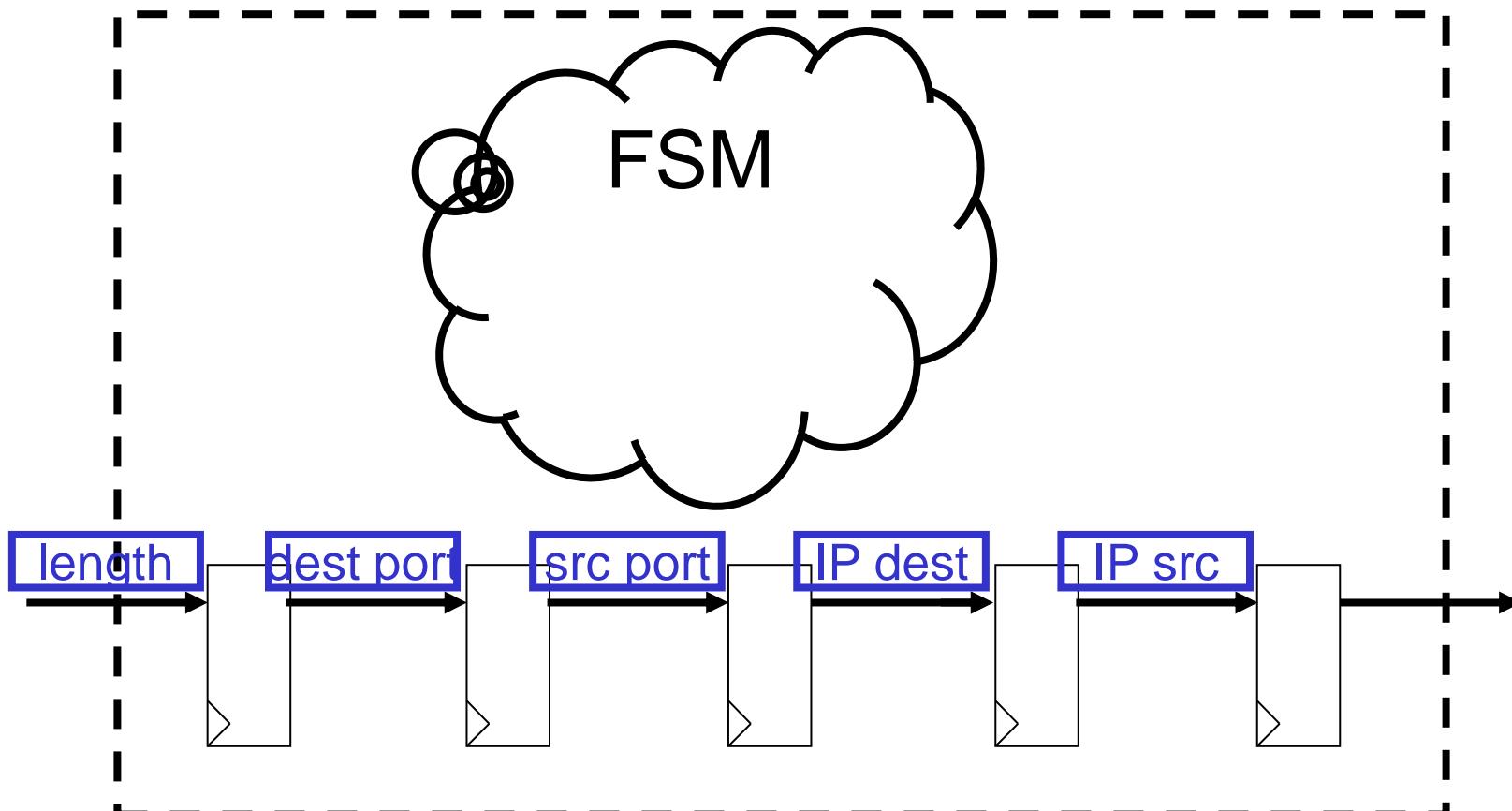- Process UDP packet headers (event driven)
- Detect patterns in payload (e.g. “Corn”)
- Modify payload based on header information




Streaming Network application (MP1)

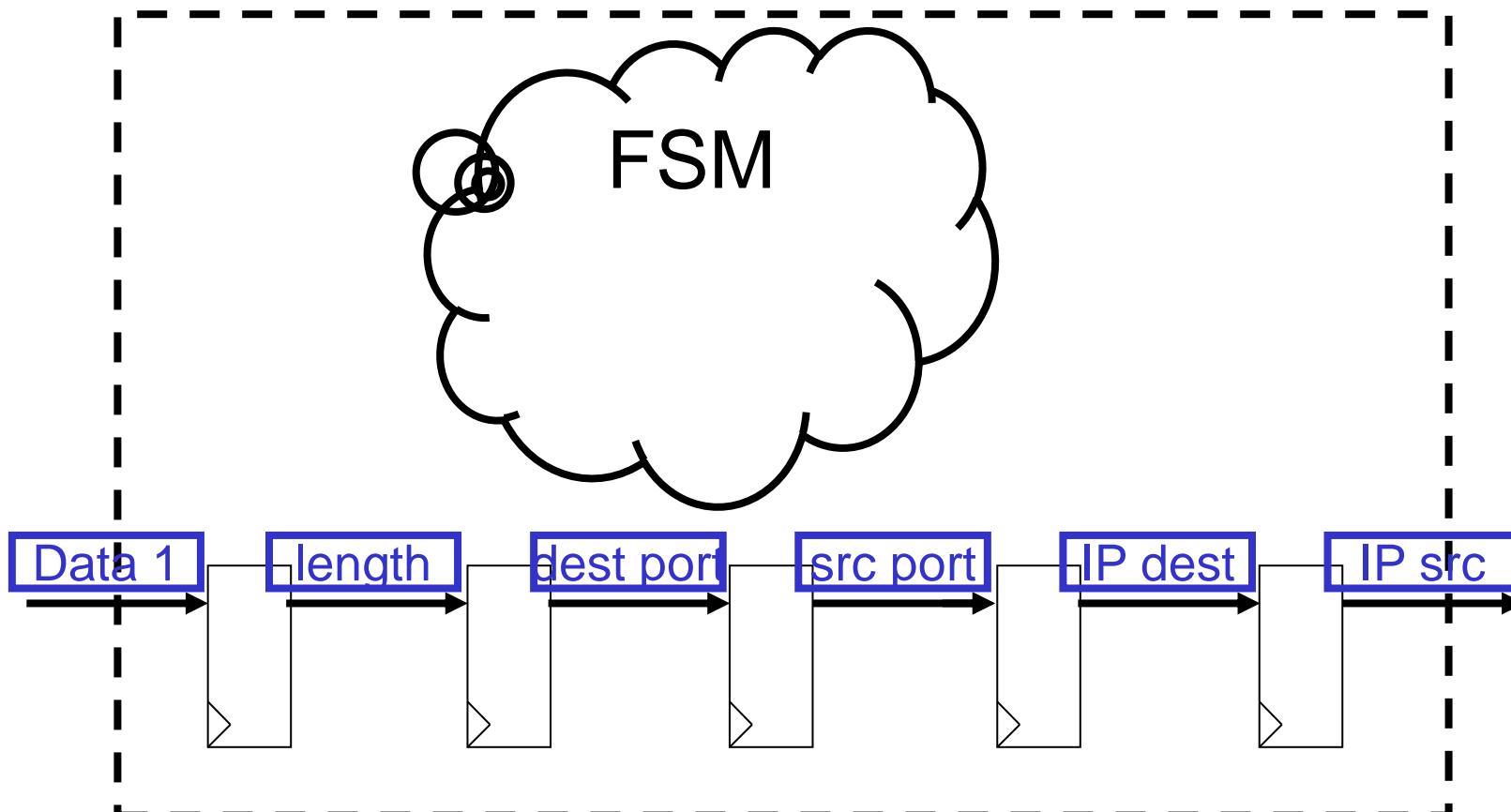- Process UDP packet headers (event driven)
- Detect patterns in payload (e.g. “Corn”)
- Modify payload based on header information




Streaming Network application (MP1)

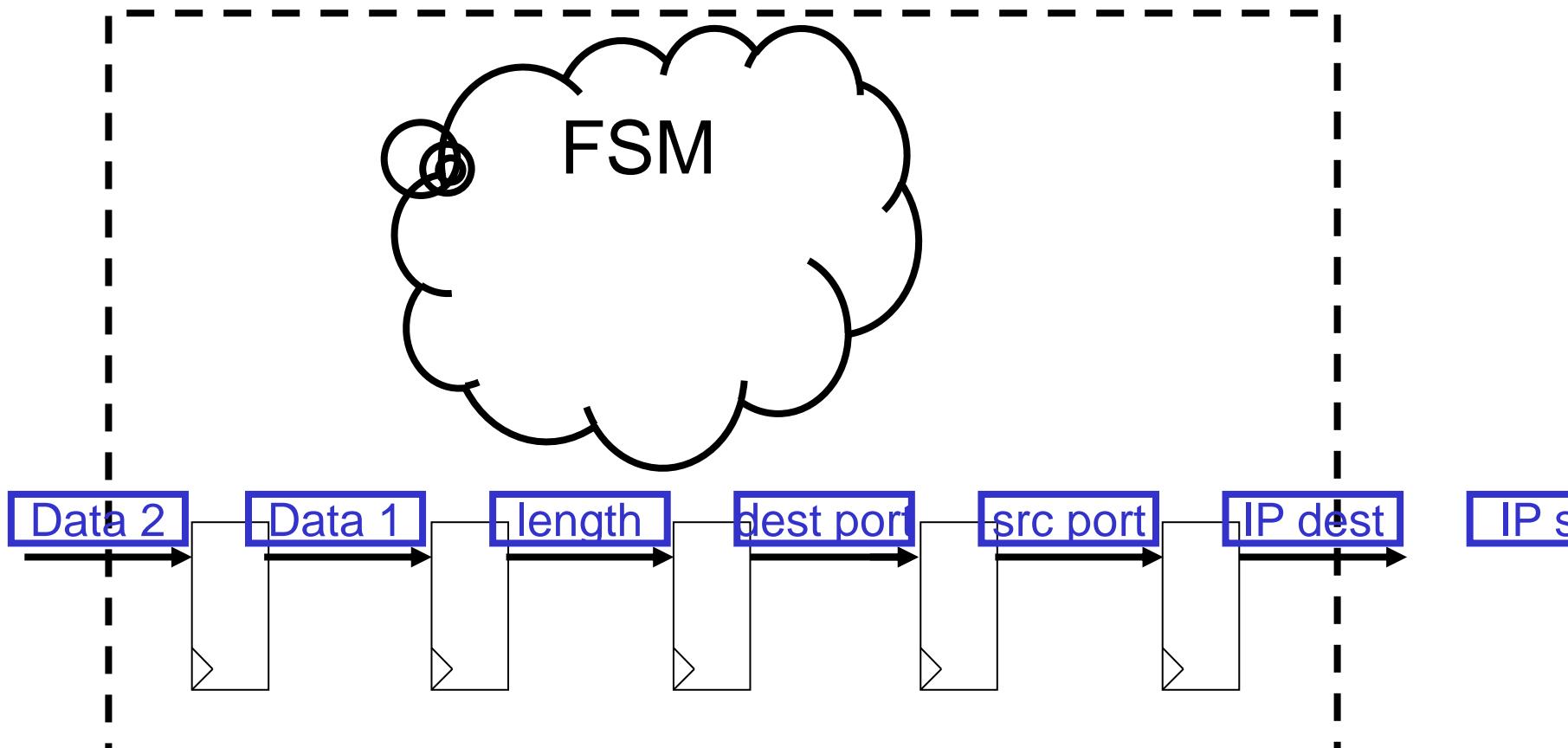- Process UDP packet headers (event driven)
- Detect patterns in payload (e.g. “Corn”)
- Modify payload based on header information




Streaming Network application (MP1)

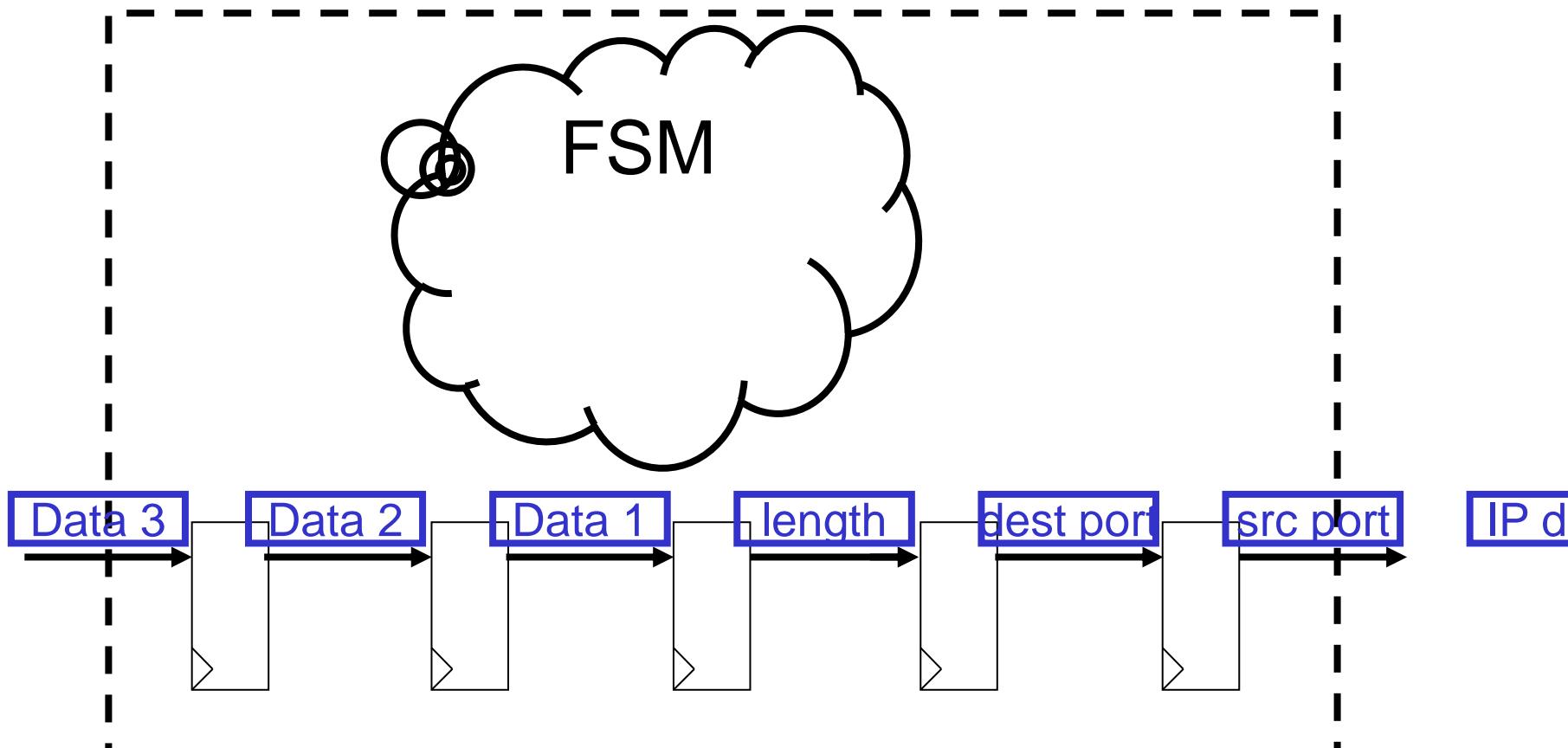- Process UDP packet headers (event driven)
- Detect patterns in payload (e.g. “Corn”)
- Modify payload based on header information




Streaming Network application (MP1)

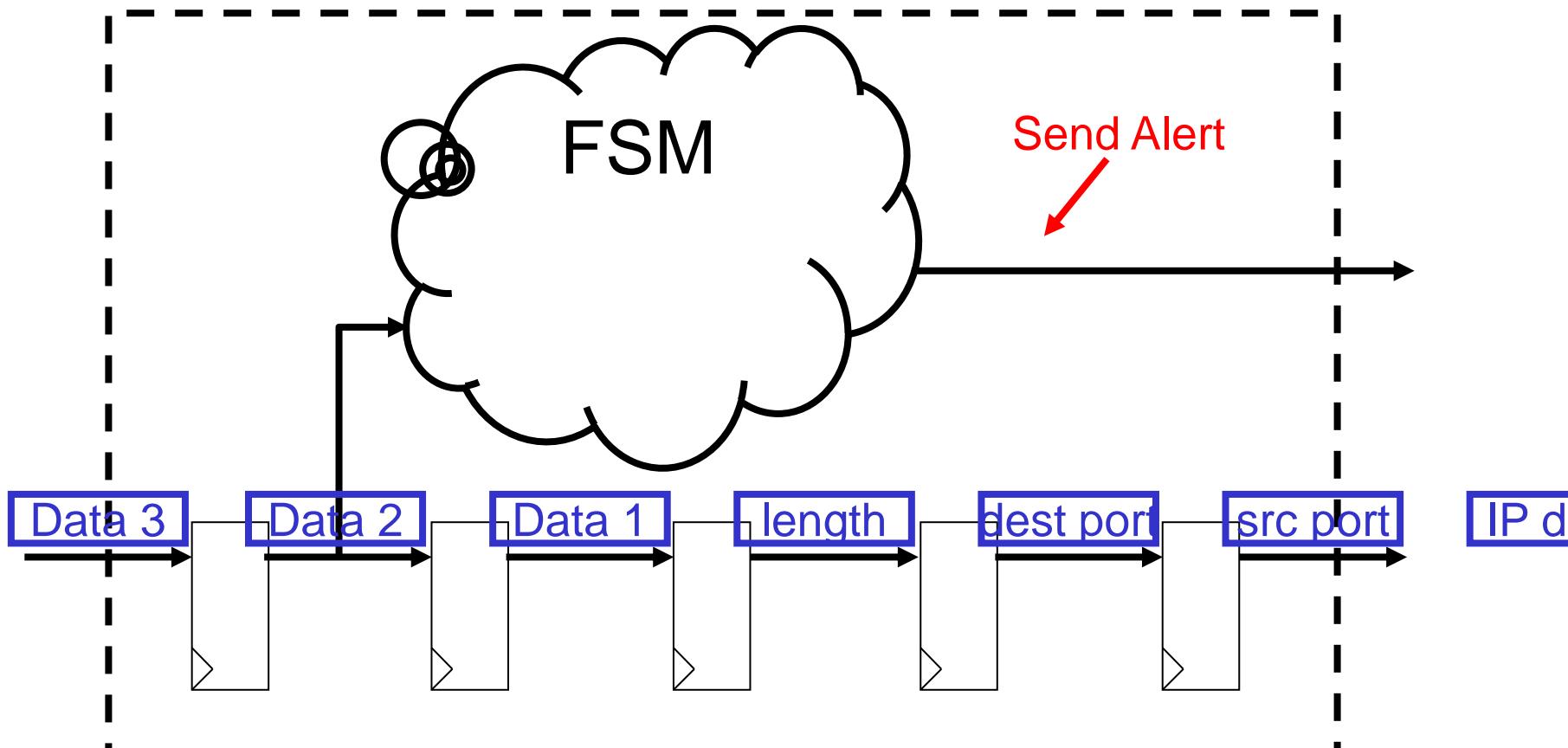- Process UDP packet headers (event driven)
- Detect patterns in payload (e.g. “Corn”)
- Modify payload based on header information




Streaming Network application (MP1)

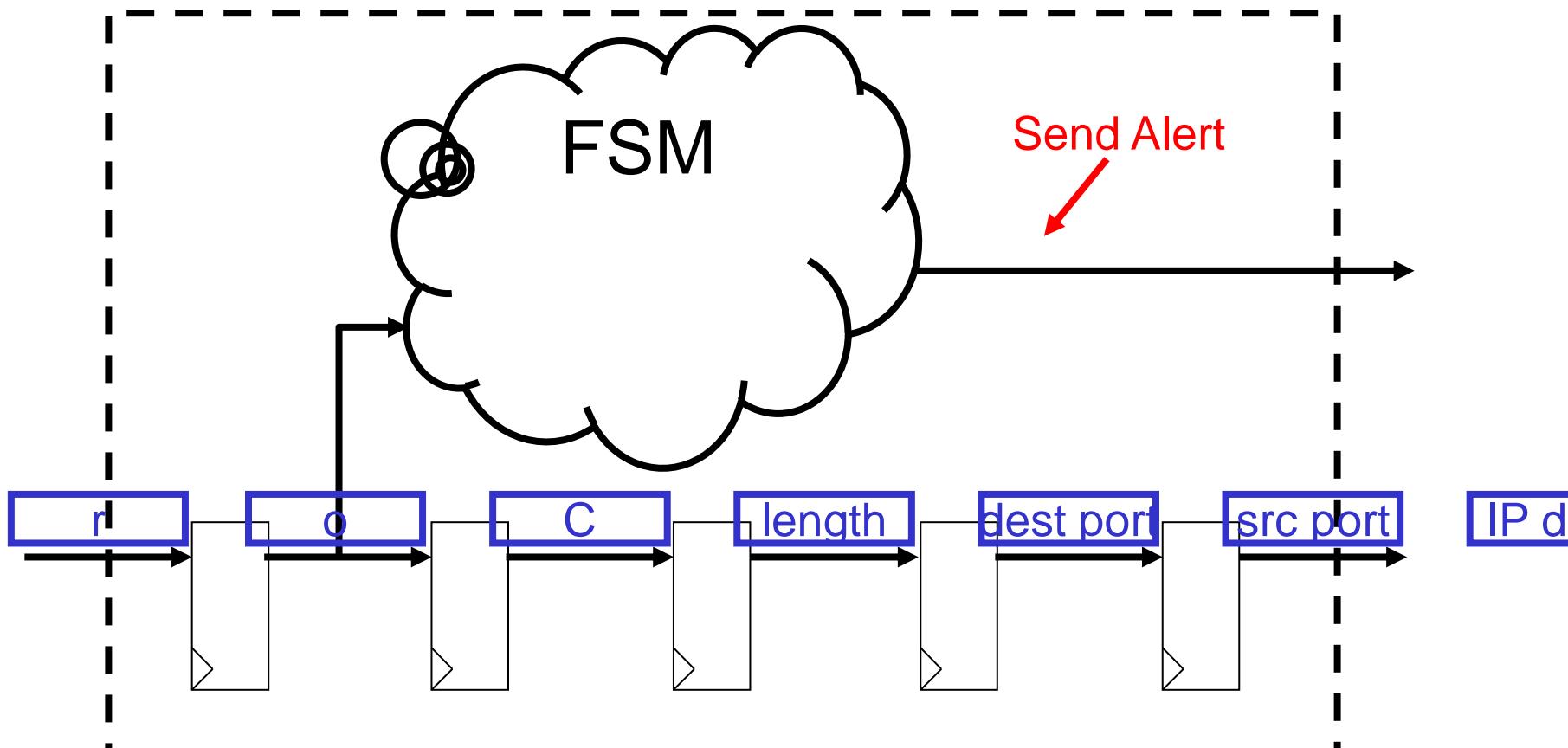- Process UDP packet headers (event driven)
- Detect patterns in payload (e.g. “Corn”)
- Modify payload based on header information




Streaming Network application (MP1)

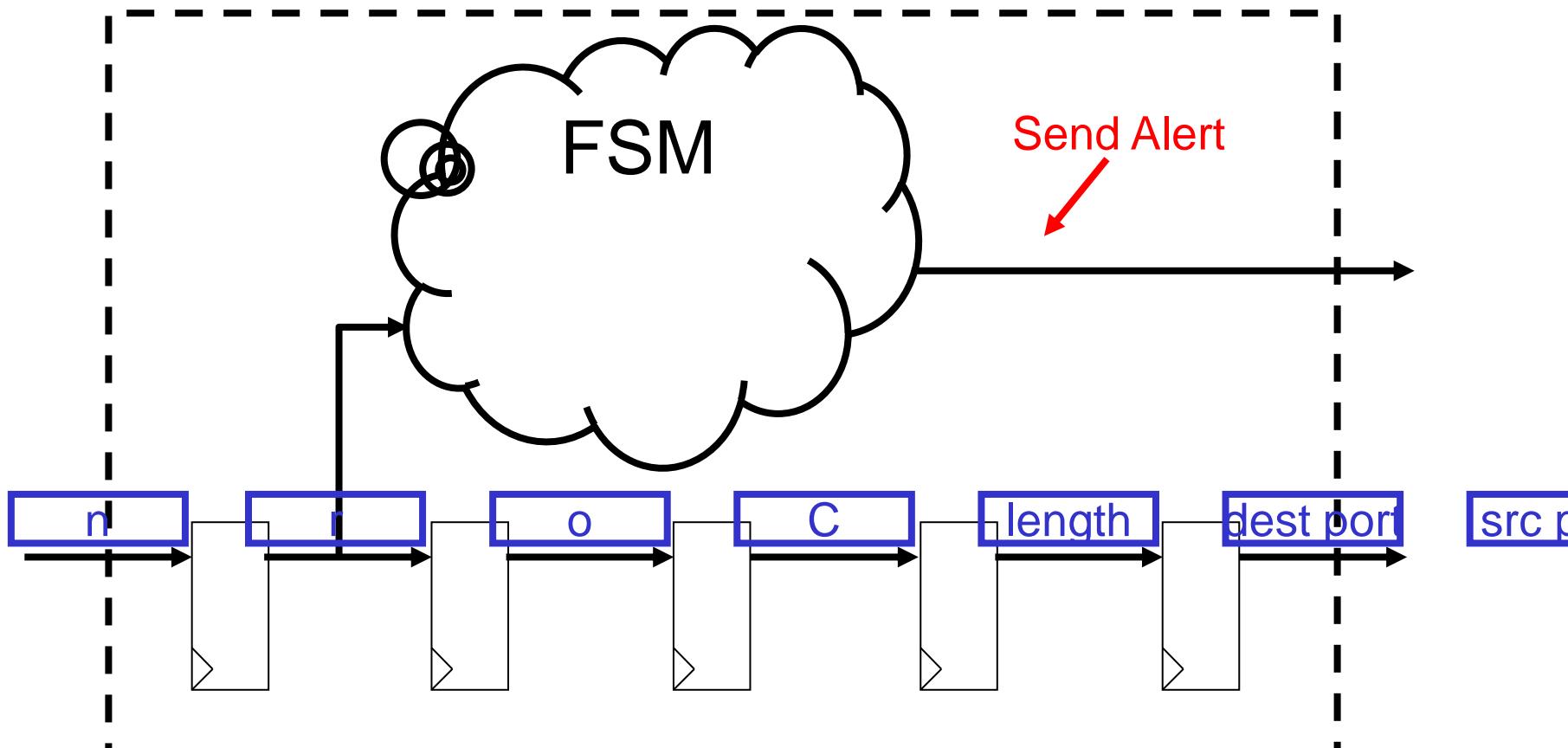- Process UDP packet headers (event driven)
- Detect patterns in payload (e.g. “Corn”)
- Modify payload based on header information




Streaming Network application (MP1)

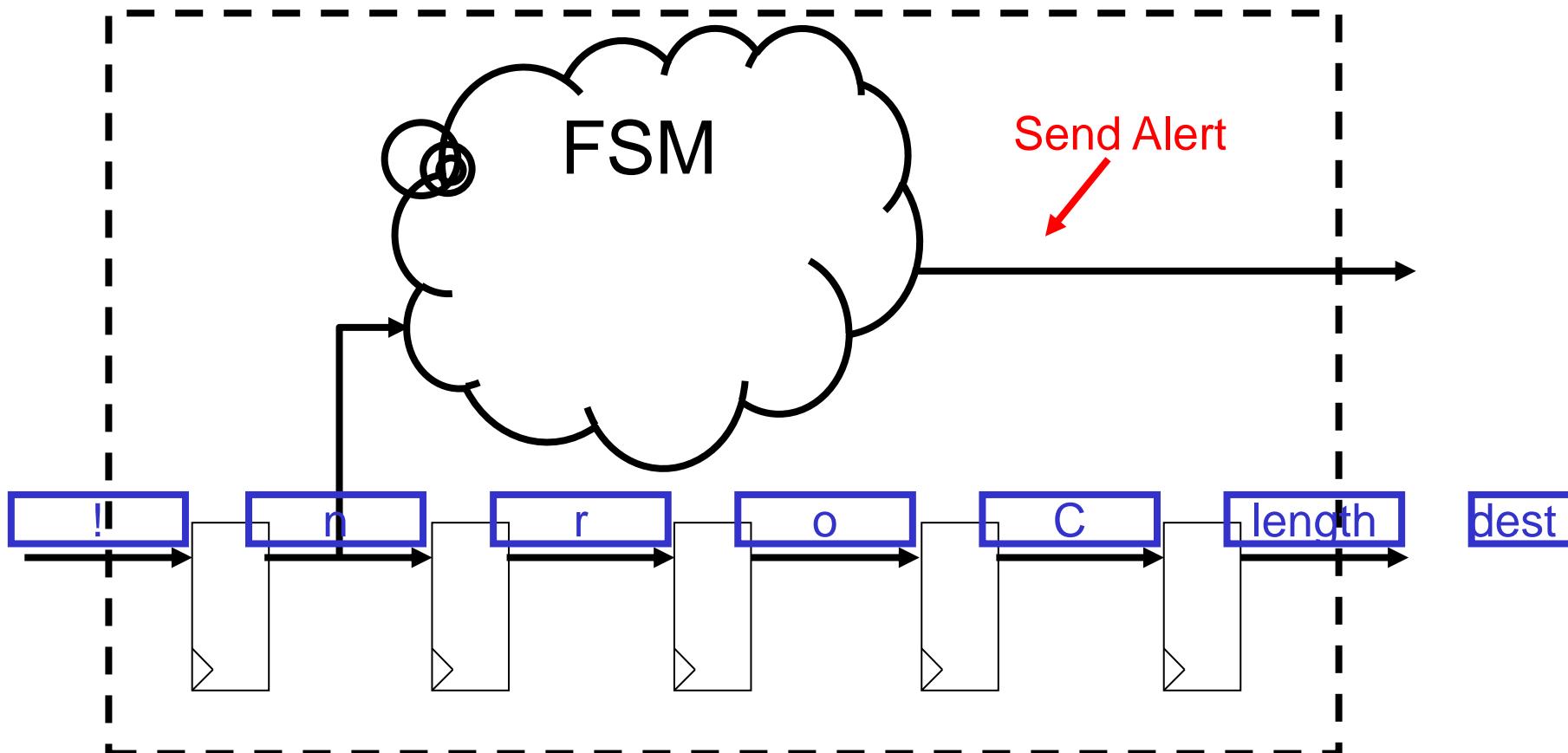- Process UDP packet headers (event driven)
- Detect patterns in payload (e.g. “Corn”)
- Modify payload based on header information



Streaming Network application (MP1)

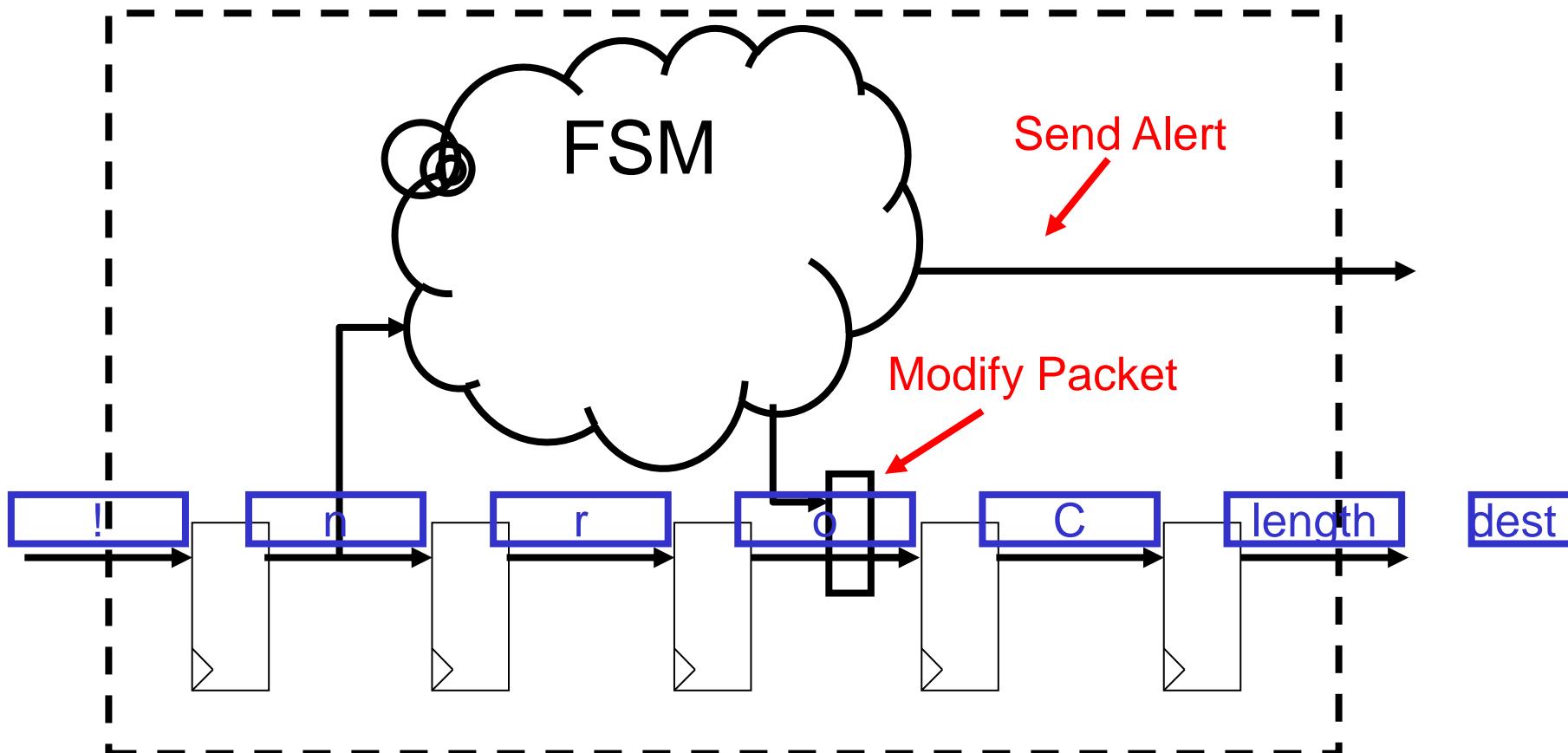- Process UDP packet headers (event driven)
- Detect patterns in payload (e.g. “Corn”)
- Modify payload based on header information




Moore and Mealy FSMs

- Moore: Output is only a function of the current state
- Mealy: Output is a function of the current state and input (“Mealy is more”)

Moore FSM

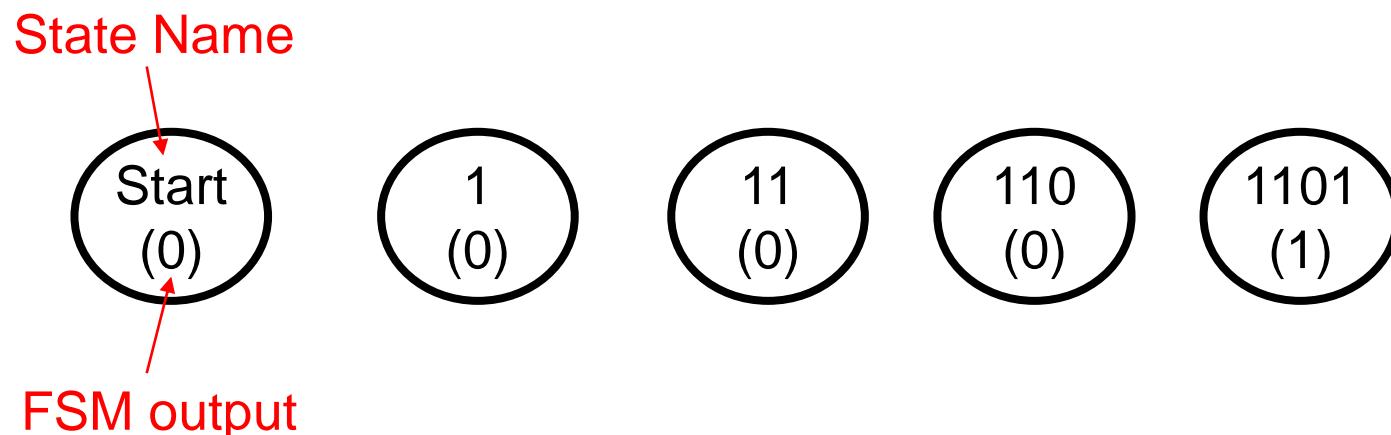
- Moore: Output is only a function of the current state
- Example detect every occurrence of “1101”



Moore FSM


- Moore: Output is only a function of the current state
- Example detect every occurrence of “1101”

Where to go on a given input

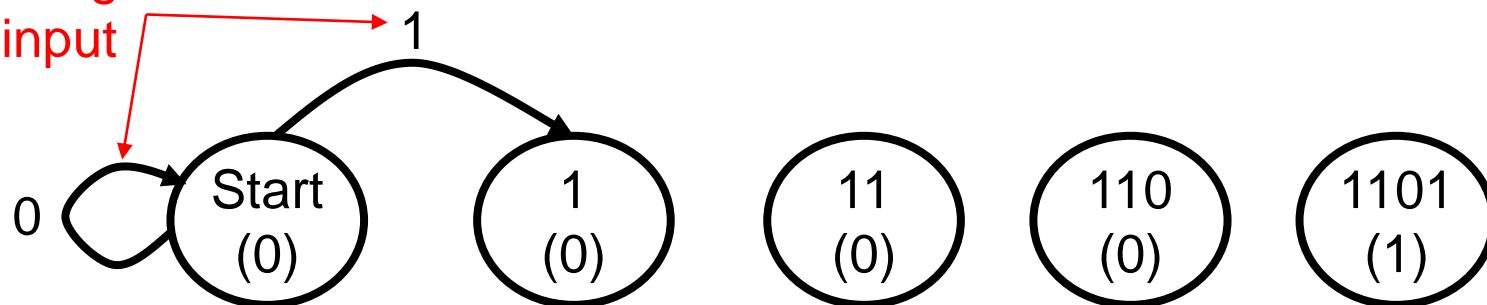

Moore FSM

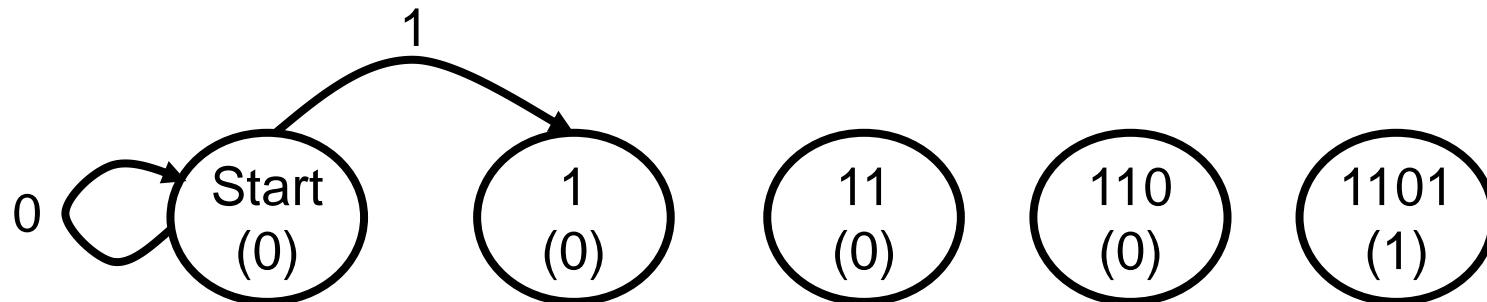- Moore: Output is only a function of the current state
- Example detect every occurrence of “1101”




Input: 1

Output: 0

Moore FSM

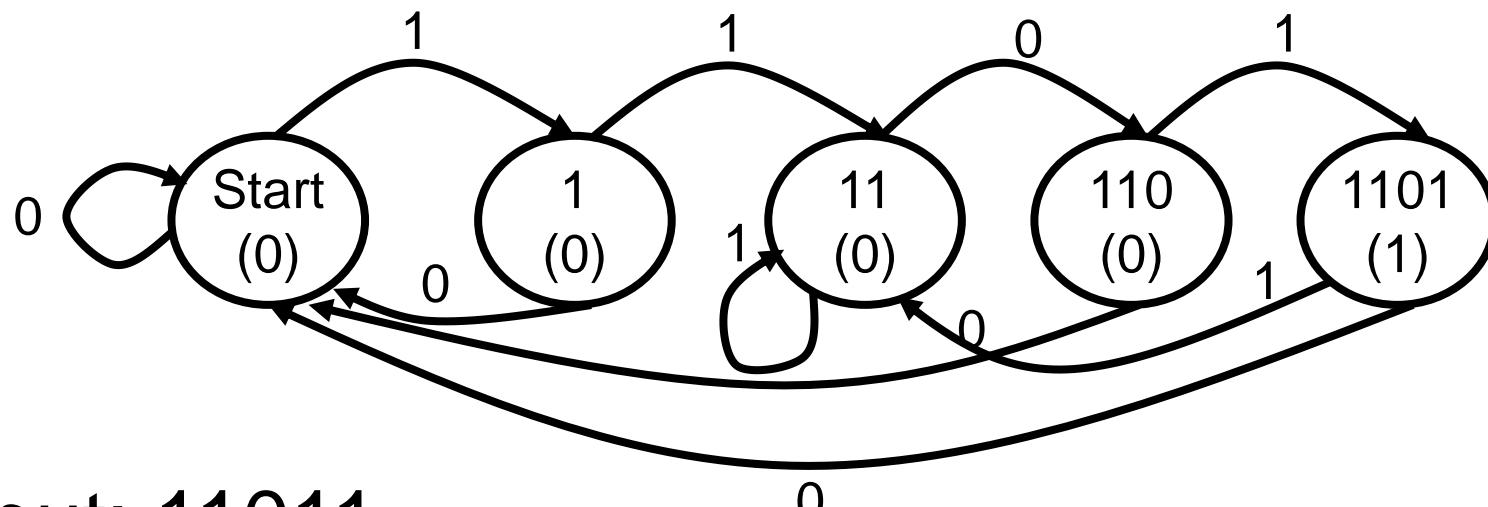- Moore: Output is only a function of the current state
- Example detect every occurrence of “1101”




Input: 11011

Output: 00010


Mealy FSM

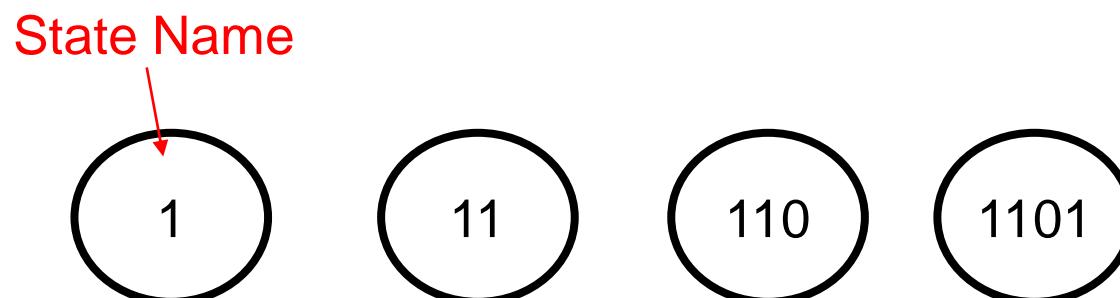- Moore: Output a function of the current state, and input
- Example detect every occurrence of “1101”




Mealy FSM

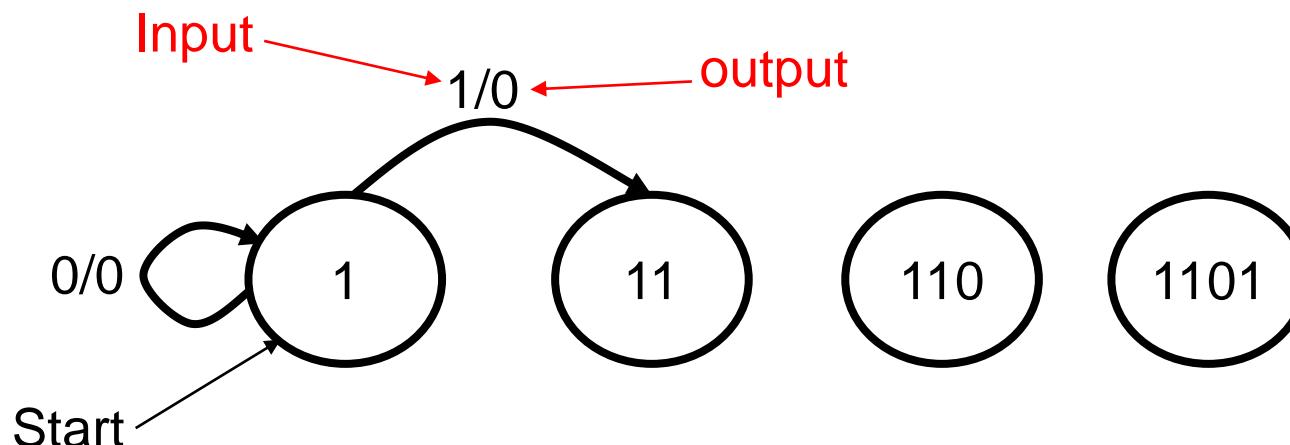- Moore: Output a function of the current state, and input
- Example detect every occurrence of “1101”




Mealy FSM

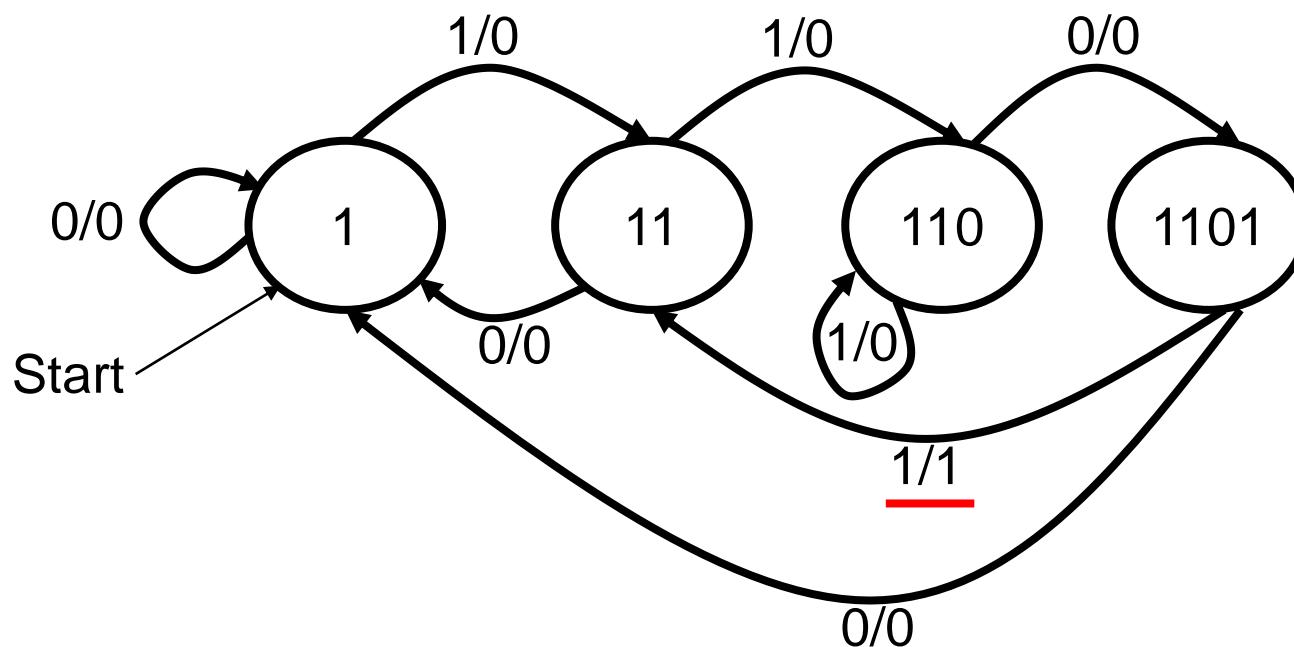- Mealy: Output a function of the current state, and input
- Example detect every occurrence of “1101”




FSM: General Circuit Architecture

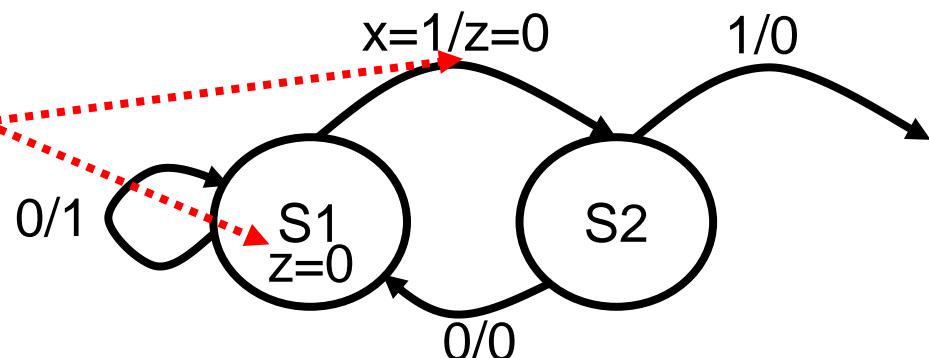- Let:
 - X be inputs
 - Z be outputs
 - $\text{State}(t)$ be the state of the FSM at the current time
 - $\text{State}(t+1)$ be the next state of the FSM
 - δ be the transition between states
- $\text{State}(t+1) = \delta(\text{State}(t), X)$
- Output
 - Moore: $Z(\text{State}(t))$
 - Mealy: $Z(\text{State}(t), X)$




FSM: General Circuit Architecture

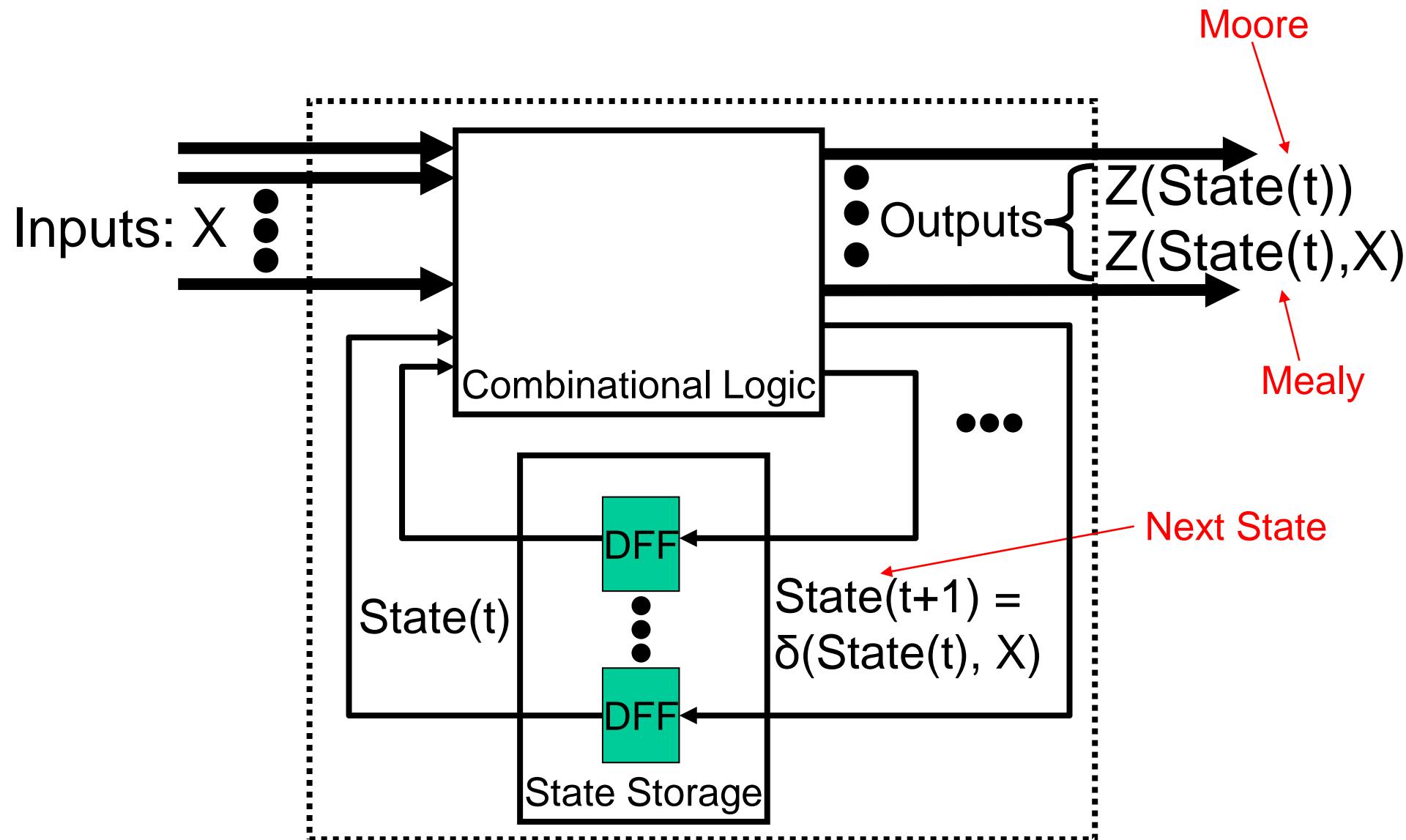

VHDL: IF and CASE constructs

- IF THEN ELSE can be mapped to a 2:1 Multiplexer (Mux)

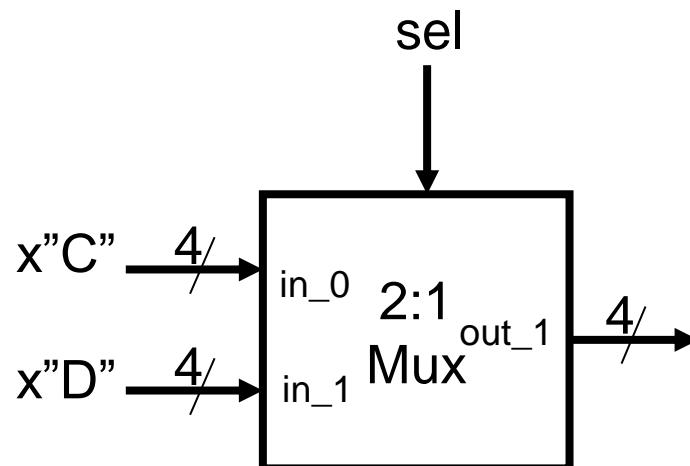
```
IF (sel = '0') THEN  
    out_1 <= in_0;  
ELSE  
    out_1 <= in_1  
END IF;
```



VHDL: IF and CASE constructs

- IF THEN ELSE can be mapped to a 2:1 Multiplexer (Mux)

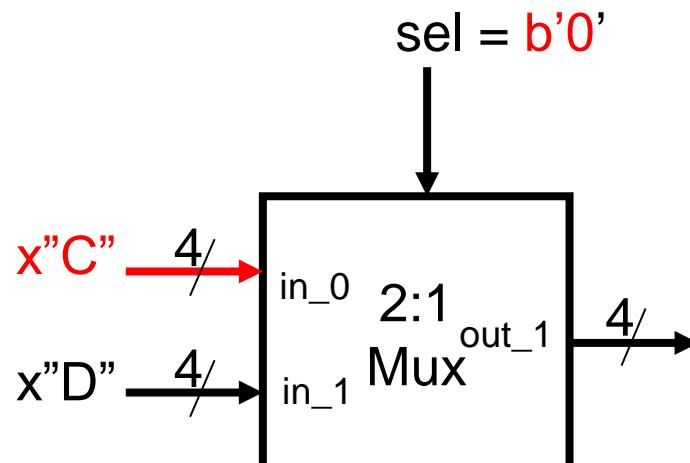
```
IF (sel = '0') THEN  
    out_1 <= in_0;  
ELSE  
    out_1 <= in_1  
END IF;
```



VHDL: IF and CASE constructs

- IF THEN ELSE can be mapped to a 2:1 Multiplexer (Mux)

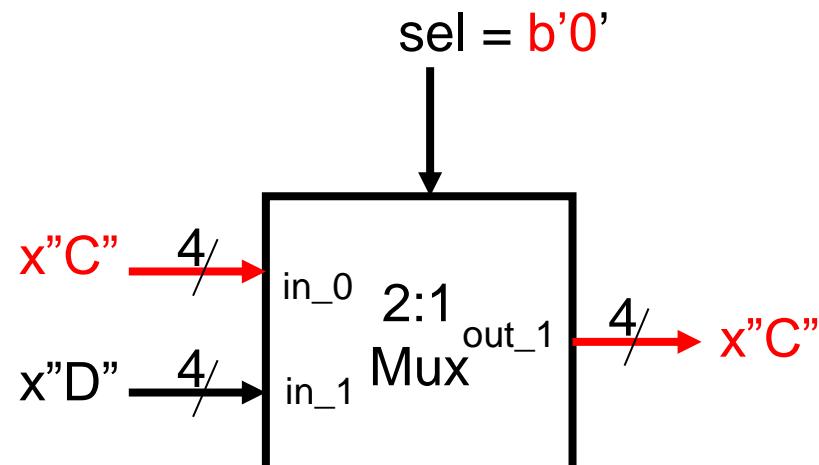
```
IF (sel = '0') THEN  
    out_1 <= in_0;  
ELSE  
    out_1 <= in_1  
END IF;
```



VHDL: IF and CASE constructs

- Mapping a CASE statement to a 4:1 Mux

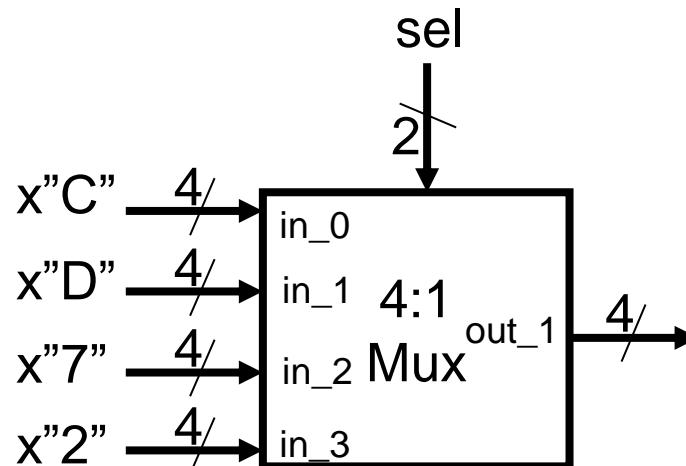
```
CASE sel is
  WHEN "00" =>
    out_1 <= in_0;
  WHEN "01" =>
    out_1 <= in_1;
  WHEN "10" =>
    out_1 <= in_2;
  WHEN "11" =>
    out_1 <= in_3
  WHEN OTHERS =>
    out_1 <= in_0;
END CASE;
```



VHDL: IF and CASE constructs

- Mapping a CASE statement to a 4:1 Mux

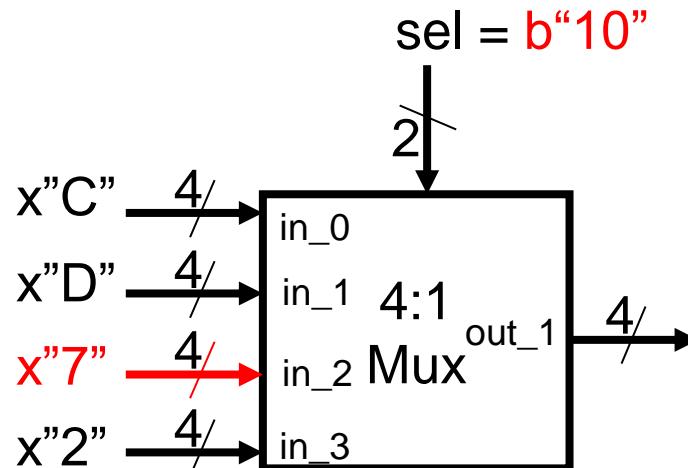
```
CASE sel is
  WHEN "00" =>
    out_1 <= in_0;
  WHEN "01" =>
    out_1 <= in_1;
  WHEN "10" =>
    out_1 <= in_2;
  WHEN "11" =>
    out_1 <= in_3;
  WHEN OTHERS =>
    out_1 <= in_0;
END CASE;
```



VHDL: IF and CASE constructs

- Mapping a CASE statement to a 4:1 Mux
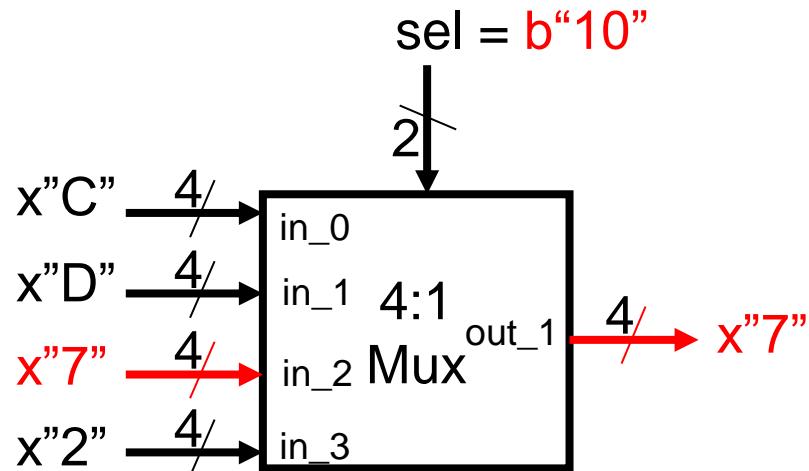
```
CASE sel is
  WHEN "00" =>
    out_1 <= in_0;
  WHEN "01" =>
    out_1 <= in_1;
  WHEN "10" =>
    out_1 <= in_2;
  WHEN "11" =>
    out_1 <= in_3;
  WHEN OTHERS =>
    out_1 <= in_0;
END CASE;
```




Why do we need others here?

VHDL: IF and CASE constructs

- Mapping an IF nested in CASE to hardware

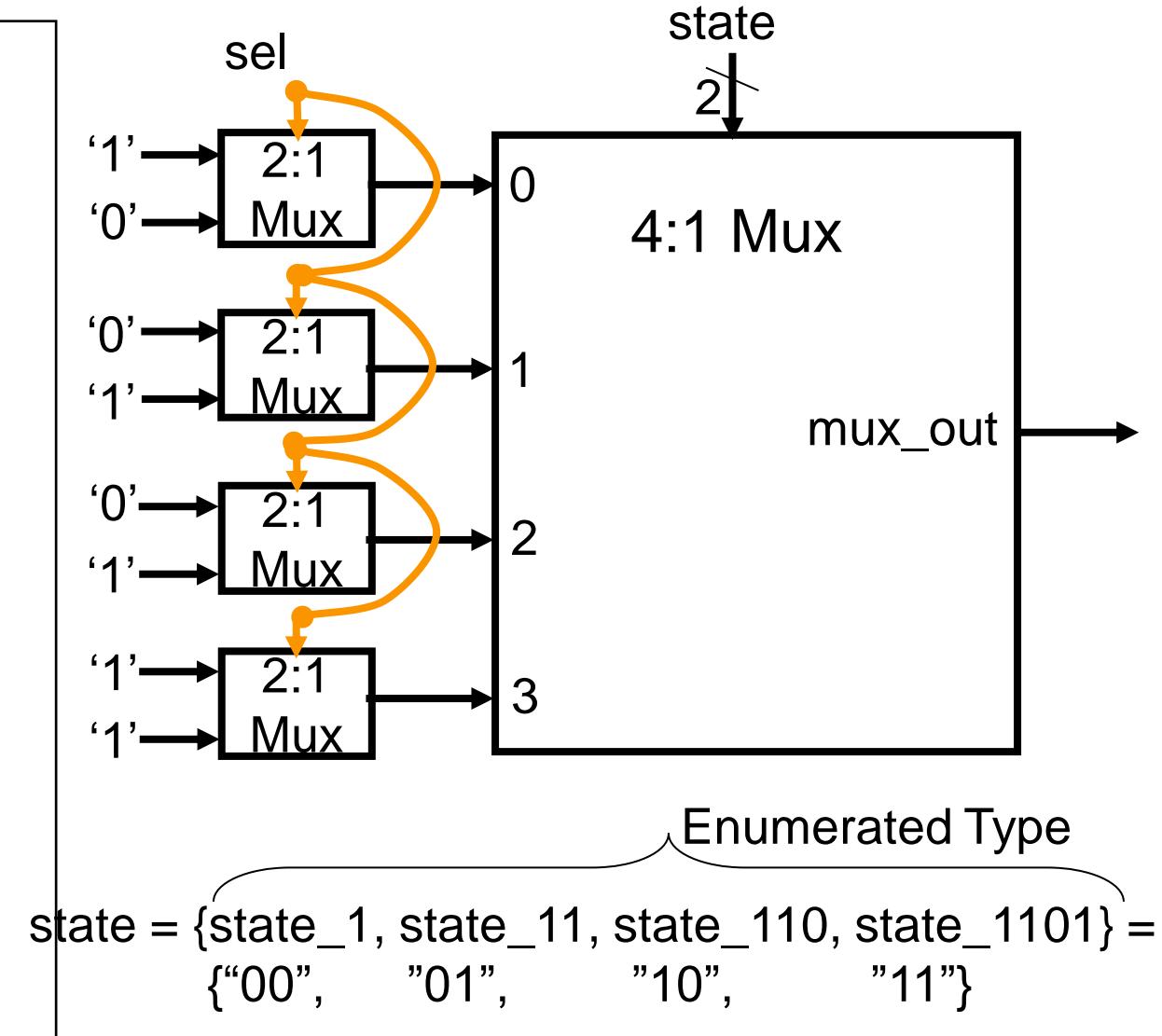
```
CASE state is
WHEN state_1 =>
  IF (sel = '0') THEN
    mux_out <= '1';
  ELSE
    mux_out <= '0';
  END IF;
WHEN state_11 =>
  -- similar code
WHEN state_110 =>
  IF (sel = '0') THEN
    mux_out <= '0';
  ELSE
    mux_out <= '1';
  END IF;
WHEN state_1101 =>
  --similar code
END CASE;
```



VHDL: IF and CASE constructs

- Mapping an IF nested in CASE to hardware

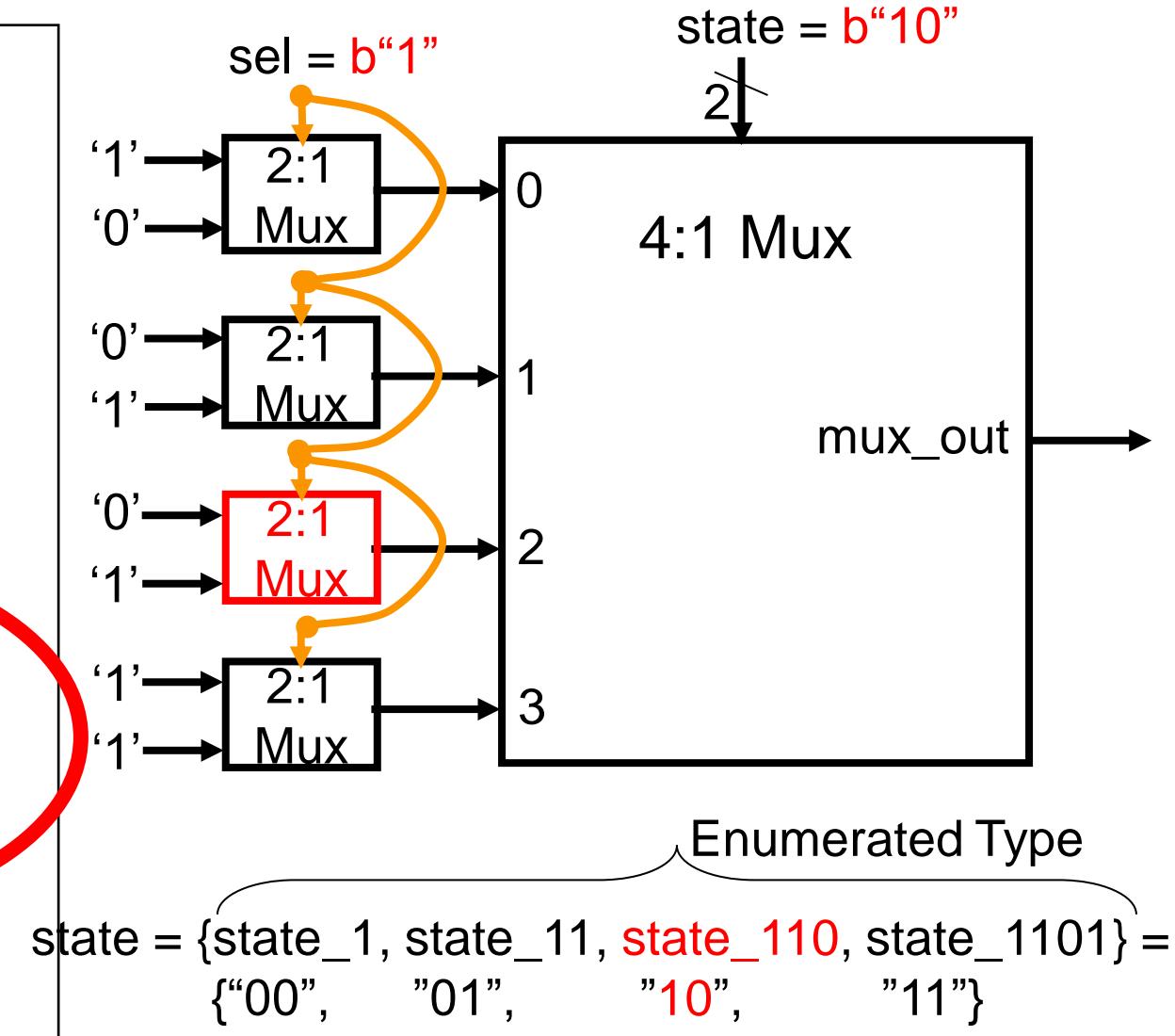
```
CASE state is
WHEN state_1 =>
  IF (sel = '0') THEN
    mux_out <= '1';
  ELSE
    mux_out <= '0';
  END IF;
WHEN state_11 =>
  -- similar code
WHEN state_110 =>
  IF (sel = '0') THEN
    mux_out <= '0';
  ELSE
    mux_out <= '1';
  END IF;
WHEN state_1101 =>
  --similar code
END CASE;
```




VHDL: IF and CASE constructs

- Mapping an IF nested in CASE to hardware
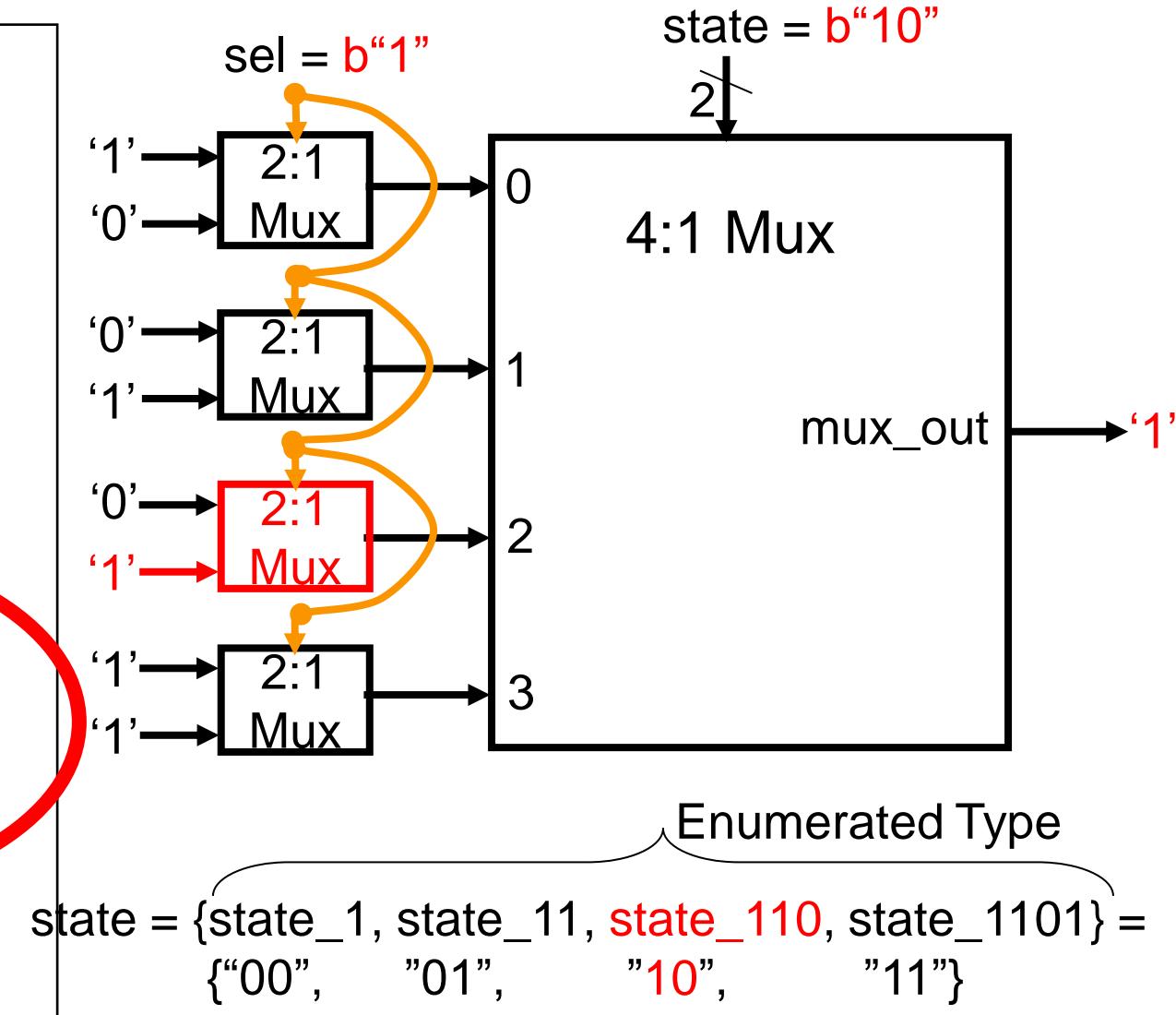
```
CASE state is
WHEN state_1 =>
  IF (sel = '0') THEN
    mux_out <= '1';
  ELSE
    mux_out <= '0';
  END IF;
WHEN state_11 =>
  -- similar code
WHEN state_110 =>
  IF (sel = '0') THEN
    mux_out <= '0';
  ELSE
    mux_out <= '1';
  END IF;
WHEN state_1101 =>
  --similar code
END CASE;
```




FSM: General Circuit Architecture

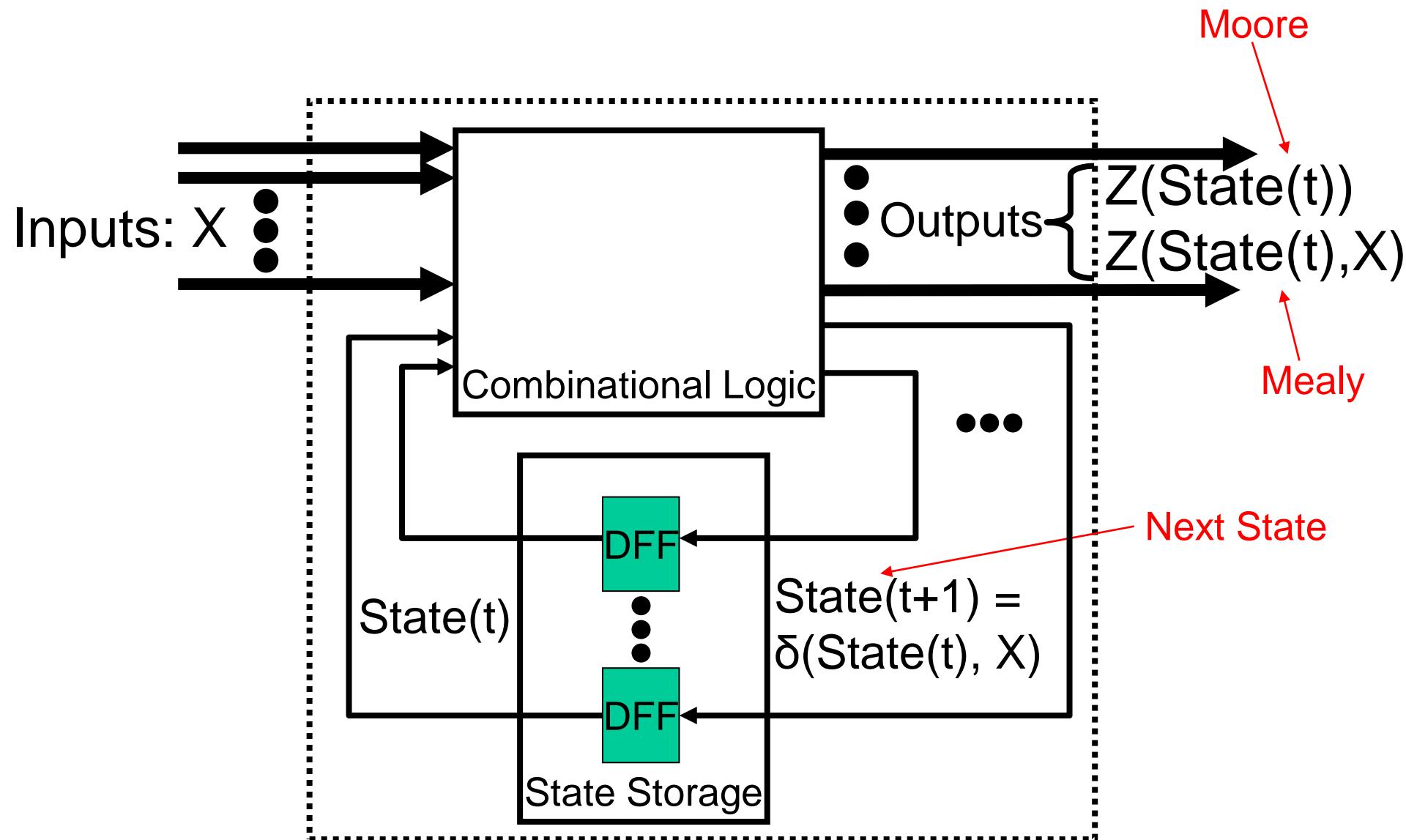

VHDL for Mealy (“1011”) Example

-- Store the “state”
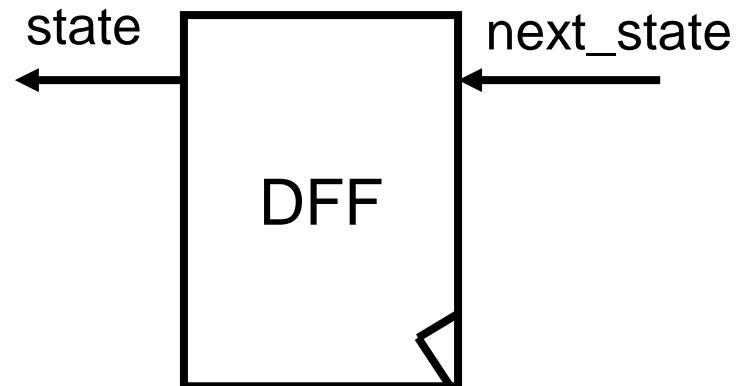
```
Update_State: process(clk)
begin
  if(clk'event and clk='1') then
    state <= next_state;
  end if;
end process Update_State;
```



VHDL for Mealy (“1011”) Example

-- Compute combinational logic

Combinational: process(x, state)

begin

case state is

when state_1 =>

if(x = '0') then
z <= '0';

next_state <= state_1;

else

z <= '0';

next_state <= state_11;

end if;

when state_11 =>

if(x = '0') then

z <= '0';

next_state <= state_1;


else

z <= '0';

next_state <= state_110 ;


end if;

Compute output
Compute next_state

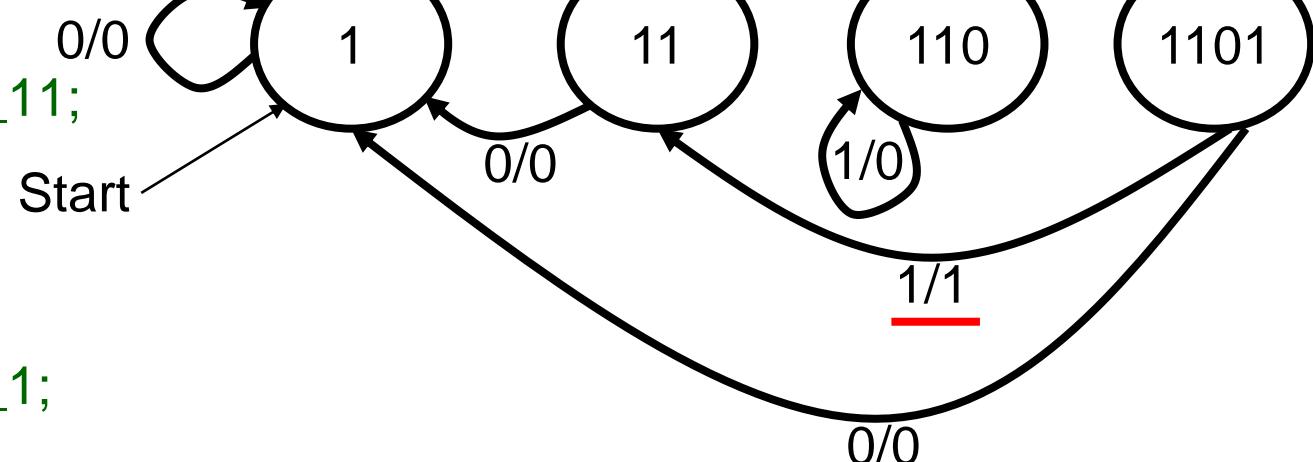

VHDL for Mealy (“1011”) Example
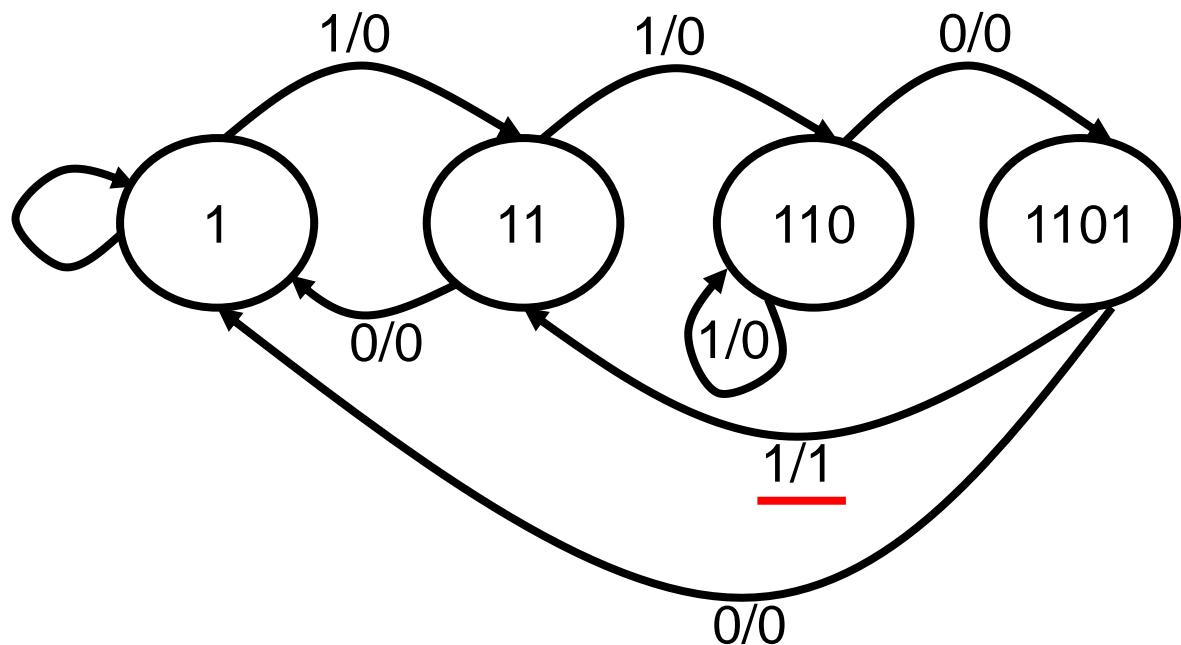
```
when state_110 =>
  if(x = '0') then
    z <= '0';
    next_state <= state_1101;
  else
    z <= '0';
    next_state <= state_110;
  end if;
when state_1101 =>
  if(x = '0') then
    z <= '0';
    next_state <= state_1;
  else
    z <= '1';
    next_state <= state_11;
  end if;
end case;
end process Combinational;
```



Network Processing Example: UDP


- UDP – User Datagram Protocol
 - Popular protocol for sending data over the internet (TCP is another popular protocol)
 - Typically encapsulated within IP (Internet Protocol)
 - UDP/IP
 - Gives no guarantee of delivery
 - Relies on application layer to implement reliability
 - Unlike TCP which has reliable delivery built in.
- Reference for more info on IP and UDP details
 - <http://www.freesoft.org/CIE/>
 - RCFs
 - Course

UDP/IP Packet Format

Note: flags 3 bits

UDP Protocol = 17

UDP length (bytes) =
UDP header+payload

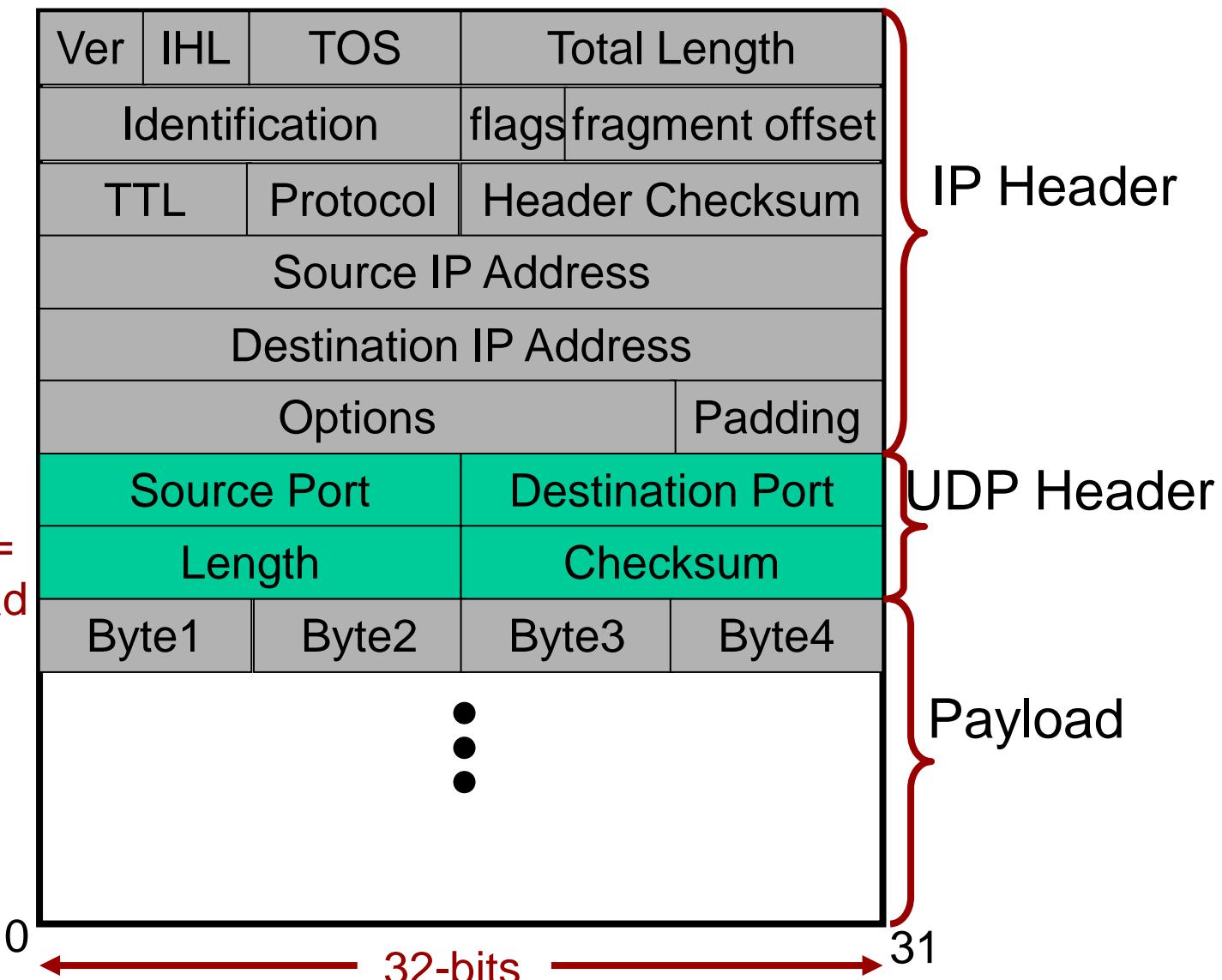


Example: Network Processing Tasks

- Raise an alert signal when the pattern “corn!” is detected
- Return the number of times “corn!” is detected
 - Place count value as the last byte of the payload

Streaming Network application (MP1)

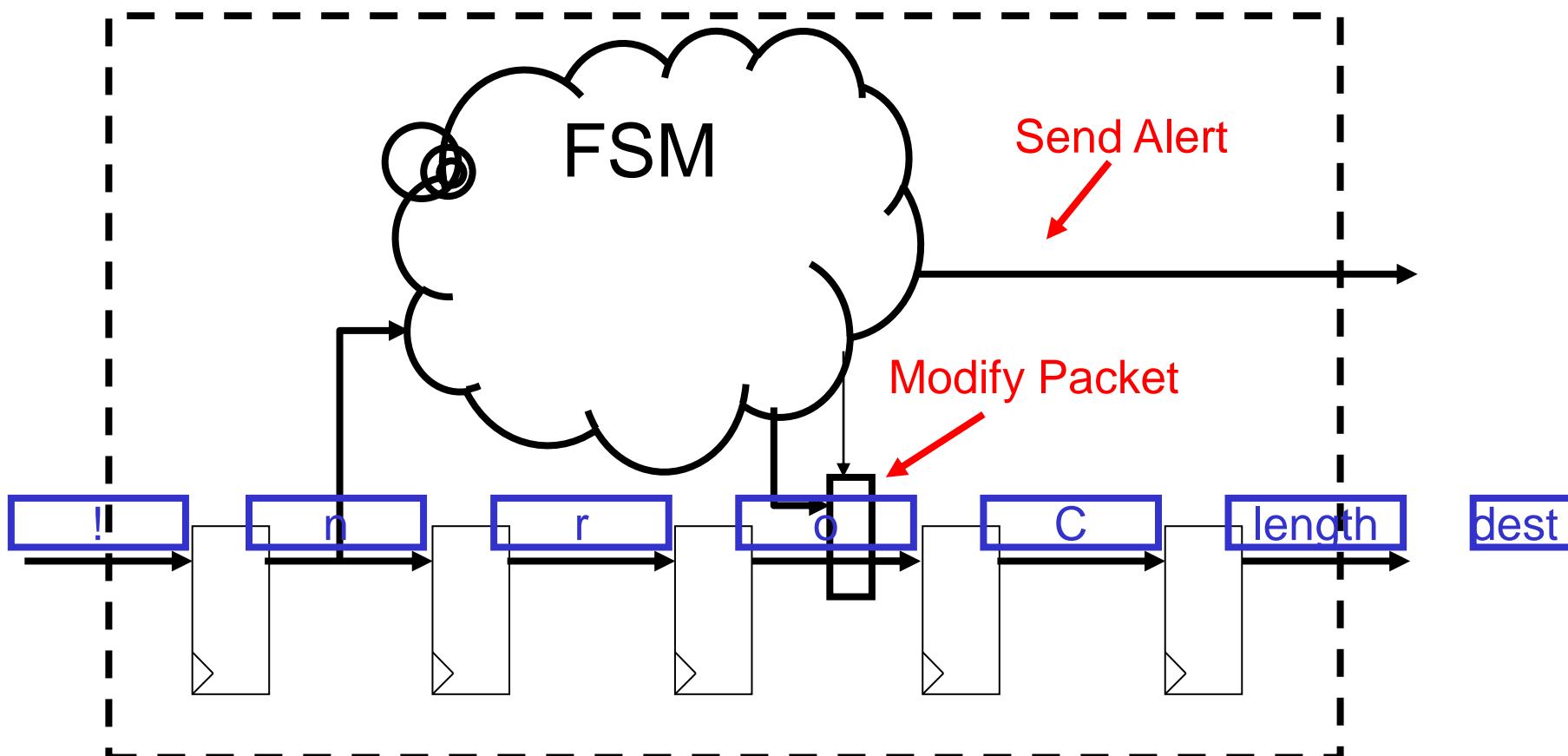
- Detect patterns in payload (e.g. “Corn!”)
- Place the number of detections in last byte of payload



Architecture


- Detect patterns in payload (e.g. “Corn!”)
- Place the number of detections in last byte of payload

Draw out logic, and data flow!!!

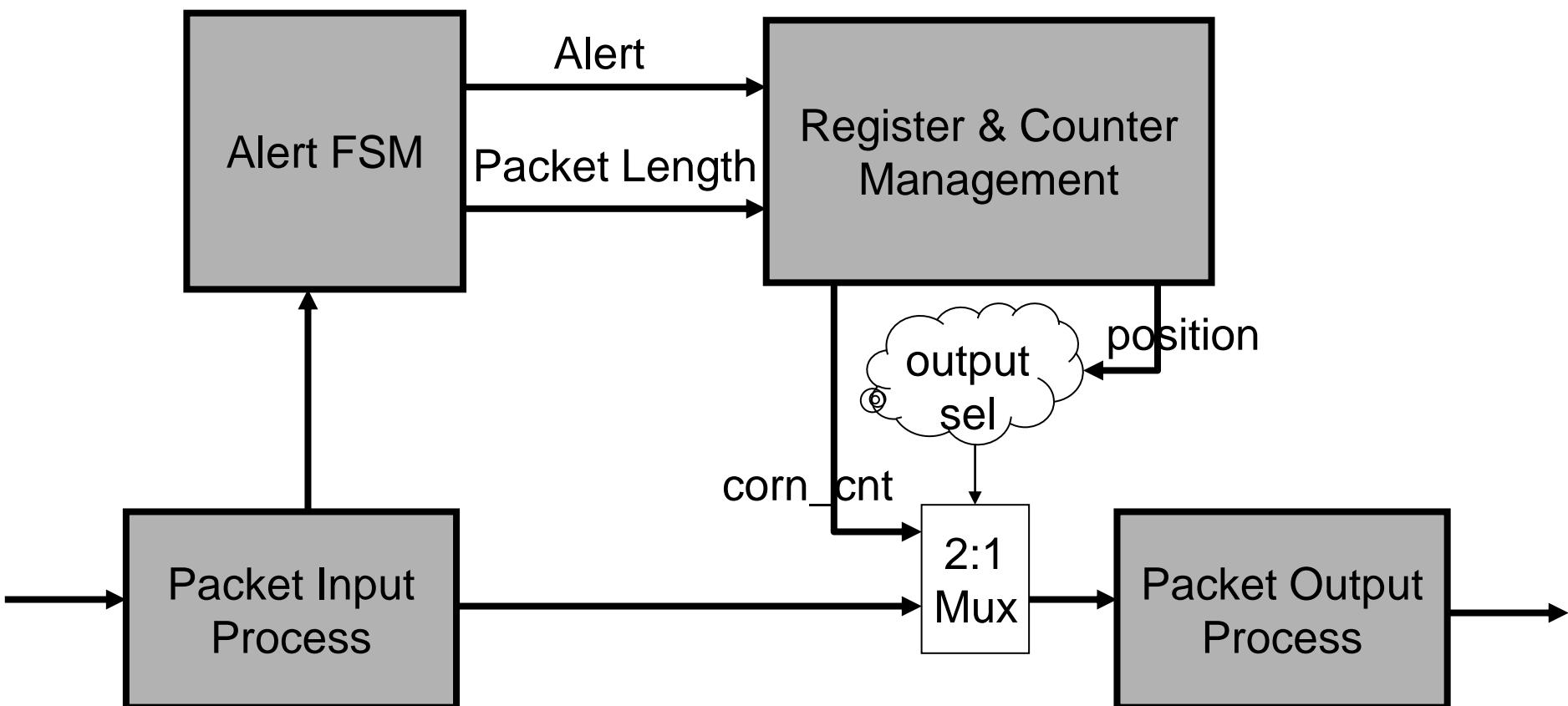


Architecture

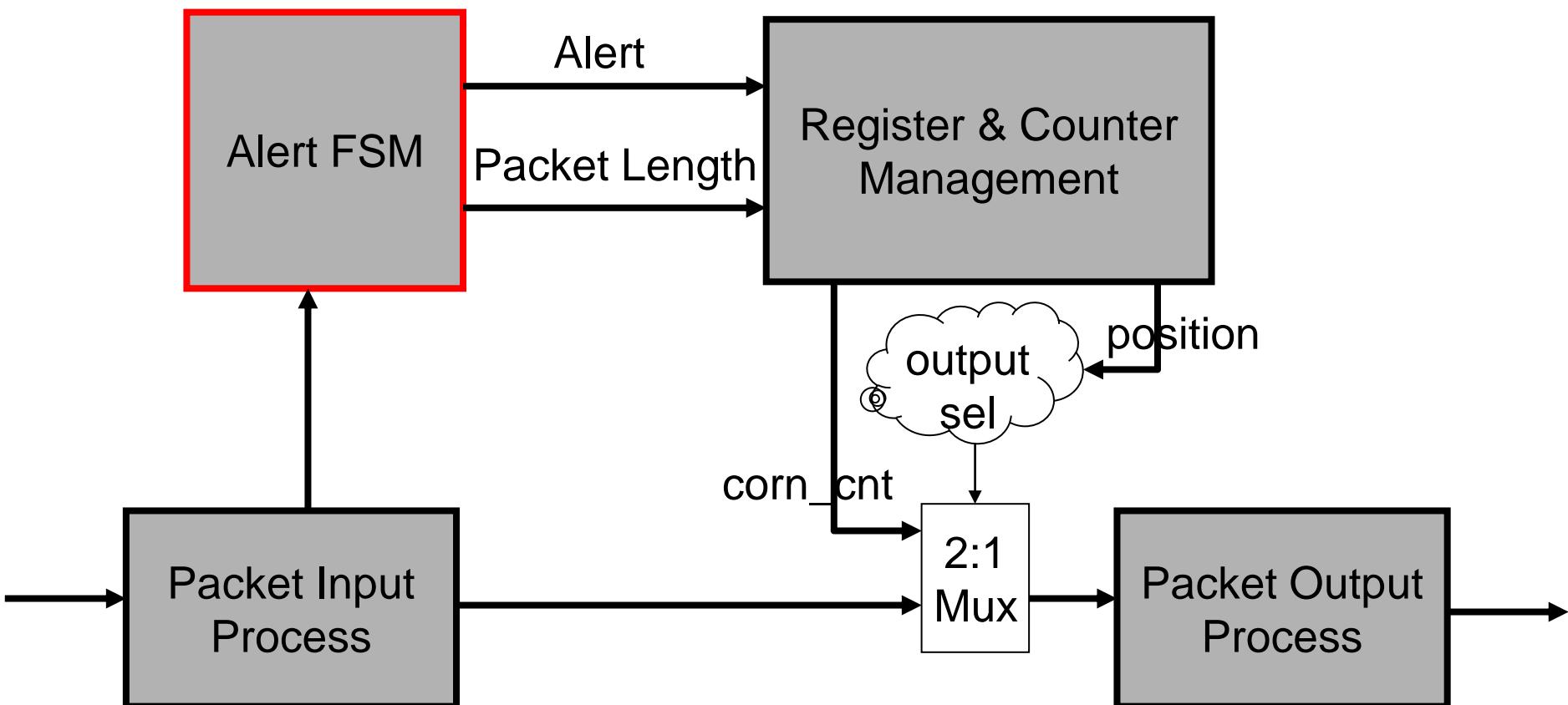- Detect patterns in payload (e.g. “Corn!”)
- Place the number of detections in last byte of payload




Alert FSM Design

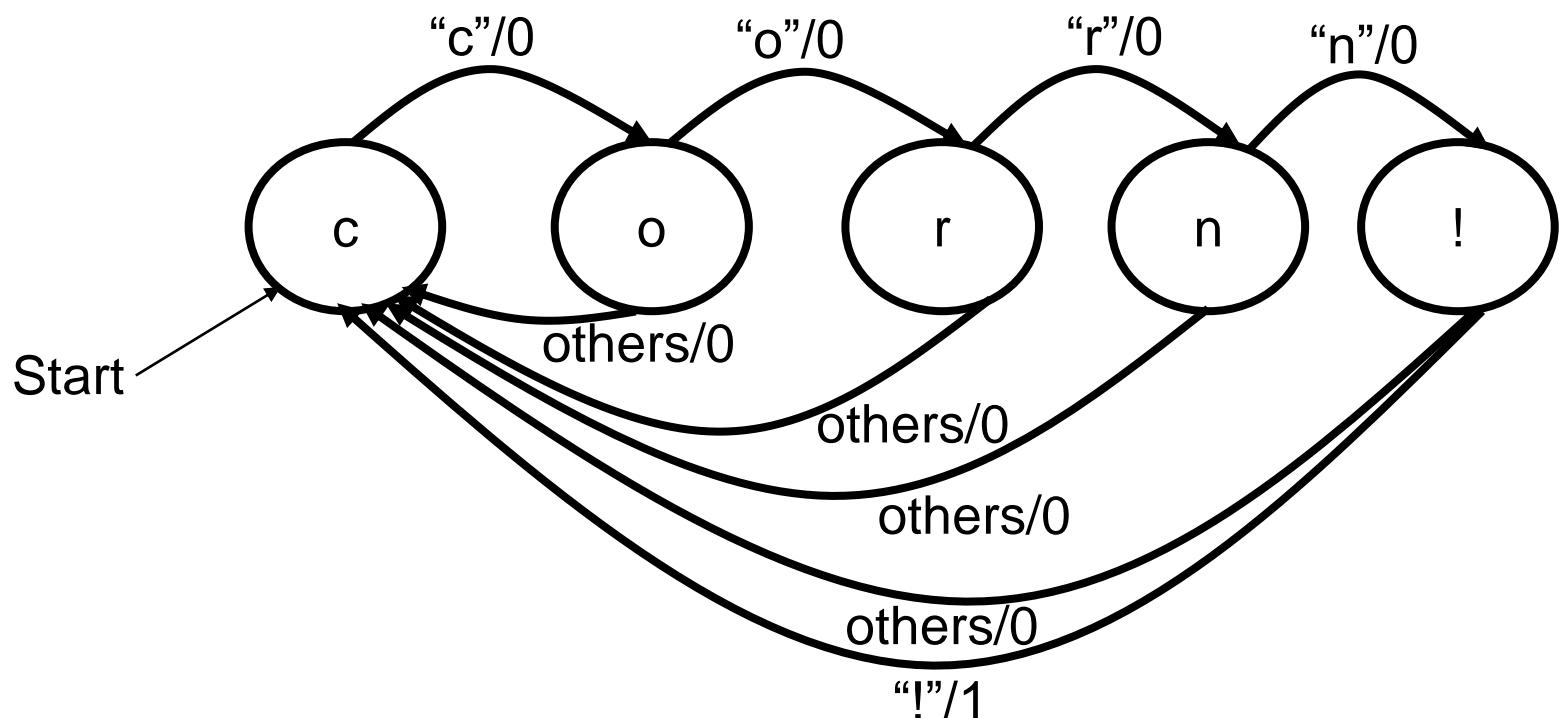- Alert signal when the pattern “corn!” is detected
 - $Z = \{\text{Alert}\}$




Alert FSM Design

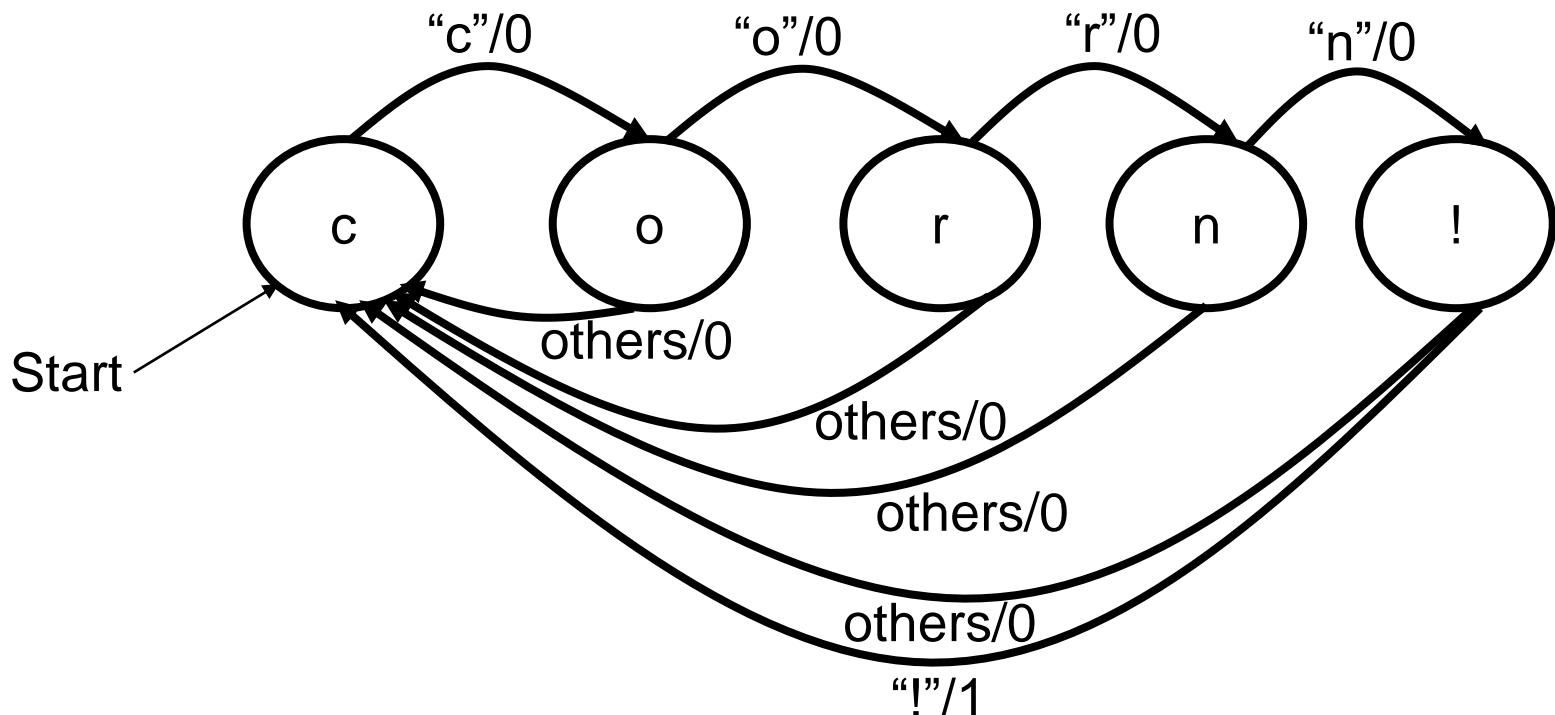- Alert signal when the pattern “corn!” is detected
- Output Packet’s Length
 - $Z = \{\text{Alert}, \text{length_vld}, \text{pack_length}\}$
 - $X = \{\text{vld}, \text{input}\}$: Note “?” is don’t care




Alert FSM Design

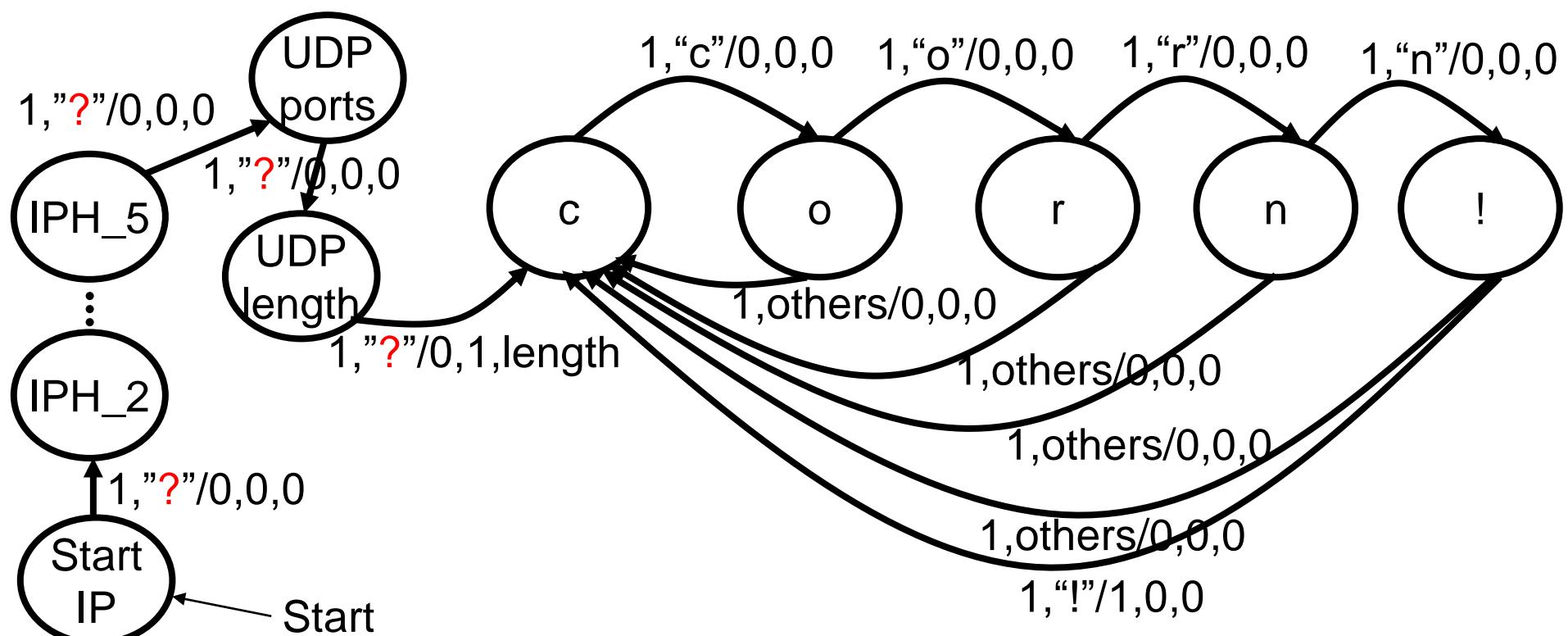- Alert signal when the pattern “corn!” is detected
- Output Packet’s Length
 - $Z = \{\text{Alert}, \text{length_vld}, \text{pack_length}\}$
 - $X = \{\text{vld}, \text{input}\}$: Note “?” is don’t care



Architecture

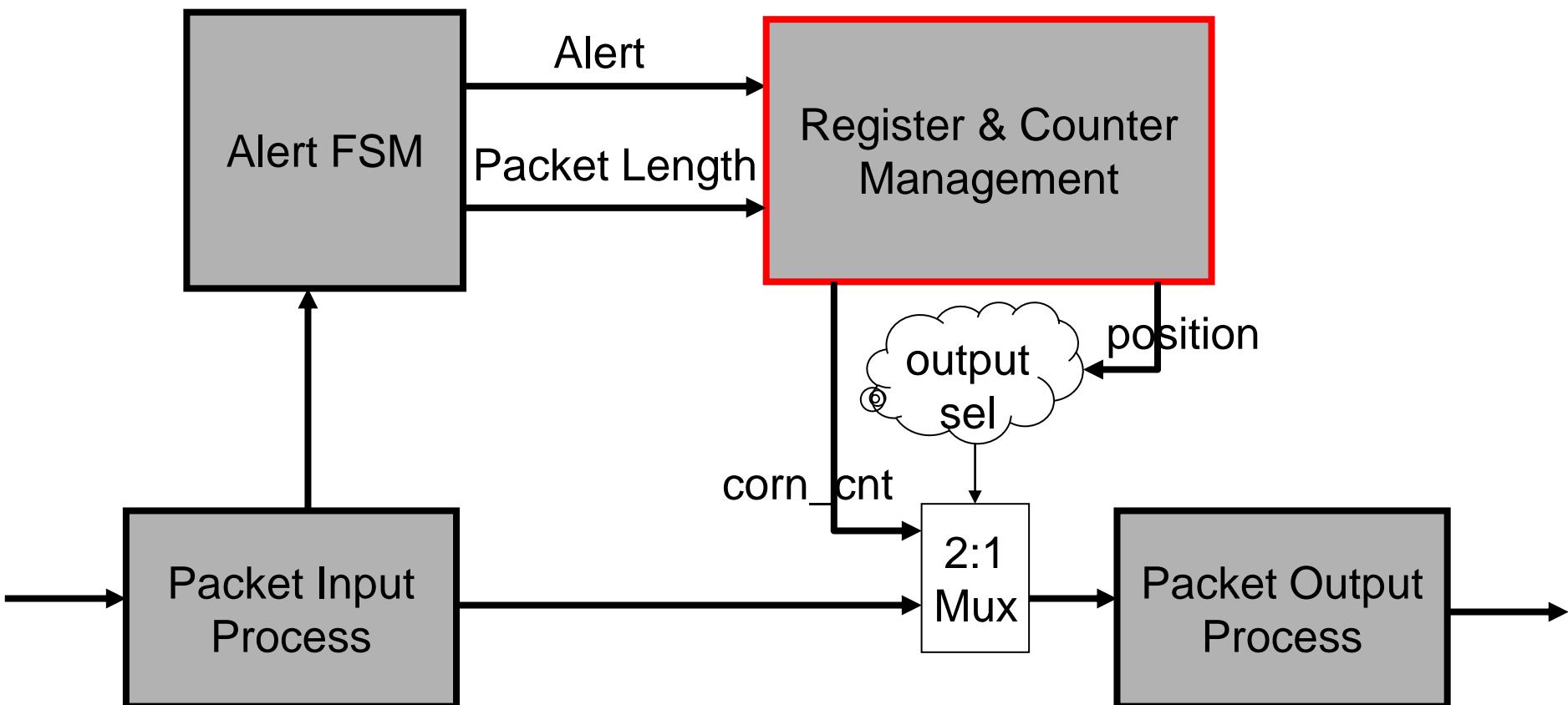
- Detect patterns in payload (e.g. “Corn!”)
- Place the number of detections in last byte of payload



Register & Counter Manager

- Register & Counter Components
- Design of Manager



Register and Counter Components

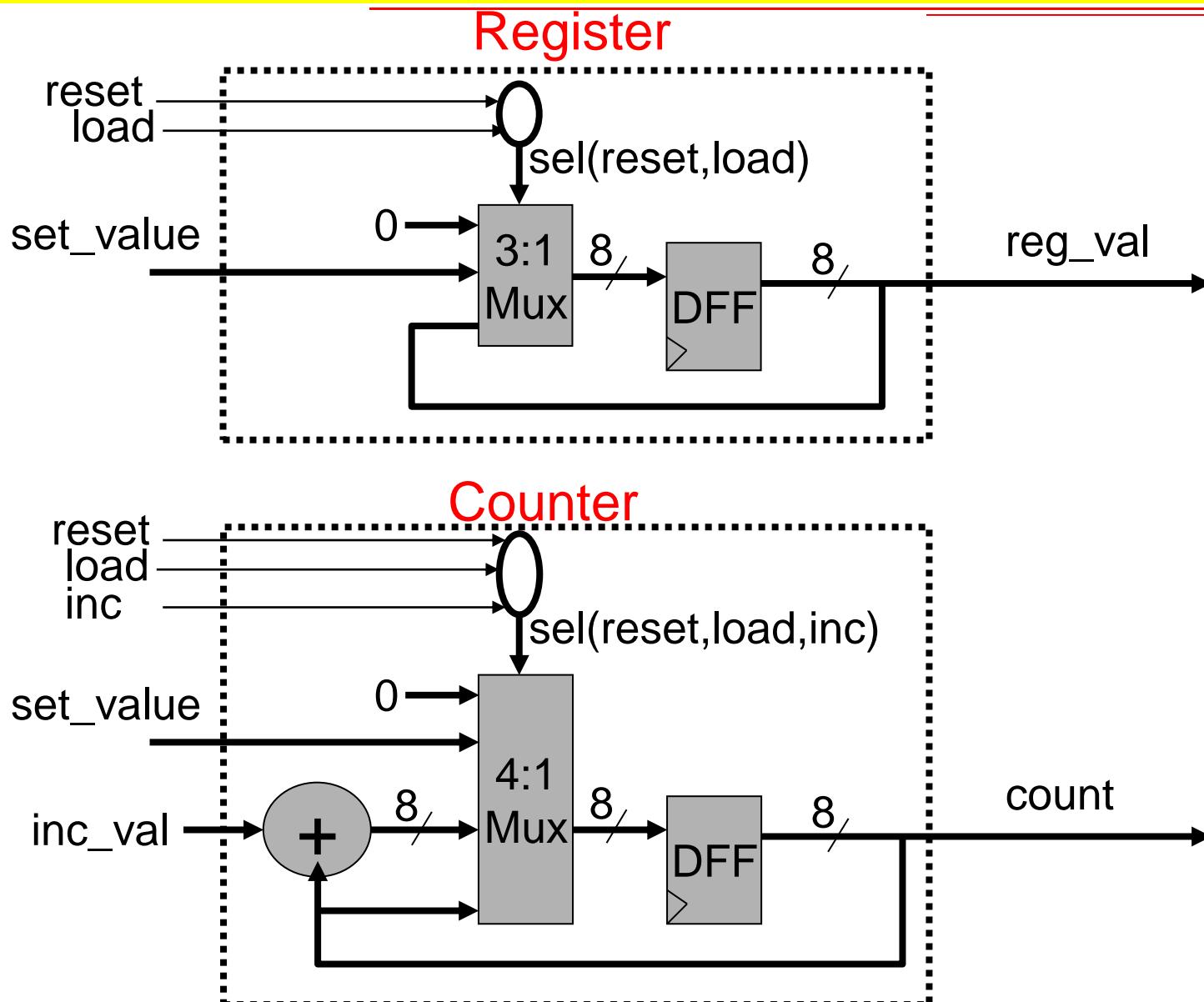

Practice: Write VHDL(process for each)


```
Name : process(clk)
begin
if(clk'event and clk='1') then
    logic here
end if;
end process Name
```

```
CASE sel is
WHEN "00" | "11"=>
    out_1 <= in_0;
WHEN "01" =>
    out_1 <= in_1;
    .
    .
    .
WHEN OTHERS =>
    out_1 <= in_0;
END CASE;
```

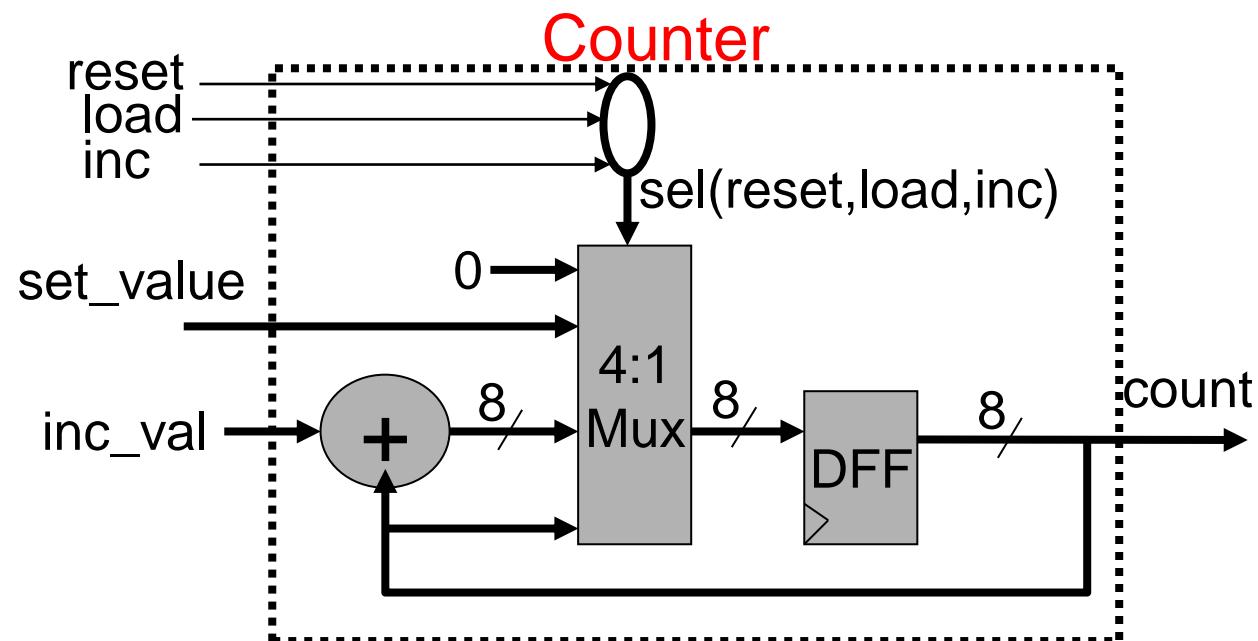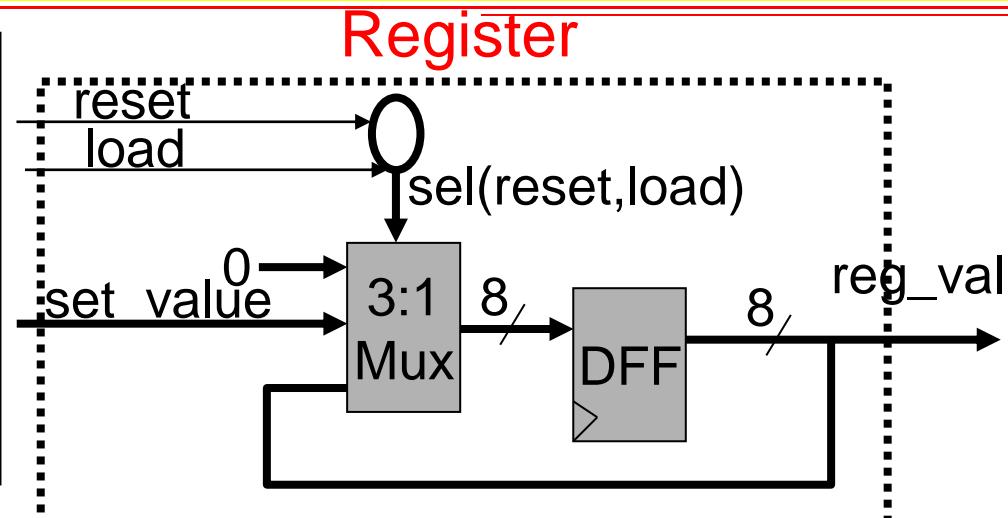

Register VHDL


```
Name : process(clk)
begin
if(clk'event and clk='1') then
CASE reset&load is
WHEN "10" | "11" =>
reg_val <= 0;
WHEN "01" =>
reg_val <= set_value;
WHEN OTHERS =>
reg_val <= reg_val;
END CASE;
end if;
end process Name
```

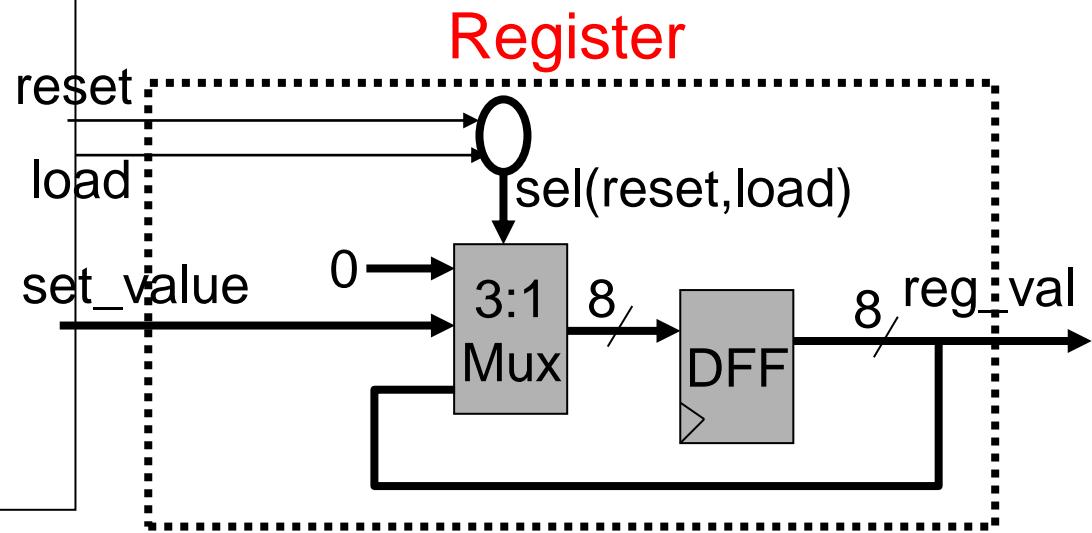

Register VHDL


```
Name : process(clk)
begin
if(clk'event and clk='1') then
CASE sel is
WHEN "10" | "11" =>
reg_val <= 0;
WHEN "01" =>
reg_val <= set_value;
WHEN OTHERS =>
reg_val <= reg_val;
END CASE;
end if;
end process Name

sel <= reset&load;
```

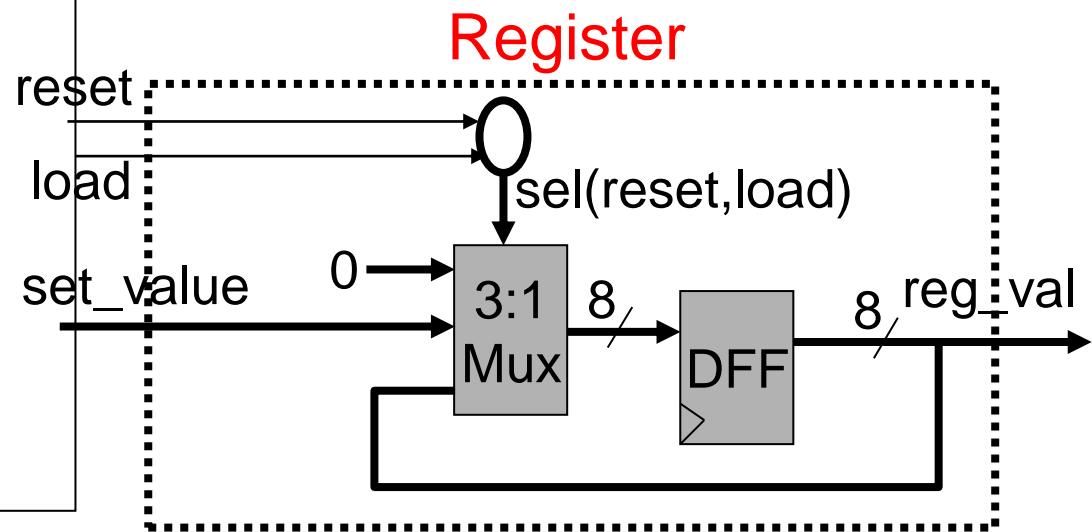


Counter VHDL

```
Name : process(clk)
begin
if(clk'event and clk='1') then
  CASE reset&load&inc is
    WHEN "100" | "101" |
      "110" | "111" =>
      count <= 0;
    WHEN "010" | "011" =>
      count <= set_value;
    WHEN "001" =>
      count <= count + inc_val;
    WHEN OTHERS =>
      count <= count;
  END CASE;
end if;
end process Name
```

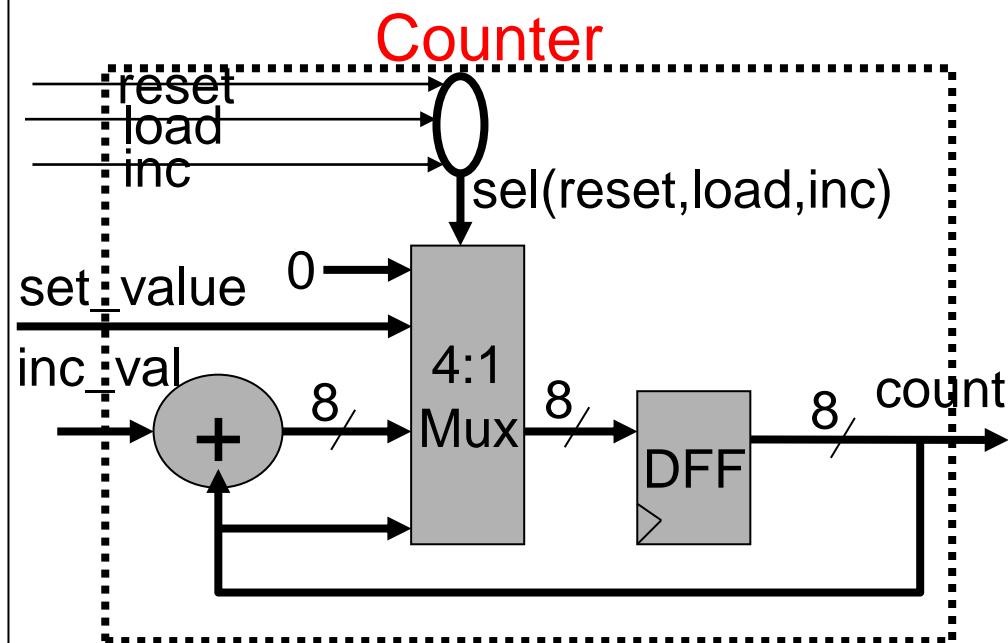


Counter VHDL

```
Name : process(clk)
begin
if(clk'event and clk='1') then
  CASE sel is
    WHEN "100" | "101" |
      "110" | "111" =>
      count <= 0;
    WHEN "010" | "011" =>
      count <= set_value;
    WHEN "001" =>
      count <= count + inc_val;
    WHEN OTHERS =>
      count <= count;
  END CASE;
end if;
end process Name
sel <= reset&load&inc;
```

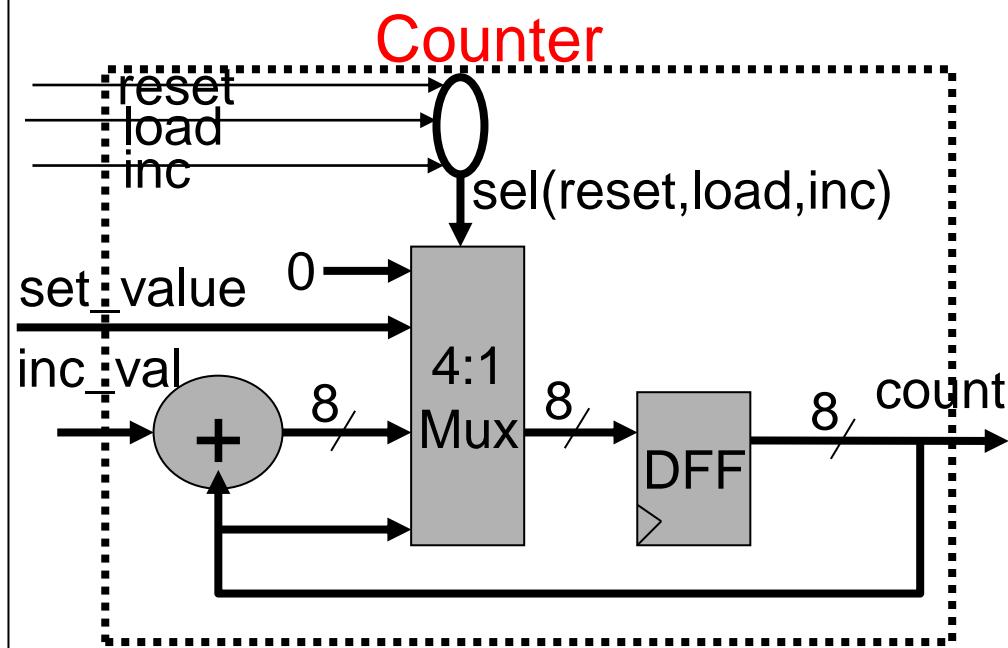


Architecture

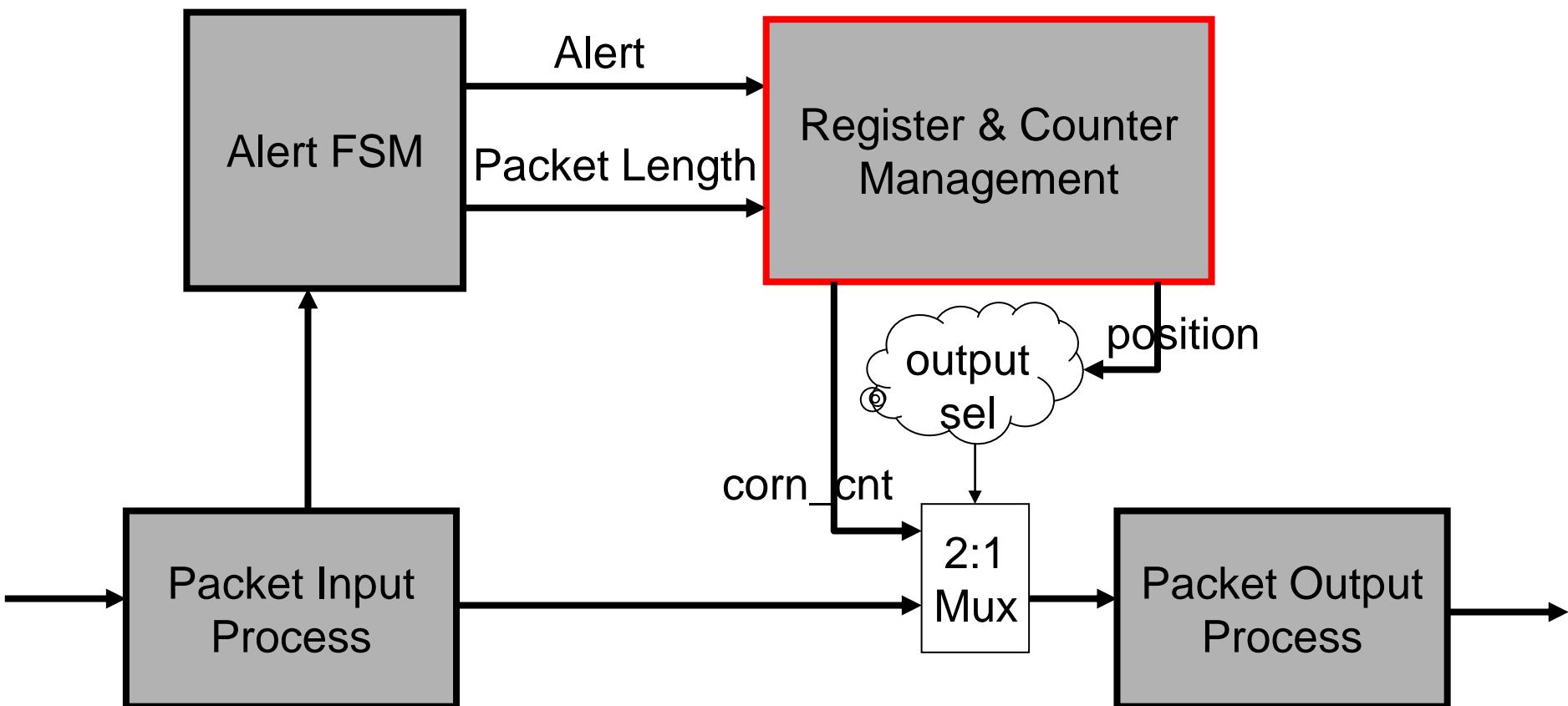- Detect patterns in payload (e.g. “Corn!”)
- Place the number of detections in last byte of payload



Architecture

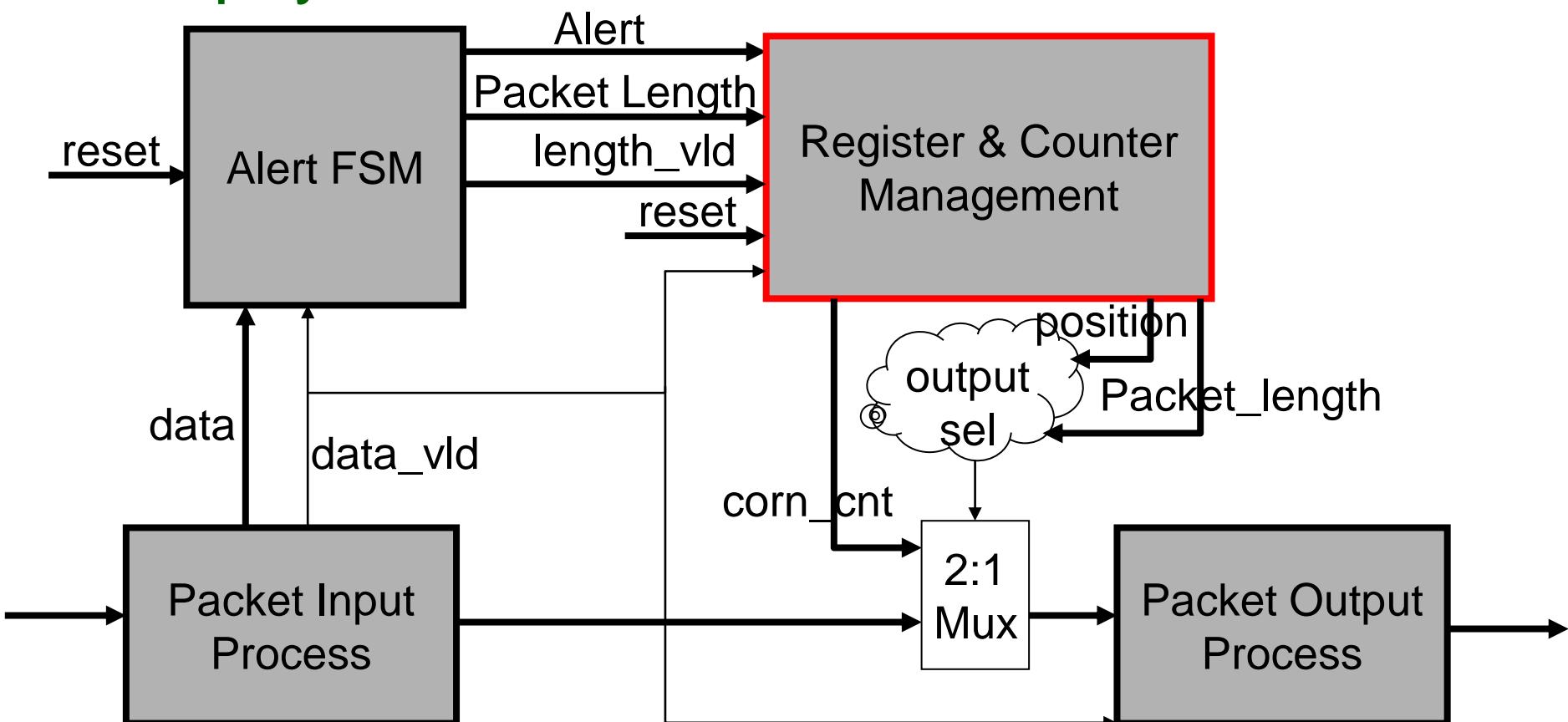
- Detect patterns in payload (e.g. “Corn!”)
- Place the number of detections in last byte of payload




Register and Counter Manager



Register and Counter Manager

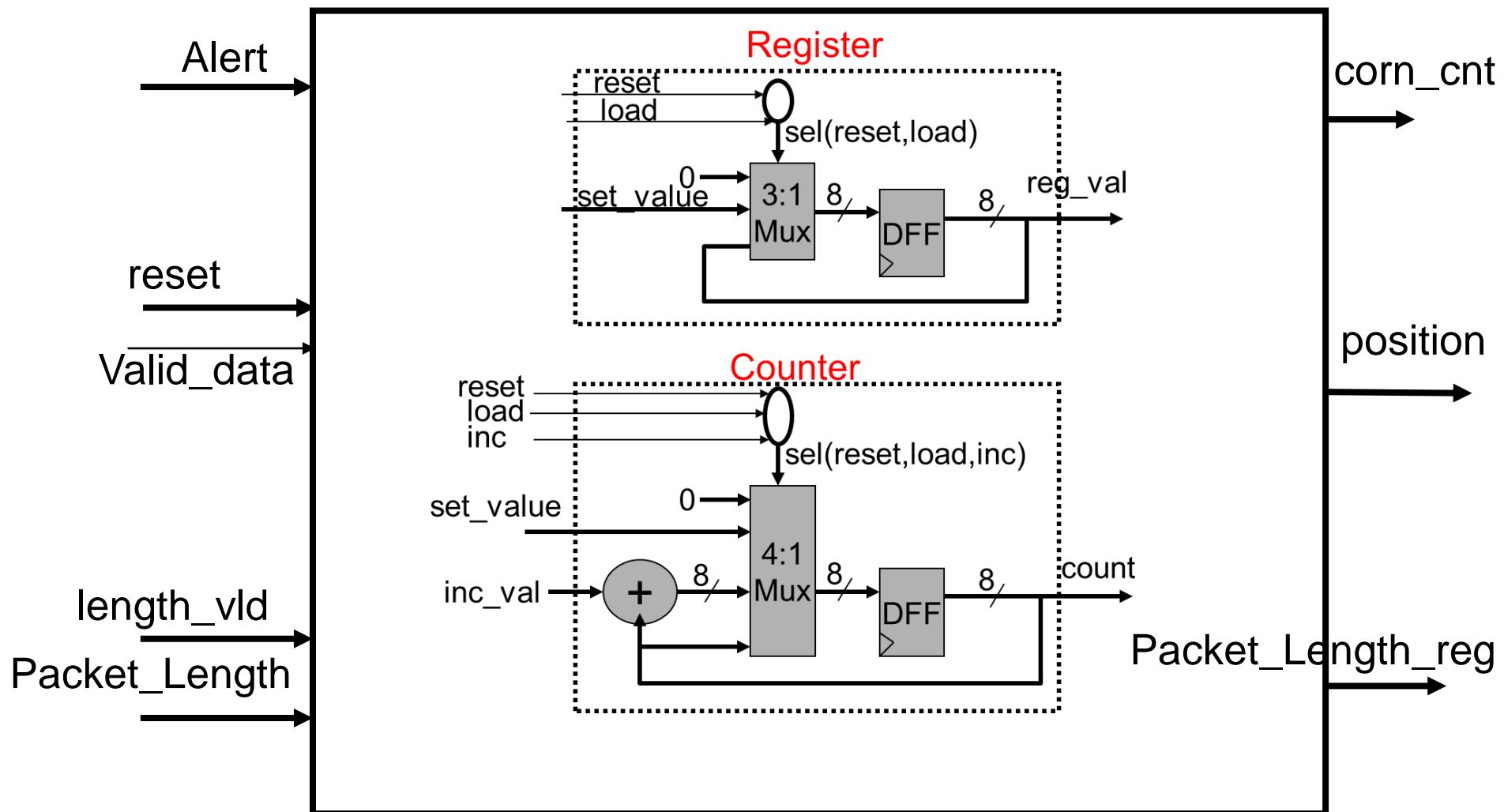


Register and Counter Manger

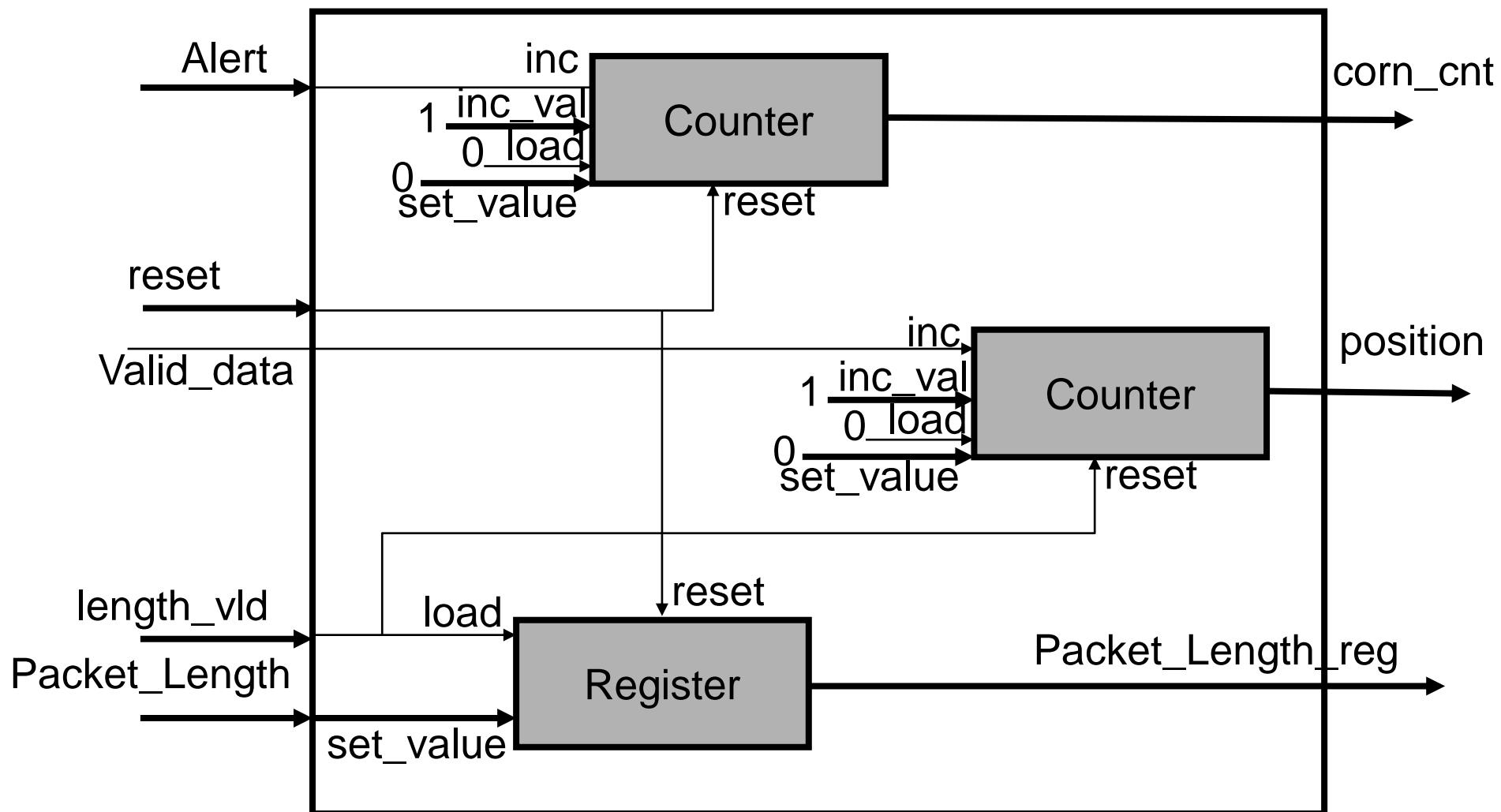


Architecture

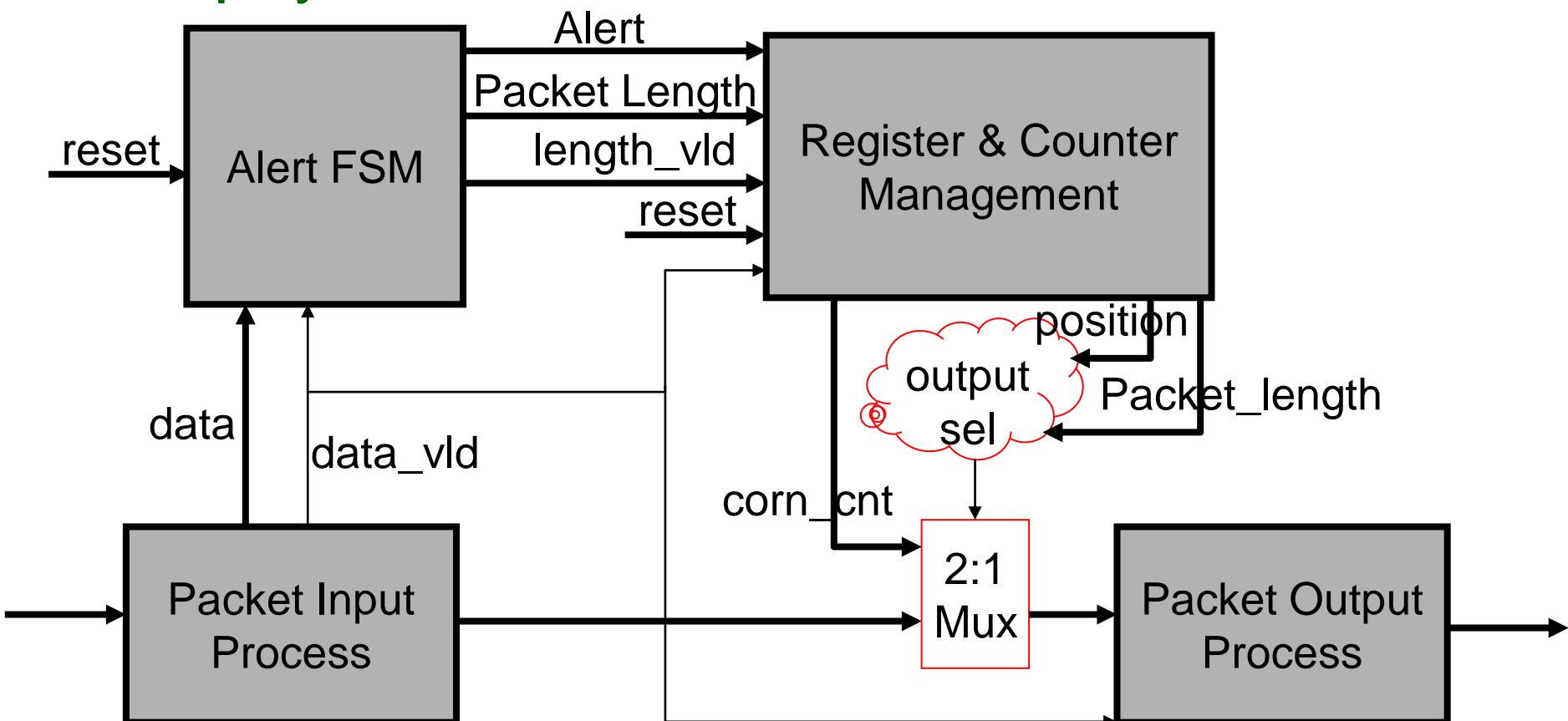- Detect patterns in payload (e.g. “Corn!”)
- Place the number of detections in last byte of payload




Output sel

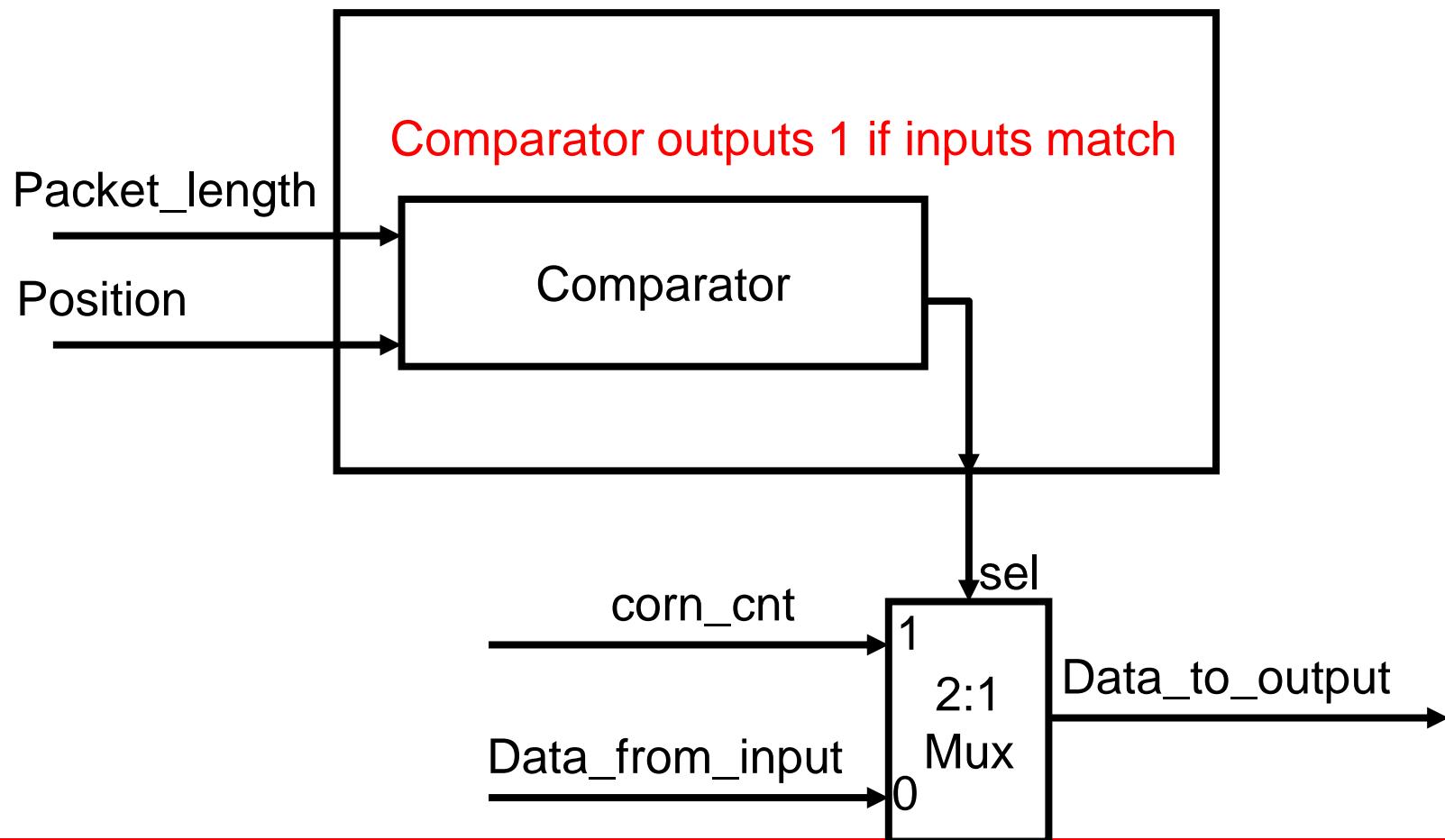

Output sel: VHDL


NOT in a process!
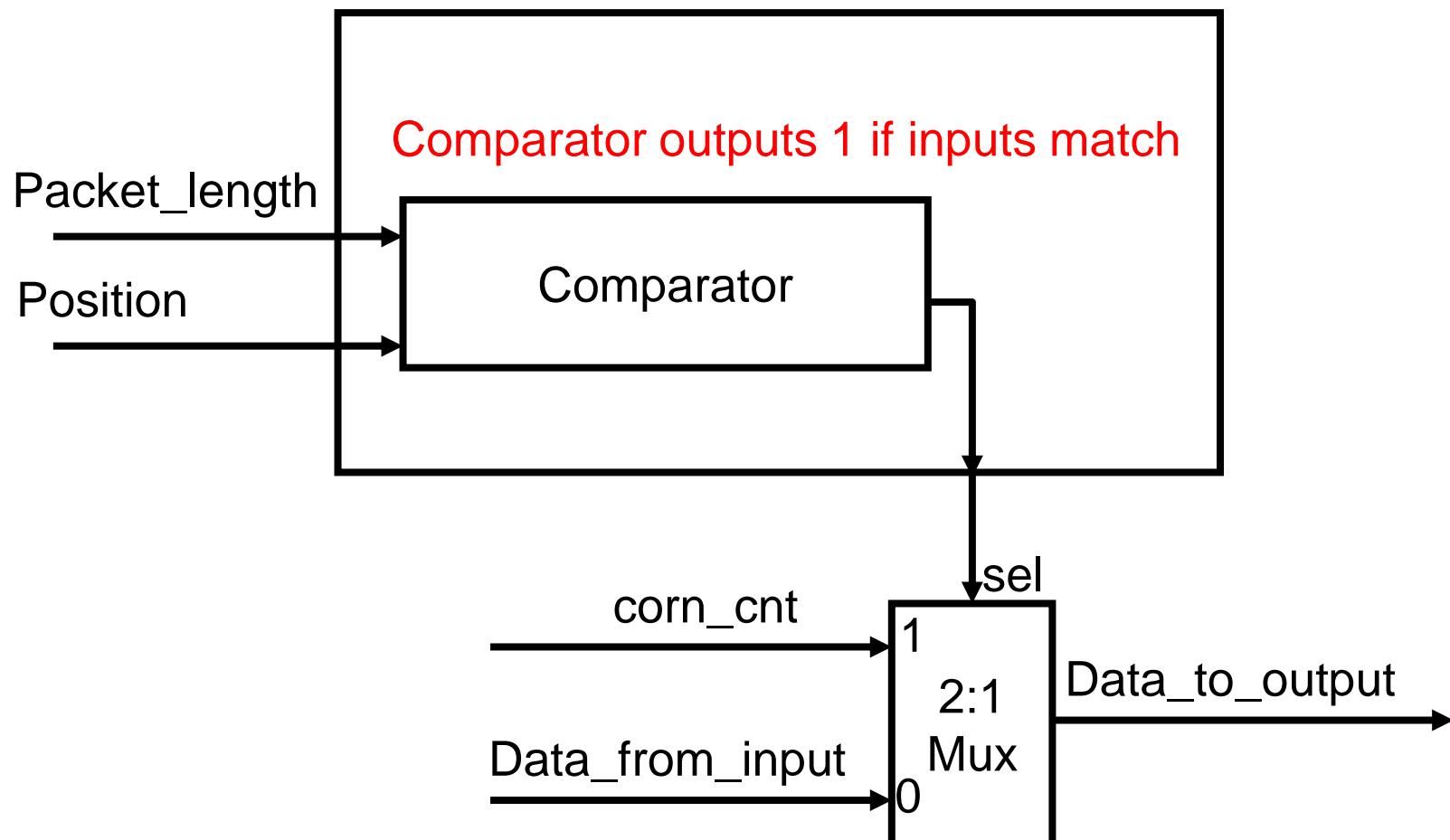
```
Data_to_output <= corn_cnt when (Packet_length = Position)  
else Data_from_input
```




Architecture

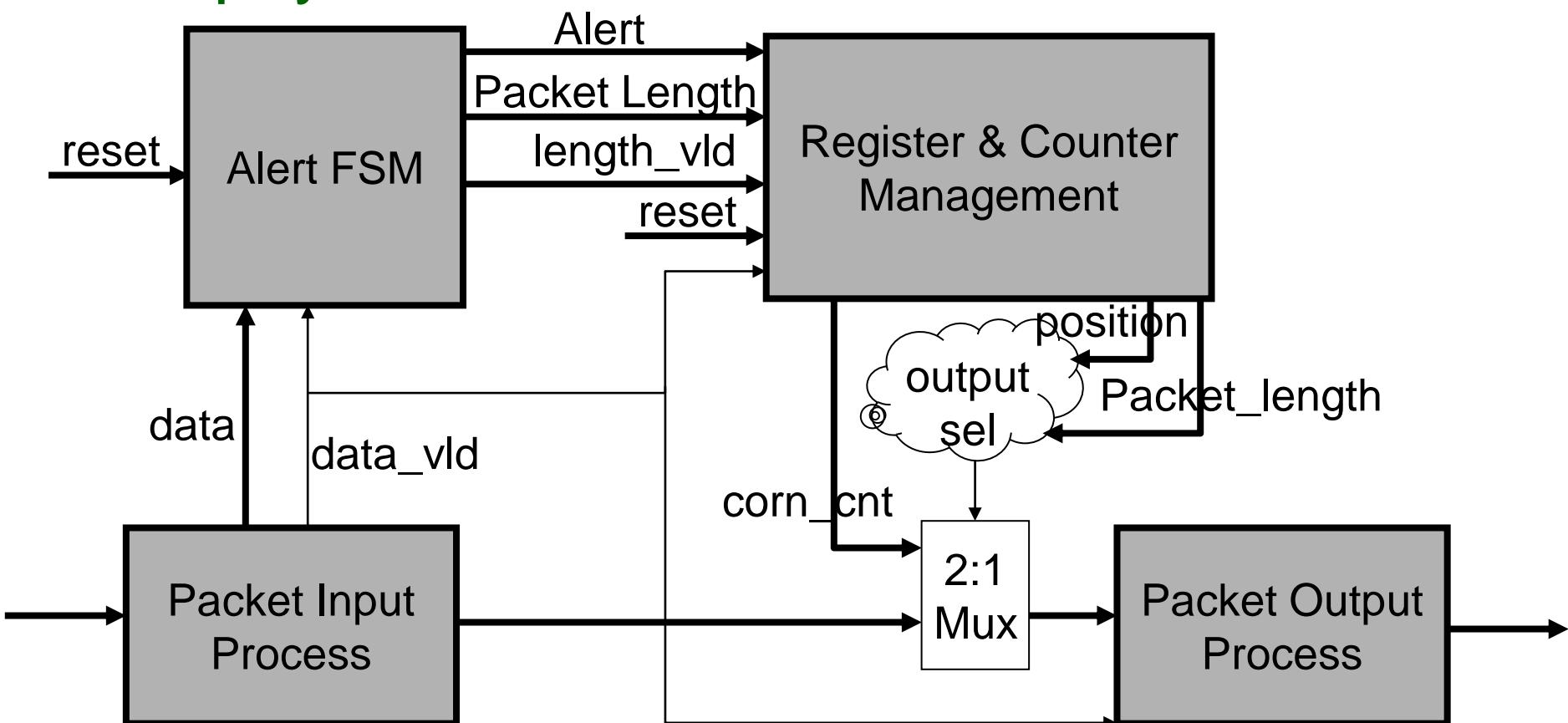- Detect patterns in payload (e.g. “Corn!”)
- Place the number of detections in last byte of payload




Multiple Characters per Clock

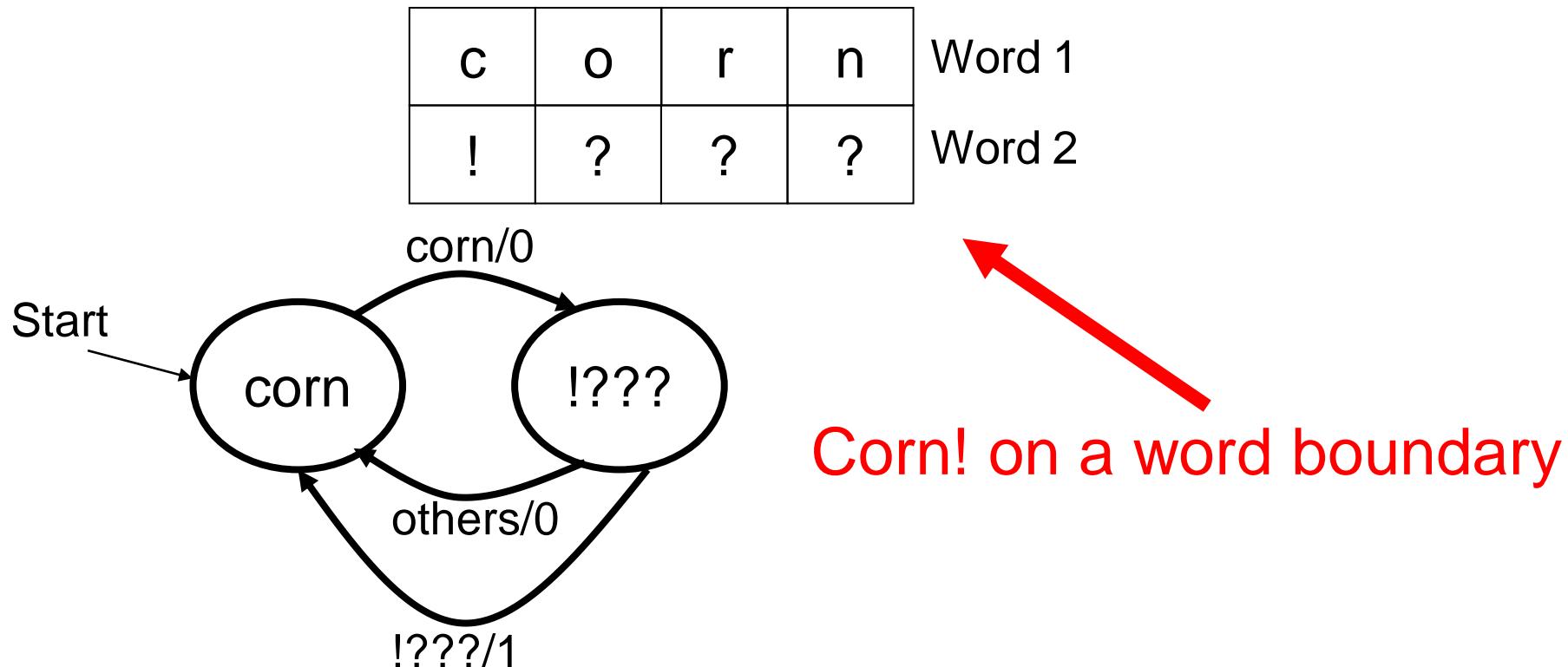- Network input stream typically 32-bit words
 - 4 8-bit characters per word.
- corn! Example




Multiple Characters per Clock

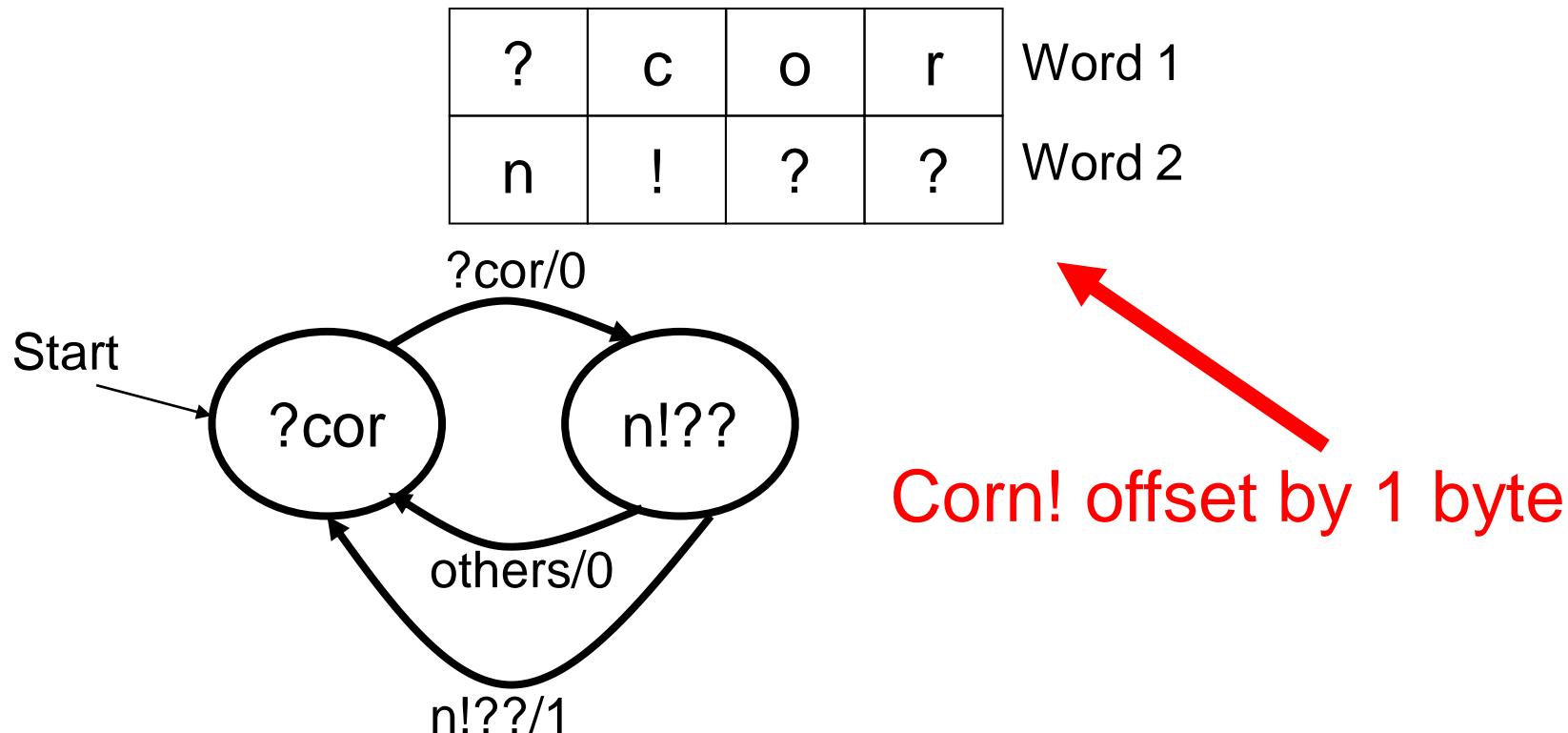- Network input stream typically 32-bit words
 - 4 8-bit characters per word.
- corn! Example




Multiple Characters per Clock

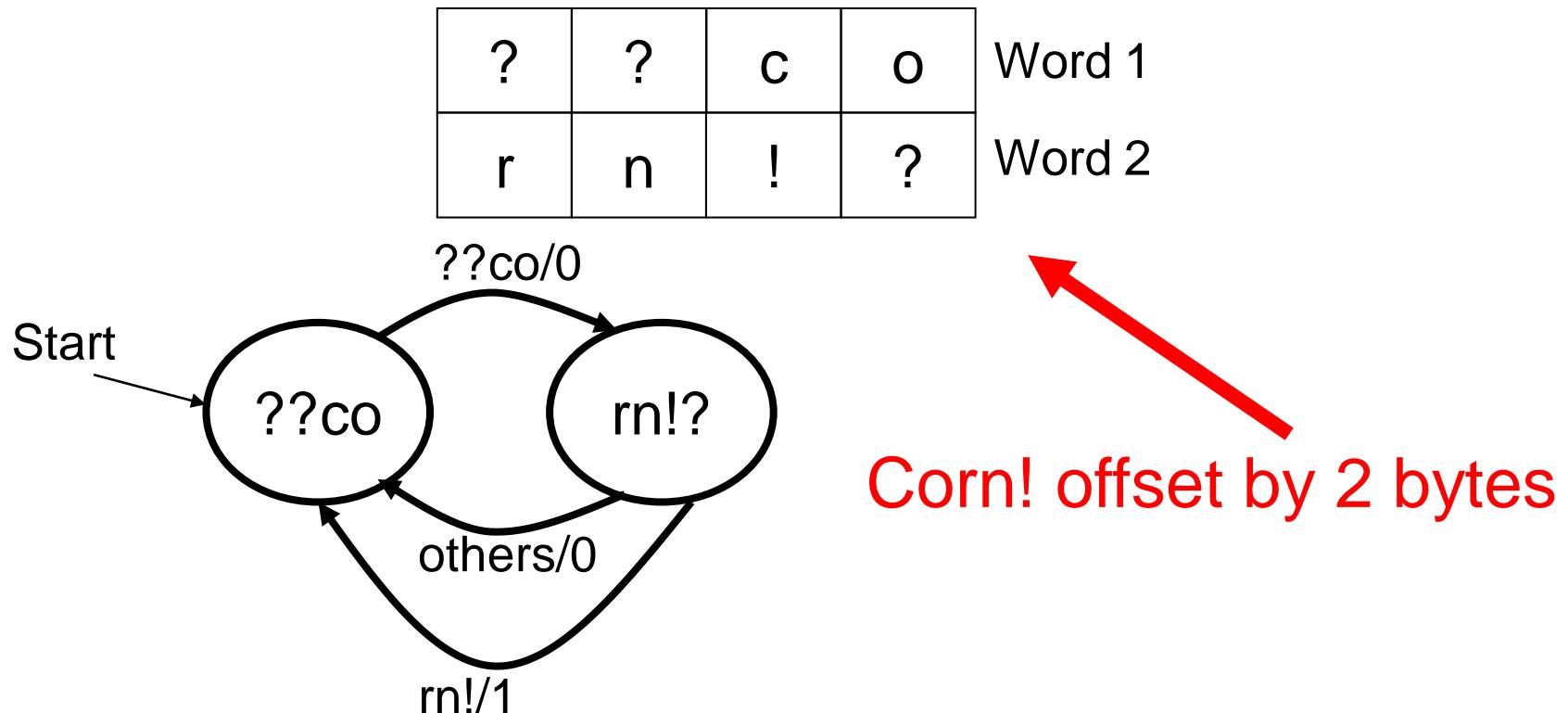- Network input stream typically 32-bit words
 - 4 8-bit characters per word.
- corn! Example




Multiple Characters per Clock

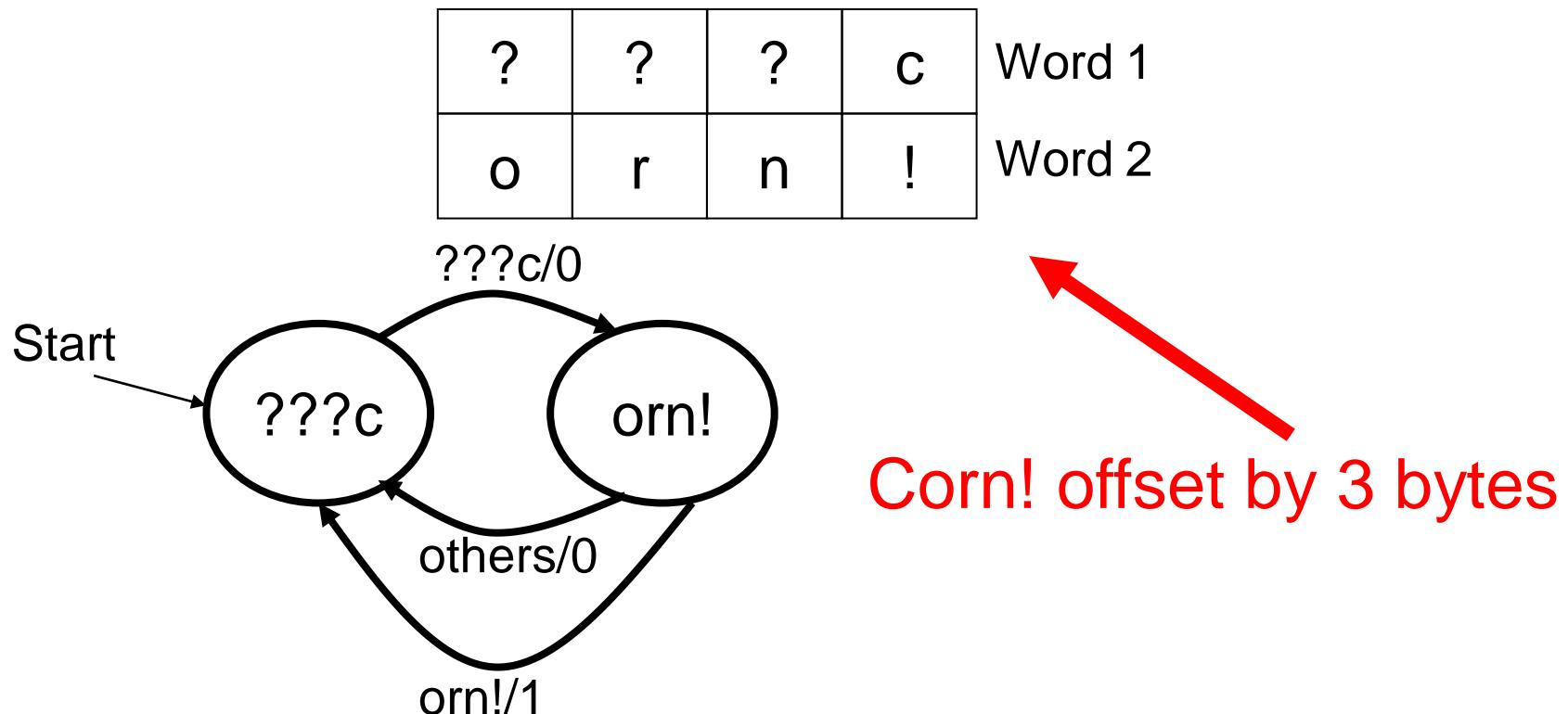- Network input stream typically 32-bit words
 - 4 8-bit characters per word.
- corn! Example




Multiple Characters per Clock

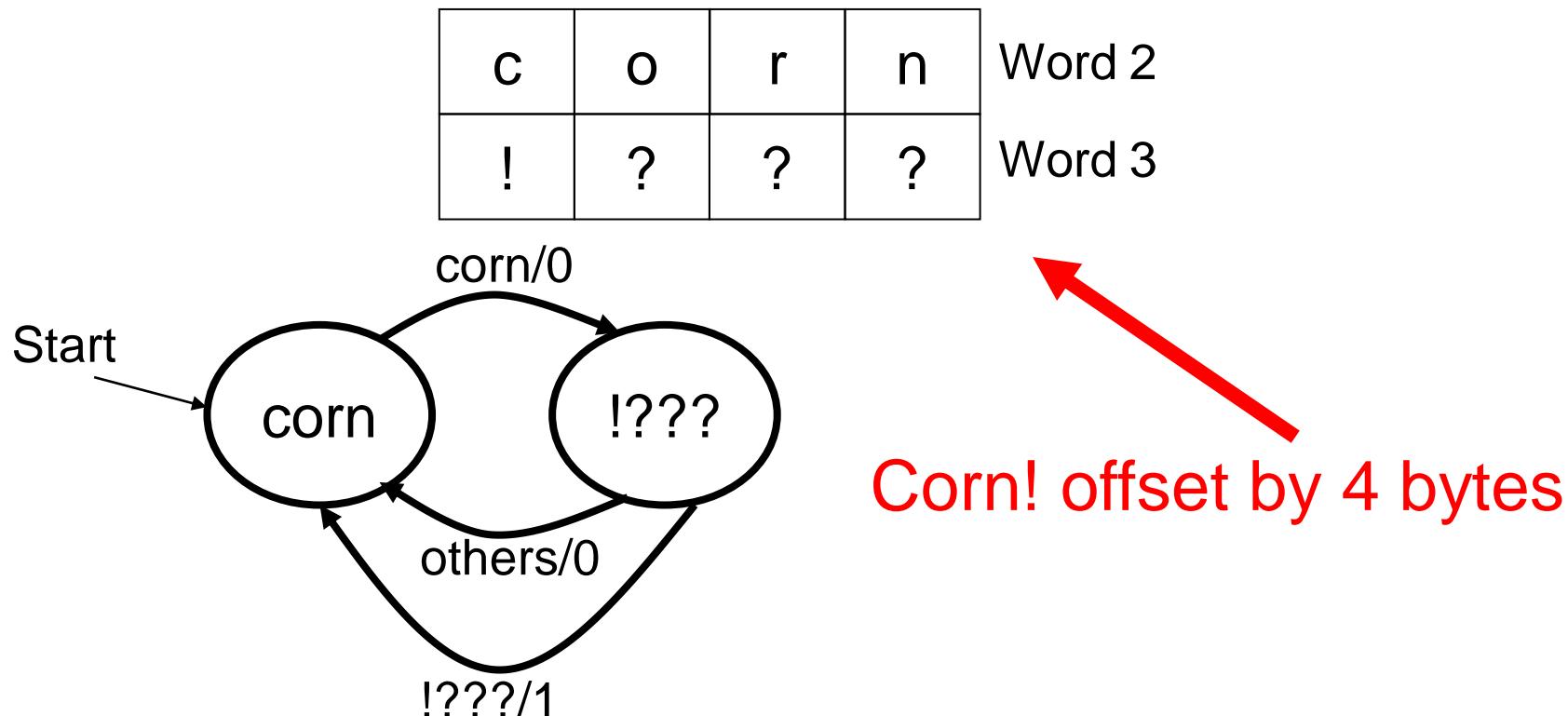
- Network input stream typically 32-bit words
 - 4 8-bit characters per word.
- corn! Example




Modify Alert FSM for Multiple characters

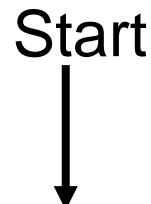


Modify Alert FSM for Multiple characters

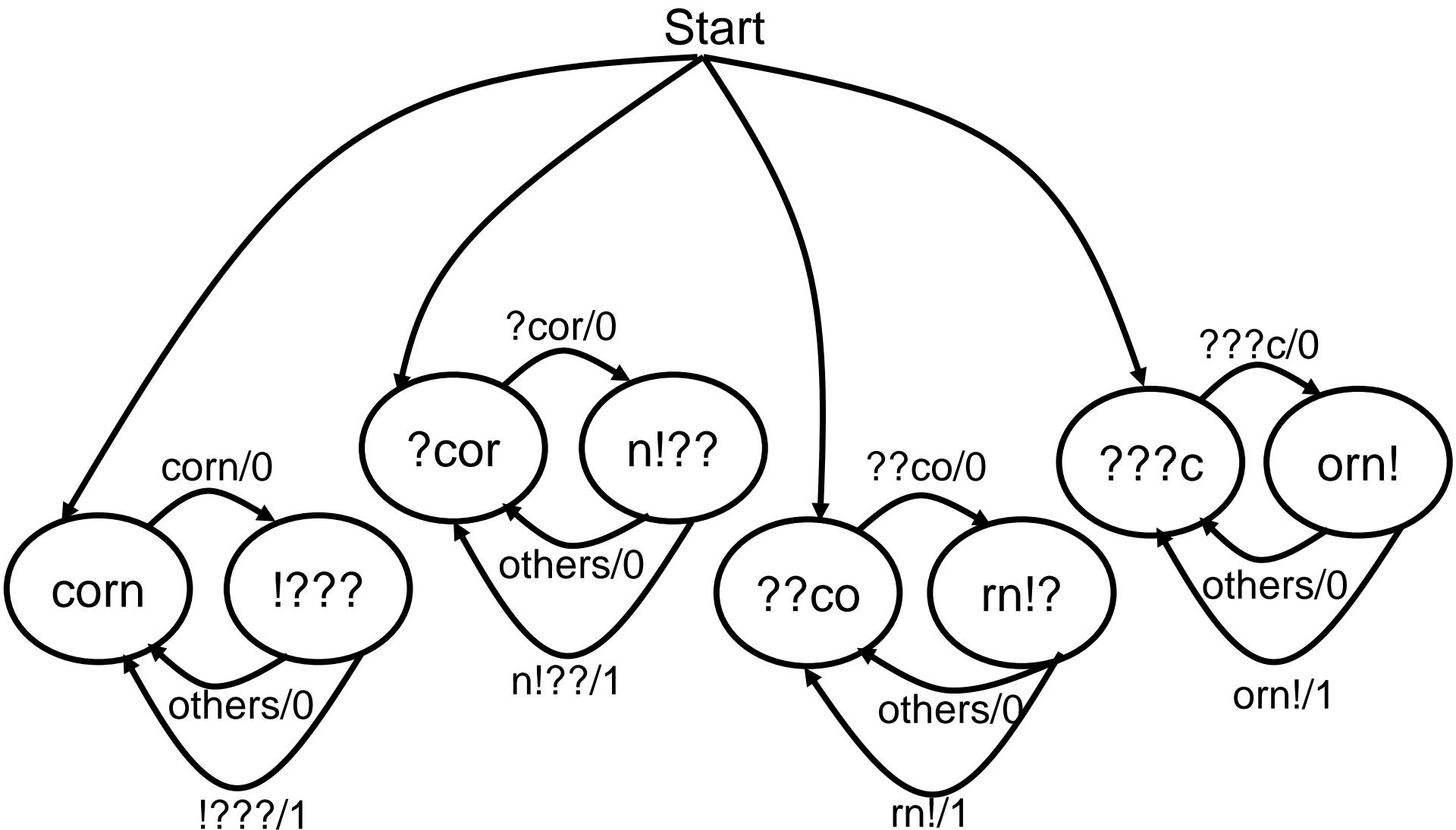

Modify Alert FSM for Multiple characters

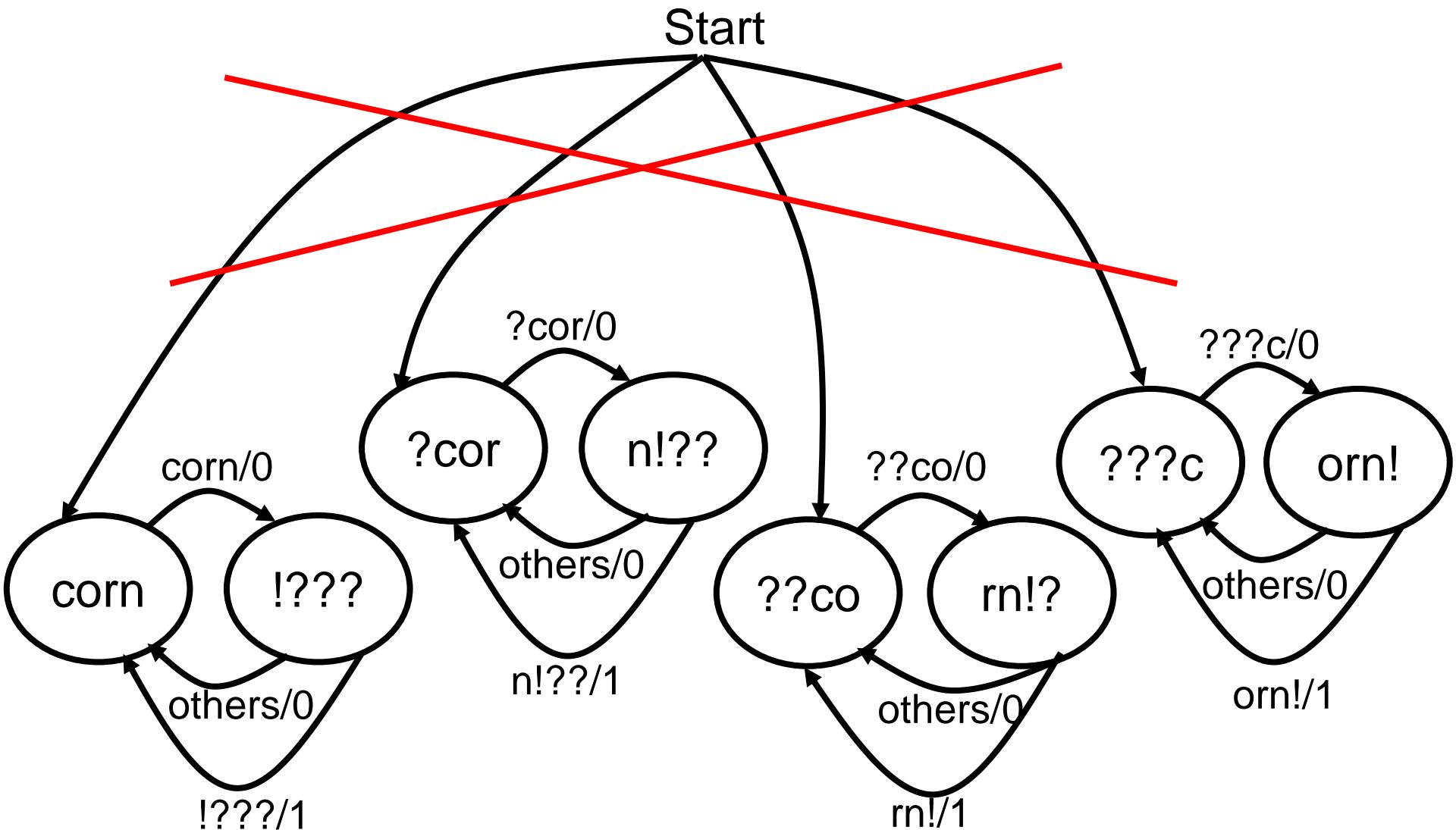


Modify Alert FSM for Multiple characters

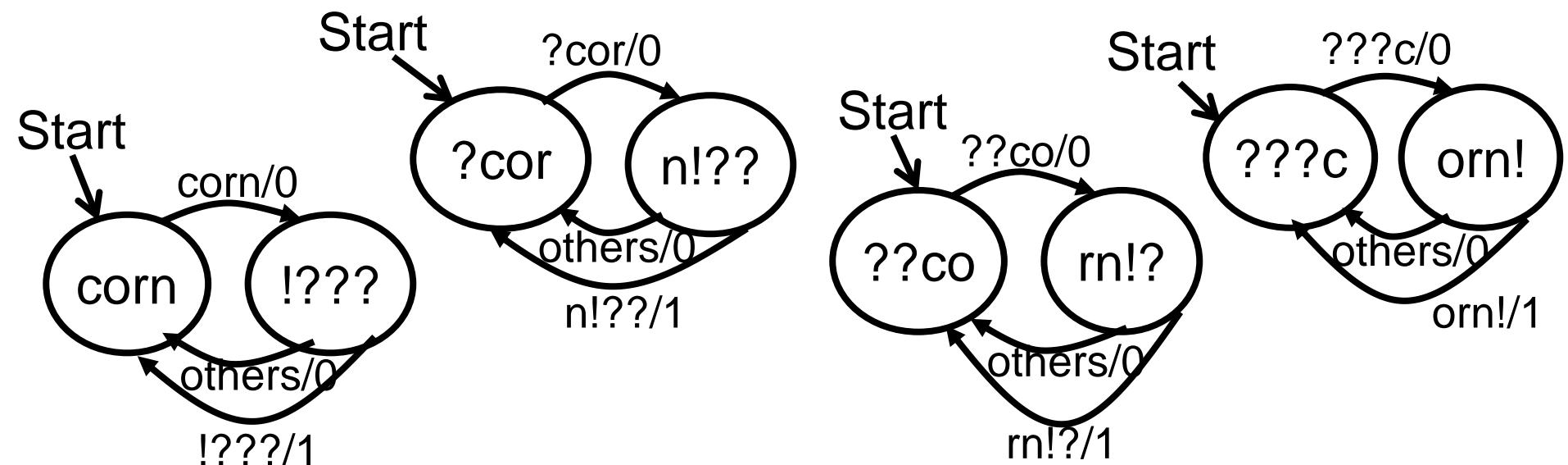


Modify Alert FSM for Multiple characters

c	b	c	o
r	n	!	c
o	r	n	!
z	c	o	r

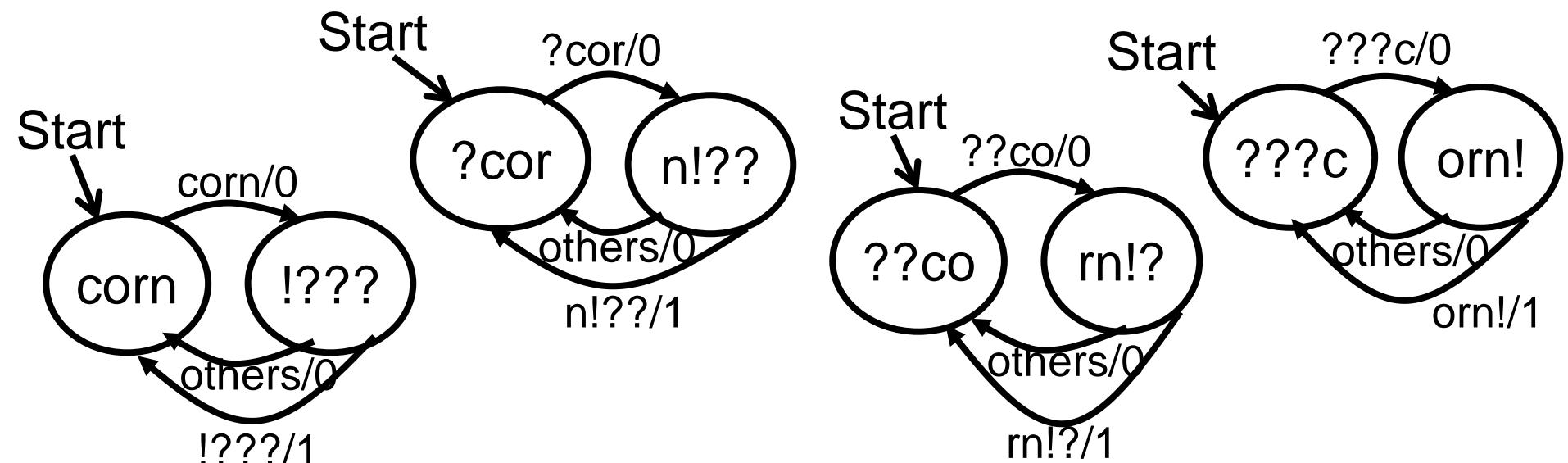


Modify Alert FSM for Multiple characters

c	b	c	o
r	n	!	c
o	r	n	!
z	c	o	r

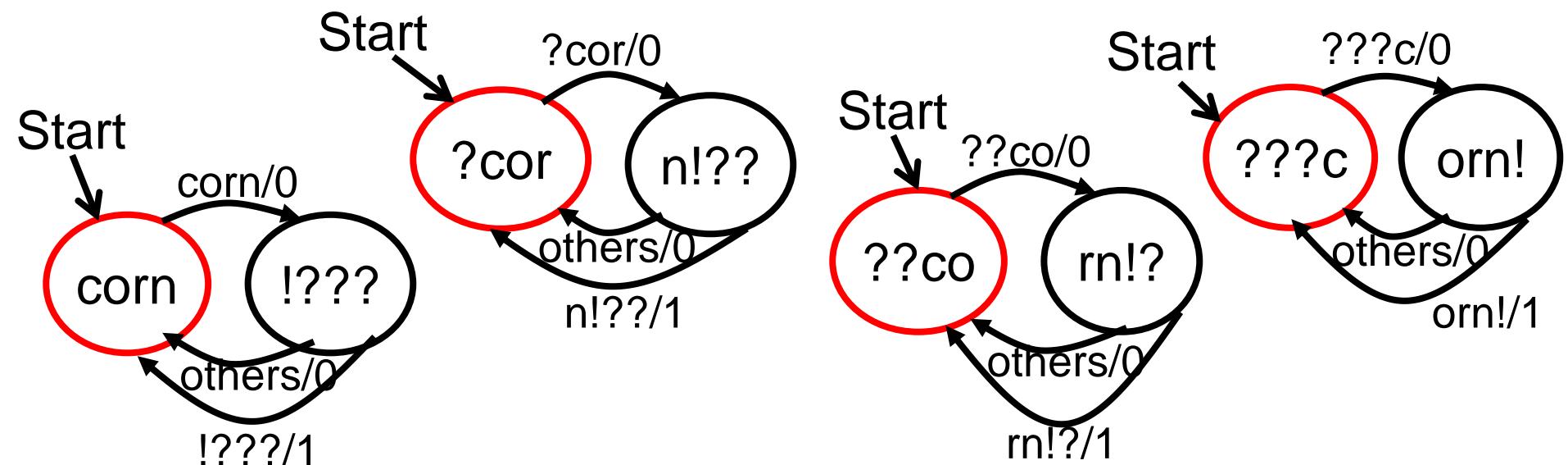


Modify Alert FSM for Multiple characters

c	b	c	o
r	n	!	c
o	r	n	!
z	c	o	r

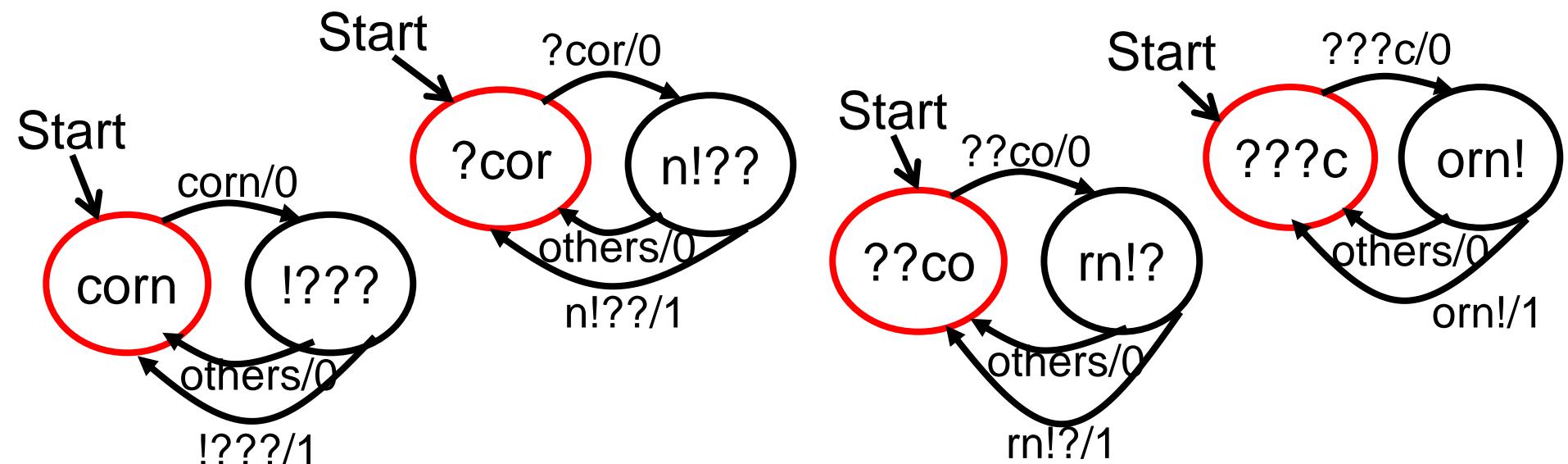


Modify Alert FSM for Multiple characters

c	b	c	o
r	n	!	c
o	r	n	!
z	c	o	r

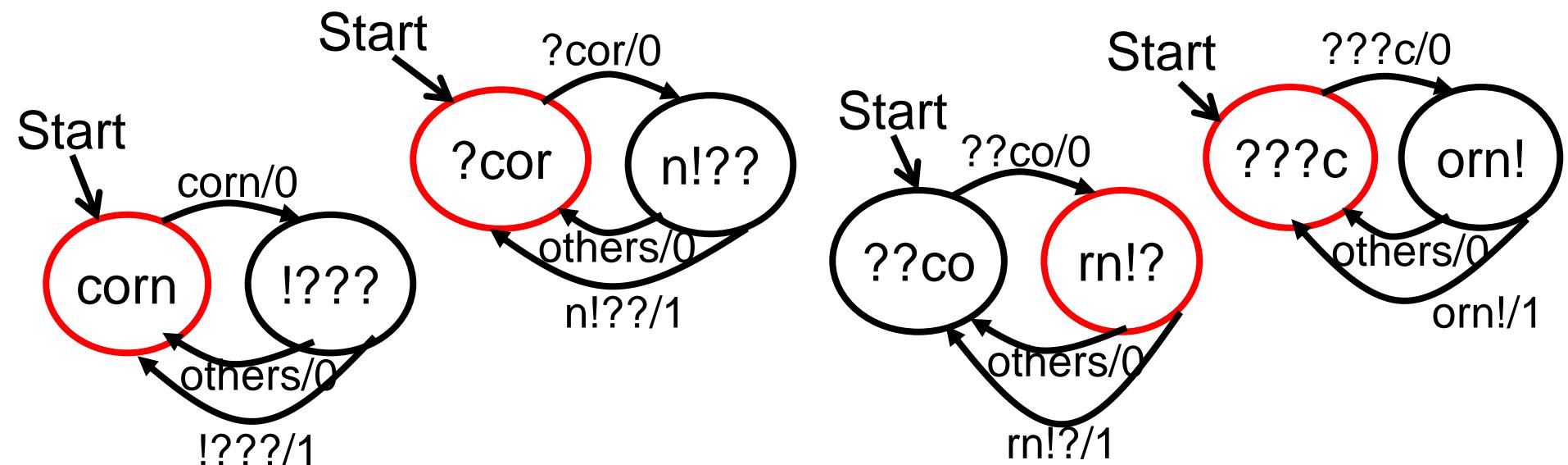


Modify Alert FSM for Multiple characters

c	b	c	o
r	n	!	c
o	r	n	!
z	c	o	r

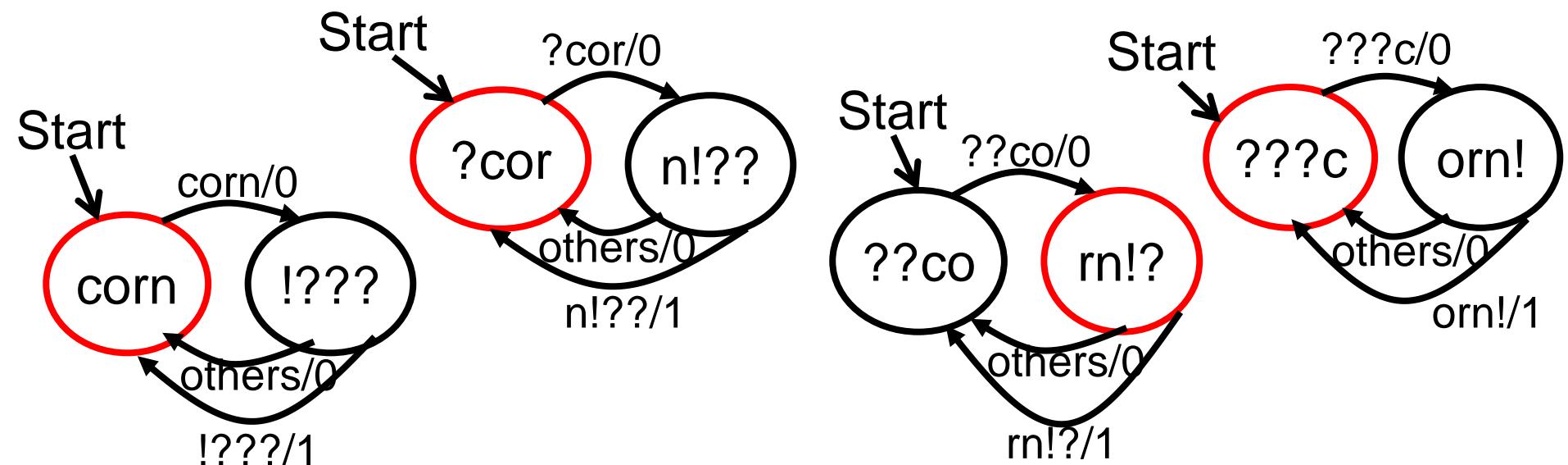


Modify Alert FSM for Multiple characters

c	b	c	o
r	n	!	c
o	r	n	!
z	c	o	r

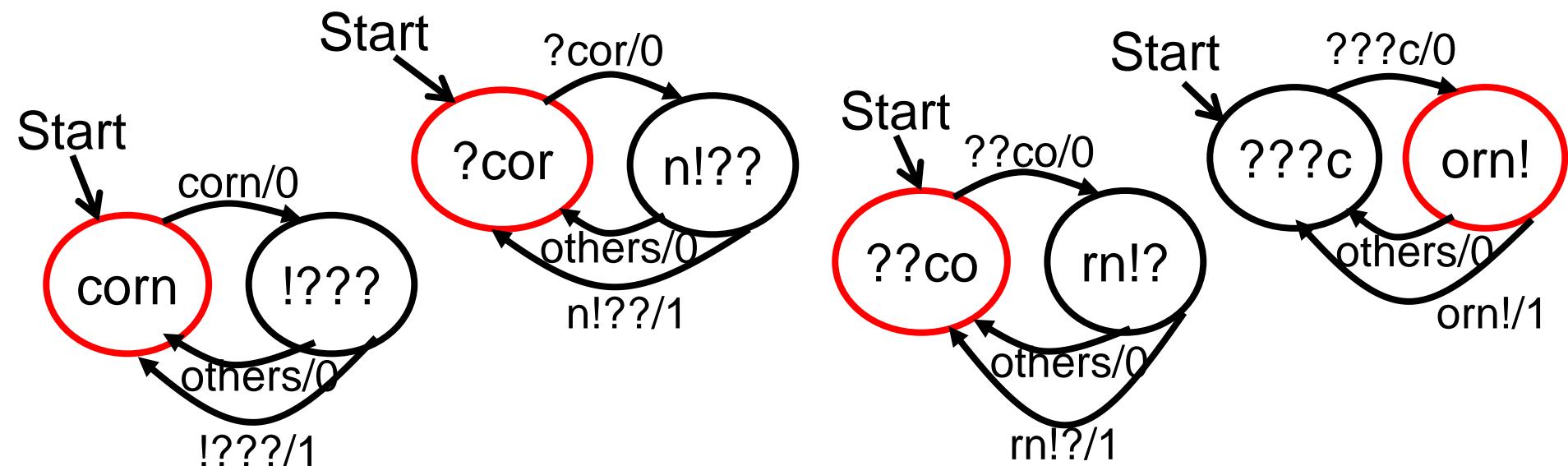


Modify Alert FSM for Multiple characters

c	b	c	o
r	n	!	c
o	r	n	!
z	c	o	r

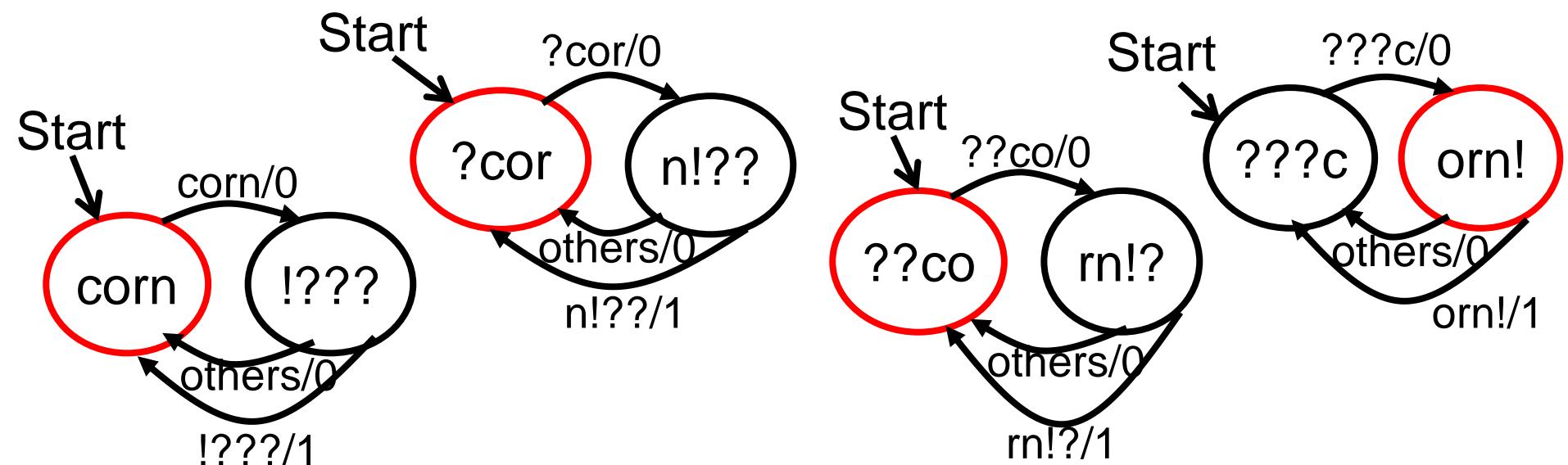


Modify Alert FSM for Multiple characters

c	b	c	o
r	n	!	c
o	r	n	!
z	c	o	r

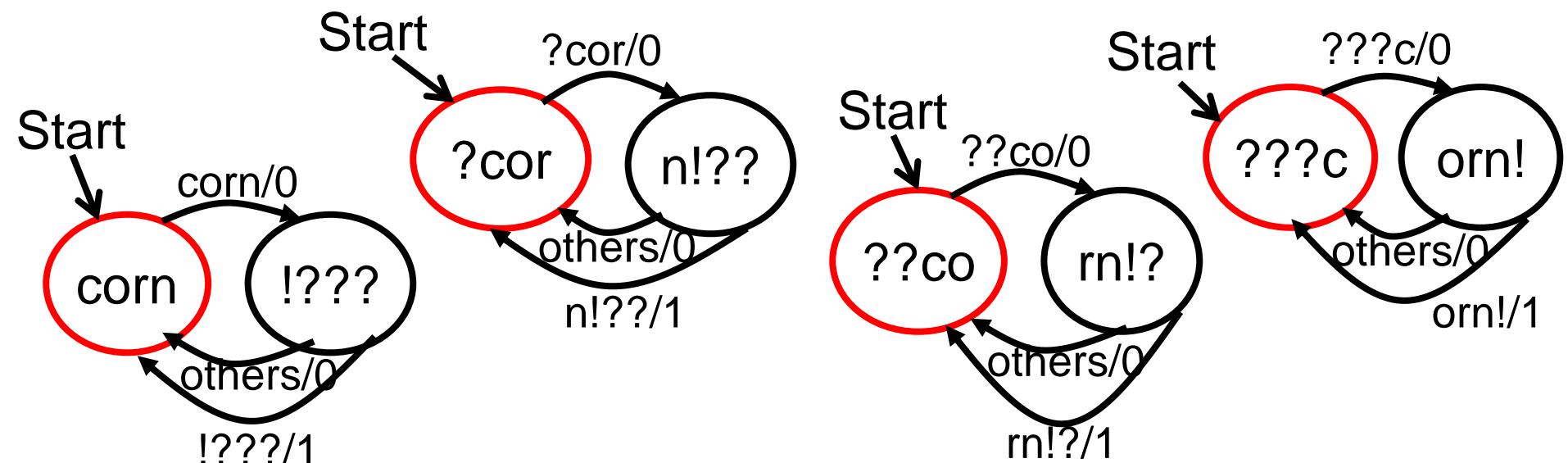


Modify Alert FSM for Multiple characters

c	b	c	o
r	n	!	c
o	r	n	!
z	c	o	r

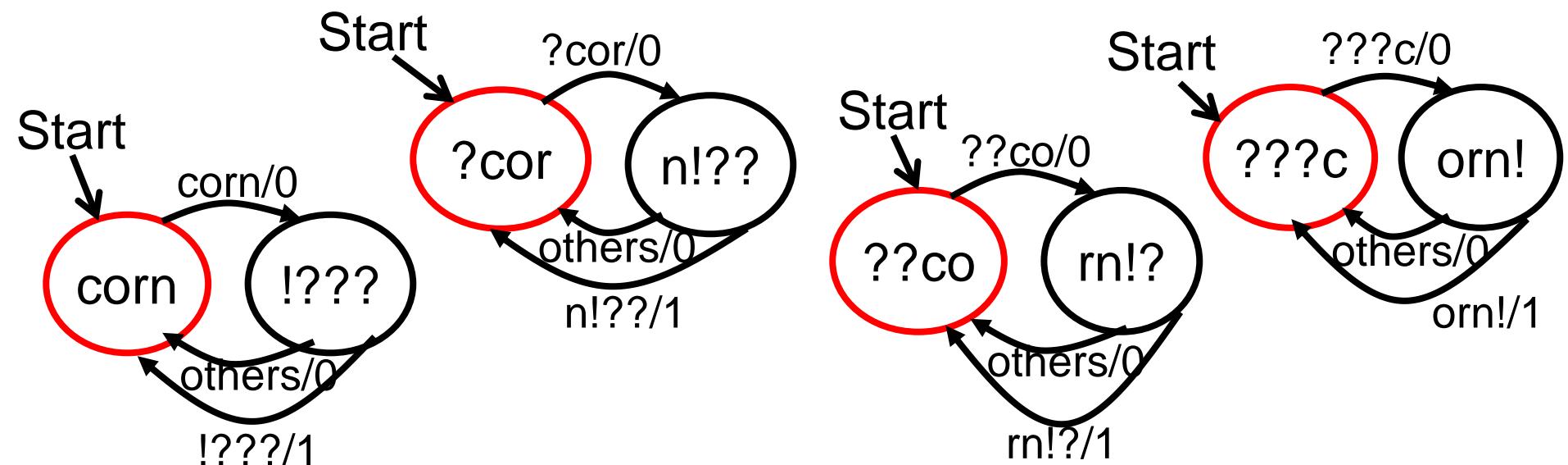


Modify Alert FSM for Multiple characters


c	b	c	o
r	n	!	c
o	r	n	!
z	c	o	r

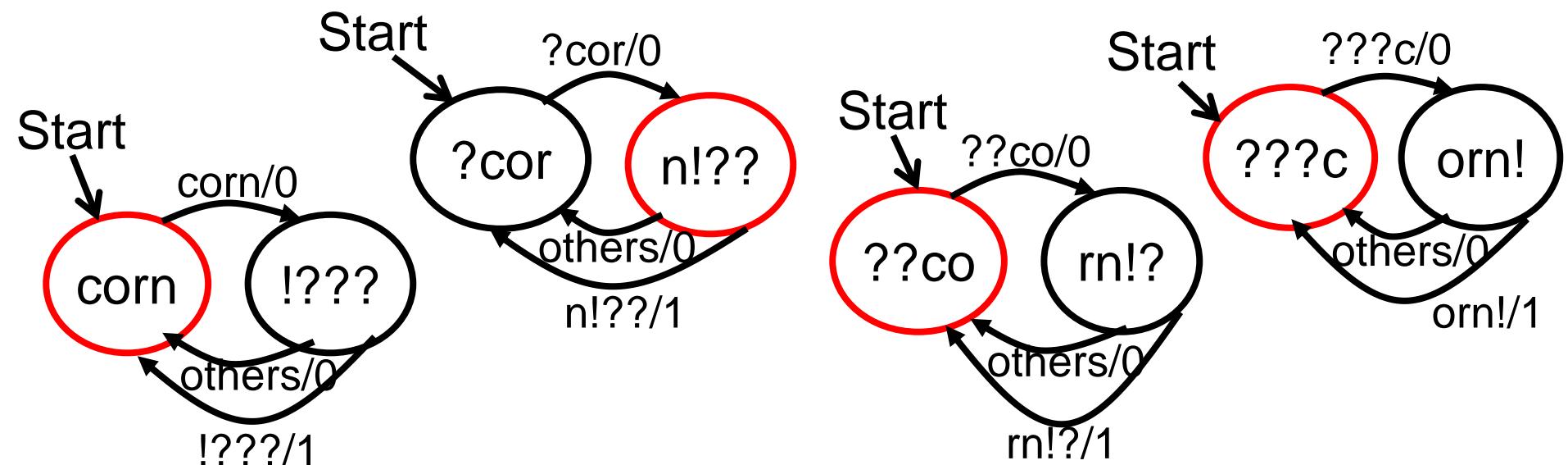

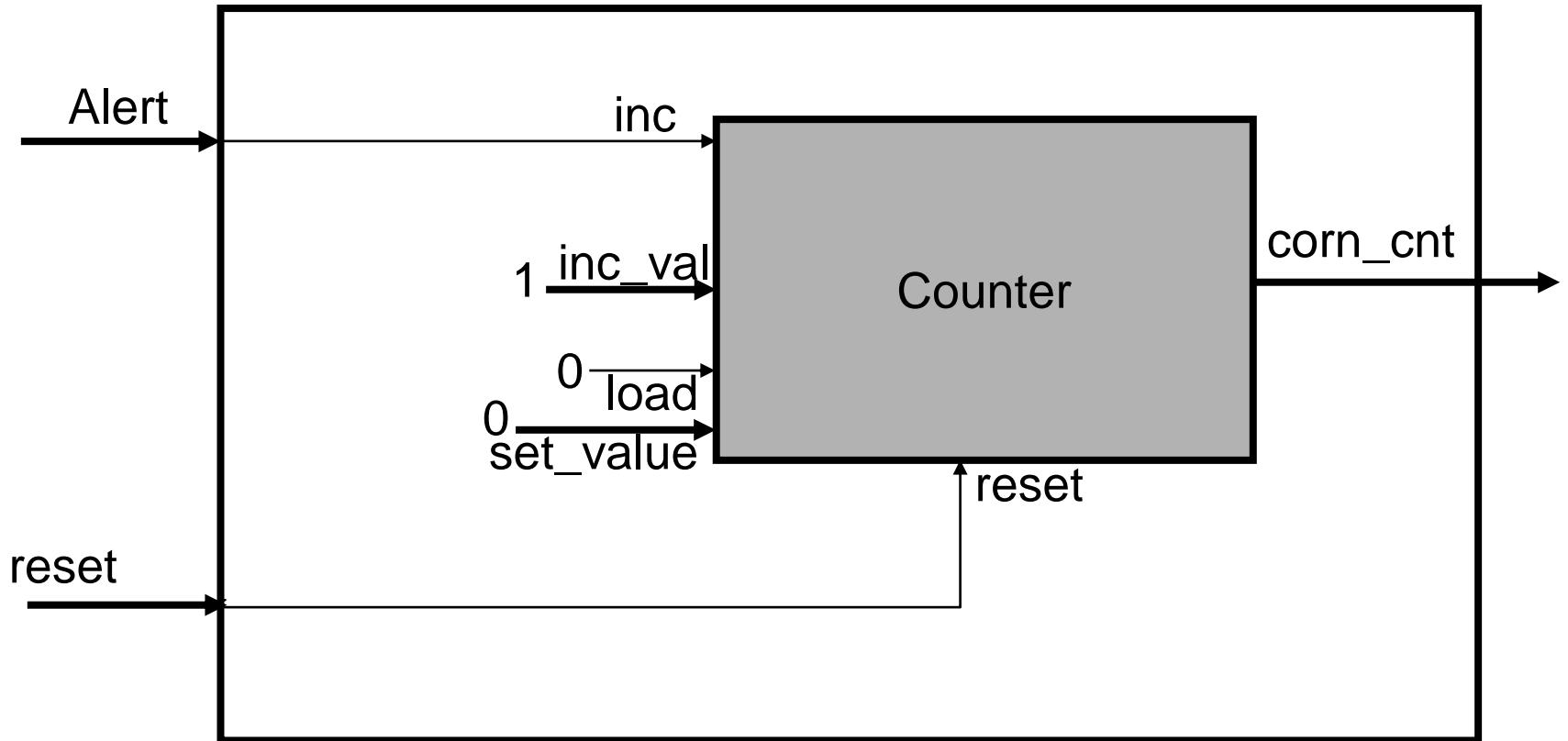
Modify corn! counter for Multiple characters



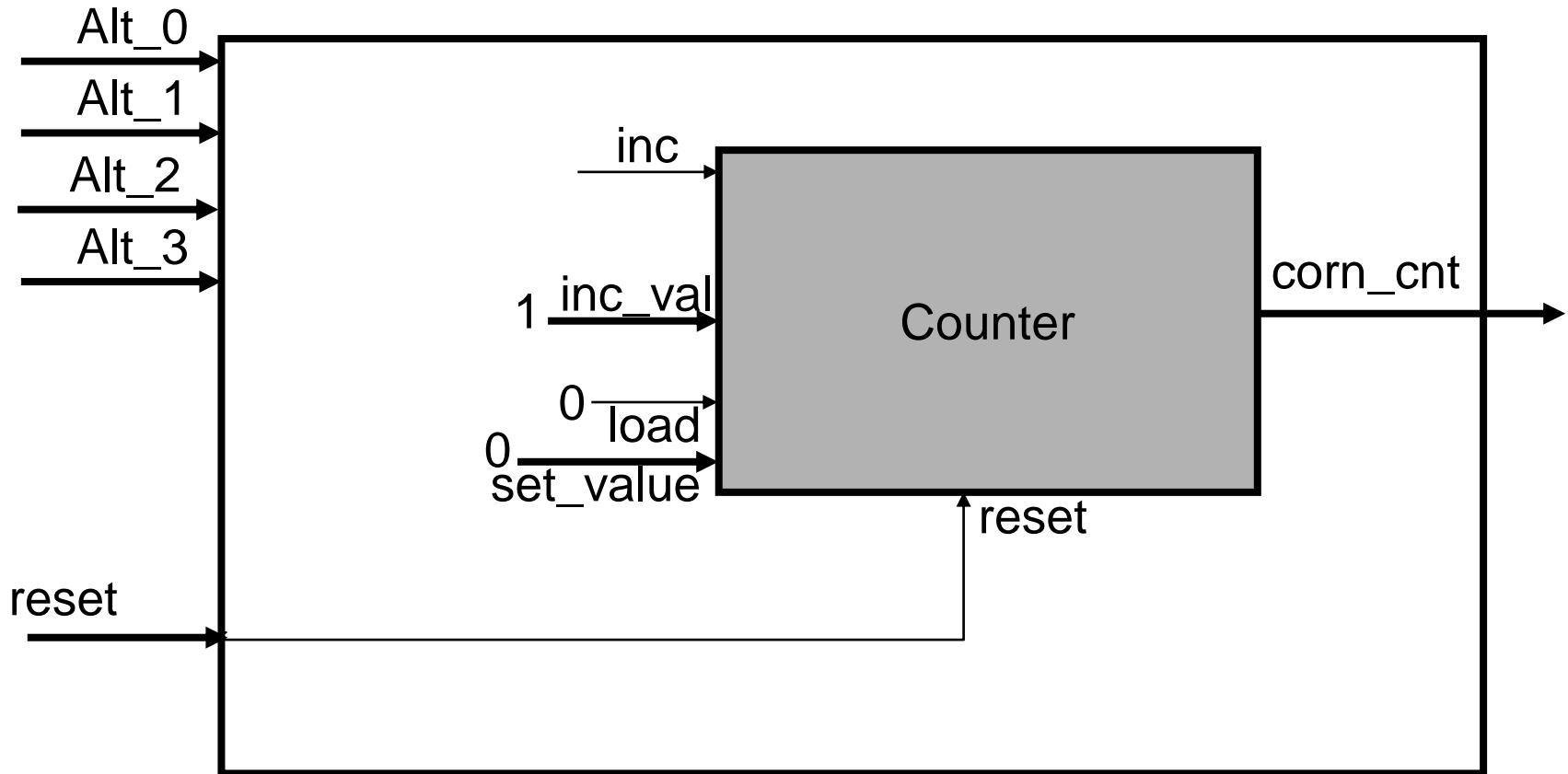
Modify corn! counter for Multiple characters



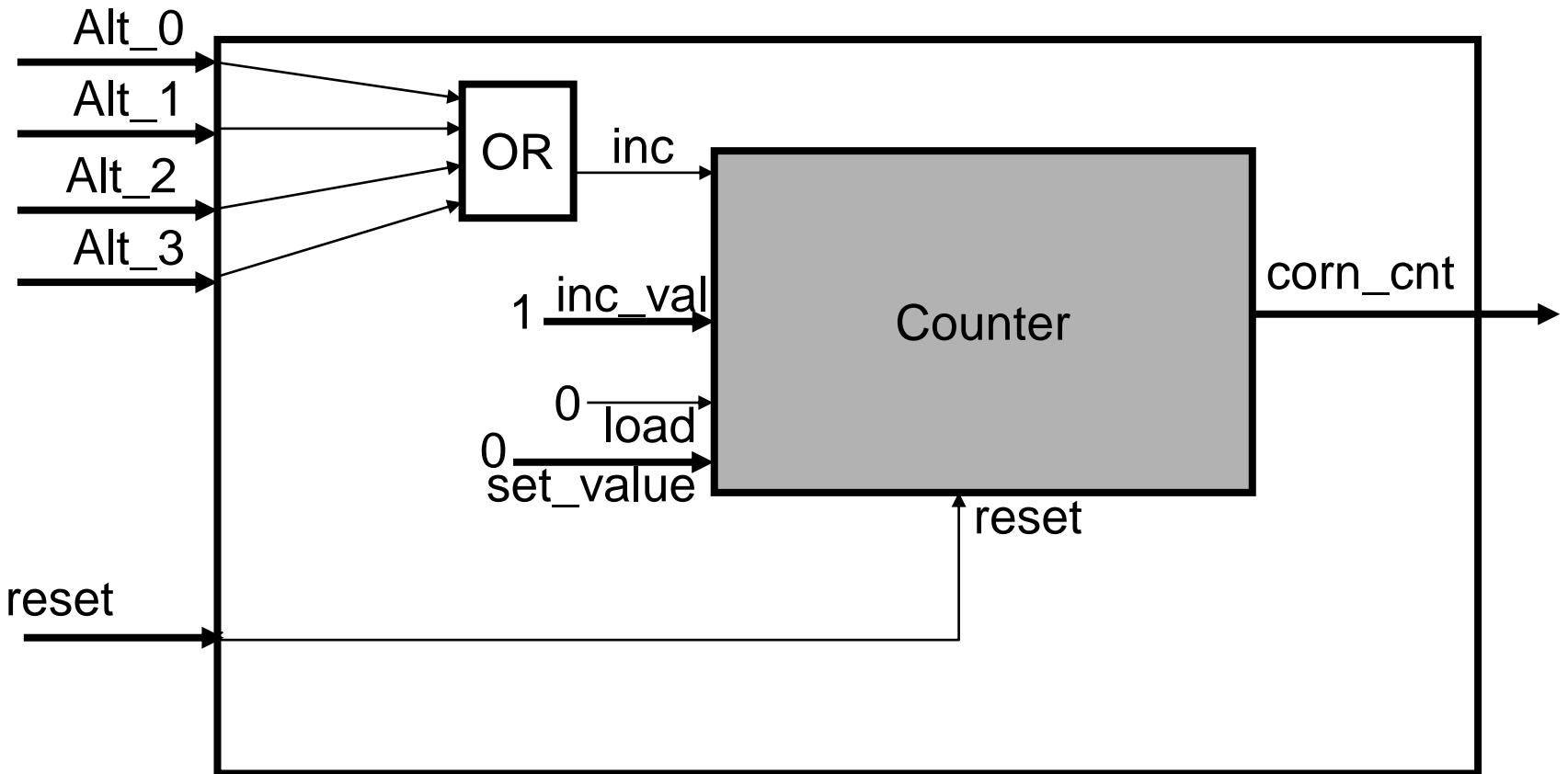Modify corn! counter for Multiple characters



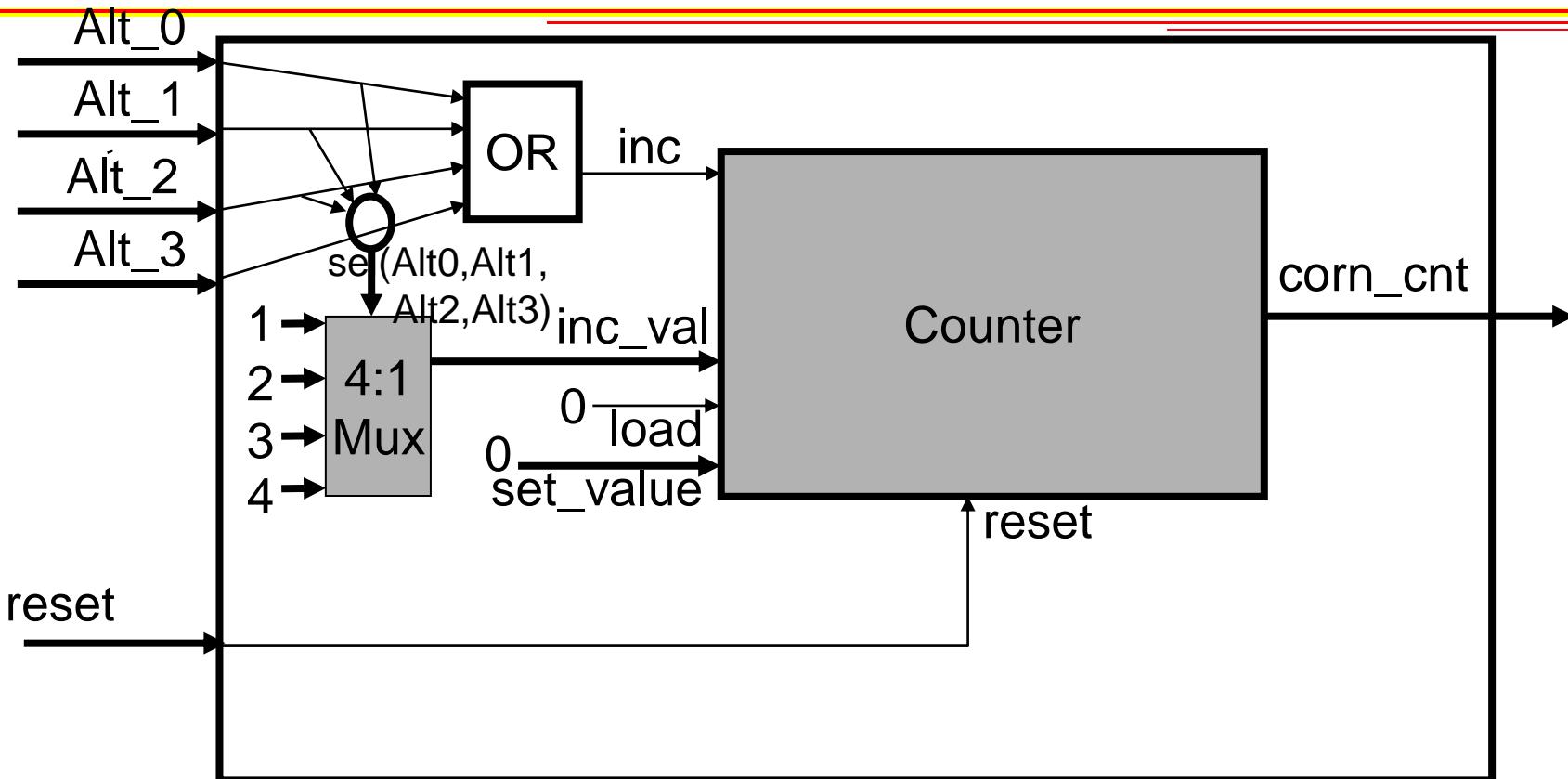
Modify corn! counter for Multiple characters



NOT in a process!

```
Alt_merge <= Alt0 & Alt1 & Alt2 & Alt3;  
inc_val <= 4 when (Alt_merge = "1111")  
            3 when (Alt_merge = "0111" or Alt_merge = "1011" ...)  
            2 when (Alt_merge = "0011" or Alt_merge = "0110" ...)  
            else 0
```

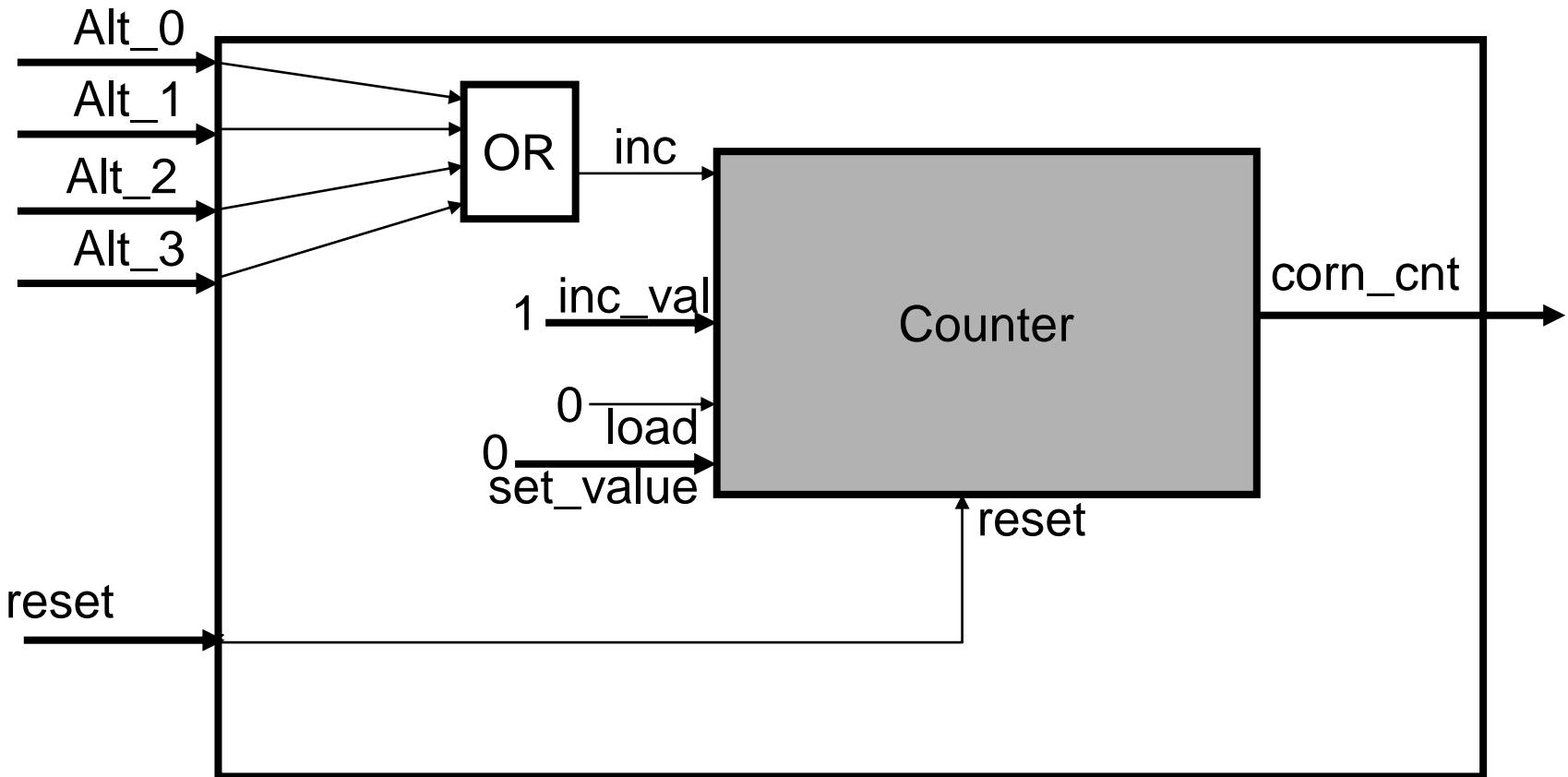
Modify corn! counter for Multiple characters



In progress Slides

Moore FSM

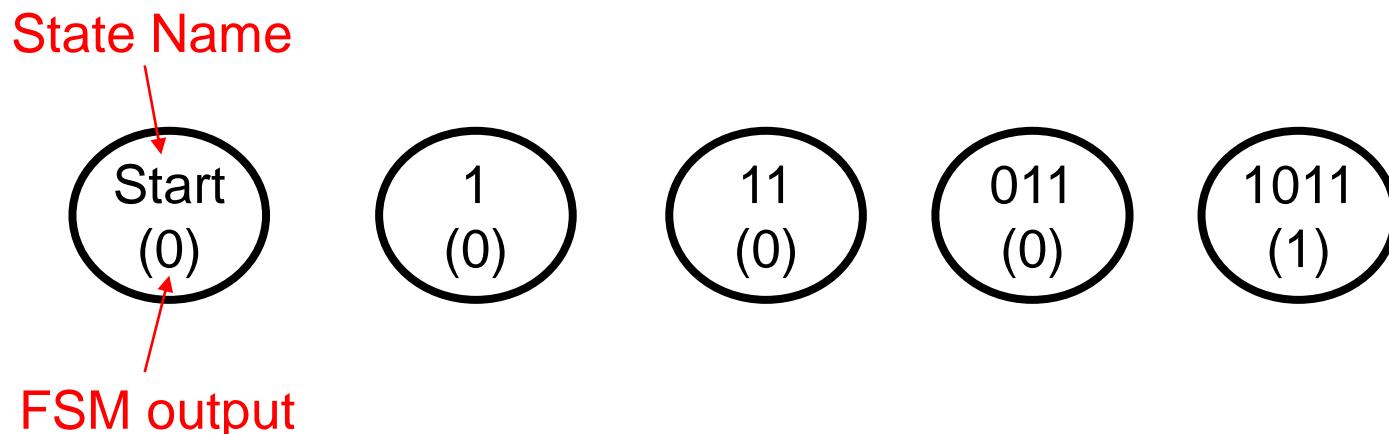
- Moore: Output is only a function of the current state
- Example detect every occurrence of “1011”



Moore FSM


- Moore: Output is only a function of the current state
- Example detect every occurrence of “1011”

Where to go on a given input

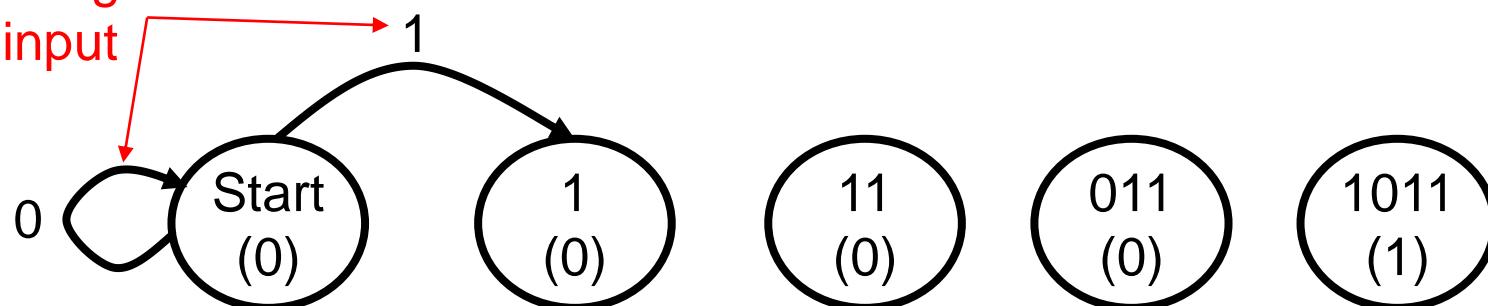

Moore FSM

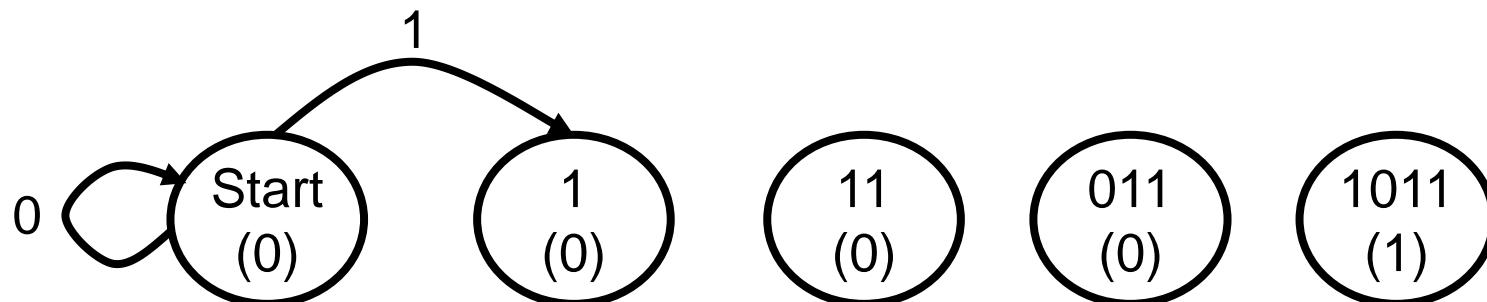
- Moore: Output is only a function of the current state
- Example detect every occurrence of “1011”



Input: 1

Moore FSM

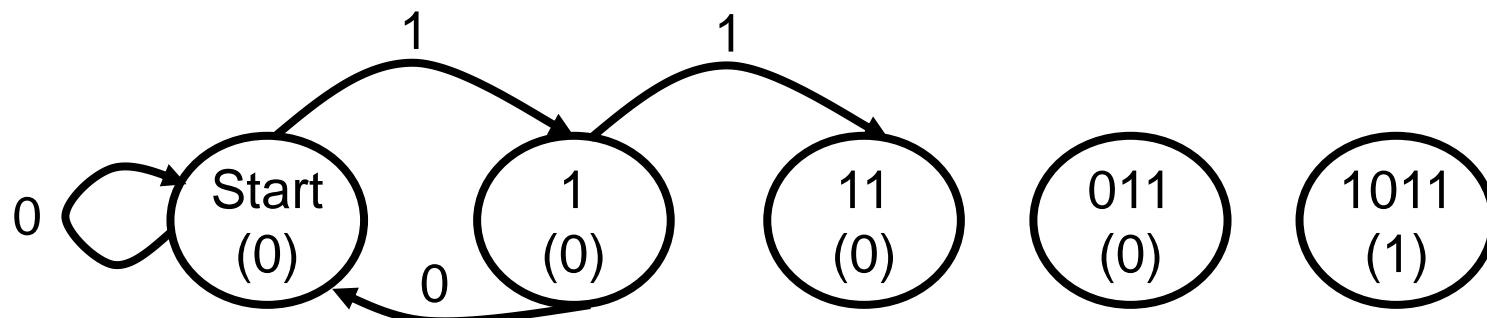
- Moore: Output is only a function of the current state
- Example detect every occurrence of “1011”



Input: 11

Moore FSM

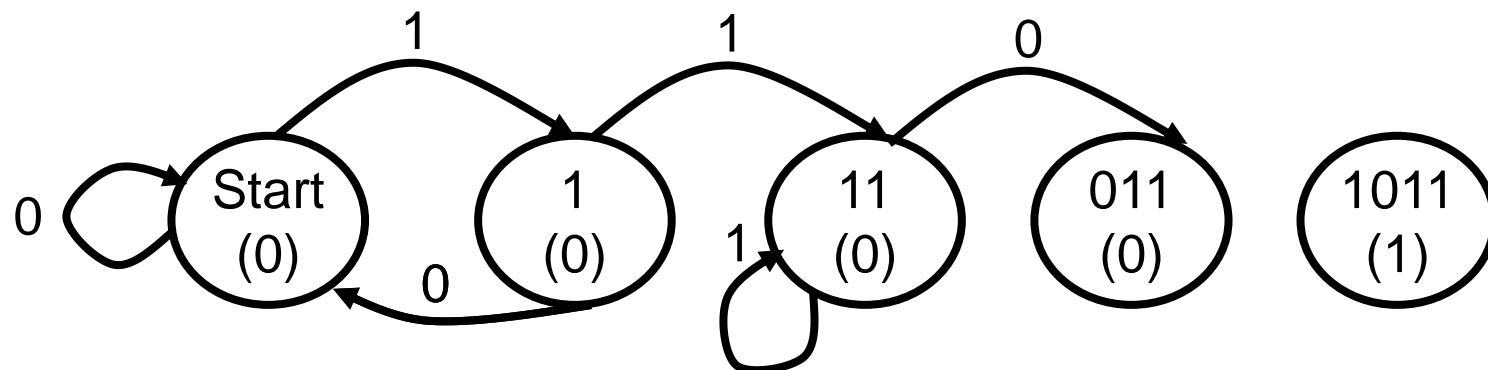
- Moore: Output is only a function of the current state
- Example detect every occurrence of “1011”



Input: 011

Moore FSM

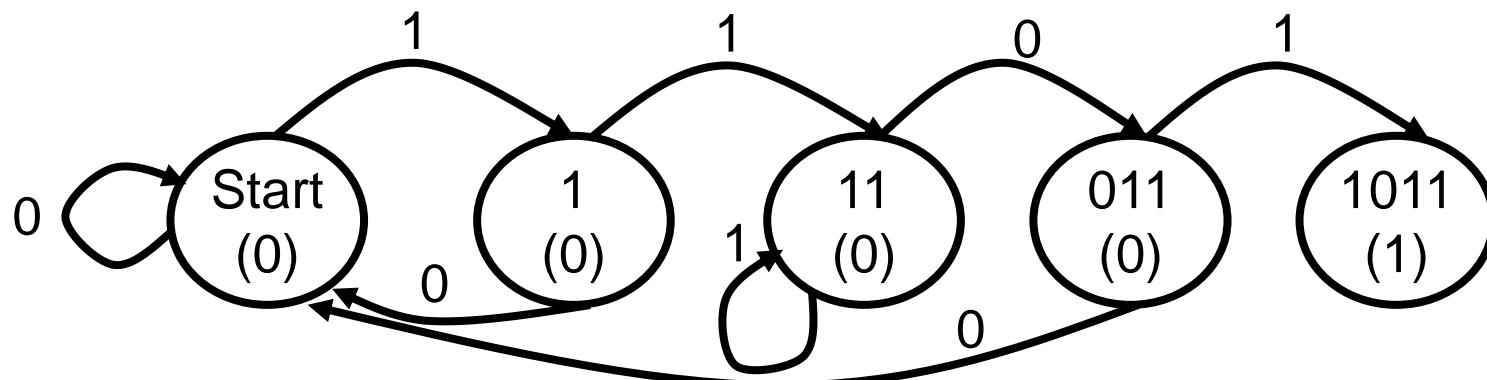
- Moore: Output is only a function of the current state
- Example detect every occurrence of “1011”



Input: 1011


Moore FSM

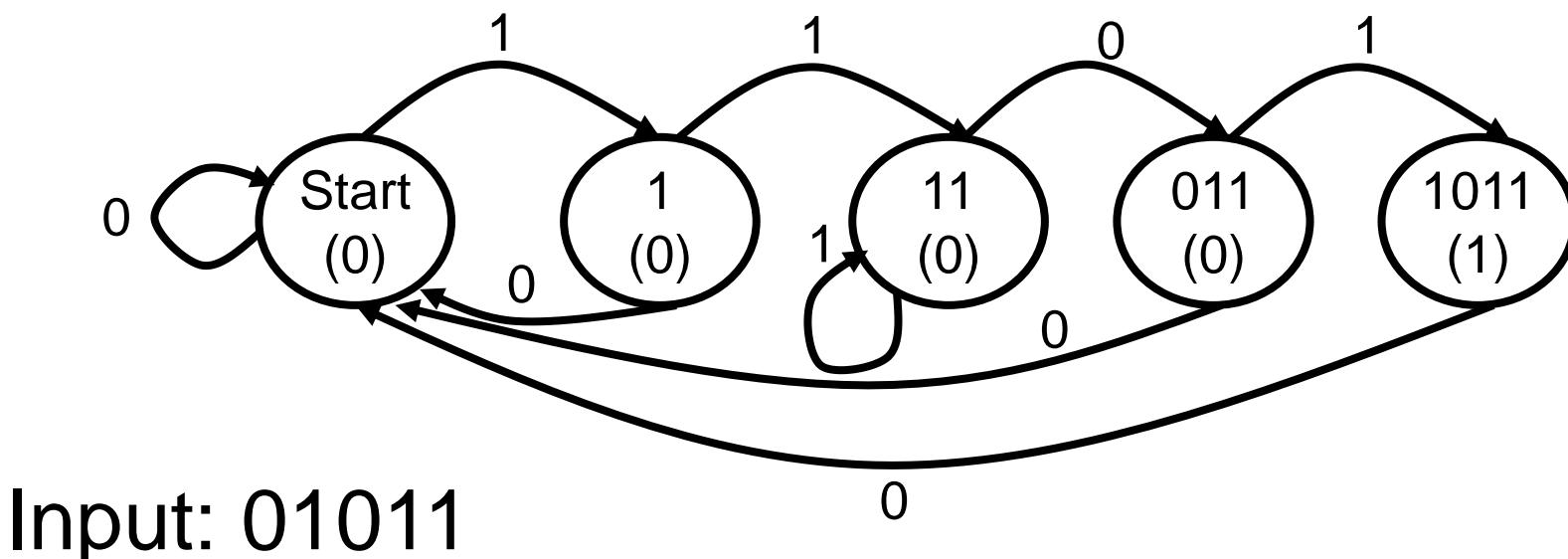- Moore: Output is only a function of the current state
- Example detect every occurrence of “1011”




Moore FSM

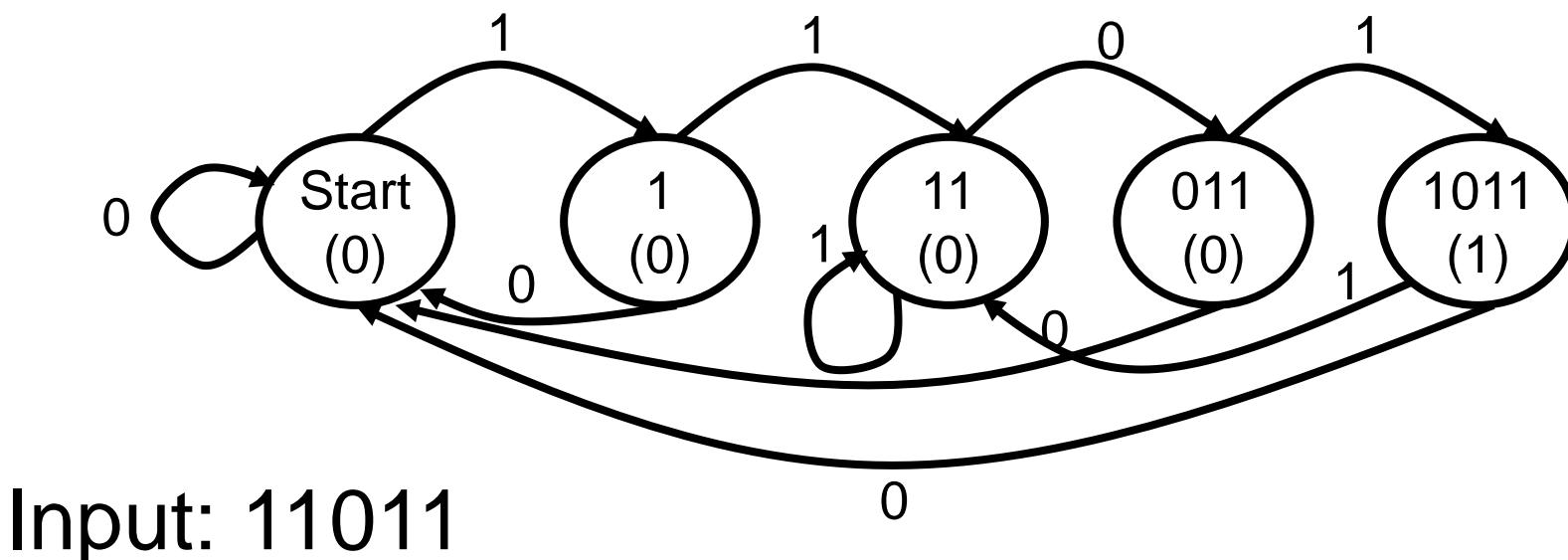- Moore: Output is only a function of the current state
- Example detect every occurrence of “1011”



Moore FSM

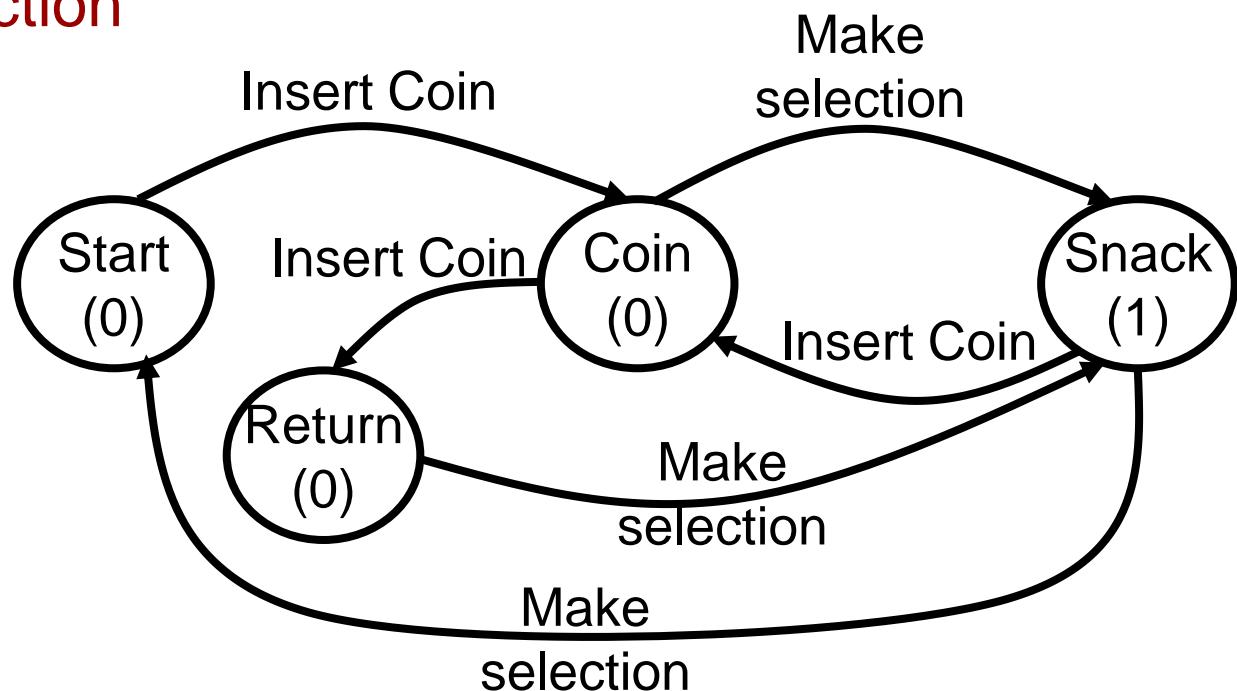
- Moore: Output is only a function of the current state
- Example: vending machine
 - Events (assume all items cost 1 coin):
 - Insert Coin
 - Make selection



Moore FSM

- Moore: Output is only a function of the current state
- Example: vending machine
 - Events (assume all items cost 1 coin):

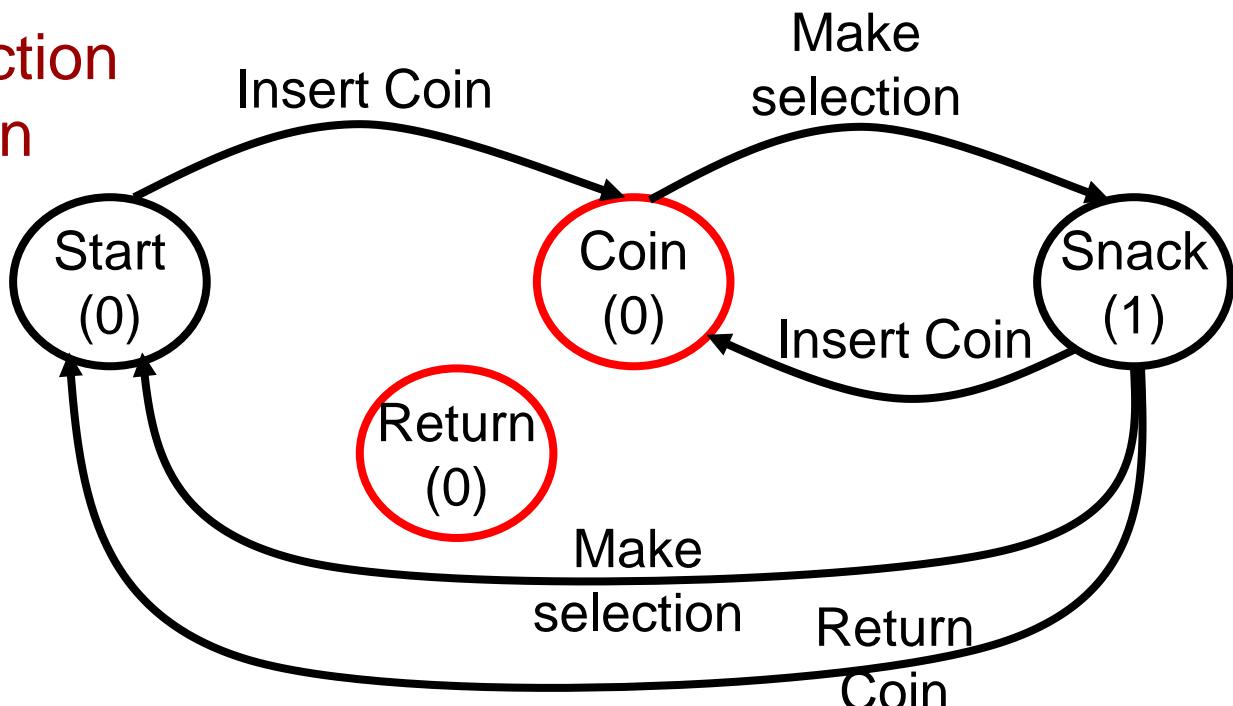
- Insert Coin
- Make selection
- Return Coin



Moore FSM

- Moore: Output is only a function of the current state
- Example: vending machine
 - Events (assume all items cost 1 coin):

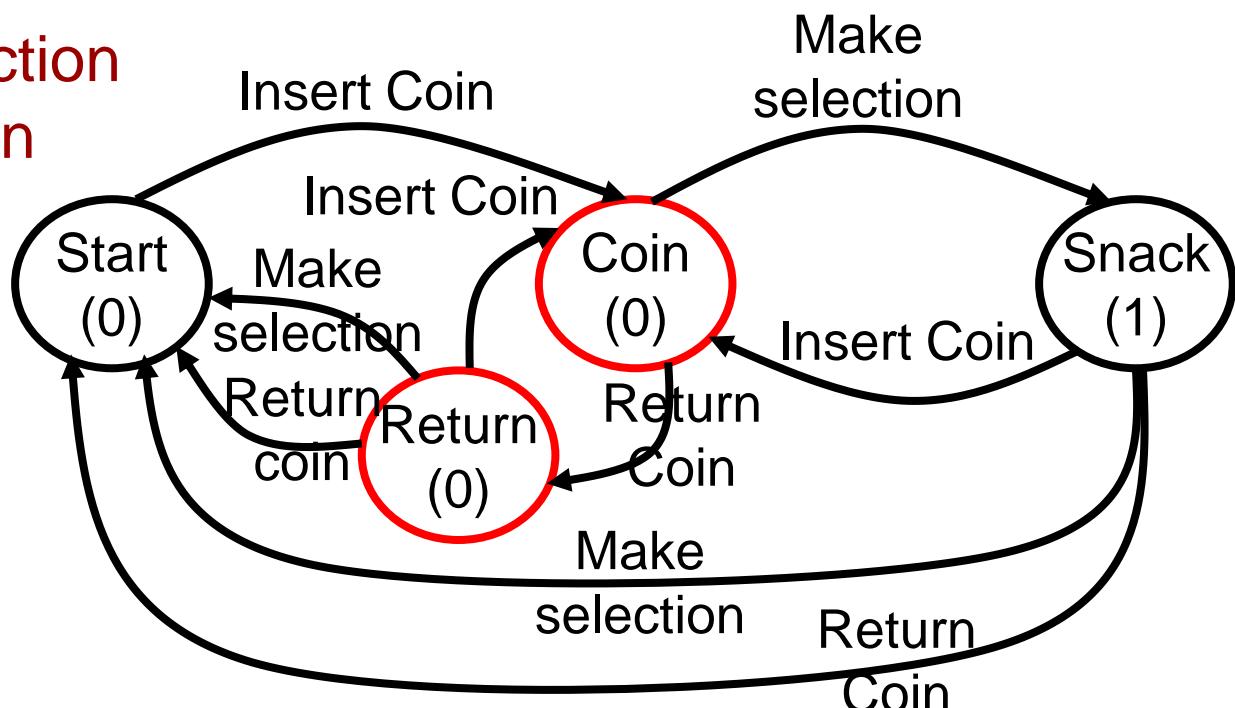- Insert Coin
- Make selection
- Return Coin



Moore FSM

- Moore: Output is only a function of the current state
- Example: vending machine
 - Events (assume all items cost 1 coin):
 - Insert Coin
 - Make selection

