


EE 330 Midterm Exam #03

Name: _____ Score _____


Instructions:

- The exam is for 50-minute individual work, with closed book and closed-notes.
- There are 5 problems, each worth 20 points.
- A simple calculator, with no wireless capability, is allowed.
- Two sheets of formulas of US letter size are allowed. No other papers allowed.
- Write brief solutions in the space provided on this exam. If necessary, you can write on the previous page backside, but clearly mark the question numbers.
- Specific parameters are given in the problem statements. Extra process and device parameters are attached at the end of the exam.
- If you need any other parameters, clearly make an assumption and proceed.

 1. Assume the capacitors are very large, the BJT is in forward active, and V_M is small.
 - a) Draw the simplified quiescent circuit and find the quiescent value of V_C .
 - b) Draw the small signal equivalent circuit.
 - c) Determine the small-signal voltage gain from $v(t)$ to v_{out} .




 2. Determine the small signal output voltage if the small signal input voltage is a sinusoidal 1 KHz signal with 0-P amplitude of 10mV.




3. Assume two unilateral amplifiers are cascaded. The first amplifier has small-signal amplifier parameters of $A_{V1} = -10$, $R_{IN1} = 4K$ and $R_{o1} = 500\Omega$. The second amplifier has small-signal amplifier parameters of $A_{V2} = -20$, $R_{IN2} = 2K$, and $R_{o2} = 1.5K$. Assume a capacitor coupled load of 500Ω is placed on the second amplifier output and the first amplifier input is driven by a voltage source with an source impedance of 1000Ω .
- Draw the small signal model of the chain from the source to the load.
 - Determine the voltage gain from the source voltage to the load voltage.
 - Determine the percentage gain loss from the ideal gain of $A_{V1}A_{V2}$.

 4. Assume MOSTs are all in saturation and BJTs are all in Forward Active.
- Determine the voltages V_{01} and V_{02} in terms of the MOS device dimensions, W and L , the emitter areas, and the resistor variables R_1 , R_2 , and R_3 .
 - If $R_1=100K$, $A_{E1}=A_{E2}=200\mu^2$, $A_{E3}=50\mu^2$, $A_{E4}=300\mu^2$, $W_5=10\mu$, $L_5=1\mu$, $W_6=20\mu$, $L_6=1\mu$, Determine R_2 and R_3 so that $V_{01}=6V$ and $V_{02}=3V$.



 5. Assume the biasing voltages have been selected so that the quiescent current is 1 mA and that all transistors are operating in the forward active region. Determine the small-signal voltage gain and R_o for the following two circuits. Assume $\beta = 100$ and $V_{AF} = 130V$ for all transistors.



- Here are some rounded-off parameters in case you prefer:
 $\mu_n C_{OX}=350\mu A/V^2$, $\mu_p C_{OX}=100\mu A/V^2$, $V_{TNO}=0.5V$, $V_{TPO}=-0.5V$, $C_{OX}=8fF/\mu^2$,
 $\lambda=0.1/V$, no V_{bs} effect ($\gamma=0$)
- Default values for diode/BJT: $J_S=9.5*10^{-16}A/\mu^2$, $AE=100\mu^2$, NPN $\beta=100$, PNP $\beta=25$,
 $k/q=8.61*10^{-5}V/K$, $kT/q=26mV$, $J_{SX}=0.37A/\mu^2$, $V_{G0}=1.17V$, and $m=2$.

MOSIS WAFER ACCEPTANCE TESTS

RUN: T68B (MM_NON-EPI)	VENDOR: TSMC
TECHNOLOGY: SCN018	FEATURE SIZE: 0.18 microns
Run type: SKD	

INTRODUCTION: This report contains the lot average results obtained by MOSIS from measurements of MOSIS test structures on each wafer of this fabrication lot. SPICE parameters obtained from similar measurements on a selected wafer are also attached.

COMMENTS: DSCN6M018_TSMC

TRANSISTOR PARAMETERS	W/L	N-CHANNEL	P-CHANNEL	UNITS
MINIMUM Vth	0.27/0.18	0.50	-0.51	volts
SHORT Idss	20.0/0.18	547	-250	uA/um
Vth		0.51	-0.51	volts
Vpt		4.8	-5.6	volts
WIDE Ids0	20.0/0.18	14.4	-4.7	pA/um
LARGE Vth	50/50	0.43	-0.42	volts
Vjbkd		3.1	-4.3	volts
Ijlk		<50.0	<50.0	pA
K' (Uo*Cox/2)		175.4	-35.6	uA/V^2
Low-field Mobility		416.52	84.54	cm^2/V*s

COMMENTS: Poly bias varies with design technology. To account for mask bias use the appropriate value for the parameters XL and XW in your SPICE model card.

Design Technology	XL (um)	XW (um)
SCN6M_DEEP (lambda=0.09)	0.00	-0.01
thick oxide	0.00	-0.01
SCN6M_SUBM (lambda=0.10)	-0.02	0.00
thick oxide	-0.02	0.00

FOX TRANSISTORS	GATE	N+ACTIVE	P+ACTIVE	UNITS
Vth	Poly	>6.6	<-6.6	volts

PROCESS PARAMETERS	N+	P+	POLY	N+BLK	PLY+BLK	M1	M2	UNITS
Sheet Resistance	6.7	7.8	8.0	59.7	313.6	0.08	0.08	ohms/sq
Contact Resistance	10.6	11.0	10.0					4.79 ohms
Gate Oxide Thickness	41							angstrom

PROCESS PARAMETERS	M3	POLY_HRI	M4	M5	M6	N_W	UNITS
Sheet Resistance	0.08		0.08	0.08	0.03	930	ohms/sq
Contact Resistance	9.24		14.05	18.39	20.69		ohms

COMMENTS: BLK is silicide block.

CAPACITANCE PARAMETERS	N+	P+	POLY	M1	M2	M3	M4	M5	M6	R_W	D_N_W	M5P	N_W	UNITS
Area (substrate)	942	1163	106	34	14	9	6	5	3		123		125	aF/um^2
Area (N+active)			8484	55	20	13	11	9	8					aF/um^2
Area (P+active)			8232											aF/um^2
Area (poly)				66	17	10	7	5	4					aF/um^2
Area (metal1)					37	14	9	6	5					aF/um^2
Area (metal2)						35	14	9	6					aF/um^2
Area (metal3)							37	14	9					aF/um^2
Area (metal4)								36	14					aF/um^2
Area (metal5)									34			984		aF/um^2
Area (r well)	920													aF/um^2
Area (d well)										582				aF/um^2
Area (no well)	137													aF/um^2
Fringe (substrate)	212	235		41	35	29	21	14						aF/um
Fringe (poly)				70	39	29	23	20	17					aF/um
Fringe (metal1)					52	34		22	19					aF/um
Fringe (metal2)						48	35	27	22					aF/um
Fringe (metal3)							53	34	27					aF/um
Fringe (metal4)								58	35					aF/um
Fringe (metal5)									55					aF/um
Overlap (N+active)			895											aF/um
Overlap (P+active)			737											aF/um

CIRCUIT PARAMETERS		UNITS
Inverters	K	
Vinv	1.0	0.74 volts
Vinv	1.5	0.78 volts
Vol (100 uA)	2.0	0.08 volts
Voh (100 uA)	2.0	1.63 volts
Vinv	2.0	0.82 volts
Gain	2.0	-23.72
Ring Oscillator Freq.		
D1024_THK (31-stg,3.3V)	300.36	MHz
DIV1024 (31-stg,1.8V)	363.77	MHz
Ring Oscillator Power		
D1024_THK (31-stg,3.3V)	0.07	uW/MHz/gate
DIV1024 (31-stg,1.8V)	0.02	uW/MHz/gate