

On this and subsequent HW assignments there will be problems that require a Verilog or VHDL solution. It will be assumed that students either have a background in Verilog or VHDL or that they will study what is needed to develop this background. There are numerous sources for material on Hardware Description Languages available on line. The text for the course also has a short discussion on HDL in Sec. 1.8 and a more extensive discussion in Appendix A.

Problem 1 1.1 of Weste and Harris (WH) but project to 2020 instead of to 2016.

Problem 2 1.5 of WH but for a 3-input NAND gate instead.

Problem 3 Assume a 300mm wafers cost \$3200. If the defect density on this wafer is $1.2/\text{cm}^2$, determine the cost per good die if the die is square with a side dimension of 5 mm. Assume the soft yield is 100%.

Problem 4 Assume the specified offset voltage for each of the 2 amplifiers in a “dual” op amp is 3mV (that is, $|V_{OS}| < 3\text{mV}$). Determine the soft yield for the “dual” op amp integrated circuit (i.e. both op amps must meet the V_{OS} specification) if the standard deviation of the offset voltage for each op amp is 2 mV and the mean is 0V. Assume the offset voltage for each of the 2 amplifiers are uncorrelated and that the distribution of the offset voltages are Gaussian.

Problem 5 Assume the offset voltage of an operational amplifier is a random variable and that the input offset voltage has a Gaussian distribution with a mean of 0V and a

standard deviation of $\sigma = \frac{A_{VT0}}{\sqrt{A}}$ where A is the gate area of two input transistors of

the op amp and $A_{VT0} = 20\text{mV}\mu\text{m}$ (the units are mV times a micrometer). Determine the area required for the two input transistors if the input offset voltage is to be at most 1.5mV if a soft yield of 98% is required.

Problem 6 Assume a particular function in a 65nm process being used today requires a die area of 0.5cm^2 and that it is fabricated on 300mm wafers that cost \$3200. Predictions now suggest that in a few years, high-end processes will have 7nm feature sizes on 450mm wafers. If the 450mm wafers cost \$10000 each, what will be the approximate cost per good die of the same function if fabricated in the new high-end process with feature sizes of 7nm? When solving this problem, assume the circuit schematic does not change but the transistor sizes scale with the feature size. Neglect the bonding pad areas. Assume the defect density in both processes is the same and is $1.2/\text{cm}^2$ and that the soft yield is 100%.

Problem 7 Using the switch-level model of n-channel and p-channel transistors, design a logic circuit comprised of only n-channel and p-channel transistors that implements the function

$$F = A + \bar{C}$$

Assume the input variables you have available are A and C (the + symbol denotes the Boolean “OR” operation).

Problem 8 Using the switch-level model of the n-channel and p-channel transistors and assuming that $V_{DD}=3V$, determine the output voltage of a 2-input NAND gate if

- a) Both inputs are 0V
- b) One input is 0V and the other input is 3V
- c) Both inputs are 3V

Problem 9 Create in Verilog the following Boolean function. Use only the NOR gate you created in the last homework assignment. Create a test bench to test the Boolean function. Include screenshots of your Verilog code and simulation results.

$$F = \bar{A} \bullet B \bullet C + A \bullet B \bullet \bar{C}$$

(The + symbol denotes the Boolean “OR” operation and the • symbol denotes the Boolean “AND” operation. In future designations of Boolean operations, the “• ” symbol will be suppressed and the same function F will be designated as $F = \bar{A}BC + A\bar{B}\bar{C}$).