

EE 330

Homework 7 Solutions

Problem 1

For the circuit on the left, the anode voltage can't exceed the cathode voltage of 15 V, so diode is off.

$$I_1 = \frac{7}{4k + 2k} = 1.17 \text{ mA}$$

For the circuit on the right, initially consider the diode is off. In this case the resistors act as a voltage divider so $V_D = 15 \cdot (4/6) = 10V > 9V$. So our initial assumption is wrong and the diode is on.

$$I_2 = \frac{9.7}{4k} = 2.4 \text{ mA}$$

Problem 2.

$$\begin{aligned} \text{A. } V_{OUT} &= I(10k\Omega) + 0.575V, V_t = \frac{kT}{q}, I(T) = \left[J_{SX} \left(T^m e^{\frac{-V_{go}}{V_t}} \right) \right] A * e^{\frac{V_D}{V_t}} \\ A * J_{SX} \left[T^m e^{\frac{-V_{go}}{V_t}} \right] * e^{\frac{0.575}{V_t}} &= \frac{0.5A}{\mu^2} * [1.63 * 10^{-18}] * 200\mu^2 * 287.19 * 10^9 \end{aligned}$$

$$\text{B. } V_{OUT} = 145V \rightarrow 20V \text{ (clipping)}$$

$$\text{C. } V_{OUT} = 12.8kV \rightarrow 20V \text{ (clipping)}$$

Problem 3



For the left figure:

Initially assume both diodes to be 'on'. Thus, $V_b = 7 - 0.6 = 6.4V$. Applying KCL at V_a will yields $V_a = 10.7V$. However, this would mean that the current through diode d1 is flowing from cathode to anode, which is incorrect. Thus, our assumption that diode d1 is on is "incorrect". Now, calculating V_a with diode d1 off and d2 on, yields $V_a = 13.5V$. Thus, $I_1 =$

$$\frac{13.5V - 0.6}{4k} = 3.2 \text{ mA}.$$

For the right figure,

Assuming both diodes are on. Thus, $V_e = -30 + 0.6 = -29.4V$ then the voltage at $V_d = -3.64V$ (using KCL). Thus, diode is off and $I_2 = 0$.

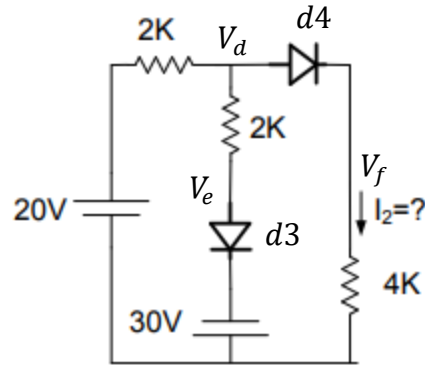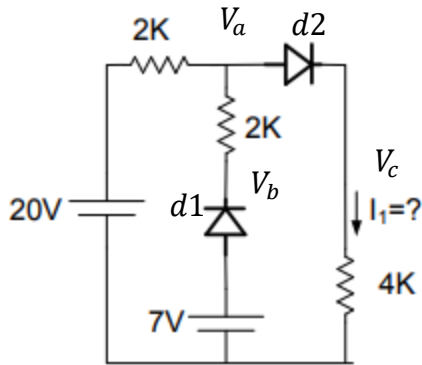

Problem 4



$$R_{sqn} = \frac{1}{\frac{\mu C_{ox} W}{L} (V_{GS} - V_T)} = \frac{1}{\frac{300 \mu A}{V^2} * \frac{5 \mu}{1 \mu} * (1.8 - 0.5)}$$

$$= 512 \Omega$$

$$R_{sqp} = \frac{1}{\frac{75 \mu A}{V^2} * \frac{20 \mu}{2 \mu} * (1.8 - 0.5)} = 1026 \Omega$$

$$C_{GSN} = C_{OX} W L = (2.5 fF \mu^{-2}) (5 \mu * 1 \mu) = 12.5 fF$$

$$C_{GSP} = (2.5 fF \mu^{-2}) (20 \mu * 2 \mu) = 100 fF$$

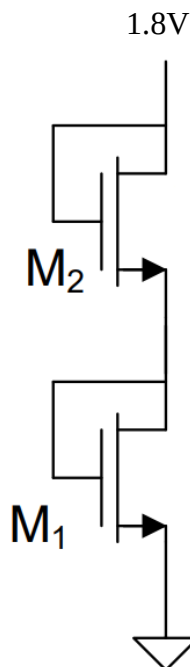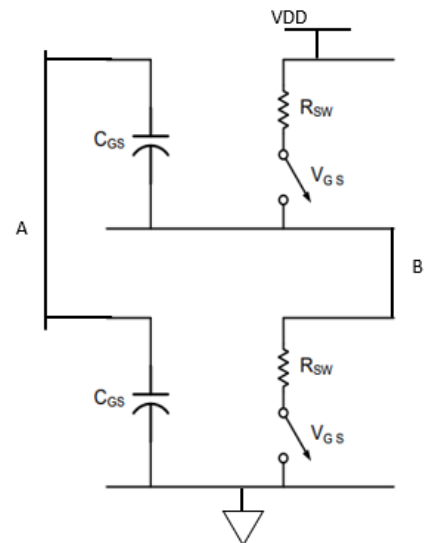

Problem 5

Both transistors are in saturation.

$$u_n C_{OX} * \frac{W_1}{2L_1} * (V_{out} - V_{ss} - V_T)^2 = u_n C_{OX} * \frac{W_2}{2L_2} * (V_{DD} - V_{out} - V_T)^2$$

$$u_n C_{OX} * \frac{W_1}{2L_1} * (1V - 0V - 0.5V)^2 = u_n C_{OX} * \frac{W_2}{2L_2} * (2.5V - 1V - 0.5V)^2$$

$$\frac{W_1}{L_1} * (0.8V - 0.5V)^2 = \frac{W_2}{L_2} * (1.8V - 0.8V - 0.5V)^2$$

$$\frac{(W_2/L_2)}{(W_1/L_1)} = \frac{(0.8V - 0.5V)^2}{(1.8V - 0.8V - 0.5V)^2} = 0.6$$

$$\text{If } \frac{W_1}{L_1} = \frac{2 \mu}{0.2 \mu} = 10 \text{ then } \frac{W_2}{L_2} = \frac{1.2 \mu}{0.2 \mu} = 6$$

Problem 6

$$A.) \alpha = \frac{I_C}{I_E} = \frac{1.00mA}{1.0250mA} = 0.9756$$

$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.9756}{1 - 0.9756} = 40$$

$$B.) \alpha = \frac{1.00mA * 1.005}{1.0250 * (1 - 0.005)} = 0.985$$

$$\beta = \frac{0.985}{1 - 0.985} = 67.56$$

$$Error = \frac{67.56 - 40}{40} = 0.689 = 68.9\%$$

Problem 7

$$I_B = \frac{I_C}{\beta} = \frac{1.00mA}{40} = 25\mu A$$

$$\beta = \frac{I_C}{I_B} = \frac{1.00mA * 1.005}{25\mu A * 0.995} = 40.402$$

$$Error = \frac{40.402 - 40}{40} = 0.01005 = 1.005\%$$

Problem 8.

Assuming saturation:

$$I_{D1} = 75 * 10^{-6} * \frac{5}{2 * 5} * (1.8 - 1 - 0.5)^2 = I_{D2} = 300 * 10^{-6} \left(\frac{5}{10} \right) (V_{out} - 0.5)^2$$

$V_{out} = 0.35V$ or $0.65V$, given $0.35 < 0.5$,

$$V_{out} = 0.65V$$

Problem 9

$$A.) I_C = \frac{8V - 5V}{3k\Omega} = 1.00mA$$

$$V_t = \left(8.617 * 10^{-5} \frac{eV}{K} \right) (300K) = 25.85mV$$

$$I_C = J_s A_E e^{\frac{V_{BE}}{V_t}} = 20 * 10^{-14} * 100 * e^{\frac{V_{BE}}{25.85mV}} \rightarrow V_{BE} = V_x = 0.4582567V$$

$$B.) I_C = J_s A_E e^{\frac{V_{BE}}{V_t}} = 20 * 10^{-14} * 100 * e^{\frac{0.536V - 10uV}{25.85mV}} = 999.6uA$$

$$V_C = 8V - 3k\Omega * 999.6uA = 5.00118V$$

$$Change = \frac{5.00118 - 5}{5} * 100 = 0.0236\%$$

$$C.) V_t = \left(8.617 * 10^{-5} \frac{eV}{K} \right) (301K) = 25.93mV$$

$$I_C = J_s A_E e^{\frac{V_{BE}}{V_t}} = 20 * 10^{-14} * 100 * e^{\frac{V_{BE}}{25.93mV}} \rightarrow V_{BE} = V_x = 0.4596749V$$

$$Change = \frac{0.4596749V - 0.4582567V}{0.4582567V} * 100 = 0.31\%$$

D.) A change of 10uV (0.002%) in V_x resulted in a change of 0.0236% at the output. Similarly, a change of 1°C in temperature(keeping the input constant at 0.458V) would result in 3% change in the output voltage. Thus, the circuit seems to be very sensitive to changes in V_x and temperature.

Problem 10

```

1 | timescale 1ns/1ps
2 | module DFF (D, Q, CLK, EN);
3 |     input D, CLK, EN;
4 |     output Q;
5 |     reg Q;
6 |
7 |     always @(posedge(CLK)) begin
8 |         if(CLK & EN) begin
9 |             assign Q = D;
10 |         end
11 |     else begin
12 |         assign Q = Q;
13 |     end
14 | end
15 | endmodule
16 |

```