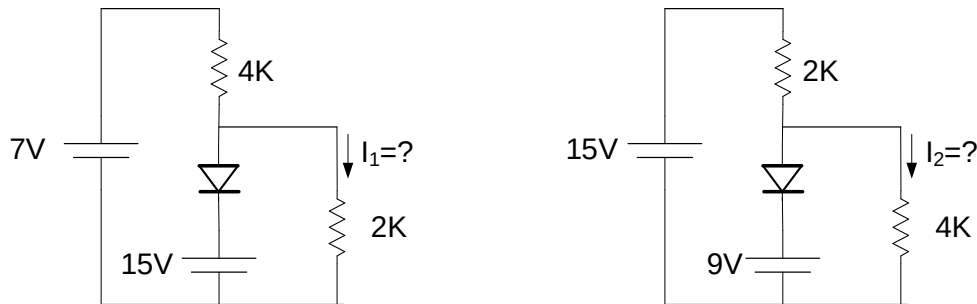


EE 330
Homework 7
Spring 2019 Due Friday March 1

Unless specified to the contrary, assume all n-channel MOS transistors have model parameters $\mu_n C_{OX} = 300 \mu A/V^2$ and $V_{Tn0} = 0.5V$, all p-channel transistors have model parameters $\mu_p C_{OX} = 75 \mu A/V^2$ and $V_{Tp0} = -0.5V$. Correspondingly, assume that at $T=300K$, all npn BJT transistors have model parameters $J_S = 10^{-14} A/\mu^2$ and $\beta = 100$ and all pnp BJT transistors have model parameters $J_S = 10^{-14} A/\mu^2$ and $\beta = 25$. If the emitter area of a transistor is not given, assume it is $100 \mu^2$. If parameters are needed for process characterization beyond what is given, use the measured parameters from the TSMC 0.18 μ process (given in HW6).


Problem 1 Determine the currents indicated with a ? in the following circuits. Assume the diodes are ideal.



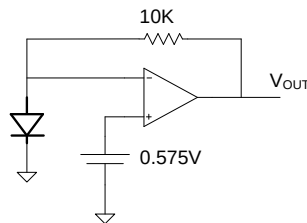
Problem 2

Assume the op amp is ideal and biased with $V_{DD} = 20V$ and $V_{SS} = -20V$ and the diode is characterized by model parameters: $J_{SX} = 0.5 A/\mu^2$, $V_{G0} = 1.17V$, $m = 2.3$. Assume the area of the junction is $200 \mu^2$.


- Determine V_{OUT} if $T = -20^\circ C$
- Repeat part a) if $T = 40^\circ C$.
- Repeat part a) if $T = 120^\circ C$



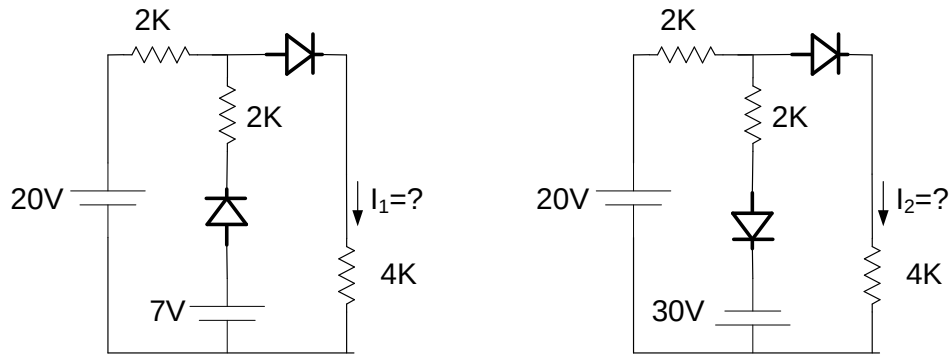Problem 3 Determine the currents indicated with a ? in the following circuits. Assume the diodes are ideal.



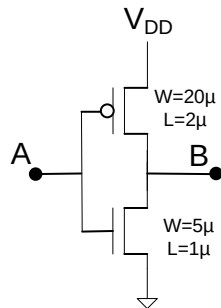
Problem 4 Consider the following inverter. Determine the switch-level model for this inverter that includes the input capacitance and the pull-up and pull-down resistors.



Problem 5 Design a circuit using only MOS transistors (no resistors or other components) that has an output voltage of 0.8V when biased with a single dc power supply of 1.8V.

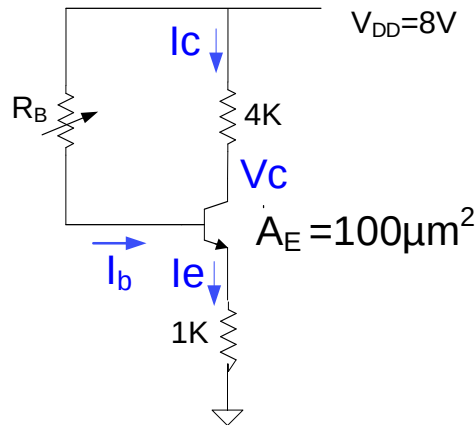Problem 6 The following circuit was constructed for measuring the β of the bipolar transistor. To obtain the β , the resistor R_B was adjusted so that the current I_C was precisely 1.000mA. The current I_E was then measured to be 1.0250mA. From these measurements the parameter α of the transistor was obtained and then β was calculated using the well-known relationship between α and β .


- What is the value of β for the transistor?
- What would be the worst-case error (in percent) in measuring the β of the transistor using this approach if the current measurements were only accurate to $\pm 0.5\%$?



Problem 7 As an alternative to measuring β in the circuit for the previous problem (assuming β is the value determined in part a of the previous problem), the currents I_b and I_c were measured. What would be the worst-case error (in percent) in measuring the β of the transistor using this alternative approach if the current measurements of I_b and I_c were only accurate to $\pm 0.5\%$?


Problem 8

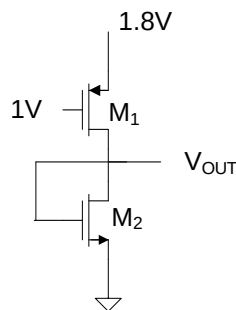- a) Determine V_{OUT} for the following circuit. Assume the devices M_1 and M_2 are identically sized with $W=L=5\mu$. The relevant model parameters of the devices are $V_{TN}=0.5V$, $V_{TP}=-0.5V$, $\mu_n C_{OX}=300\mu A V^{-2}$ and $\mu_p C_{OX}=75\mu A V^{-2}$.



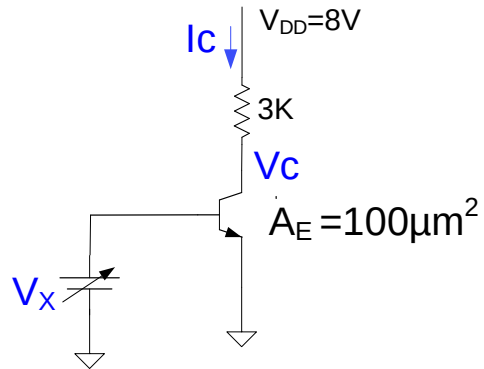Problem 9 Assume the transistor in the following circuit is operating at $T=300K$ and the β of the transistor is 200. Assume the parameter $J_{SX} = 20 \times 10^{-14} A / \mu^2$.

- Precisely determine the value of V_X required to force the collector voltage, V_C , to be 5V.
- If the value of V_X is decreased by 10uV from the value determined by V_X in part a), how much change will occur in the voltage V_C ?
- If the temperature is increased by $1^\circ C$, how much will the voltage obtained in part a) change?
- Comment on how sensitive this circuit is to change in V_X and to changes in T .



Problem 10 Using ModelSim create a D-flip flop. The D-flip flop should take in a one-bit input and produce a one-bit output. Turn in the D-flip flop code, the test bench code, and the output waveform.

