

SOLUTIONS:

Problem 1:

First we solve for quiescent I_{DS} :

$$I_{DSQ} = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 = \frac{350\mu}{2} \frac{12}{2} (1 - 0.5)^2 = 0.2625 \text{ mA}$$

Then we will use I_{DSQ} to get g_m :

$$g_m = \frac{2I_{DSQ}}{V_{GS} - V_T} = \frac{2 * 0.2625 \text{ m}}{1 - 0.5} = 1.05 \text{ mA/V}$$

Solving for small signal gain we get the following (we will ignore g_{ds}):

$$-g_m V_{gs} = V_{ds} \frac{1}{R_L} \rightarrow \frac{V_{ds}}{V_{gs}} = \frac{V_{out}}{V_{in}} = -g_m * R_L = -1.05 \text{ m} * 5 \text{ k} = -5.25 \text{ V/V}$$

Problem 2:

First we solve for quiescent I_{DS} :

$$I_{DSQ} = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 = \frac{350\mu}{2} \frac{6}{4} (1 - 0.5)^2 = 0.065625 \text{ mA}$$

Then we will use I_{DSQ} to get g_m :


$$g_m = \frac{2I_{DSQ}}{V_{GS} - V_T} = \frac{2 * 0.065625 \text{ m}}{1 - 0.5} = 0.2625 \text{ mA/V}$$

Solving for small signal gain we get the following (we will ignore g_{ds}):

$$-g_m V_{in} = V_{out} \frac{1}{R_L} \rightarrow \frac{V_{out}}{V_{in}} = -g_m * R_L = -0.2625 \text{ m} * 4 \text{ k} = -1.05 \text{ V/V}$$

Problem 3:

a)

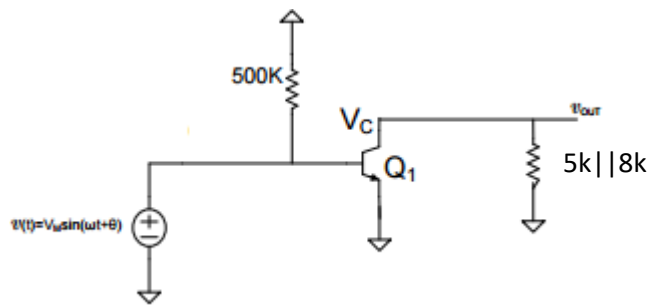

b) $V_{CQ} = 10V - (5k * I_{CQ})$

$$I_{CQ} = \frac{\beta(10 - 0.6)}{500k} = 1.88 \text{ mA}$$

$$V_{CQ} = 10V - (5k * 1.88m)$$

$$V_{CQ} = 0.6V$$

$$V_{outQ} = 0$$

c) $v_{out} = (-g_m v_{IN}) * (\frac{1}{g_o} || R_L)$

$$A_v = \frac{v_{OUT}}{v_{in}} = -g_m (\frac{1}{g_o} || R_L)$$

d) Approximate gain, $A_V = -g_m R_L$


$$A_V = -g_m (5k || 8k) = -g_m (3.077k)$$

$$g_m = \frac{I_Q}{V_t} = \frac{1.88 \text{ m}}{0.0258} = 0.0729V$$

$$A_V = -0.0729 * 3077$$


$$A_V = -224.22 \text{ V/V}$$

Problem 4:

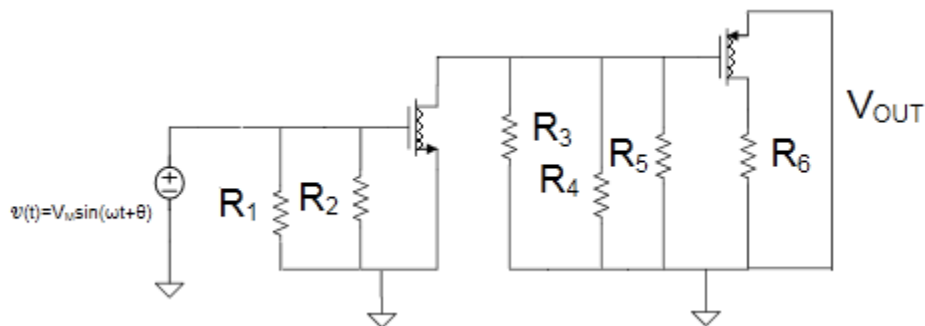

Problem 5:

a)

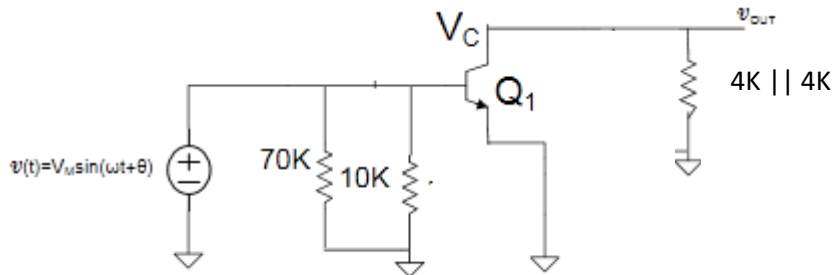

b)

$$V_B = 32 * \left(\frac{10}{10 + 70} \right) \text{ k} = 4\text{V}$$

$$I_{CQ} = \frac{4 - 0.6}{2\text{k}} = 1.7 \text{ mA}$$

$$V_{CQ} = 32 - (2\text{k})(I_{CQ})$$

$$V_{CQ} = 26.6\text{V}$$

$$V_{outq} = 0\text{V}$$

c) $v_{out} = (-g_m v_{IN}) * \left(\frac{1}{g_o} // R_L \right)$

$$A_v = \frac{v_{OUT}}{v_{in}} = -g_m \left(\frac{1}{g_o} // R_L \right) \approx -g_m R_L$$

d)

$$A_v = \frac{I_{cq} R_L}{v_t} = \frac{2000 * 0.0017}{0.0258} = 131.783 \frac{\text{V}}{\text{V}}$$

Problem 6:

MOSFET:

$V_{gs} = V_{ds}$, putting a test voltage V_{test} and solving for current we get:

$$I_{test} = g_m * V_{test} + V_{test} * g_o \rightarrow \frac{V_{test}}{I_{test}} = \frac{1}{g_m + g_o} \approx \frac{1}{g_m}$$

$$g_m = \sqrt{2 * \mu_n C_{ox} \left(\frac{W}{L} \right) * I_D} = 1.183 \text{ m}$$

$$R_{eq} = g_m^{-1} = 845.15 \text{ k}\Omega$$

BJT:



$$V * (g_m + g_\pi + g_o) = I \rightarrow R_{eq} = \frac{1}{(g_m + g_\pi + g_o)} \cong \frac{1}{g_m}$$

$$g_m = \frac{I_{CQ}}{V_t} = \frac{2 \text{ mA}}{0.0258}$$

$$R_{eq} = 12.9 \Omega$$

Problem 7:

a.) DC equivalent circuit

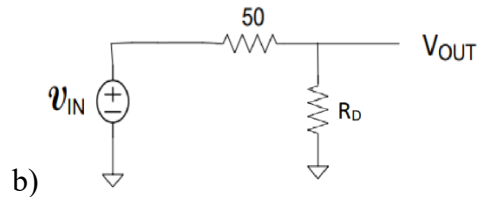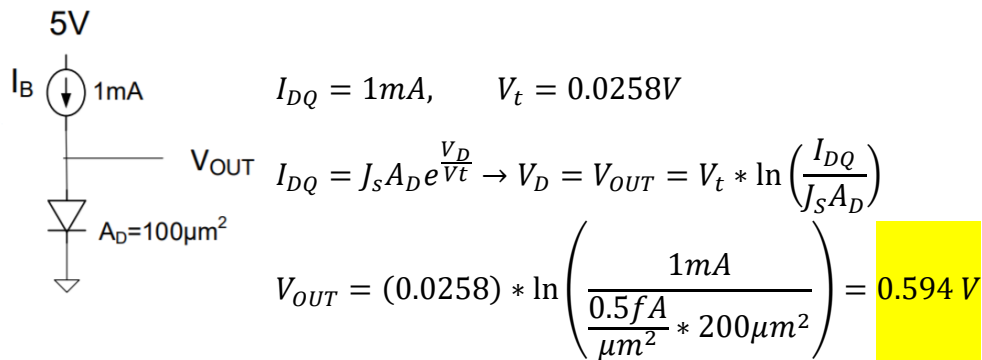

c.) Treat Diode as a box with V_d as one terminal and I_d as another, we know that $V_D = V_t * \ln\left(\frac{I_{DQ}}{J_S A_D}\right)$

$$\frac{dV_D}{dI_{DQ}} = V_t * \frac{J_S A_D}{I_{DQ}} * J_S A_D = \frac{V_t}{I_{DQ}} = R_D$$

$$R_D = \frac{V_t}{I_{DQ}} = \frac{0.0258}{1 \text{ mA}} = 25.8 \Omega$$


$$v_{out} = \frac{R_D}{R_D + 50 \Omega} v_{in}$$

$$A_v = \frac{v_{out}}{v_{in}} = \frac{R_D}{R_D + 50 \Omega} = \frac{25.8 \Omega}{25.8 \Omega + 50 \Omega} = 0.34 \text{ V/V}$$

$$\text{d) } R_D = \frac{V_t}{I_{DQ}} = \frac{0.0258}{5 \text{ mA}} = 5.16 \Omega \rightarrow A_v = \frac{v_{out}}{v_{in}} = \frac{R_D}{R_D + 50 \Omega} = \frac{5.16 \Omega}{5.16 \Omega + 50 \Omega} = 0.0935 \text{ V/V}$$

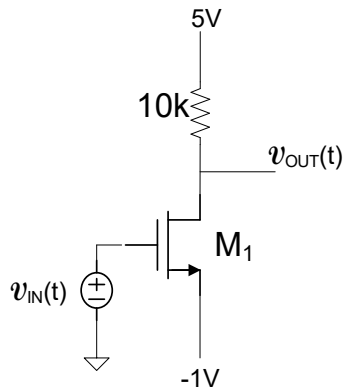Problem 8:

There are multiple approaches to this problem, one is shown below:



I will start from my gain and load specifications, I know that for my circuit choice, my gain has the following relationship:

$$A_v = \frac{v_{OUT}}{v_{in}} = -g_m \left(\frac{1}{g_o} // R_L \right) \approx -g_m R_L = -15 \rightarrow gm = \frac{A_v}{R_L} = \frac{15}{10000} = 1.5 \text{ mA/V}$$

I also know $g_m = \frac{2I_{DSQ}}{V_{GS} - V_T}$, I can set $V_s = -1V$ and solve for I_{DSQ} to get 0.375 mA

$V_{outQ} = V_{DD} - I_{DSQ} * R_L$ and for the transistor to be in saturation (and for our models to hold) we need $V_{outQ} \geq V_{GS} - V_t \geq 0.5$, solving this inequality:

$$0.5 \leq V_{DD} - I_{DSQ} * R_L \rightarrow V_{DD} \geq 0.5 + I_{DSQ} * R_L \geq 4.25 \text{ V}$$

I will choose V_{DD} to be $5V$.

Problem 9:

Code:

```
Ln# |  
1 | `timescale 1ns/1ps  
2 | module demux(F, a,b,c, Y1,Y2,Y3,Y4,Y5,Y6,Y7,Y8);  
3 | input F, a, b, c; //inputs  
4 | output Y1,Y2,Y3,Y4,Y5,Y6,Y7,Y8; // output variables  
5 | reg y1,y2,y3,y4,y5,y6,y7,y8; //internal variables  
6 |  
7 | assign Y1 = y1;  
8 | assign Y2 = y2;  
9 | assign Y3 = y3;  
10 | assign Y4 = y4;  
11 | assign Y5 = y5;  
12 | assign Y6 = y6;  
13 | assign Y7 = y7;  
14 | assign Y8 = y8;  
15 |  
16 | always @ (F or a or b or c)  
17 | begin  
18 | case({a,b,c})  
19 | 3'b000: begin  
20 | y1 = F;  
21 | {y2,y3,y4,y5,y6,y7,y8} = 7'b0000000;  
22 | end  
23 | 3'b001: begin  
24 | y2 = F;  
25 | {y1,y3,y4,y5,y6,y7,y8} = 7'b0000000;  
26 | end  
27 | 3'b010: begin  
28 | y3 = F;  
29 | {y1,y2,y4,y5,y6,y7,y8} = 7'b0000000;  
30 | end  
31 | 3'b011: begin  
32 | y4 = F;  
33 | {y2,y3,y1,y5,y6,y7,y8} = 7'b0000000;  
34 | end  
35 | 3'b100: begin  
36 | y5 = F;  
37 | {y2,y3,y4,y1,y6,y7,y8} = 7'b0000000;  
38 | end  
39 | 3'b101: begin  
40 | y6 = F;  
41 | {y2,y3,y4,y5,y1,y7,y8} = 7'b0000000;  
42 | end  
43 | 3'b110: begin  
44 | y7 = F;  
45 | {y2,y3,y4,y5,y6,y1,y8} = 7'b0000000;  
46 | end  
47 | 3'b111: begin  
48 | y8 = F;  
49 | {y2,y3,y4,y5,y6,y7,y1} = 7'b0000000;  
50 | end  
51 | endcase  
52 | end  
53 | endmodule  
54 |
```

Testbench:

Ln#	
1	<code>`timescale 1ns/1ps</code>
2	<code>module demux_tb();</code>
3	<code>reg F,a,b,c;</code>
4	<code>wire Y1,Y2,Y3,Y4,Y5,Y6,Y7,Y8;</code>
5	
6	<code>demux d(F, a,b,c, Y1,Y2,Y3,Y4,Y5,Y6,Y7,Y8);</code>
7	
8	<code>initial</code>
9	<code>begin</code>
10	<code>F = 1;</code>
11	<code>a = 0;</code>
12	<code>b = 0;</code>
13	<code>c = 0;</code>
14	<code>end</code>
15	
16	<code>always</code>
17	<code>#10 c = ~c;</code>
18	<code>always</code>
19	<code>#20 b = ~b;</code>
20	<code>always</code>
21	<code>#40 a = ~a;</code>
22	
23	<code>endmodule</code>
24	

Waveform:

