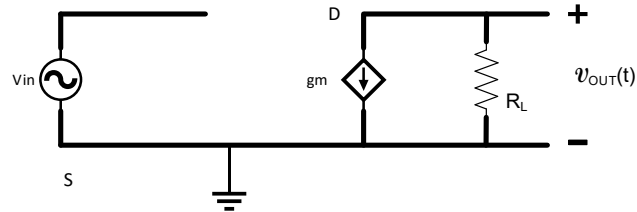


SOLUTIONS:

Problem 1:


a) The small signal equivalent signal is shown below:



Note that the output resistance was simplified $\frac{1}{g_0} || R_L \approx R_L$


$$-g_m V_{gs} = V_{ds} \frac{1}{R_L} \rightarrow \frac{V_{ds}}{V_{gs}} = \frac{V_{out}}{V_{in}} = -g_m * R_L$$

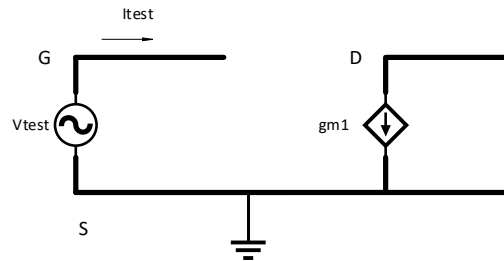b) The small signal equivalent signal is shown below:



There is no current flowing in the input terminal (due to the open circuit). $R_{in} = \infty$

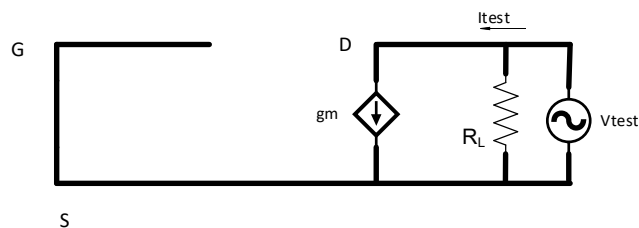c) The small signal equivalent signal is shown below:



$$\text{Since } V_{in} = 0, V_T = I_T * R_L \rightarrow R_{out} = \frac{V_T}{I_T} = R_L$$

Problem 2:

$$a) g_m V_{gs} = V_{ds} \frac{1}{R_L} \rightarrow \frac{V_{ds}}{V_{gs}} = \frac{V_{out}}{V_{in}} = g_m * R_L$$

$$b) I_T = I_T * g_m \rightarrow R_{in} = \frac{V_T}{I_T} = g_m^{-1}$$

$$c) V_T = I_T * R_L \rightarrow R_{out} = \frac{V_T}{I_T} = R_L$$

Problem 3:

$$a) g_m(V_{in} - V_{out}) = V_{out} \frac{1}{R_L} \rightarrow \frac{V_{out}}{V_{in}} = \frac{g_m}{\frac{1}{R_L} + g_m} \approx 1$$

$$b) R_{in} = \frac{V_T}{I_T} = \infty$$

$$c) I_T = V_T * \frac{1}{R_L} + V_T * g_m \approx V_T * g_m \rightarrow R_{out} = \frac{V_T}{I_T} = g_m^{-1}$$

Problem 4:

$$I_{DSQ} = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 = \frac{350 \mu}{2} \frac{W}{L} (1 - 0.5)^2 = 43.75 \left(\frac{W}{L}\right) \mu$$

$$A_v = \frac{V_{out}}{V_{in}} = -g_m * R_L = -10 \rightarrow gm = \frac{10}{20 k} = 0.5 m$$

$$g_m = \frac{2I_{DSQ}}{V_{GS} - V_T} \rightarrow 0.5 m = \frac{2 * 43.75 \left(\frac{W}{L}\right) \mu}{1 - 0.5} \rightarrow \frac{W}{L} = 2.86$$

Problem 5:

a)

$$y_{11} = \frac{dI_1}{dV_1} = V_2^3, \quad y_{12} = \frac{dI_1}{dV_2} = 3V_1V_2^2$$

$$y_{21} = \frac{dI_2}{dV_1} = 0.01V_1V_2e^{0.2V_1^2V_2}, \quad y_{22} = \frac{dI_2}{dV_2} = 0.05V_1^2e^{0.2V_1^2V_2}$$

b)

$$y_{11} = 1^3 = 1 \frac{A}{V}, \quad y_{12} = 3(5)(1)^2 = 15 \frac{A}{V}$$

$$y_{21} = 0.01(5)(1)e^{0.2(5^2)1} = 7.42 \frac{A}{V}, \quad y_{22} = 0.05(5^2)e^{0.2(5^2)1} = 185.52 \frac{A}{V}$$

c)

$$I_{1Q} = V_1V_2^3 = 5(1^3) = 5 \text{ A}$$

$$I_{2Q} = 0.25e^{0.2V_1^2V_2} = 0.25e^{0.2(5^2)1} = 37.1 \text{ A}$$

d)

$$i_1 = 1(1mV_{RMS}) + 15(2mV_{RMS}) = 31 \text{ mI}_{RMS}$$

$$i_2 = 7.42(1mV_{RMS}) + 185.52(2mV_{RMS}) = 378.46 \text{ mI}_{RMS}$$

Problem 6:

The transistor is in saturation. $V_{DS} = 4 + 2 = 6\text{V}$ & $V_{GS} - V_T = 0 + 2 - 0.5 = 1.5\text{V}$

$$I_{DS} = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 = \frac{350\mu}{2} \frac{12}{4} (2 - 0.5)^2 = 1.18125 \text{ mA}$$


$$g_m = \frac{2I_{DSQ}}{V_{GS} - V_T} = \frac{2 * 1.18125 \text{ m}}{2 - 0.5} = 1.575 \text{ m}$$

$$V_{OUT} = I_f * R_f = g_m * v_{in} * R_f = 1.575 \text{ m} * 25 \text{ mV} * 1.25 \text{ k} = 49.22 \text{ mV}$$

V_{OUT} is sinusoidal 1 KHz signal with 0-P amplitude of 49.22 mV

Problem 7:

a.) Small signal equivalent circuit

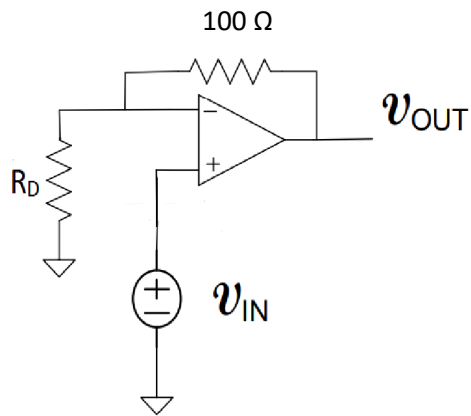

$$R_D = \frac{V_t}{I_{DQ}} = \frac{25.85\text{mV}}{1\text{mA}} = 25.85\ \Omega$$

$$A_v = 1 + \frac{100\ \Omega}{R_D} = 1 + \frac{100\ \Omega}{25.85\ \Omega} = 4.87\ \text{V/V}$$

b.) $R_D = \frac{25.85\text{mV}}{10\text{mA}} = 2.59\ \Omega$

$$A_v = 1 + \frac{100\ \Omega}{2.59\ \Omega} = 39.68\ \text{V/V}$$

Problem 8:

Code:

```
1 | timescale 1ns/1ps
2 | module add_mul (A,B,S,F);
3 |   input[3:0]    A,B;
4 |   input         S;
5 |   output[7:0]   F;
6 |
7 |   assign F = S ? A * B : A + B;
8 | endmodule
```

Test bench:

```
1  | `timescale 1ns/1ps
2  | module add_mul_tb();
3  |     reg[3:0] A,B;
4  |     reg      S;
5  |     wire[7:0] F;
6  |
7  |     add_mul a_m(A,B,S,F);
8  |
9  |     initial begin
10 |         A = 10;
11 |         B = 2;
12 |         S = 0;
13 |     end
14 |
15 |     always #10 S = -S;
16 |     always #20 A = A + 1;
17 |     always #30 B = B + 1;
18 |
19 | endmodule
```

Waveform:

 	/add_mul_tb/A	4'd10	10				11				12				13
 	/add_mul_tb/B	4'd2	2				3								4
 	/add_mul_tb/S	1'd0													
 	/add_mul_tb/F	8'd12	12		20		13		33		15		36		17