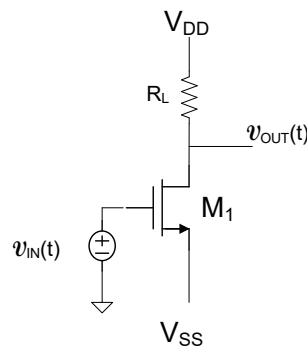


EE 330  
Homework 10  
Spring 2019  
Due on Fri March 29<sup>th</sup>


Unless specified to the contrary, assume all n-channel MOS transistors have model parameters  $\mu_n C_{OX} = 350 \mu\text{A}/\text{V}^2$  and  $V_{Tn} = 0.5\text{V}$ , all p-channel transistors have model parameters  $\mu_p C_{OX} = 70 \mu\text{A}/\text{V}^2$  and  $V_{Tp} = -0.5\text{V}$ . Correspondingly, assume all npn BJT transistors have model parameters  $J_S = 10^{-14} \text{A}/\mu^2$  and  $\beta = 100$  and all pnp BJT transistors have model parameters  $J_S = 10^{-14} \text{A}/\mu^2$  and  $\beta = 25$ . If the emitter area of a transistor is not given, assume it is  $100 \mu^2$ . If parameters are needed for CMOS process characterization beyond what is given, use the measured parameters from the TSMC  $0.18 \mu$  process given in previous assignments as model parameters. Assume all diodes are characterized by the model parameters  $J_{SX} = 0.5 \text{fA}/\mu\text{m}^2$ ,  $V_{G0} = 1.17\text{V}$ , and  $m = 2.3$ .

**Problem 1** The amplifier shown below is called a common source amplifier. You can assume the transistor is operating in saturation.




- Draw the small signal equivalent circuit (showing  $g_m$  and  $g_0$ ), and solve for the small signal gain.
- Solve for the input resistance of this amplifier by shorting the output terminal and applying a test voltage source  $V_T$  at the input terminal, then solving for  $R_{in} = \frac{V_T}{I_T}$ , where  $I_T$  is the test current supplied by  $V_T$ . Redraw the small signal equivalent circuit (showing  $g_m$  and  $g_0$ ) and apply the appropriate changes.
- Solve for the output resistance of this amplifier by shorting the input terminal and applying a test voltage source  $V_T$  at the output terminal, then solving for  $R_{out} = \frac{V_T}{I_T}$ , where  $I_T$  is the test current supplied by  $V_T$ . Redraw the small signal equivalent circuit (showing  $g_m$  and  $g_0$ ) and apply the appropriate changes.

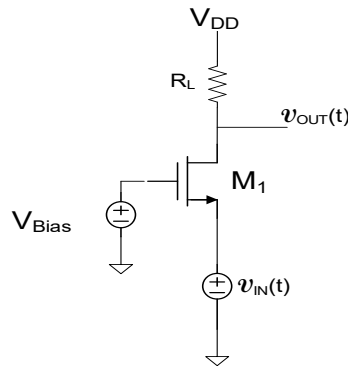
**Problem 2** Repeat **Problem 1** but for the amplifier shown below. This amplifier is called a common gate amplifier.



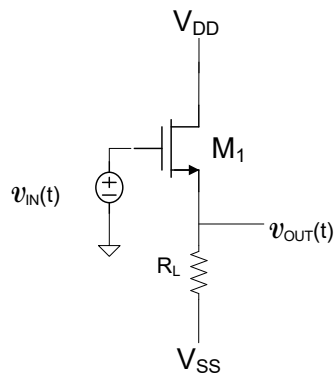**Problem 3** Repeat **Problem 1** but for the amplifier shown below. This amplifier is called a common drain amplifier.



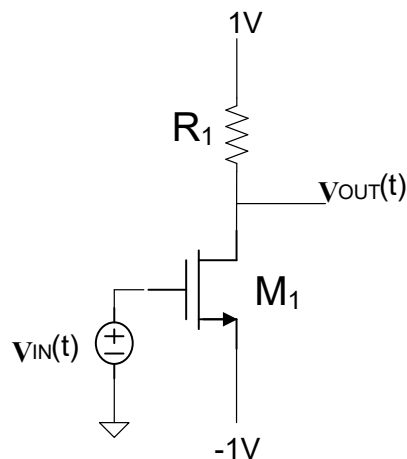
**Problem 4** Consider the following circuit where  $R_1 = 20\text{K}$ . Size the device so that the amplifier has a voltage gain of -10. Assume  $M_1$  is in saturation.



**Problem 5** Consider a device characterized by the equations


$$I_1 = V_1 V_2^3$$

$$I_2 = 0.25 e^{0.2 V_1^2 V_2}$$

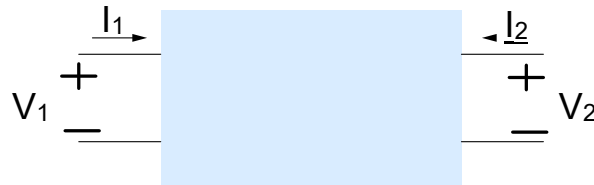


- Determine the small signal model for a two-terminal device characterized by the equations given above
- Determine the numerical values for the small signal model parameters if the quiescent value of the port voltages are  $V_1=5V$ ,  $V_2=1V$ .
- Determine the quiescent currents at the Q-point established in part b.
- Determine the small signal currents  $i_1$  and  $i_2$  if the small signal voltages  $v_1$  and  $v_2$  were measured to be  $1mV_{RMS}$  and  $2mV_{RMS}$  respectively. Assume the same Q-point as established in part b.

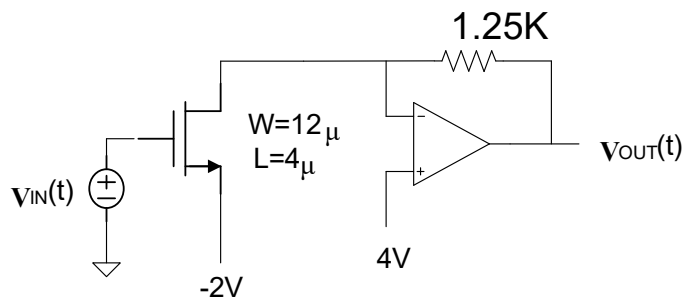**Problem 6** Determine the small signal output voltage if the small signal input voltage is a sinusoidal 1 KHz signal with 0-P amplitude of 25mV.



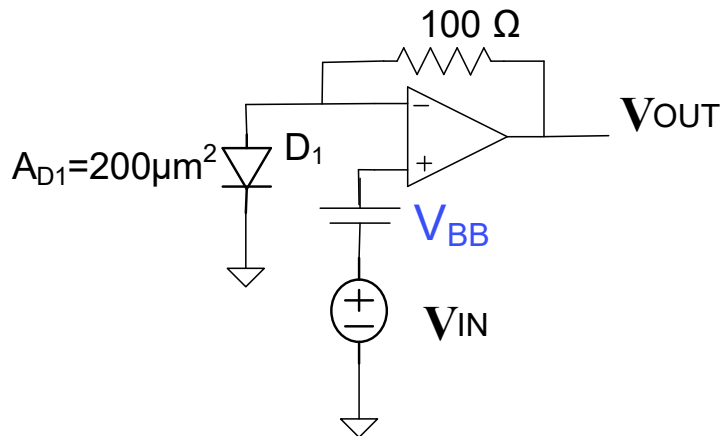**Problem 7** Consider the following circuit operating at  $T=300\text{K}$ . Assume  $V_{\text{IN}}$  is a small-signal voltage source.

- If the voltage  $V_{\text{BB}}$  is adjusted so that the quiescent diode current is  $1\text{mA}$ , determine the small signal voltage gain.
- Repeat part a) if  $V_{\text{BB}}$  is adjusted so that the quiescent diode current is  $10\text{mA}$



**Problem 8** Using ModelSim create a circuit that takes in 2 4-bit inputs and computes their sum or product depending on a select signal  $S$ . If  $S$  is 0, the output should be  $A + B$ , if  $S$  is 1, the output should be  $A * B$ . Choose the output size so it won't overflow.

