

EE 330

Lecture 25

- Small Signal Analysis Example Circuits
- Graphical Small Signal Analysis
- Model Extensions and Simplifications

Small-signal Operation of Nonlinear Circuits

- Small-signal principles
- Example Circuit
- Small-Signal Models
- • Small-Signal Analysis of Nonlinear Circuits

Recall:

Alternative Approach to small-signal analysis of nonlinear networks

1. Linearize nonlinear devices

(have small-signal model for key devices!)

2. Replace all devices with small-signal equivalent

3. Solve linear small-signal network

- Remember that the small-signal model is operating point dependent!
- Thus need Q-point to obtain values for small signal parameters
- Expressions for circuit characteristics such as gain can be expressed in terms of small-signal parameters or nonlinear device model parameters and Q-points
- Expressions for circuit characteristics such as gain in terms of small-signal parameters often give little insight into performance or design





Recall:

Q-point Computation

- Open all caps and short all inductors
- Assume correct region for all nonlinear devices
 - Diodes on, MOS in saturation, BJT in forward active
- Write down device models and KCL's
 - One KCL at each non-trivial node in nodal analysis
 - For hand calculation, use simplified device models
- Solve the simultaneous equations
 - Produce Q values for all node voltages and branch currents
- Check correctness of assumptions in 2nd step


Recall:

Small Signal Model for Active Devices

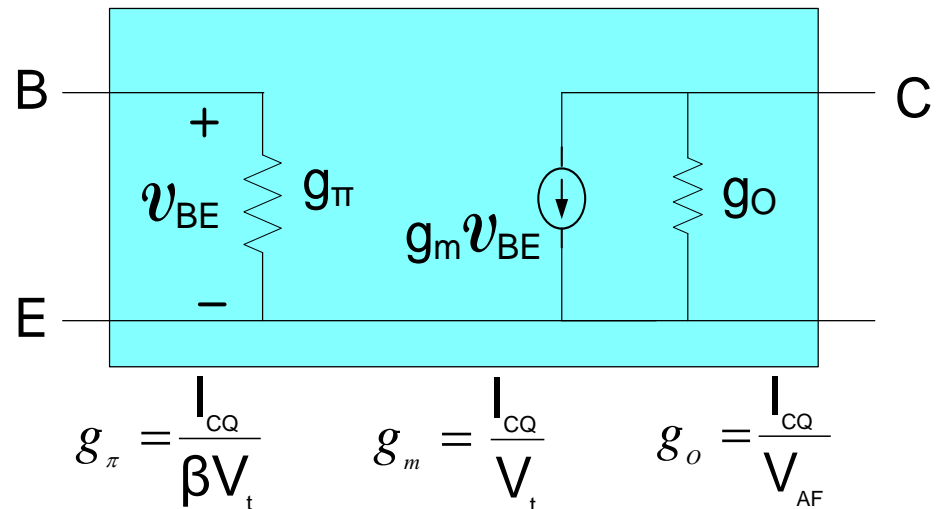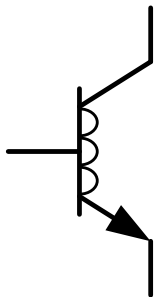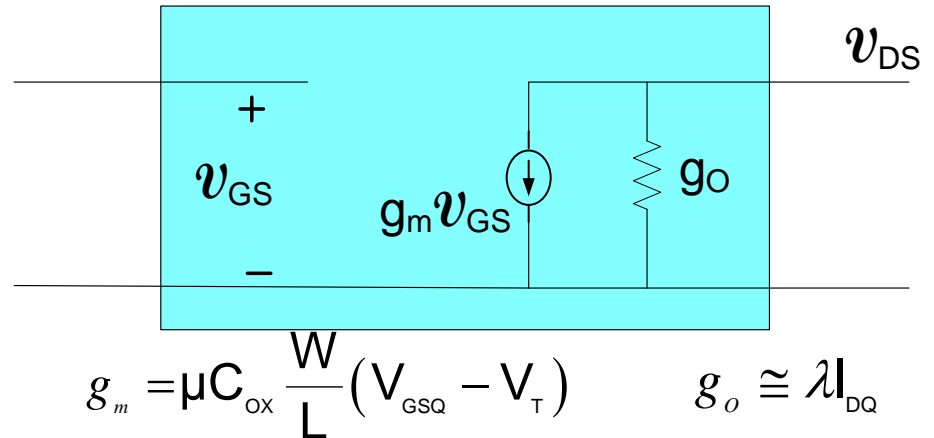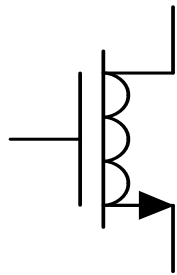

Recall:

Small Signal Model for Active Devices

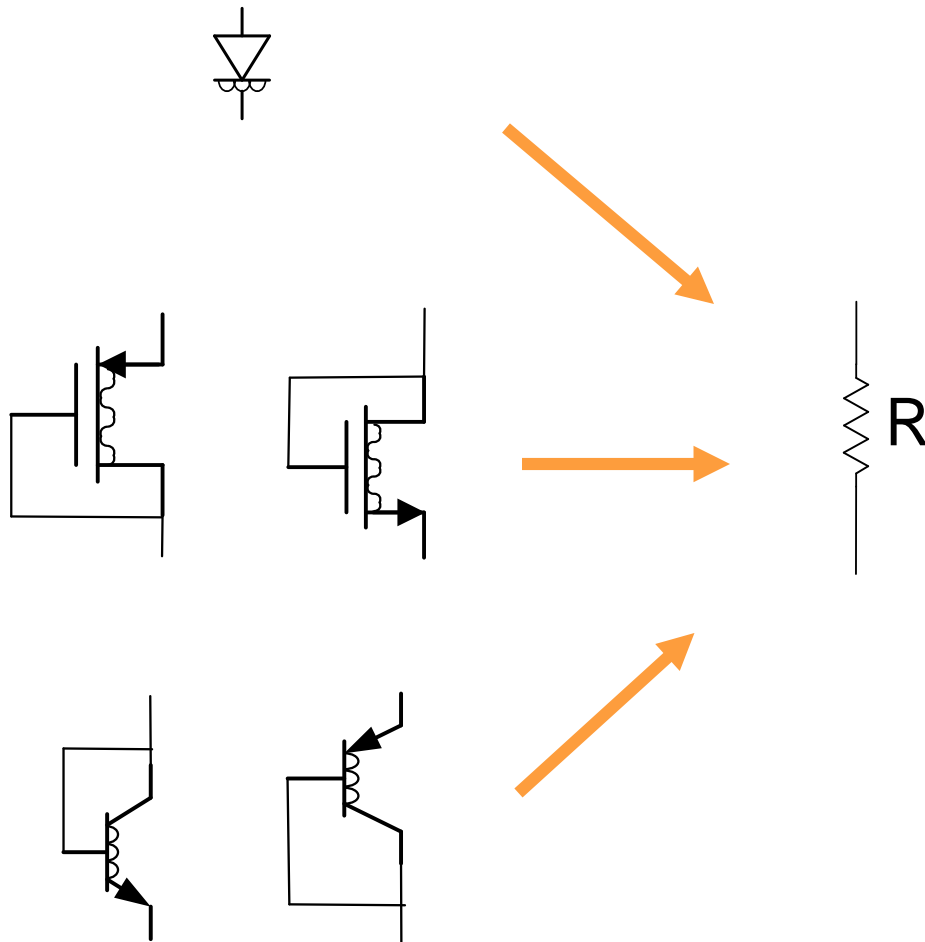


$$\frac{1}{R} = g_{diode} = \frac{I_{diodeQ}}{V_t}$$

$$\frac{1}{R} = g_m = \frac{2I_{DQ}}{V_{GSQ} - V_{TH}}$$

$$\frac{1}{R} = g_m = \frac{I_{CQ}}{V_t}$$

Recall: Small-signal analysis example

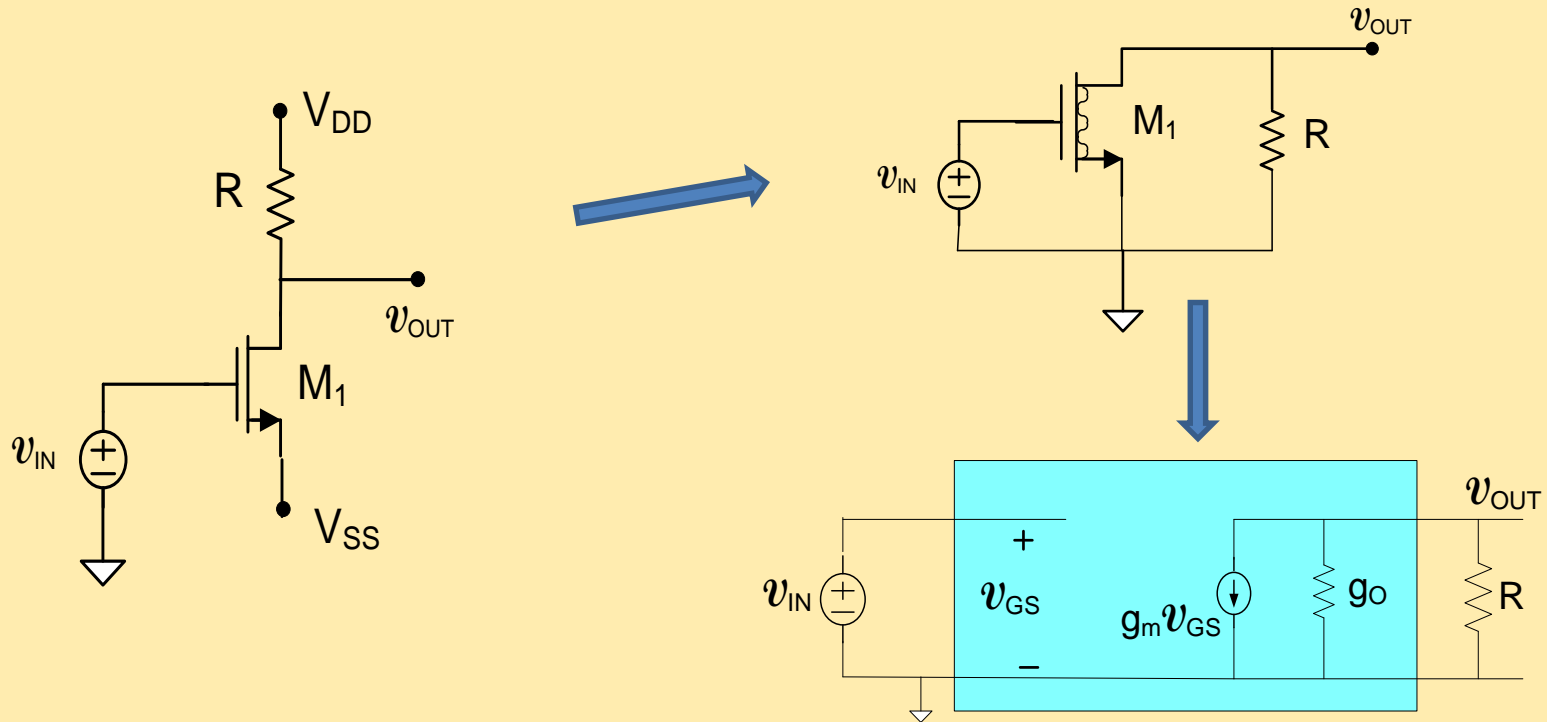

$$A_v = \frac{2I_{DQ} R}{[V_{SS} + V_T]}$$


$$A_v = -g_m R$$

$$A_v = \frac{2I_{DQ} R}{[V_{SS} + V_T]}$$

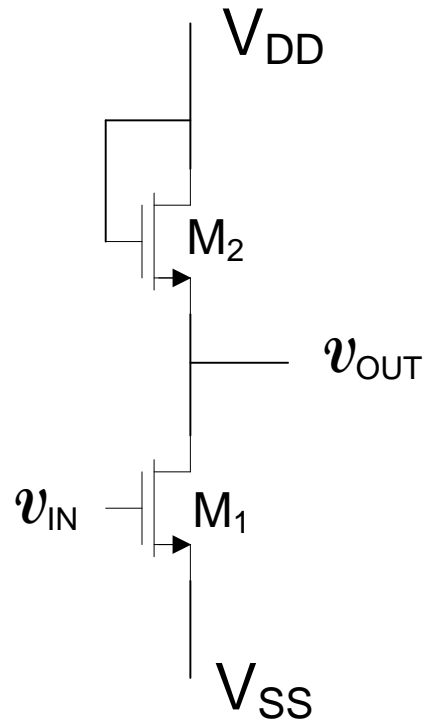
Example:

Assume M_1 and M_2 are operating in the saturation region and that $\lambda=0$

- Determine the small signal voltage gain $A_V = v_{OUT}/v_{IN}$ in terms of the small-signal model parameters
- Determine the small signal voltage gain $A_V = v_{OUT}/v_{IN}$ in terms of the Q-points and the nonlinear model parameters





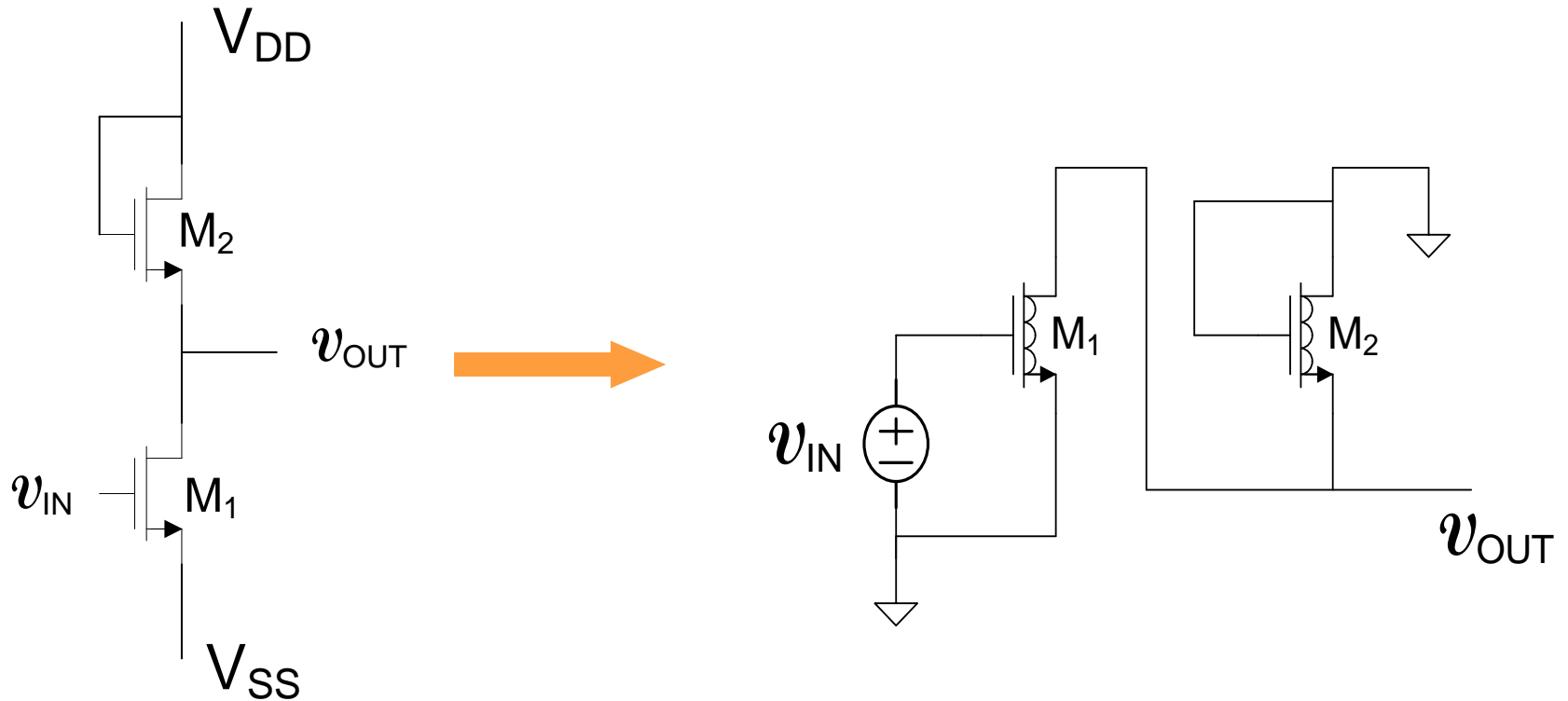Example: Determine the small signal voltage gain $A_V = v_{OUT}/v_{IN}$. Assume M_1 and M_2 are operating in the saturation region and that $\lambda=0$




Small-signal circuit

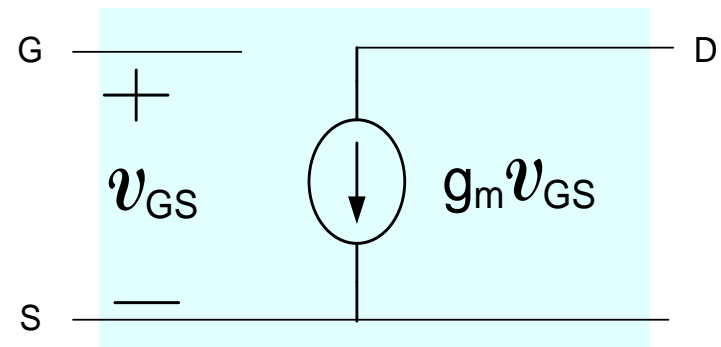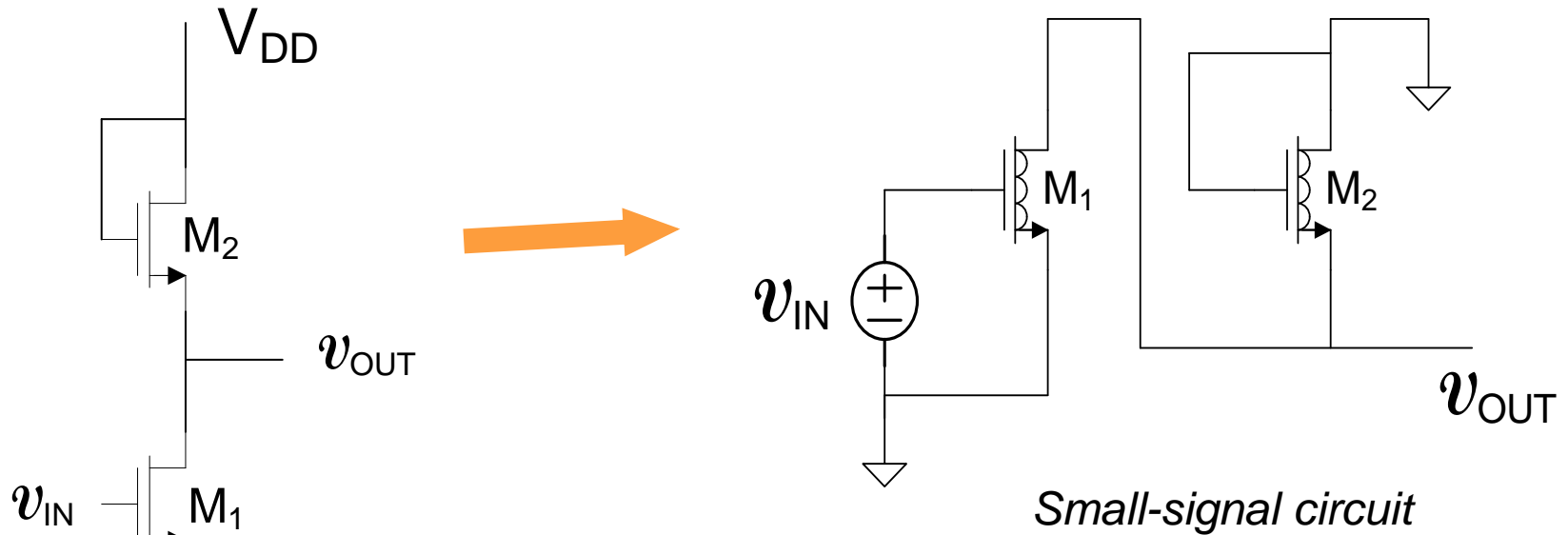Example: Determine the small signal voltage gain $A_V = v_{OUT}/v_{IN}$. Assume M_1 and M_2 are operating in the saturation region and that $\lambda=0$




Small-signal MOSFET model for $\lambda=0$

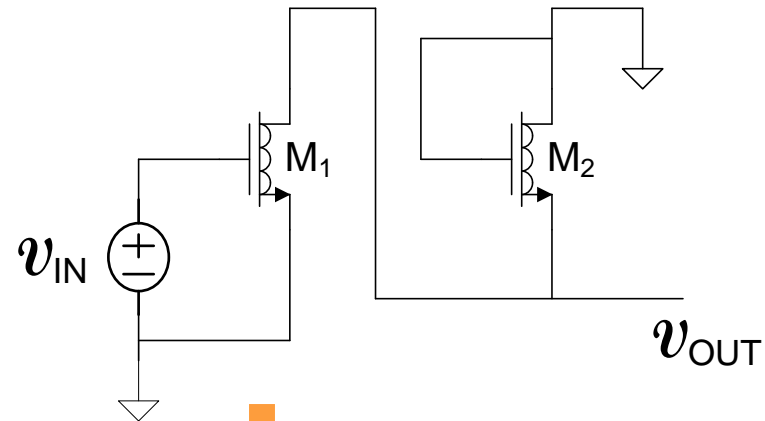Example: Determine the small signal voltage gain $A_V = v_{OUT}/v_{IN}$. Assume M_1 and M_2 are operating in the saturation region and that $\lambda=0$




Small-signal circuit for $\lambda=0$

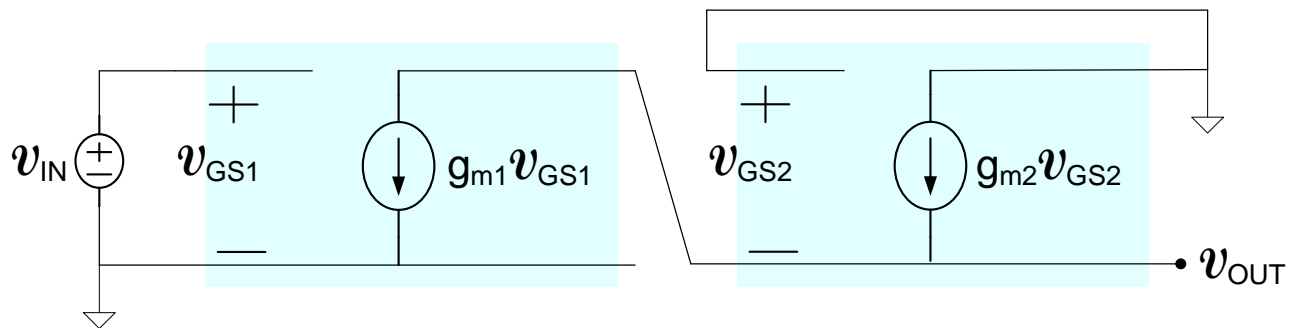

Small-signal circuit

Example:

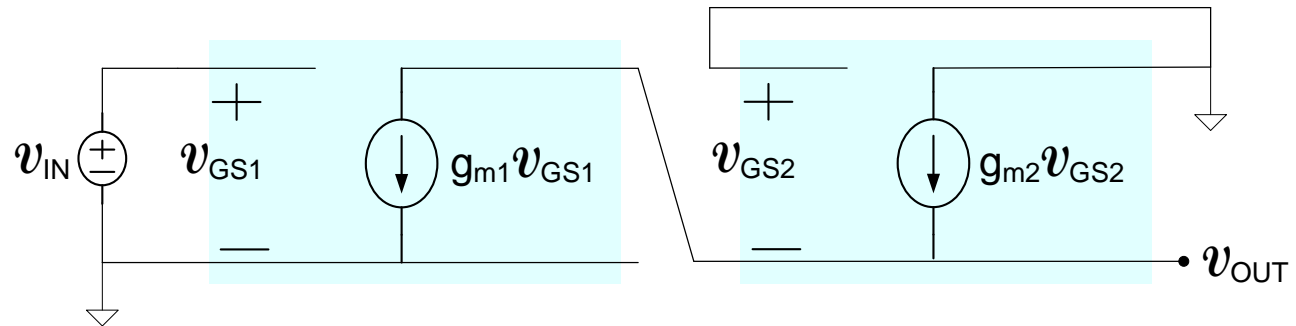

Small-signal circuit for $\lambda=0$

Analysis:

By KCL

$$g_{m1}v_{GS1} = g_{m2}v_{GS2}$$


$$v_{GS1} = v_{IN}$$

$$-v_{GS2} = v_{OUT}$$

thus:

$$A_v = \frac{v_{OUT}}{v_{IN}} = -\frac{g_{m1}}{g_{m2}}$$

Example:

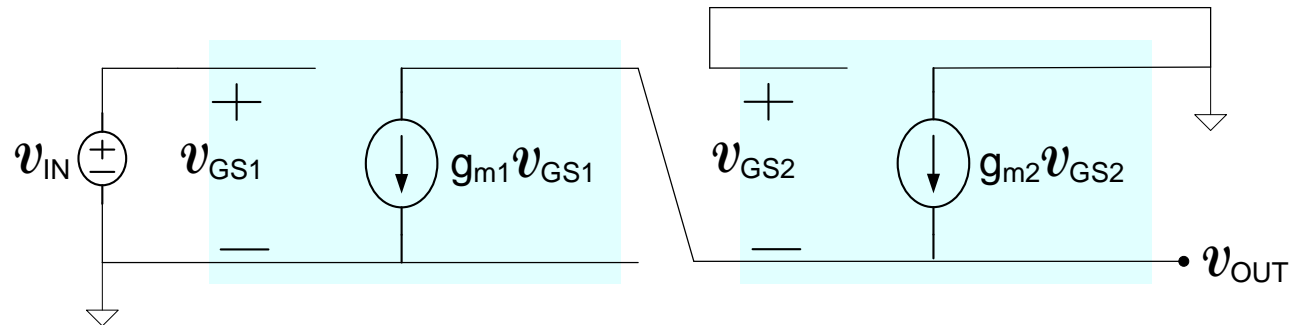

Analysis:

Small-signal circuit for $\lambda=0$


$$A_v = \frac{v_{OUT}}{v_{IN}} = -\frac{g_{m1}}{g_{m2}}$$

Recall:

$$g_m = -\sqrt{2I_D\mu C_{ox}}\sqrt{\frac{W_1}{L_1}}$$

$$A_v = -\frac{\sqrt{2I_{D1}\mu C_{ox}}\sqrt{\frac{W_1}{L_1}}}{\sqrt{2I_{D2}\mu C_{ox}}\sqrt{\frac{W_2}{L_2}}} = -\sqrt{\frac{W_1}{W_2}}\sqrt{\frac{L_2}{L_1}}$$

Example Summary:

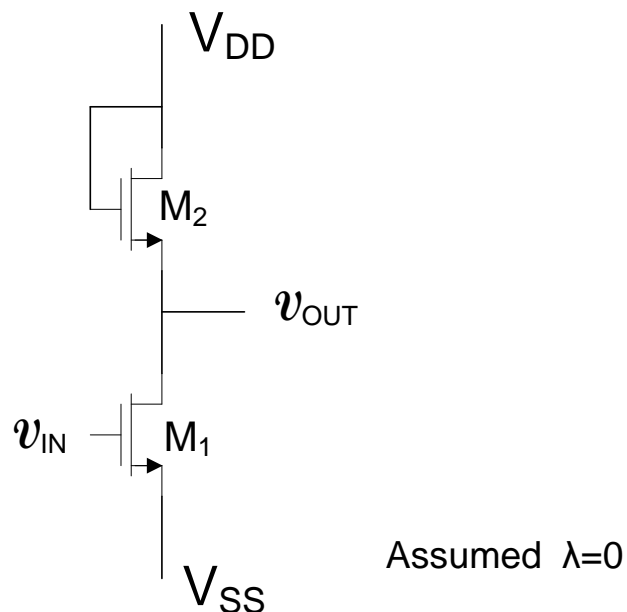

$$A_v = -\frac{g_{m1}}{g_{m2}}$$

In terms of small-signal parameters

$$A_v = -\sqrt{\frac{W_1}{W_2}} \sqrt{\frac{L_2}{L_1}}$$

In terms of Q-point and nonlinear model parameters


If $L_1=L_2$, obtain

$$A_v = -\sqrt{\frac{W_1}{W_2}} \sqrt{\frac{L_2}{L_1}} = -\sqrt{\frac{W_1}{W_2}}$$

The width and length ratios can be accurately controlled with good layout when designed in a standard CMOS process !


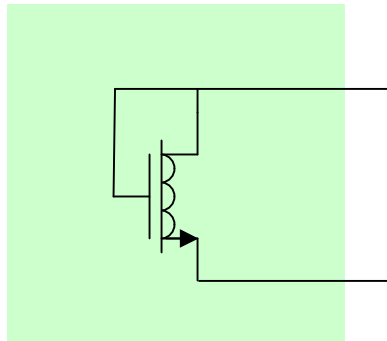
Example: Obtain the small signal model of the following circuit. Assume MOSFET is operating in the saturation region

Note: $g_m \gg g_o$ for MOS devices in most processes so also obtain model under this assumption



Example: Obtain the small signal model of the following circuit. Assume MOSFET is operating in the saturation region.

Solution:

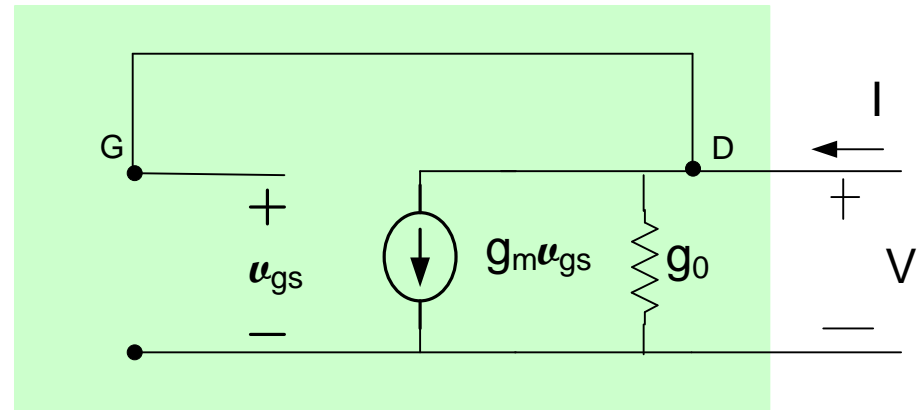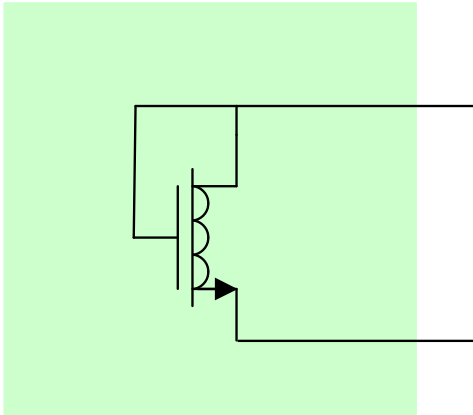


$$V(g_m + g_o) = I$$

$$R_{EQ} = \frac{V}{I} = \frac{1}{g_m + g_o}$$

for $g_m \gg g_o$

$$R_{EQ} \cong \frac{1}{g_m}$$

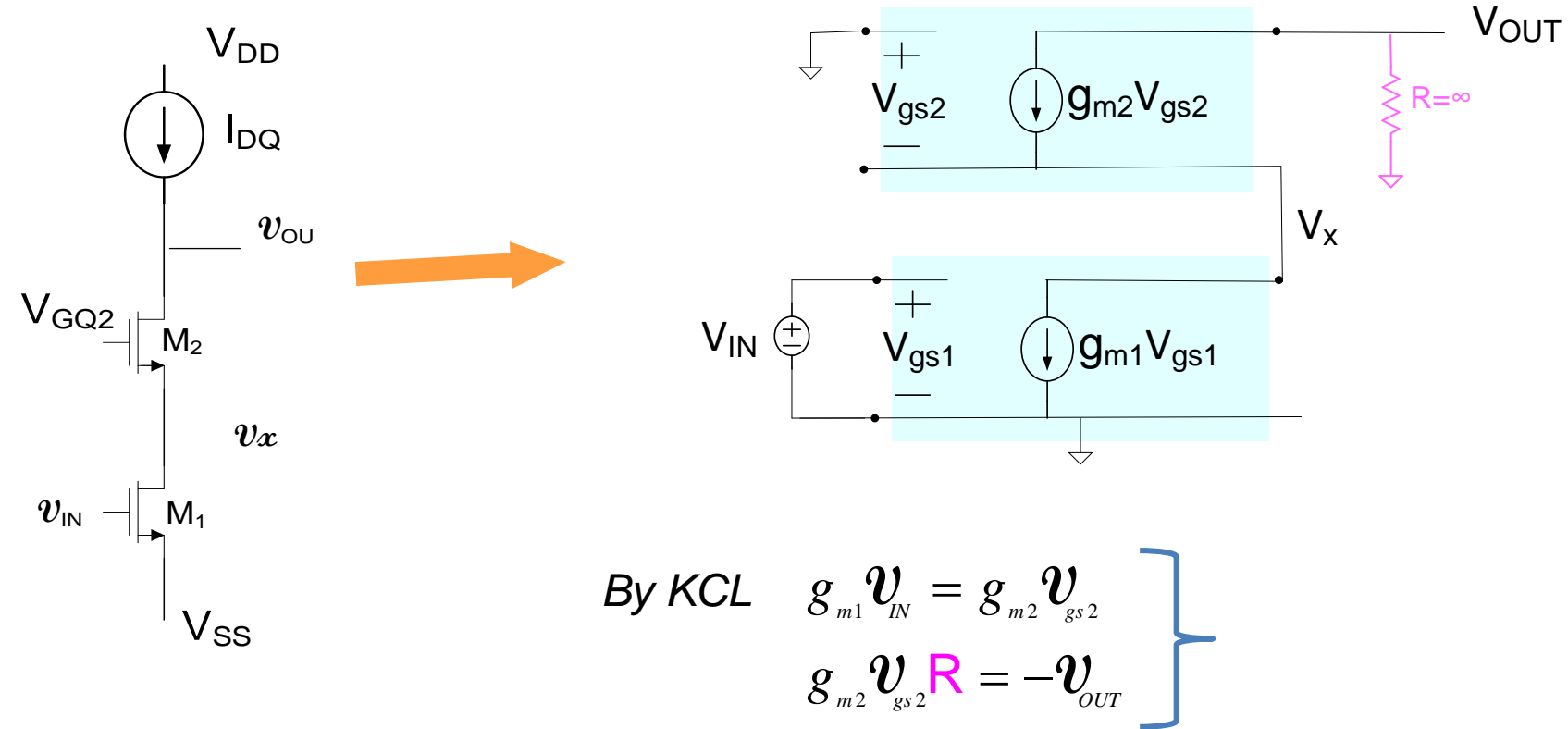Example: Determine the small signal voltage gain $A_V = v_{OUT}/v_{IN}$. Assume M_1 and M_2 are operating in the saturation region and that $\lambda=0$




Solving obtain:

$$A_V = \frac{v_{OUT}}{v_{IN}} = -g_{m1} R \xrightarrow{R=\infty} \infty$$

Unexpectedly large, need better device models!

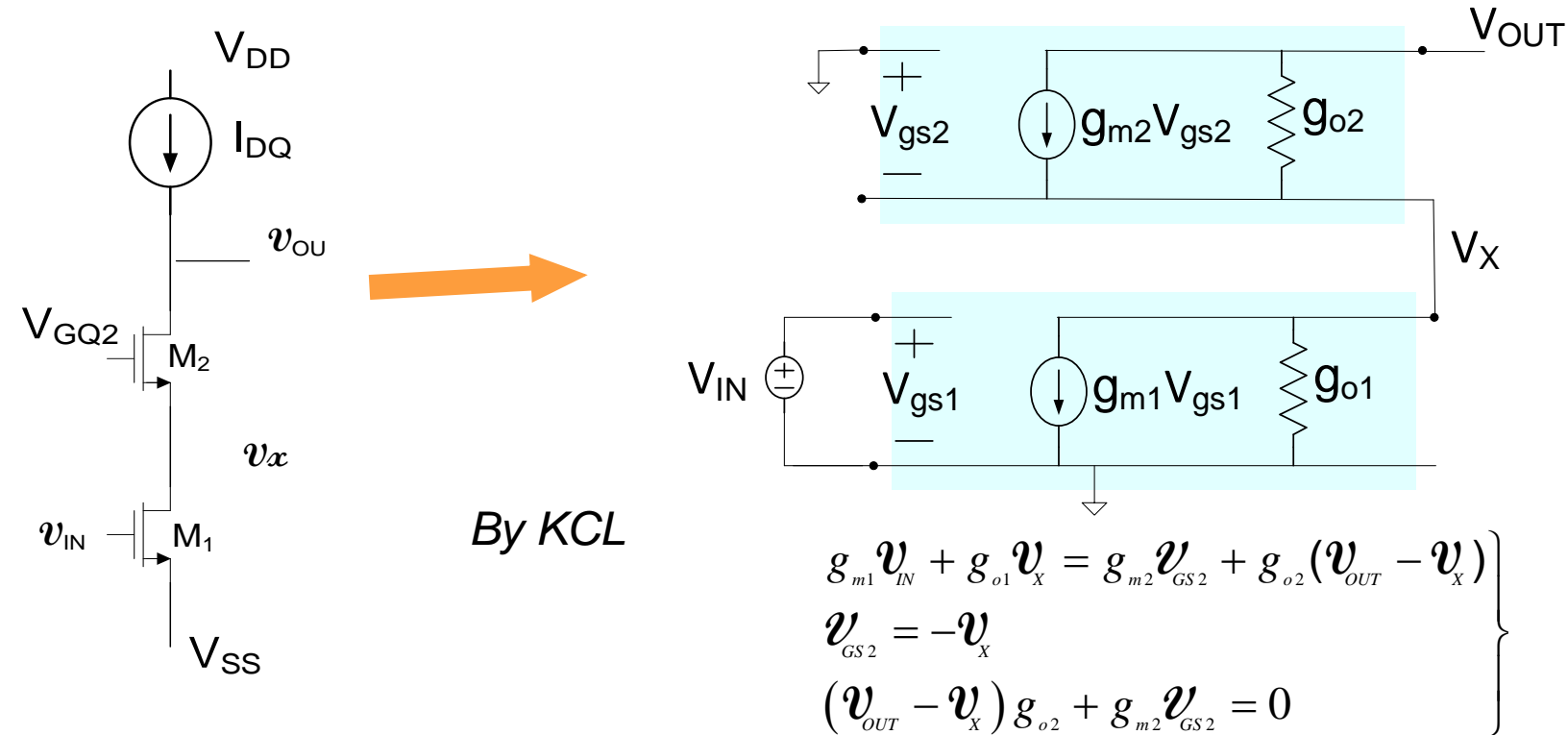Example: Determine the small signal voltage gain $A_V = v_{OUT}/v_{IN}$. Assume M_1 and M_2 are operating in the saturation region and that $\lambda \neq 0$



$$\left. \begin{aligned} g_{m1} v_{IN} + g_{o1} v_X &= g_{m2} v_{GS2} + g_{o2} (v_{OUT} - v_X) \\ v_{GS2} &= -v_X \\ (v_{OUT} - v_X) g_{o2} + g_{m2} v_{GS2} &= 0 \end{aligned} \right\}$$

$$\left. \begin{aligned} g_{m1} v_{IN} + (g_{m2} + g_{o1} + g_{o2}) v_X &= g_{o2} v_{OUT} \\ v_{OUT} g_{o2} &= (g_{m2} + g_{o2}) v_X \end{aligned} \right\}$$


thus:

$$A_V = \frac{v_{OUT}}{v_{IN}} = -\frac{g_{m1} g_{m2} + g_{m1} g_{o2}}{g_{o1} g_{o2}} \cong -\frac{g_{m1}}{g_{o1}} \frac{g_{m2}}{g_{o2}}$$

- Analysis is straightforward but a bit tedious
- A_V is very large and would go to ∞ if g_{o1} and g_{o2} were both 0

Graphical Analysis and Interpretation

Consider Again

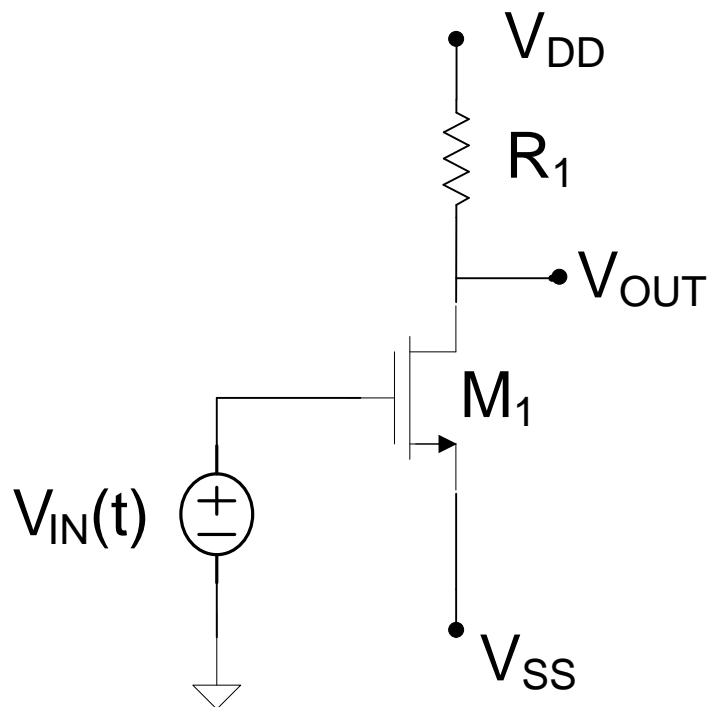



$$V_{OUT} = V_{DD} - I_D R$$

$$I_D = \frac{\mu C_{ox} W}{2L} (V_{IN} - V_{SS} - V_T)^2$$

$$I_{DQ} = \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$

Graphical Analysis and Interpretation

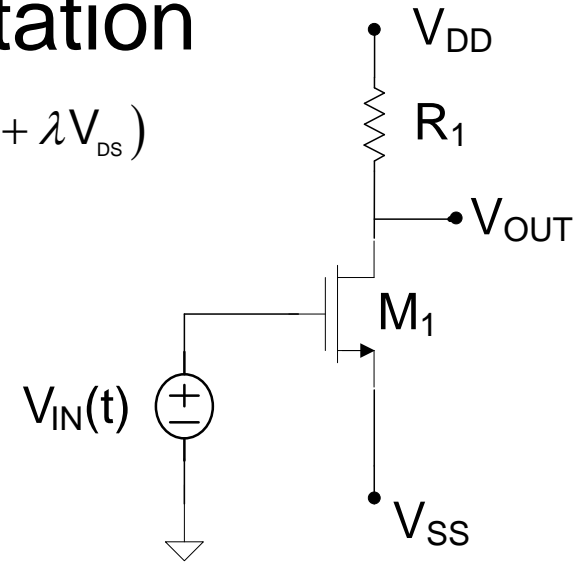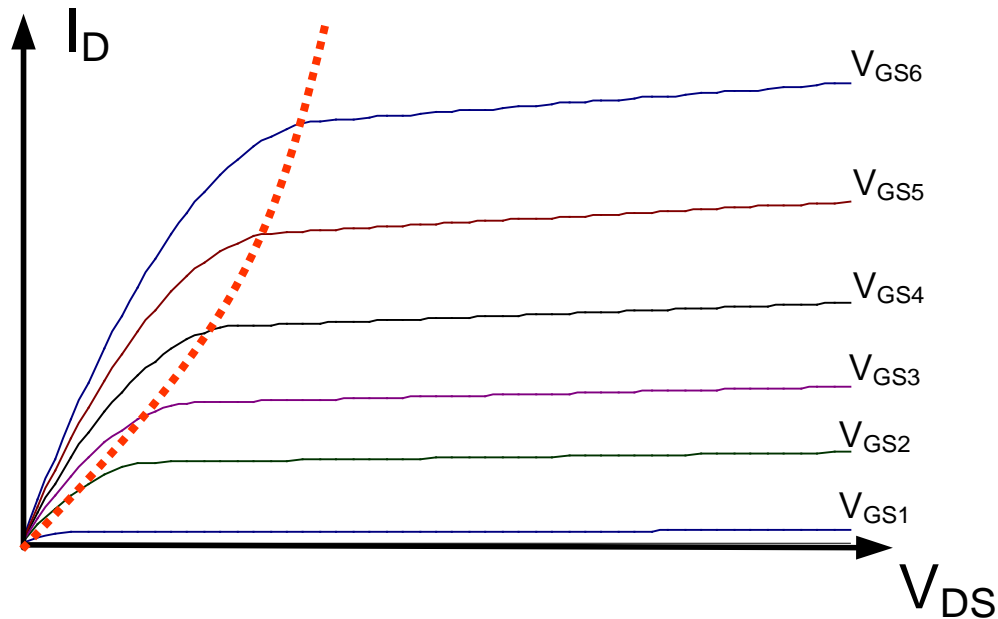Device Model (family of curves)
$$I_D = \frac{\mu C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$



Load Line



Device Model




Device Model at Operating Point



$$V_{OUT} = V_{DD} - I_D R$$



$$I_D = \frac{\mu C_{ox} W}{2L} (V_{IN} - V_{SS} - V_T)^2$$
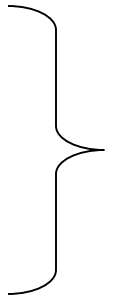
$$I_{DQ} = \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$



Graphical Analysis and Interpretation

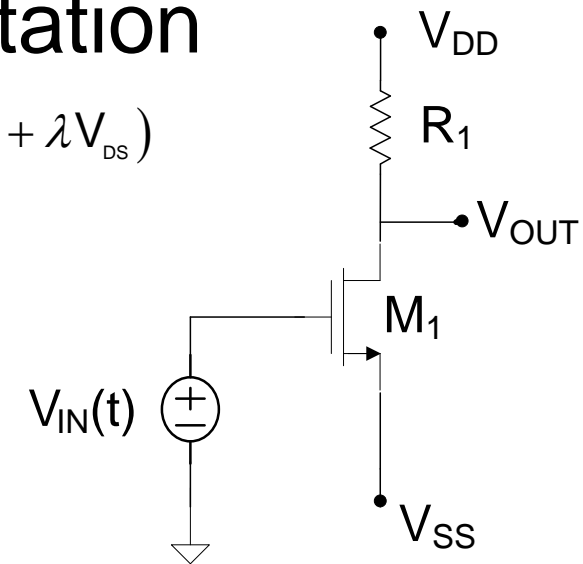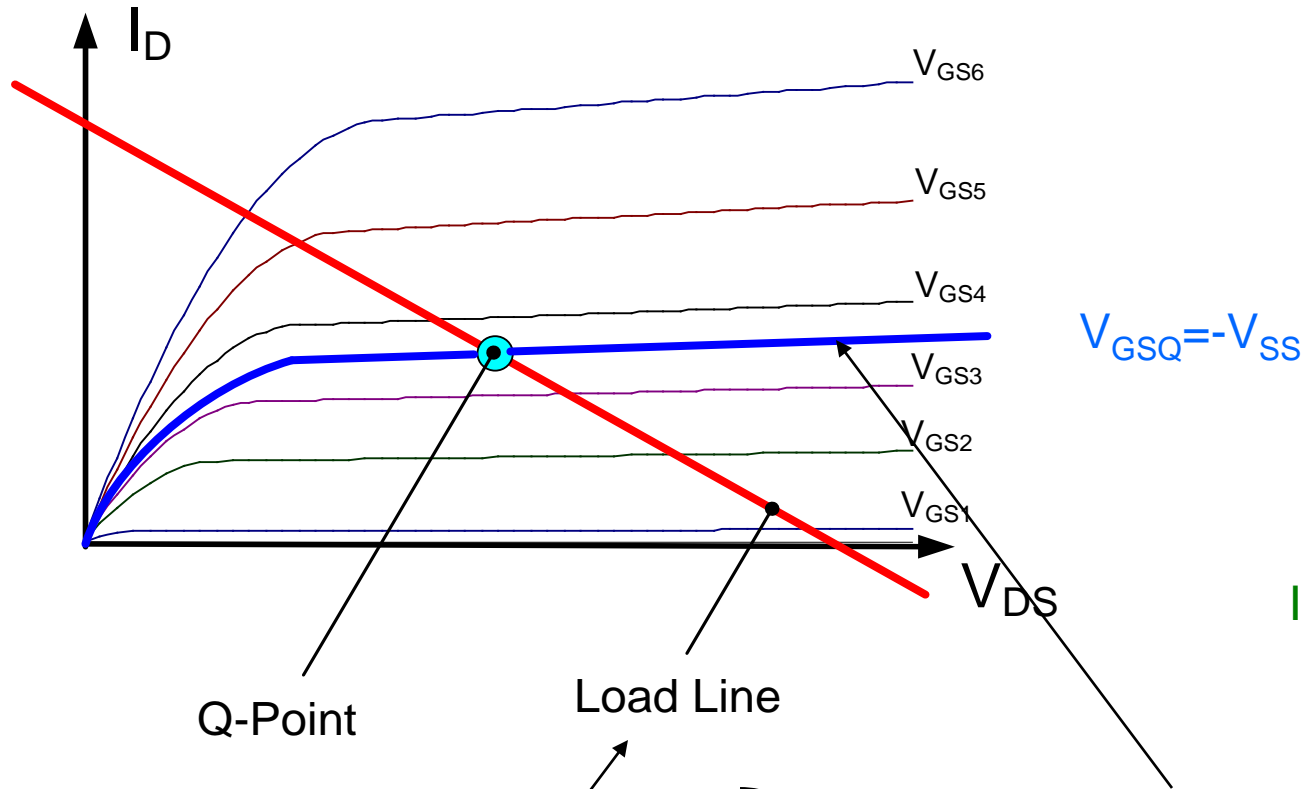Device Model (family of curves) $I_D = \frac{\mu C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$



$$I_{DQ} \cong \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$



$$V_{OUT} = V_{DD} - I_D R$$

$$I_D = \frac{\mu C_{ox} W}{2L} (V_{IN} - V_{SS} - V_T)^2 \quad ?$$

Must satisfy both equations
all of the time !

Graphical Analysis and Interpretation

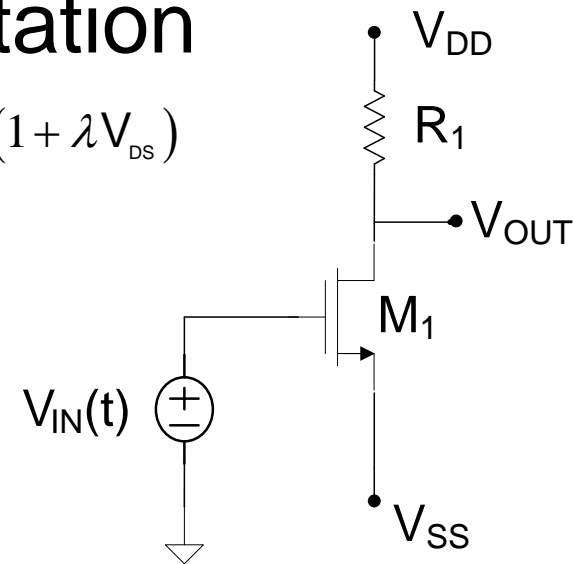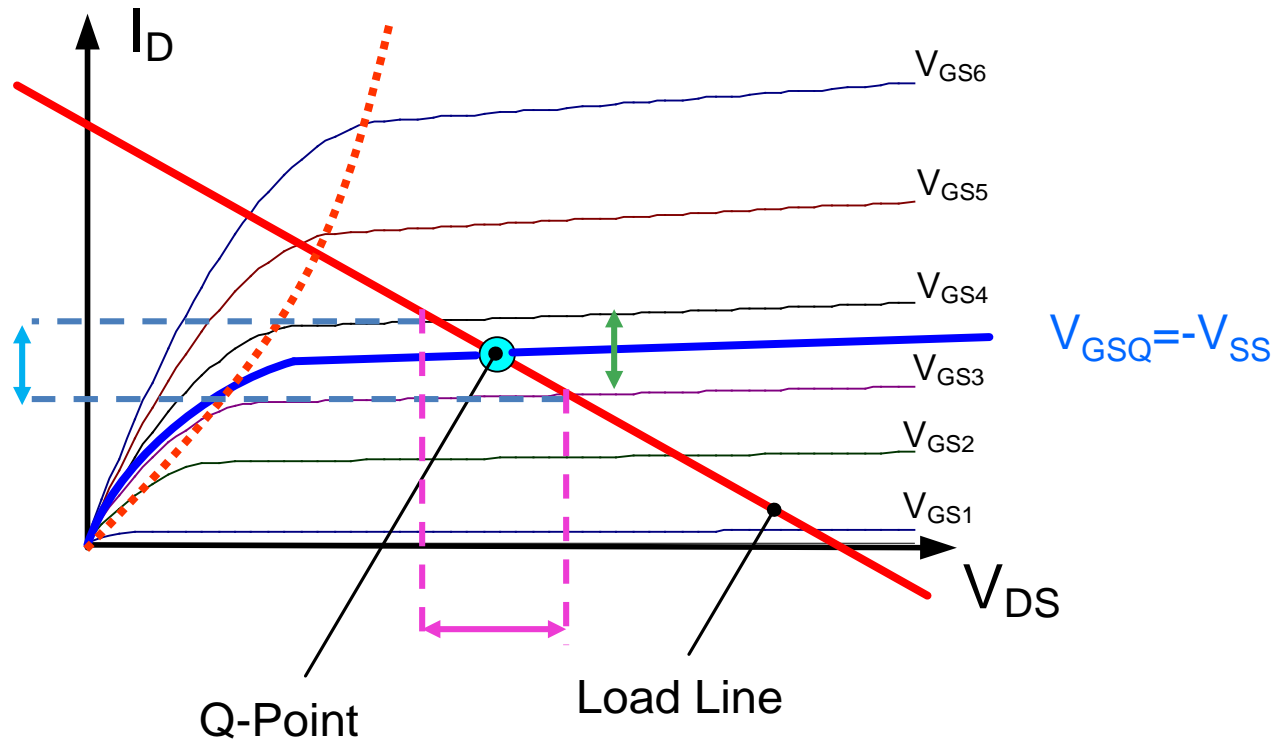Device Model (family of curves)
$$I_D = \frac{\mu C_{ox} W}{2L} (V_{IN} - V_{SS} - V_T)^2 (1 + \lambda V_{DS})$$





The diagram shows a yellow oval containing the expression $\frac{\Delta V_{OUT}}{\Delta V_{IN}} = A_V$, where ΔV_{OUT} is represented by a vertical green double-headed arrow and ΔV_{IN} is represented by a horizontal pink double-headed arrow.

- As V_{IN} changes around Q-point, V_{IN} induces changes in V_{GS} . The operating point must remain on the load line!
- Small sinusoidal changes of V_{IN} will be nearly symmetric around the V_{GSQ} line
- This will cause nearly symmetric changes in both I_D and V_{DS} !
- Since V_{SS} is constant, change in V_{DS} is equal to change in V_{OUT}

Graphical Analysis and Interpretation

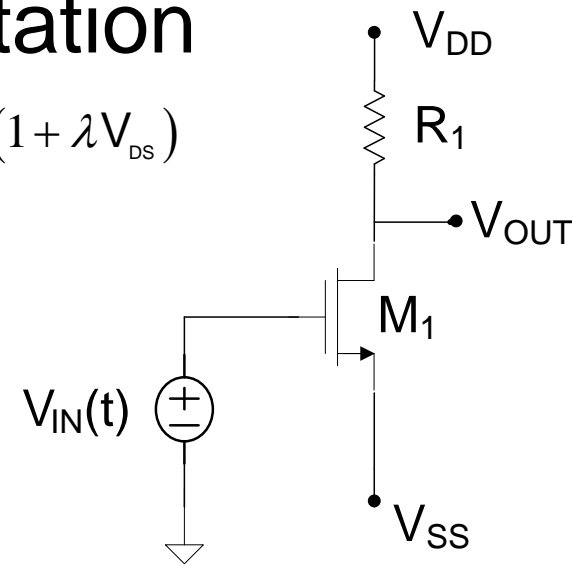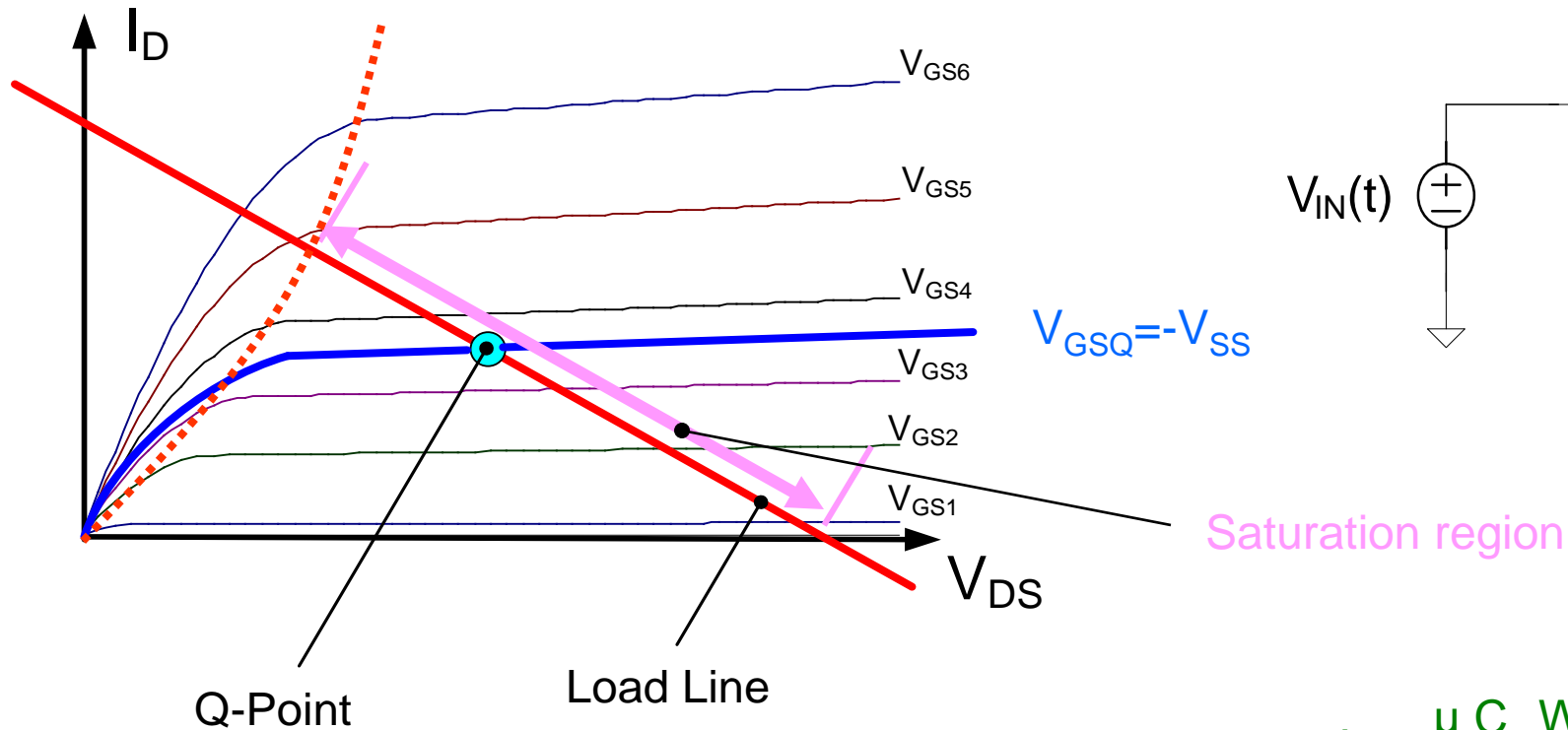Device Model (family of curves)
$$I_D = \frac{\mu C_{ox} W}{2L} (V_{IN} - V_{SS} - V_T)^2 (1 + \lambda V_{DS})$$





$$I_{DQ} \cong \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$

As V_{IN} changes around Q-point, due to changes V_{IN} induces in V_{GS} , the operating point must remain on the load line!

Graphical Analysis and Interpretation

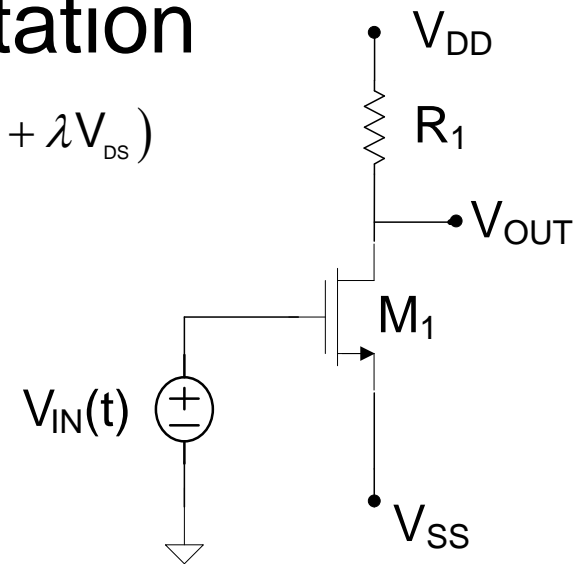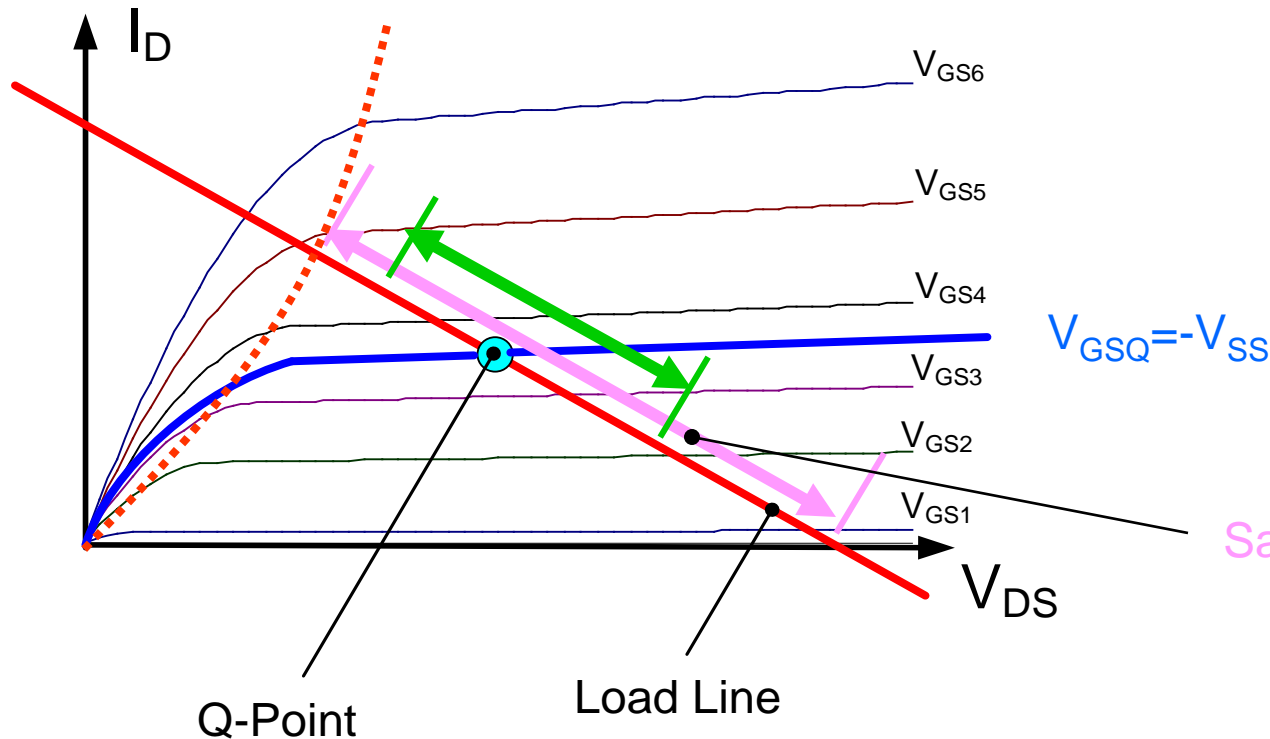Device Model (family of curves)
$$I_{DQ} = \frac{\mu C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$





Saturation region

$$I_{DQ} \cong \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$

- Linear signal swing region smaller than saturation region
- Modest nonlinear distortion provided saturation region operation maintained
- Symmetric swing about Q-point
- Signal swing can be maximized by judicious location of Q-point

Graphical Analysis and Interpretation

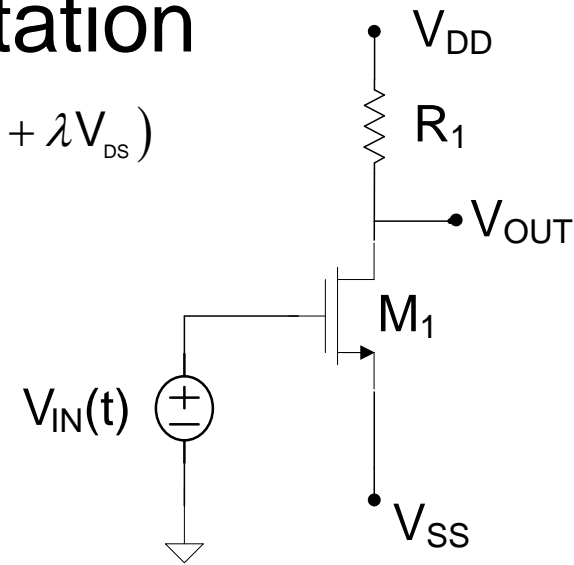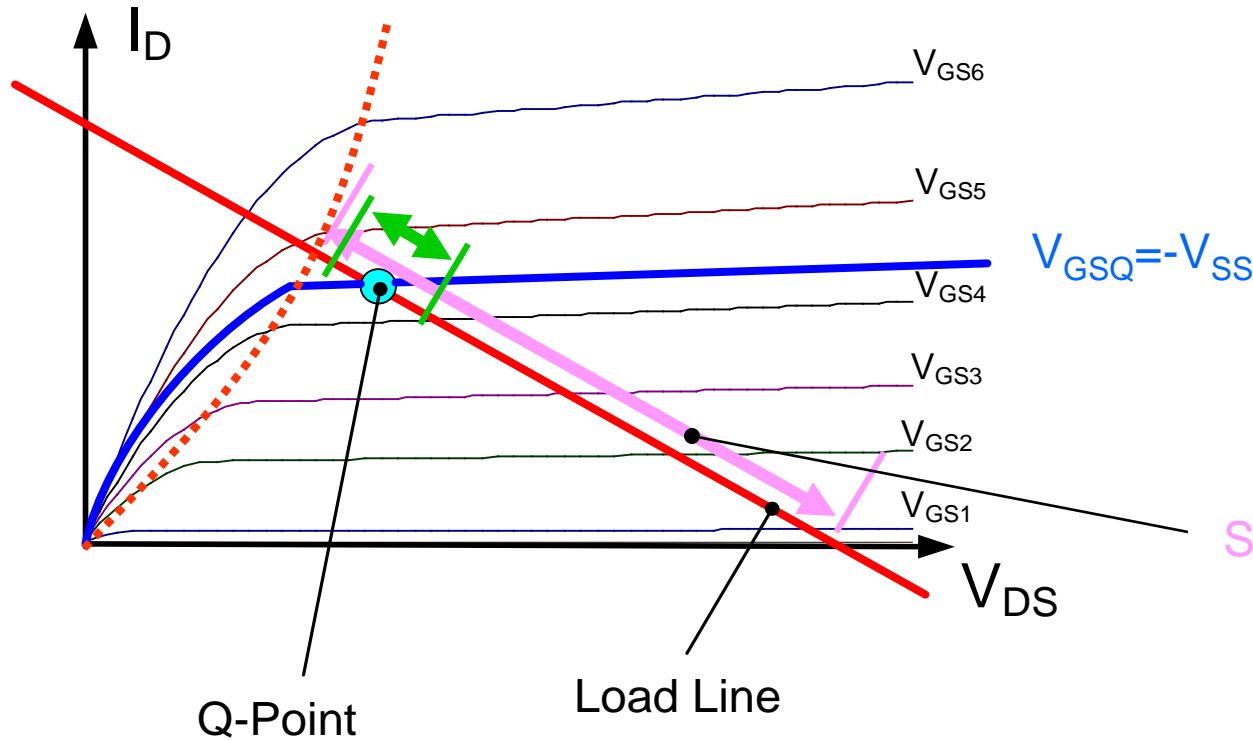Device Model (family of curves)
$$I_{DQ} = \frac{\mu C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$





$$I_{DQ} \cong \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$

Very limited signal swing with non-optimal Q-point location

Graphical Analysis and Interpretation

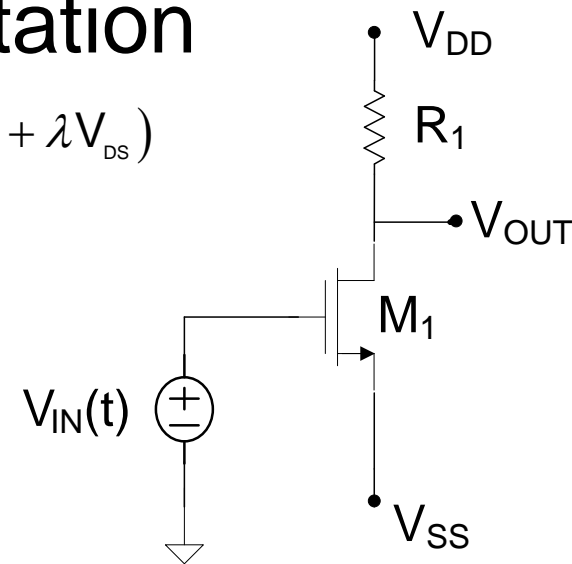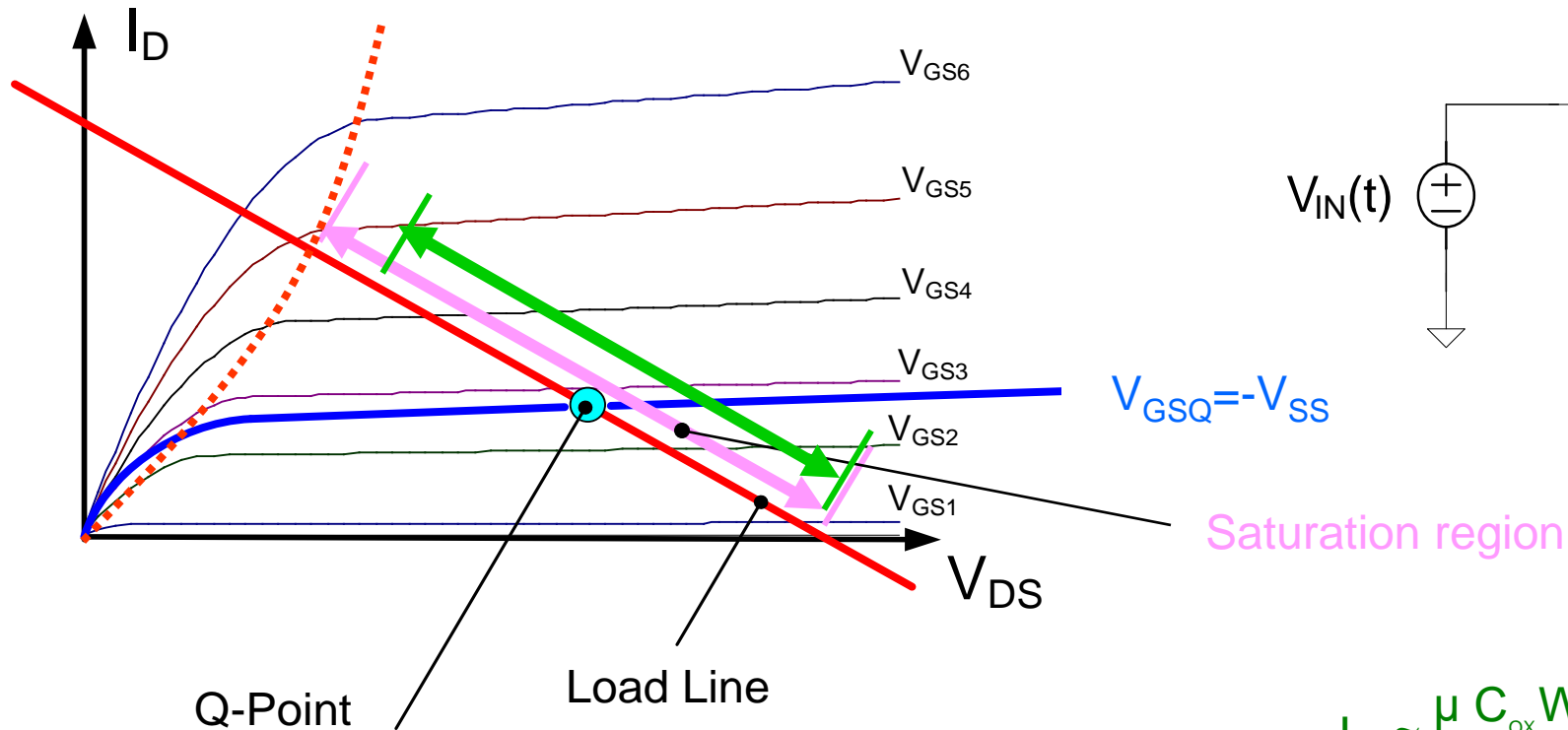Device Model (family of curves)
$$I_{DQ} = \frac{\mu C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$



$$I_{DQ} \cong \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$


- Signal swing can be maximized by judicious location of Q-point
- Often selected to be at middle of load line in saturation region

Small-Signal MOSFET Model Extension

Existing 3-terminal small-signal model does not depend upon the bulk voltage !



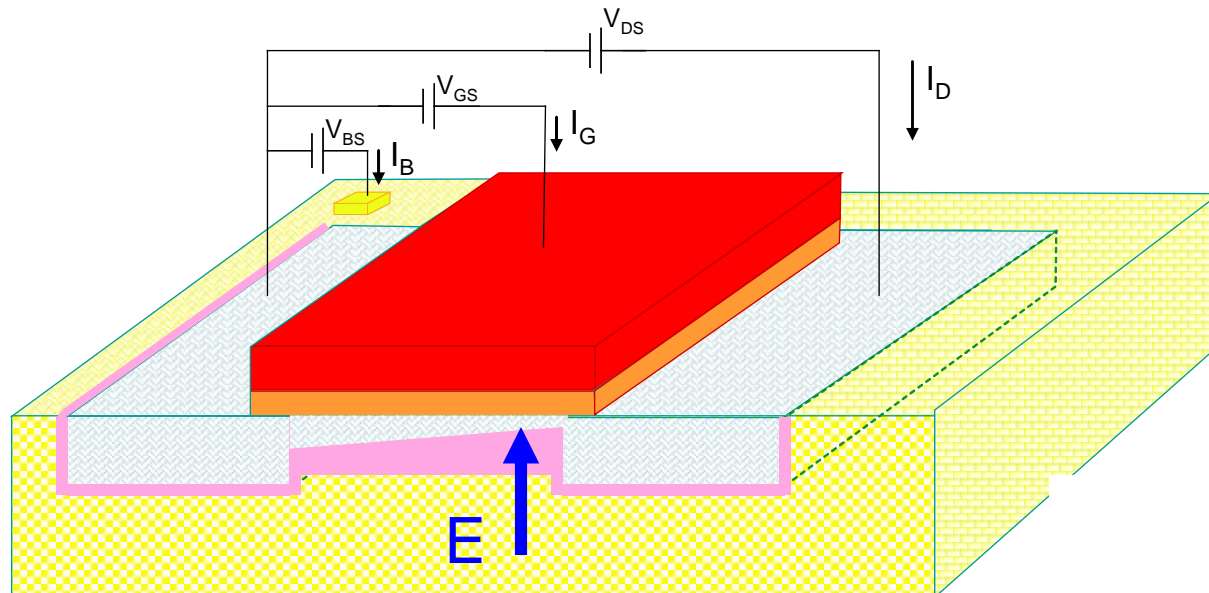
Recall that changing the bulk voltage changes the electric field in the channel region and thus the threshold voltage!



Recall: Typical Effects of Bulk on Threshold Voltage for n-channel Device

$$V_T = V_{T0} + \gamma \left[\sqrt{\phi - V_{BS}} - \sqrt{\phi} \right]$$
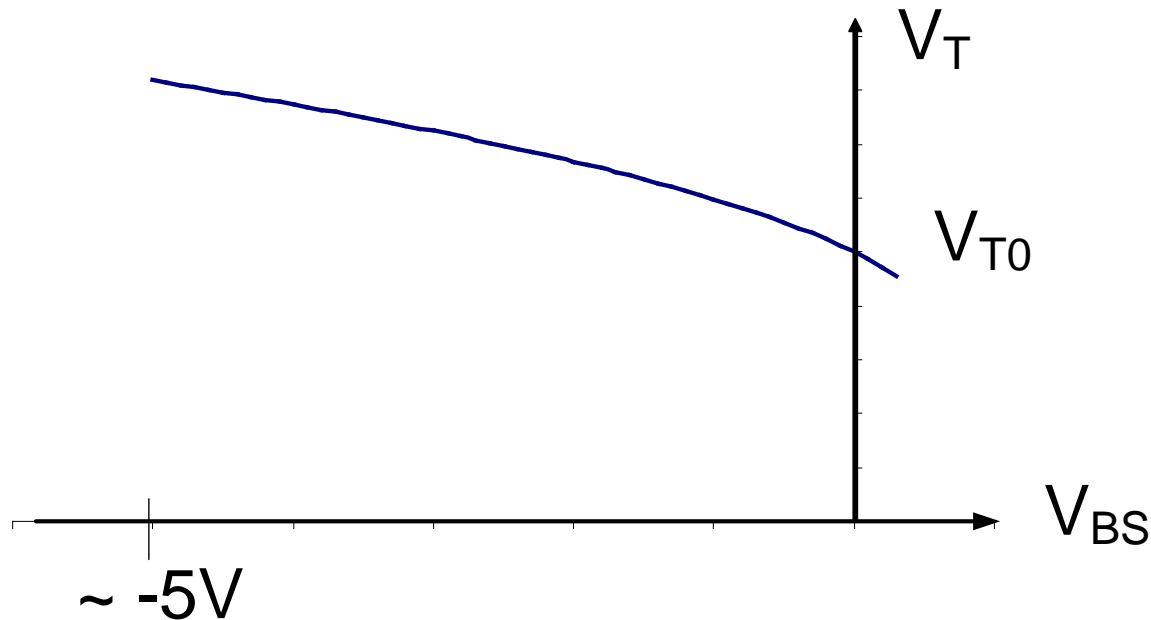
$$\gamma \cong 0.4V^{-\frac{1}{2}} \quad \phi \cong 0.6V$$



Bulk-Diffusion Generally Reverse Biased ($V_{BS} < 0$ or at least less than 0.3V) for n-channel

Shift in threshold voltage with bulk voltage can be substantial


Often $V_{BS} = 0$

Recall: Typical Effects of Bulk on Threshold Voltage for p-channel Device

$$V_T = V_{T0} - \gamma \left[\sqrt{\phi + V_{BS}} - \sqrt{\phi} \right]$$

$$\gamma \cong 0.4V^{-\frac{1}{2}}$$

$$\phi \cong 0.6V$$

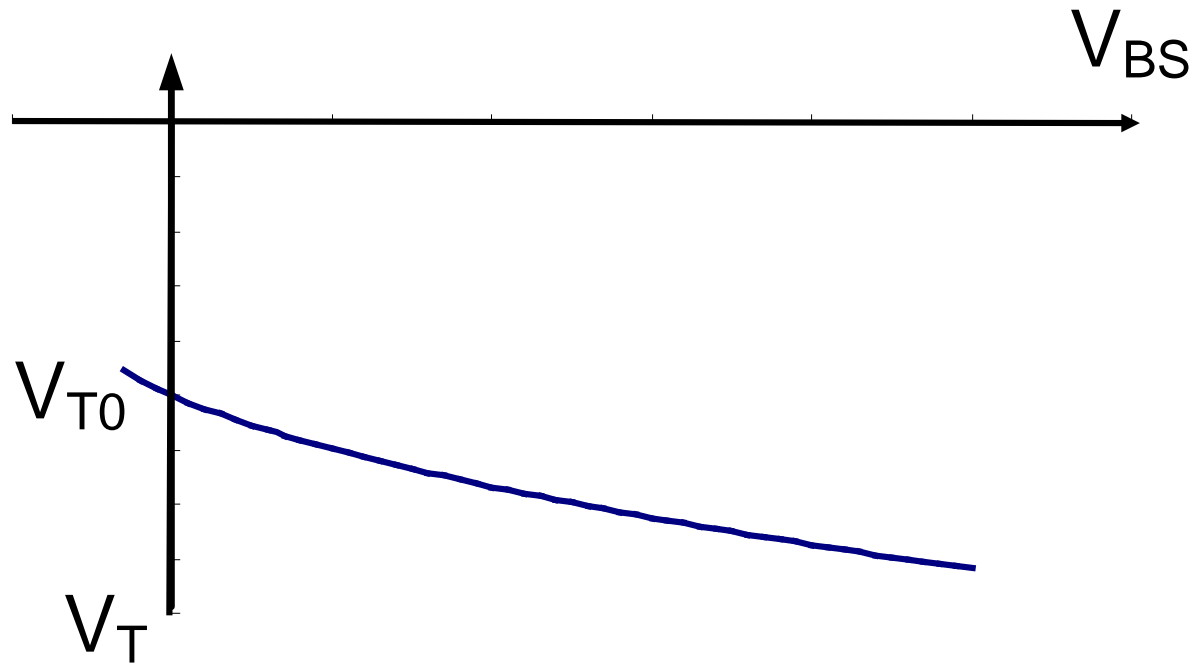

Bulk-Diffusion Generally Reverse Biased ($V_{BS} > 0$ or at least greater than $-0.3V$) for n-channel


Same functional form as for n-channel devices but V_{T0} is now negative and the magnitude of V_T still increases with the magnitude of the reverse bias

Recall:

4-terminal model extension

$$I_G = 0$$

$$I_B = 0$$

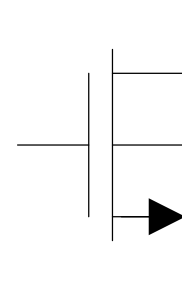

$$I_D = \begin{cases} 0 & V_{GS} \leq V_T \\ \mu C_{ox} \frac{W}{L} \left(V_{GS} - V_T - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} \geq V_T \quad V_{DS} < V_{GS} - V_T \\ \mu C_{ox} \frac{W}{2L} (V_{GS} - V_T)^2 \bullet (1 + \lambda V_{DS}) & V_{GS} \geq V_T \quad V_{DS} \geq V_{GS} - V_T \end{cases}$$

$$V_T = V_{T0} + \gamma \left(\sqrt{\phi - V_{BS}} - \sqrt{\phi} \right)$$

Model Parameters : $\{\mu, C_{ox}, V_{T0}, \phi, \gamma, \lambda\}$

Design Parameters : $\{W, L\}$ but only one degree of freedom W/L
biasing or quiescent point

Small-Signal 4-terminal Model Extension

$$I_G = 0$$

$$I_B = 0$$

$$I_D = \begin{cases} 0 \\ \mu C_{ox} \frac{W}{L} \left(V_{GS} - V_T - \frac{V_{DS}}{2} \right) V_{DS} \\ \mu C_{ox} \frac{W}{2L} (V_{GS} - V_T)^2 \bullet (1 + \lambda V_{DS}) \end{cases}$$

$$V_{GS} \leq V_T$$

$$V_{GS} \geq V_T \quad V_{DS} < V_{GS} - V_T$$

$$V_{GS} \geq V_T \quad V_{DS} \geq V_{GS} - V_T$$

$$V_T = V_{T0} + \gamma \left(\sqrt{\phi - V_{BS}} - \sqrt{\phi} \right)$$

$$y_{11} = \left. \frac{\partial I_G}{\partial V_{GS}} \right|_{\bar{V}=\bar{V}_Q} = 0 \quad y_{12} = \left. \frac{\partial I_G}{\partial V_{DS}} \right|_{\bar{V}=\bar{V}_Q} = 0 \quad y_{13} = \left. \frac{\partial I_G}{\partial V_{BS}} \right|_{\bar{V}=\bar{V}_Q} = 0$$

$$y_{21} = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{\bar{V}=\bar{V}_Q} = g_m \quad y_{22} = \left. \frac{\partial I_D}{\partial V_{DS}} \right|_{\bar{V}=\bar{V}_Q} = g_o \quad y_{23} = \left. \frac{\partial I_D}{\partial V_{BS}} \right|_{\bar{V}=\bar{V}_Q} = g_{mb}$$

$$y_{31} = \left. \frac{\partial I_B}{\partial V_{GS}} \right|_{\bar{V}=\bar{V}_Q} = 0 \quad y_{32} = \left. \frac{\partial I_B}{\partial V_{DS}} \right|_{\bar{V}=\bar{V}_Q} = 0 \quad y_{33} = \left. \frac{\partial I_B}{\partial V_{BS}} \right|_{\bar{V}=\bar{V}_Q} = 0$$

Small-Signal 4-terminal Model Extension

$$I_D = \mu C_{ox} \frac{W}{2L} (V_{GS} - V_T)^2 \bullet (1 + \lambda V_{DS})$$

Definition:

$$V_{EB} = V_{GS} - V_T$$

$$V_{EBQ} = V_{GSQ} - V_{TQ}$$

$$V_T = V_{T0} + \gamma \left(\sqrt{\phi - V_{BS}} - \sqrt{\phi} \right)$$

$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{\vec{V}=\vec{V}_Q} = \mu C_{ox} \frac{W}{2L} 2(V_{GS} - V_T)^1 \bullet (1 + \lambda V_{DS}) \Big|_{\vec{V}=\vec{V}_Q} \cong \mu C_{ox} \frac{W}{L} V_{EBQ}$$

Same as 3-term

$$g_o = \left. \frac{\partial I_D}{\partial V_{DS}} \right|_{\vec{V}=\vec{V}_Q} = \mu C_{ox} \frac{W}{2L} 2(V_{GS} - V_T)^2 \bullet \lambda \Big|_{\vec{V}=\vec{V}_Q} \cong \lambda I_{DQ}$$


Same as 3-term

$$g_{mb} = \left. \frac{\partial I_D}{\partial V_{BS}} \right|_{\vec{V}=\vec{V}_Q} = \mu C_{ox} \frac{W}{2L} 2(V_{GS} - V_T)^1 \bullet \left(-\frac{\partial V_T}{\partial V_{BS}} \right) \bullet (1 + \lambda V_{DS}) \Big|_{\vec{V}=\vec{V}_Q}$$

$$g_{mb} = \left. \frac{\partial I_D}{\partial V_{BS}} \right|_{\vec{V}=\vec{V}_Q} \cong \mu C_{ox} \frac{W}{L} V_{EBQ} \bullet \left. \frac{\partial V_T}{\partial V_{BS}} \right|_{\vec{V}=\vec{V}_Q} = \left(\mu C_{ox} \frac{W}{L} V_{EBQ} \right) (-1) \gamma \frac{1}{2} (\phi - V_{BS})^{-\frac{1}{2}} \Big|_{\vec{V}=\vec{V}_Q} (-1)$$

$$g_{mb} \cong g_m \frac{\gamma}{2\sqrt{\phi - V_{BSQ}}}$$

Small Signal Model Summary

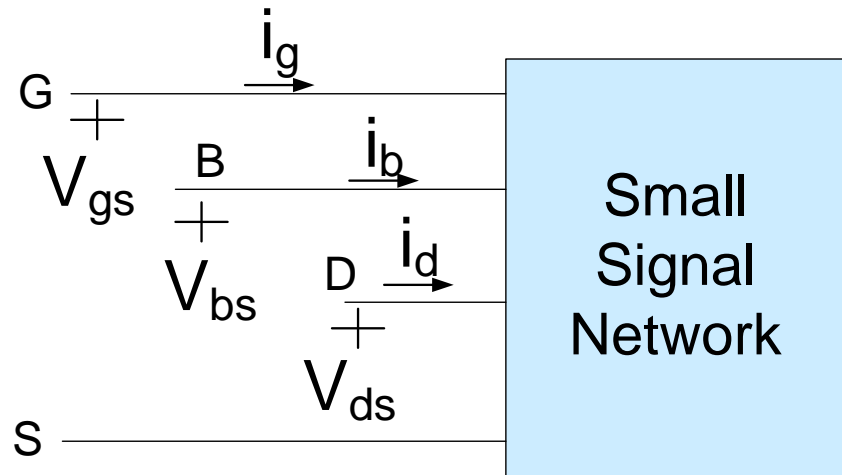

$$i_g = 0$$

$$i_b = 0$$

$$i_d = g_m v_{gs} + g_{mb} v_{bs} + g_o v_{ds}$$

$$g_m = \frac{\mu C_{ox} W}{L} v_{EBQ}$$

$$g_o = \lambda I_{DQ}$$

$$g_{mb} = g_m \left(\frac{\gamma}{2\sqrt{\phi - V_{BSQ}}} \right)$$

Relative Magnitude of Small Signal MOS Parameters

Consider:

$$i_d = g_m v_{gs} + g_{mb} v_{bs} + g_o v_{ds}$$

3 alternate equivalent expressions for g_m

$$g_m = \frac{\mu C_{ox} W}{L} V_{EBQ} \quad g_m = \sqrt{\frac{2\mu C_{ox} W}{L}} \sqrt{I_{DQ}} \quad g_m = \frac{2I_{DQ}}{V_{EBQ}}$$

If $\mu C_{ox} = 100 \mu A/V^2$, $\lambda = .01 V^{-1}$, $\gamma = 0.4 V^{0.5}$, $V_{EBQ} = 1V$, $W/L = 1$, $V_{BSQ} = 0V$

$$I_{DQ} \cong \frac{\mu C_{ox} W}{2L} V_{EBQ}^2 = \frac{10^{-4} W}{2L} (1V)^2 = 5E-5$$

$$g_m = \frac{\mu C_{ox} W}{L} V_{EBQ} = 1E-4$$

$$g_o = \lambda I_{DQ} = 5E-7$$

$$g_{mb} = g_m \left(\frac{\gamma}{2\sqrt{\phi - V_{BSQ}}} \right) = .26g_m$$

In this example

$$g_o \ll g_m, g_{mb}$$

$$g_{mb} < g_m$$


This relationship is common

In many circuits, $V_{BS} = 0$ as well

- Often the g_o term can be neglected in the small signal model because it is so small
- Be careful about neglecting g_o prior to obtaining a final expression

Large and Small Signal Model Summary

Large Signal Model

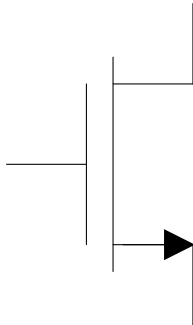


$$I_D = \begin{cases} 0 & V_{GS} \leq V_T \\ \mu C_{OX} \frac{W}{L} \left(V_{GS} - V_T - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} \geq V_T \quad V_{DS} < V_{GS} - V_T \\ \mu C_{OX} \frac{W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) & V_{GS} \geq V_T \quad V_{DS} \geq V_{GS} - V_T \end{cases}$$

saturation

$$V_T = V_{T0} + \gamma \left(\sqrt{\phi - V_{BS}} - \sqrt{\phi} \right)$$

Small Signal Model

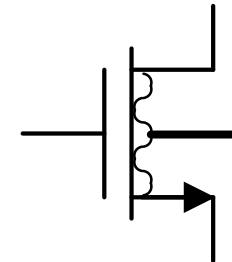

saturation

$$i_g = 0$$

$$i_b = 0$$

$$i_d = g_m v_{gs} + g_{mb} v_{bs} + g_o v_{ds}$$

where


$$g_m = \frac{\mu C_{OX} W}{L} V_{EBQ}$$

$$g_{mb} = g_m \left(\frac{\gamma}{2\sqrt{\phi - V_{BSQ}}} \right)$$

$$g_o = \lambda I_{DQ}$$

Large and Small Signal Model Summary

Large Signal Model

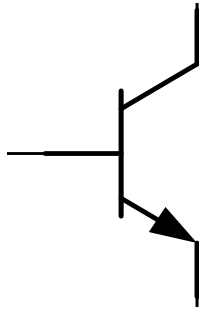

$$I_C = \beta I_B \left(1 + \frac{V_{CE}}{V_{AF}} \right)$$

$$I_B = \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}}$$

$$V_{BE} > 0.4V$$

$$V_{BC} < 0$$

Forward Active

$$V_{BE} = 0.7V$$

$$V_{CE} = 0.2V$$


$$I_C < \beta I_B$$

$$I_C = I_B = 0$$

$$V_{BE} < 0$$

$$V_{BC} < 0$$

Small Signal Model

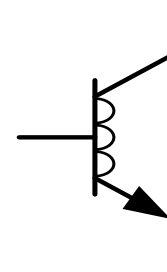

Forward Active

$$i_b = g_\pi v_{be}$$

$$i_c = g_m v_{be} + g_o v_{ce}$$

where

$$g_m = \frac{I_{CQ}}{V_t}$$

$$g_\pi = \frac{I_{CQ}}{\beta V_t}$$


$$g_o \cong \frac{I_{CQ}}{V_{AF}}$$

Relative Magnitude of Small Signal BJT Parameters

$$g_m = \frac{I_{CQ}}{V_t}$$

$$g_\pi = \frac{I_{CQ}}{\beta V_t}$$

$$g_o \cong \frac{I_{CQ}}{V_{AF}}$$

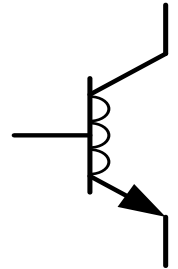

$$\frac{g_m}{g_\pi} = \frac{\left[\frac{I_Q}{V_t} \right]}{\left[\frac{I_Q}{\beta V_t} \right]}$$

$$\frac{g_\pi}{g_o} = \frac{\left[\frac{I_Q}{\beta V_t} \right]}{\left[\frac{I_Q}{V_{AF}} \right]}$$

$$g_m \gg g_\pi \gg g_o$$


Often the g_o term can be neglected in the small signal model because it is so small

Relative Magnitude of Small Signal Parameters

$$g_m = \frac{I_{CQ}}{V_t}$$

$$g_\pi = \frac{I_{CQ}}{\beta V_t}$$

$$g_o \cong \frac{I_{CQ}}{V_{AF}}$$

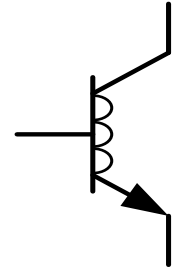


$$\frac{g_m}{g_\pi} = \frac{\left[\frac{I_Q}{V_t} \right]}{\left[\frac{I_Q}{\beta V_t} \right]} = \beta$$

$$\frac{g_\pi}{g_o} = \frac{\left[\frac{I_Q}{\beta V_t} \right]}{\left[\frac{I_Q}{V_{AF}} \right]} = \frac{V_{AF}}{\beta V_t} \approx \frac{200V}{100 \cdot 26mV} = 77$$



$$g_m \gg g_\pi \gg g_o$$

- Often the g_o term can be neglected in the small signal model because it is so small
- Be careful about neglecting g_o prior to obtaining a final expression

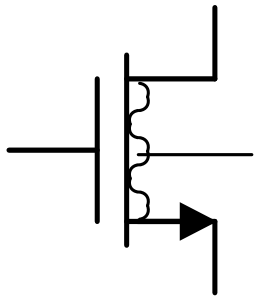Small Signal Model Simplifications for the MOSFET and BJT



MOSFET

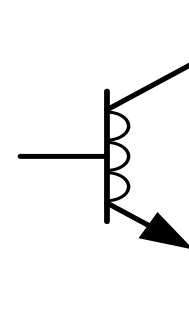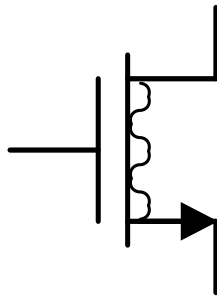


BJT


Often simplifications of the small signal model are adequate for a given application

These simplifications will be discussed next

Small Signal MOSFET Model Summary

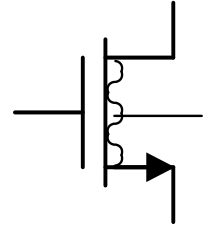

An equivalent Circuit:

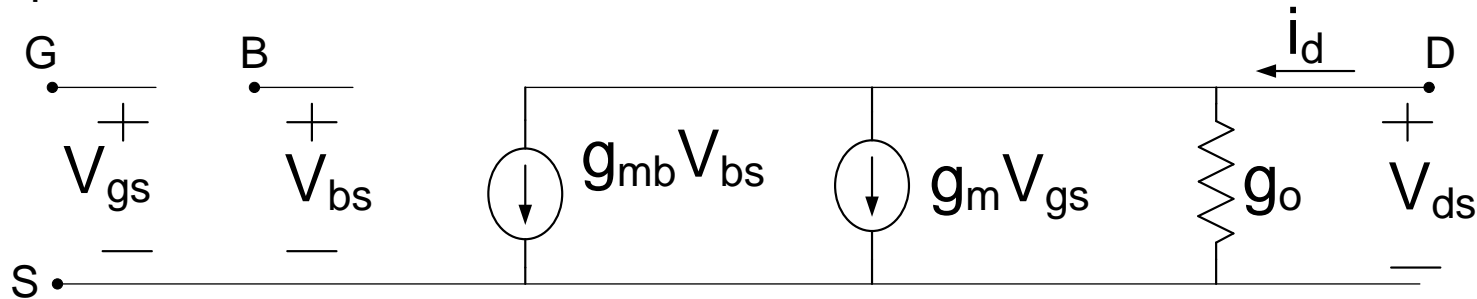

$$g_m = \frac{\mu C_{ox} W}{L} (V_{GSQ} - V_T)$$

$$g_o = \lambda I_{DQ}$$

$$g_{mb} = g_m \left(\frac{\gamma}{2\sqrt{\phi - V_{BSQ}}} \right)$$

Alternate equivalent representations for g_m from $I_D \cong \mu C_{ox} \frac{W}{2L} (V_{GS} - V_T)^2$



$$g_m = \sqrt{\frac{2\mu C_{ox} W}{L}} \sqrt{I_{DQ}}$$

$$g_m = \frac{2I_{DQ}}{V_{GSQ} - V_T} = \frac{2I_{DQ}}{V_{EBQ}}$$


$$g_{mb} < g_m$$

$$g_o \ll g_m, g_{mb}$$



Small Signal Model Simplifications

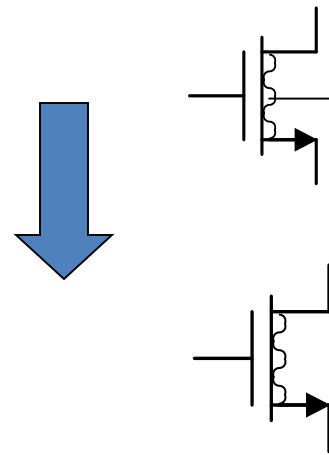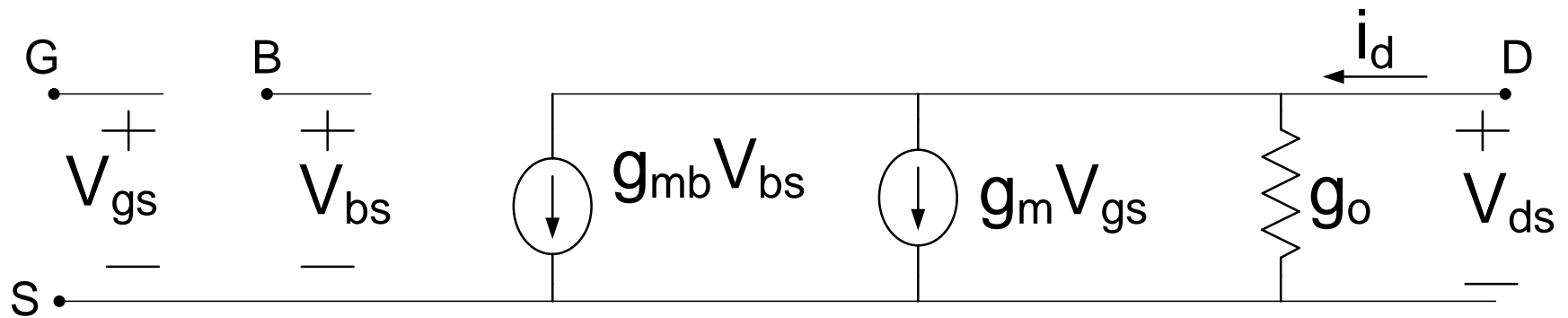


Simplification that is often adequate

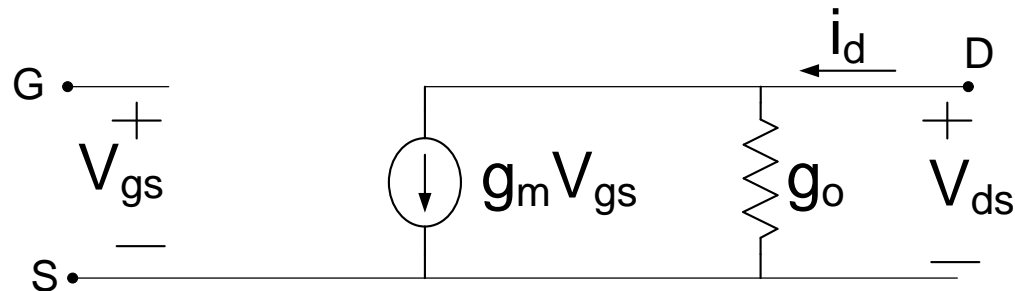

Small Signal Model Simplifications

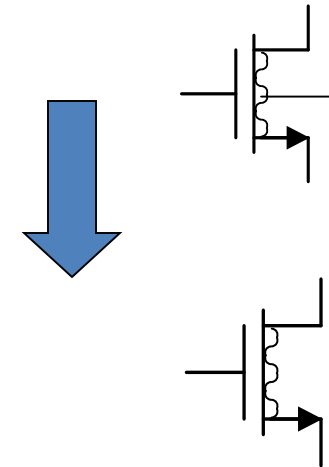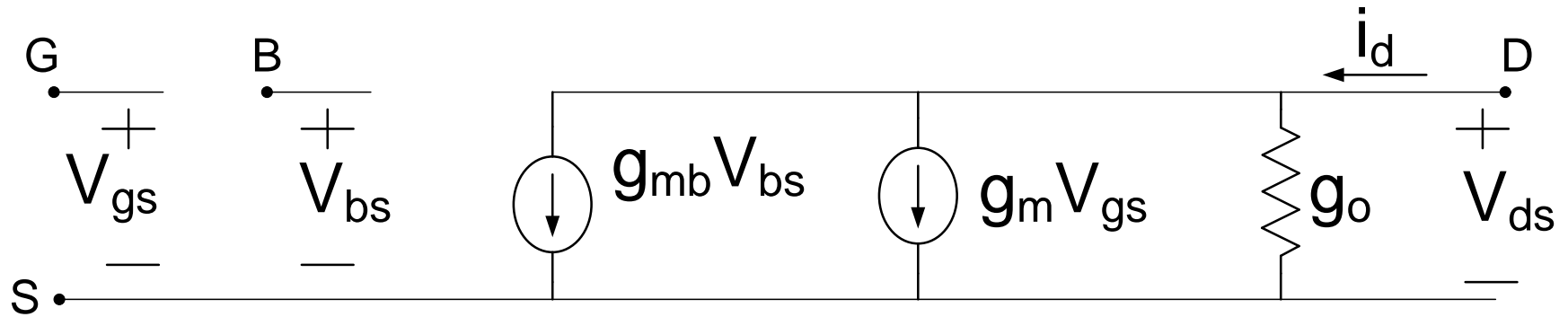


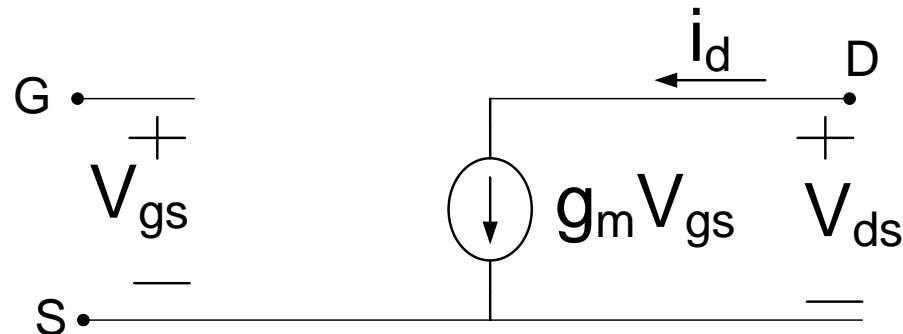Even further simplification that is often adequate



Small Signal BJT Model Summary

An equivalent circuit

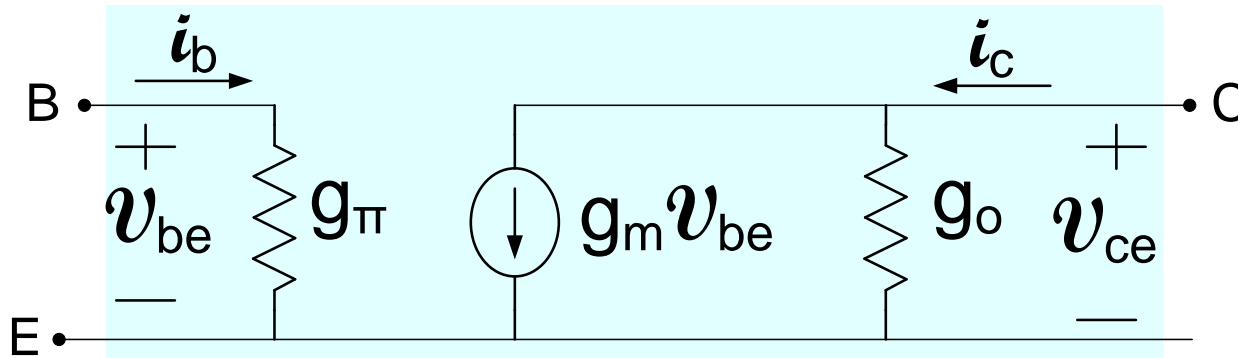

$$g_m = \frac{I_{CQ}}{V_t}$$




$$g_\pi = \frac{I_{CQ}}{\beta V_t}$$

$$g_o \cong \frac{I_{CQ}}{V_{AF}}$$


$$g_m \gg g_\pi \gg g_o$$

This contains absolutely no more information than the set of small-signal model equations

Small Signal BJT Model Simplifications

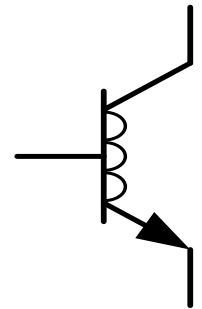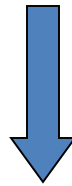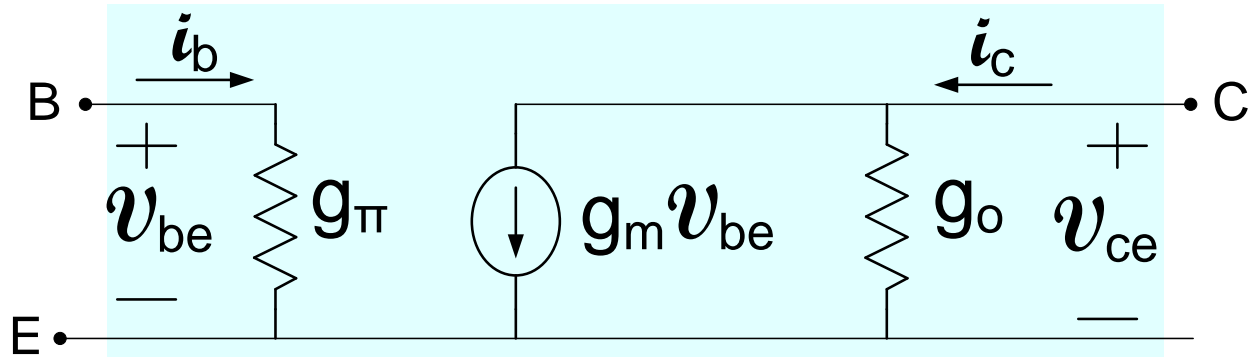


Simplification that is often adequate

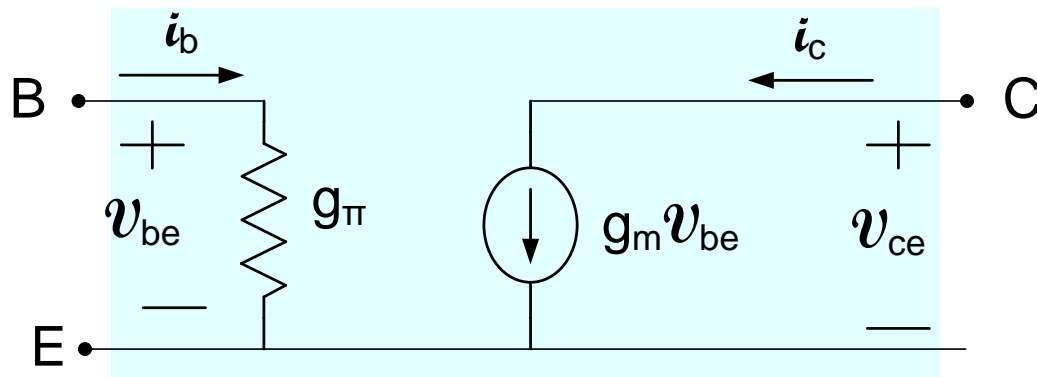


Gains for MOSFET and BJT Circuits


BJT

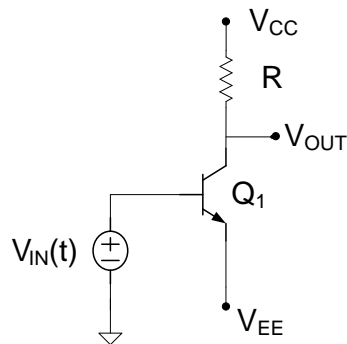


$$A_{VB} = -\frac{I_{CQ} R_1}{V_t}$$

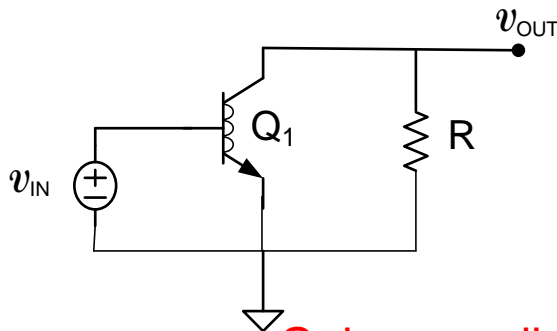

MOSFET

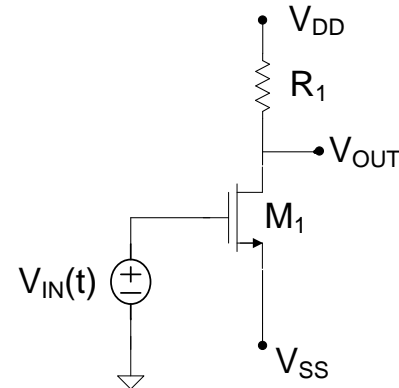
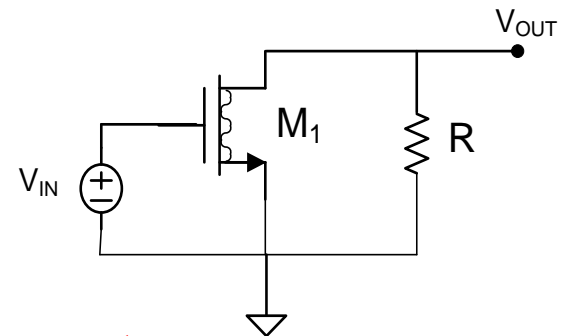
$$A_{VM} = \frac{2I_{DQ} R}{[V_{SS} + V_T]}$$



For both circuits


$$A_v = -g_m R$$

Gains vary linearly with small signal parameter g_m

Power is often a key resource in the design of an integrated circuit

In both circuits, power is proportional to I_{CQ} , I_{DQ}

How does g_m vary with I_{DQ} ?

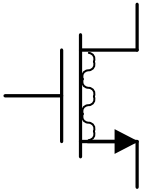

$$g_m = \sqrt{\frac{2\mu C_{ox} W}{L}} \sqrt{I_{DQ}}$$

Varies with the square root of I_{DQ}

$$g_m = \frac{2I_{DQ}}{V_{GSQ} - V_T} = \frac{2I_{DQ}}{V_{EBQ}}$$

Varies linearly with I_{DQ}

$$g_m = \frac{\mu C_{ox} W}{L} (V_{GSQ} - V_T)$$

Doesn't vary with I_{DQ}

How does g_m vary with I_{DQ} ?

All of the above are true – but with qualification

g_m is a function of more than one variable (I_{DQ}) and how it varies depends upon how the remaining variables are constrained

End of Lecture 25