

EE 330

Lecture 26


Bipolar Processes

- Device Sizes
- Parasitic Devices
 - JFET
 - Thyristors


Thyristors

- SCR – Basic operation

Amplifier Biasing (precursor)

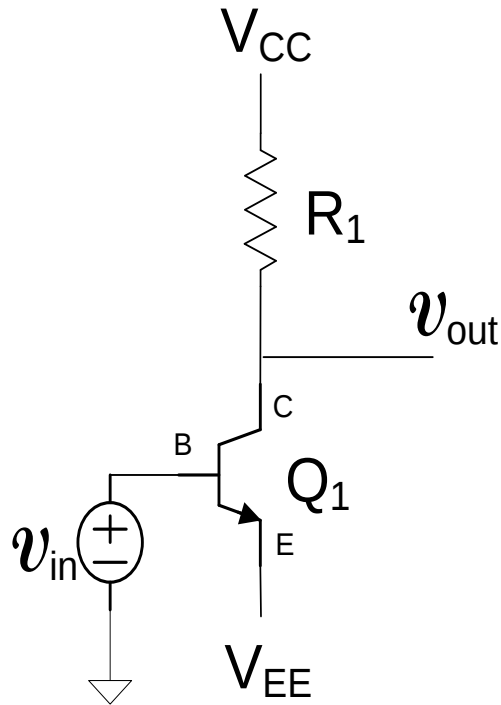


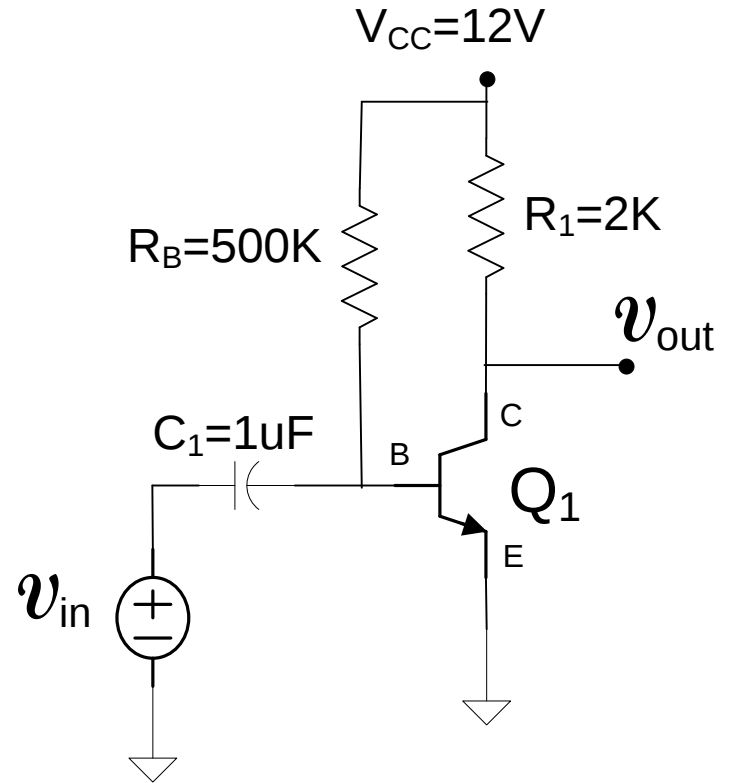
Not convenient to have multiple dc power supplies
 V_{OUTQ} very sensitive to V_{EE}





Single power supply
Additional resistor and capacitor

Compare the small-signal equivalent circuits of these two structures
Compare the small-signal voltage gain of these two structures

Amplifier Biasing (precursor)

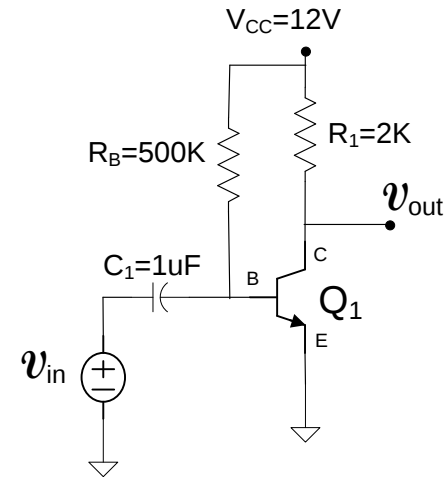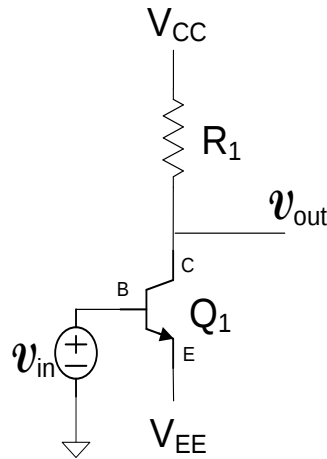

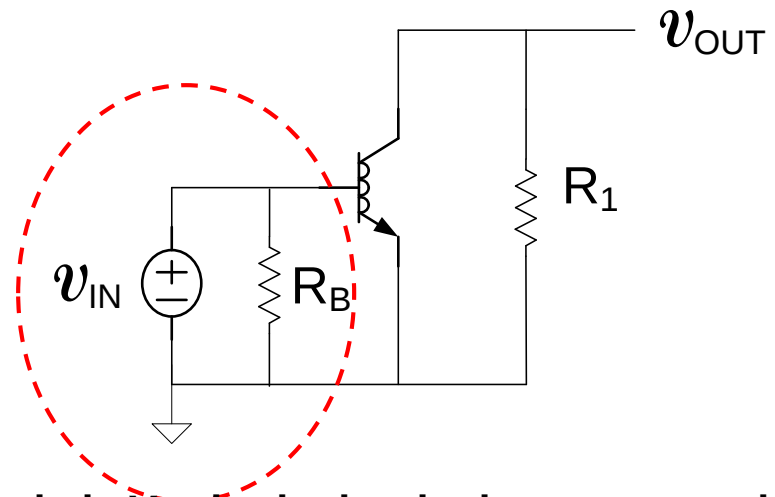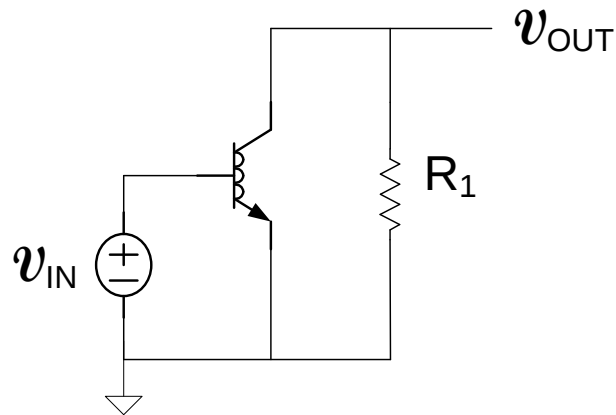Compare the small-signal equivalent circuits of these two structures



Since Thevenin equivalent circuit in red circle is V_{IN} , both circuits have same voltage gain


But the load placed on V_{IN} is different

Method of characterizing the amplifiers is needed to assess impact of difference

Amplifier Characterization (an example)

Determine V_{OUTQ} , A_v , R_{IN}

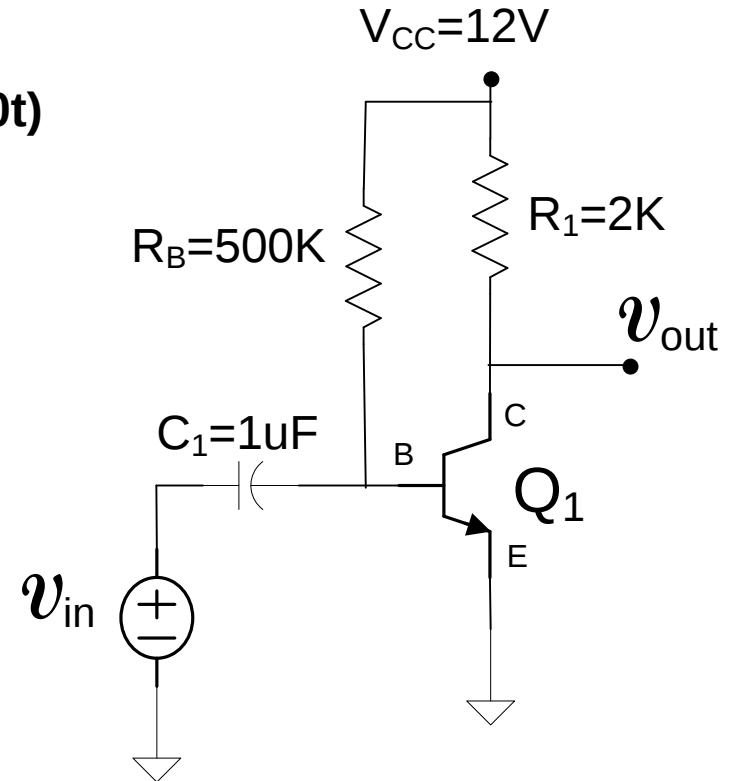Determine v_{OUT} and $V_{OUT}(t)$ if $v_{IN}=.002\sin(400t)$



In the following slides we will analyze this circuit

Topical Coverage Change

Will have several additional lectures on amplifier structures but will temporarily suspend discussion of amplifiers to consider Thyristors

This is being done to get ready for the Thyristor laboratory experiments

Outline




Bipolar Processes

- Comparison of MOS and Bipolar Process
- Parasitic Devices in CMOS Processes
- JFET


Special Bipolar Processes

- Thyristors
SCR
TRIAC





Review from a Previous Lecture

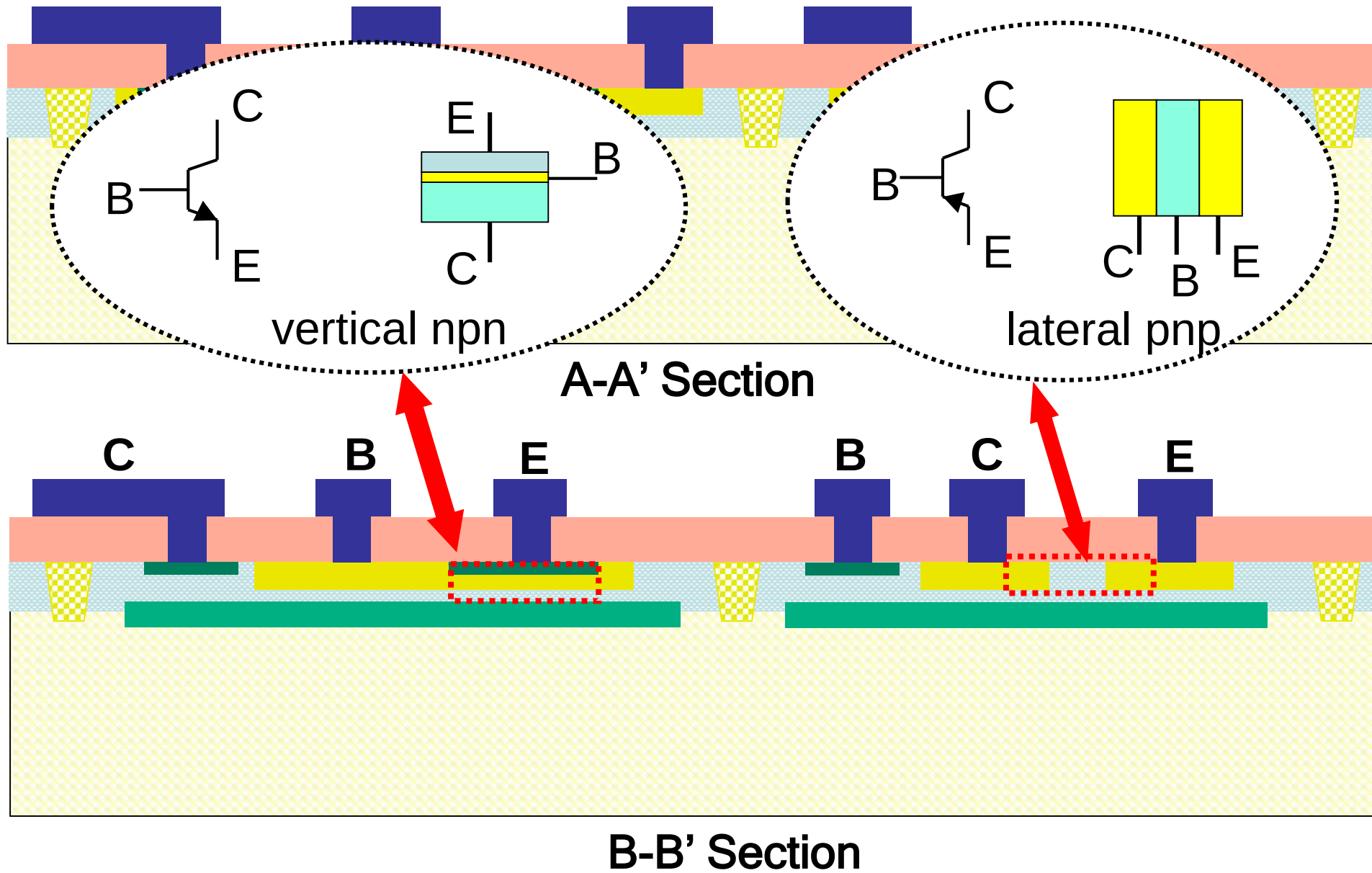

Review from a Previous Lecture



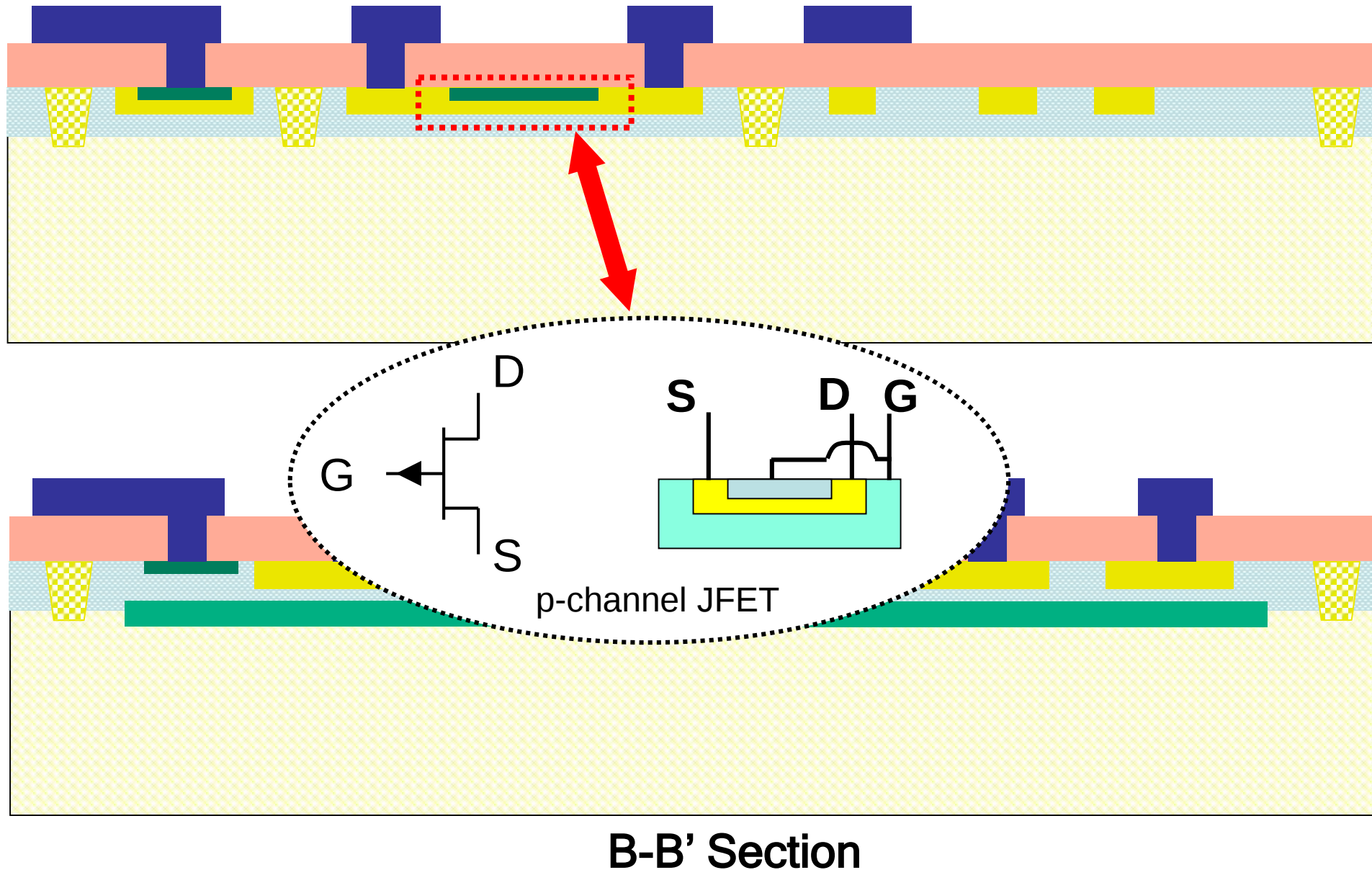


Review from a Previous Lecture

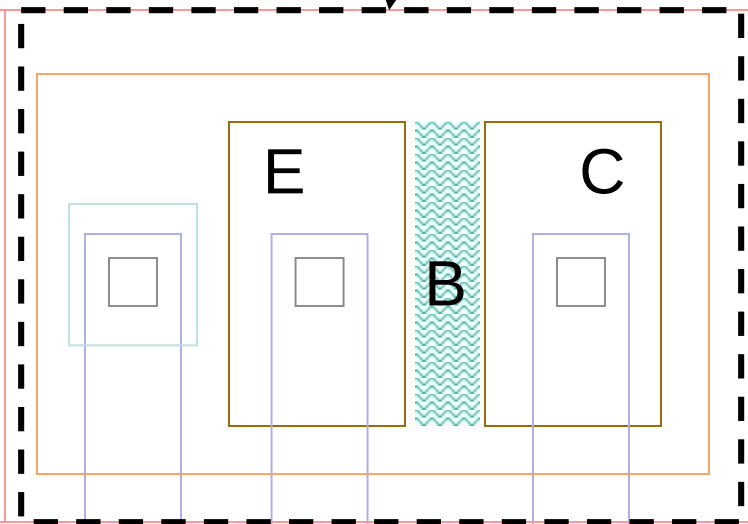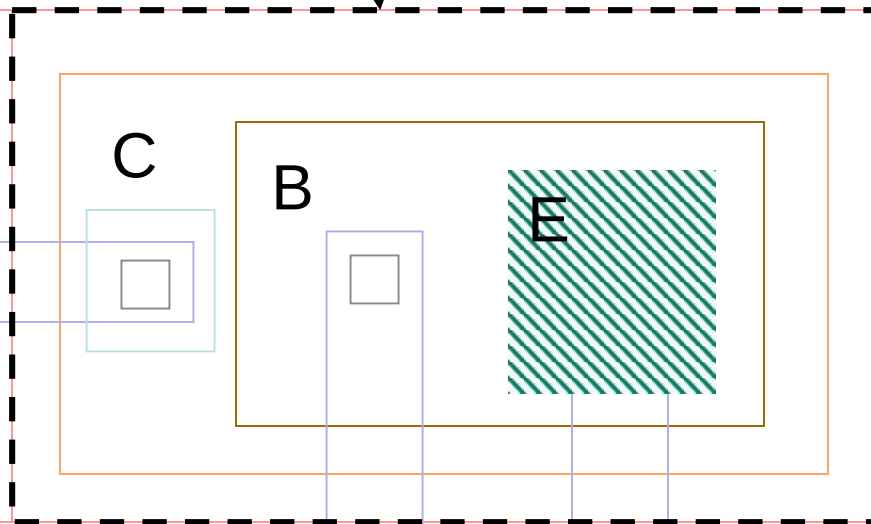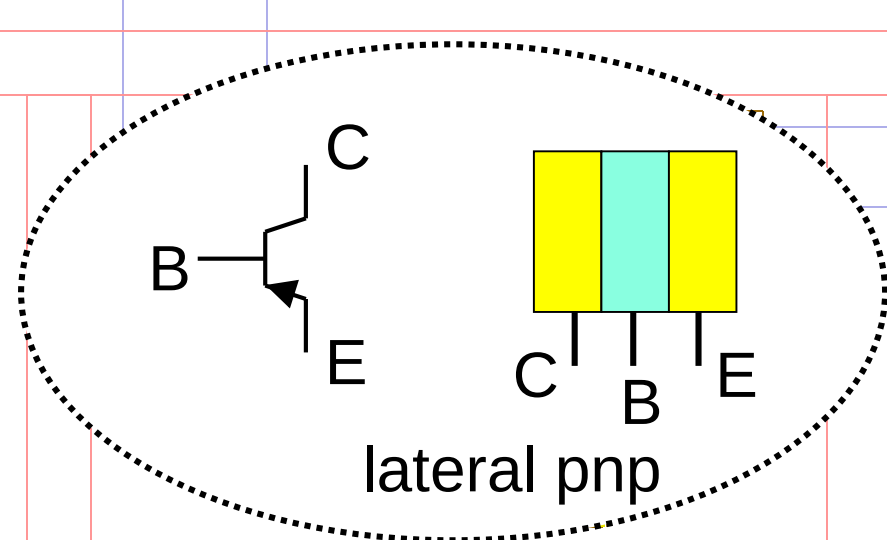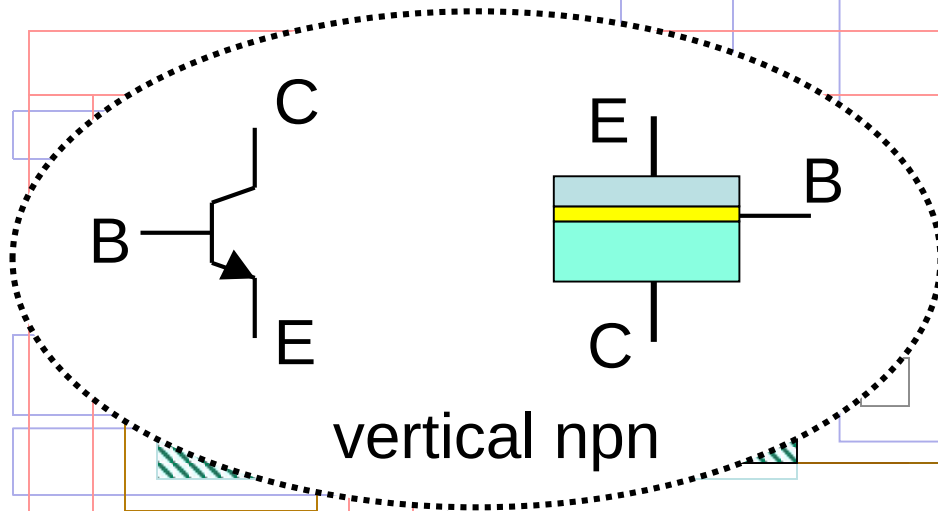


Review from a Previous Lecture

Diode (capacitor)

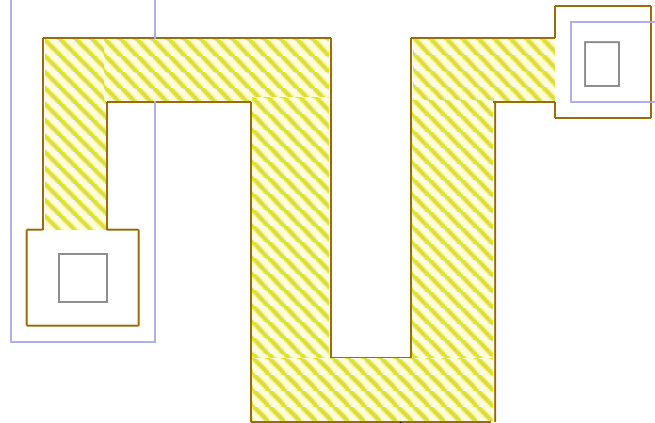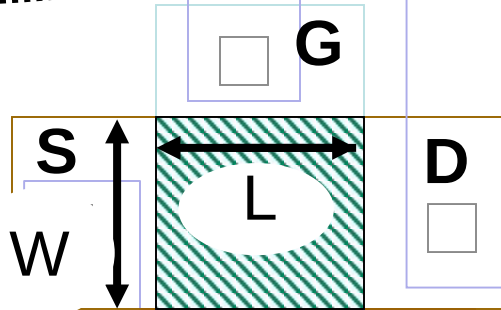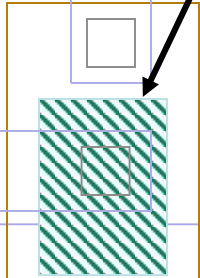

Resistor

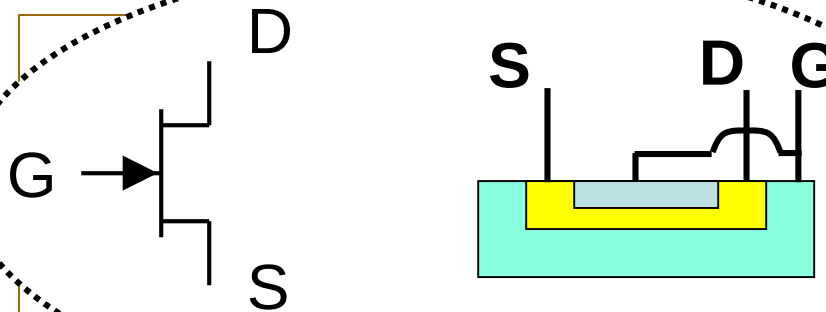

p-channel JFET

Will consider next the JFET but first some additional information about MOS Devices

Enhancement and Depletion MOS Devices

- Enhancement Mode n-channel devices

$$V_T > 0$$

- Enhancement Mode p-channel devices

$$V_T < 0$$

- Depletion Mode n-channel devices

$$V_T < 0$$


- Depletion Mode p-channel devices

$$V_T > 0$$



Enhancement and Depletion MOS Devices

n-channel


p-channel

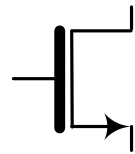

Enhancement

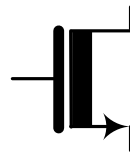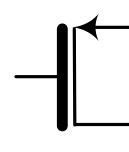



Depletion

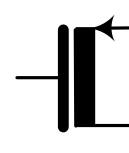

- Depletion mode devices require only one additional mask step
- Older n-mos and p-mos processes usually had a depletion device and an enhancement device
- Depletion devices usually not available in CMOS because applications usually do not justify the small increasing costs in processing



Under sufficiently large reverse bias (depletion region widens and channel disappears - “pinches off”)

The JFET

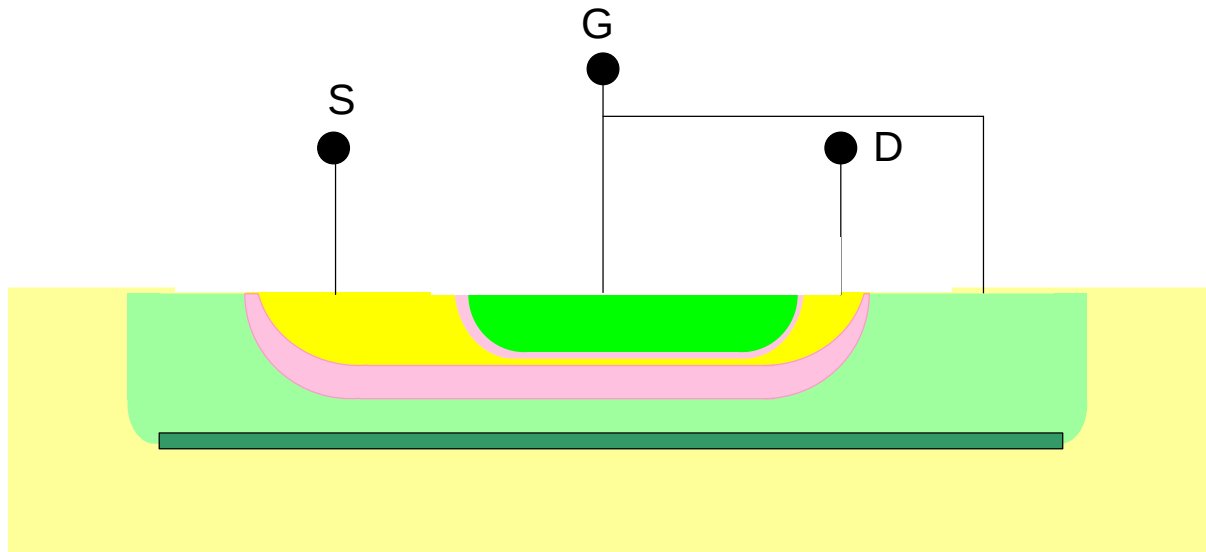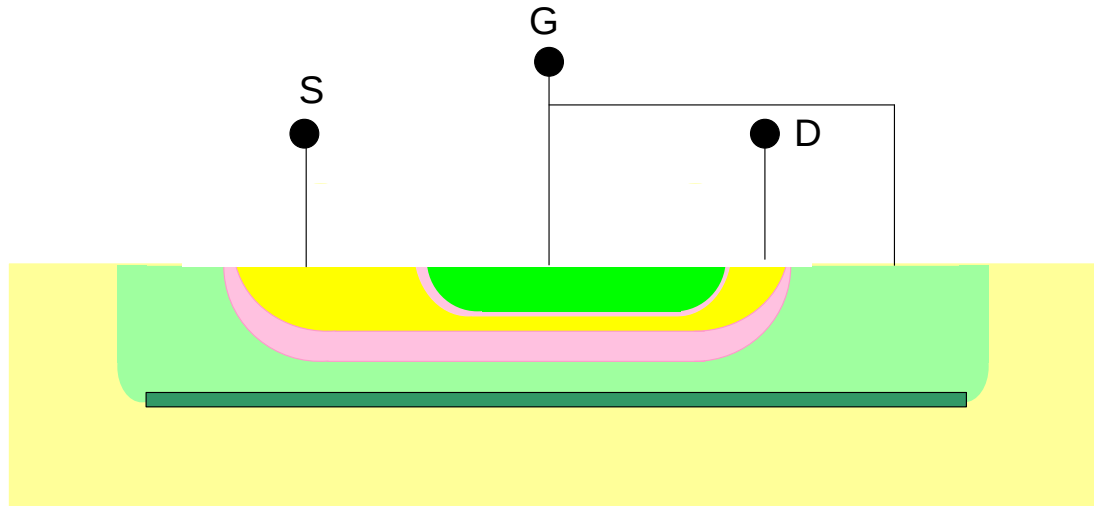


Under smaller reverse bias (depletion region widens and channel thins)

The JFET

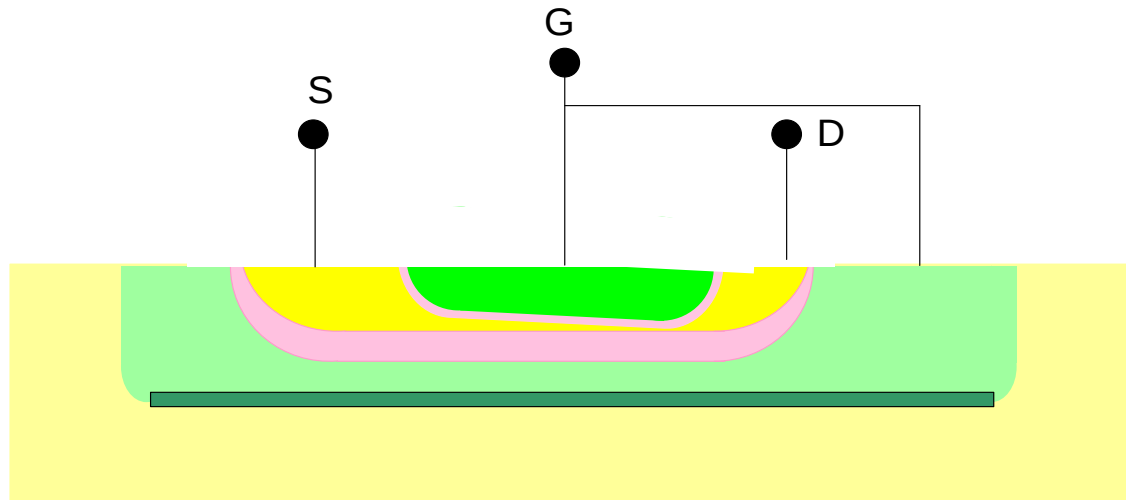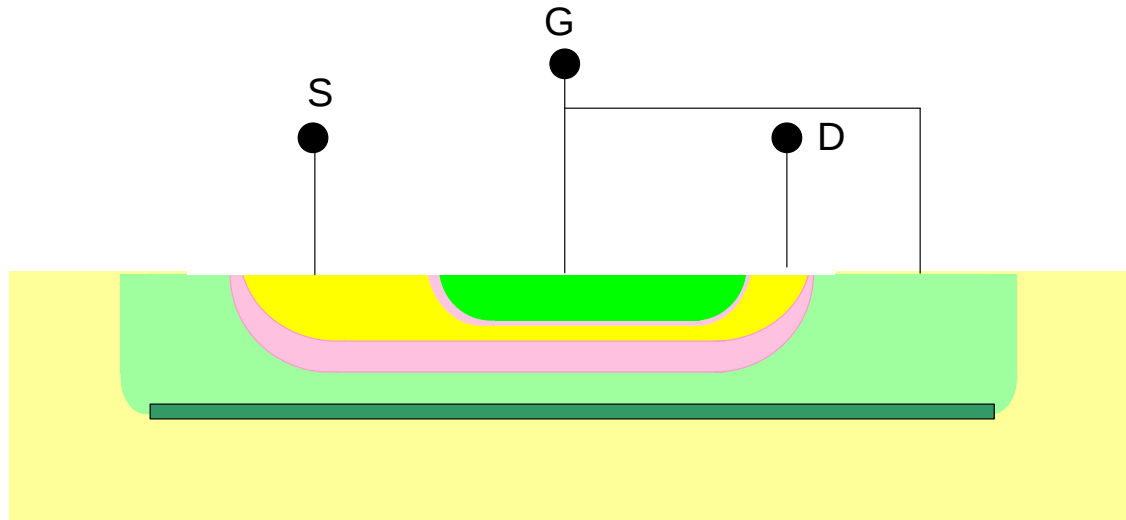


Under small reverse bias and large negative V_{DS} (channel pinches off)


The JFET

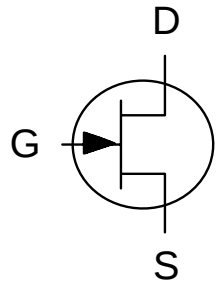

n-channel

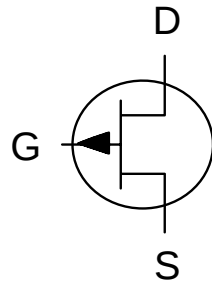

p-channel

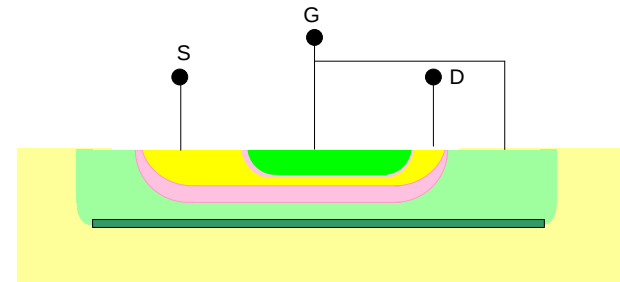

p-channel JFET


Square-law model of p-channel JFET

$$I_D = \begin{cases} 0 & V_{GS} > V_P \\ \frac{2I_{DSSp}}{V_P^2} \left(V_{GS} - V_P - \frac{V_{DS}}{2} \right) V_{DS} & -0.3 < V_{GS} < V_P \quad V_{GS} + 0.3 > V_{DS} > V_{GS} - V_P \\ I_{DSSp} \left(1 - \frac{V_{GS}}{V_P} \right)^2 & -0.3 < V_{GS} < V_P \quad V_{DS} < V_{GS} - V_P \end{cases}$$


(I_{DSSp} carries negative sign)

- Functionally identical to the square-law model of MOSFET
- Parameters I_{DSS} and V_P characterize the device
- I_{DSS} proportional to W/L where W and L are width and length of n+ diff
- V_P is negative for n-channel device, positive for p-channel device thus JFET is depletion mode device
- Must not forward bias GS junction by over about 300mV or excessive base current will flow (red constraint)
- Widely used as input stage for bipolar op amps


The JFET

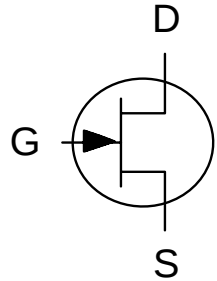

n-channel

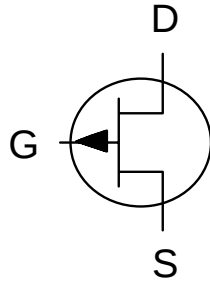

p-channel

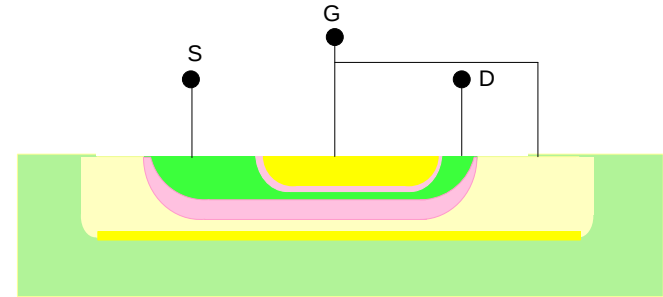



n-channel JFET
(not available in this process)

Square-law model of n-channel JFET

$$I_D = \begin{cases} 0 & V_{GS} < V_P \\ \frac{2I_{DSS}}{V_P^2} \left(V_{GS} - V_P - \frac{V_{DS}}{2} \right) V_{DS} & 0.3 > V_{GS} > V_P \quad V_{GS} - 0.3 < V_{DS} < V_{GS} - V_P \\ I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 & 0.3 > V_{GS} > V_P \quad V_{DS} > V_{GS} - V_P \end{cases}$$


- Functionally identical to the square-law model of MOSFET
- Parameters I_{DSS} and V_P characterize the device
- I_{DSS} proportional to W/L where W and L are width and length of n+ diff
- V_P is negative for n-channel device, positive for p-channel device thus JFET is depletion mode device
- Must not forward bias GS junction by over about 300mV or excessive base current will flow (red constraint)
- Widely used as input stage for bipolar op amps

The Schottky Diode

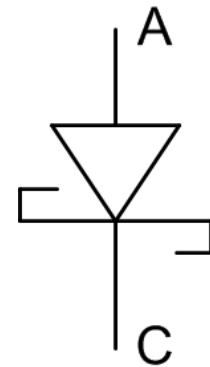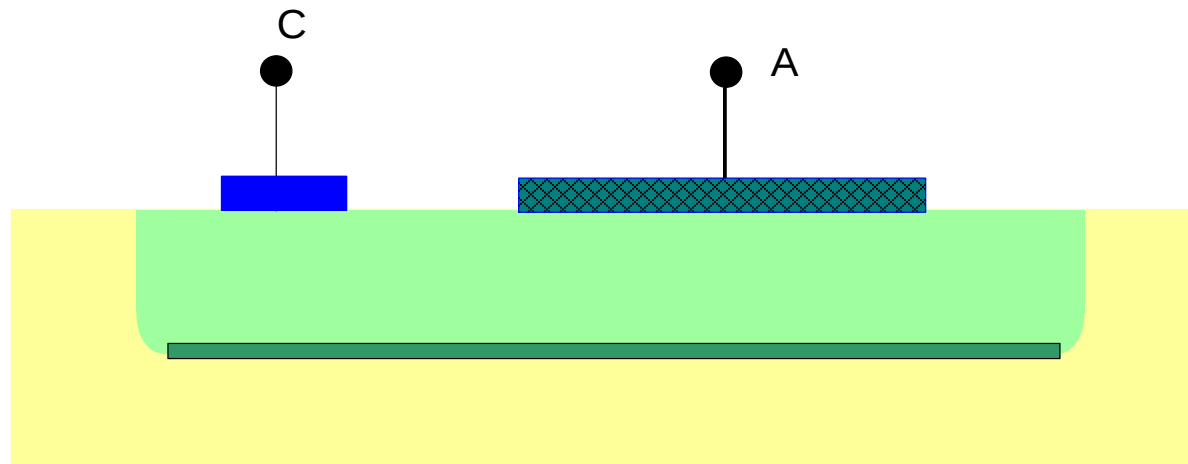

- Metal-Semiconductor Junction
- One contact is ohmic, other is rectifying
- Not available in all processes
- Relatively inexpensive adder in some processes
- Lower cut-in voltage than pn junction diode
- High speed

The MESFET

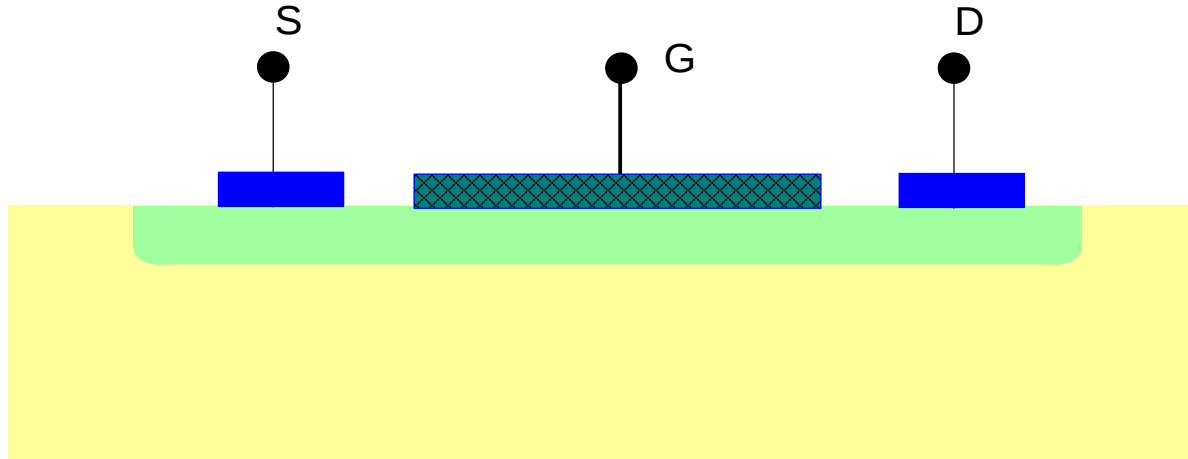


- Metal-Semiconductor Junction for Gate
- Drain and Source contacts ohmic, other is rectifying
- Usually not available in standard CMOS processes
- Must not forward bias very much
- Lower cut-in voltage than pn junction diode
- High speed

The Thyristor

A bipolar device in CMOS Processes

Consider a Bulk-CMOS Process

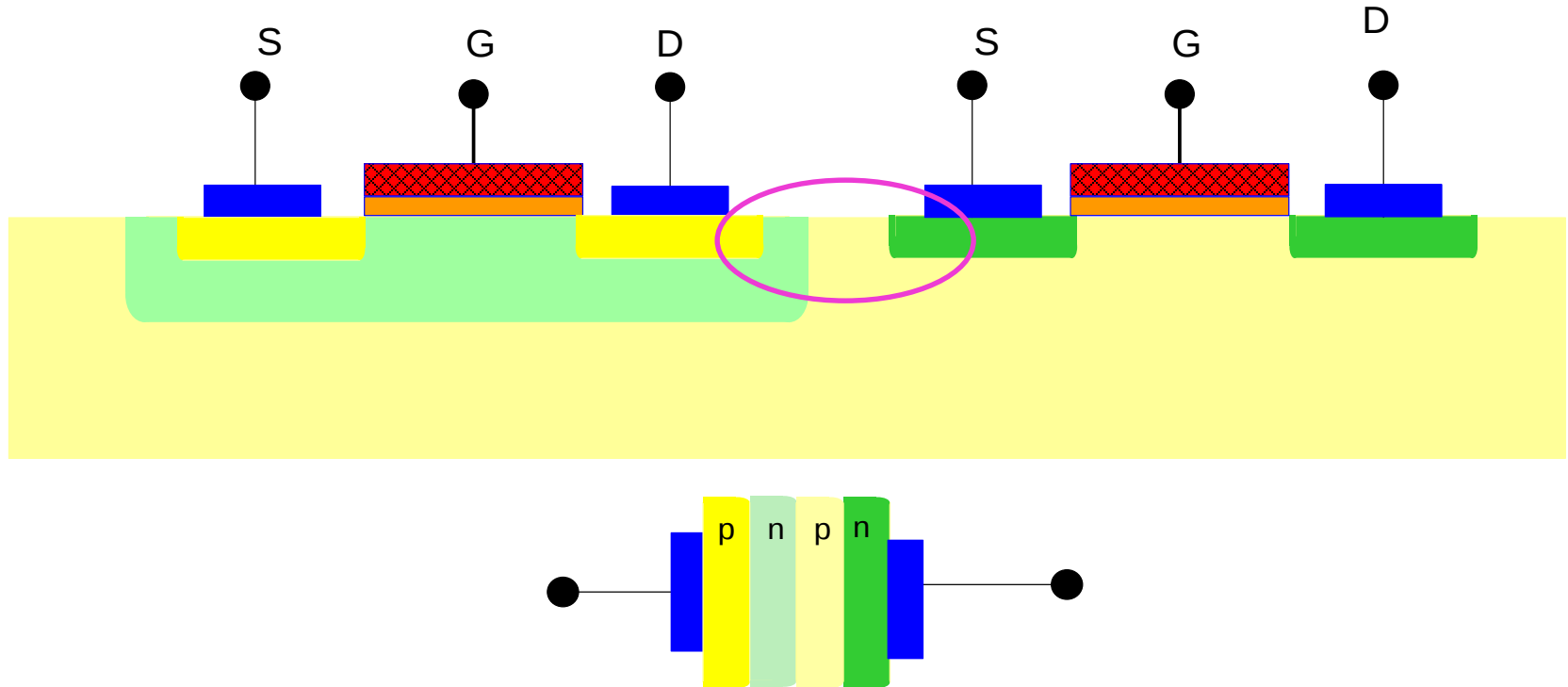

Have formed a lateral pnpn device !

Will spend some time studying pnpn devices

Outline

Two-Port Amplifier Models

Bipolar Processes

- Comparison of MOS and Bipolar Process
- Parasitic Devices in CMOS Processes
- JFET



Special Bipolar Processes

- Thyristors
SCR
TRIAC

Thyristors

The good and the bad!

Thyristors

The good

SCRs

Triacs


The bad

Parasitic Device that can destroy integrated circuits




The SCR

Silicon Controlled Rectifier

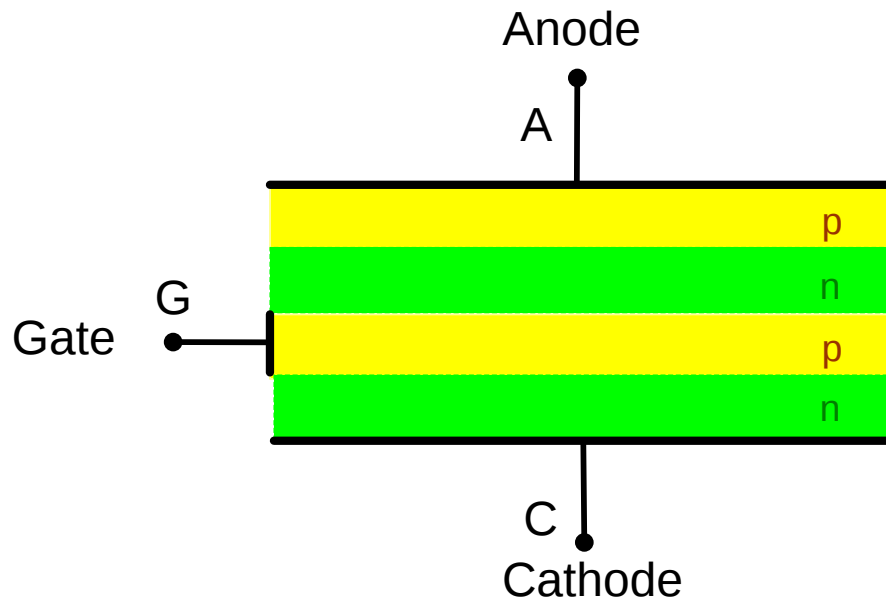- Widely used to switch large resistive or inductive loads
- Widely used in the power electronics field
- Widely used in consumer electronic to interface between logic and power







Usually made by diffusions in silicon

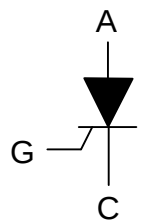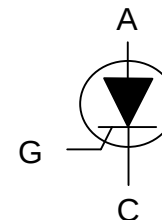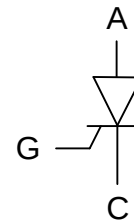

Symbols


Consider first how this 4-layer 3-junction device operates

Operation of the SCR

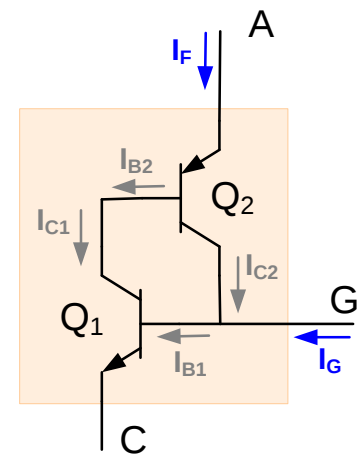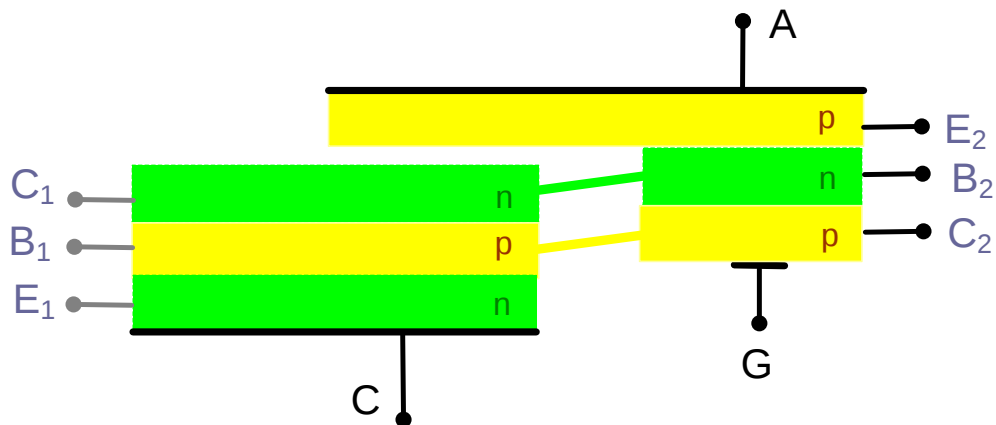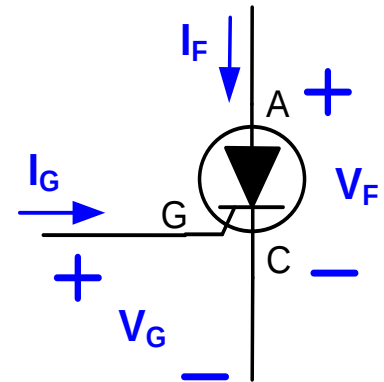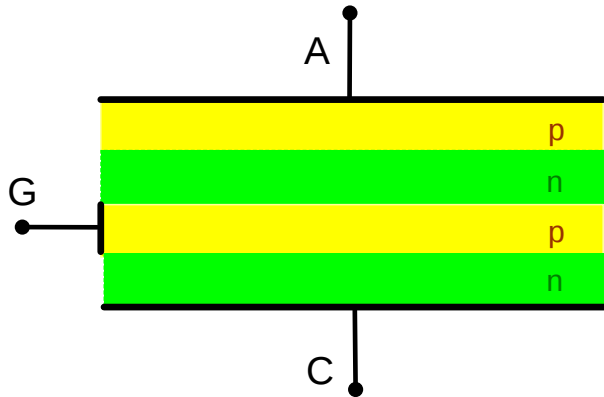


Not actually separated but useful for describing operation

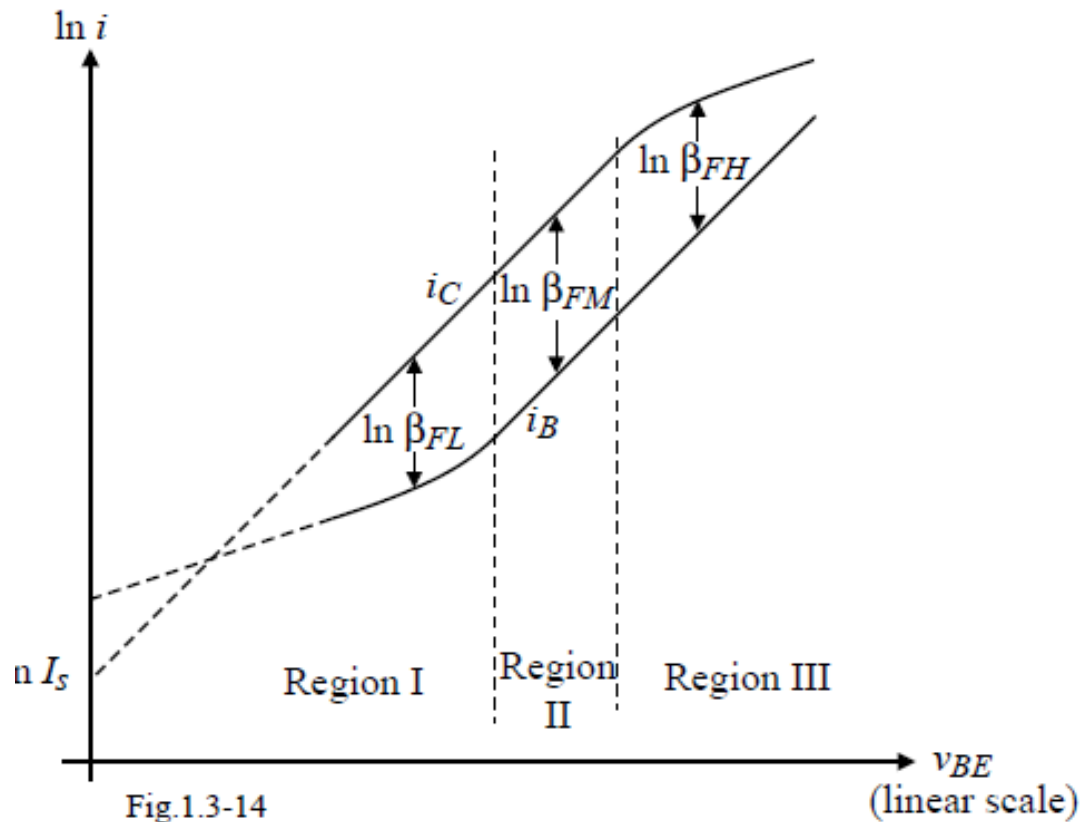Variation of Current Gain (β) with Bias for BJT



Note that current gain gets very small at low base current levels

Operation of the SCR

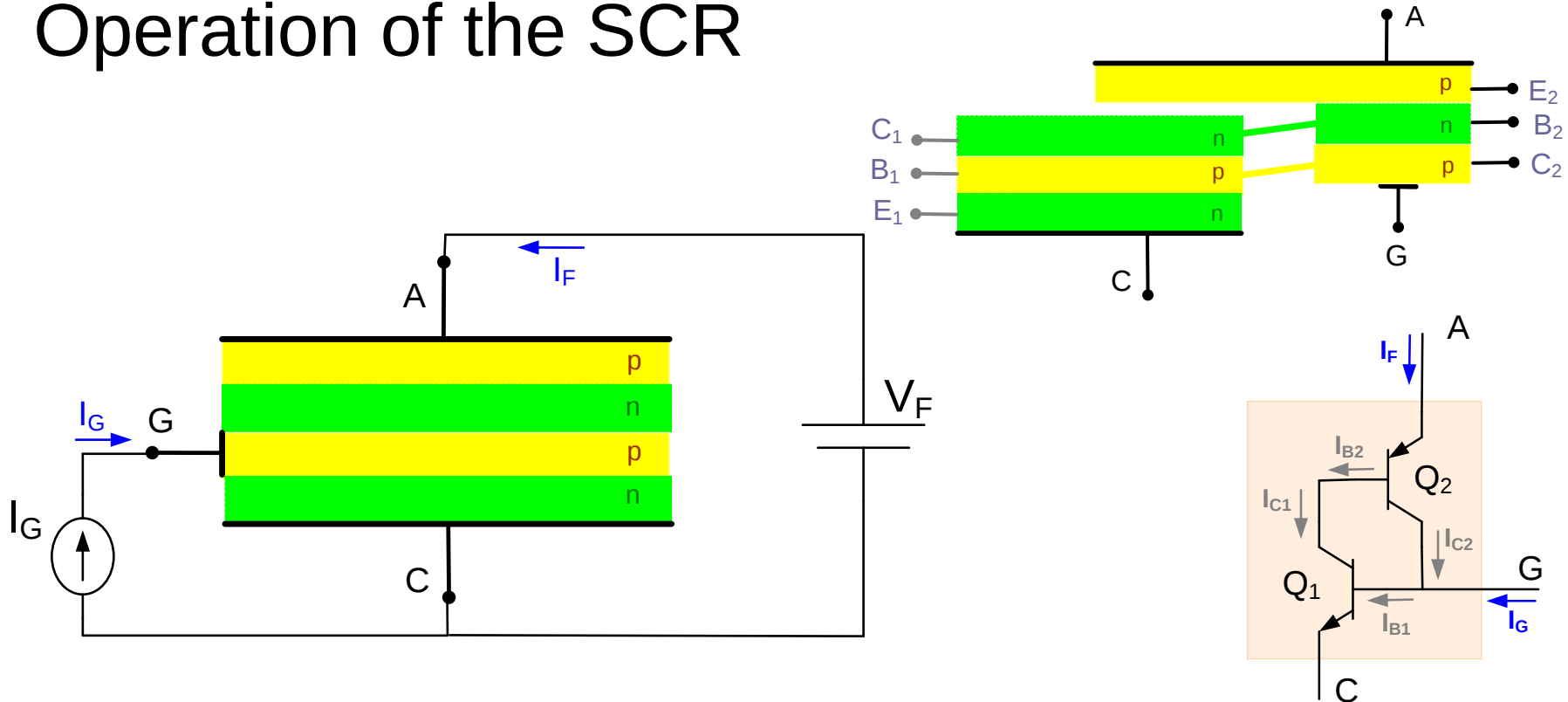

Consider a small positive bias (voltage or current) on the gate ($V_{GC} < 0.5V$) and a positive and large voltage V_F




Will have $V_{C1} \geq V_F - 0.5V$

Thus Q_1 has a large positive voltage on its collector

Since $V_{B_{E1}}$ is small, I_{C1} will be small as will I_{C2} so diode equation governs BE junction of Q_1

I_F will be very small

Operation of the SCR

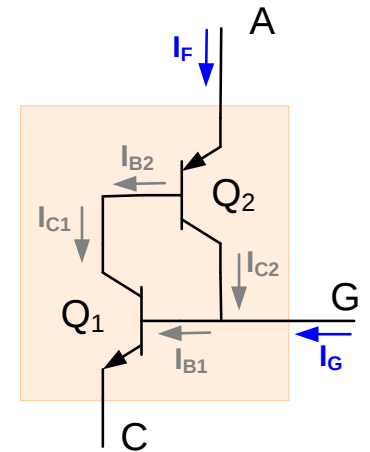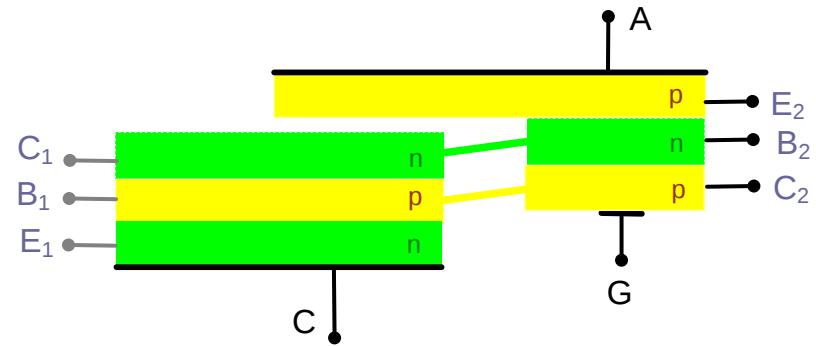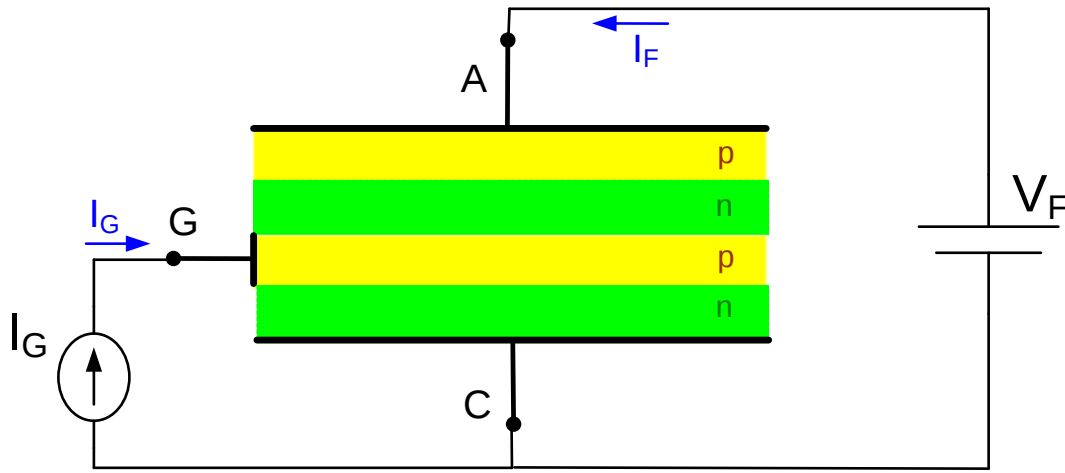

Now let bias on the gate increase (V_{GC} around 0.6V) so Q_1 and Q_2 in FA $V_{C1} \geq V_F - 0.5V$

From diode equation, base voltage V_{BE1} will increase and collector current I_{C1} will increase



Thus base current I_{B2} will increase as will the collector current of I_{C2}

Under assumption of operation in FA region get expression

$$I_{B1} = I_G + \beta_1 \beta_2 I_{B1}$$

This is regenerative feedback (actually can show pole in RHP)

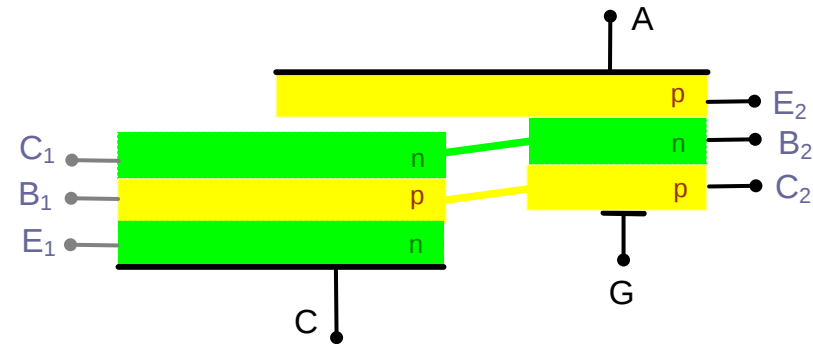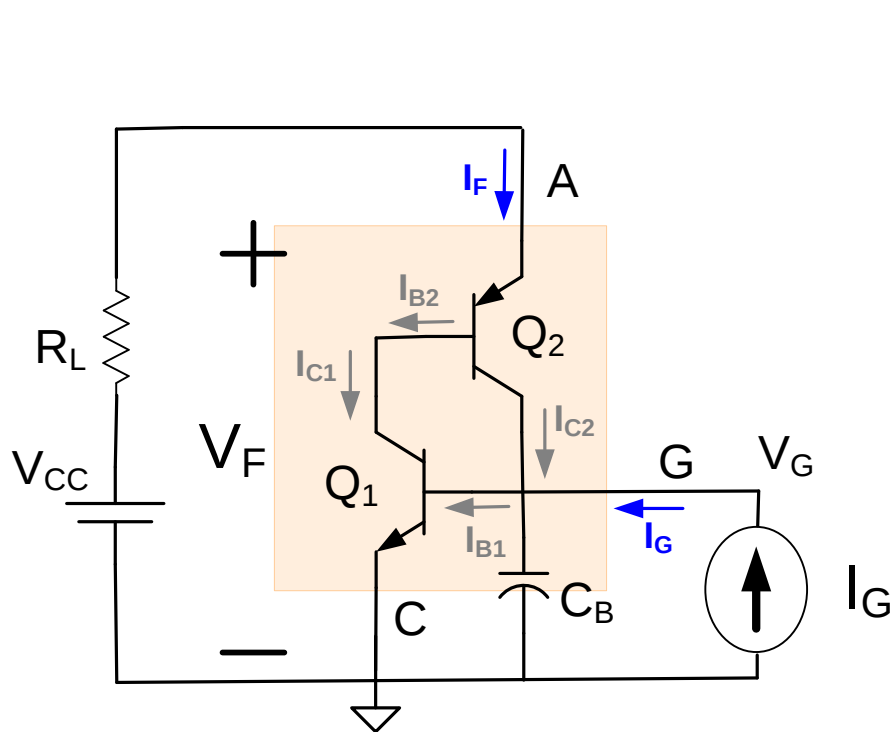Very Approximate Analysis Showing RHP Pole



$$V_G = I_G \frac{R_{BE}}{sR_{BE}C_B + 1 - \beta_1\beta_2}$$


$$V_G sC_B + I_{B1} = I_{C2} + I_G$$

$$I_{C2} = \beta_1\beta_2 I_{B1}$$

$$I_{B1} R_{BE} = V_G$$

$$p = \frac{\beta_1\beta_2 - 1}{R_{BE}C_B}$$

Operation of the SCR

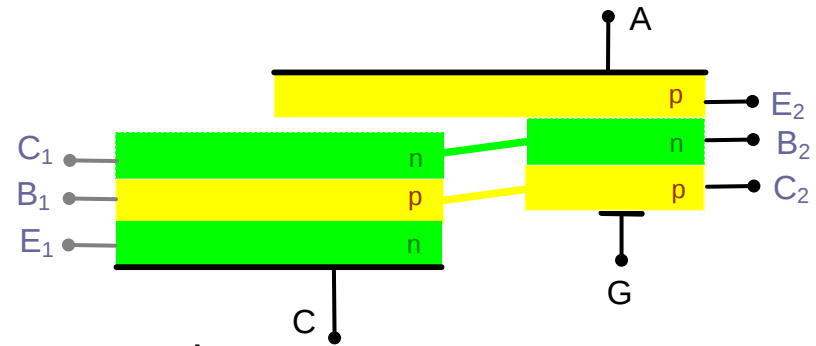

$$V_{C1} \cong V_F - 0.6V$$

Under assumption of operation in FA region get expression

$$I_{B1} = I_G + \beta_1 \beta_2 I_{B1}$$

What will happen with this is regenerative feedback?

If I_G is small (and thus β_1 and β_2 are small) I_F will be very small

If I_G larger but less than $\beta_1 \beta_2 I_{B1}$ it can be removed and current will continue to flow

I_{C1} will continue to increase and drive Q_1 into SAT


This will try to drive V_A towards 0.9V (but forced to be V_F !)

The current in V_F will go towards ∞

The SCR will self-destruct because of excessive heating !





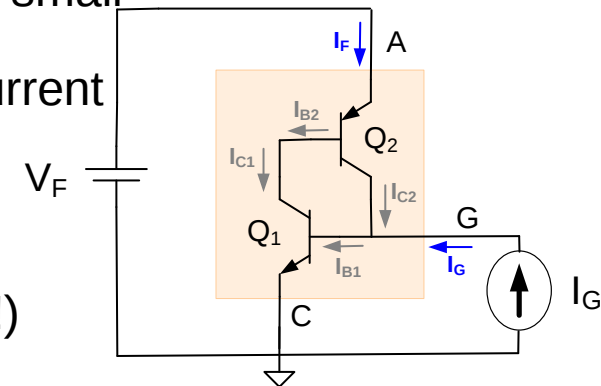Too bad the circuit self-destructed because the small gate current was able to control a lot of current!



Operation of the SCR

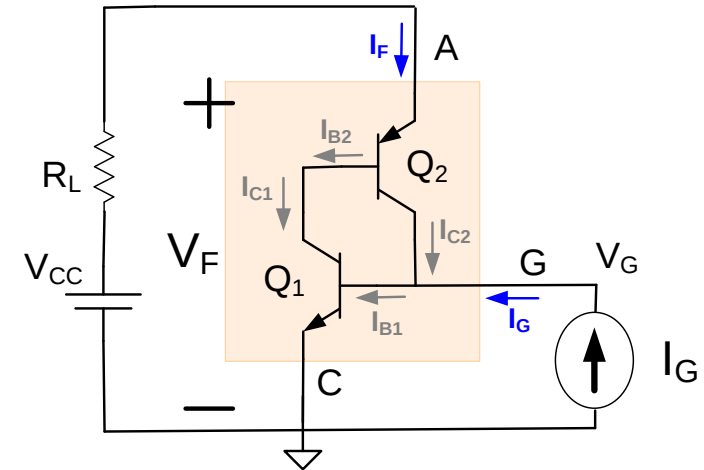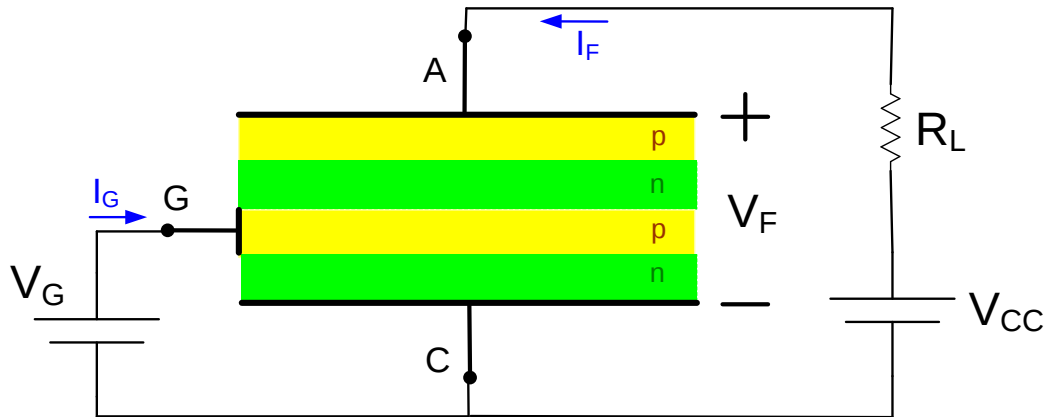Consider a modified application by adding a load (depicted as R_L)



All operation is as before, but now, after the triggering occurs, the voltage V_F will drop to approximately 0.8 V and the voltage $V_{CC} - 0.8$ will appear across R_L

If V_{CC} is very large, the SCR has effectively served as a switch putting V_{CC} across the load and after triggering occurs, I_G can be removed!


But, how can we turn it off?

Will discuss that later

Operation of the SCR

SCR model
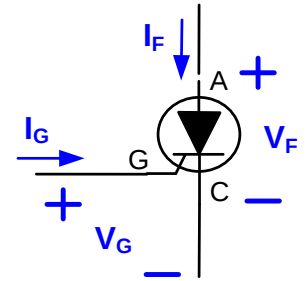
$$\left. \begin{aligned} I_F &= f_1(V_F, V_G) \\ I_G &= f_2(V_G) \end{aligned} \right\}$$



As for MOSFET, Diode, and BJT, several models for SCR can be developed

The Ideal SCR Model

$$\left. \begin{aligned} I_F &= f_{1I}(V_F, I_G) \\ I_G &= f_{2I}(V_G) \end{aligned} \right\}$$



or

$$\left. \begin{aligned} I_F &= f_{1A}(V_F, V_G) \\ I_G &= f_{2I}(V_G) \end{aligned} \right\}$$


Operation of the SCR

Consider the Ideal SCR Model
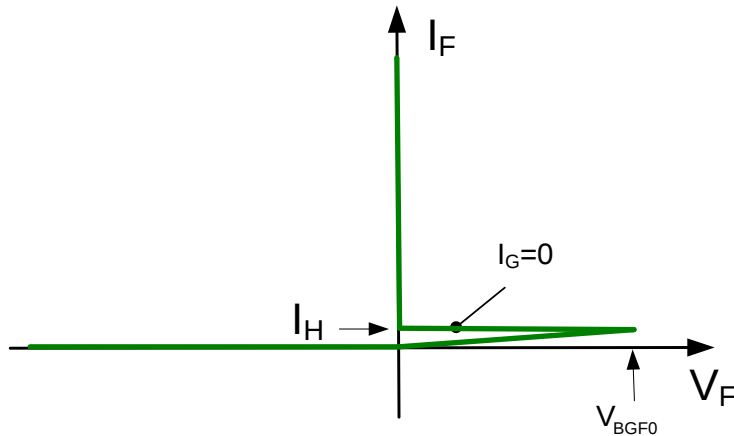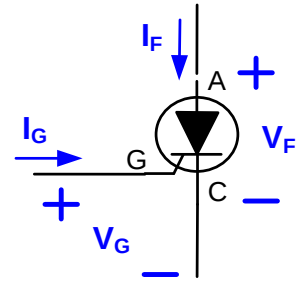
$$\left. \begin{aligned} I_F &= f_{1I}(V_F, I_G) \\ I_G &= f_{2I}(V_G) \end{aligned} \right\}$$



I_H is very small

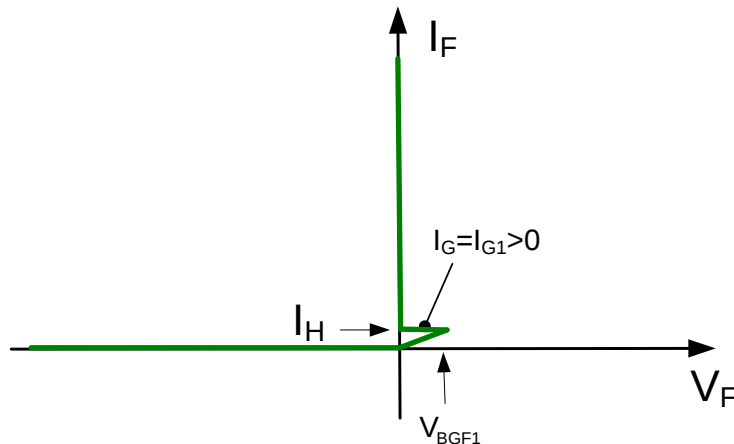


I_{G1} is small (but not too small)

Operation of the SCR


Operation with the Ideal SCR

Load Line: $V_{CC} = I_F R_L + V_F$

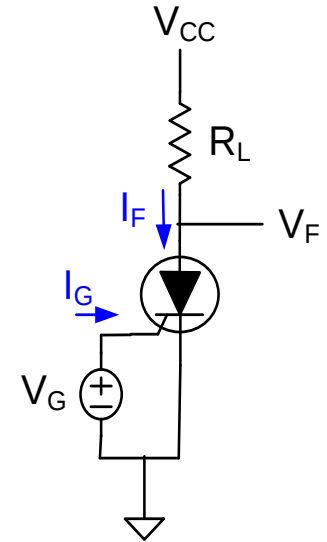Analysis:
$$\left. \begin{aligned} V_{CC} &= I_F R_L + V_F \\ I_F &= f_{II}(V_F, I_G) \end{aligned} \right\}$$



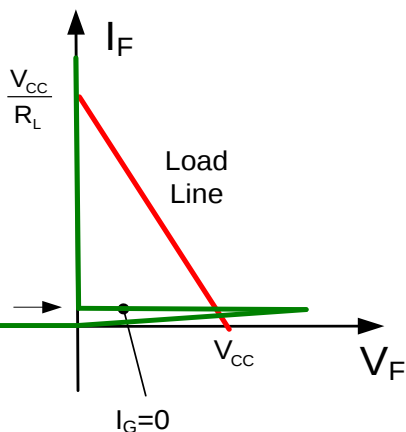The solution of these two equations is at the intersection of the load line and the device characteristics



when $I_G = 0$

Note three intersection points

Two (upper and lower) are stable equilibrium points, one is not

When operating at upper point, $V_F = 0$ so V_{CC} appears across R_L We say SCR is ON



When operating at lower point, I_F approx 0 so no signal across R_L We say SCR is OFF

When $I_G = 0$, will stay in whatever state it was in

Operation of the SCR

Operation with the Ideal SCR

$$I_F = f_1(V_F, I_G)$$

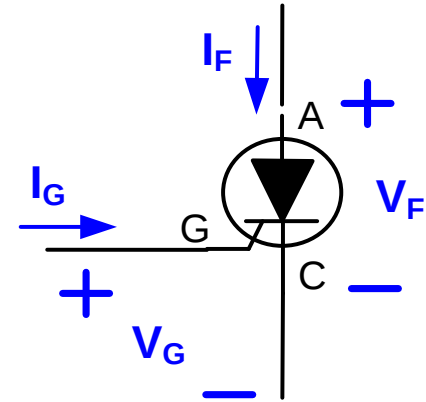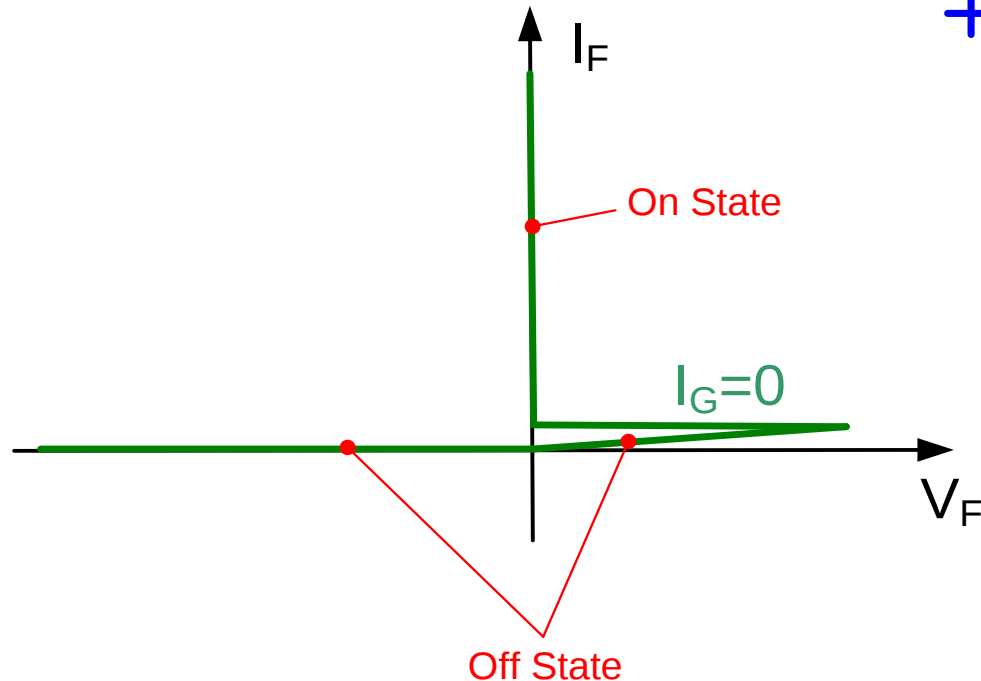


For notational convenience will drop subscript unless emphasis is needed

$$I_F = f_1(V_F, I_G) \quad \longrightarrow \quad I_F = f(V_F, I_G)$$



Operation of the SCR

Operation with the Ideal SCR

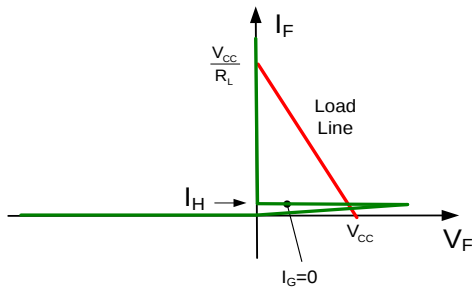Now assume it was initially in the OFF state and then a gate current was applied


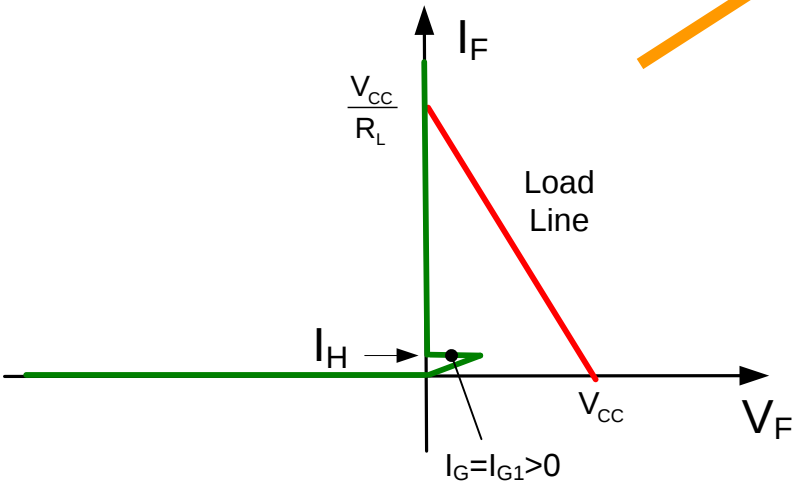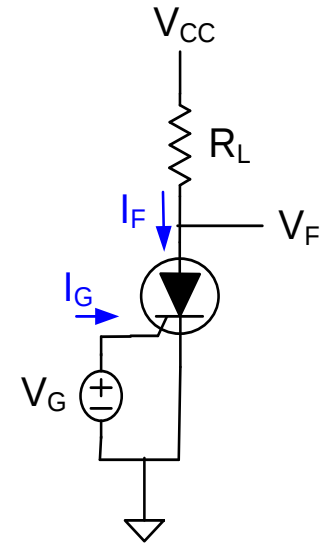
$$\left. \begin{aligned} V_{CC} &= I_F R_L + V_F \\ I_F &= f(V_F, I_G) \end{aligned} \right\}$$



Now there is a single intersection point so a unique solution



The SCR is now ON

Removing the gate current will return to the previous solution (which has 3 intersection points) but it will remain in the ON state

Operation of the SCR

Operation with the Ideal SCR

Turning SCR off when $I_G=0$

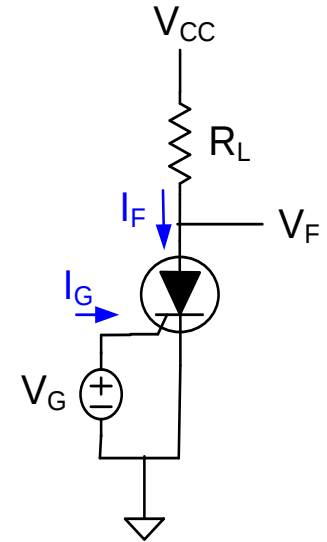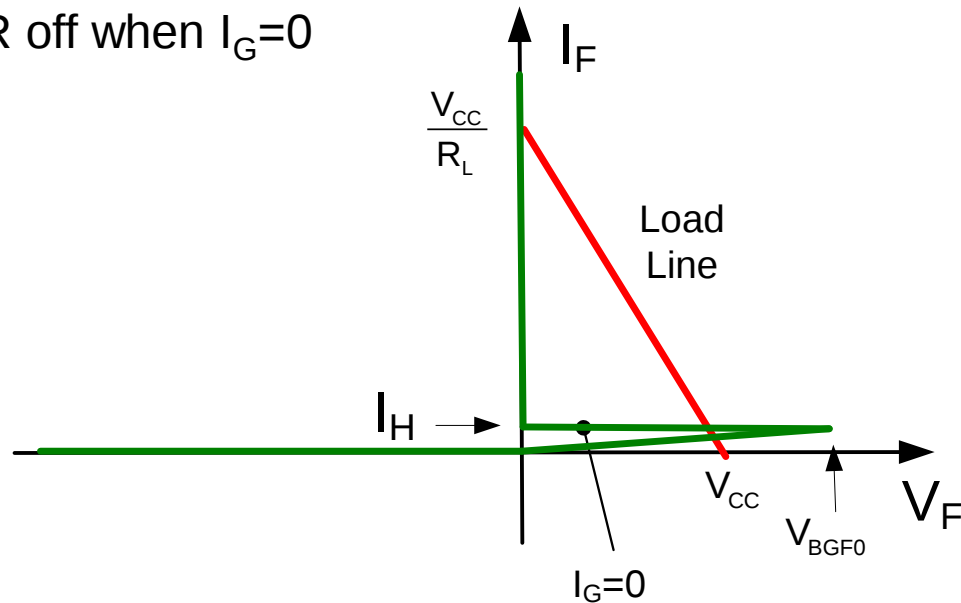

Reduce V_{CC} so that V_{CC}/R_L goes below I_H

This will provide a single intersection point



V_{CC} can then be increased again and SCR will stay off

Must not increase V_{CC} much above V_{BGF0} else will turn on

Operation of the SCR

Operation with the Ideal SCR

Turning SCR off when $I_G=0$

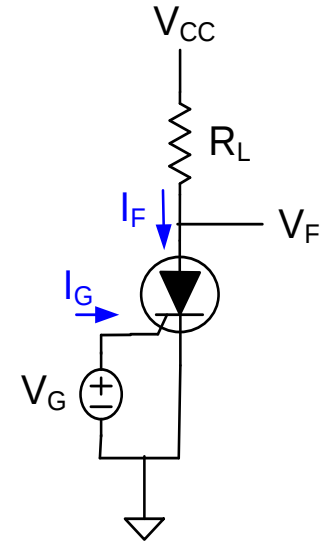
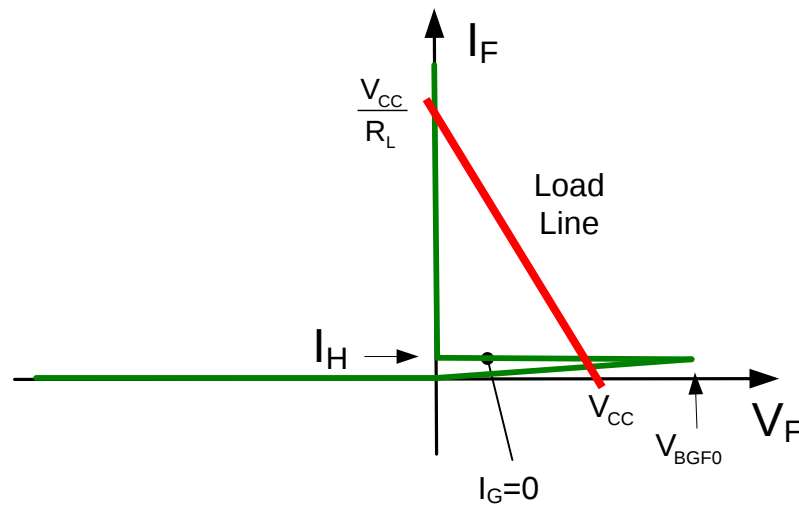


Operation of the SCR

Operation with the Ideal SCR

Often V_{CC} is an AC signal (often 110V)

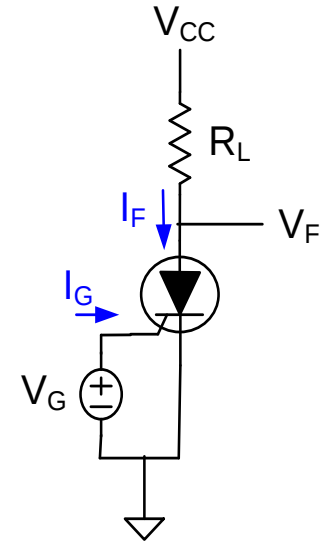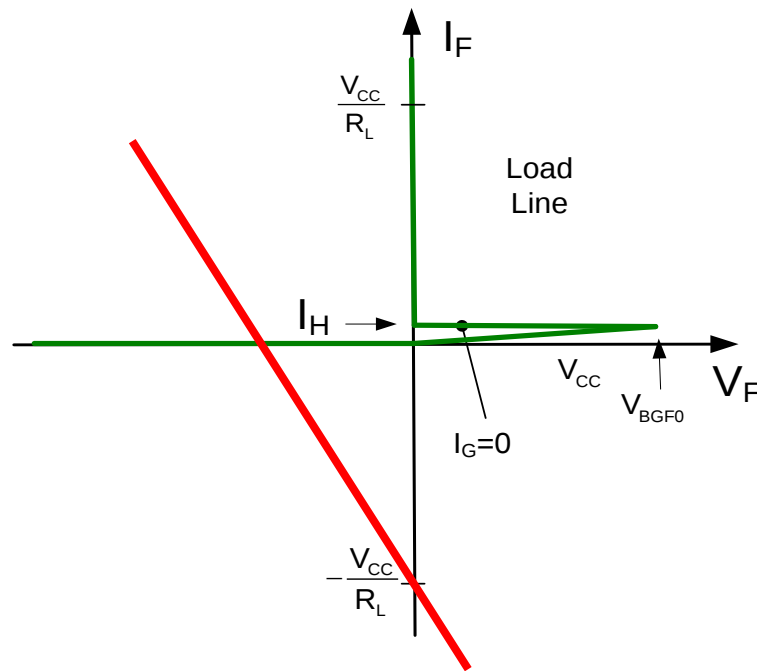SCR will turn off whenever AC signal goes negative





Operation of the SCR

Operation with the Ideal SCR

Often V_{CC} is an AC signal (often 110V)

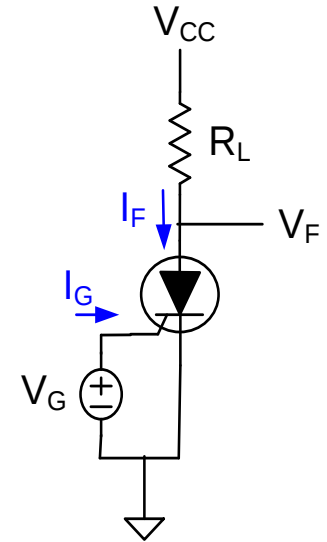
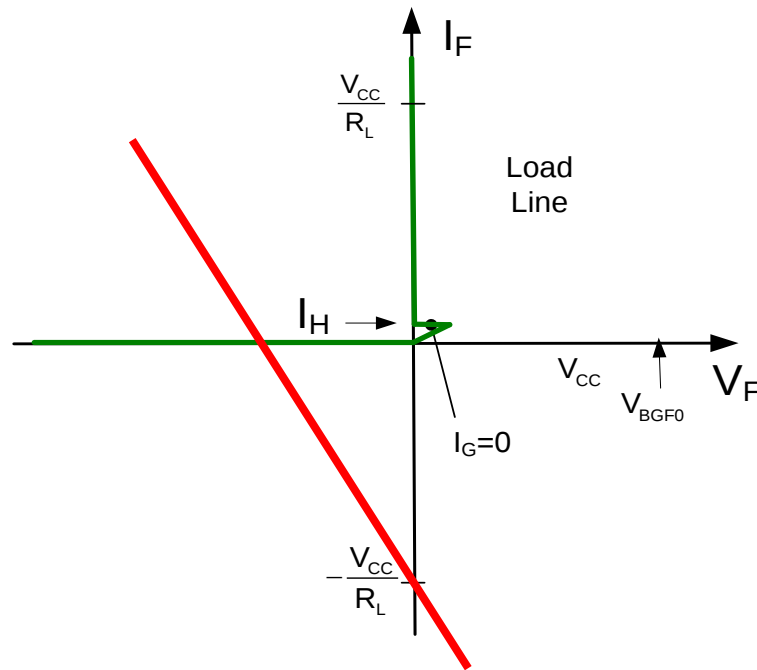
SCR will turn off whenever AC signal goes negative



Operation of the SCR

Operation with the Ideal SCR

Turning SCR off when $I_G > 0$

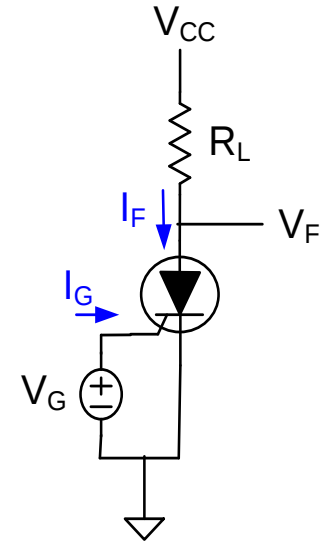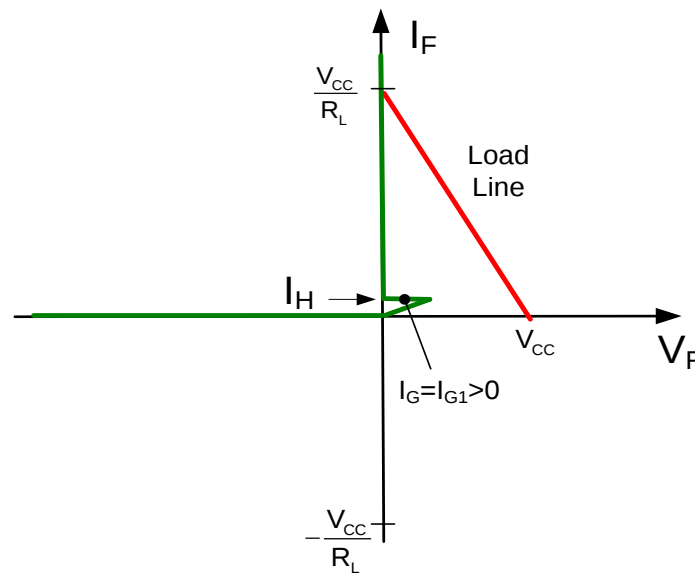

Reduce V_{CC} so that V_{CC}/R_L goes below I_H

This will provide a single intersection point

But when V_{CC} is then increased SCR will again turn on

Will not turn off if I_G is very large

End of Lecture 26