

EE 330


Lecture 29

Amplifier Biasing (a precursor)

Amplifier Characterization


- Amplifier parameters
- Two-port amplifier models
- Dependent Sources

Amplifier Biasing (precursor)

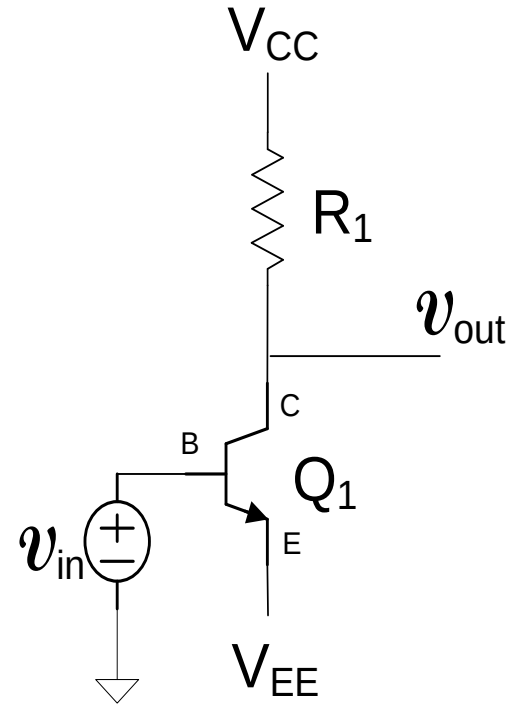


- Voltage sources V_{EE} and V_{CC} used for biasing
 - Not convenient to have multiple dc power supplies
 - V_{OUTQ} very sensitive to V_{EE}
-
- Biasing is used to obtain the desired operating point of a circuit
 - Ideally the biasing circuit should not distract significantly from the basic operation of the circuit

Amplifier Biasing (precursor)

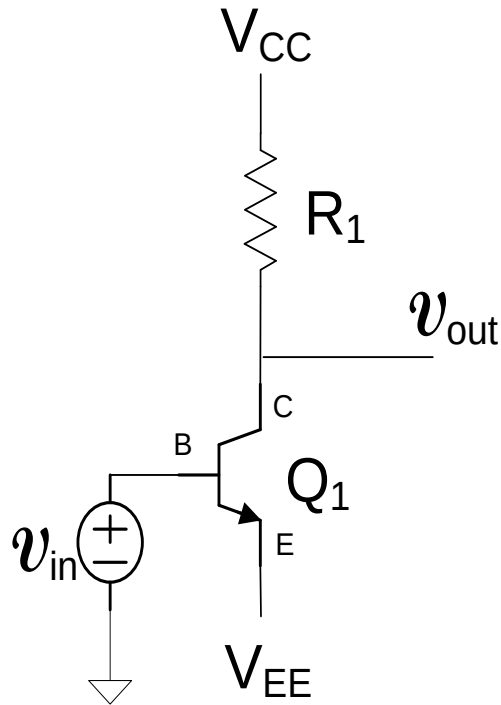

Not convenient to have multiple dc power supplies
 V_{OUTQ} very sensitive to V_{EE}



Will See this
is the Biasing
Circuit

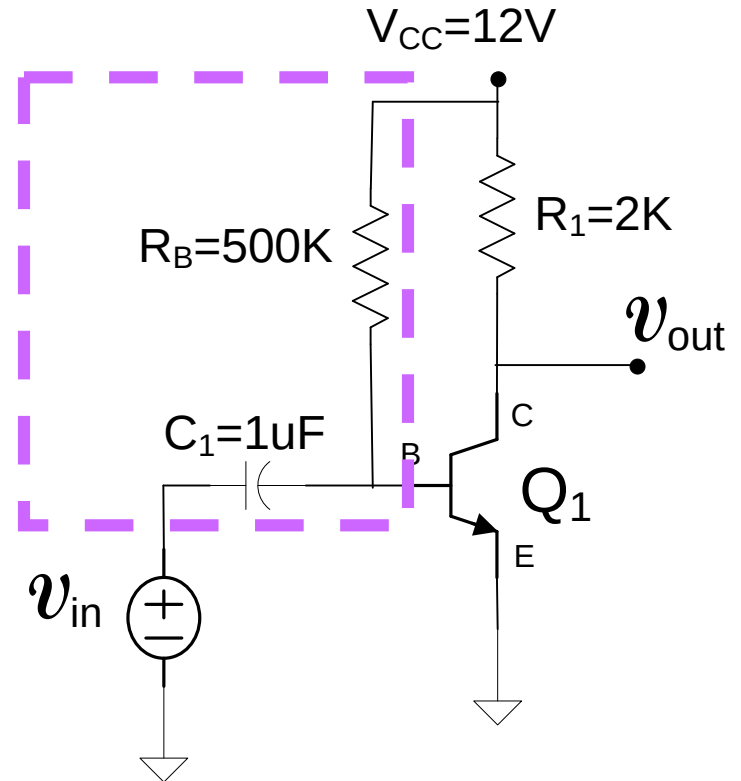



Single power supply
Additional resistor and capacitor

Compare the small-signal equivalent circuits of these two structures
Compare the small-signal voltage gain of these two structures

Amplifier Biasing (precursor)

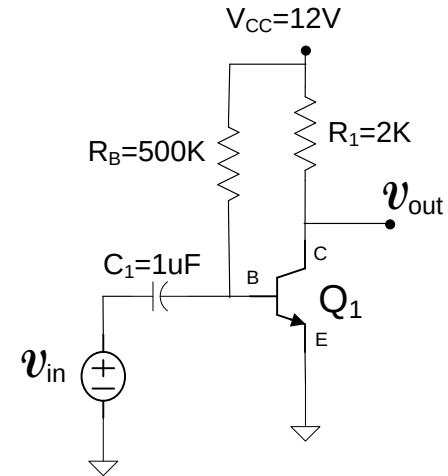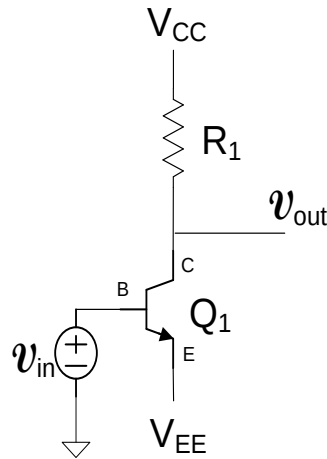

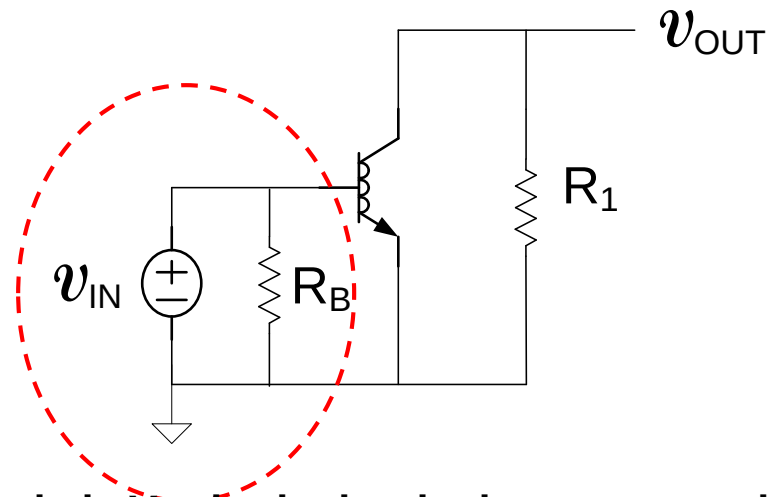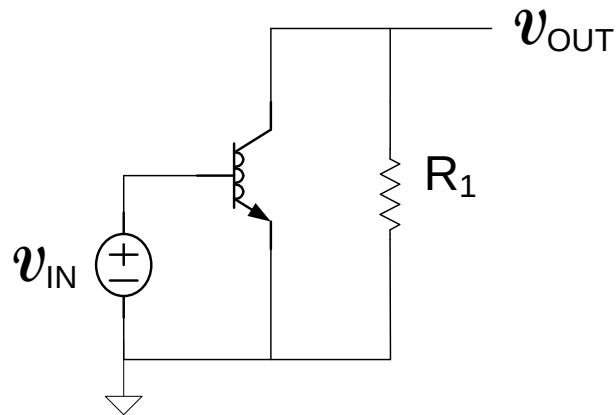Compare the small-signal equivalent circuits of these two structures



Since Thevenin equivalent circuit in red circle is V_{IN} , both circuits have same voltage gain

But the load placed on V_{IN} is different

Method of characterizing the amplifiers is needed to assess impact of difference

Amplifier Biasing (a precursor)


 Amplifier Characterization

- ✓• Amplifier parameters
- Two-port amplifier models
- Dependent Sources

Amplifier Characterization (an example)


Determine V_{OUTQ} , A_v , R_{IN} Assume $\beta=100$

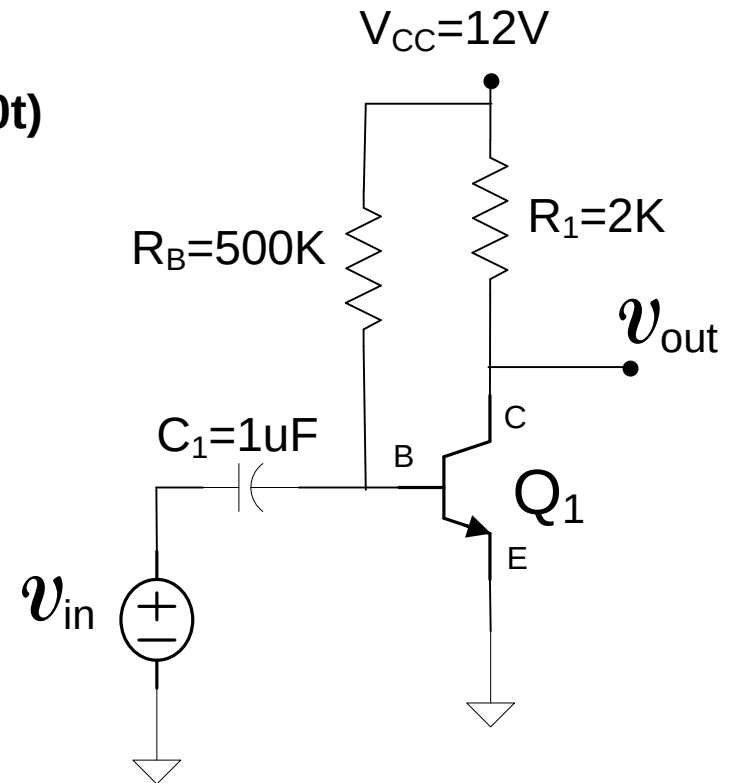Determine v_{OUT} and $V_{OUT}(t)$ if $v_{IN}=.002\sin(400t)$



In the following slides we will analyze this circuit

Amplifier Characterization (an example)

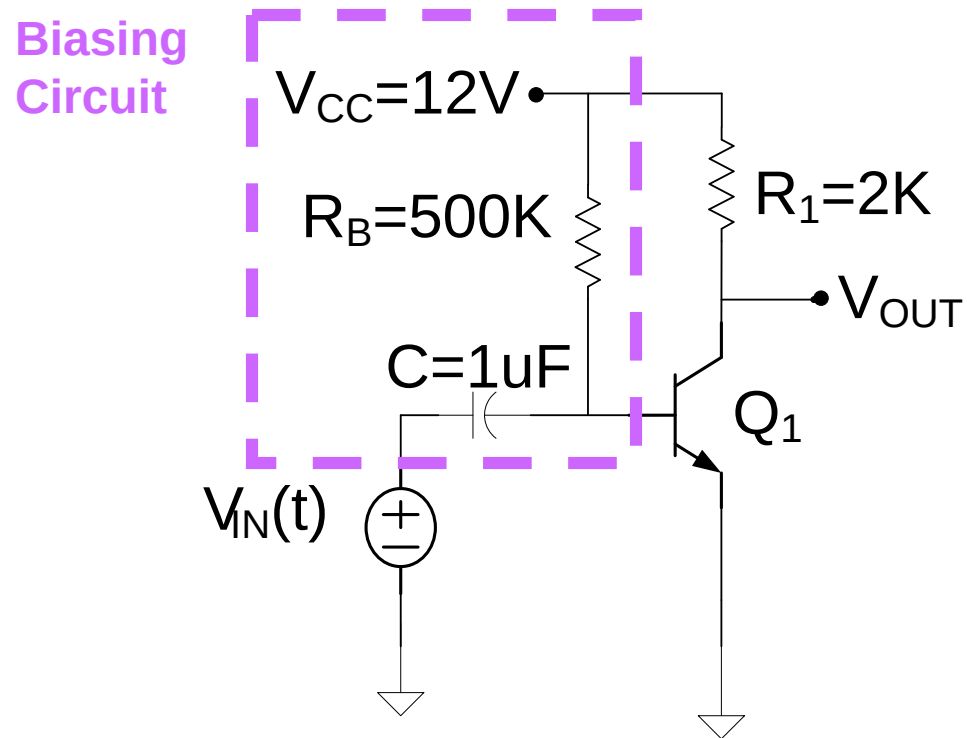


(biasing components: C , R_B , V_{CC} in this case, all disappear in small-signal gain circuit)

Several different biasing circuits can be used

Amplifier Characterization (an example)



Determine V_{OUTQ} , A_V , R_{IN}

Biased
Circuit

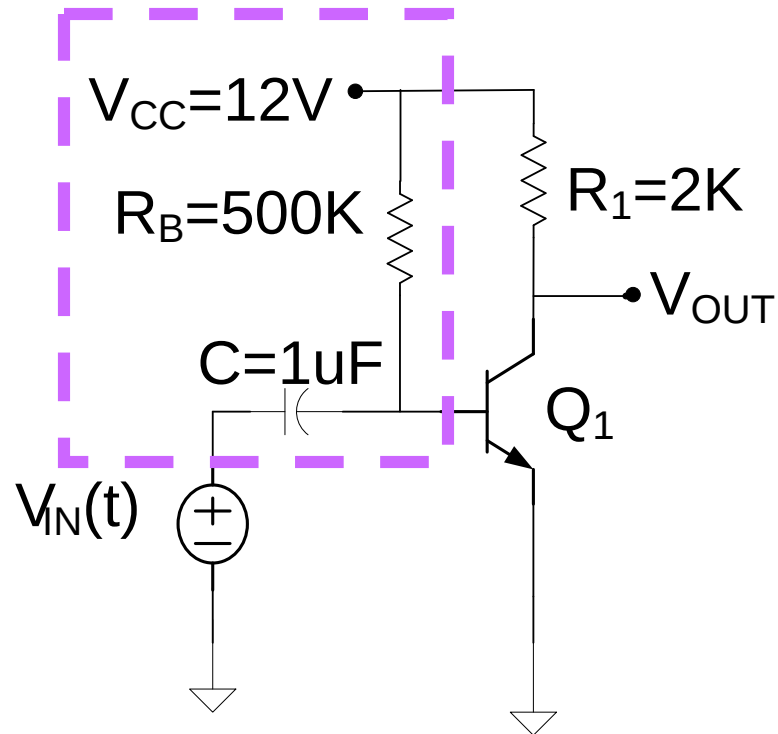

Amplifier Characterization (an example)

Determine V_{OUTQ}

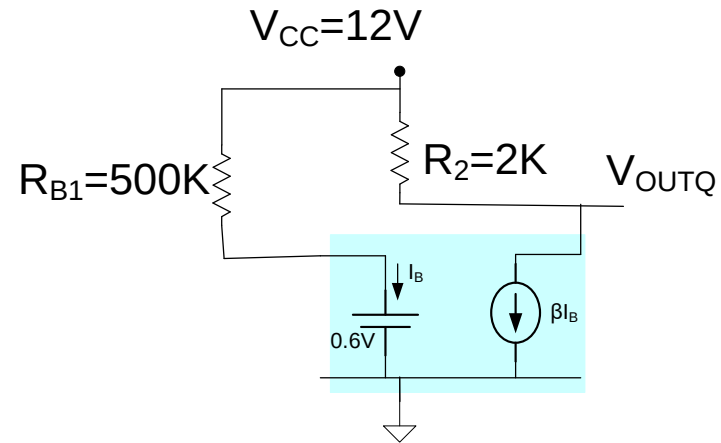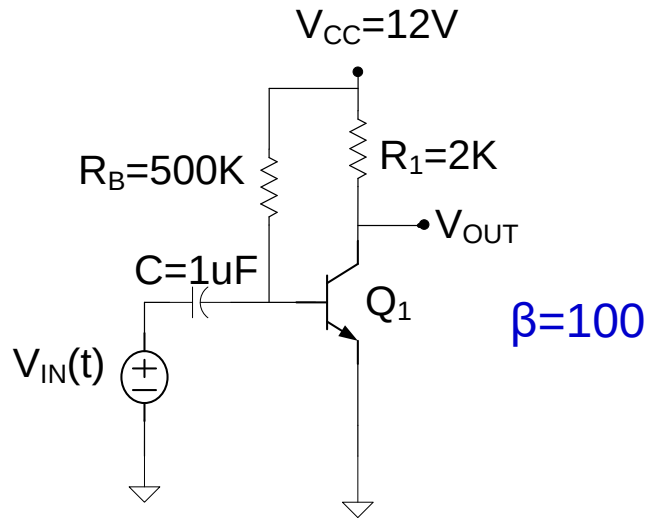


dc equivalent circuit

$$I_{CQ} = \beta I_{BQ} = 100 \left(\frac{12V - 0.6V}{500K} \right) = 2.3mA$$

$$V_{OUTQ} = 12V - I_{CQ} R_1 = 12V - 2.3mA \cdot 2K = 7.4V$$


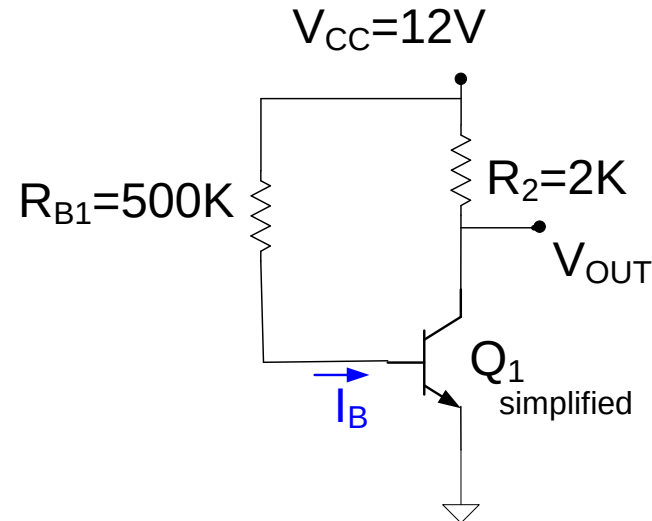
Check: $V_{CE} = V_{OUTQ} = 7.4V > 0.4V$ in F.A.




dc equivalent circuit

Amplifier Characterization (an example)

Determine the SS voltage gain (A_V)

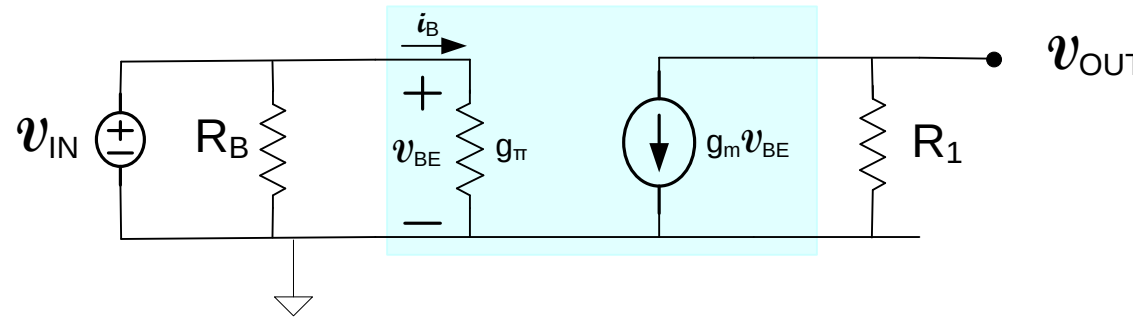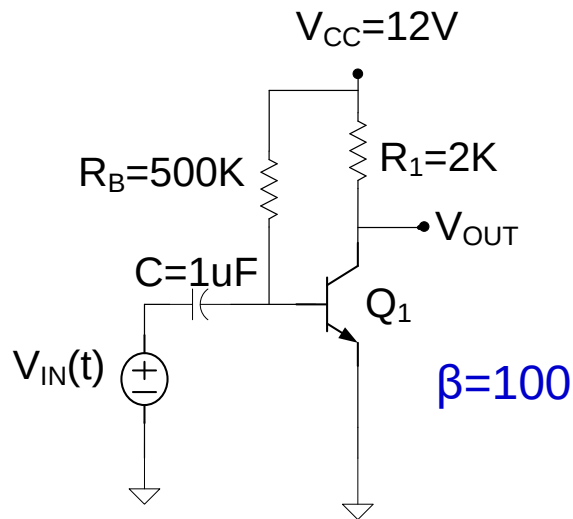

ss equivalent circuit

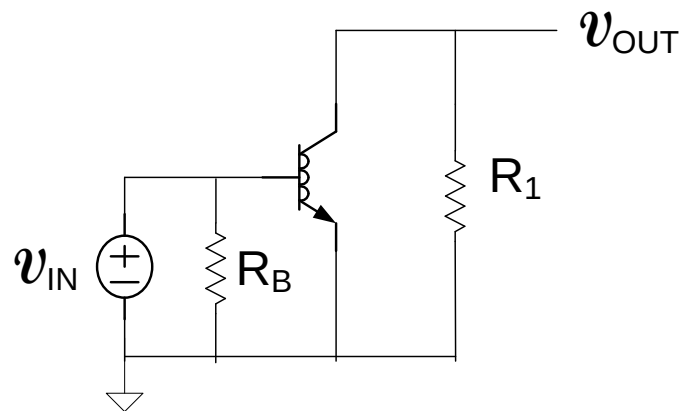

ss equivalent circuit

$$\left. \begin{aligned} v_{OUT} &= -g_m v_{BE} R_1 \\ v_{IN} &= v_{BE} \end{aligned} \right\}$$

$$A_V = -R_1 g_m$$


$$A_V \cong -\frac{I_{CQ} R_1}{V_t}$$

$$A_V \cong -\frac{2.3mA \cdot 2K}{26mV} \cong -177$$

This basic amplifier structure is widely used and repeated analysis serves no useful purpose


Have seen this circuit before but will repeat for review purposes

Amplifier Characterization (an example)

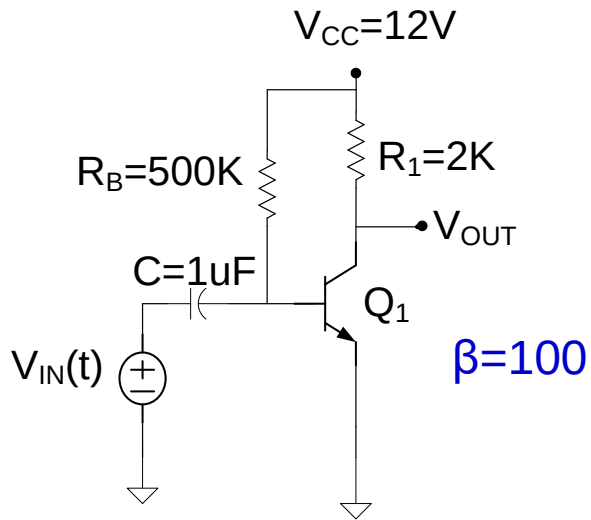




Determine V_{OUTQ} , A_V , R_{IN} ✓

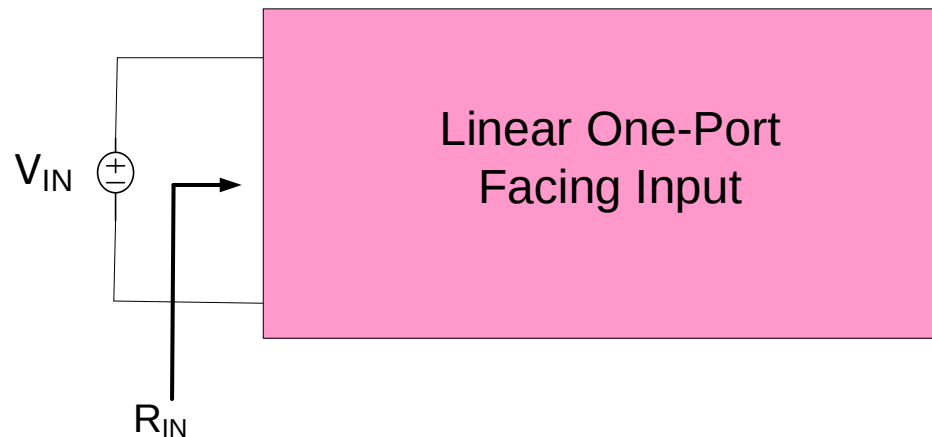- Here R_{IN} is defined to be the impedance facing V_{IN}
- Here any load is assumed to be absorbed into the one-port
- Later will consider how load is connected in defining R_{IN}



Amplifier Characterization (an example)

Determine R_{IN}

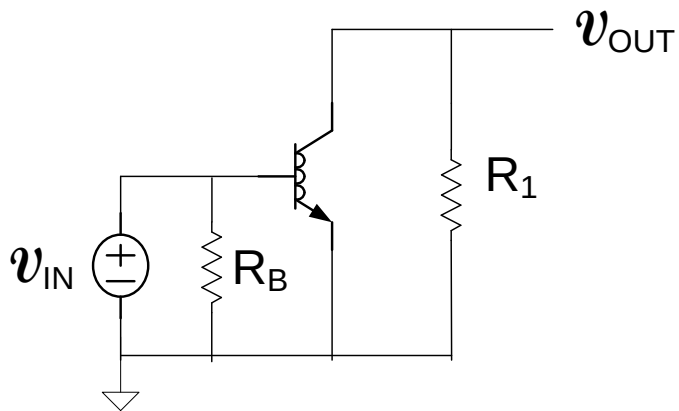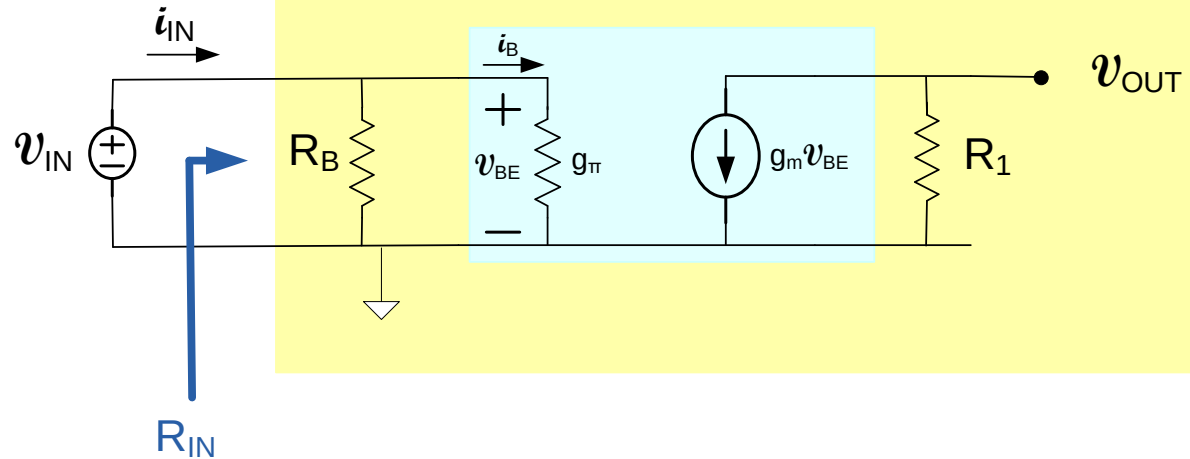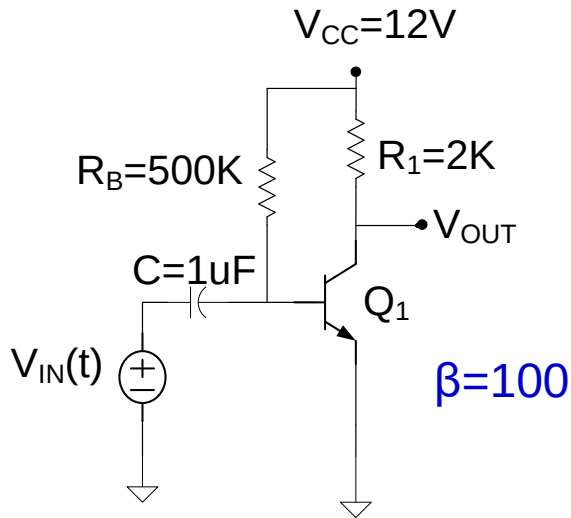

ss equivalent circuit

$$R_{in} = \frac{v_{IN}}{i_{IN}}$$

$$R_{in} = R_B // r_{\pi}$$


Usually $R_B \gg r_{\pi}$

$$R_{in} = R_B // r_{\pi} \cong r_{\pi}$$

$$R_{in} \cong r_{\pi} = \frac{I_{CQ}}{\beta V_t}$$

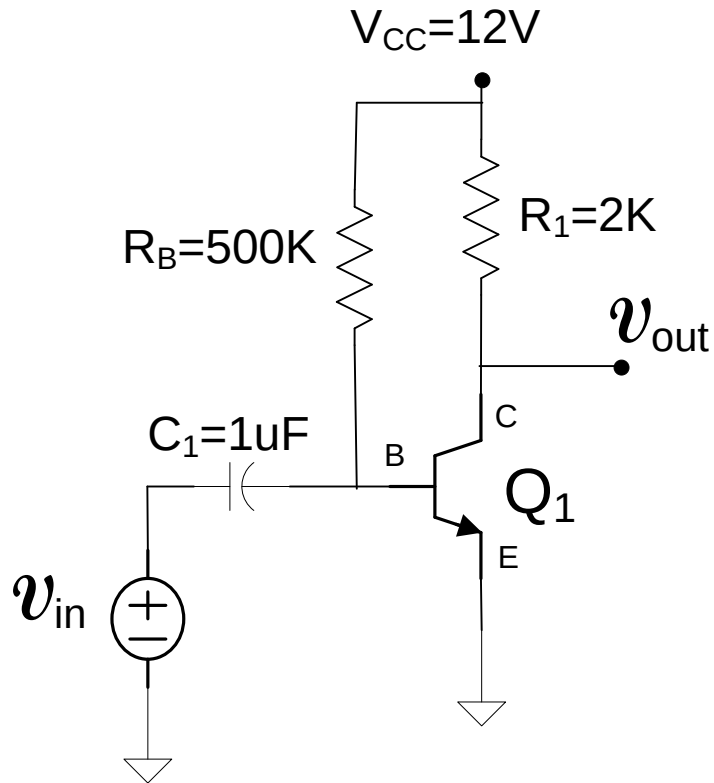Examples

Determine v_{OUT} and $V_{OUT}(t)$ if $v_{IN} = .002\sin(400t)$



$$v_{OUT} = A_V v_{IN}$$

$$v_{OUT} = -177 \cdot .002 \sin(400t) = -0.354 \sin(400t)$$

$$V_{OUT}(t) \cong V_{OUTQ} + A_V v_{IN}$$




$$V_{OUT} \cong 7.4V - 0.35 \cdot \sin(400t)$$

Amplifier Biasing (a precursor)

Amplifier Characterization

- Amplifier parameters
- ✓• Two-port amplifier models
- Dependent Sources


Two-Port Representation of Amplifiers

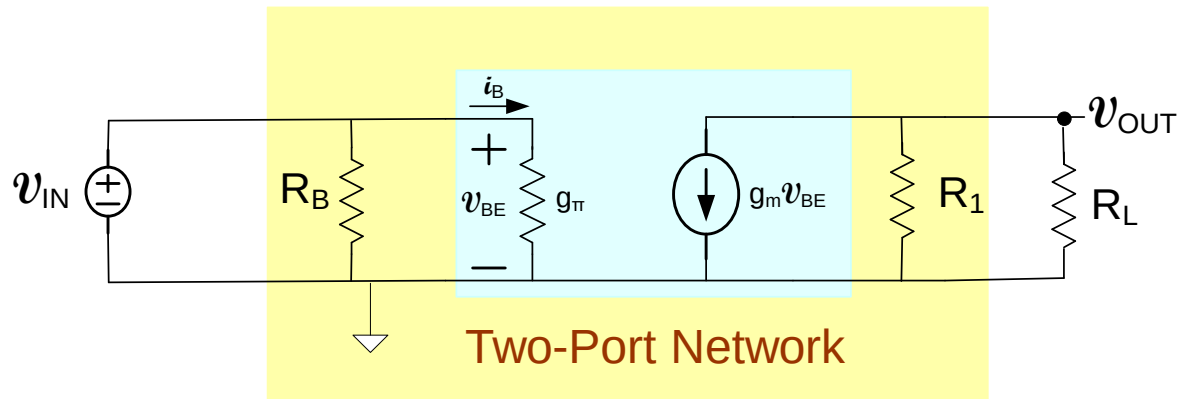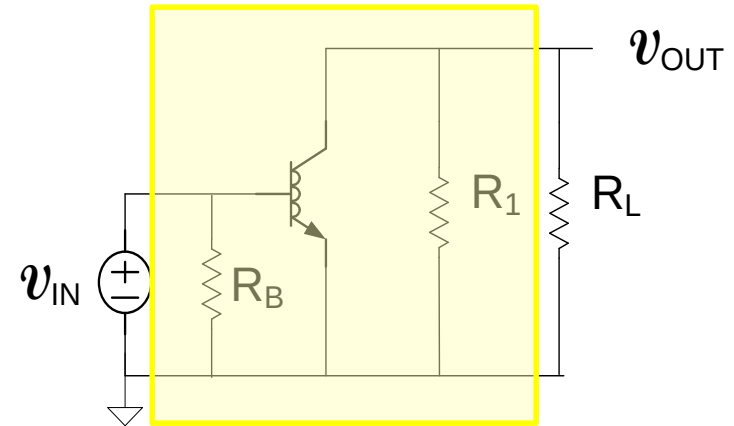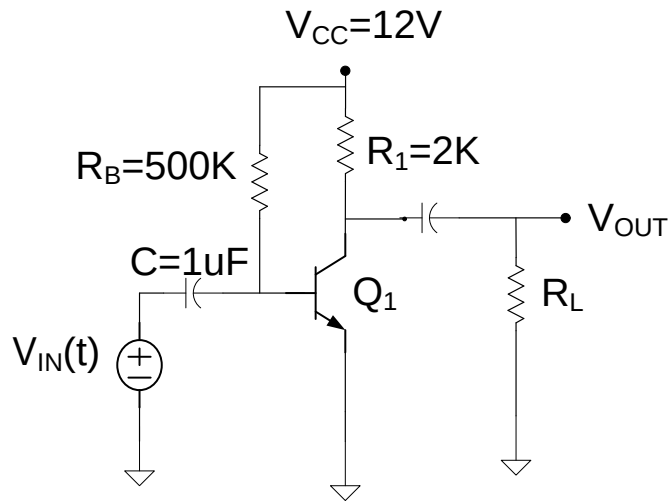

- Two-port model representation of amplifiers useful for insight into operation and analysis
- Internal components to the two-port can be quite complicated but equivalent two-port model is quite simple

Two-port representation of amplifiers

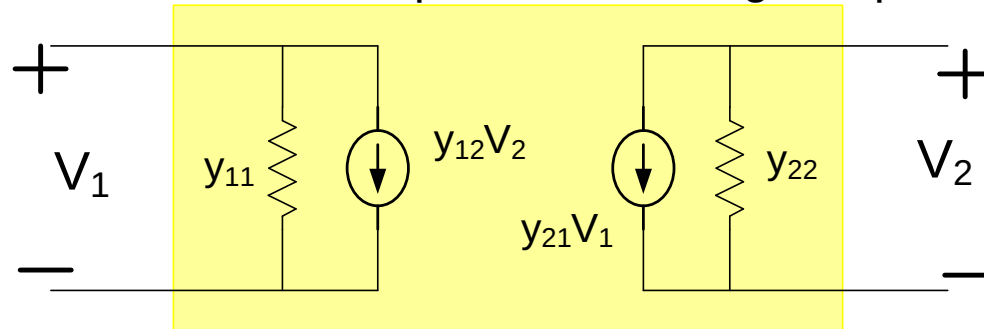
Amplifiers can be modeled as a two-port for small-signal operation



In terms of y-parameters


Other parameter sets could be used

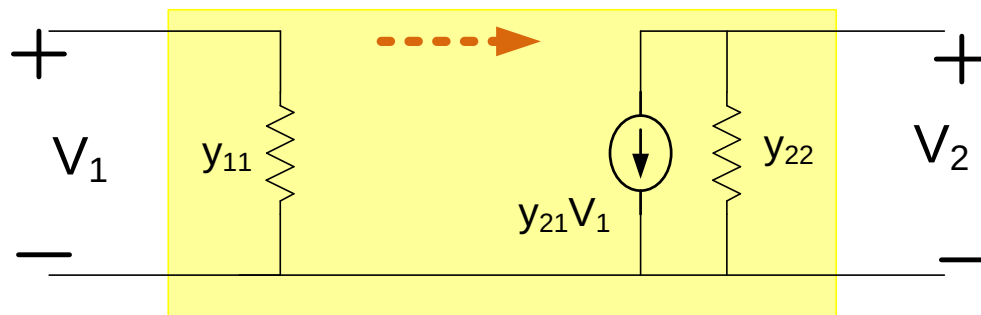- Amplifier often **unilateral** (signal propagates in only one direction: wlog $y_{12}=0$)
- One terminal is often common




Two-port representation of amplifiers

Unilateral amplifiers:

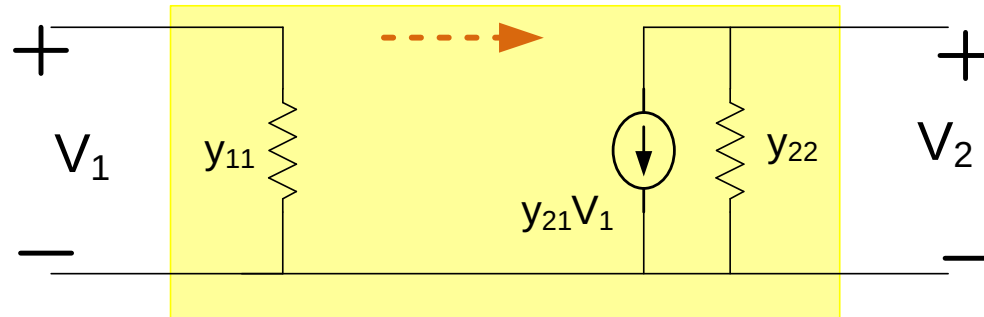

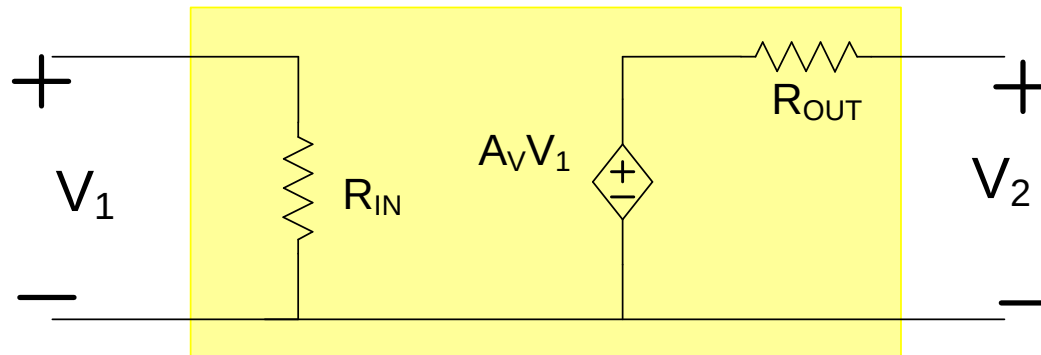- Thevenin equivalent output port often more standard
- R_{IN} , A_V , and R_{OUT} often used to characterize the two-port of amplifiers



Unilateral amplifier in terms of “amplifier” parameters

$$R_{IN} = \frac{1}{y_{11}}$$



$$A_V = -\frac{y_{21}}{y_{22}}$$

$$R_{OUT} = \frac{1}{y_{22}}$$

Amplifier input impedance, output impedance and gain are usually of interest

Why?

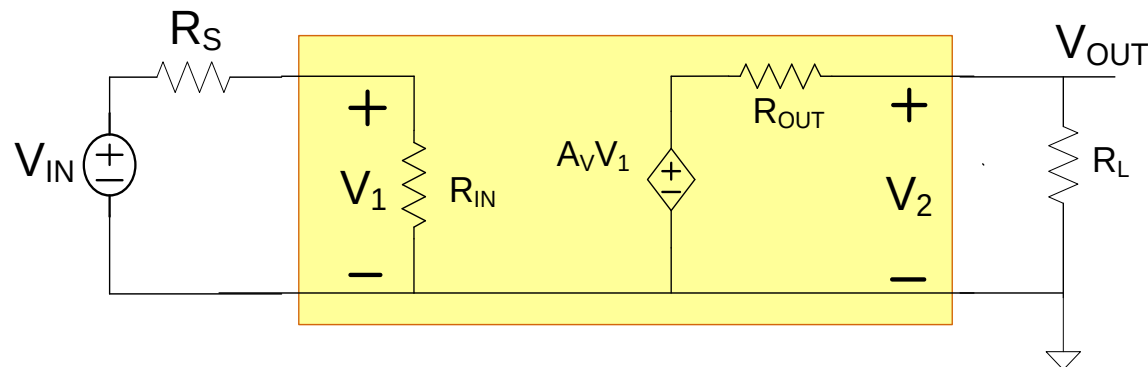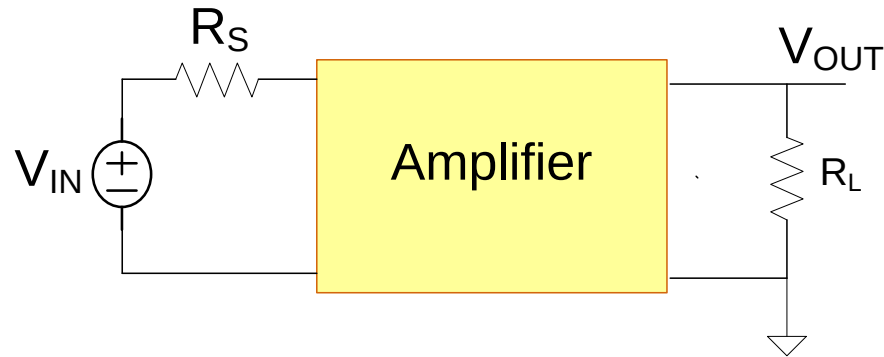Example 1: Assume amplifier is unilateral



$$V_{OUT} = \left(\frac{R_L}{R_L + R_{OUT}} \right) A_V \left(\frac{R_{IN}}{R_S + R_{IN}} \right) V_{IN}$$



$$A_{VAMP} = \frac{V_{OUT}}{V_{IN}} = \left(\frac{R_L}{R_L + R_{OUT}} \right) \left(\frac{R_{IN}}{R_S + R_{IN}} \right) A_V$$

- Can get gain without reconsidering details about components internal to the Amplifier !!!
- Analysis more involved when not unilateral

Amplifier input impedance, output impedance and gain are usually of interest

Why?

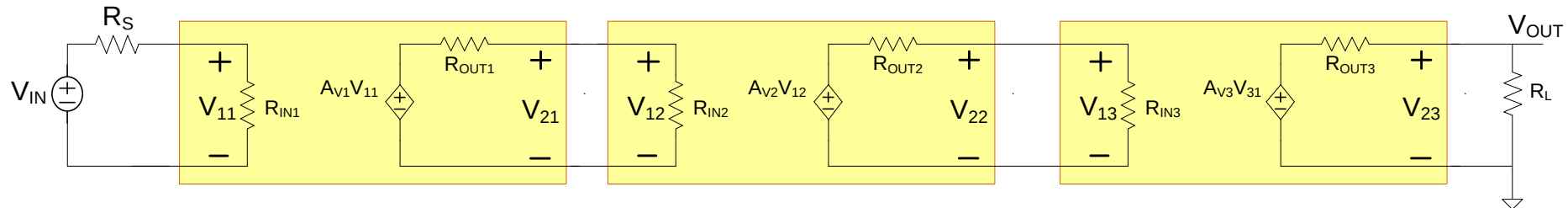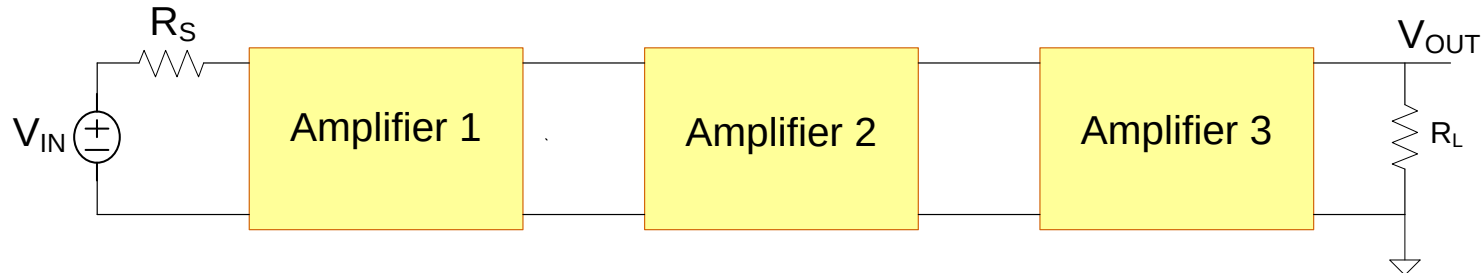Example 2: Assume amplifiers are unilateral




$$V_{OUT} = \left(\frac{R_L}{R_L + R_{OUT3}} \right) A_{V3} \left(\frac{R_{IN3}}{R_{OUT2} + R_{IN3}} \right) A_{V2} \left(\frac{R_{IN2}}{R_{OUT1} + R_{IN2}} \right) A_{V1} \left(\frac{R_{IN1}}{R_S + R_{IN1}} \right) V_{IN}$$

$$A_{VAMP} = \frac{V_{OUT}}{V_{IN}} = \left(\frac{R_L}{R_L + R_{OUT3}} \right) A_{V3} \left(\frac{R_{IN3}}{R_{OUT2} + R_{IN3}} \right) A_{V2} \left(\frac{R_{IN2}}{R_{OUT1} + R_{IN2}} \right) A_{V1} \left(\frac{R_{IN1}}{R_S + R_{IN1}} \right)$$


- Can get gain without reconsidering details about components internal to the Amplifier !!!
- Analysis more involved when not unilateral

Two-port representation of amplifiers

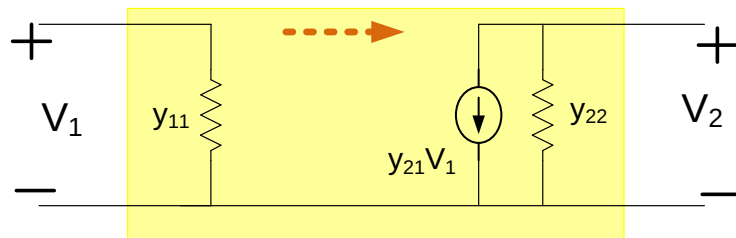- Amplifier usually **unilateral** (signal propagates in only one direction: wlog $y_{12}=0$)
- One terminal is often common
- “Amplifier” parameters often used




y parameters

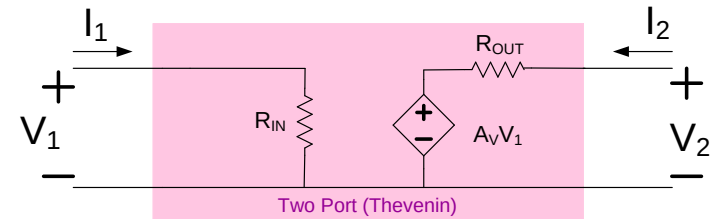


Amplifier parameters

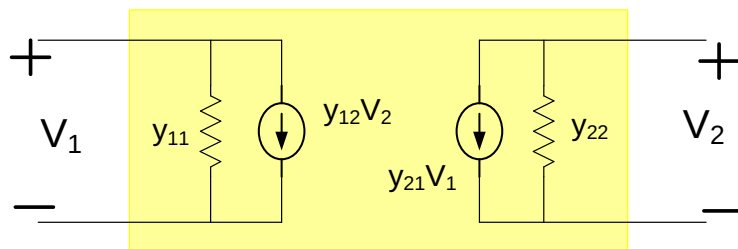-
- Amplifier parameters can also be used if not **unilateral**
 - One terminal is often common




y parameters

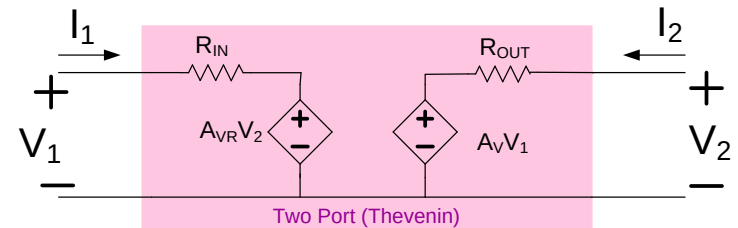

Amplifier parameters

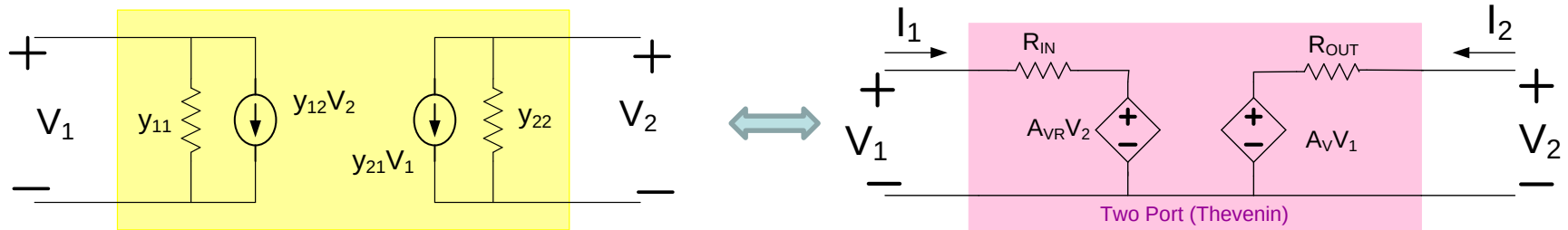Determination of small-signal model parameters:




In the past, we have determined small-signal model parameters of electronic devices from the nonlinear port characteristics

$$\left. \begin{aligned} I_1 &= \mathbf{f}_1(\mathbf{V}_1, \mathbf{V}_2) \\ I_2 &= \mathbf{f}_2(\mathbf{V}_1, \mathbf{V}_2) \end{aligned} \right\} \quad \mathbf{y}_{ij} = \left. \frac{\partial \mathbf{f}_i(\mathbf{V}_1, \mathbf{V}_2)}{\partial \mathbf{V}_j} \right|_{\bar{\mathbf{V}} = \bar{\mathbf{V}}_Q}$$

- Will now determine small-signal model parameters for two-port comprised of linear networks (instead of just electronic devices)
- Could go back to the nonlinear models and analyze as we did for electronic devices
- Will follow a different approach (results are identical) that is often much easier

Two-Port Equivalents of Interconnected Two-ports



Example:

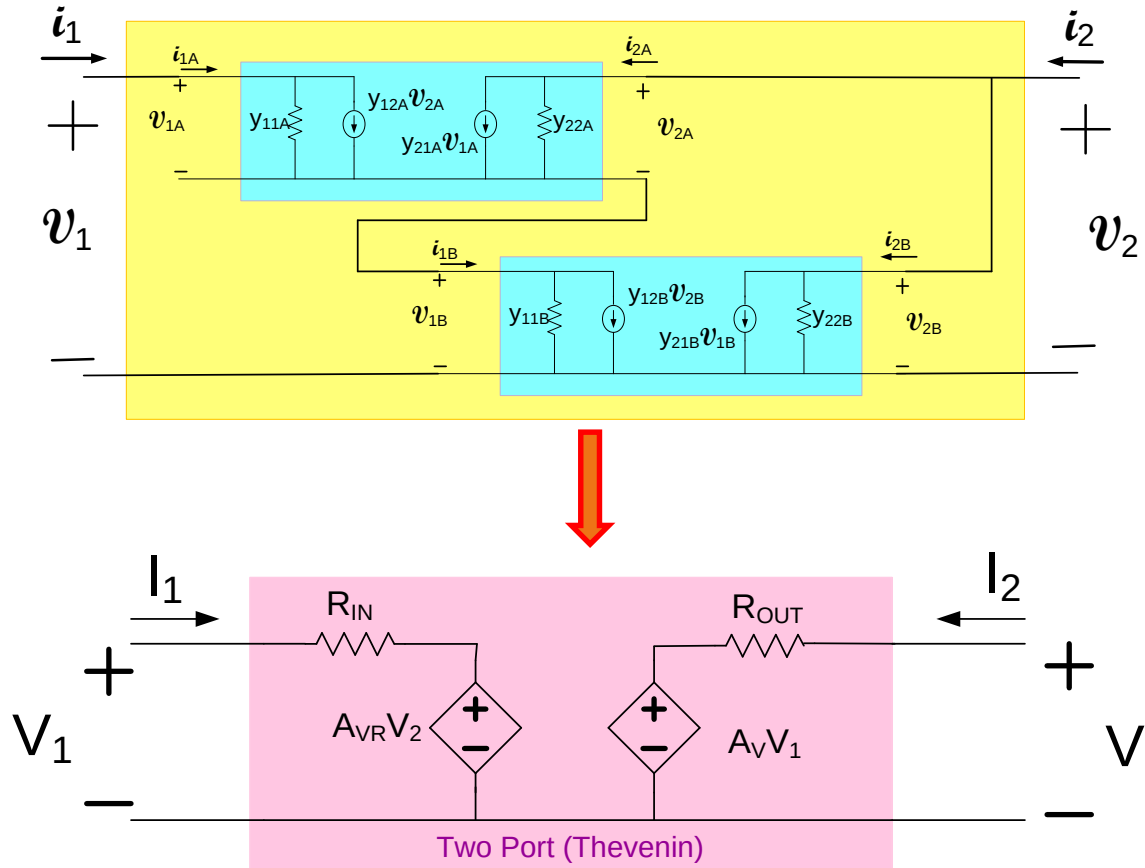


- could obtain two-port in any form
- often obtain equivalent circuit w/o identifying independent variables
- Unilateral iff $A_{VR}=0$
- Thevenin-Norton transformations can be made on either or both ports

Two-Port Equivalents of Interconnected Two-ports

Example:

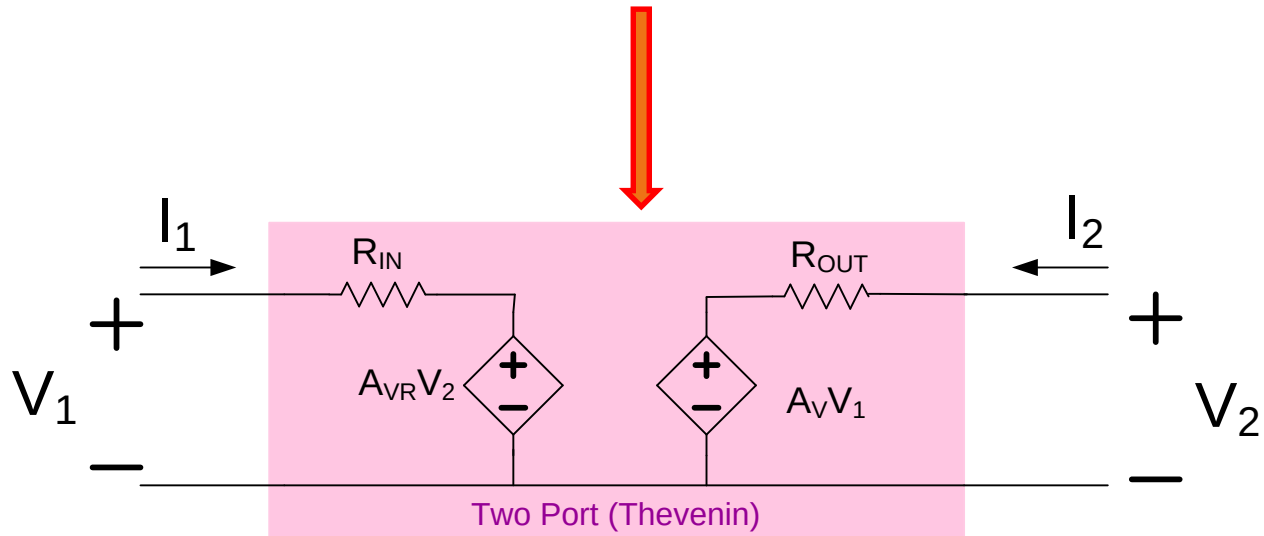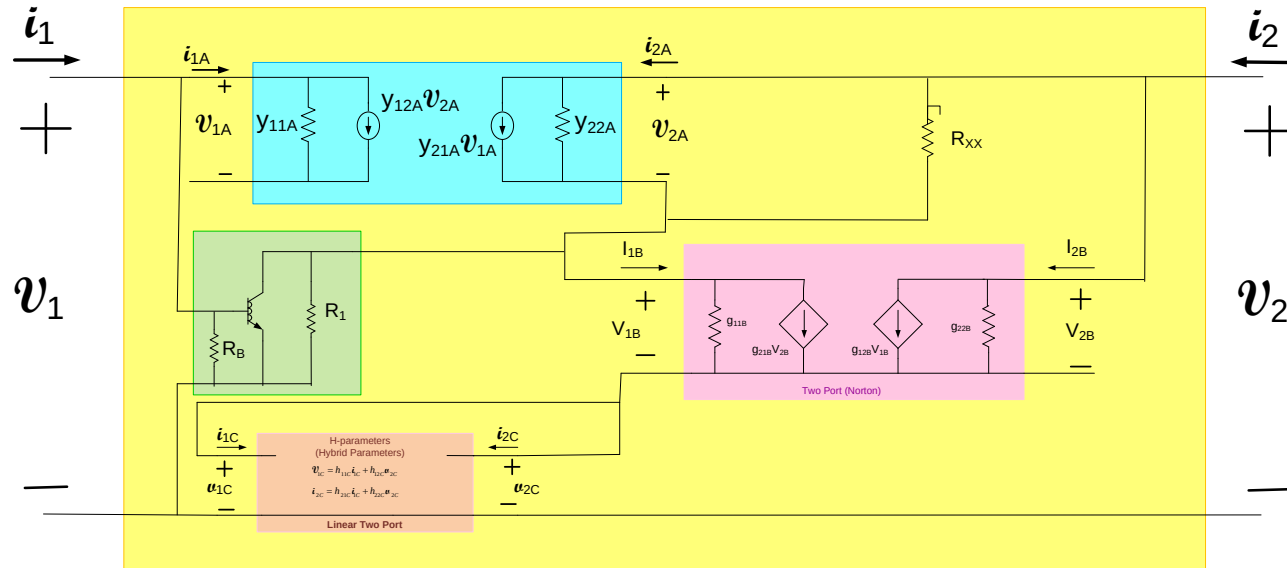

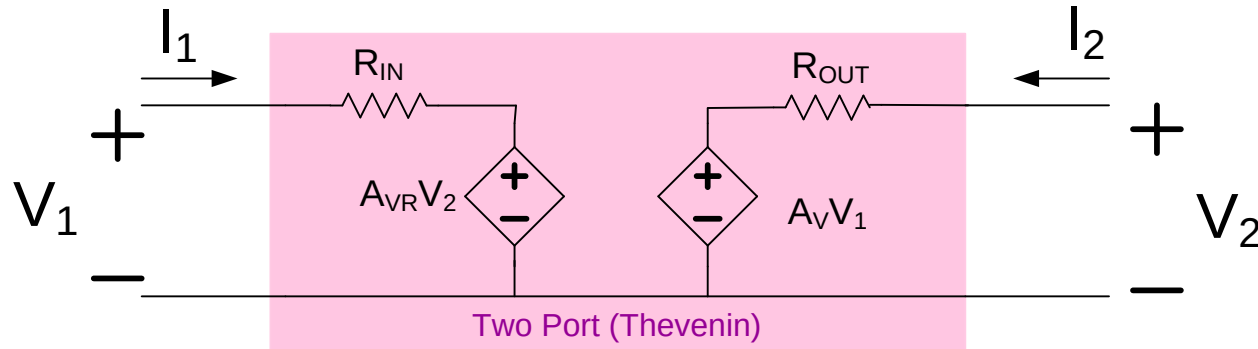Two-Port Equivalents of Interconnected Two-ports



$$v_1 = i_1 R_{in} + A_{VR} v_2$$

$$v_2 = i_2 R_0 + A_{V0} v_1$$

Or equivalently



$$i_1 = v_1 \left(\frac{1}{R_{in}} \right) + v_2 \left(\frac{-A_{VR}}{R_{in}} \right)$$

$$i_2 = v_1 \left(\frac{-A_{V0}}{R_0} \right) + v_2 \left(\frac{1}{R_0} \right)$$

Determination of two-port model parameters

(One method will be discussed here)

A method of obtaining R_{in}

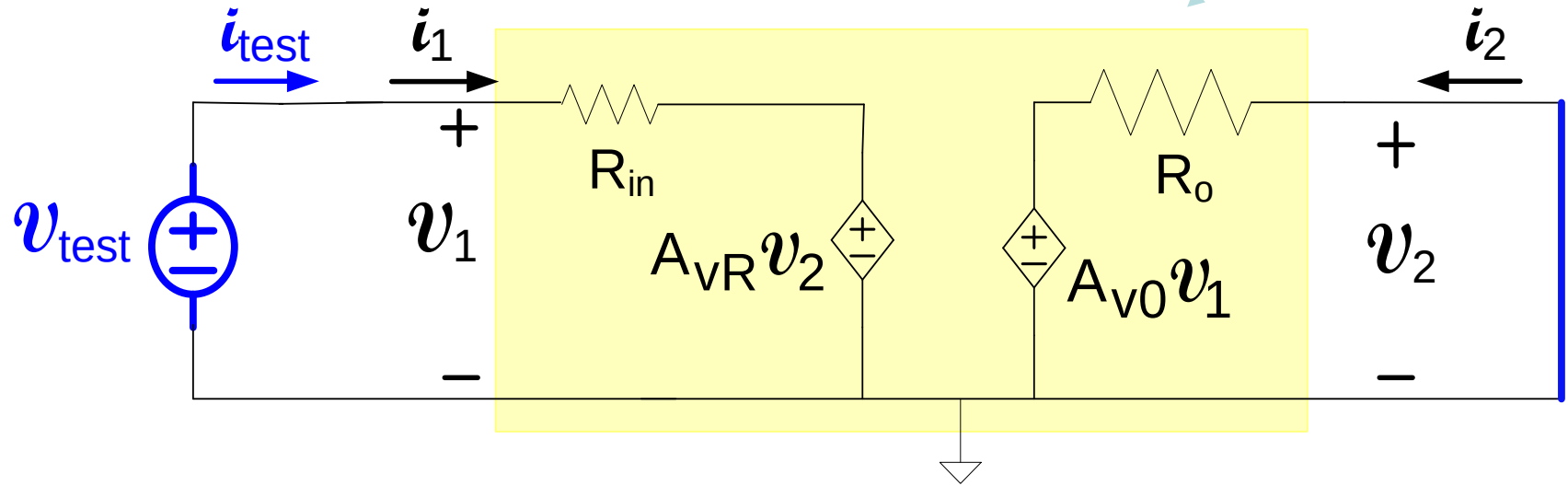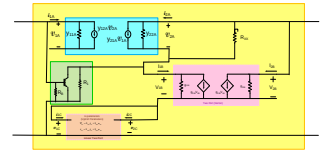

Terminate the output in a short-circuit



$$\left. \begin{aligned} i_1 &= v_1 \left(\frac{1}{R_{in}} \right) + v_2 \left(\frac{-A_{VR}}{R_{in}} \right) \\ i_2 &= v_1 \left(\frac{-A_{V0}}{R_0} \right) + v_2 \left(\frac{1}{R_0} \right) \end{aligned} \right\}$$

$$\begin{aligned} v_2 &= 0 \\ v_1 &= v_{test} \\ i_1 &= i_{test} \end{aligned}$$

$$R_{in} = \frac{v_{test}}{i_{test}}$$

Determination of two-port model parameters


A method of obtaining A_{V0}

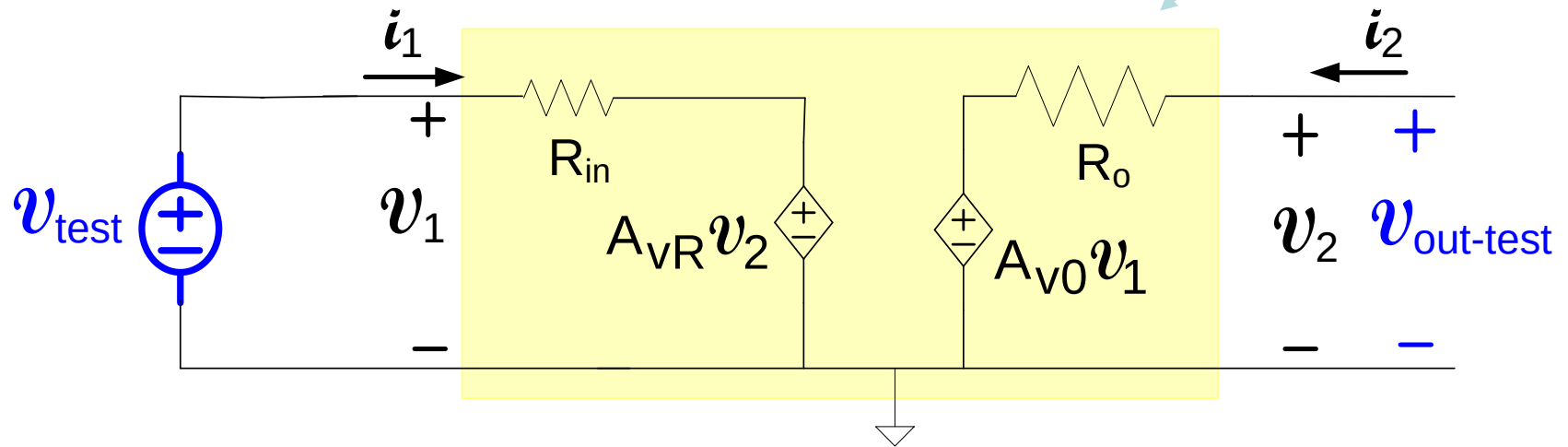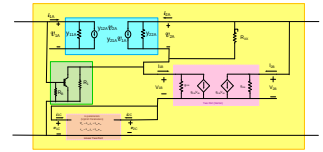


Terminate the output in an open-circuit

$$\left. \begin{aligned} i_1 &= v_1 \left(\frac{1}{R_{in}} \right) + v_2 \left(\frac{-A_{VR}}{R_{in}} \right) \\ i_2 &= v_1 \left(\frac{-A_{V0}}{R_o} \right) + v_2 \left(\frac{1}{R_o} \right) \end{aligned} \right\} \xrightarrow{i_2 = 0} \begin{aligned} v_1 &= v_{test} \\ v_2 &= v_{out-test} \end{aligned} \quad A_{V0} = \frac{v_{out-test}}{v_{test}}$$

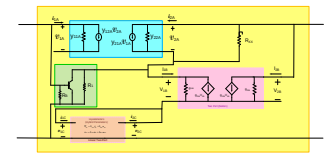Determination of two-port model parameters



A method of obtaining R_0

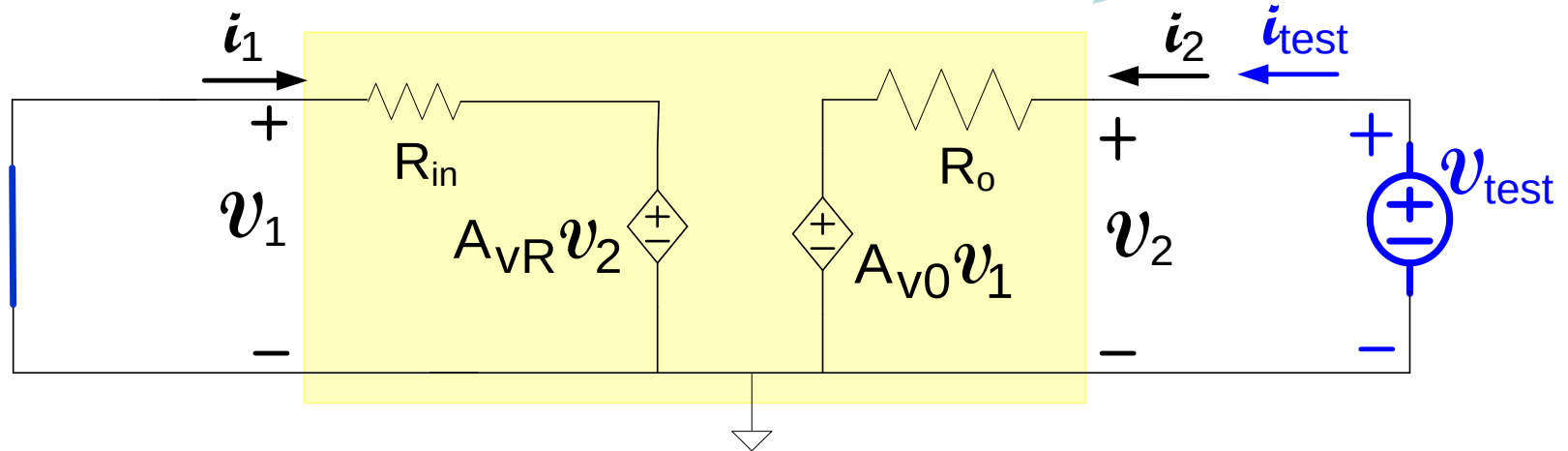


Terminate the input in a short-circuit

$$\left. \begin{aligned} i_1 &= v_1 \left(\frac{1}{R_{in}} \right) + v_2 \left(\frac{-A_{VR}}{R_{in}} \right) \\ i_2 &= v_1 \left(\frac{-A_{V0}}{R_0} \right) + v_2 \left(\frac{1}{R_0} \right) \end{aligned} \right\} \xrightarrow{v_1 = 0} R_0 = \frac{v_{test}}{i_{test}}$$

Determination of two-port model parameters

A method of obtaining A_{VR}

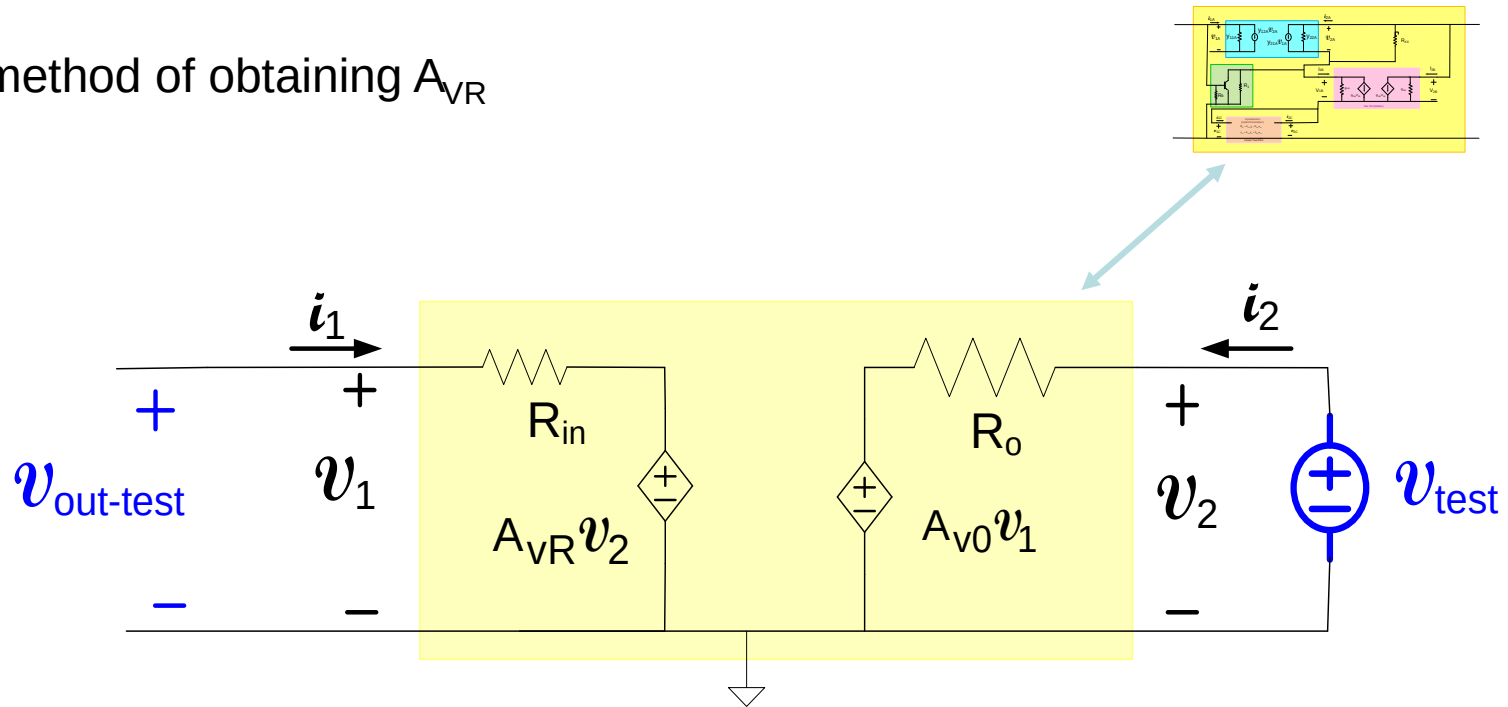

Terminate the input in an open-circuit


$$\left. \begin{aligned} i_1 &= v_1 \left(\frac{1}{R_{in}} \right) - v_2 \left(\frac{A_{VR}}{R_{in}} \right) \\ i_2 &= v_1 \left(\frac{-A_{V0}}{R_0} \right) + v_2 \left(\frac{1}{R_0} \right) \end{aligned} \right\} \xrightarrow{i_1 = 0} A_{VR} = \frac{v_{out-test}}{v_{test}}$$

Determination of Amplifier Two-Port Parameters

- Input and output parameters are obtained in exactly the same way, only distinction is in the notation used for the ports.
- Methods given for obtaining amplifier parameters R_{in} , R_{OUT} and A_v for unilateral networks are a special case of the non-unilateral analysis by observing that $A_{vR}=0$.
- In some cases, other methods for obtaining the amplifier parameters are easier than what was just discussed

Examples




Biasing
Circuit

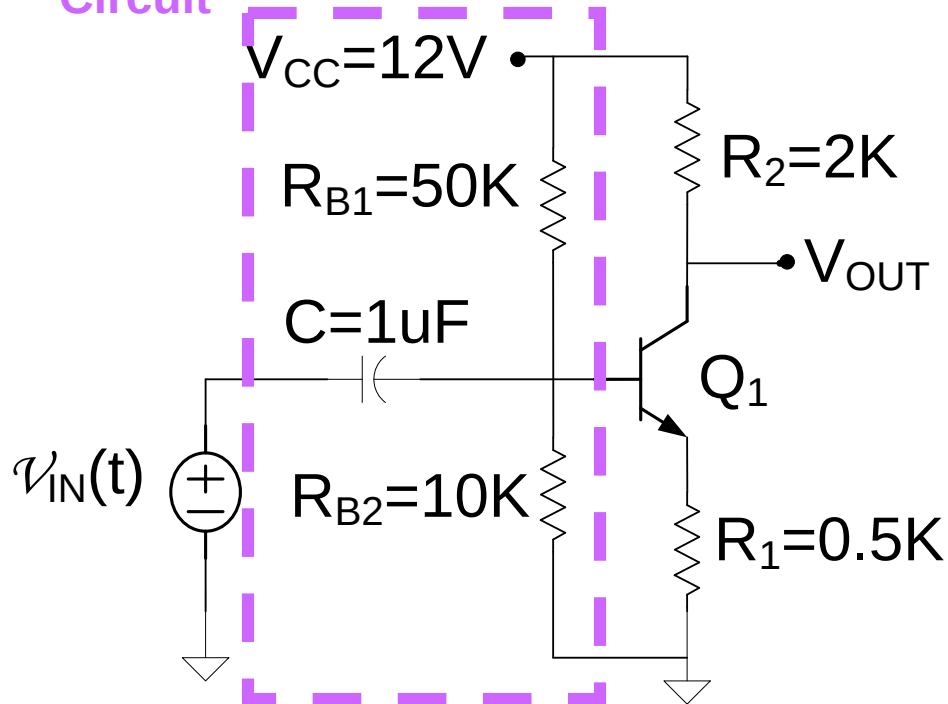

Determine V_{OUTQ} and the SS voltage gain (A_V), assume $\beta=100$

(A_V is one of the small-signal model parameters for this circuit)



Examples

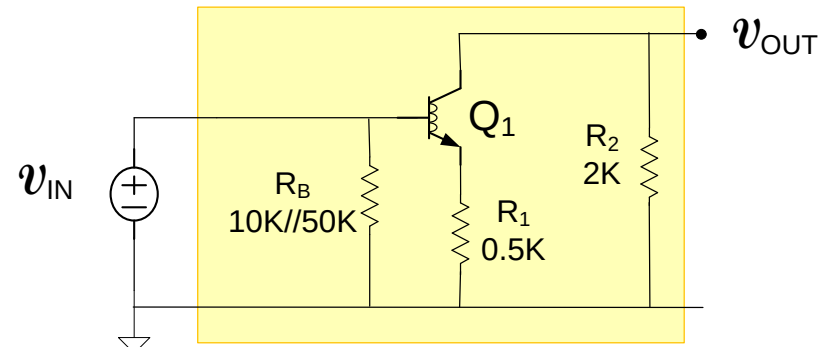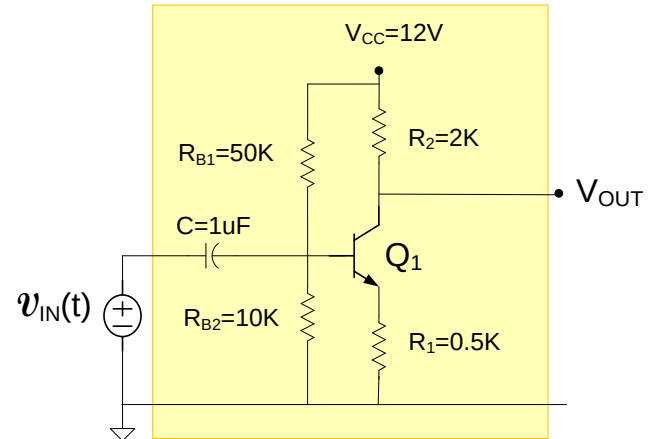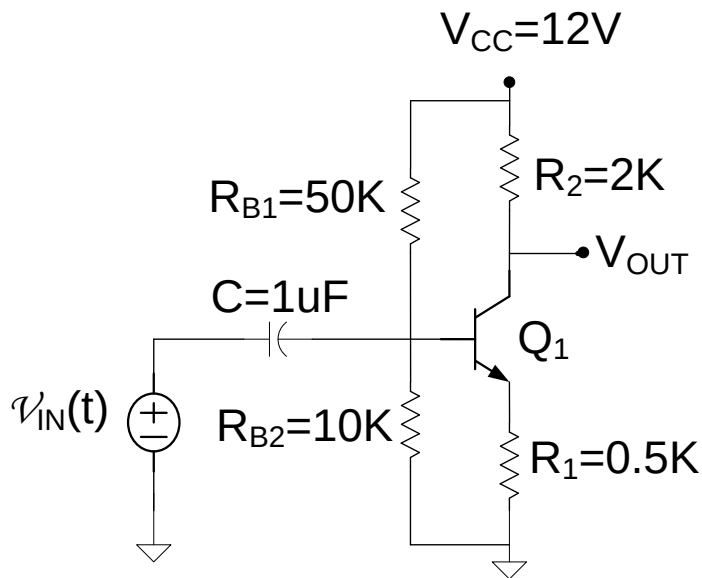

Determine V_{OUTQ} and the SS voltage gain (A_v), assume $\beta=100$


(A_v is one of the small-signal model parameters for this circuit)

Examples

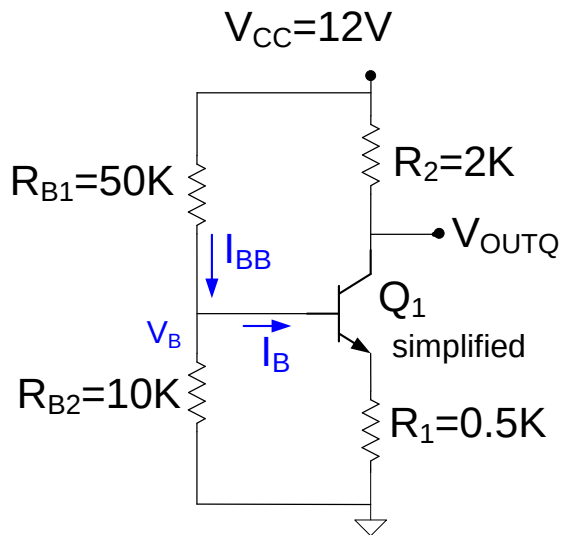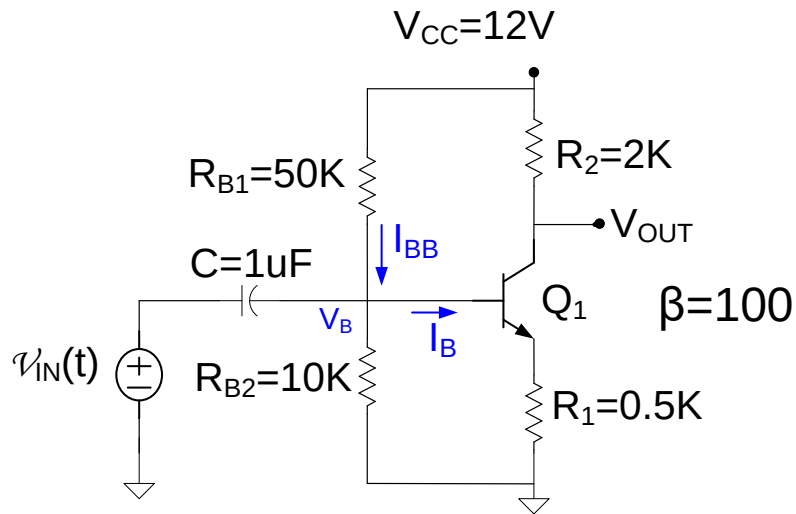

dc equivalent circuit

Determine V_{OUTQ}

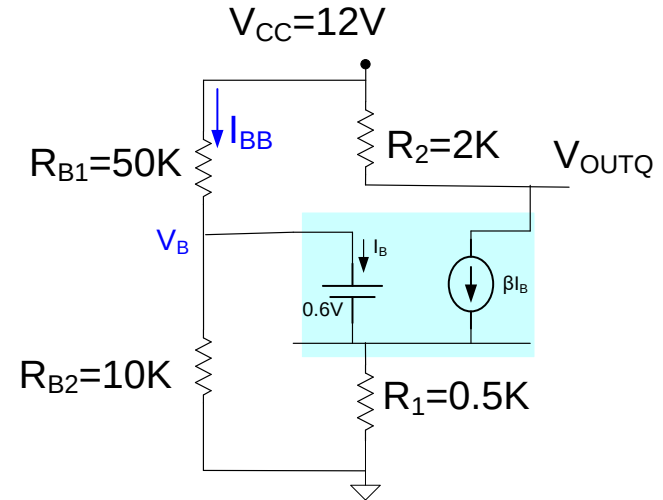

dc equivalent circuit

This circuit is most practical when $I_B \ll I_{BB}$

With this assumption,


$$V_B = \left(\frac{R_{B2}}{R_{B1} + R_{B2}} \right) 12V$$

$$I_{CQ} = I_{EQ} = \left(\frac{V_B - 0.6V}{R_1} \right) = \frac{1.4V}{.5K} = 2.8mA$$

$$V_{OUTQ} = 12V - I_{CQ} R_1 = 6.4V$$

Note: This Q-point is nearly independent of the characteristics of the nonlinear BJT !

Examples


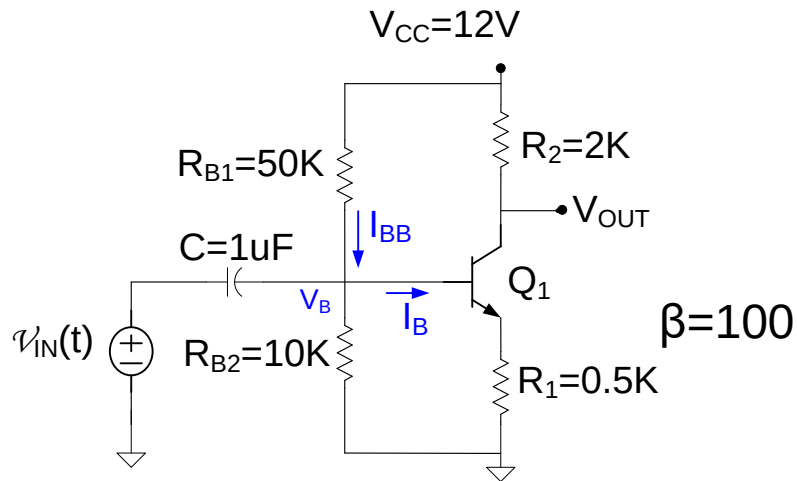


This voltage gain is nearly independent of the characteristics of the nonlinear BJT !

This is a fundamentally different amplifier structure

It can be shown that this is slightly non-unilateral

Determine SS voltage gain

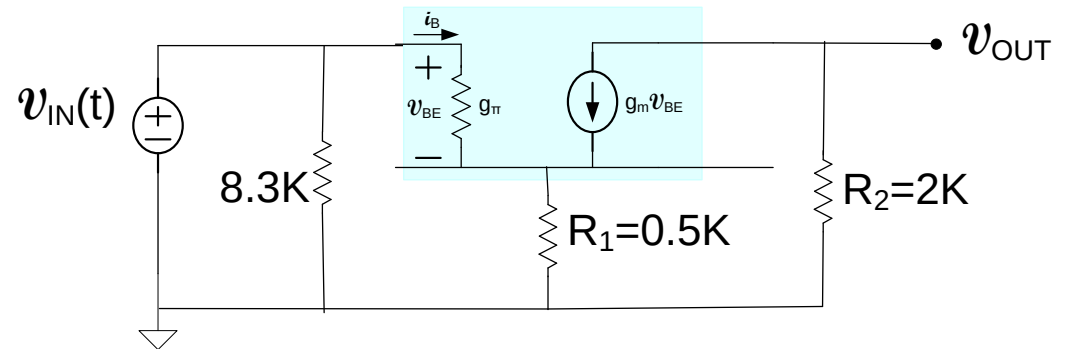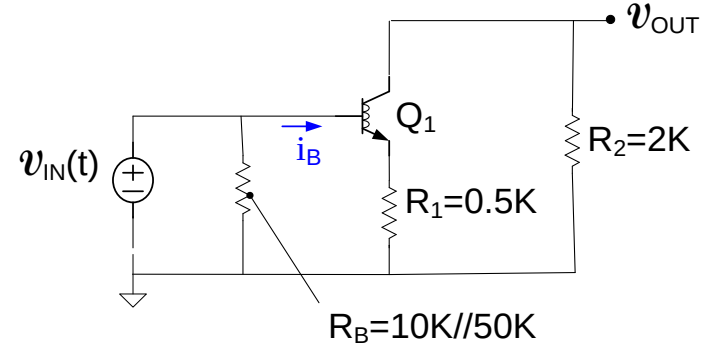

$$v_{OUT} = -g_m v_{BE} R_2$$

$$v_{IN} = v_{BE} + R_1 (v_{BE} [g_{\pi} + g_m])$$

$$A_V = \frac{-R_2 g_m v_{BE}}{v_{BE} + R_1 (v_{BE} [g_{\pi} + g_m])} = \frac{-R_2 g_m}{1 + R_1 ([g_{\pi} + g_m])}$$

$$A_V \cong \frac{-R_2 g_m}{R_1 g_m} = \frac{-R_2}{R_1} = -4$$

End of Lecture 29