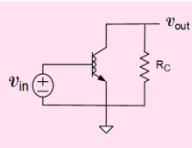
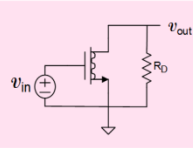
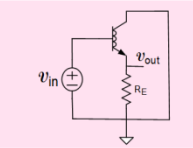
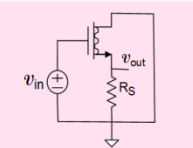
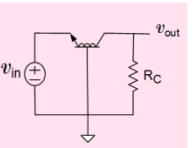
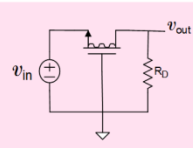
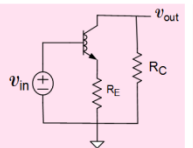
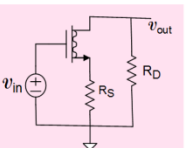


EE 330

Lecture 33

- High Gain Amplifiers
- Current Source Biasing
- Current Sources and Mirrors

Basic Amplifier Gain Table


	CE/CS		CC/CD		CB/CG		CEwRE/CSwRS	
	BJT	MOS	BJT	MOS	BJT	MOS	BJT	MOS
A_V	 $-g_m R_C$ $-\frac{I_{CQ} R_C}{V_t}$	 $-\frac{2I_{DQ} R_D}{V_{EB}}$	 $\frac{g_m}{g_m + g_E}$ $\frac{I_{CQ} R_E}{I_{CQ} R_E + V_t}$	 $\frac{2I_{DQ} R_E}{2I_{DQ} R_E + V_{EB}}$	 $g_m R_C$ $\frac{I_{CQ} R_C}{V_t}$	 $\frac{2I_{DQ} R_C}{V_{EB}}$	 $-\frac{R_C}{R_E}$	
R_{in}	r_{π} $\frac{\beta V_t}{I_{CQ}}$	∞	$r_{\pi} + \beta R_E$ $\beta \left(\frac{V_t}{I_{CQ}} + R_E \right)$	∞	g_m^{-1} $\frac{V_t}{I_{CQ}}$	$\frac{V_{EB}}{2I_{DQ}}$	$r_{\pi} + \beta R_E$ $\beta \left(\frac{V_t}{I_{CQ}} + R_E \right)$	∞
R_{out}	R_C		g_m^{-1} $\frac{V_t}{I_{CQ}}$	$\frac{V_{EB}}{2I_{DQ}}$	R_C		R_C	

Can use these equations only when small signal circuit is EXACTLY like that shown !!

Cascaded Amplifier Analysis and Operation


Case 2: One or more stages are not unilateral

➤ Standard two-port cascade

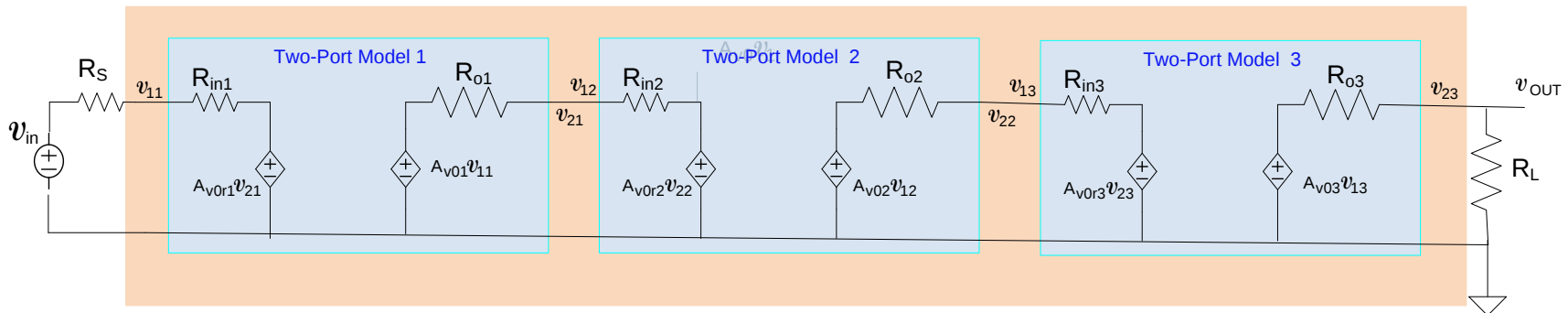




Analysis by creating new two-port of entire amplifier quite tedious because of the reverse-gain elements

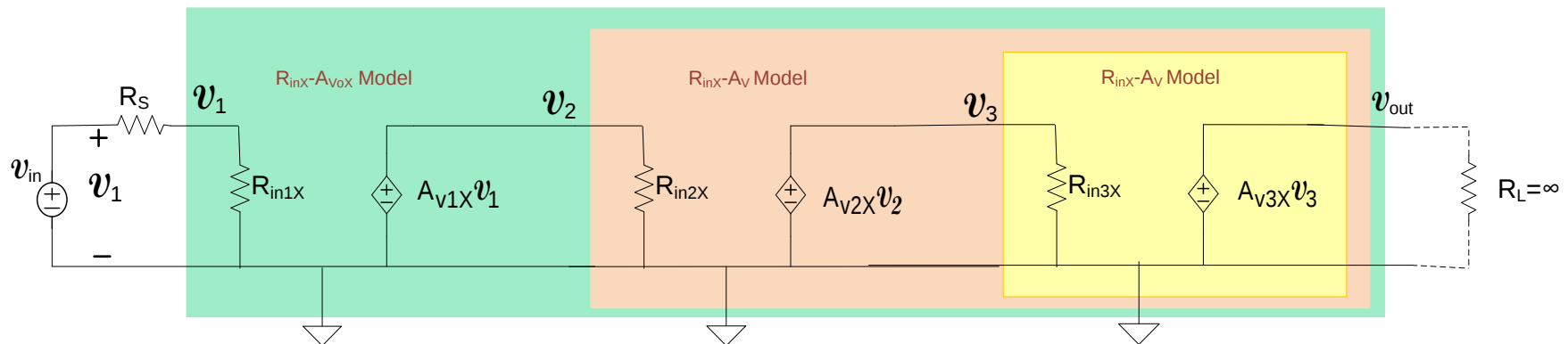➤ Right-to-left nested R_{inx}, A_{vX} approach



- R_{inx} includes effects of all loading
- AV_X is the voltage ratio from input to output of a stage
- AV_X 's include all loading
- Can not change any loading without recalculating everthing!

High-gain amplifier

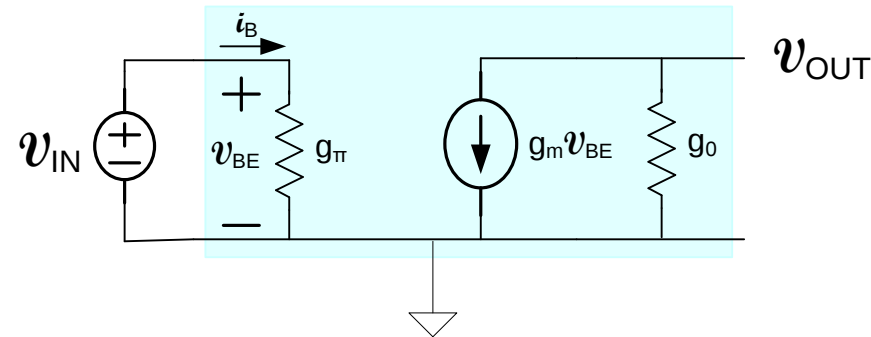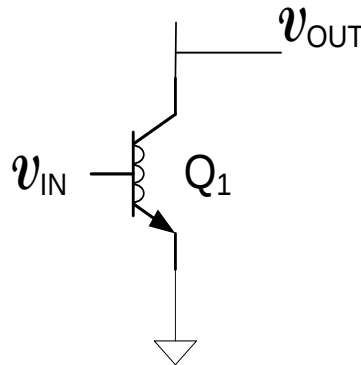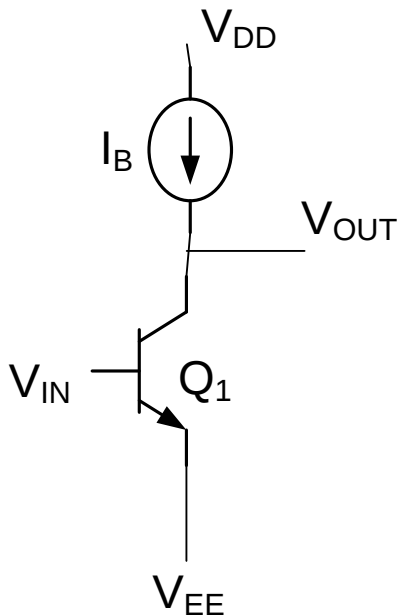

$$A_V = \frac{-g_m}{g_o}$$

$$A_V = \frac{-I_{CQ}}{V_t I_{CQ}/V_{AF}} = -\frac{V_{AF}}{V_t}$$


$$A_V = -\frac{V_{AF}}{V_t} \cong \frac{200V}{25mV} = -8000$$

This gain is very large (but realistic) !


And no design parameters affect the gain

But how can we make a current source?

High-gain amplifier

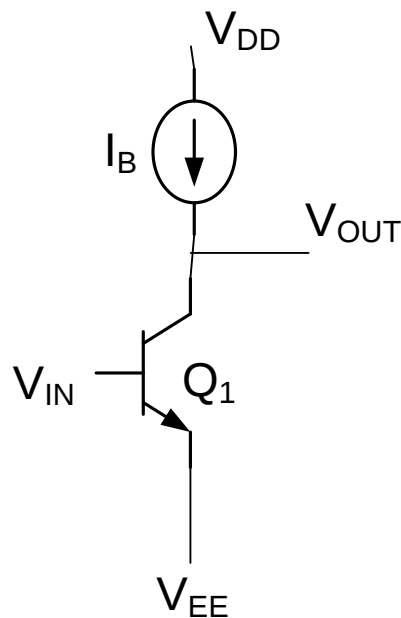

$$A_V \cong -8000$$

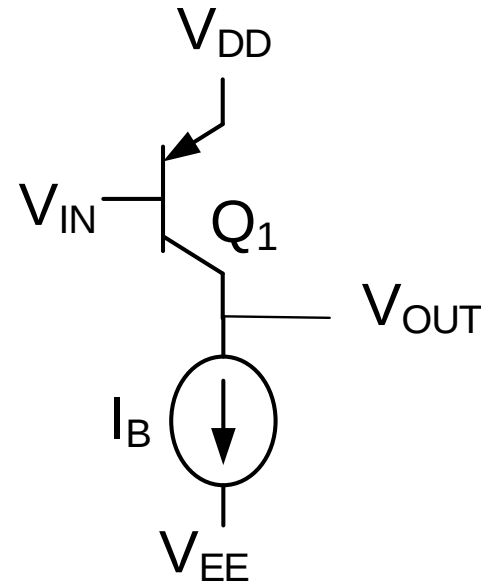



Same gain with both npn and pnp transistors

How can we build the ideal current source?

What is the small-signal model of an actual current source?

Simple Current Sources

a “sinking” current source

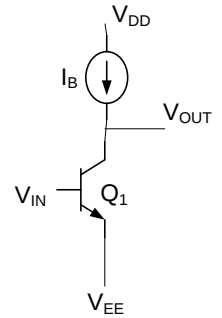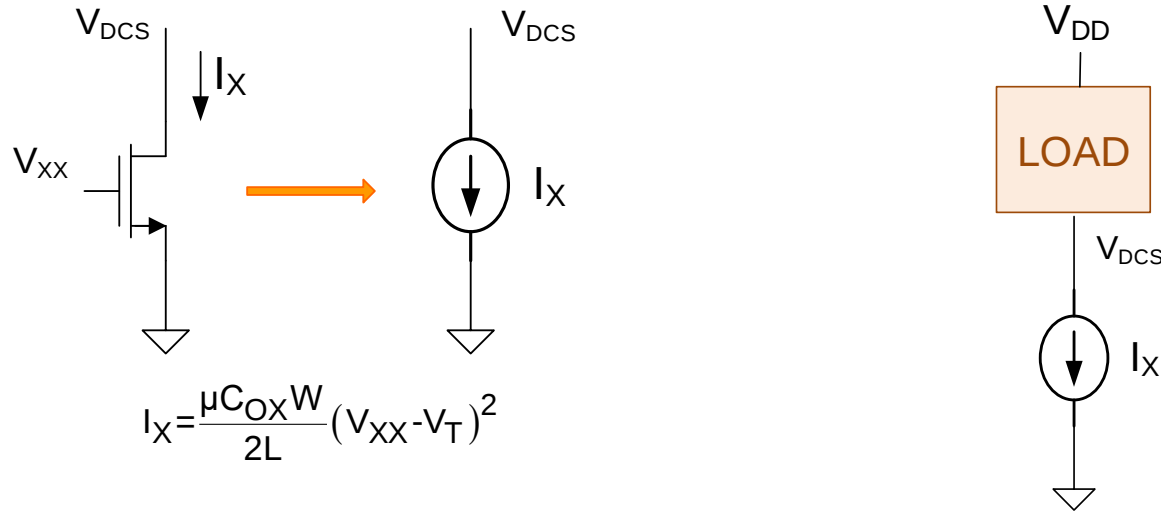

Since I_X is independent of V_{DCS} , acts as an ideal current source (with this model)

Termed a “sinking” current source since current is pulled out of the load

If V_{XX} is available, each dc current source requires only one additional transistor !



Have several methods for generating V_{XX} from V_{DD} (see HW problems)

But for the npn high-gain amplifier considered need a sourcing current

But how good is this current “sink”?

Simple Current Sources

a “sourcing” current source

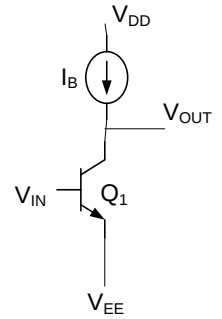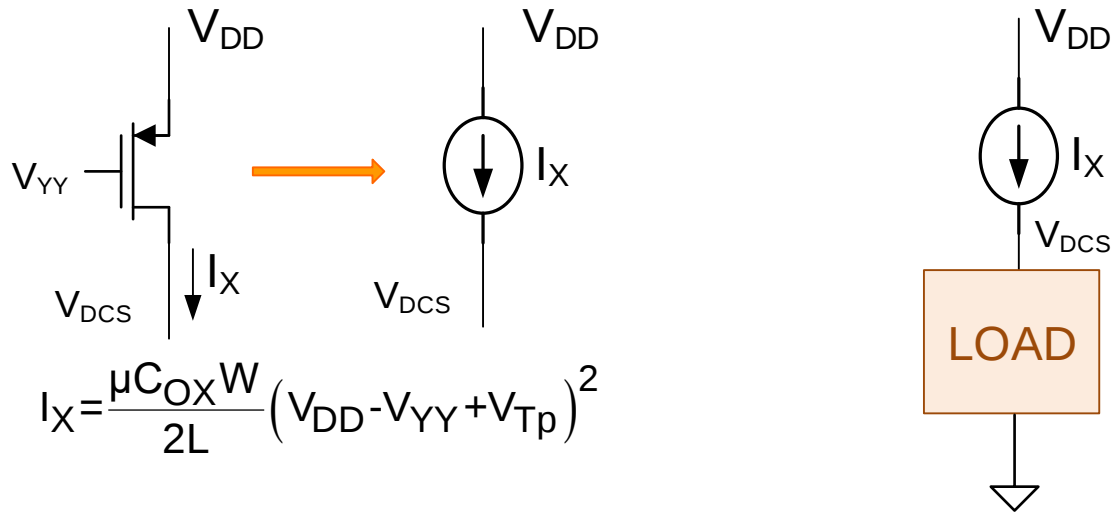

Since I_X is independent of V_{DCS} , acts as an ideal current source (with this model)

Termed a “sourcing” current source since pushed into the load



If V_{XX} is available, each dc current source requires only one additional transistor !

Have several methods for generating V_{XX} from V_{DD} (see HW problems)

But how good is this current “source”?

Simple Current Sources

a “sinking” current source

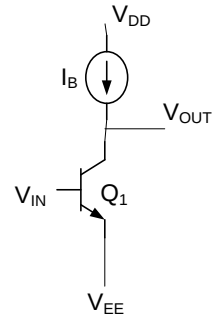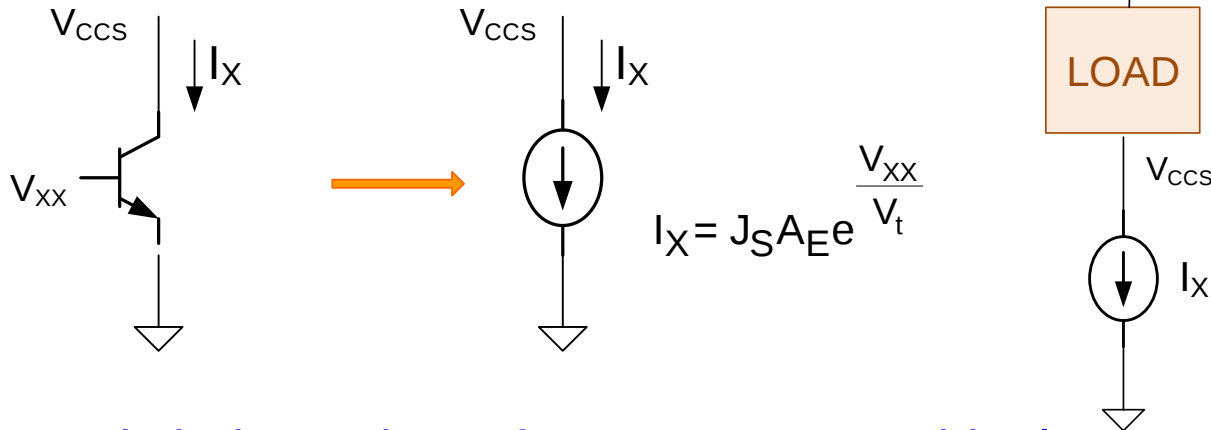

Since I_X is independent of V_{CCS} , acts as an ideal current source (with this model)

Termed a “sinking” current source since current is pulled out of the load

If V_{XX} is available, each dc current source requires only one additional transistor !



Have several methods for generating V_{XX} from V_{DD} (see HW problems)

But for the npn high-gain amplifier considered need a sourcing current

But how good is this current “sink”?

Simple Current Sources

a “sourcing” current source

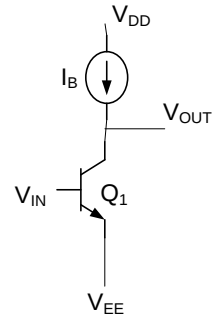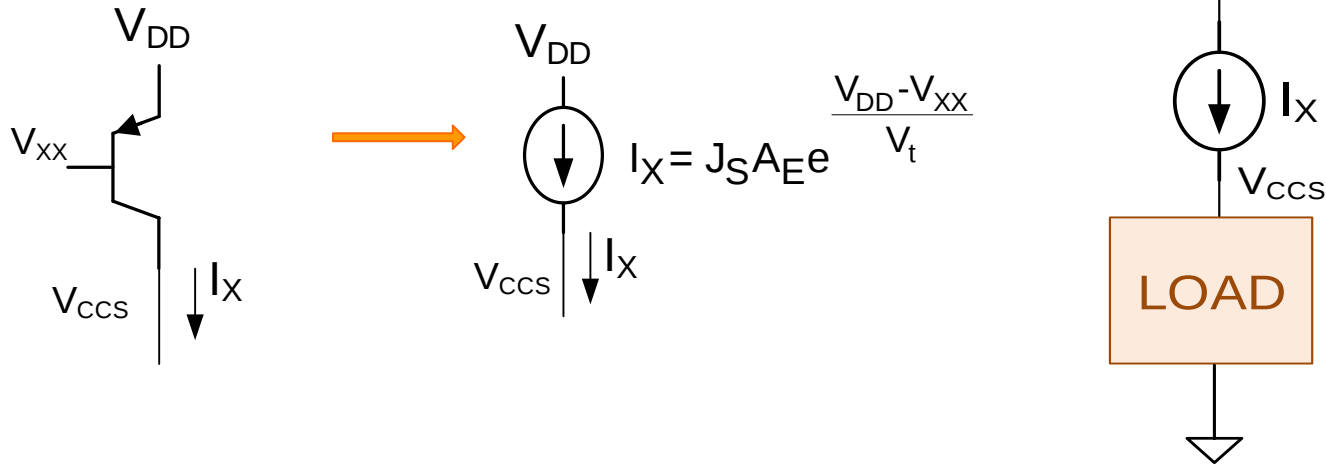

Since I_X is independent of V_{CCS} , acts as an ideal current source (with this model)

Termed a “sourcing” current source since pushed into the load


If V_{XX} is available, each dc current source requires only one additional transistor !

Have several methods for generating V_{XX} from V_{DD} (see HW problems)


But how good is this current “source”?

Before addressing the issue of how a current source is designed, will consider another circuit that uses current source biasing

The Basic Differential Amplifier


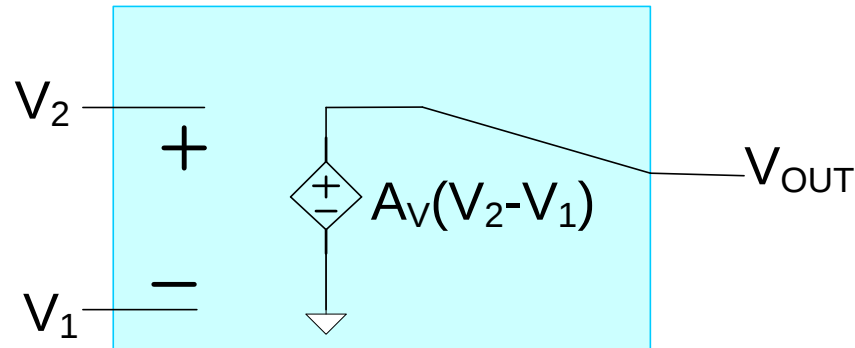


If A_V is large

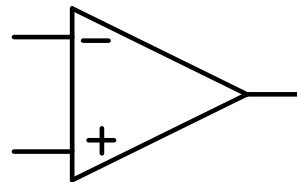

Operational Amplifier (Op Amp)

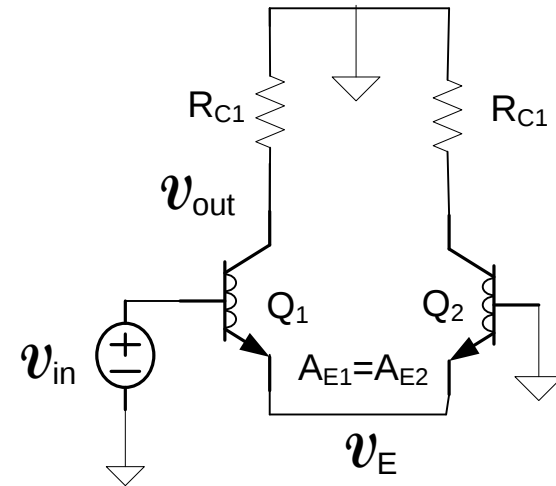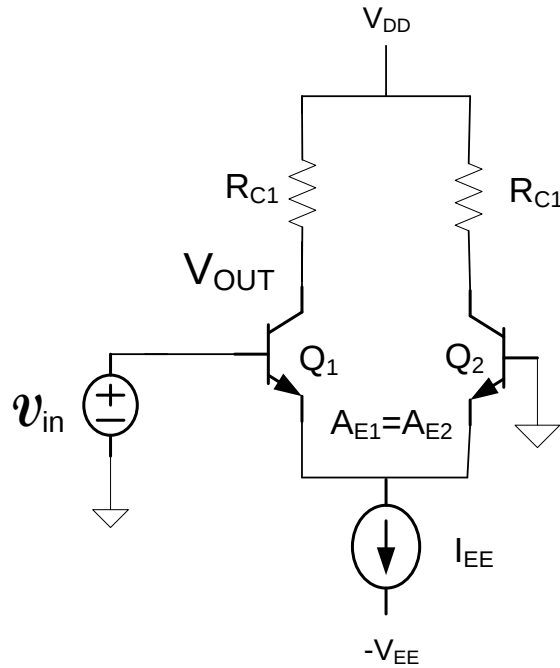
Example: Determine the voltage gain of the following circuit




Since symmetric when $v_{IN}=0$

$$I_{C1} = I_{C2} = \frac{I_{EE}}{2}$$
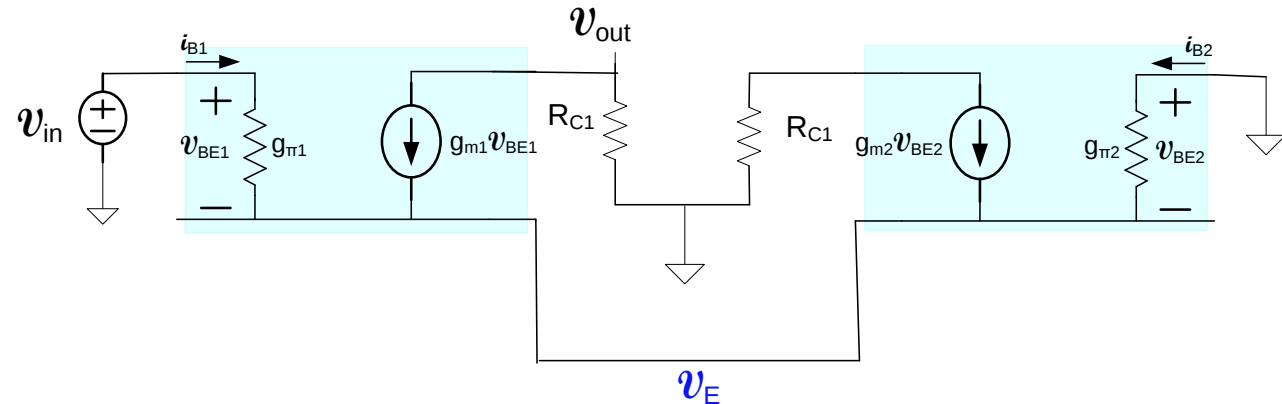
$$g_{m1} = g_{m2} = \frac{I_{EE}}{2V_t}$$



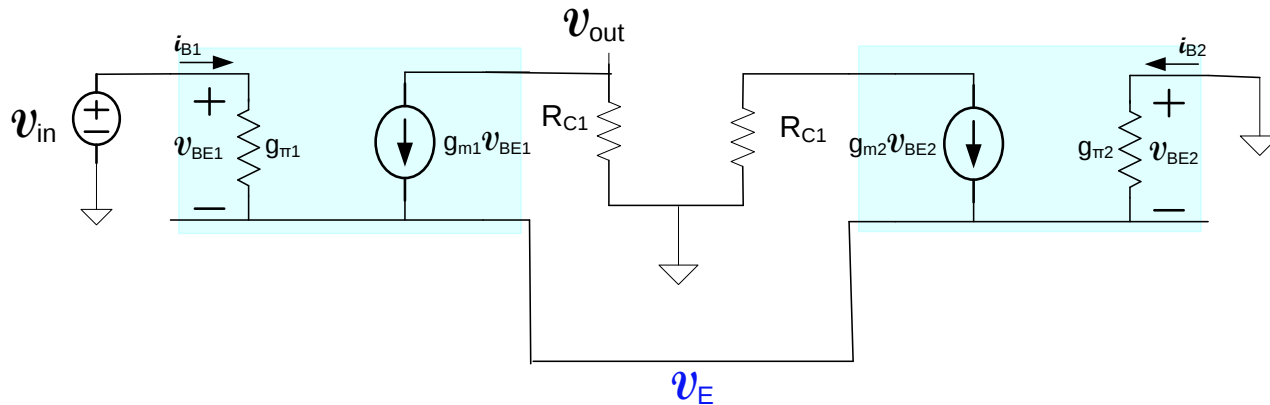Example: Determine the voltage gain of the following circuit



$$v_E (g_{\pi 1} + g_{\pi 2}) = g_{\pi 1} v_{IN} + g_{m1} (v_{IN} - v_E) + g_{m2} (-v_E)$$

$$v_{OUT} = -R_{C1} g_{m1} (v_{IN} - v_E)$$


$$v_E (g_{\pi 1} + g_{\pi 2} + g_{m1} + g_{m2}) = v_{IN} (g_{m1} + g_{\pi 1})$$

$$v_E = \frac{(g_{m1} + g_{\pi 1})}{(g_{\pi 1} + g_{\pi 2} + g_{m1} + g_{m2})} v_{IN}$$

$$v_{OUT} = -R_{C1} g_{m1} v_{IN} \left[1 - \frac{(g_{m1} + g_{\pi 1})}{(g_{\pi 1} + g_{\pi 2} + g_{m1} + g_{m2})} \right]$$

$$v_{OUT} = -R_{C1} g_{m1} v_{IN} \left[\frac{g_{\pi 1} + g_{\pi 2} + g_{m1} + g_{m2} - (g_{m1} + g_{\pi 1})}{(g_{\pi 1} + g_{\pi 2} + g_{m1} + g_{m2})} \right]$$

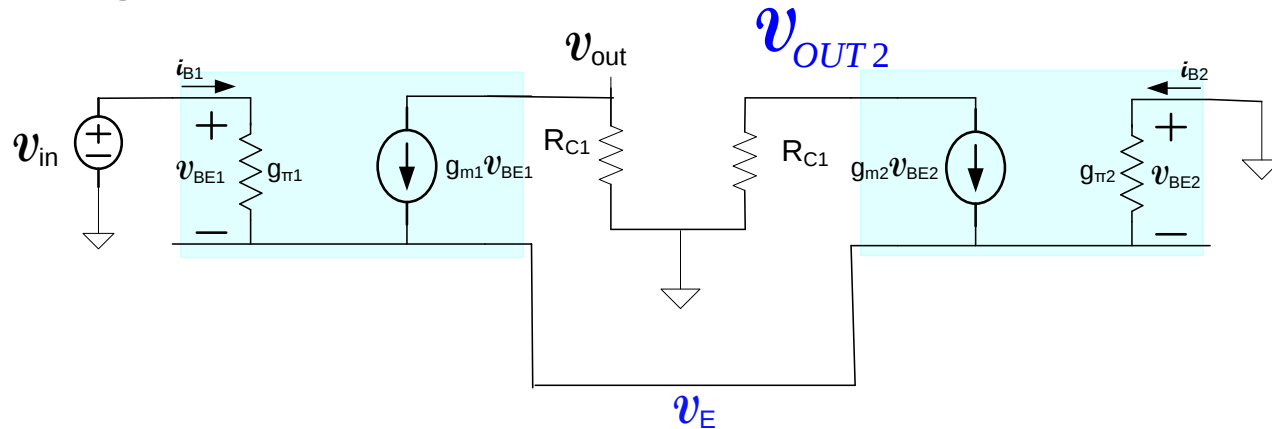Example: Determine the voltage gain of the following circuit




$$v_{OUT} = -R_{C1}g_{m1}v_{IN} \left[\frac{g_{\pi1} + g_{\pi2} + g_{m1} + g_{m2} - (g_{m1} + g_{\pi1})}{(g_{\pi1} + g_{\pi2} + g_{m1} + g_{m2})} \right]$$

$$v_{OUT} \cong -R_{C1}g_{m1}v_{IN} \left[\frac{g_{m2}}{(g_{m1} + g_{m2})} \right]$$

$$v_{OUT} \cong \left[\frac{-R_{C1}g_{m1}}{2} \right] v_{IN}$$

$$v_{OUT2} \cong \left[\frac{R_{C1}g_{m1}}{2} \right] v_{IN}$$



Differential amplifier

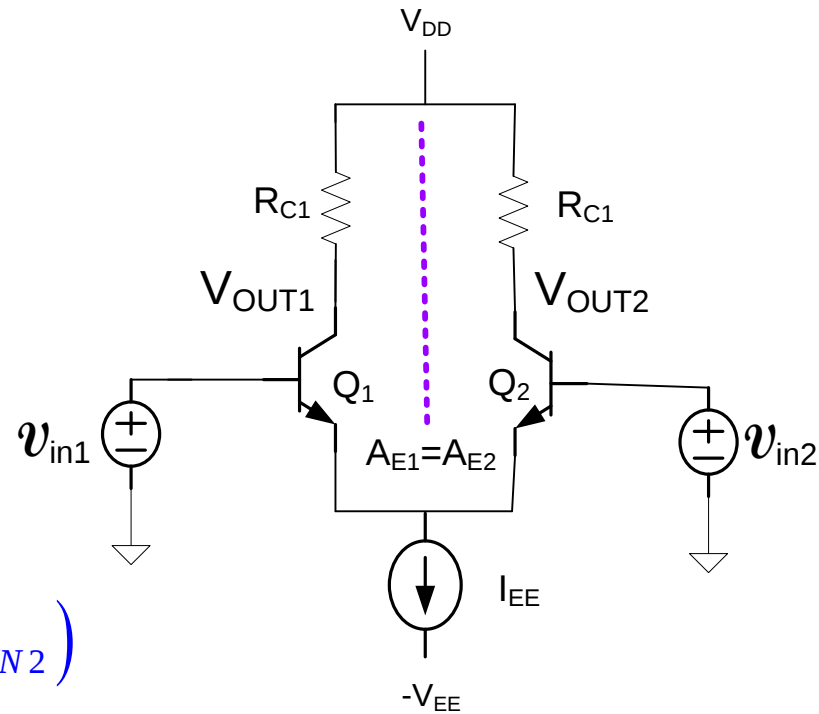

$$v_{OUT1} \cong -\left[\frac{R_{C1}g_{m1}}{2}\right](v_{IN1} - v_{IN2})$$
$$v_{OUT2} \cong \left[\frac{R_{C1}g_{m1}}{2}\right](v_{IN1} - v_{IN2})$$

- Very useful circuit
- This is a basic Op Amp
- Uses a current source and V_{DD} for biasing (no biasing resistors or caps!)
- But – needs a dc current source !!!!


Simple Current Sources

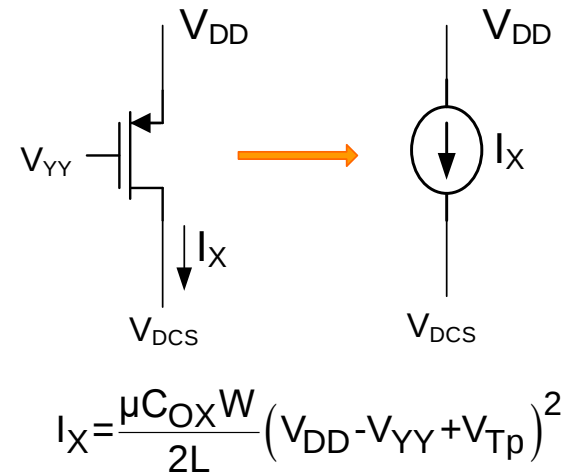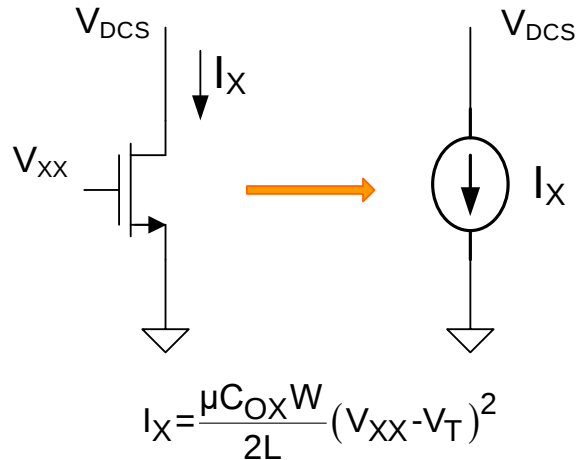

But how good are these current sources?


Model of dc Current Source

“Reasonable dc Current Source”

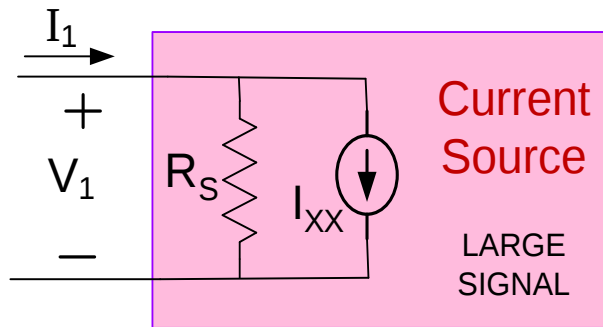


I_{XX} independent of V_1 and t , R_S large

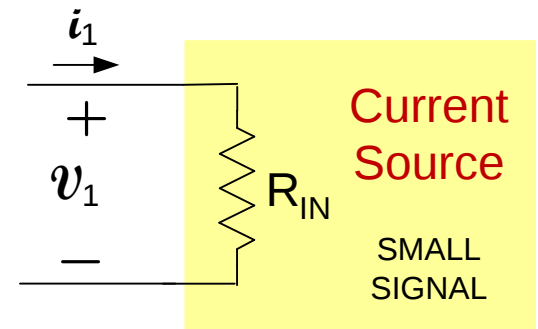Small-signal model of dc current source (since one-port)




want R_{IN} large

Ideal dc Current Source

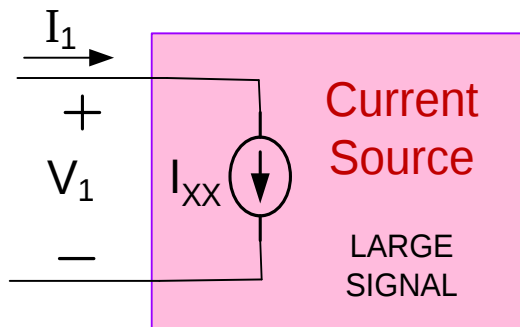


I_{XX} independent of V_1 and t

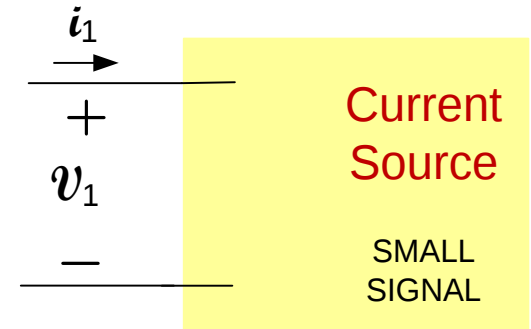

$R_{IN} = \infty$


Current Sources/Mirrors

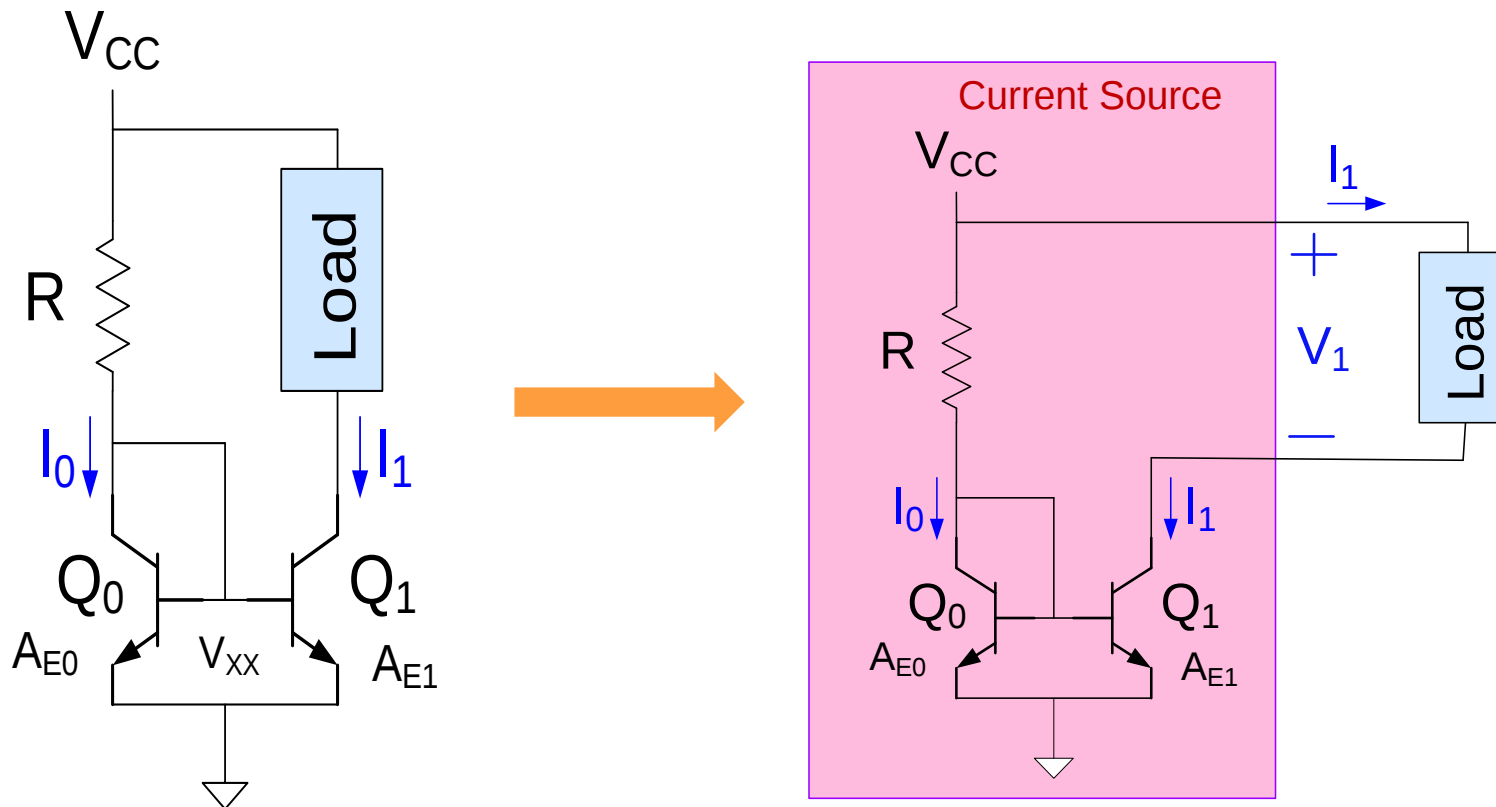Will show circuit in red behaves as a current source



R and Q_0 simply generate voltage V_{XX} in previous circuit


Current Sources/Mirrors

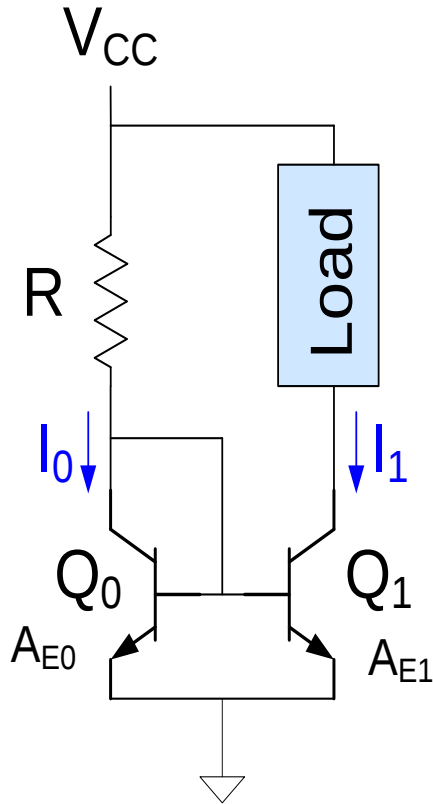

$$I_0 \cong \frac{(V_{CC} - 0.6V)}{R}$$

If the base currents are neglected

Current Sources/Mirrors

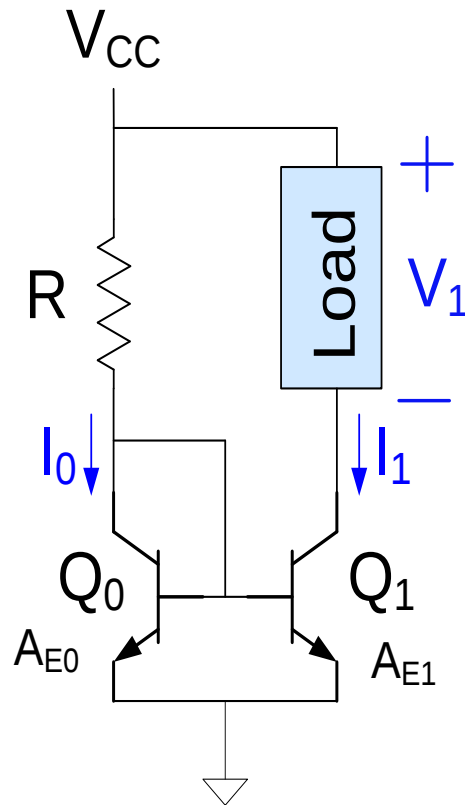

$$I_0 \cong \frac{(V_{CC} - 0.6V)}{R}$$

If the base currents are neglected

$$\left. \begin{aligned} I_0 &= J_S A_{E0} e^{\frac{V_{BE0}}{V_t}} \\ I_1 &= J_S A_{E1} e^{\frac{V_{BE1}}{V_t}} \end{aligned} \right\}$$

since $V_{BE1} = V_{BE2}$


$$I_1 \cong \left(\frac{A_{E1}}{A_{E0}} \right) I_0 = \left(\frac{A_{E1}}{A_{E0}} \right) \frac{V_{CC} - 0.6V}{R}$$

Note I_1 is not a function of V_1

Behaves as a current sink ! So is ideal with this model !!


And does not require an additional dc voltage source !!!

Current Sources/Mirrors

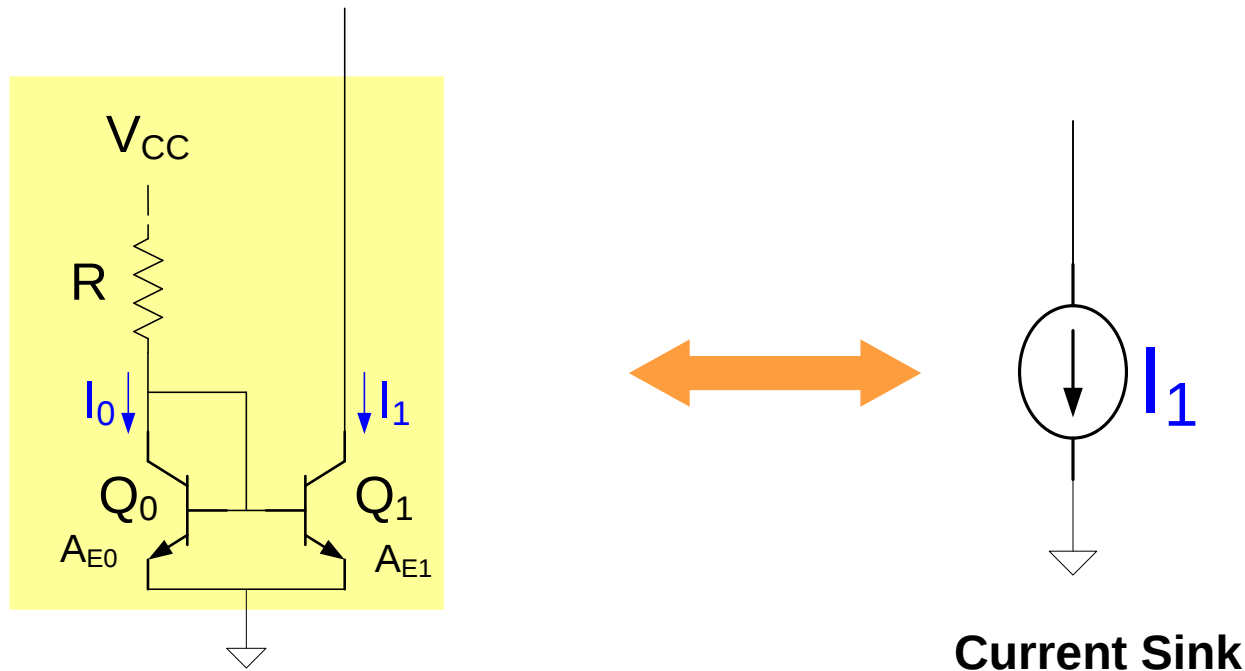

- Multiple Outputs Possible
- Can be built for sourcing or sinking currents
- Also useful as a current amplifier
- MOS counterparts work very well and are not plagued by base current


Current Sources/Mirrors

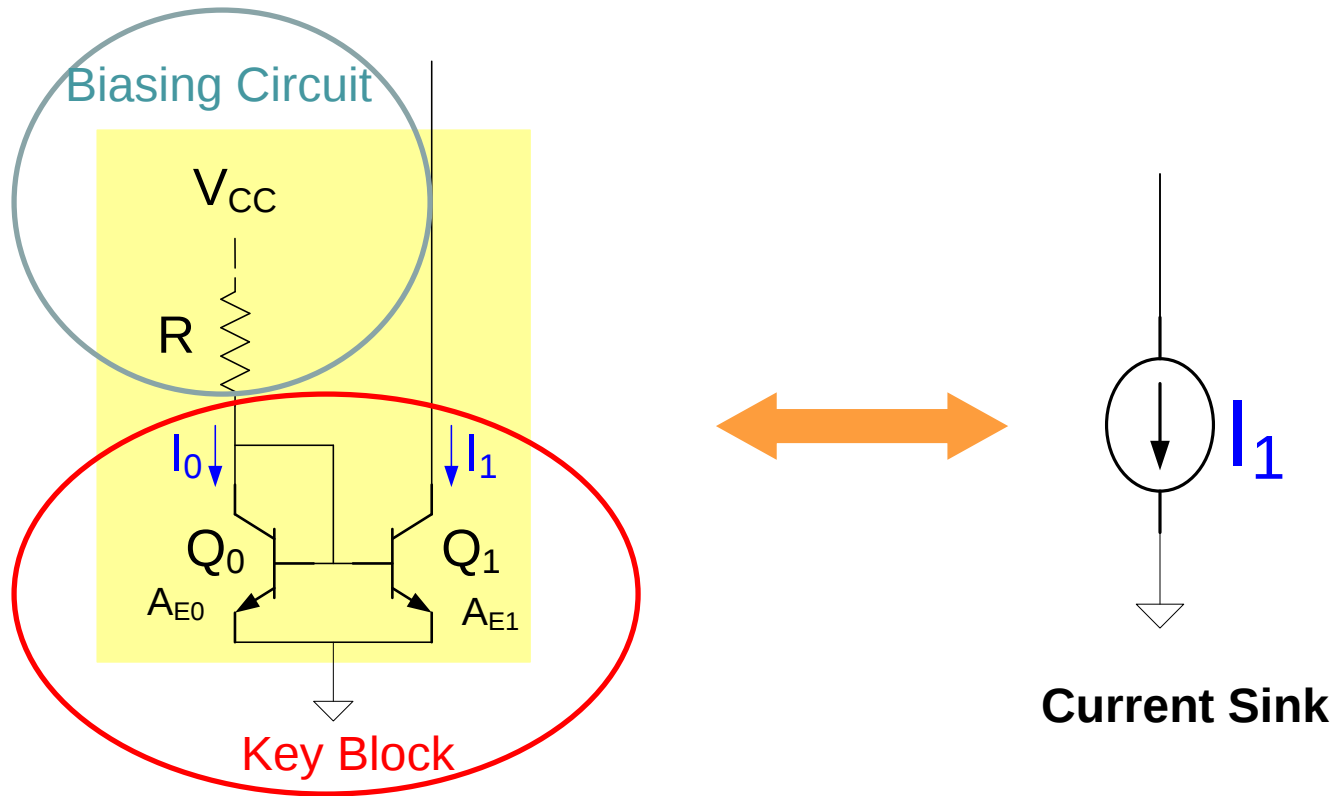

Two ways to look at this circuit:

- Q_0 and R bias Q_1
- R biases the $Q_0 : Q_1$ block


Current Sources/Mirrors

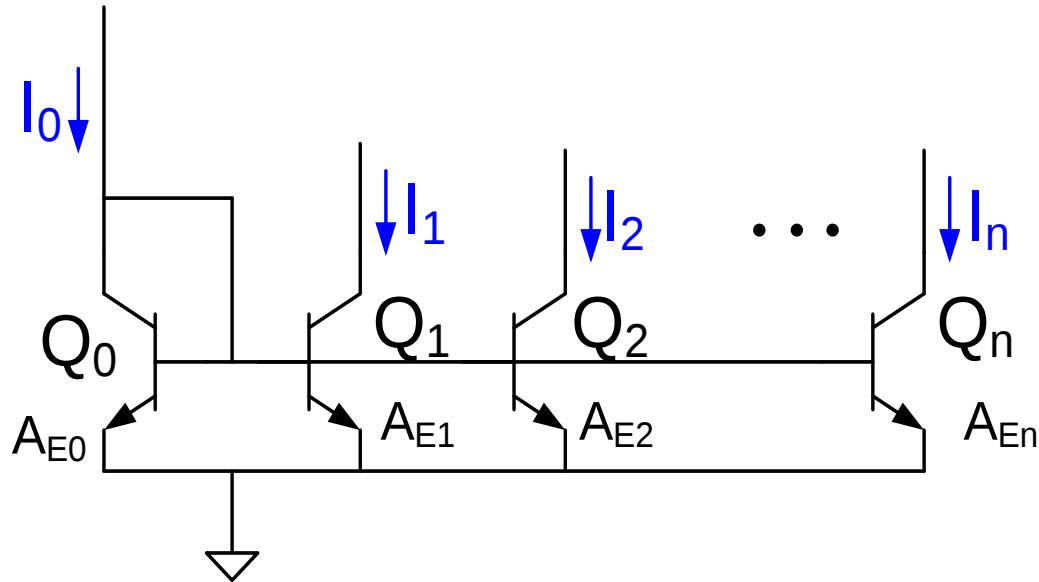

Multiple-Output Bipolar Current Sink

$$I_k = \left[\frac{A_{Ek}}{A_{E0}} \right] I_0$$


Current Sources/Mirrors

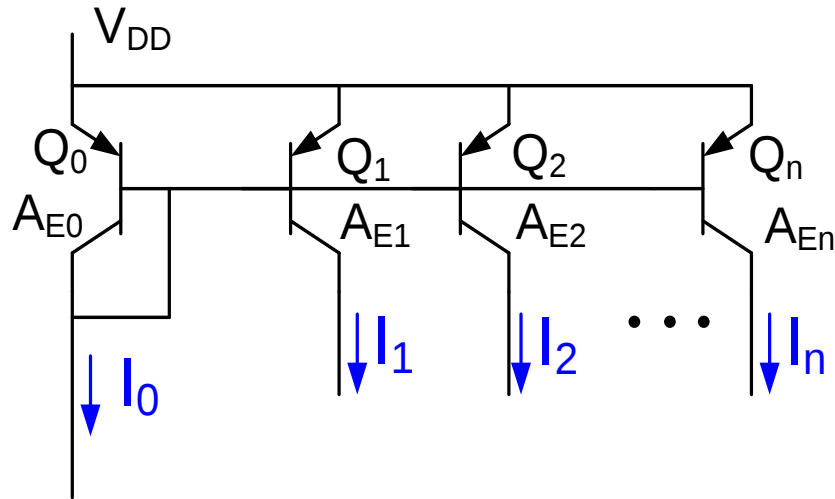

Multiple-Output Bipolar Current Source

$$I_k = \left[\frac{A_{Ek}}{A_{E0}} \right] I_0$$


Current Sources/Mirrors

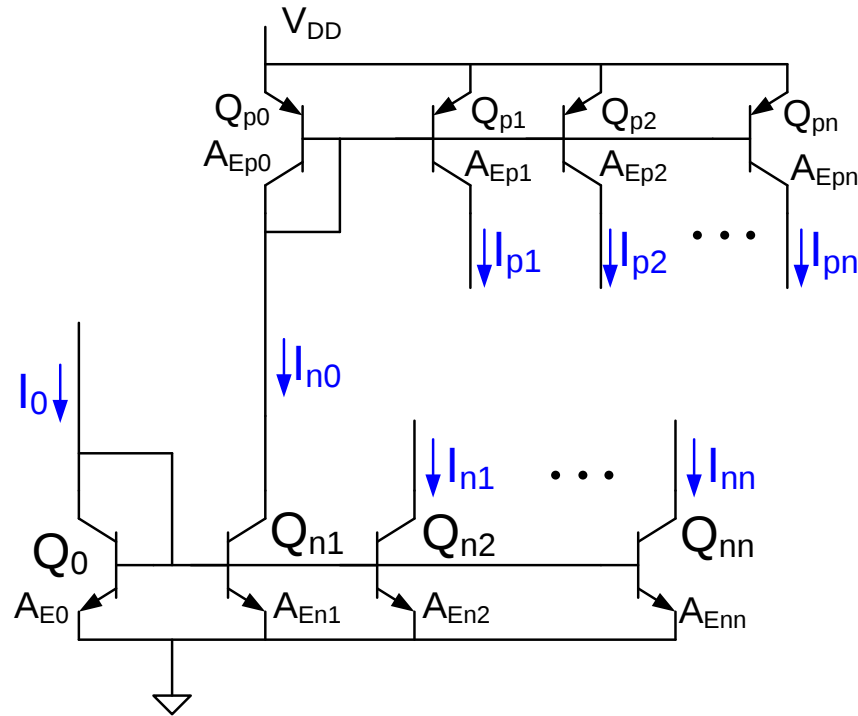

Multiple-Output Bipolar Current Source and Sink

$$I_{nk} = ? \quad I_{pk} = ?$$


Current Sources/Mirrors

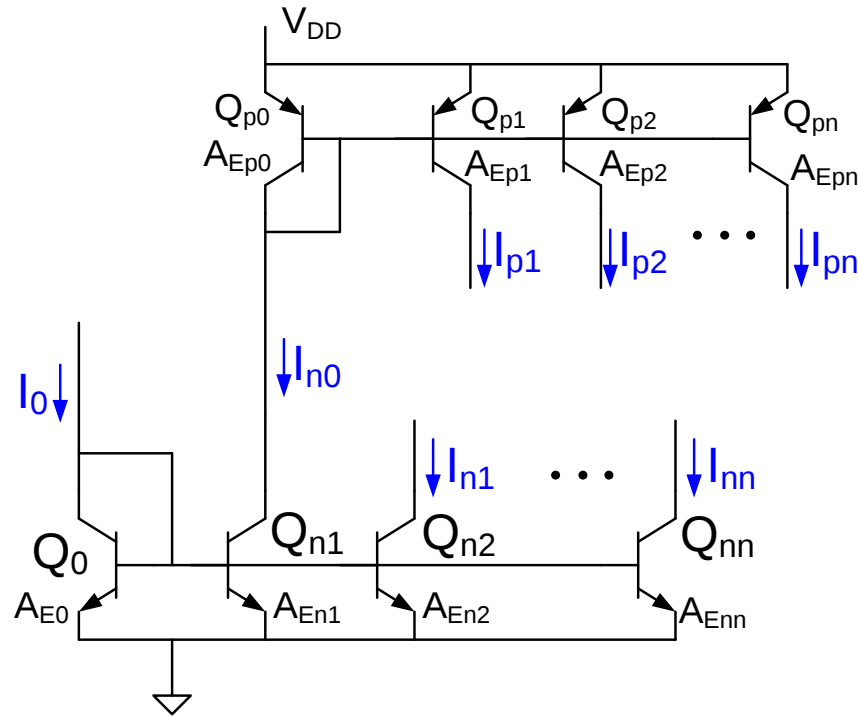

Multiple-Output Bipolar Current Source and Sink

$$I_{nk} = \left[\frac{A_{Enk}}{A_{E0}} \right] I_0 \quad I_{pk} = \left[\frac{A_{En1}}{A_{E0}} \right] \left[\frac{A_{Epk}}{A_{Ep0}} \right] I_0$$

Current Sources/Mirrors

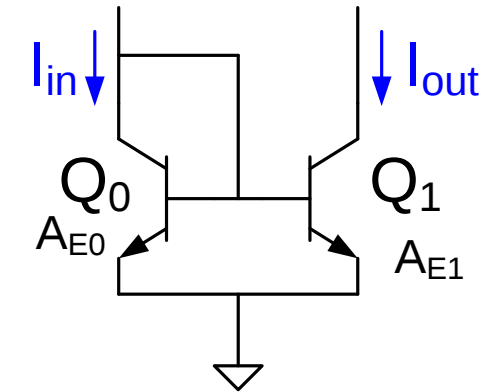


npn Current Mirror

$$I_{out} = \left[\frac{A_{E1}}{A_{E0}} \right] I_{in}$$

- Termed a “current mirror”
- Output current linearly dependent on I_{in}
- Serves as a current amplifier
- Widely used circuit

But I_{in} and I_{out} must be positive !

Current Sources/Mirrors

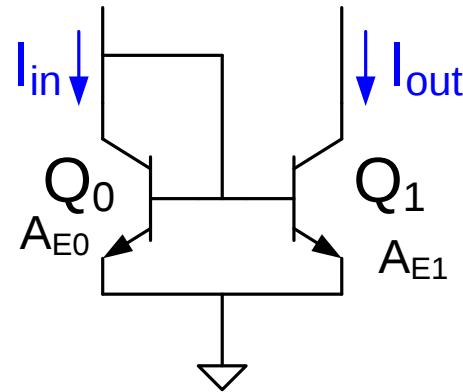


npn Current Mirror

$$I_{out} = \left[\frac{A_{E1}}{A_{E0}} \right] I_{in}$$

- Termed a “current mirror”
- Output current linearly dependent on I_{in}
- Small-signal and large-signal relationships the same since linear
- Serves as a current amplifier
- Widely used circuit

But I_{in} must be positive !

Current Sources/Mirrors

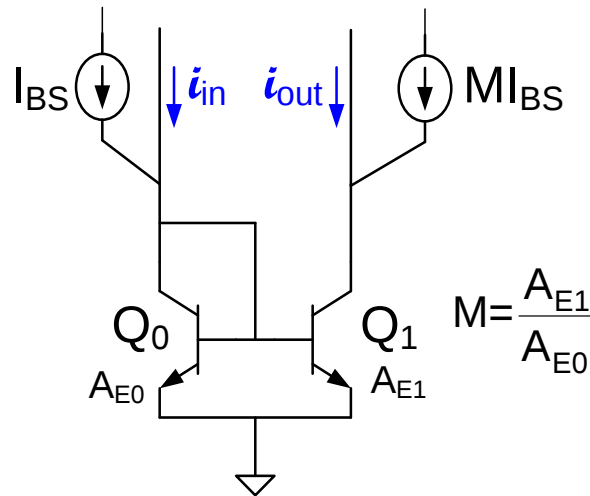

npn current mirror amplifier

$i_{out} = ?$

$$\frac{i_{OUT} + MI_{BS}}{i_{in} + I_{BS}} = M$$


$$i_{OUT} + MI_{BS} = M(i_{in} + I_{BS})$$

$$i_{OUT} + M\cancel{I}_{BS} = M(i_{in} + \cancel{I}_{BS})$$

$$\frac{i_{OUT}}{i_{in}} = M$$

But $I_{BS} + i_{in} > 0$!

Current Sources/Mirrors

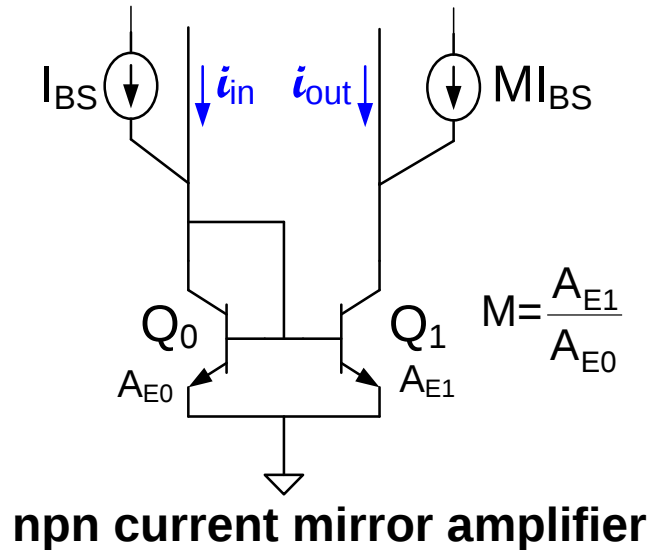


$$i_{out} = \left[\frac{A_{E1}}{A_{E0}} \right] i_{in}$$

Amplifiers both positive and negative currents (provided $i_{IN} > -I_{BS}$)


Current amplifiers are easy to build !!

Current gain can be accurately controlled with appropriate layout !!

Current Sources/Mirrors

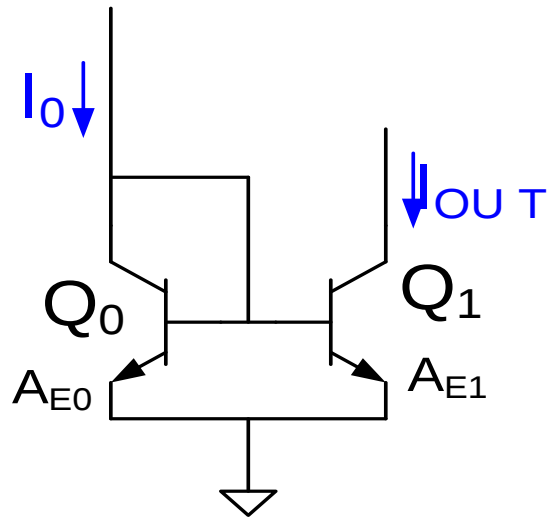


npn Current Mirror

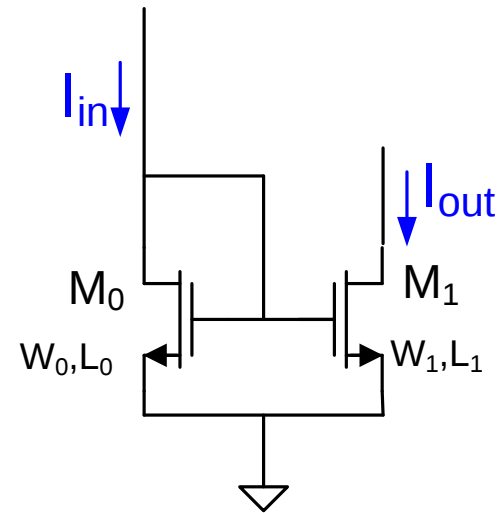

n-channel Current Mirror

$$I_{out} = ?$$

Current Sources/Mirrors

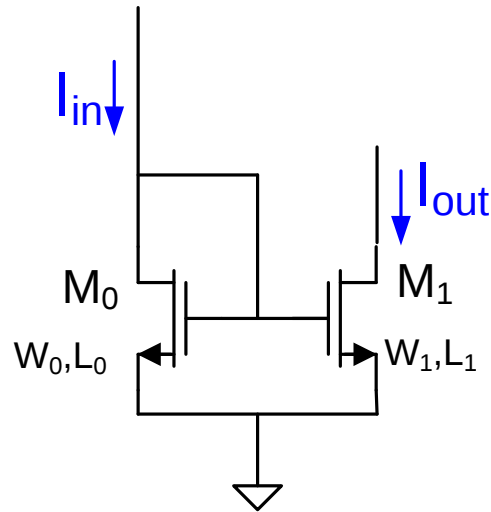

n-channel Current Mirror


$$\left. \begin{aligned} I_{in} &= \frac{\mu C_{ox} W_0}{2L_0} (V_{GS0} - V_{T0})^2 \\ I_{out} &= \frac{\mu C_{ox} W_1}{2L_1} (V_{GS1} - V_{T1})^2 \end{aligned} \right\}$$

If process parameters are matched, it follows that

$$I_{out} = \left[\frac{W_1}{W_0} \frac{L_0}{L_1} \right] I_{in}$$


- Current mirror gain can be accurately controlled !
- Layout is important to get accurate gain (for both MOS and BJT)

Current Sources/Mirrors Summary

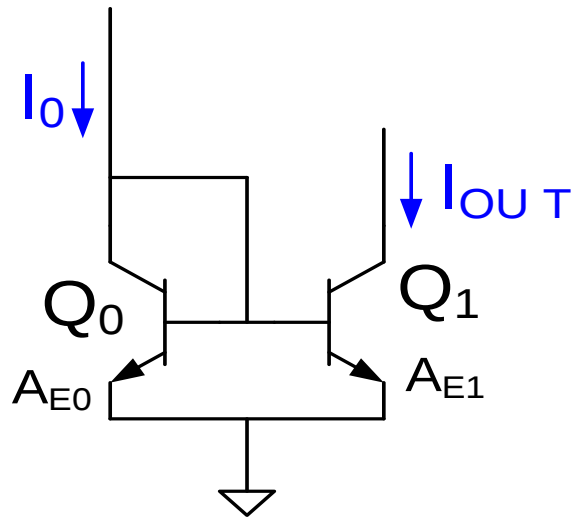

npn Current Mirror

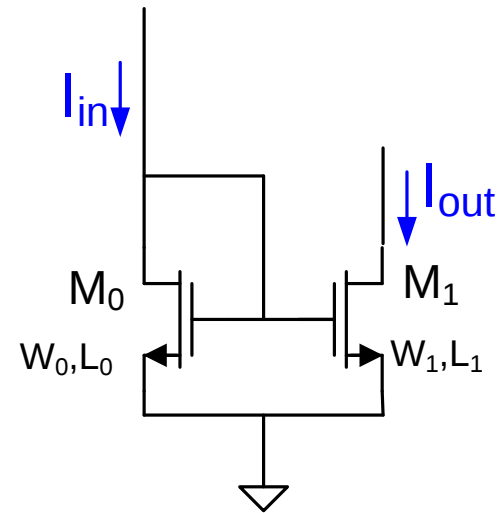
$$I_{out} = \left[\frac{A_{E1}}{A_{E0}} \right] I_{in}$$




n-channel Current Mirror

$$I_{out} = \left[\frac{W_1}{W_0} \frac{L_0}{L_1} \right] I_{in}$$

Layout of Current Mirrors

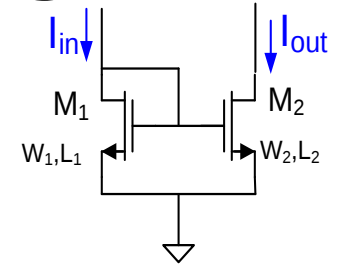


Example with $M = 2$

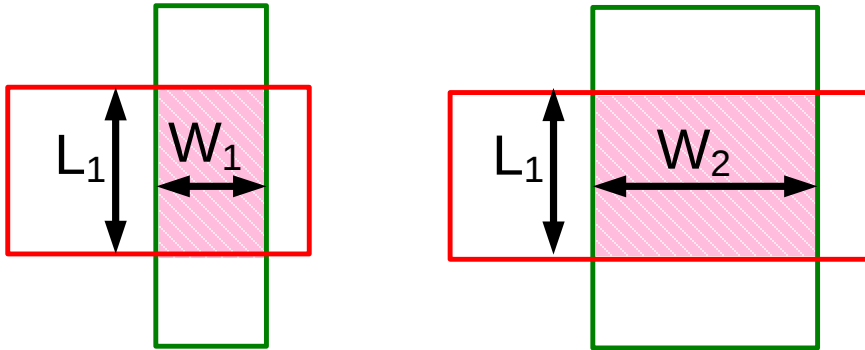

$$M = \left[\frac{W_2}{W_1} \frac{L_1}{L_2} \right]$$

Standard layout

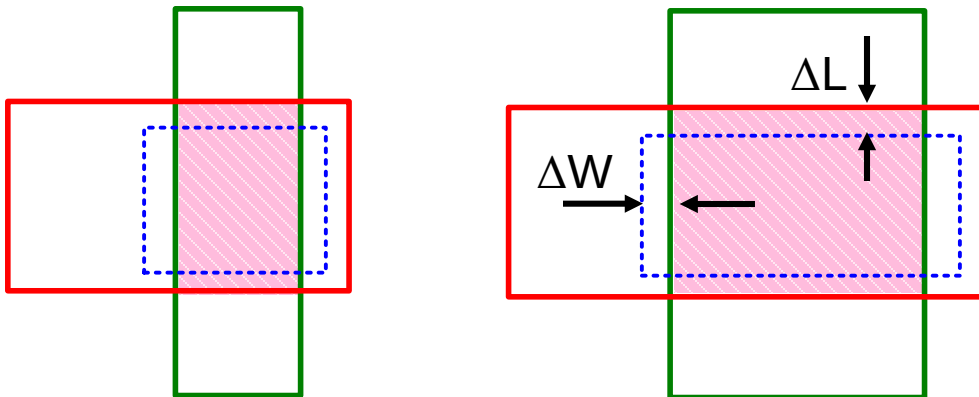

$$M = \left[\frac{W_2 + 2\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_2 + 2\Delta L} \right]$$


$$M = \left[\frac{2W_1 + 2\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] \neq 2$$

Gate area after fabrication depicted



Layout of Current Mirrors


Example with $M = 2$

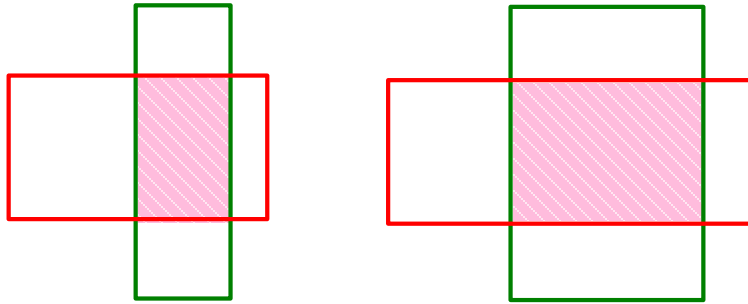

Standard layout

$$M = \left[\frac{W_2}{W_1} \frac{L_1}{L_2} \right]$$
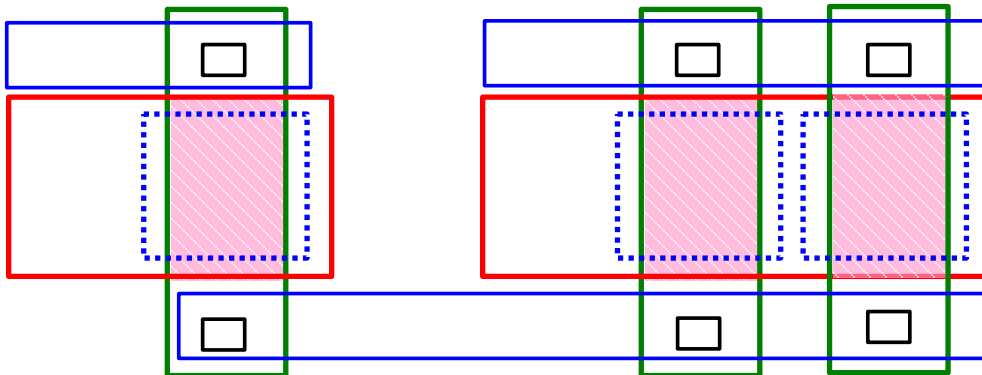
$$M = \left[\frac{2W_1 + 2\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] \neq 2$$




Better Layout

$$M = \left[\frac{2W_1 + 4\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] = 2$$


Layout of Current Mirrors

Example with $M = 2$

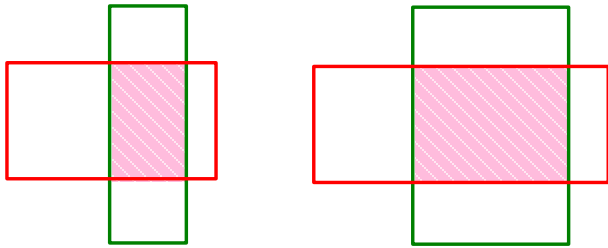


Standard layout
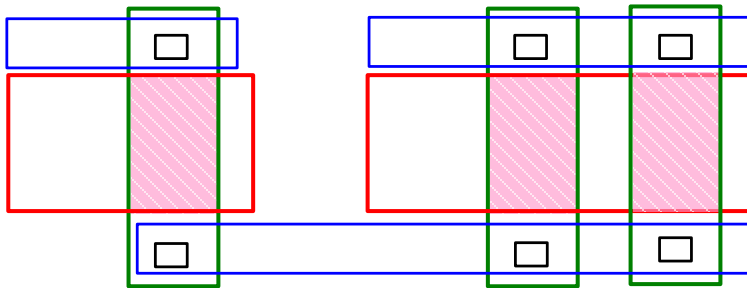
$$M = \left[\frac{W_2}{W_1} \frac{L_1}{L_2} \right]$$



Better Layout
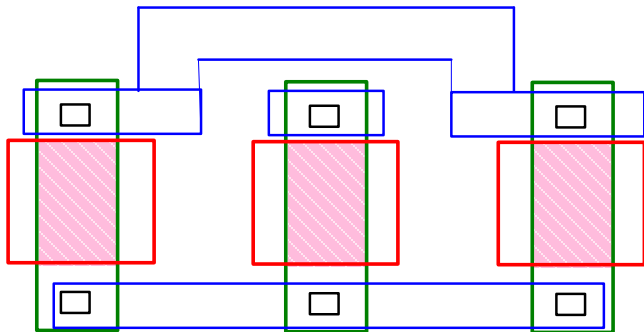
$$M = \left[\frac{2W_1 + 4\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] = 2$$




Even Better Layout

$$M = \left[\frac{2W_1 + 4\Delta W}{W_1 + 2\Delta W} \cdot \frac{L_1 + 2\Delta L}{L_1 + 2\Delta L} \right] = 2$$

This is termed a common-centroid layout

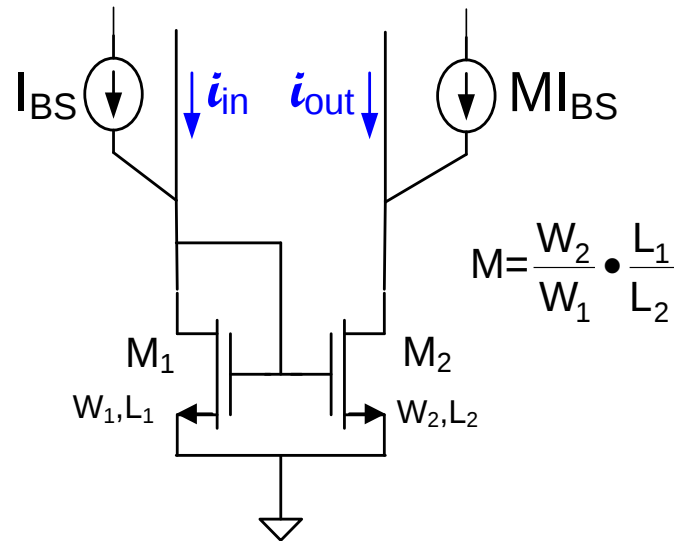
n-channel current mirror current amplifier




$$i_{out} = \left[\frac{W_2}{W_1} \frac{L_1}{L_2} \right] i_{in}$$

Amplifies both positive and negative currents

Current Sources/Mirrors

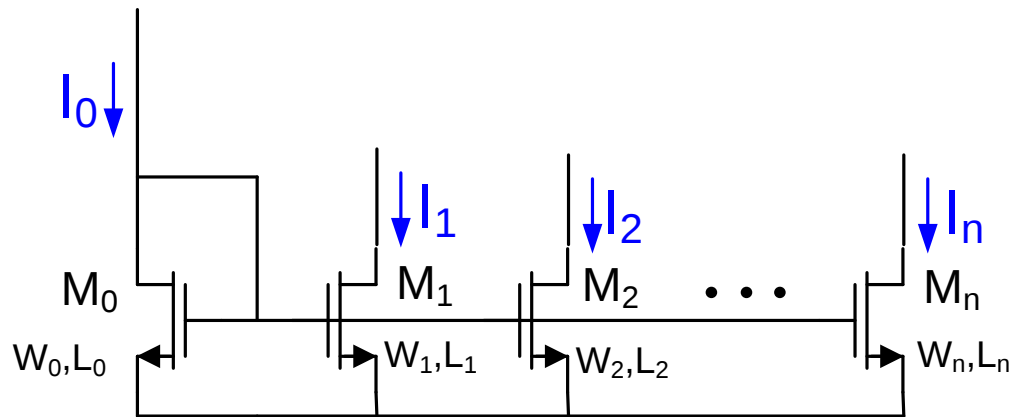

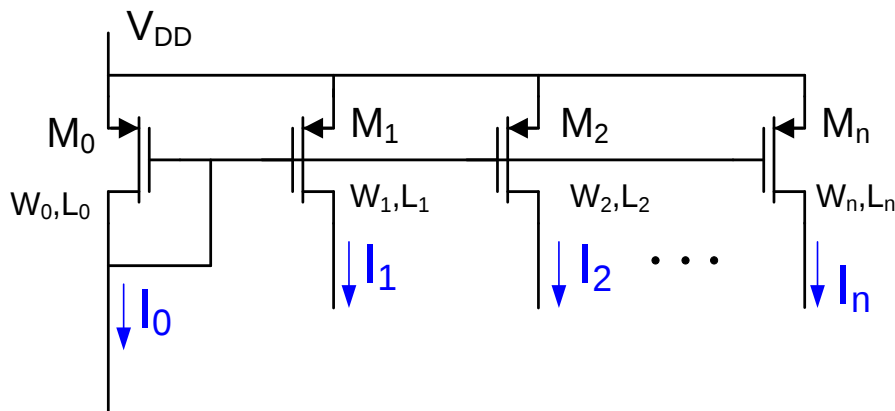multiple output n-channel current sink array




multiple output p-channel current source array

$$I_k = \left[\frac{W_k}{W_0} \frac{L_0}{L_k} \right] I_0$$

Current Sources/Mirrors

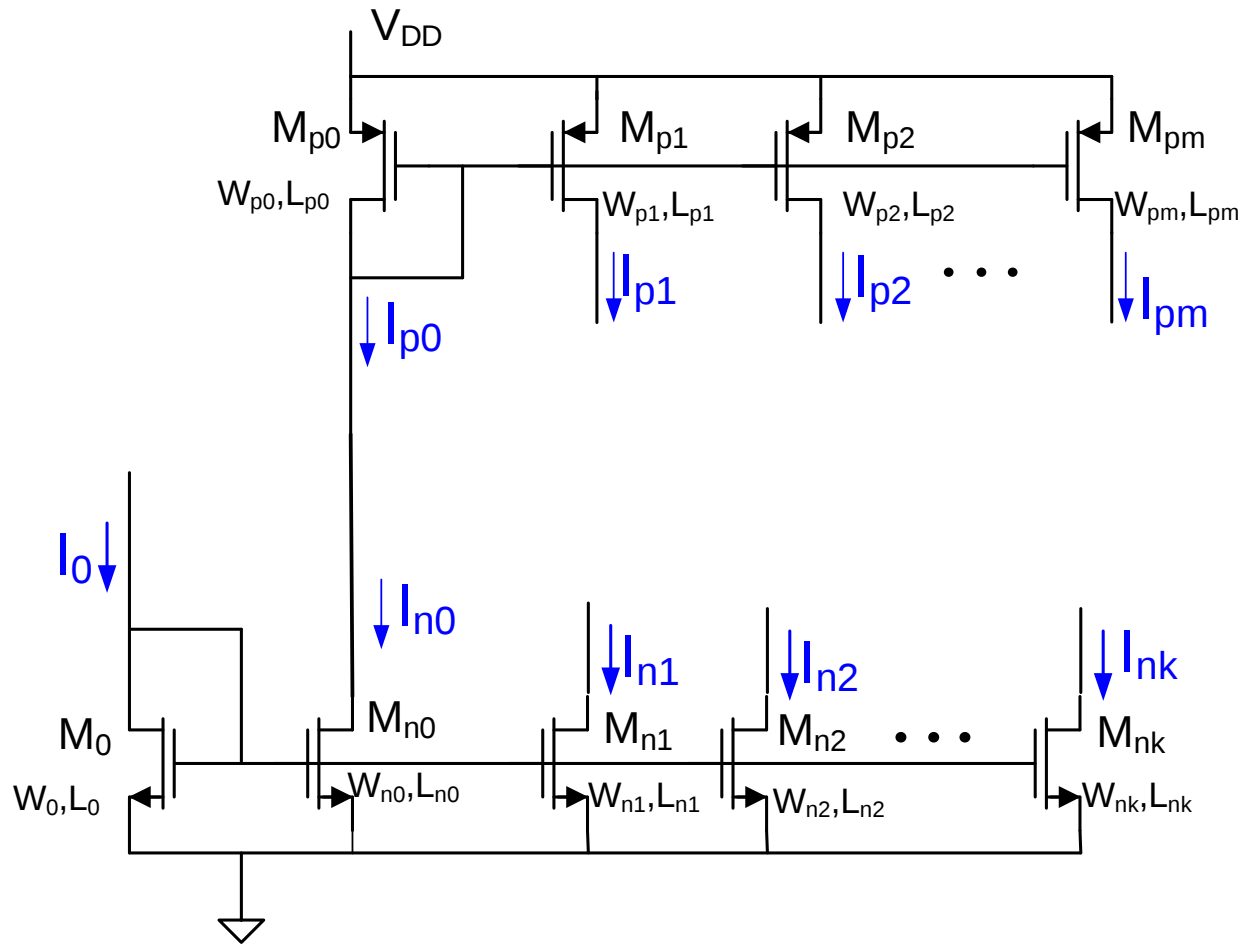multiple sourcing and sinking current outputs




$$I_{pj} = \left[\frac{W_{pj}}{L_{pj}} \cdot \frac{L_{p0}}{W_{p0}} \right] M I_0$$

$$M = \left[\frac{W_{n0}}{L_{n0j}} \cdot \frac{L_0}{W_0} \right]$$

$$I_{nj} = \left[\frac{W_{nj}}{L_{nj}} \cdot \frac{L_0}{W_0} \right] I_0$$

m and k may be different
Often $M=1$

High-gain amplifier

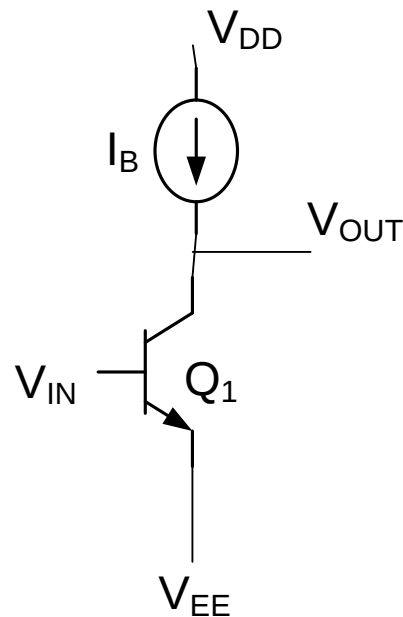


$$A_V \cong -8000$$

→ How can we build the current source?


What is the small-signal model of an actual current source?

Basic Current Sources and Sinks

Bipolar Mirror-Based Current Sink

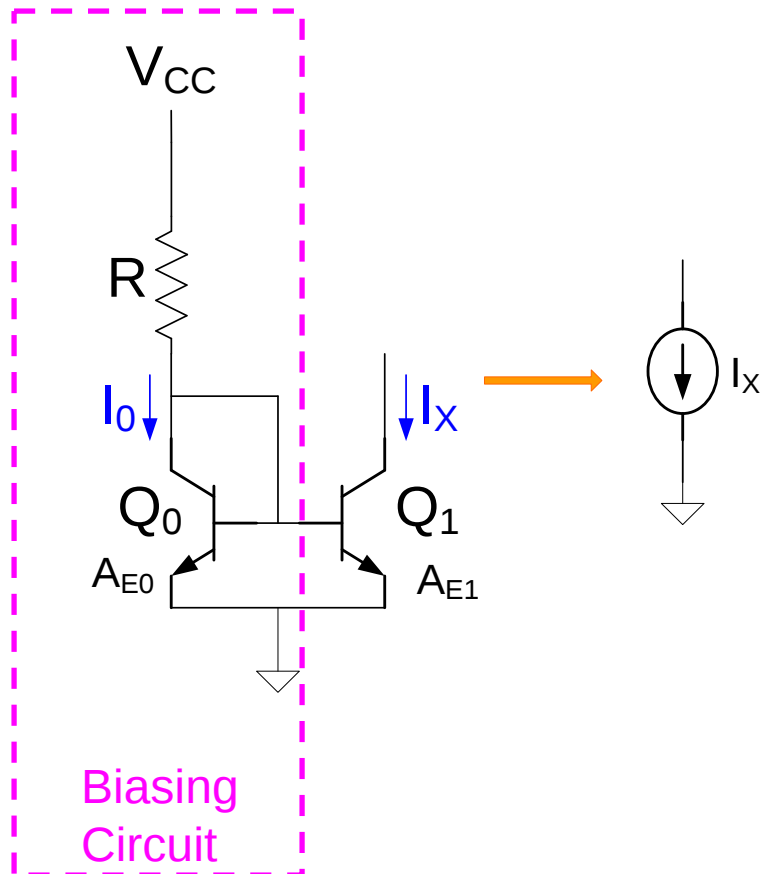


Bipolar Mirror-Based Current Source

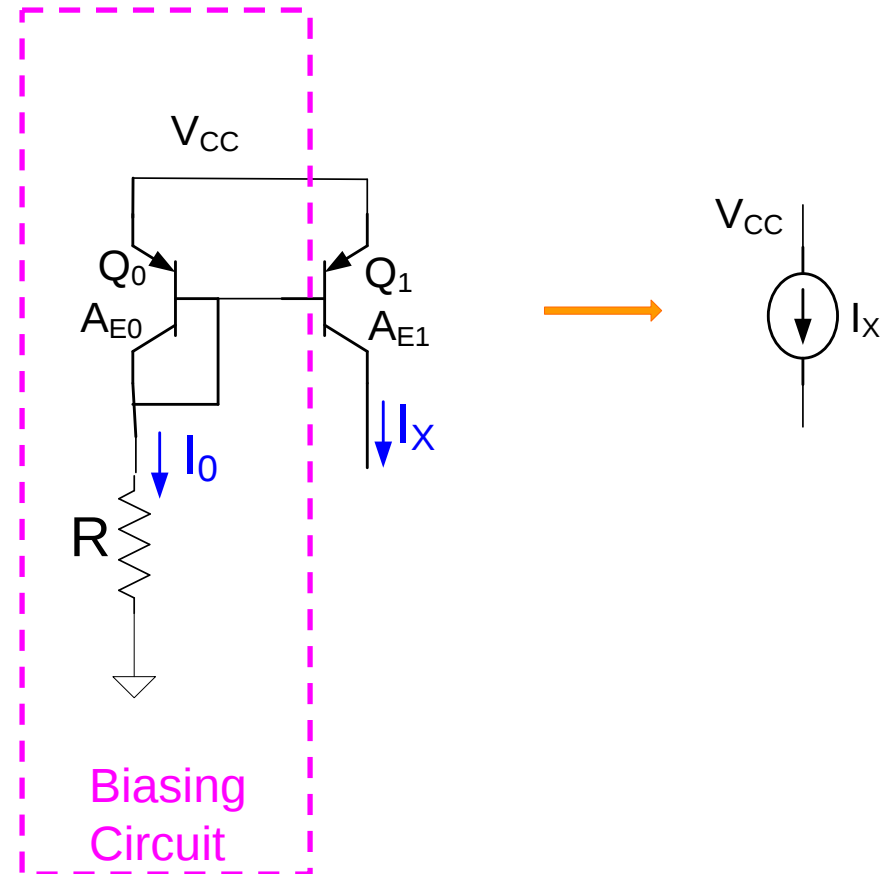

Biasing circuit uses same V_{CC} as amplifier and no other independent sources


High-gain amplifier

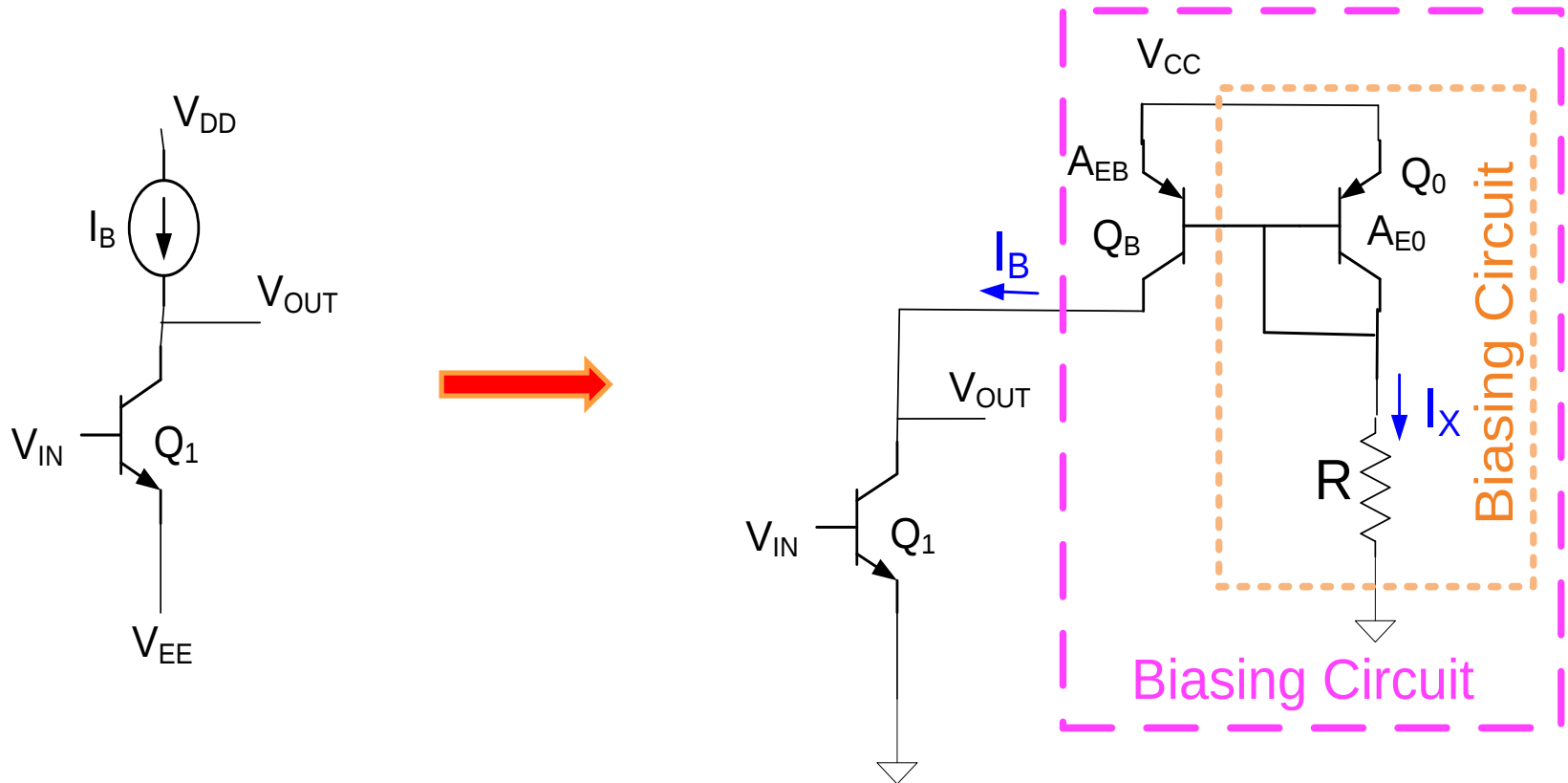


- Bias circuitry requires only a single independent dc voltage source !
- Incremental overhead is only one transistor, Q_B

Basic Current Sources and Sinks

Basic Bipolar Current Sinks

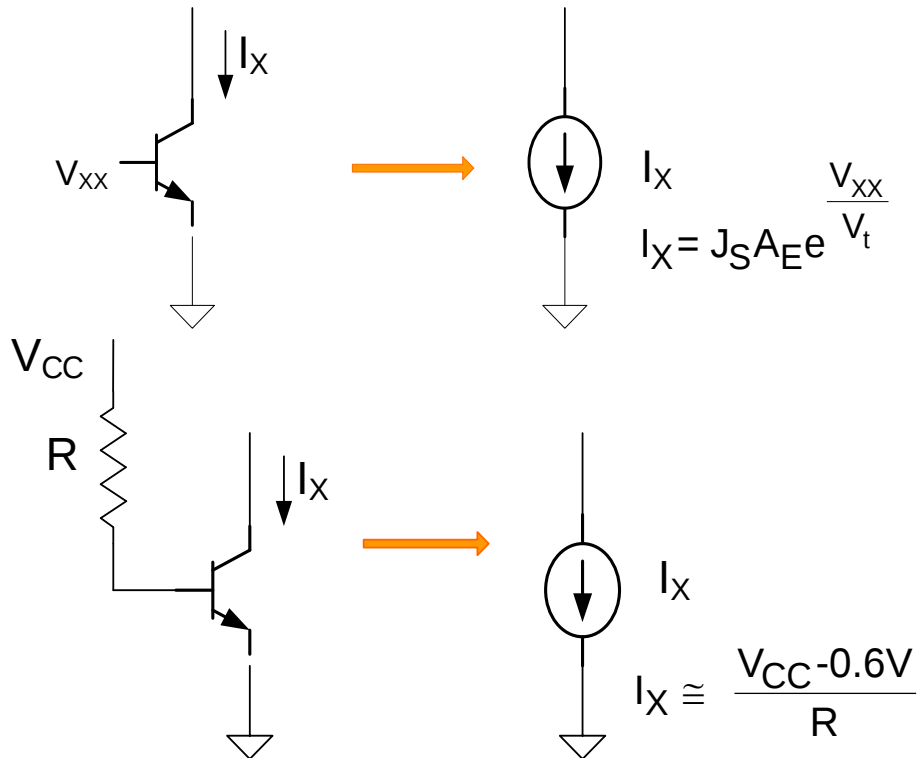


Basic Bipolar Current Sources

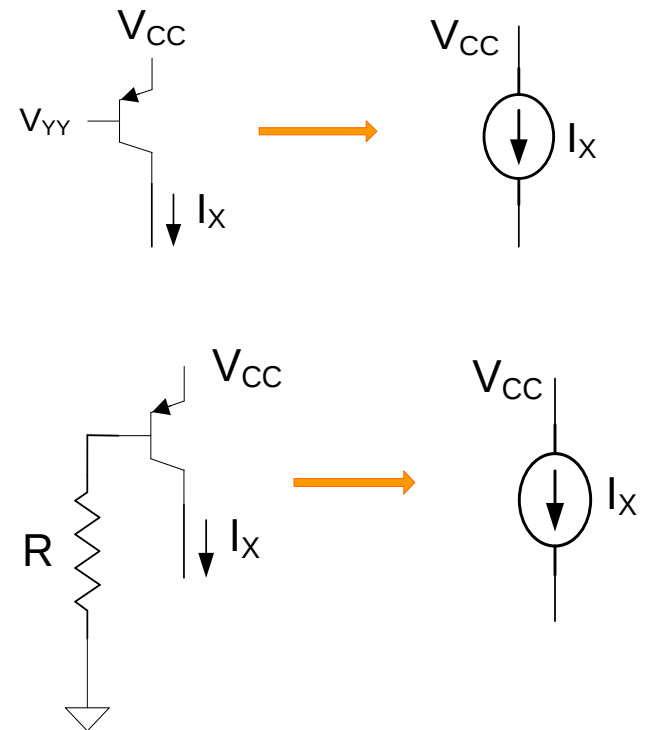

- Very practical methods for biasing the BJTs (or MOSFETs) can be used
- Current Mirrors often used for generating sourcing and sinking currents
- Can think of biasing transistors with V_{XX} and V_{YY} in these current sources

High-gain amplifier

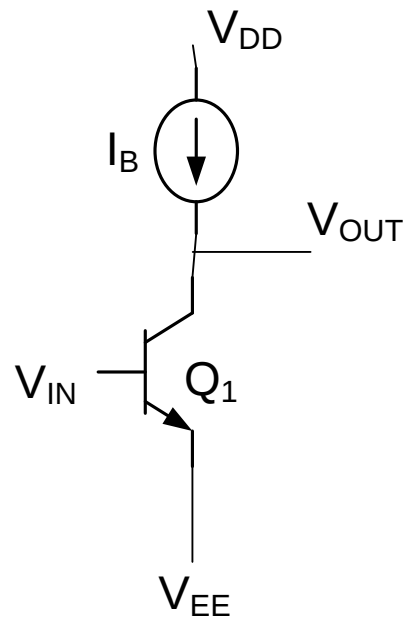


$$A_V \cong -8000$$

How can we build the current source?

→ What is the small-signal model of an actual current source?

Basic Current Sources and Sinks

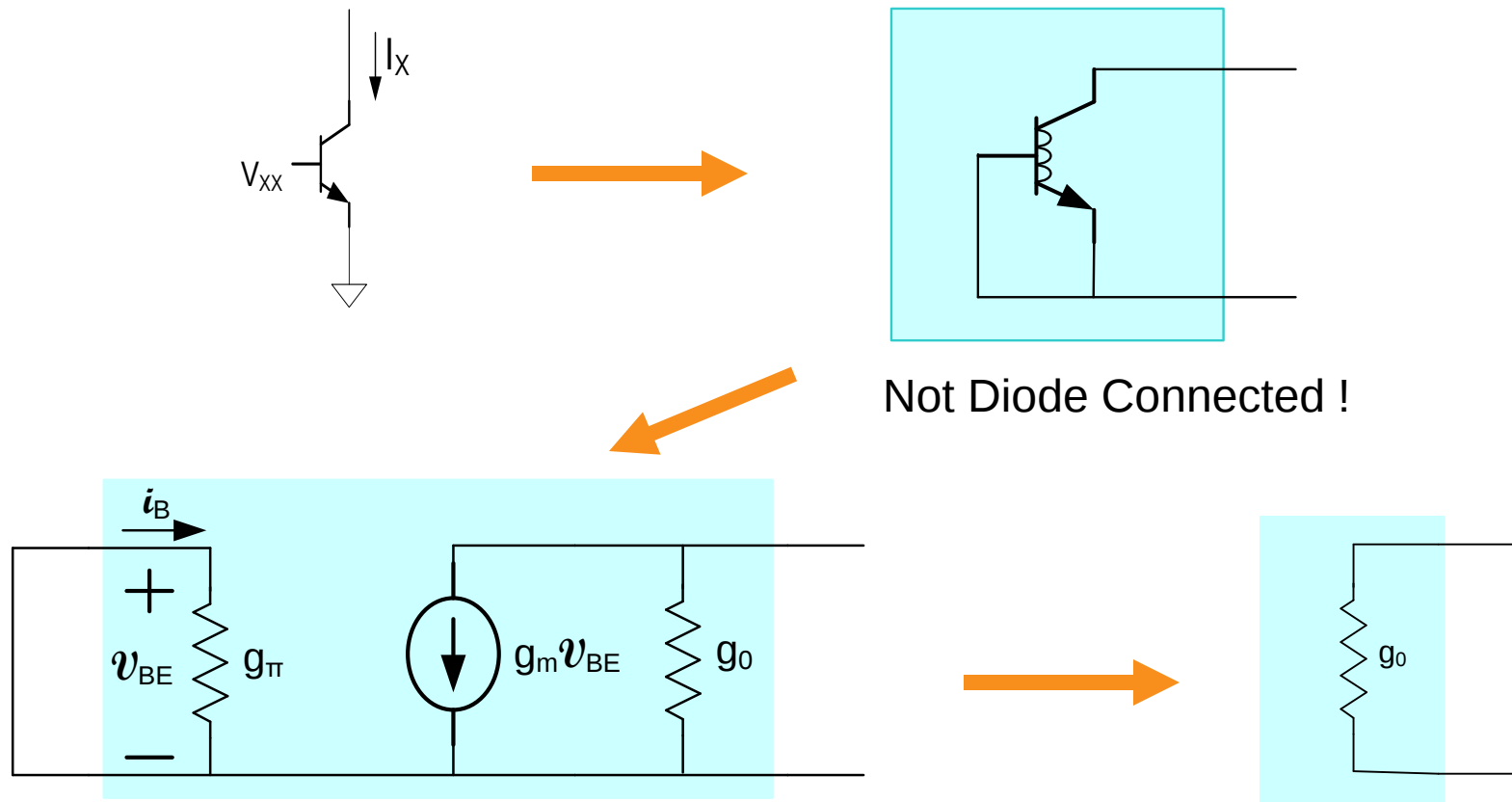
Small-signal Model of BJT Current Sinks and Sources



Small-signal model of all other BJT Sinks and Sources introduced so far are the same



Basic Current Sources and Sinks

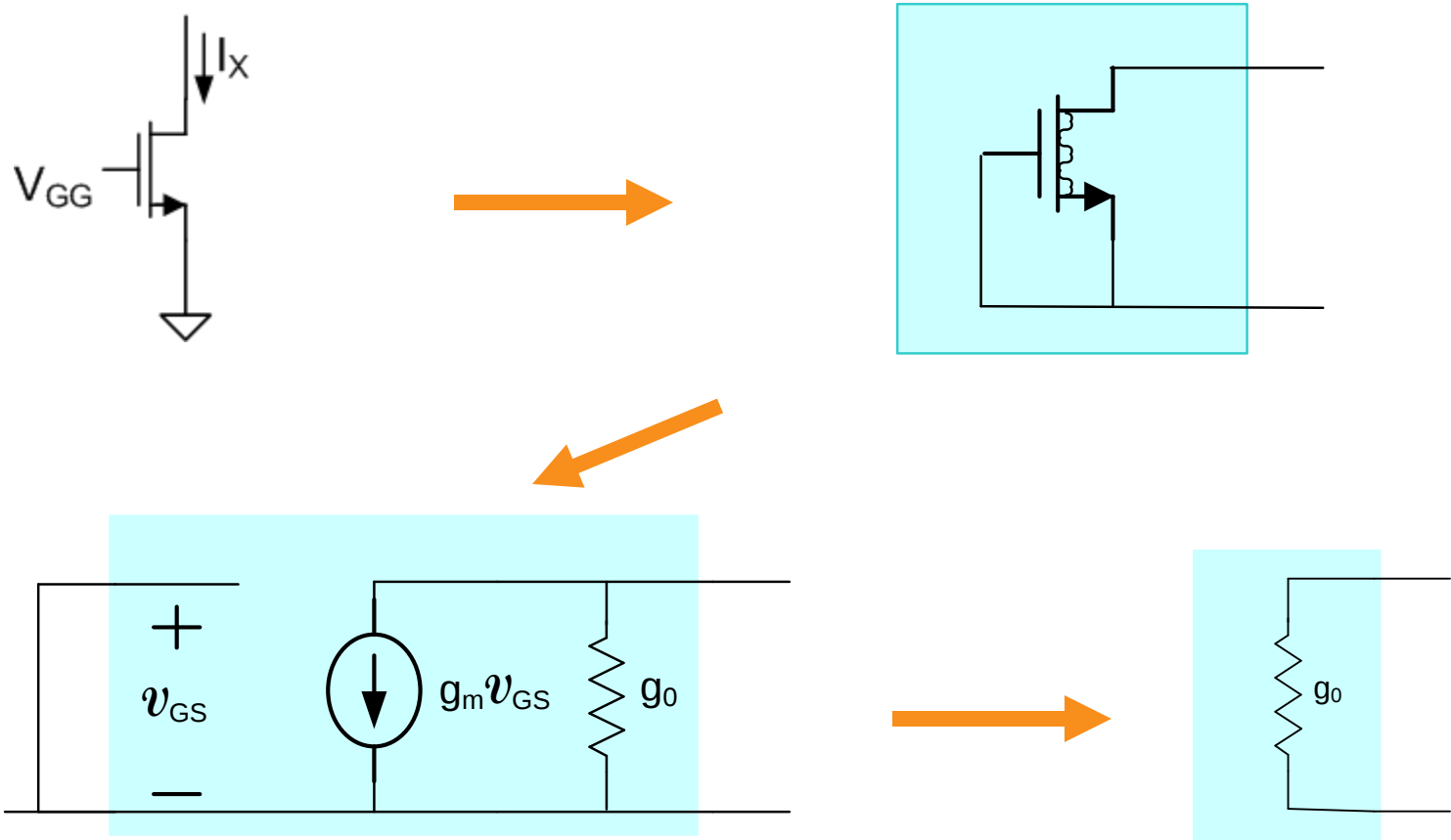Small-signal Model of MOS Current Sinks and Sources






Small-signal model of all other MOS Sinks and Sources introduced thus far are the same

High-gain amplifier

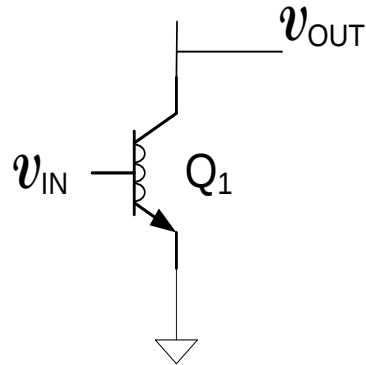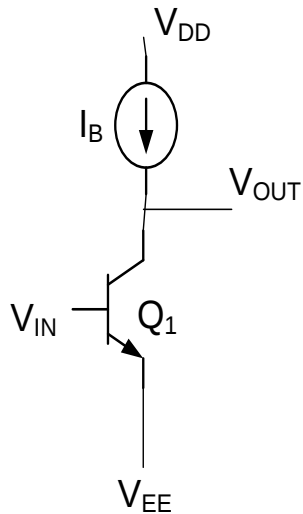


$$A_V = \frac{-g_m}{g_o}$$

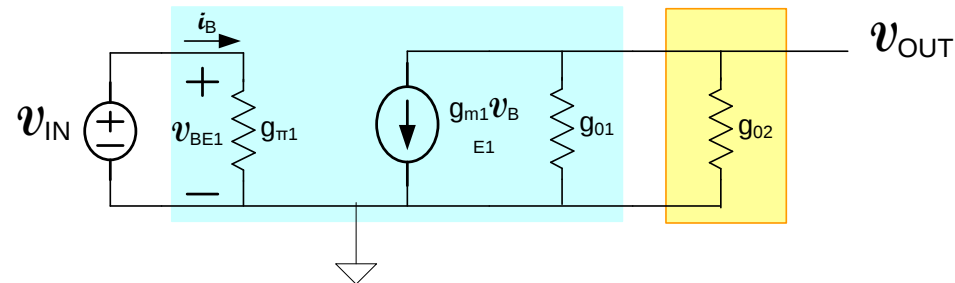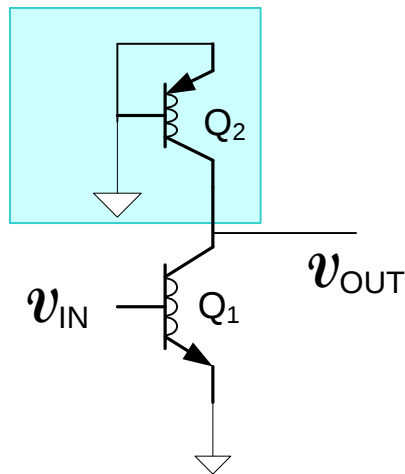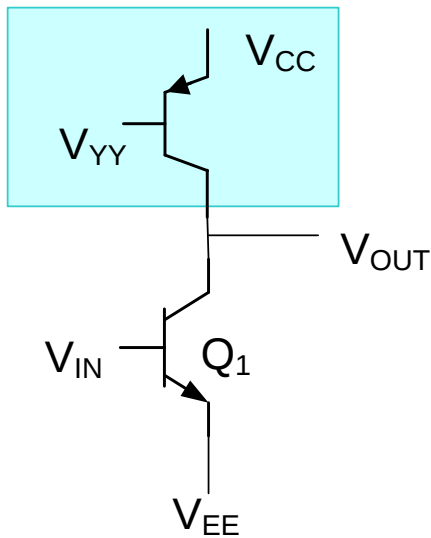

$$A_V = \frac{-g_{m1}}{g_{o1} + g_{o2}} \approx \frac{-g_{m1}}{2g_{o1}}$$


High-gain amplifier

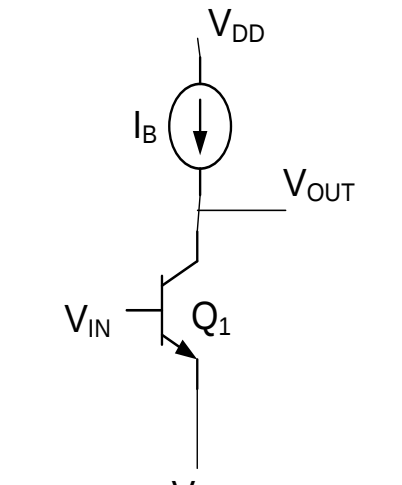

Circuit diagram of a common-emitter amplifier. The input signal V_{IN} is applied to the base of transistor Q_1 . The emitter is connected to V_{EE} . The collector is connected to V_{DD} through an ideal current source I_B . The output voltage V_{OUT} is taken from the collector.

$$A_V = \frac{-g_m}{g_o} = -8000$$
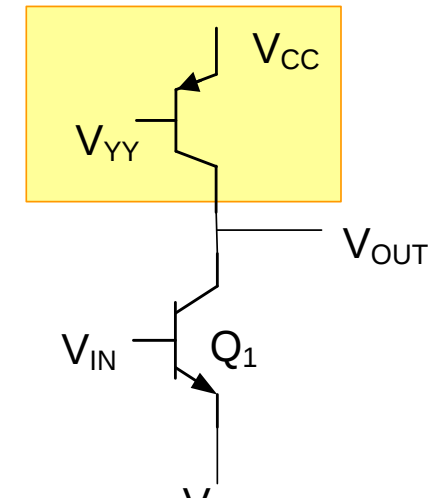
$$\frac{g_m}{g_o} = \frac{g_{m1}}{g_{o1}} = \frac{V_{AF}}{V_t} \cong 8000$$



Circuit diagram of a common-emitter amplifier with a nonideal current source load. The input signal V_{IN} is applied to the base of transistor Q_1 . The emitter is connected to V_{EE} . The collector is connected to V_{CC} through a nonideal current source V_{YY} . The output voltage V_{OUT} is taken from the collector.

$$A_V \cong \frac{-g_{m1}}{2g_{o1}} = -4000$$

- Nonideal current source decreased the gain by a factor of 2
- But the voltage gain is still quite large (-4000)

Can the gain be made even larger?

End of Lecture 33