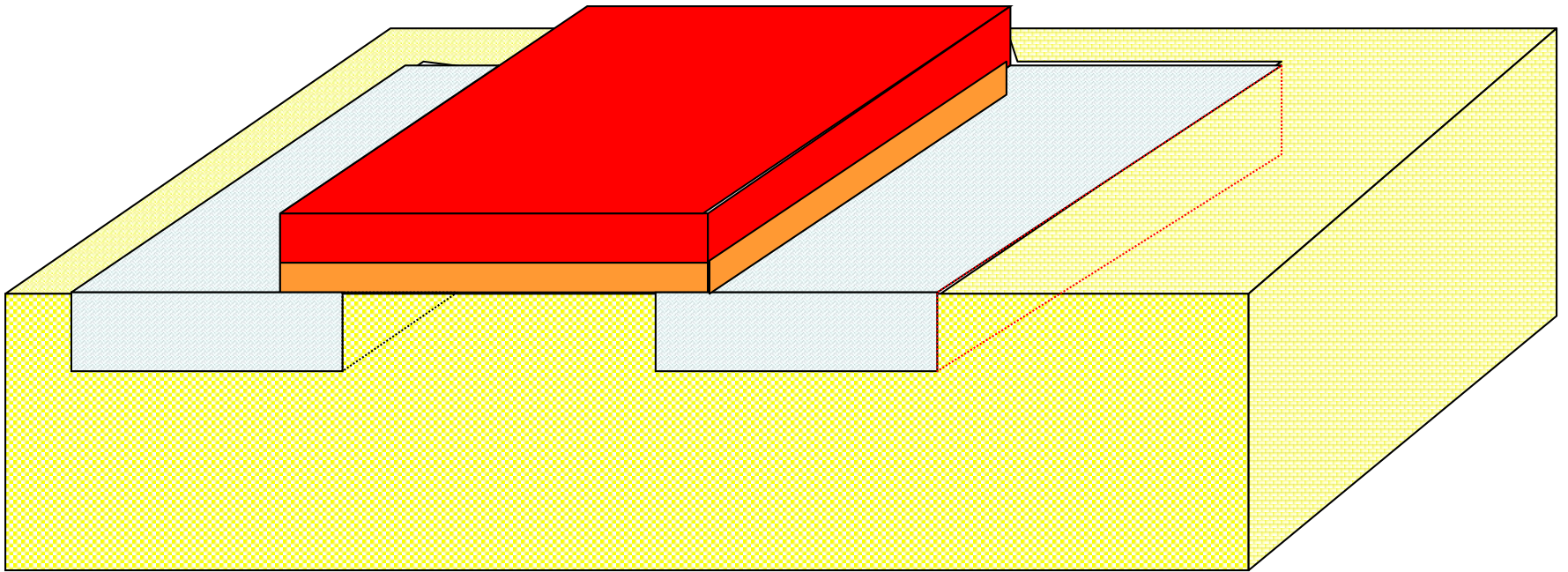


EE 330


Lecture 35

- Parasitic Capacitances in MOS Devices
- Digital Systems

Parasitic Capacitors in MOSFET




Parasitic Capacitors in MOSFET

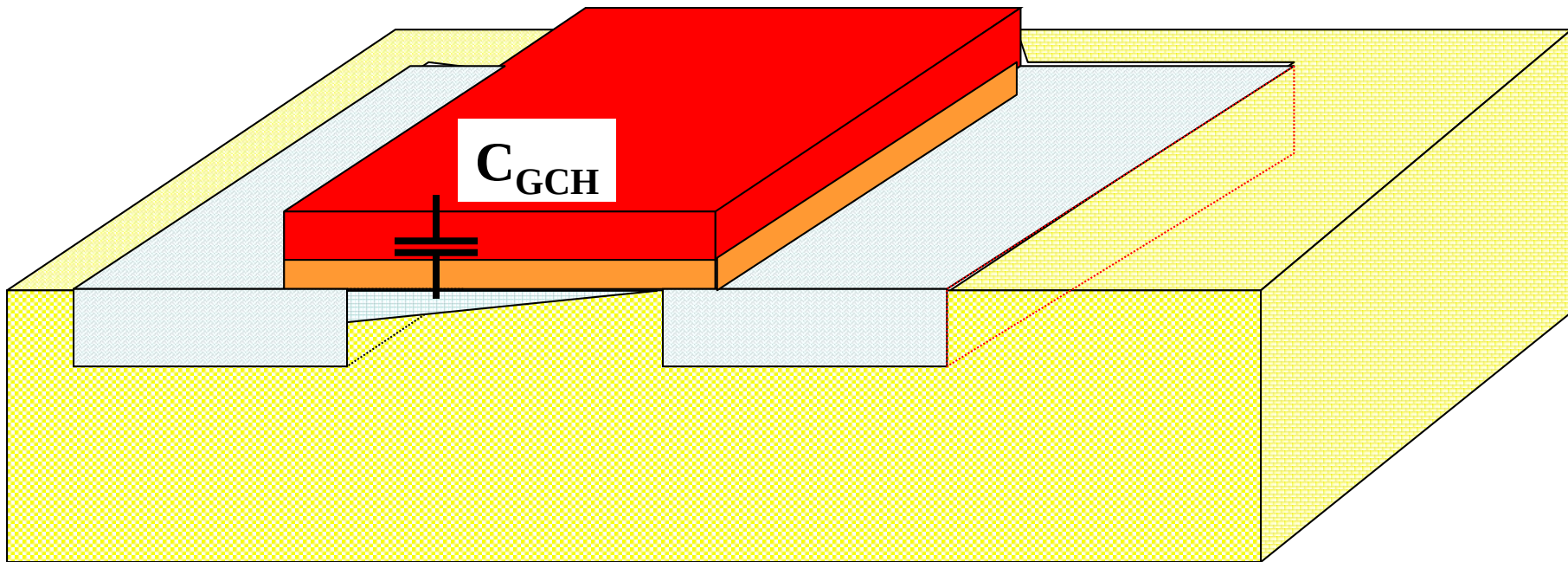


- This capacitance was modeled previously and exists when the transistor is operating in triode or saturation
- But there are others that also affect high-frequency or high-speed operation

Parasitic Capacitors in MOSFET




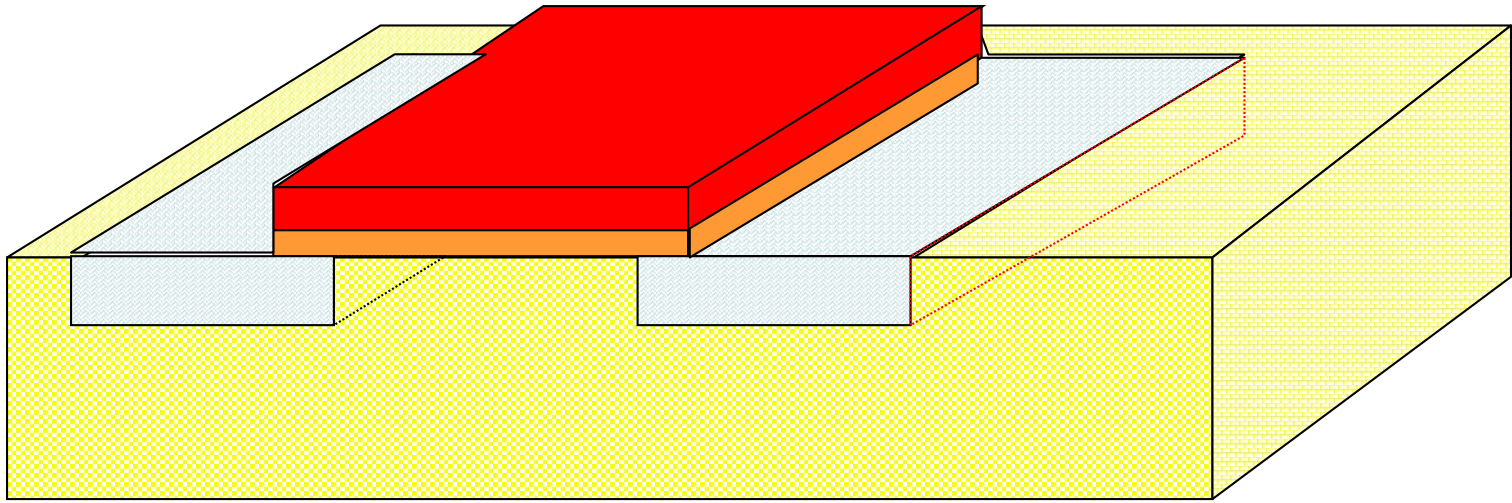


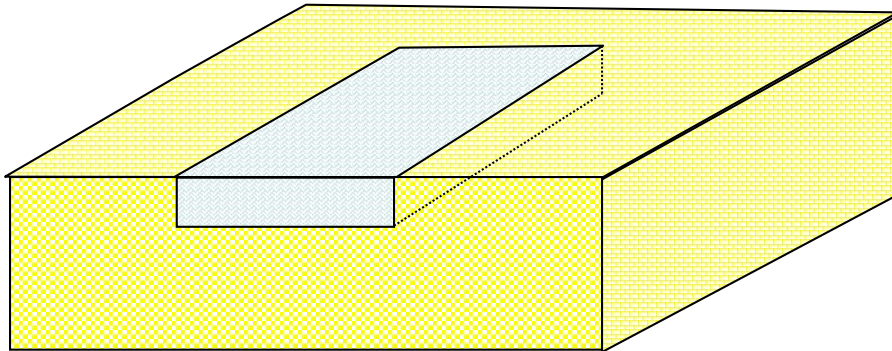Recall that pn junctions have a depletion region!




Parasitic Capacitors in MOSFET

pn junction capacitance

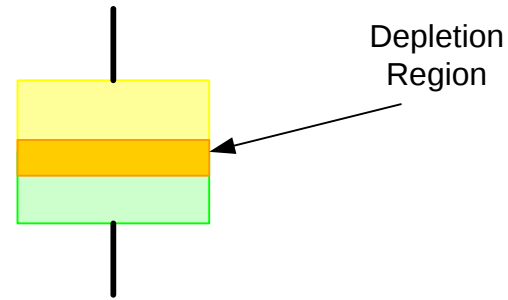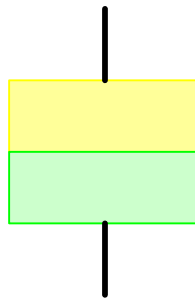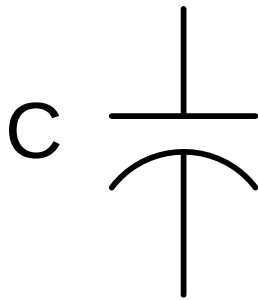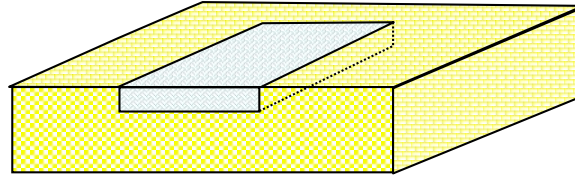


For $V_{FB} < \phi_B/2$

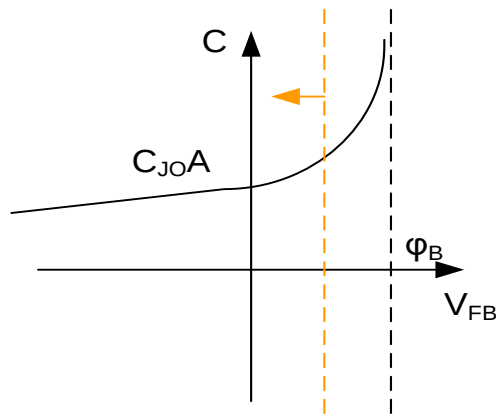

$$C = \frac{C_{JO} A}{\left(1 - \frac{V_{FB}}{\phi_B}\right)^m}$$

Parasitic Capacitors in MOSFET





pn junction capacitance

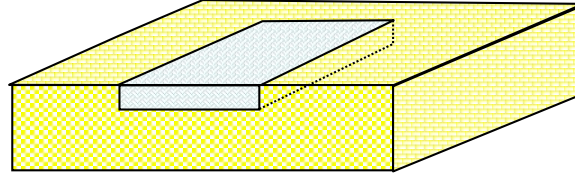

The bottom and the sidewall:

Parasitic Capacitors in MOSFET

pn junction capacitance

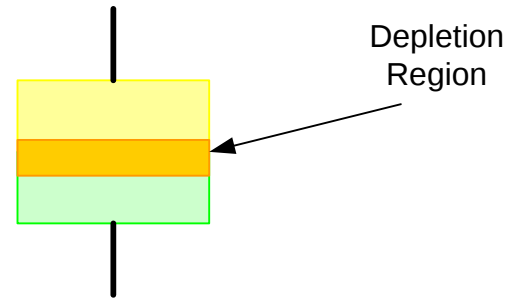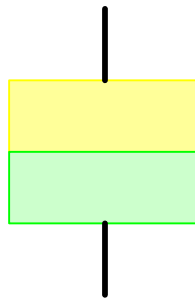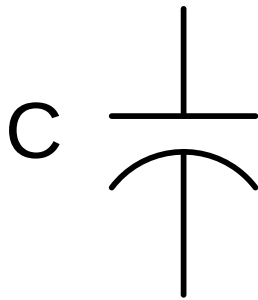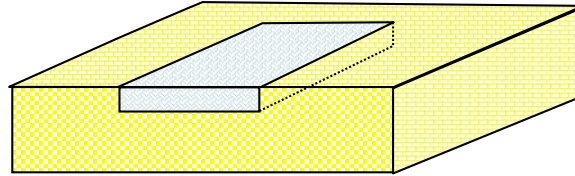

For a pn junction capacitor

$$C_J = C_{BOT} A + C_{SW} P$$

$$C_{BOT} = \frac{C_{BOT} A}{\left(1 - \frac{V_{FB}}{\phi_B}\right)^m}$$

$$C_{SW} = \frac{C_{SW} P}{\left(1 - \frac{V_{FB}}{\phi_B}\right)^m}$$

Types of Capacitors in MOSFETs

1. Fixed Capacitors




a. Fixed Geometry

b. Junction

2. Operating Region Dependent


Parasitic Capacitors in MOSFET

Fixed Capacitors – Fixed Geometry

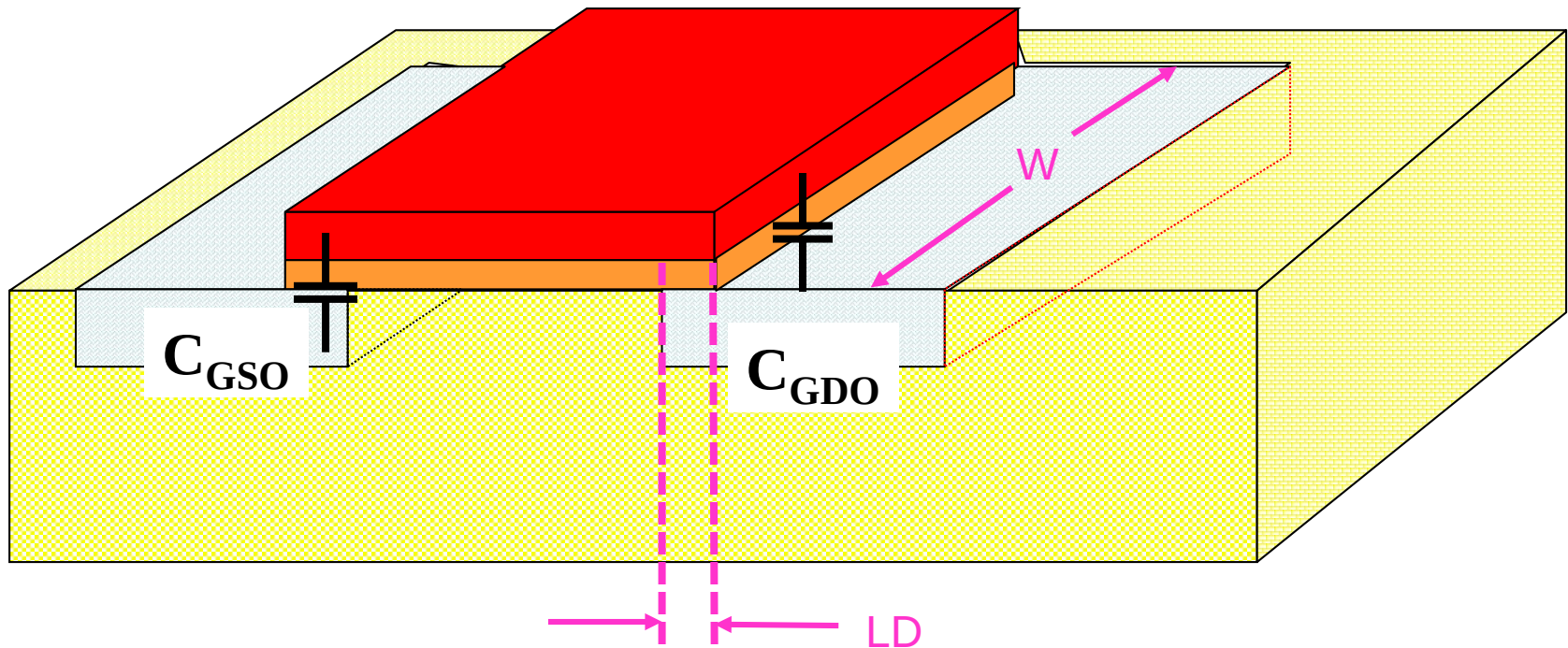

Overlap Capacitors: C_{GDO} , C_{GSO}

Parasitic Capacitance Summary

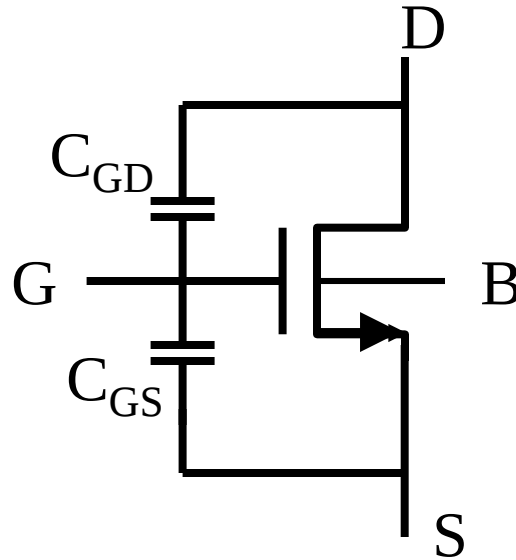

	Cutoff	Ohmic	Saturation
C_{GS}	$C_{ox}WL_D$	$C_{ox}WL_D$	$C_{ox}WL_D$
C_{GD}	$C_{ox}WL_D$	$C_{ox}WL_D$	$C_{ox}WL_D$

L_D is a model parameter

Overlap Capacitance Model Parameters

CAPACITANCE PARAMETERS	N+	P+	POLY	M1	M2	M3	M4	M5	M6	R_W	D_N_W	M5P	N_W	UNITS
Area (substrate)	942	1163	106	34	14	9	6	5	3			123	125	aF/ μm^2
Area (N+active)			8484	55	20	13	11	9	8					aF/ μm^2
Area (P+active)			8232											aF/ μm^2
Area (poly)				66	17	10	7	5	4					aF/ μm^2
Area (metal1)					37	14	9	6	5					aF/ μm^2
Area (metal2)						35	14	9	6					aF/ μm^2
Area (metal3)							37	14	9					aF/ μm^2
Area (metal4)								36	14					aF/ μm^2
Area (metal5)									34			984		aF/ μm^2
Area (r well)	920													aF/ μm^2
Area (d well)										582				aF/ μm^2
Area (no well)	137													aF/ μm^2
Fringe (substrate)	212	235		41	35	29	21	14						aF/ μm
Fringe (poly)				70	39	29	23	20	17					aF/ μm
Fringe (metal1)					52	34		22	19					aF/ μm
Fringe (metal2)						48	35	27	22					aF/ μm
Fringe (metal3)							53	34	27					aF/ μm
Fringe (metal4)								58	35					aF/ μm
Fringe (metal5)									55					aF/ μm
Overlap (N+active)			895											aF/ μm
Overlap (P+active)			737											aF/ μm


Types of Capacitors in MOSFETs

1. Fixed Capacitors
 - a. Fixed Geometry
 -  b. Junction

2. Operating Region Dependent

Parasitic Capacitors in MOSFET


Fixed Capacitors- Junction

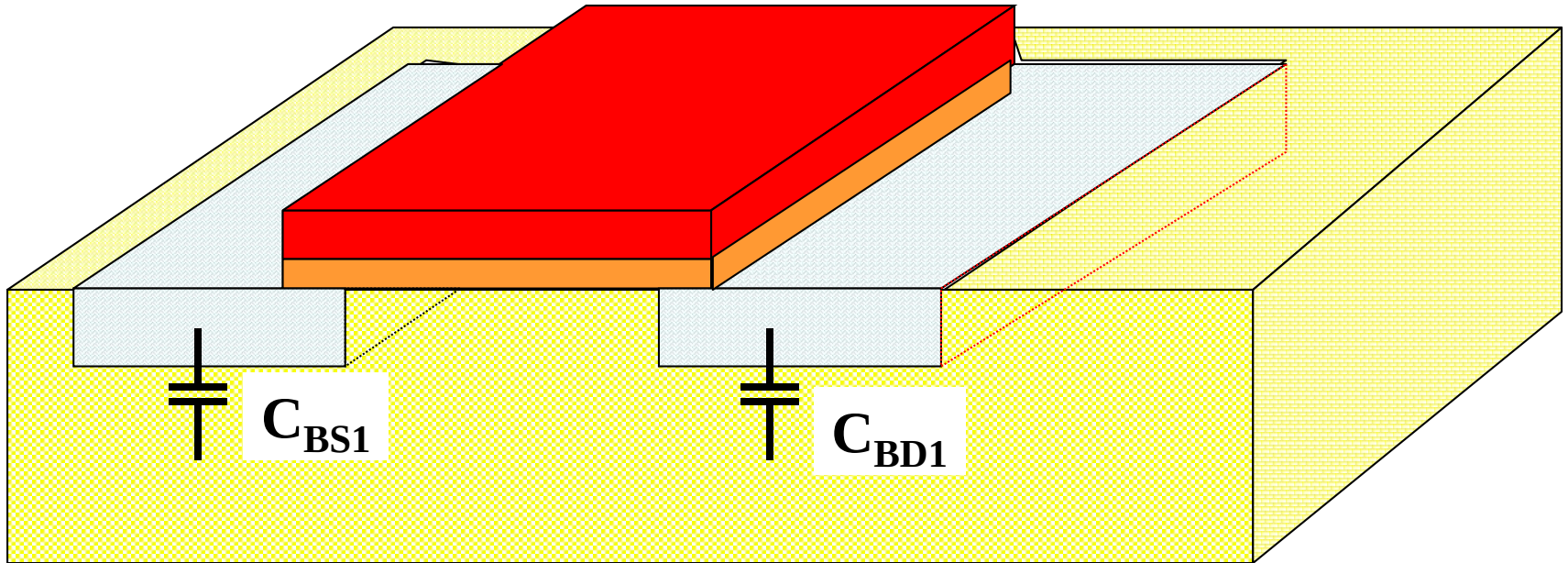

Junction Capacitors: C_{BS1} , C_{BD1}

Parasitic Capacitors in MOSFET


Fixed Capacitors

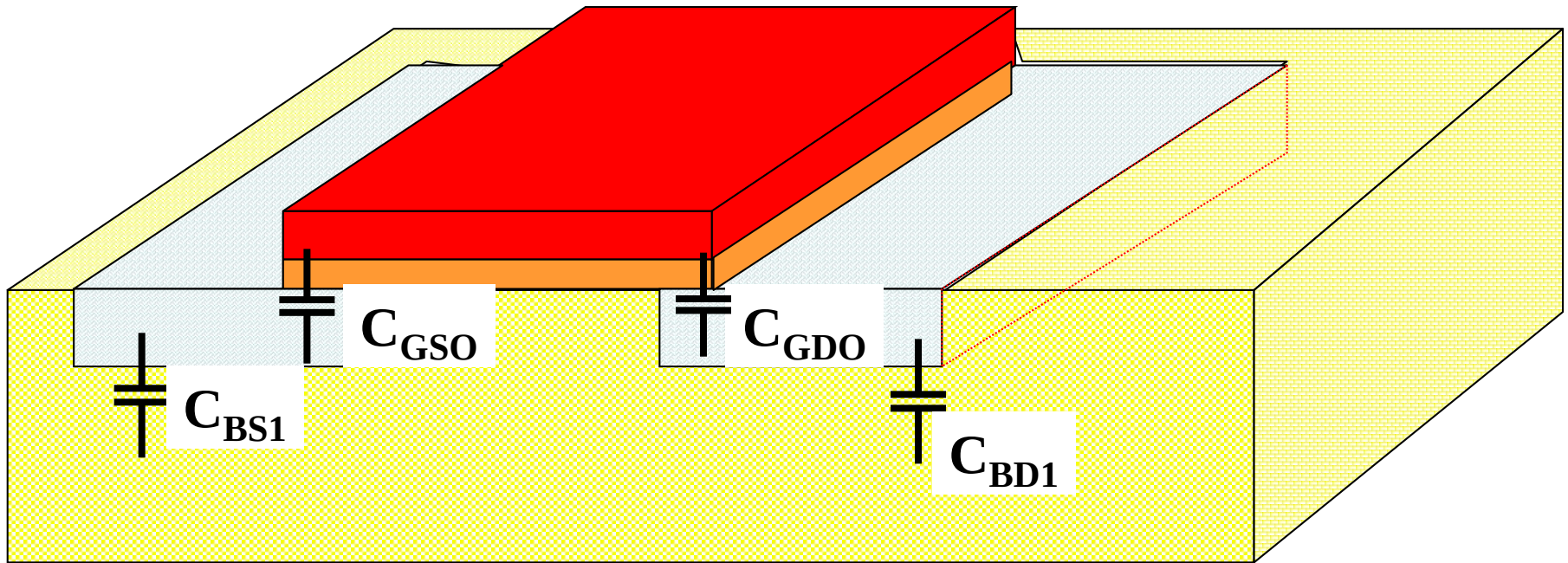

Overlap Capacitors: C_{GDO} , C_{GSO}

Junction Capacitors: C_{BS1} , C_{BD1}

Fixed Parasitic Capacitance Summary

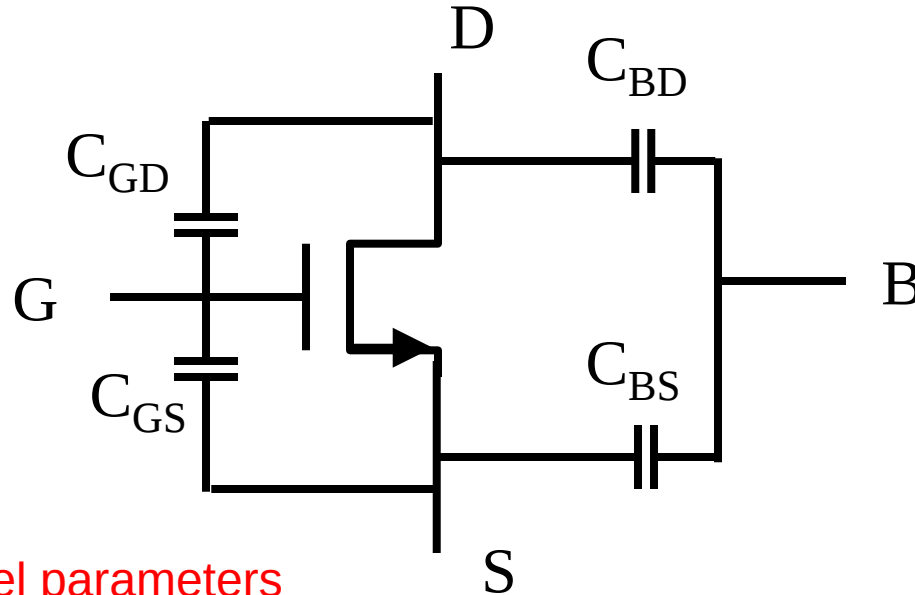

C_{BOT} and C_{SW} are model parameters

	Cutoff	Ohmic	Saturation
C_{GS}	$C_{ox}WL_D$	$C_{ox}WL_D$	$C_{ox}WL_D$
C_{GD}	$C_{ox}WL_D$	$C_{ox}WL_D$	$C_{ox}WL_D$
C_{BG}			
C_{BS}	$C_{BS1} = C_{BOT}A_S + C_{SW}P_S$	$C_{BS1} = C_{BOT}A_S + C_{SW}P_S$	$C_{BS1} = C_{BOT}A_S + C_{SW}P_S$
C_{BD}	$C_{BD1} = C_{BOT}A_D + C_{SW}P_D$	$C_{BD1} = C_{BOT}A_D + C_{SW}P_D$	$C_{BD1} = C_{BOT}A_D + C_{SW}P_D$

C_{BOT} and C_{SW} model parameters

CAPACITANCE PARAMETERS	N+	P+	POLY	M1	M2	M3	M4	M5	M6	R_W	D_N_W	M5P	N_W	UNITS
Area (substrate)	942	1163	106	34	14	9	6	5	3		123		125	aF/ μm^2
Area (N+active)			8484	55	20	13	11	9	8					aF/ μm^2
Area (P+active)			8232											aF/ μm^2
Area (poly)				66	17	10	7	5	4					aF/ μm^2
Area (metal1)					37	14	9	6	5					aF/ μm^2
Area (metal2)						35	14	9	6					aF/ μm^2
Area (metal3)							37	14	9					aF/ μm^2
Area (metal4)								36	14					aF/ μm^2
Area (metal5)								34				984		aF/ μm^2
Area (r well)	920													aF/ μm^2
Area (d well)										582				aF/ μm^2
Area (no well)	137													aF/ μm^2
Fringe (substrate)	212	235		41	35	29	21	14						aF/ μm
Fringe (poly)				70	39	29	23	20	17					aF/ μm
Fringe (metal1)					52	34		22	19					aF/ μm
Fringe (metal2)						48	35	27	22					aF/ μm
Fringe (metal3)							53	34	27					aF/ μm
Fringe (metal4)								58	35					aF/ μm
Fringe (metal5)									55					aF/ μm
Overlap (N+active)			895											aF/ μm
Overlap (P+active)			737											aF/ μm

Types of Capacitors in MOSFETs


1. Fixed Capacitors
 - a. Fixed Geometry
 - b. Junction



2. Operating Region Dependent

Parasitic Capacitors in MOSFET


Operation Region Dependent -- **Cutoff**

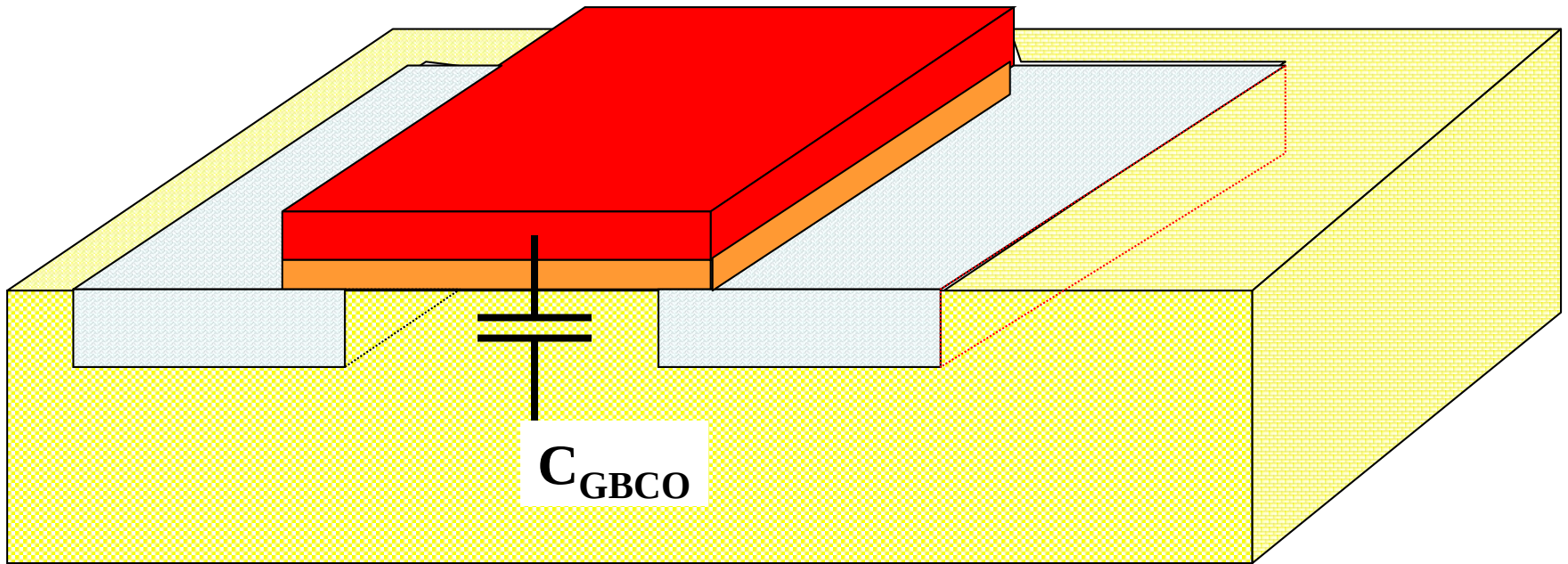

Cutoff Capacitor: C_{GBCO}

Parasitic Capacitors in MOSFET


Operation Region Dependent -- Cutoff

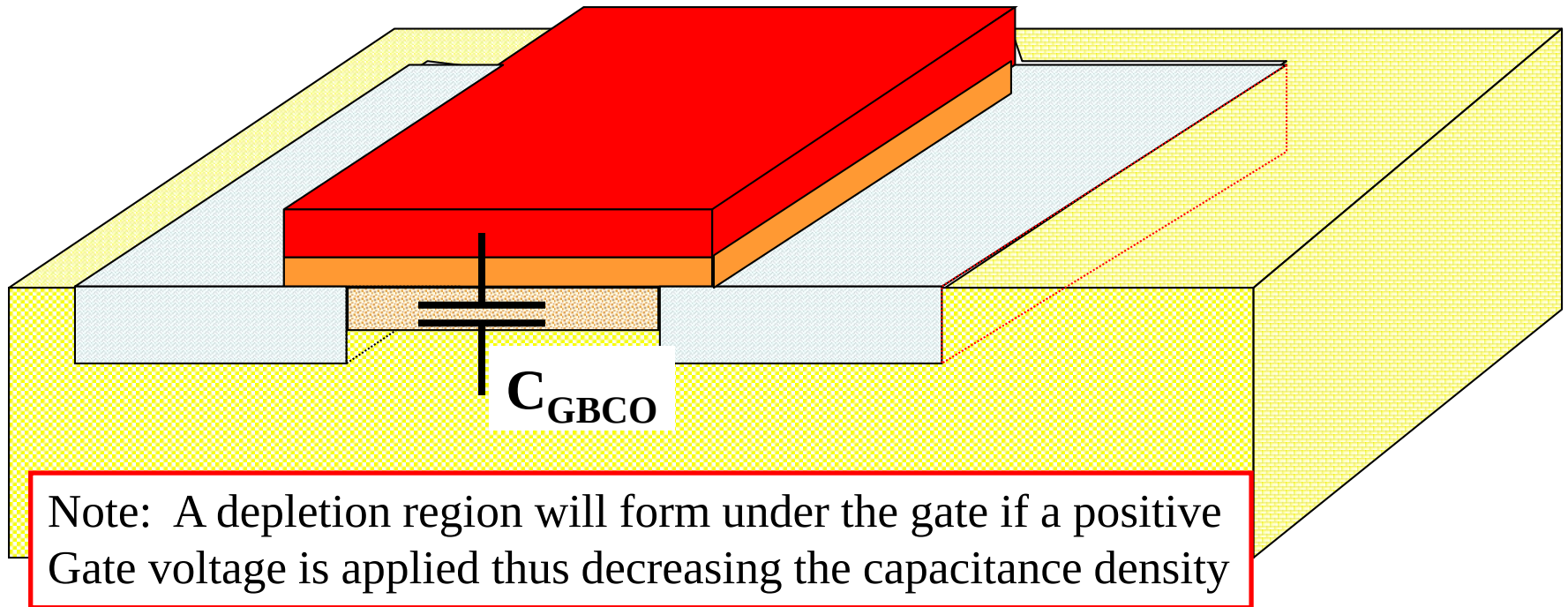

Cutoff Capacitor: C_{GBCO}

Parasitic Capacitors in MOSFET

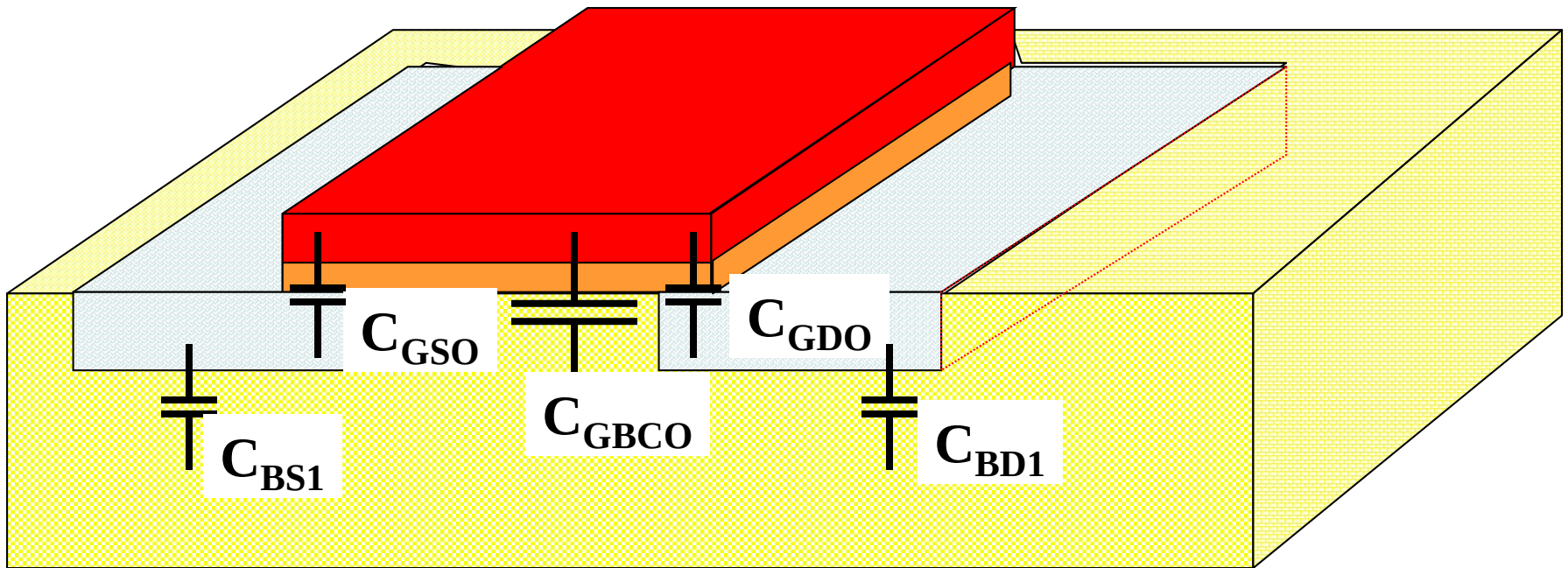Operation Region Dependent and Fixed -- Cutoff




Overlap Capacitors: C_{GDO} , C_{GSO}

Junction Capacitors: C_{BS1} , C_{BD1}

Cutoff Capacitor: C_{GBCO}


Parasitic Capacitance Summary

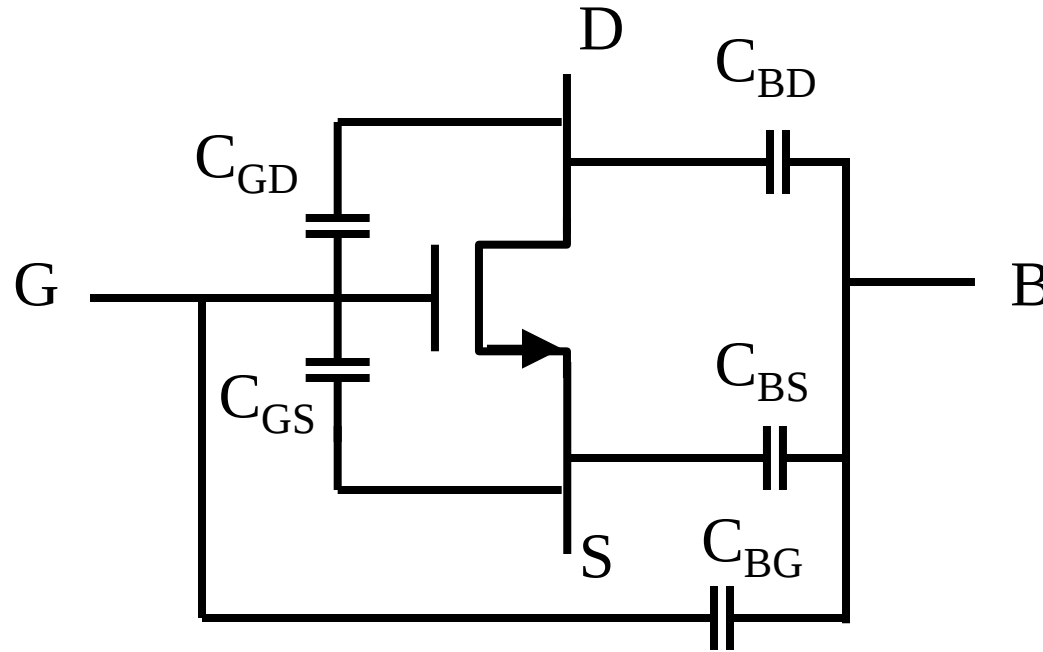

	Cutoff	Ohmic	Saturation
C_{GS}	$C_{ox}W L_D$		
C_{GD}	$C_{ox}W L_D$		
C_{BG}	$C_{ox}W L$ (or less)		
C_{BS}	$C_{BOT}A_S + C_{SW}P_S$		
C_{BD}	$C_{BOT}A_D + C_{SW}P_D$		

Parasitic Capacitors in MOSFET

Operation Region Dependent -- Ohmic

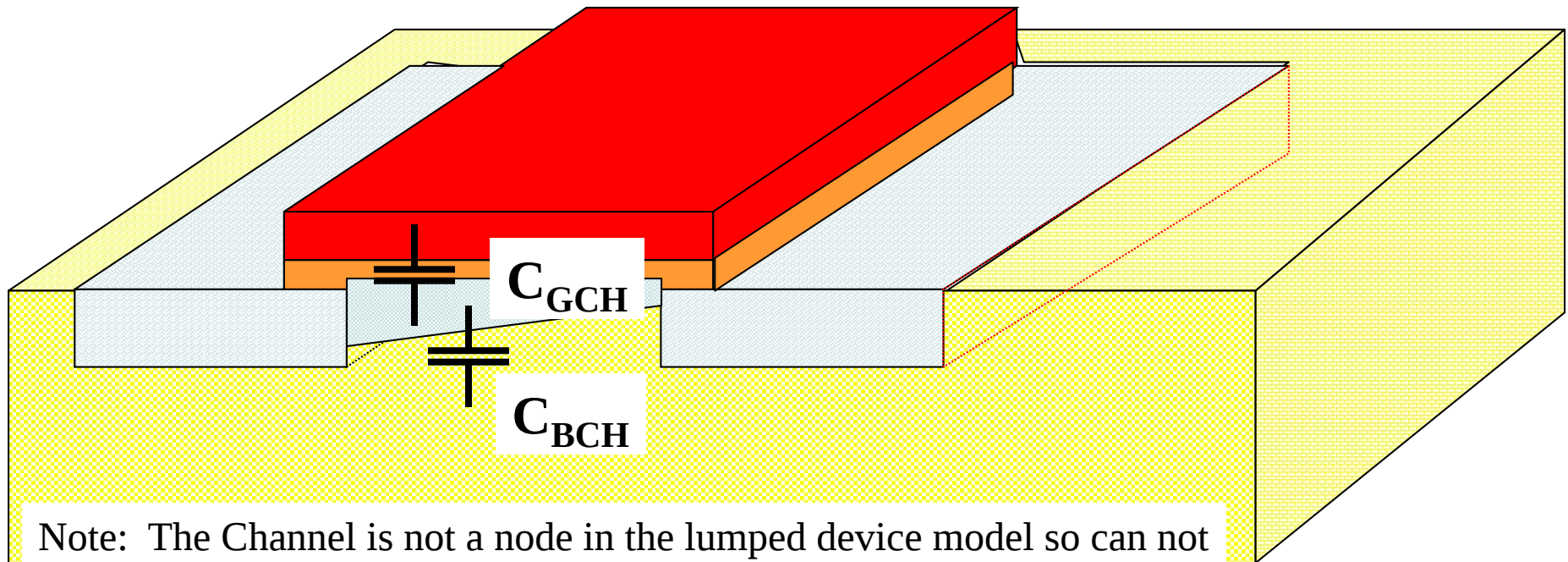


Note: The Channel is not a node in the lumped device model so can not directly include this distributed capacitance in existing models

Note: The distributed channel capacitance is usually lumped and split evenly between the source and drain nodes

Ohmic Capacitor: C_{GCH} , C_{BCH}

Parasitic Capacitors in MOSFET

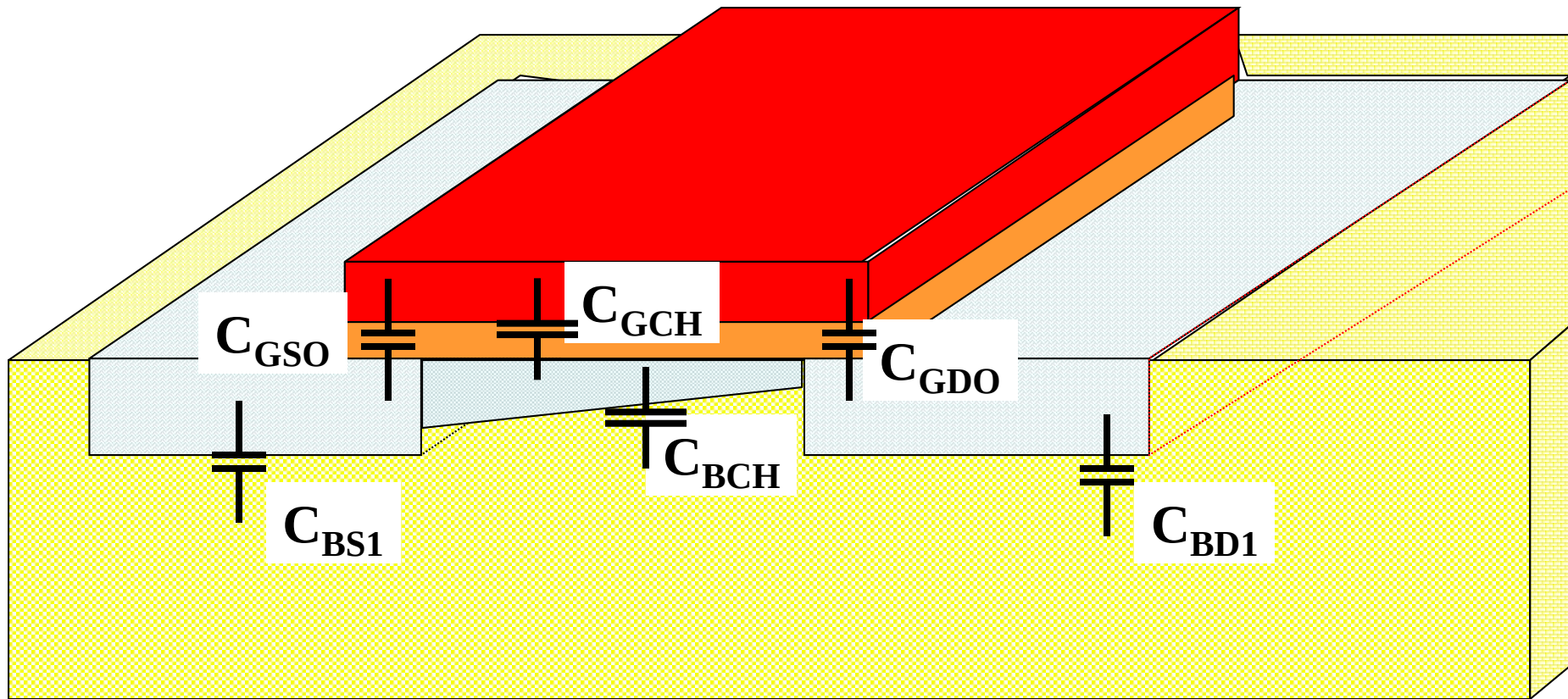Operation Region Dependent and Fixed -- Ohmic




Overlap Capacitors: C_{GDO} , C_{GSO}

Junction Capacitors: C_{BS1} , C_{BD1}

Ohmic Capacitor: C_{GCH} , C_{BCH}


Parasitic Capacitance Summary

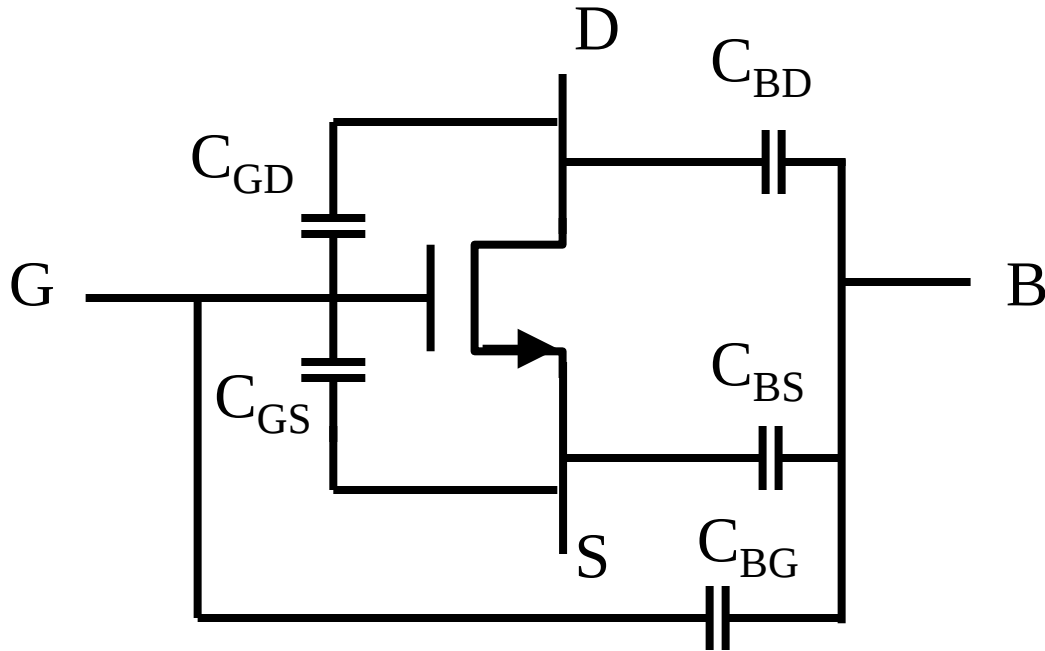

	Cutoff	Ohmic	Saturation
C_{GS}	$C_{ox}W L_D$	$C_{ox}W L_D$	
C_{GD}	$C_{ox}W L_D$	$C_{ox}W L_D$	
C_{BG}	$C_{ox}W L$ (or less)	0	
C_{BS}	$C_{BOT}A_S + C_{SW}P_S$	$C_{BS1} = C_{BOT}A_S + C_{SW}P_S$	
C_{BD}	$C_{BOT}A_D + C_{SW}P_D$	$C_{BD1} = C_{BOT}A_D + C_{SW}P_D$	

Parasitic Capacitors in MOSFET

Operation Region Dependent -- Saturation

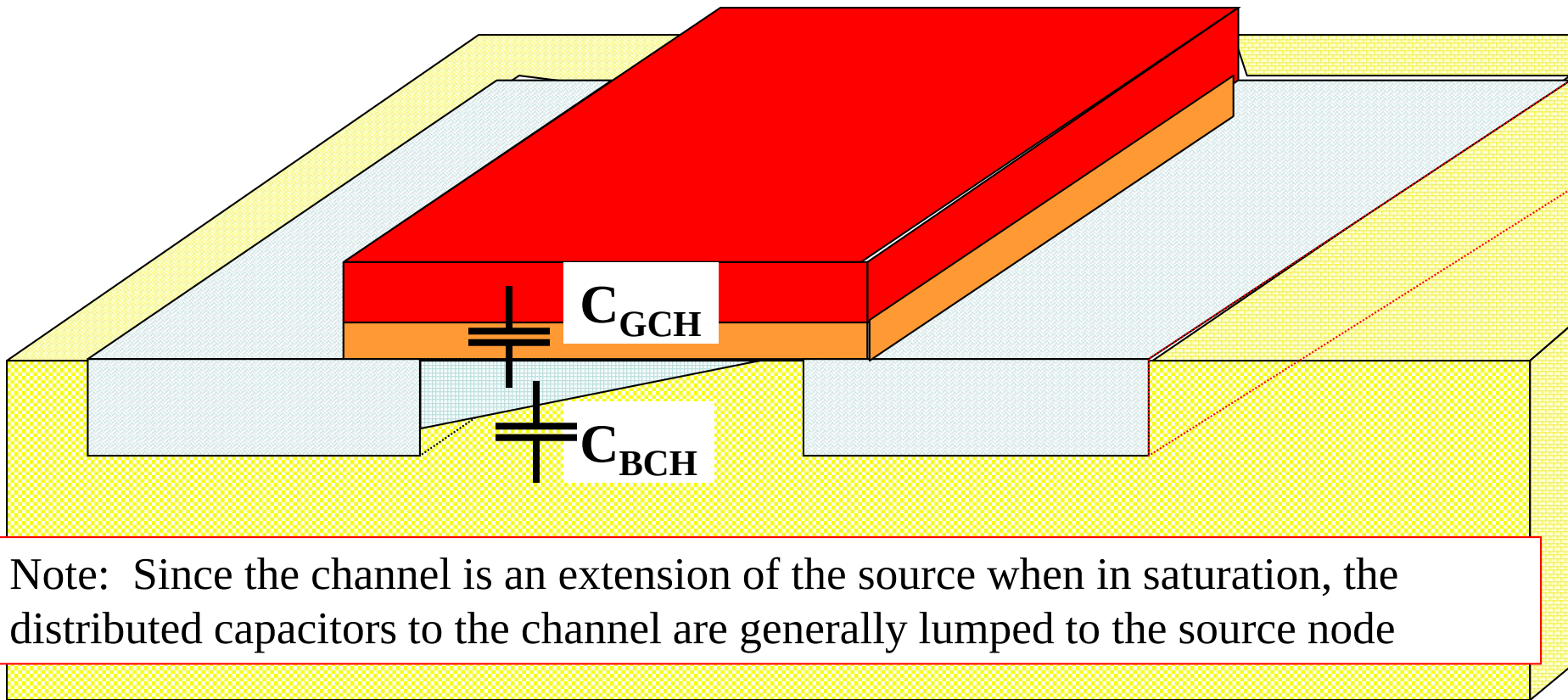


Note: Since the channel is an extension of the source when in saturation, the distributed capacitors to the channel are generally lumped to the source node

Saturation Capacitors: C_{GCH} , C_{BCH}

Parasitic Capacitors in MOSFET

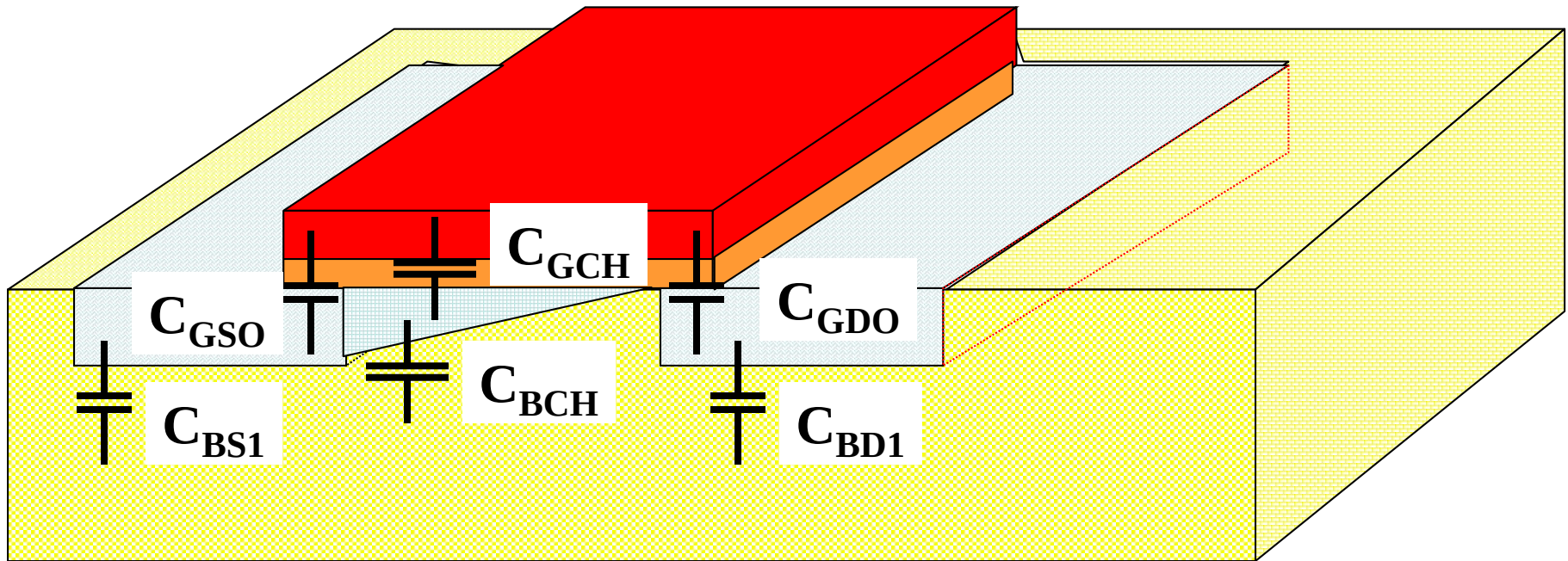Operation Region Dependent and Fixed --Saturation




Overlap Capacitors: C_{GDO} , C_{GSO}

Junction Capacitors: C_{BS1} , C_{BD1}

Saturation Capacitors: C_{GCH} , C_{BCH}


- $2/3 C_{OX}WL$ is often attributed to C_{GCH} to account for LD and saturation
- This approximation is reasonable for minimum-length devices but not so good for longer devices

Parasitic Capacitance Summary

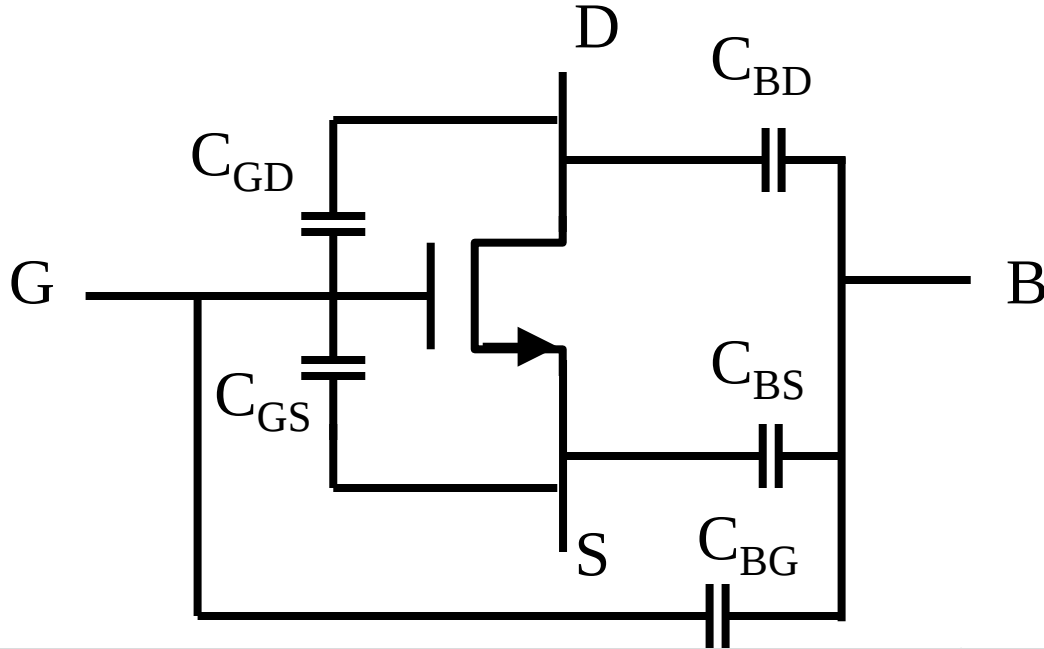

	Cutoff	Ohmic	Saturation
C_{GS}	$C_{ox}W L_D$	$C_{ox}W L_D + 0.5C_{ox}WL$	$C_{ox}W L_D + (2/3)C_{ox}WL$
C_{GD}	$C_{ox}W L_D$	$C_{ox}W L_D + 0.5C_{ox}WL$	$C_{ox}W L_D$
C_{BG}	$C_{ox}WL$ (or less)	0	0
C_{BS}	$C_{BOT}A_S + C_{SW}P_S$	$C_{BOT}A_S + C_{SW}P_S + 0.5WLC_{BOTCH}$	$C_{BOT}A_S + C_{SW}P_S + (2/3)WLC_{BOTCH}$
C_{BD}	$C_{BOT}A_D + C_{SW}P_D$	$C_{BOT}A_D + C_{SW}P_D + 0.5WLC_{BOTCH}$	$C_{BOT}A_D + C_{SW}P_D$








Parasitic Capacitance Summary

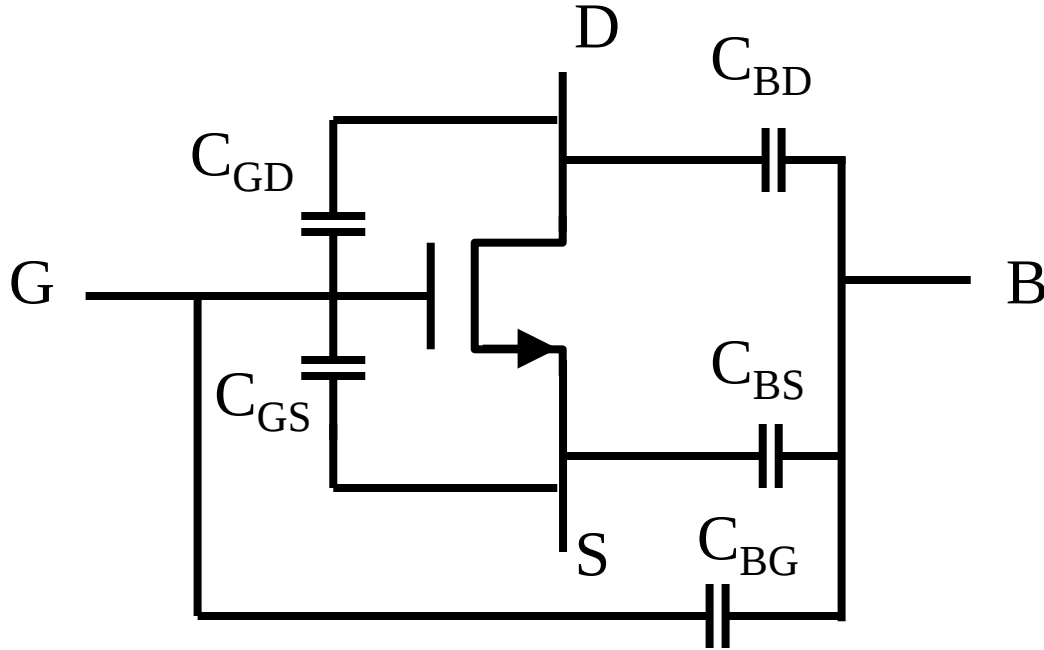

	Cutoff	Ohmic	Saturation
C_{GS}	$C_{ox}W L_D$	$C_{ox}W L_D + 0.5C_{ox}WL$	$C_{ox}W L_D + (2/3)C_{ox}WL$
C_{GD}	$C_{ox}W L_D$	$C_{ox}W L_D + 0.5C_{ox}WL$	$C_{ox}W L_D$
C_{BG}	$C_{ox}WL$ (or less)	0	0
C_{BS}	$C_{BOT}A_S + C_{SW}P_S$	$C_{BOT}A_S + C_{SW}P_S + 0.5WLC_{BOTCH}$	$C_{BOT}A_S + C_{SW}P_S + (2/3)WLC_{BOTCH}$
C_{BD}	$C_{BOT}A_D + C_{SW}P_D$	$C_{BOT}A_D + C_{SW}P_D + 0.5WLC_{BOTCH}$	$C_{BOT}A_D + C_{SW}P_D$

Recall:


Small-signal and simplified dc equivalent elements

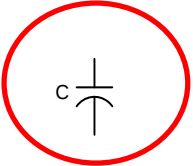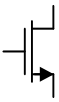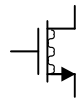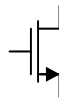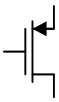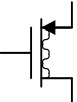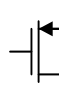	Element	ss equivalent	Simplified dc equivalent
Capacitors	C Large		
	C Small		
Inductors	L Large		
	L Small		
Diodes			 Simplified
MOS transistors (MOSFET (enhancement or depletion), JFET)			 Simplified
			 Simplified


Have not yet considered situations where the small capacitor is relevant in small-signal analysis

Amplifiers with Small Capacitors

Recall:

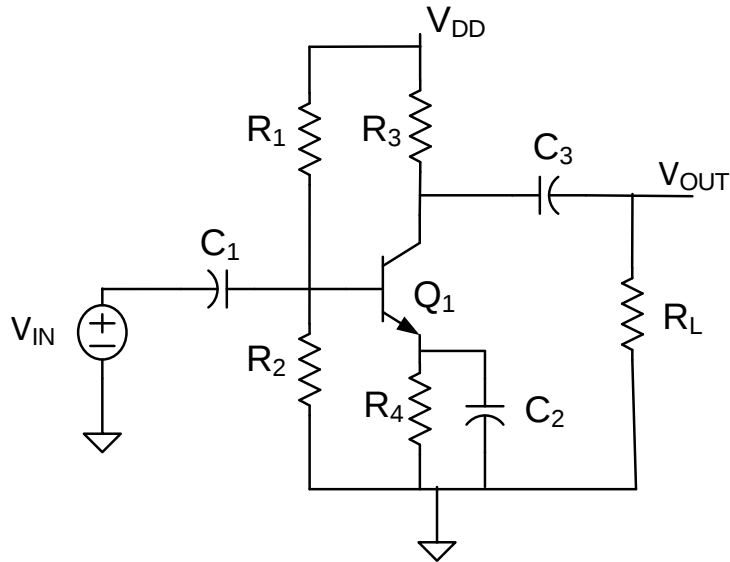




If capacitors are large

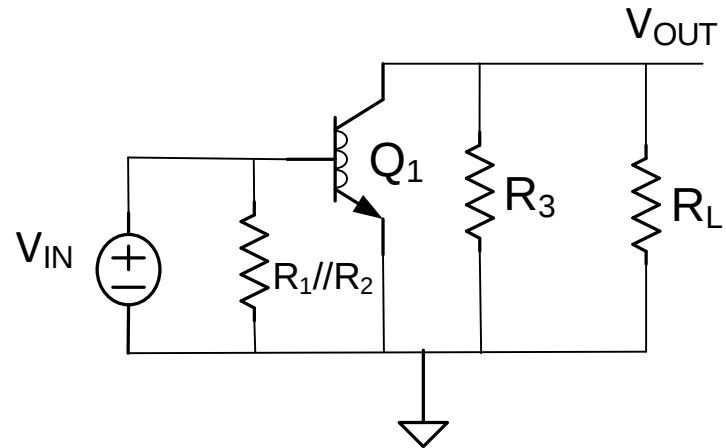

$$A_V = -g_{m1} \bullet R_3 // R_L$$


Amplifiers with Small Capacitors

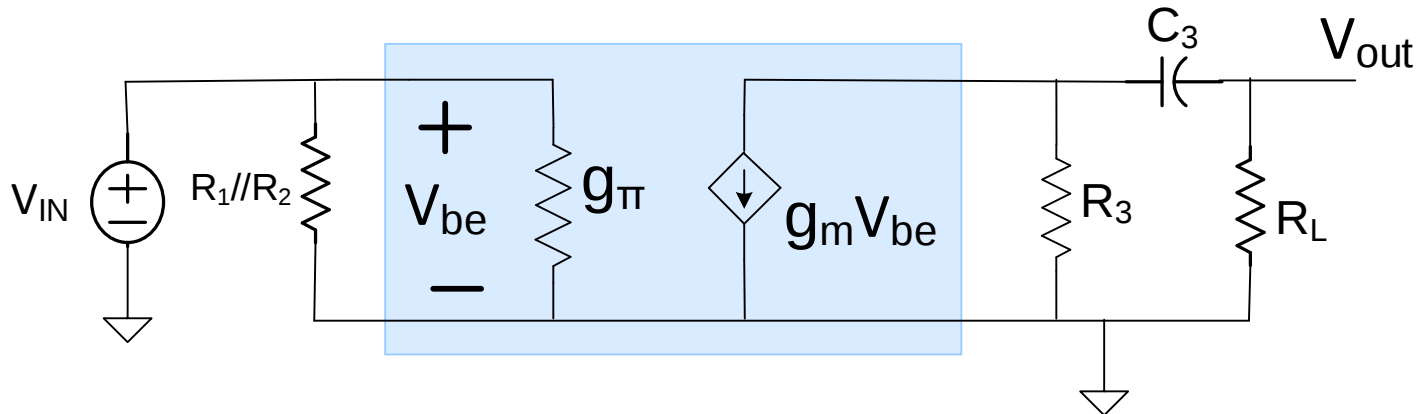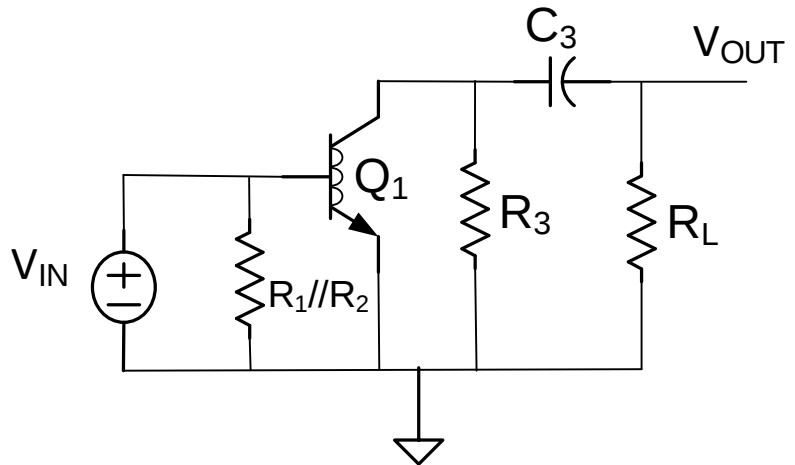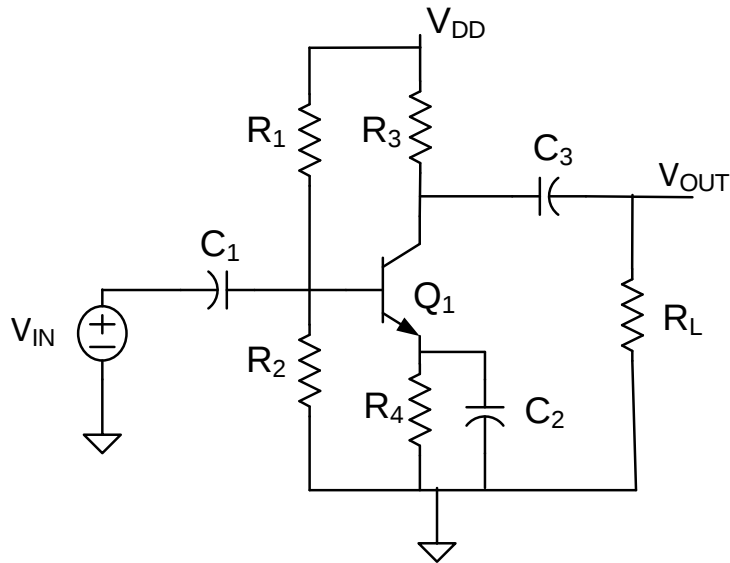What if C_1 and C_2 large but C_3 not large?:



Amplifiers with Small Capacitors

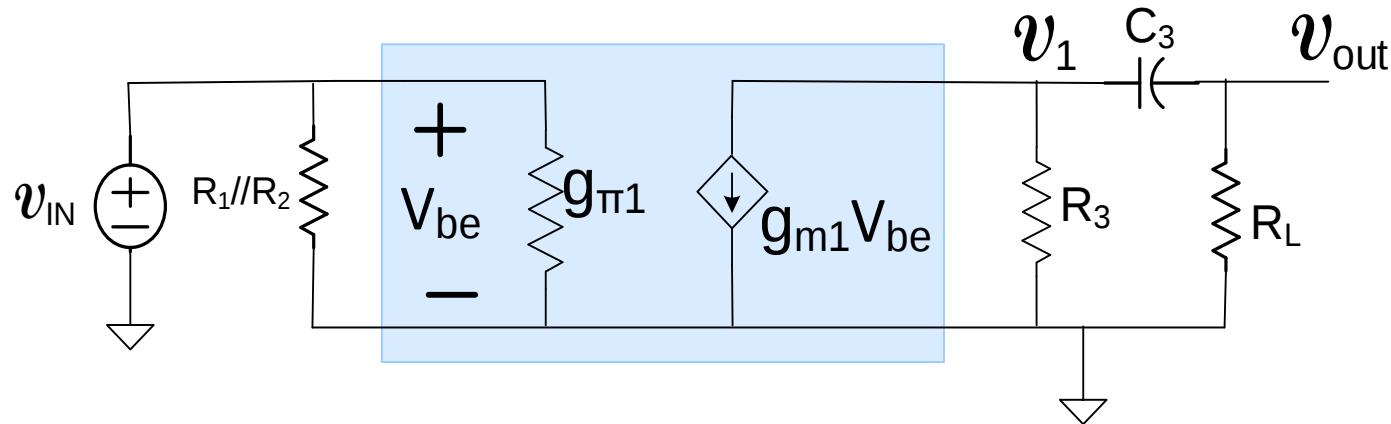What if C_1 and C_2 large but C_3 not large?:



From KCL:

$$\left. \begin{aligned} v_{OUT}(sC_3 + G_L) &= v_1 sC_3 \\ v_1(sC_3 + G_3) + g_{m1}v_{IN} &= v_{OUT} sC_3 \end{aligned} \right\}$$


Solving:

$$\frac{v_{OUT}}{v_{IN}} = -\frac{-sC_3 g_{m1}}{sC_3(G_L + G_3) + G_3 G_L}$$

Equivalently:



$$\frac{v_{OUT}}{v_{IN}} = -\frac{g_{m1} sC_3 R_3 R_L}{sC_3(R_L + R_3) + 1}$$

Serves as a first-order high-pass filter

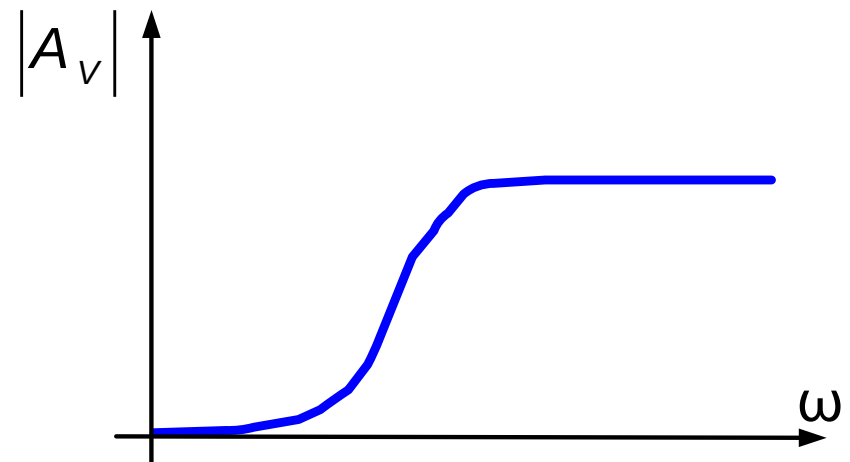

Amplifiers with Small Capacitors

Consider parasitic C_{DB}

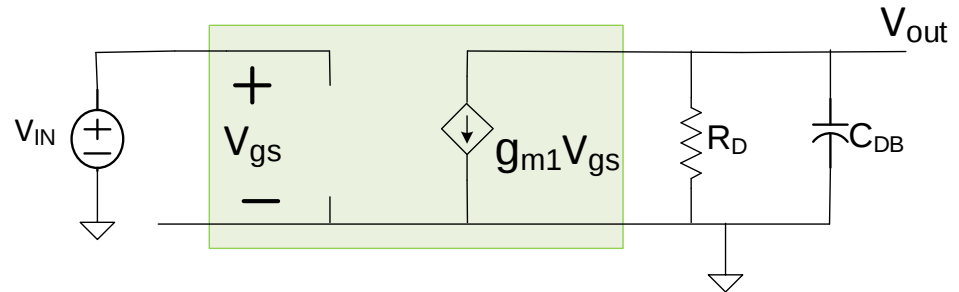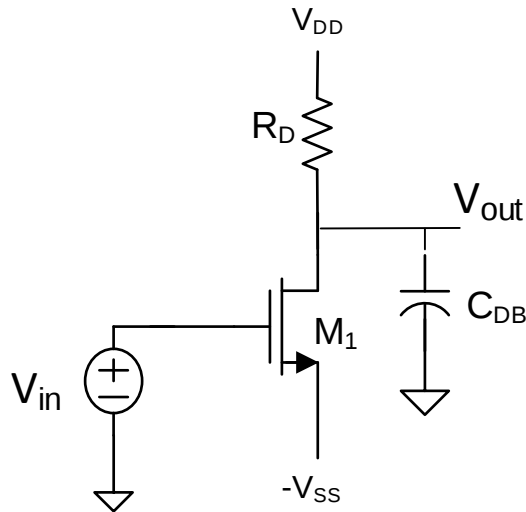

By KCL:

$$v_{OUT}(sC_{DB} + G_D) = -g_{m1}v_{IN}$$


Causes gain to decrease at high frequencies

Solving:

$$\frac{v_{OUT}}{v_{IN}} = -\frac{g_{m1}}{sC_{DB} + G_D}$$



Equivalently:
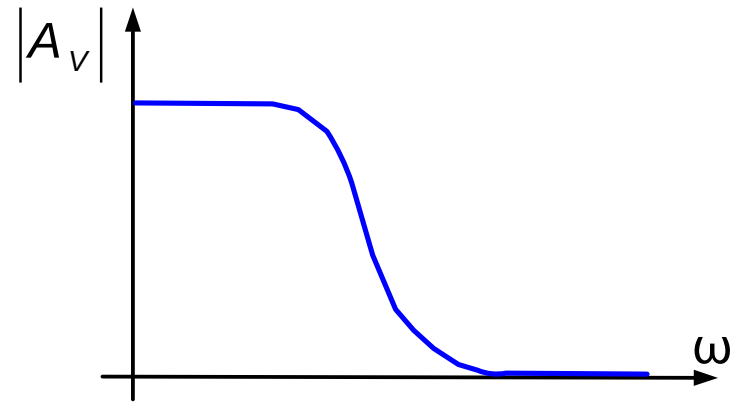
$$\frac{v_{OUT}}{v_{IN}} = -\frac{g_{m1}R_D}{sC_{DB}R_D + 1}$$



Amplifiers with Small Capacitors

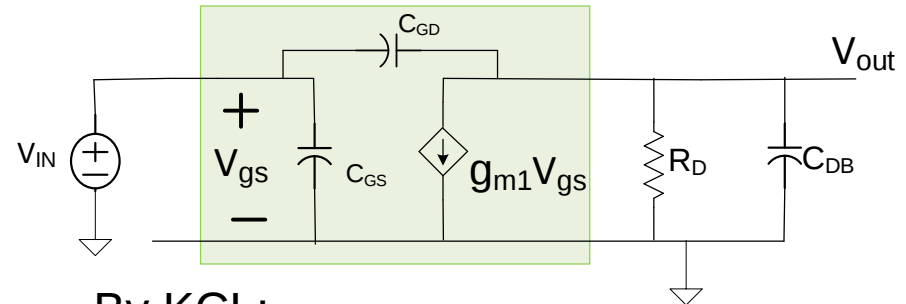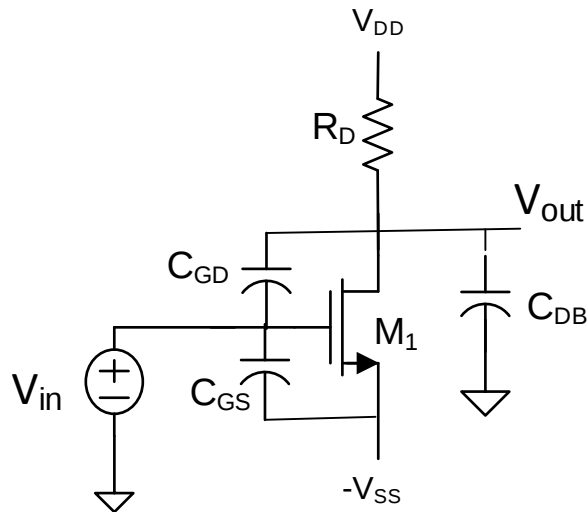Consider parasitic C_{GS} , C_{GD} , and C_{DB}



By KCL:

$$v_{OUT} (s[C_{DB} + C_{GD}] + G_D) = -g_{m1} v_{IN} + sC_{GD} v_{IN}$$


Causes gain to decrease at high frequencies
Has one LHP pole and one RHP zero

Solving:

$$\frac{v_{OUT}}{v_{IN}} = -\frac{-g_{m1} + sC_{GD}}{s[C_{DB} + C_{GD}] + G_D}$$


Equivalently:
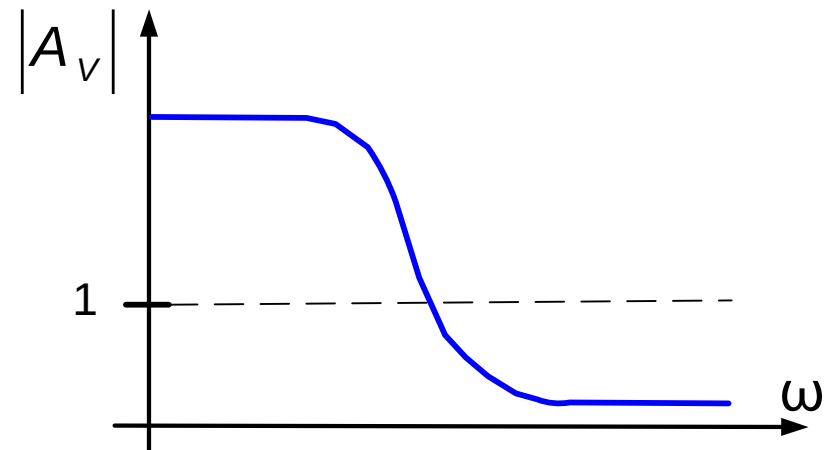
$$\frac{v_{OUT}}{v_{IN}} = -\frac{-R_D (g_{m1} - sC_{GD})}{s[C_{DB} + C_{GD}]R_D + 1}$$



Amplifiers with Small Capacitors

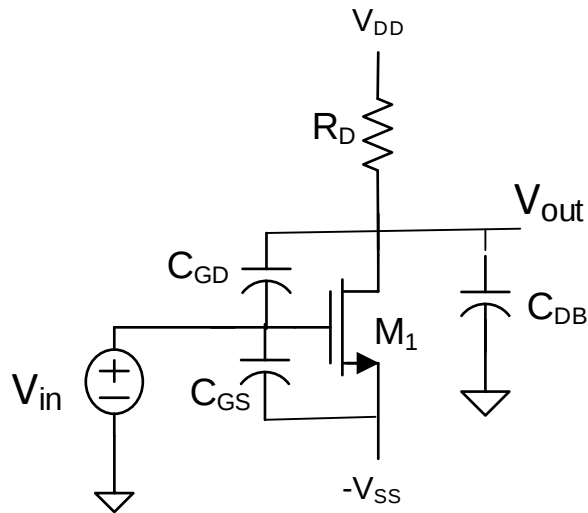Consider parasitic C_{GS} , C_{GD} , and C_{DB}



Device parasitics problematic at high frequencies

C_{DB} , C_{GD} and C_{GS} effects can be significant

Value of parasitic capacitances strongly dependent upon layout

Device parasitics usually not a problem at audio frequencies

Causes gain to decrease at high frequencies:
has one high frequency LHP pole and one high frequency RHP zero.

End of Lecture 35