

EE 330

Lecture 6


- Pass Transistor Logic
- Improved Switch-Level Model
- Propagation Delay

Pass Transistor Logic

- Improved Switch-Level Model
- Propagation Delay
- Stick Diagrams
- Technology Files

Consider $Y = A \bullet B$

Standard CMOS Implementation

 


2 levels of Logic

6 Transistors if Basic CMOS Gates are Used

Basic noninverting functions generally require more complexity if basic CMOS gates are used for implementation


Pass Transistor Logic

 

$$Y = A \bullet B$$

Requires only 2 transistors rather than 6 for a standard CMOS gate (and a resistor).

Pass Transistor Logic

 

Even simpler pass transistor logic implementations are possible


Requires only 1 transistor (and a resistor).



Will see later that the area of a single practical resistor for this circuit may be comparable to that needed for hundreds or even thousands of transistors




Pass Transistor Logic

 

- May be able to replace resistor with transistor (one of several ways shown)
- But high logic level can not be determined with existing device model (or even low logic level for circuit on right)
- Power dissipation can not be determined with existing device model for circuit on right

Better device model is needed (Power? Signal Swing? Speed?)

Pass Transistor Logic

 


$$Y = A \oplus B$$


6 transistors, 1 resistor, two levels of logic

(the 4 transistors in the two inverters are not shown)

Pass Transistor Logic

 


$$Y = A \oplus B$$

 

$$Y = A \oplus B$$

2 transistors, 1 resistor, one level of logic

Pass Transistor Logic

 

$$Y = A \cdot B$$

Requires only 1 transistor (and a resistor)

- Pass transistor logic can offer significant reductions in complexity for some functions (particularly noninverting)
- Resistor may require more area than several hundred or even several thousand transistors
- Signal levels may not go to V_{DD} or to 0V
- Static power dissipation may not be zero
- Signals may degrade unacceptably if multiple gates are cascaded
- “resistor” often implemented with a transistor to reduce area but signal swing and power dissipation problems still persist
- Pass transistor logic is widely used

Logic Design Styles

- Several different logic design styles are often used throughout a given design (3 considered thus far)
 - Static CMOS
 - Complex Logic Gates
 - Pass Transistor Logic
- The designer has complete control over what is placed on silicon and governed only by cost and performance
- New logic design strategies have been proposed recently and others will likely emerge in the future
- The digital designer needs to be familiar with the benefits and limitations of varying logic styles to come up with a good solution for given system requirements

- Pass Transistor Logic
- Improved Switch-Level Model
- Propagation Delay
- Stick Diagrams
- Technology Files


MOSFET Modeling



- Simple model of MOSFET was developed (termed switch-level model)
- Simple gates designed in CMOS Process were introduced
 - Some have zero power dissipation
 - Some have or appeared to have rail to rail logic voltage swings
 - All appeared to be Infinitely fast
 - Logic levels of some can not be predicted with simple model
 - Simple model is not sufficiently accurate to provide insight relating to some of these properties
- MOSFET modeling strategy
 - hierarchical model structure will be developed
 - generally use simplest model that can be justified

MOS Transistor Models

1, Switch-Level model

 


Advantages:

Simple, does not require understanding of semiconductor properties, does not depend upon process, adequate for understanding basic operation of many digital circuits

Limitations:

Does not provide timing information (surfaced when looking at static CMOS circuits, and several others that have not yet become apparent from the applications that have been considered) and can not support design of “resistor” used in Pass Transistor Logic

Improved Device Models

 

With the simple switch-level model, it was observed that basic static CMOS logic gates have the following three properties:

- Rail to rail logic swings
- Zero static power dissipation in both $Y=1$ and $Y=0$ states
- Arbitrarily fast (too good to be true? will consider again with better model)

It can be shown that the first two properties are nearly satisfied in actual fabricated circuits with p-channel/n-channel PU/PD logic but though the circuits are fast, they are observably not arbitrarily fast





None of these properties are observed for some logic styles such as Pass Transistor Logic

Will now extend switch-level model to predict speed of basic gates in static CMOS and logic levels and power dissipation in PTL

Recall

MOS Transistor

  
 
 
Qualitative Discussion of n-channel Operation



This was the first model introduced and was termed the basic switch-level mode

MOS Transistor

   Qualitative Discussion of n-channel Operation



Conceptual view of basic switch-level model


Qualitative Discussion of n-channel Operation



A cross-sectional diagram of a MOSFET structure. The substrate is a yellow rectangle labeled "Resistor". On top of the substrate, there are three green rectangular regions representing the "Source", "Gate", and "Drain" electrodes. The "Gate" region is the central one. Above the "Gate" region, there is a red rectangular layer labeled "Insulator". A blue arrow points from the "Insulator" label to this red layer. Another blue arrow points from the "Resistor" label to the yellow substrate. A black dot labeled "Bulk" is connected to the "Source" region by a black line.

n-channel MOSFET

 
- Region under gate termed the “channel”
- When “resistor” is electrically created, it is termed an “inversion region”



MOSFET actually 4-terminal device


MOS Transistor

 Qualitative Discussion of n-channel Operation



n-channel MOSFET


For V_{GS} small

 

n-channel MOSFET


For V_{GS} large

 - Electrically created inversion layer forms a “thin “film” resistor
- Capacitance from gate to channel region is distributed
- Lumped capacitance much easier to work with




Discrete Resistors often use thin films too though not electrically created


- Thin-film spiral wound

 

- Carbon composition



 


Improved Switch-Level Model



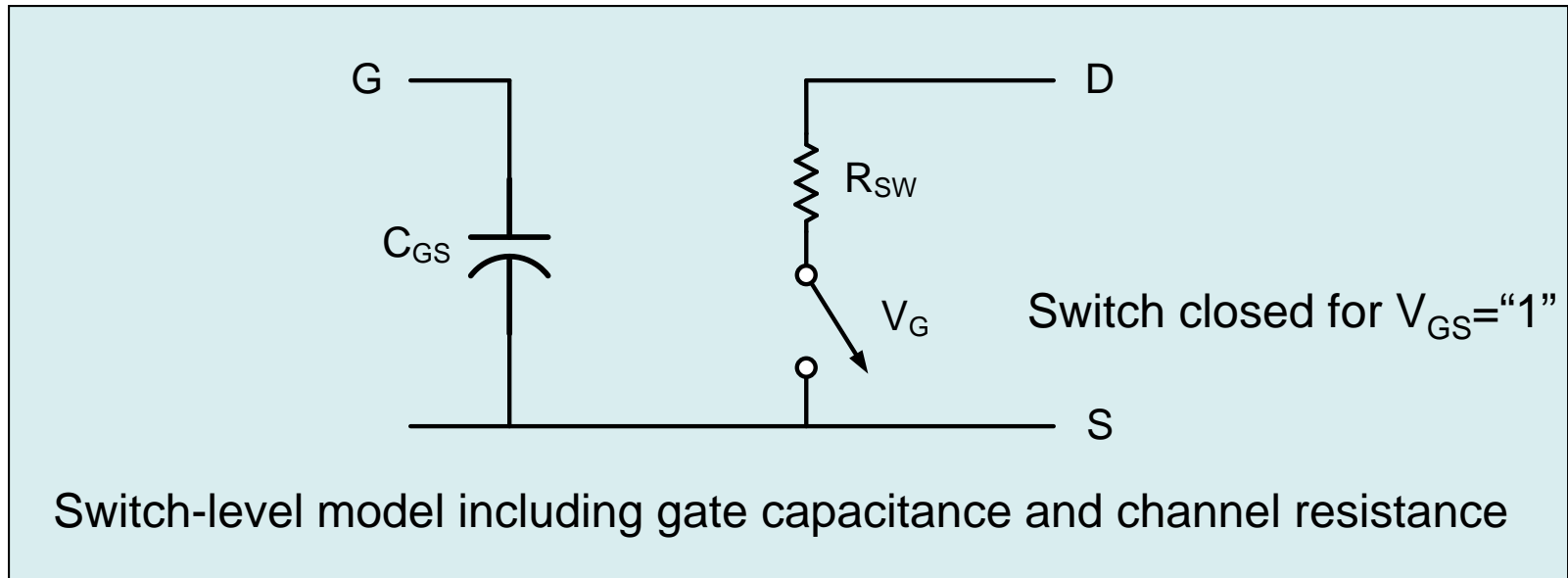


- Connect the gate capacitance to the source to create lumped model
- Still neglect bulk connection

Improved Switch-Level Model

   

Improved Switch-Level Model

   


Switch closed for V_{GS} large and neg

*Alt: If S near V_{DD} ,
closed for $G=0$*

Switch-level model including gate capacitance and channel resistance

Improved Switch-Level Model

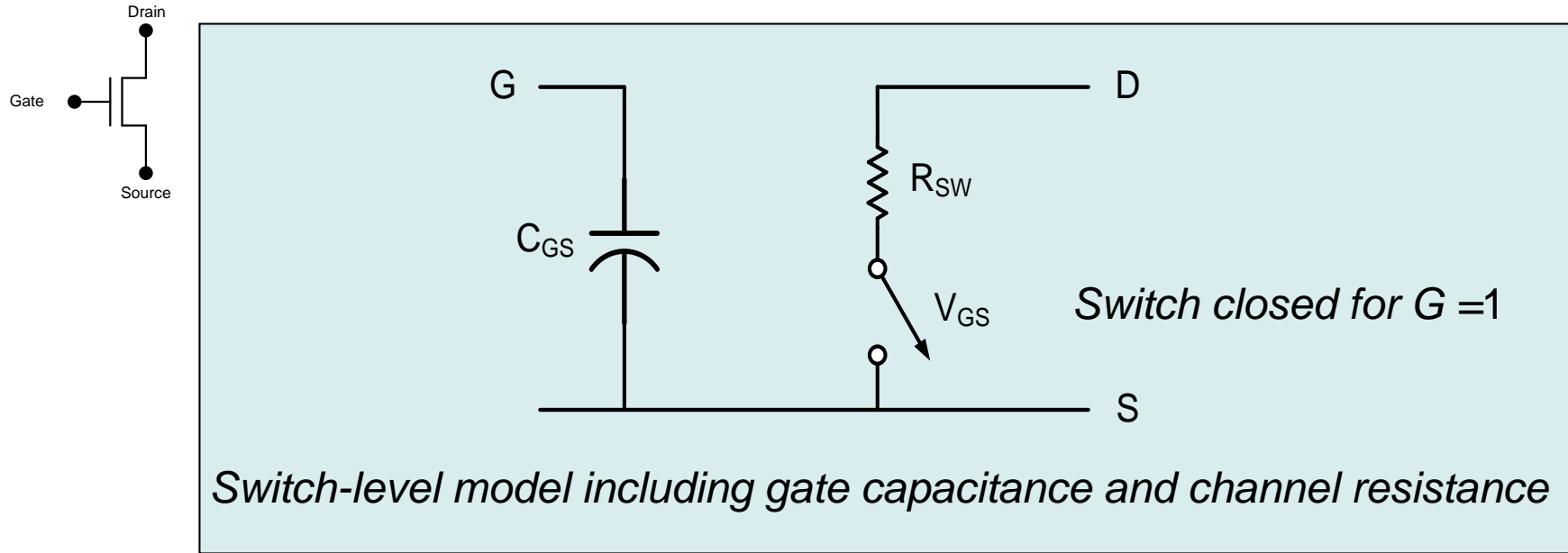


C_{GS} and R_{SW} dependent upon device sizes and process

For minimum-sized devices in a 0.5u process

$$C_{GS} \cong 1.5\text{fF} \quad R_{sw} \cong \left. \begin{array}{l} 2\text{K}\Omega \text{ n-channel} \\ 6\text{K}\Omega \text{ p-channel} \end{array} \right\}$$


Considerable emphasis will be placed upon device sizing to manage C_{GS} and R_{SW}

 Is a capacitor of 1.5fF small enough to be neglected?



Area allocations shown to relative scale:

 
Is a capacitor of 1.5fF small enough to be neglected?




Area allocations shown to relative scale:

- Not enough information at this point to determine whether this very small capacitance can be neglected
- Will answer this important question later


Model Summary (for n-channel)

 

1, Switch-Level model

 


2, Improved switch-level model

 

Switch closed for $V_{GS} = \text{large}$
Switch open for $V_{GS} = \text{small}$


Other models will be developed later

- Pass Transistor Logic
- Improved Switch-Level Model
-  • Propagation Delay
- Stick Diagrams
- Technology Files

Example

What are t_{HL} and t_{LH} ?


Assume $V_{DD}=5V$

 

With basic switch level model ?



With improved switch level model ?

Example

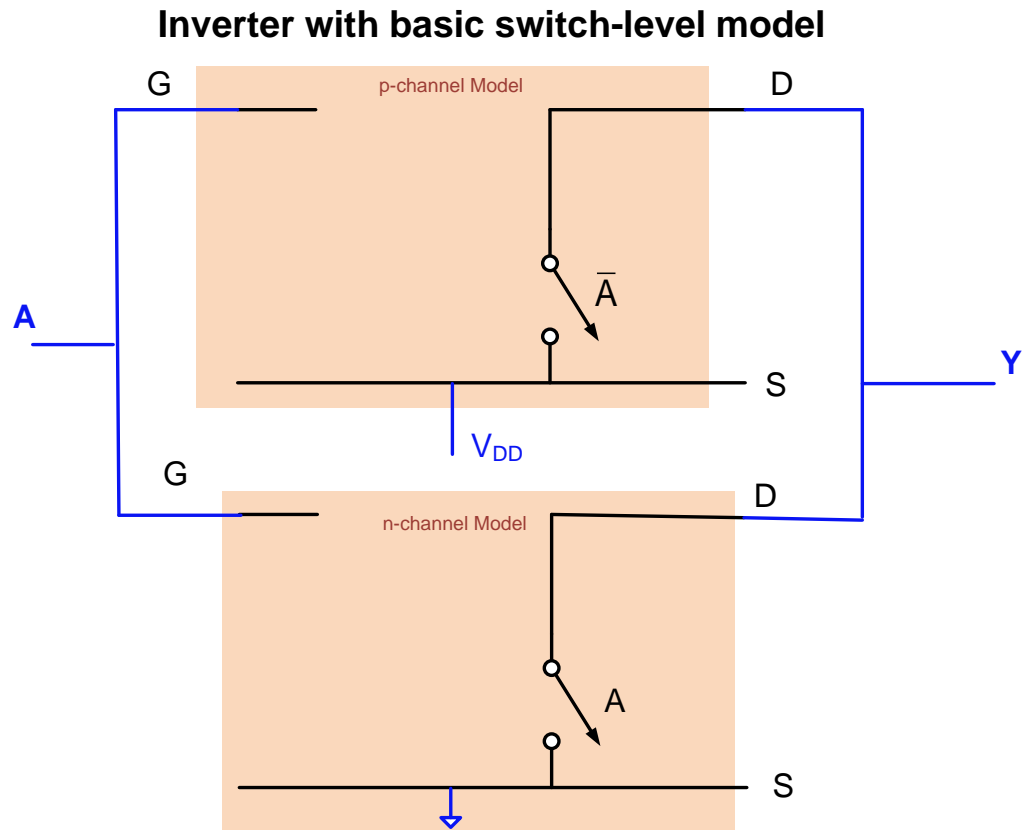


Example

What are t_{HL} and t_{LH} ?

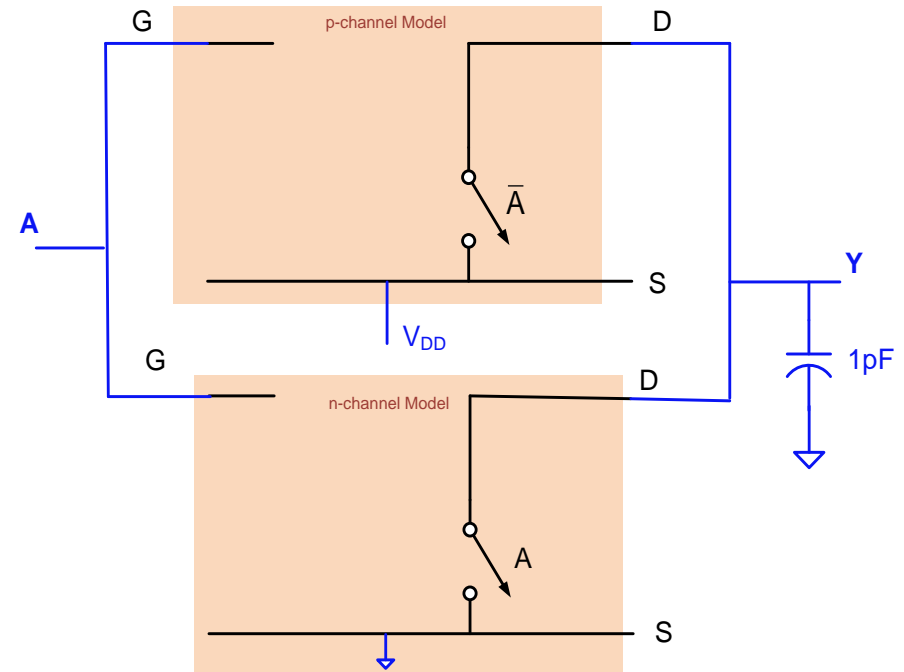 


With basic switch level model

 

$$t_{HL} = t_{LH} = 0$$

 
Example (cont)

With simple switch-level model $t_{HL}=t_{LH}=0$



Inverter

With improved model ?

 


Example (cont)

Inverter with improved model



Inverter

Inverter with Improved Model

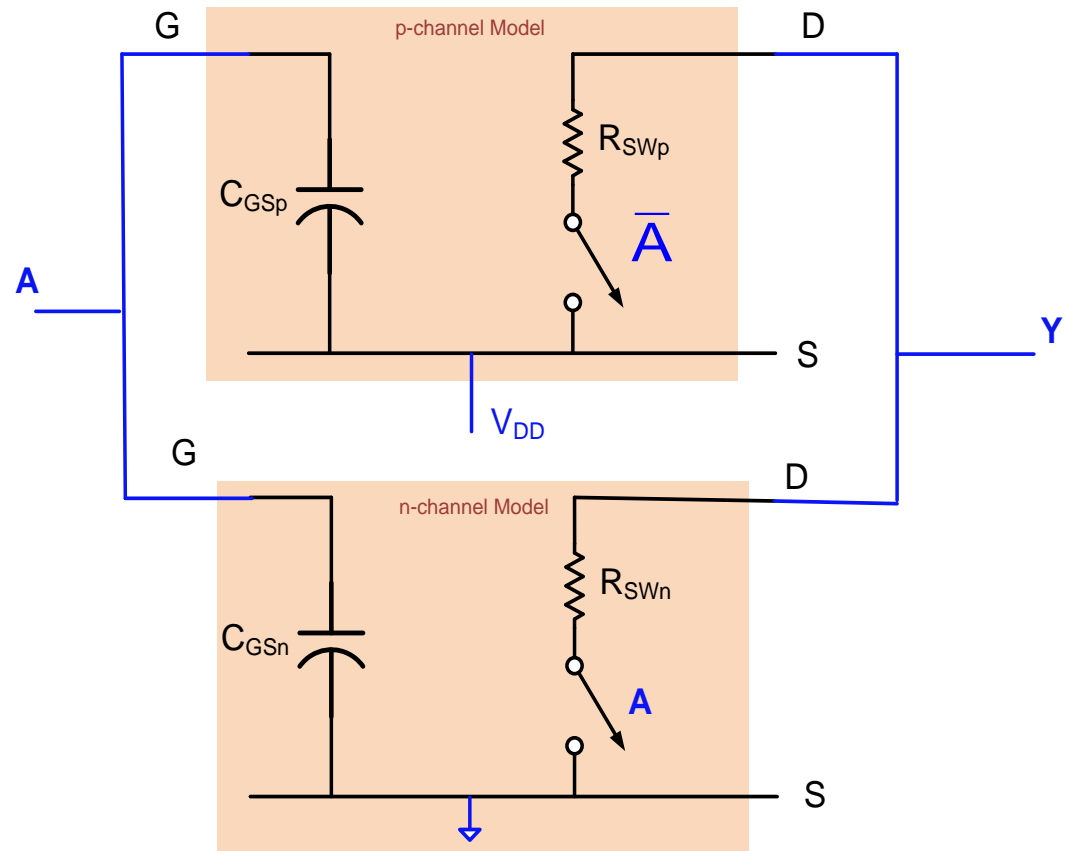


Example (cont)

With improved model $t_{HL}=?$

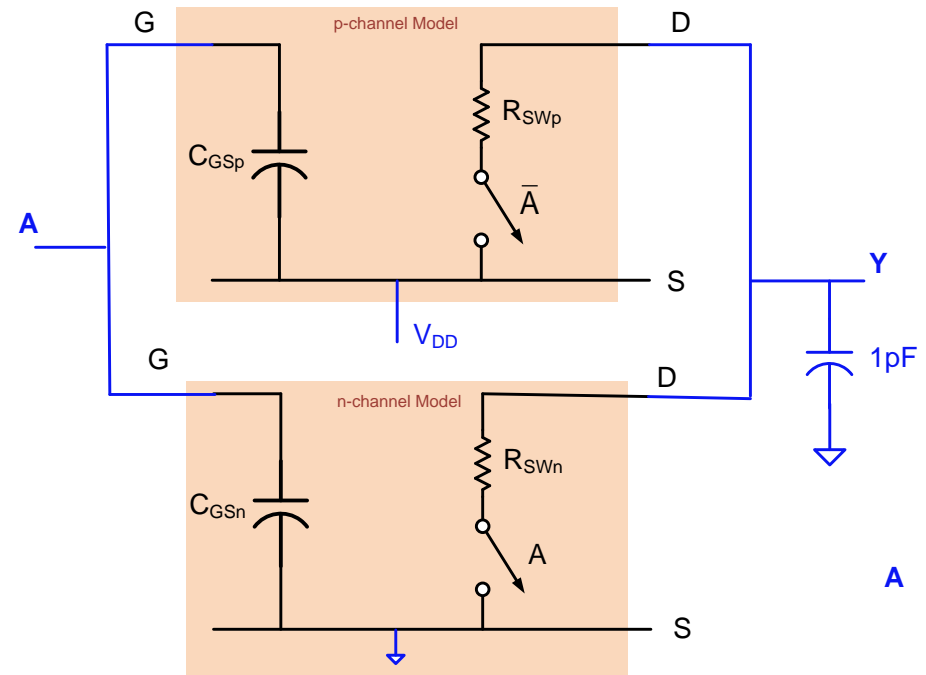 

 
To initiate a HL output transition, assume Y has been in the high state for a long time and lower switch closes at time $t=0$



Example (cont)

With improved model

$$t_{HL}=?$$

 

Recognize as a first-order RC network

Recall: Step response of any first-order network with LHP pole can be written as

$$y(t) = F + (I - F)e^{-\frac{t}{\tau}}$$


where F is the final value, I is the initial value and τ is the time constant of the circuit

(from Chapter 7 of Nilsson and Riedel)

For the circuit above, $F=0$, $I=5$ and $\tau = R_{SWn} C_L$

Example (cont)

With improved model

 


$$t_{HL}=?$$

$$V_{OUT}(t) = F + (I - F)e^{-\frac{t}{\tau}}$$

$$V_{OUT}(t) = 5e^{-\frac{t}{\tau}}$$



$$\tau = R_{SWn} C_L$$

 

how is t_{HL} defined?

Example (cont)

$$t_{HL}=?$$

  


Define t_{HL} to be the time taken for output to drop to I/e

$$V_{OUT}(t) = F + (I - F)e^{-\frac{t}{\tau}} \quad \longrightarrow \quad \frac{I}{e} = F + (I - F)e^{-\frac{t_{HL}}{\tau}}$$

t_{HL} as defined here has proved useful at analytically predicting response time of circuits

Example (cont)

With improved model

 

$$\frac{I}{e} = F + (I - F)e^{-\frac{t_{HL}}{\tau}}$$

$$\frac{I}{e} = Ie^{-\frac{t_{HL}}{\tau}}$$

$$\frac{1}{e} = e^{-\frac{t_{HL}}{\tau}}$$


$$t_{HL} = \tau$$




$$t_{HL} = R_{swn} C_L$$

Example (cont)

With improved model $t_{LH}=?$

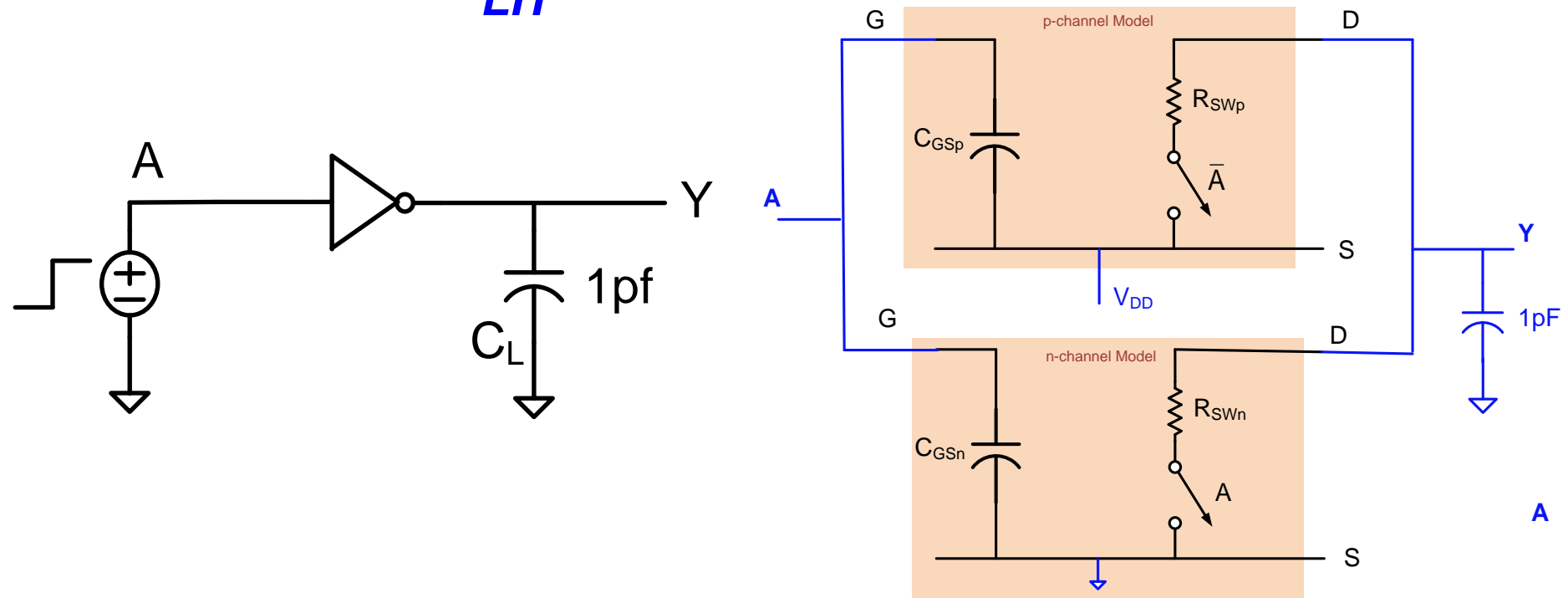


 Assume output in low state for a long time and upper switch closes at time $t=0$



Example (cont)

With improved model $t_{LH}=?$

 


$$y(t) = F + (I - F)e^{-\frac{t}{\tau}}$$

For this circuit, $F=5$, $I=0$ and $\tau = R_{swp} C_L$

Example (cont)

With improved model

 


$t_{LH} = ?$

$$V_{OUT}(t) = F + (I - F)e^{-\frac{t}{\tau}}$$

$$V_{OUT}(t) = 5\left(1 - e^{-\frac{t}{\tau}}\right)$$

$$\tau = R_{SWp} C_L$$

 



how is t_{LH} defined?

Example (cont)

With improved model

$t_{LH}=?$

Define t_{LH} as shown on figure

  

t_{LH} as defined has proven useful for analytically predicting response time of circuits

$$V_{OUT}(t) = F + (I - F)e^{-\frac{t}{\tau}} \quad \longrightarrow \quad F\left(1 - \frac{1}{e}\right) = F + (I - F)e^{-\frac{t_{LH}}{\tau}}$$

Example (cont)

With improved model


$$t_{LH}=?$$

$$F\left(1 - \frac{1}{e}\right) = F + (I - F)e^{-\frac{t_{LH}}{\tau}}$$


$$F\left(1 - \frac{1}{e}\right) = F + (F)e^{-\frac{t_{LH}}{\tau}}$$

$$1 - \frac{1}{e} = 1 + e^{-\frac{t_{LH}}{\tau}}$$

$$t_{LH} = \tau$$


 


$$t_{LH} = R_{SWp} C_L$$

 

Example (cont)

With improved model

  

$$t_{HL} \cong R_{SWn} C_L$$

$$t_{LH} \cong R_{SWp} C_L$$

In the ON 0.5u process
 $= 2K \bullet 1pF = 2n \text{ sec}$


$$= 6K \bullet 1pF = 6n \text{ sec}$$

Note this circuit is quite fast !

Note that t_{HL} is much shorter than t_{LH}

Often C_L will be even smaller and the circuit will be much faster !!

 Summary: What is the delay of a minimum-sized inverter driving a 1pF load?





In the ON 0.5u process

$$t_{HL} \cong R_{SWn} C_L = 2K \bullet 1pF = 2n \text{ sec}$$

$$t_{LH} \cong R_{SWp} C_L = 6K \bullet 1pF = 6n \text{ sec}$$

Improved switch-level model

  

Switch closed for $V_{GS} = \text{large}$

Switch open for $V_{GS} = \text{small}$

- Previous example showed why R_{SW} in the model was important
- But of what use is the C_{GS} which did not enter the previous calculations?

For minimum-sized devices in a 0.5u process

$$C_{GS} \cong 1.5\text{fF} \quad R_{sw} \cong \left. \begin{array}{l} 2\text{K}\Omega \text{ n-channel} \\ 6\text{K}\Omega \text{ p-channel} \end{array} \right\}$$

End of Lecture 6