
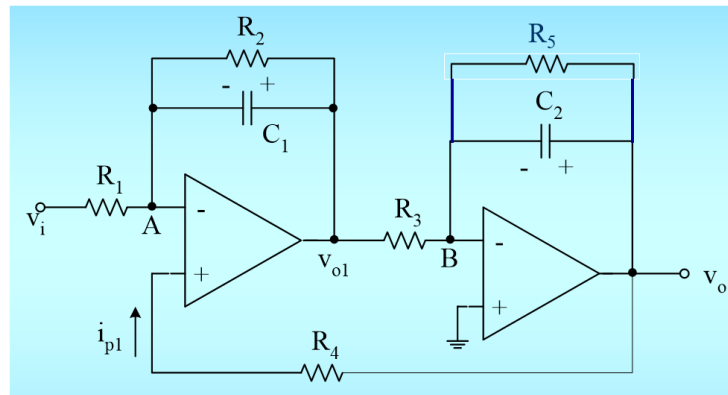


EE 475 HW #2

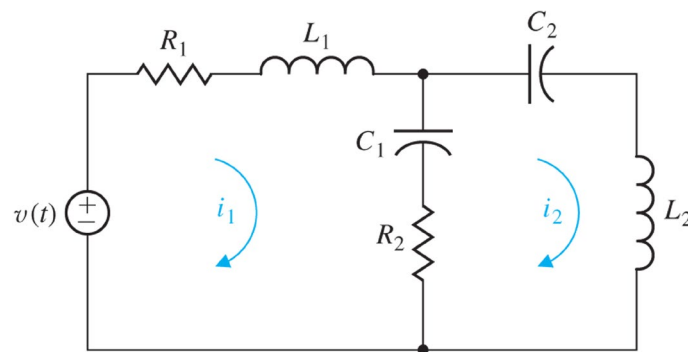1. The book derived the transfer function of the PID controller given in Table 3-1 on page 85. Use this result to obtain the results given in item 3 and item 4 in the same table.
2. Derive the e_i to e_o transfer function for the Lag-lead controller given in item 7 of Table 3-1. Assume ideal op amps.
3. For the op amp circuit given below, v_i is input, v_o is output, v_{c1} and v_{c2} are state variables. Derive the state space model for the circuit.



4. B-3-7
5. B-3-9
6. B-3-11
7. B-3-12
8. B-3-13, take gear ratio = 1
9. For the electric circuit given below. Use v as input, i_1 and i_2 as output, and your choice of state variables to derive a state space model for the circuit. Get the transfer function from v to i_2 .



10. A CMOS low noise amplifier (LNA) that is typically used in your cell phone is given below in the left half of the graph. There is also an R_L connecting from V_o to ground not shown. A simplified small signal circuit for the LNA is represented in the right half of the graph. V_s is input and V_o is output. 1) Identify the energy-storing elements. 2) Determine the state variables, the node to write KCL and the loops to write KVL. 3) Derive a state space model for the low noise amplifier together with the load R_L .

