

EE 475 Quiz #3

Name: Solution

1. For an ideal op amp, its

a. $V_p - V_n = \underline{0}$

b. $I_p = I_n = \underline{0}$

c. $R_{in} = \underline{\infty}$

d. $R_o = \underline{0}$

e. DC gain = ∞

2. In control system modeling, you can never create your own equations. You can use algebra to manipulate/simplify/solve equations, but all of your key equations must be based on: physical laws

3. In modeling electric circuits, name two most important physical laws: KCL, KVL, charge conservation, energy conservation, ...

4. In modeling mechanical motions, name two most important physical laws: Newton's law, Euler's law, Lagrange principle, conservation of energy, conservation of mass, Hooke's law, ...