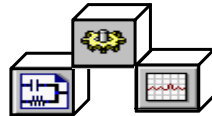





Topic 1:

ADS and Circuit Simulation Fundamentals



Here is ADS Simplified: 3 steps

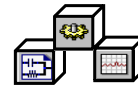

STEP 1: design capture

Insert circuit &
system components
and set up the
simulation.



STEP 2: Simulate

Netlist is
automatically sent to
the simulator.



Simulation results
(data) are written to
a *dataset*.



STEP 3: display the results

Plot or list data &
write equations.

Layout / Momentum.

User Variables, Licenses, Directories

Just in case you need to know:

\$HOME (UNIX variable) or %HOME% (PC variable)
is usually where you run and use ADS.

\$HPEESOF_DIR (UNIX variable) or %HPEESOF_DIR% (PC variable)
points to where you get ADS.


LM_LICENSE_FILE points to the license file
(default is: LM_LICENSE_FILE = \$HPEESOF_DIR/licenses/license.dat.).

NOTE: When you install ADS, you will be prompted where to load ADS
(HPEESOF_DIR) and where you want to run ADS (PC: C:\users\default).

For this class (US laptops), you should be working in either:
D:\user\ads15
or on the HP 3000- C:\user\ads15


ADS Windows: Main, Schematic, Status, Data Display

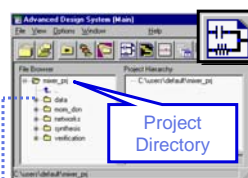Main window: manage projects and
open other windows...




Open a schematic

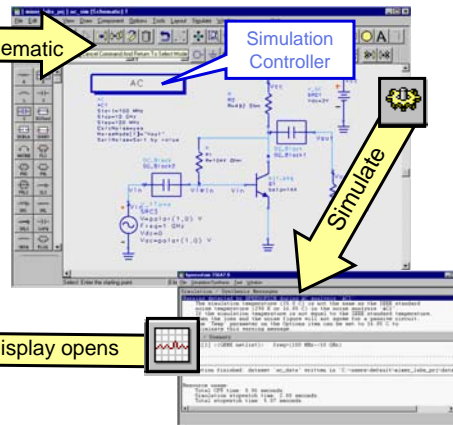Schematic window:
create / refine circuits & run simulations...



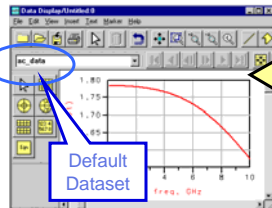Data Display window:
plots, lists, equations



Display opens

Status window:
simulation info: messages, errors, etc...

How to Start ADS...

Note the ADS tools:

Menu commands

Toolbar icons

Project with lower level directories

First step:
To create a project, click: **File > New Project** and name it: **lab_1**

Help = online manuals using internet explorer.

You can also create an ADS shortcut.

ADS Project Directory Structure and Files

Project for example: *lab_1_prj*

- preferences & ADS netlist.log
- **filename.dds** **Data Display files** (windows to display data)
- **data**
 - **filename.ds** **Dataset files** (simulation data)
- **networks**
 - **filename.dsn** **Schematic & Layout files**
 - filename.ael (application extension language)
 - filename.atf (compiled ael)

Automatically created by ADS

- mom_dsn (Momentum only)
- synthesis (used for E-Syn & DSP)
- verification (used for DRC)

} Not required for most simulations (can be removed)

Main window: File, View, and more...

Use icons or commands. However, not all commands have icons. But all icons have commands.

File commands:

- New Project...
- Open Project...
- Example Project...
- Copy Project...
- Delete Project...
- Include/Remove Projects...
- Archive Project...
- Unarchive Project...
- Copy Design...
- Delete Design...
- Save All Designs...
- Close All Designs...
- Import...
- Exit Advanced Design System... Alt+F4

View commands:

- Working Directory
- Example Directory
- Directory...
- Top Directory
- Startup Directory
- Project Listing
- Expand All
- Toolbar

Examples directory

Zap your files : more on this later

Spice or IFF

Click **+** box to expand or **-** box to collapse.

Main window: Options

Main Preference

- Warning Bell
- Error Bell
- Balloon Help
- Design Simulation Checking
- Large Toolbar Bitmap
- Save Project State on Exit
- Create Initial Schematic Window
- Create Initial Layout Window
- Add Project Extension
- View Thickness:
 - Thin
 - Medium
 - Thick
- External Text Editor: NOTEPAD.EXE
- Web Browser
- Preferences

Advanced Design System Setup

Design Type Supported

- Analog/RF Only
- Digital Signal Processing Only
- Both, With Default:
 - Analog/RF Design
 - DSP Design


New settings will be effective once the application is restarted.

AEL


Main window preferences are global, they apply to all projects. The Schematic window has its own preferences.

Main window: Window commands...

Notice the default Hot Keys

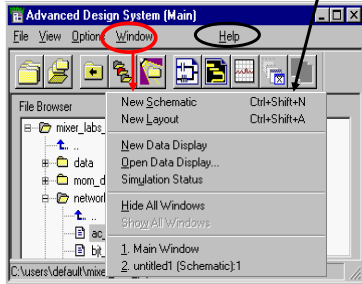

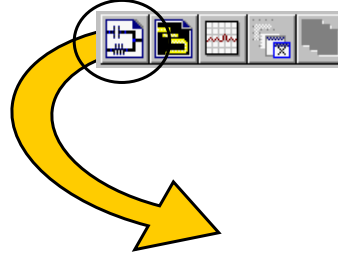If you are in a project, you can open one of these windows:




So, let's open the Schematic window...



Schematic window

Save your work often...

All icons have labels (balloon help).

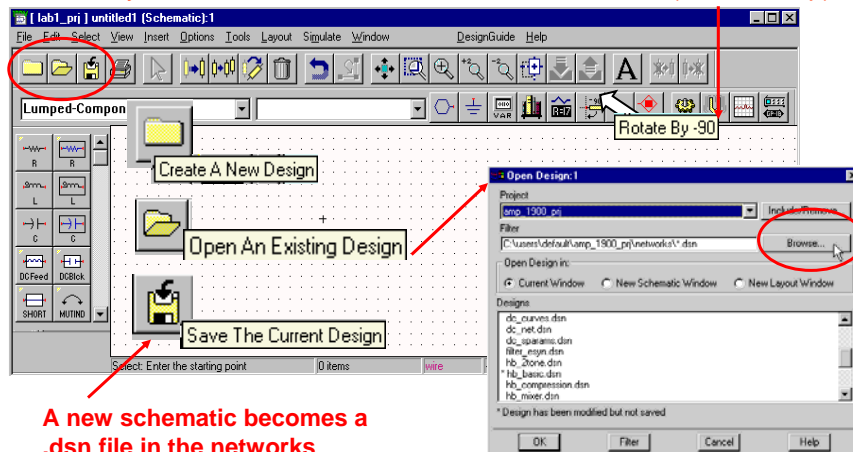

A new schematic becomes a .dsn file in the networks directory only after you save it.

Also – use Window > Open Designs

Inserting and Editing components

Also known as schematic capture!

End command or use ESC.

Component History: type name to insert component.

Select palettes. Insert components.

Parameters are defined: `_M` is multiplicity.

Edit a component: use icon or double click.

Wires and node names.

Editing commands and icons

Edit > Component has many uses.

Push / Pop for sub-circuits.

Select command is also useful...

Library vendor parts + all your circuits

Component Library/Schematic: 1 Schematic...Click:

The screenshot shows the 'Component Library/Schematic: 1' window. The 'Libraries' pane on the left is expanded to 'RF Transistor Library' > 'Packaged GaAs FETs'. The 'Components' table lists various parts with columns for Component, Vendor, and Description. A red circle highlights the search icon in the toolbar. A red arrow points from the search icon to a 'Find' dialog box where 'ATF2' is entered in the search field. A red box highlights the '+' and '-' icons in the Libraries pane with the text 'Click the + or - to expand or collapse.' Another red box highlights the search icon with the text 'FIND any part or search the WWW for parts.'

Click the + or - to expand or collapse.

FIND any part or search the WWW for parts.

Select the part and it is attached to your cursor, ready to insert.

Wiring and Moving components

Tips for wiring!

- Use the wire or connect pins = wired
- Point and click to snap to grid
- Drag a wired component and it stays wired.
- Wire colors are in Options > Layers

Options

- Snap Enabled Ctrl+E
- Pin Snap
- Grid Snap

Click to wire:

Red pin = not connected

Two rotation icons:

Edit wired components:

- Move Using Reference Ctrl+M
- Move Edge
- Move Relative...
- Move & Disconnect** X
- Move To Layer...
- Move Wire Endpoint Ctrl+Shift+M
- Move Component Text F5

Check Representation for errors

Use this if your simulation results look wrong!

Check Representation:1

- Unconnected pins
- Nodal mismatches (layout vs schematic)
- Component pin vs Symbol port mismatches
- Rep port vs Symbol port mismatch
- Overlaid components
- Overlap wires

OK Cancel Help

Check Representation Report:5

Report for C:\ZAPS\mixer.prj\networks\dc_curves (schem...

Unconnected pins: 1
I_DC SRC2, pin 2 (3.125,-1.125)

Overlaid items: None

Click: Options > Check Representation


Node Names in Schematics

Click the icon: 

- Node names result in simulation **data** (node voltage) in the dataset.
- Node names can also connect two points without using a wire.
- Global nodes can connect node names in sub-circuits:




Insert > Global Node


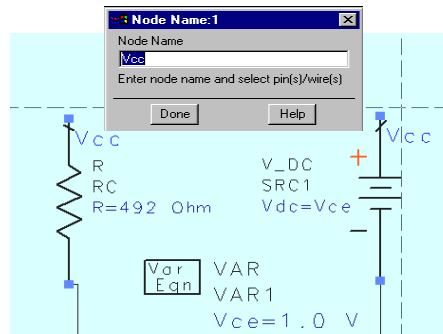


To remove a node name:

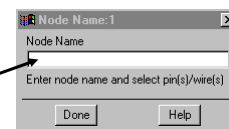Edit > Component > Remove Node Name
or **use the icon with a blank name.**



Variable Equations: VAR

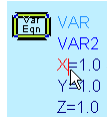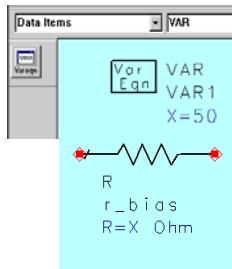

Click:


TIP: Add dummy (X,Y,Z) variables and then edit on-screen.

VAR is a declaration (initialization). Component parameters can be assigned a value using a variable equation.


Variables can be used with optimization, parameter sweeps, and many ...

Symbols, units, and names

Circle for mutual inductance:

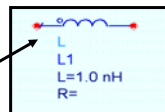


Slash for pin# 1 (layout):

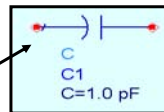

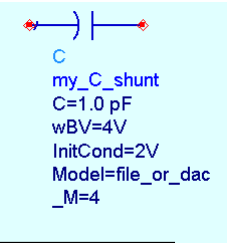Example of on-screen control:

- C** (component name): changes the component
- C1** (instance name): rename it: c_shunt
- C=** (parameter): a number (unit) or valid variable.



QUIZ: Is this valid?	C coupling_c C = x	Answer: _____
-----------------------------	--------------------------	----------------------


Units and case sensitivity

- General Rule #1: UNIX is always case sensitive.
- General Rule #2: PCs are case sensitive, except for:
 - *Inserting some components: R or r is OK, because after the first insert, PC will recognize either one.*

However, some rules apply to both, for example:


m = milli, M = Mega, V = volts

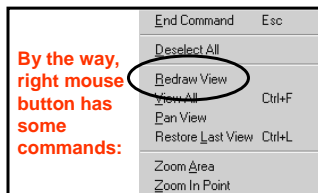& variable names are always case sensitive!



And now, let's Simulate...

First, select the Simulation Controller


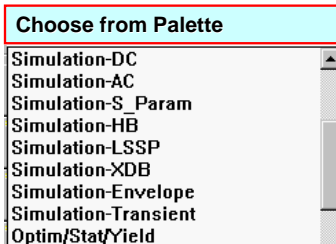


Click the gear to insert the controller.

S-Parameter

HB

DC

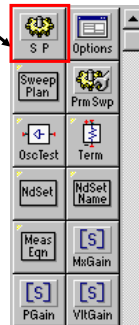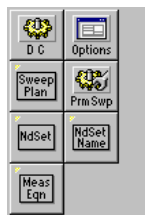


NOTE: all palettes have many of the same components (Prm Swp) and specific Meas Eqns.



Set up the Simulation

Simulation requires setting the simulation controller.

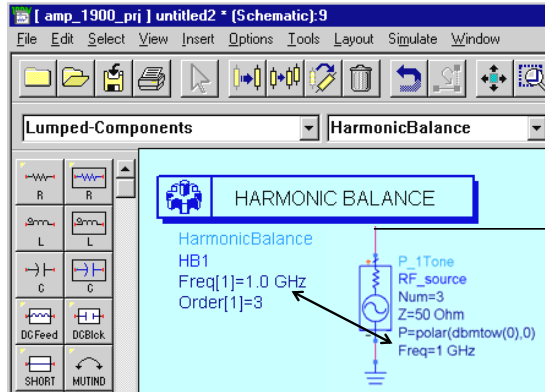*NOTE asterisk means schematic is not yet saved.



Some simulations, like HB, require more setup.


DC requires no setup in most cases.

S-param requires Terms.


Edit on-screen or double click for dialog box.



Example dialog for Controller

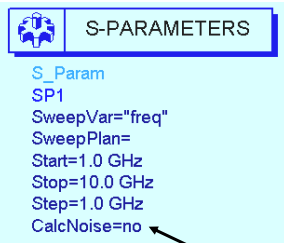

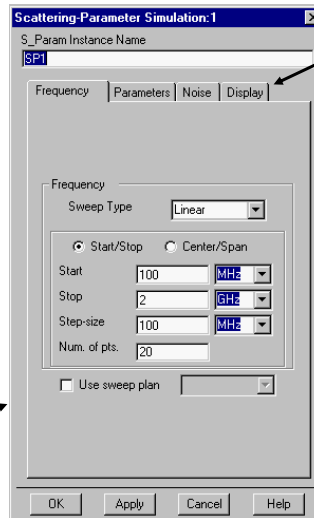Edit on-screen if the parameter is displayed or use the dialog box.



Display the parameters: **Display tab** lists all the settings you can show on-screen.

You will get lots of practice in the labs.



Templates for simulation

Insert & setup circuit, nodes and variables.


ADS 1.5 has many new templates.

Specifying a Dataset and Data Display

Before you simulate: you can name the dataset.
If not, the default dataset = schematic name or the last dataset named.

Click: **Simulate > Setup:**

Uncheck this box if desired.

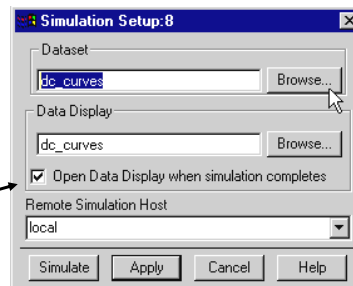

NOTE: Dataset files (.ds) are in the DATA directory.

Data Displays (.dds) are in the PROJECT directory & read datasets.

To run the simulation, click F7 key or click the gear...




During Simulation: Status Window appears!

One way to stop a simulation, click:


Simulation/Synthesis > Stop Simulation

A successful simulation results in a dataset:

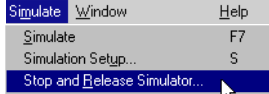To stop a simulation from the schematic window.




Or click: Window > Simulation Status

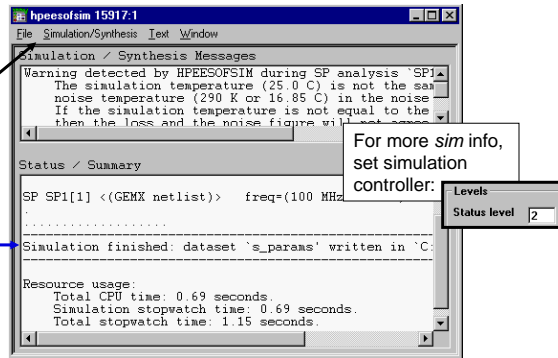

When finished, the Data Display opens...

Data Display window

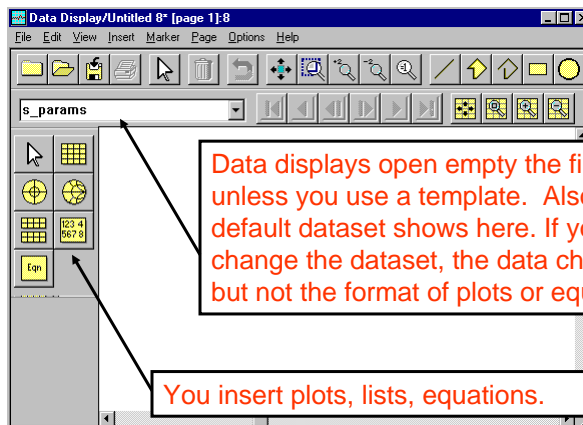Also, open Data Displays from schematic or the Main window:



List or plot your simulation data

Default dataset

Other datasets and DDS equations, click here!

Edit the data trace or equation here.

Measurement equations from schematics will also appear here.

STEPS:
 1) Select the type: plot or list.
 2) Select the data or equations.
 3) Options - edit data or plot.
 4) Save/name the DDS window.

→

Data Displays are powerful...

Insert Templates.

Scroll through lists.

View and zoom data.

Write equations to manipulate data to be listed or plotted.

Markers have readout properties you can edit. Use cursor or arrow keys to move a marker.


Traces can be edited for color and thickness.

Explicit dataset..path if not default.


Tune mode is simulation!

 Simulate > Tuning...

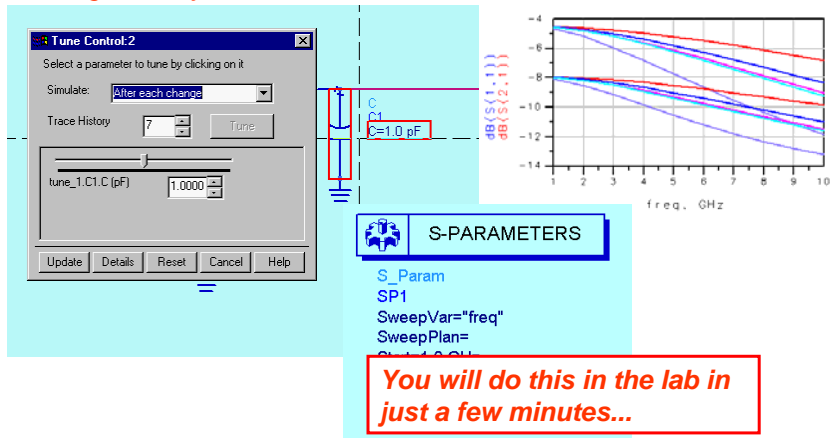
Tuning allows you to “tweak” values and see the results!





Printing data or schematics

File >  Ctrl+P

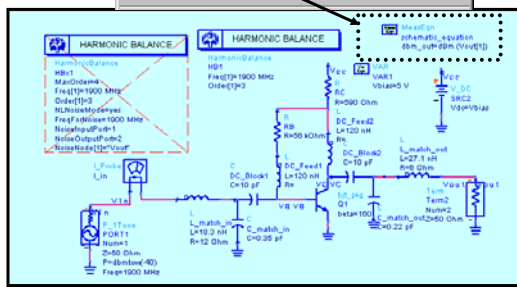For Data, you can print selected plots, lists, equations.



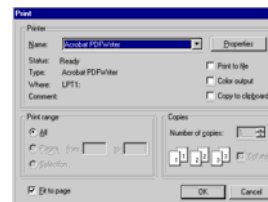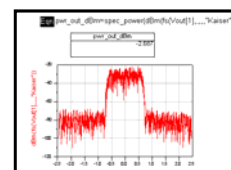Print Setup - select the printer, style, etc. →



NOTE on ending ADS processes

If your computer is locked up or if there is any other problem (Data Display), you can safely stop some processes:

hpeesofde.exe - closes the ADS program (same as exit)

Hpeesofsim.exe - stops the simulation

hpeesofdds.exe - end to stop the data display server } *These 2 work together!*


hpeesofdss.exe - end to stop the dataset server

UNIX users kill processes - PC users end processes

PC task manager -

NT: ctrl-alt-delete

In a UNIX window,
use: ps -ef | tail
and you can kill (xxx)
a processes.

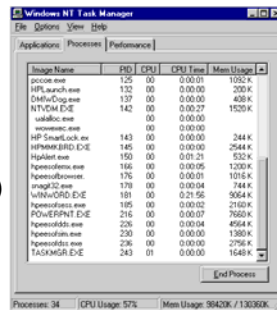



AVOID killing these:

hpeesofsess.exe
hpeesofbrowser.exe
hpeesofemx.exe

Killing these will require re-starting ADS.

To mail or send ADS projects: ZAP

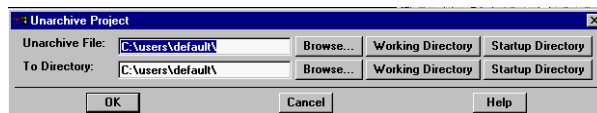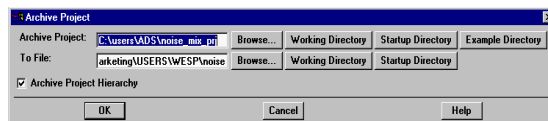From the Main window, click: File > Archive or Unarchive



NOTE: Archive files become .ZAP files (like .ZIP files). They can include all networks, data, and display files (entire project).

When you leave this class, archive the projects to C:\temp and then copy the ZAP to the A drive. Be sure to delete the datasets or it will not fit on a floppy disk (not necessary if you e-mail a zap file).


For any ADS problems, call support and send the ZAP file. In the United States call: 1 - 800 473-3763.




What the lab is about ...

Lab 1:


Circuit Simulation Fundamentals

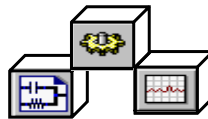

Learn Circuit Simulation Basics

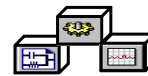

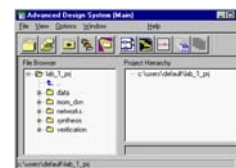- Create a project and schematic
- Build a low-pass filter
- Set up and run an S-parameter simulation
- Display the results and Tune the filter
- Copy an example RFIC amplifier
- Insert a library part and simulate with a Template
- Simulate an RFIC amp with Harmonic Balance
- Display the results and write equations



NOTE: Lab 1 can be skipped if students already know the basic operation of ADS: schematic capture, simple simulation, basics of plotting data.

Also, it's OK to make mistakes...you won't need the work you do in this lab for any of the other exercises.

But starting in Lab 2, you will!

STEPS IN THE LAB:



Build and simulate a low-pass filter

After setting up the S-parameter simulation, tune the filter.


The screenshot shows a circuit simulation window with a schematic of a low-pass filter. The filter consists of two series inductors (L1 and L2) and two shunt capacitors (C1 and C2) connected to ground. The input and output ports are terminated with 50 Ohm resistors. The component values are: L1 = 1.0 nH, L2 = 1.0 nH, C1 = 1.0 pF, and C2 = 3.0 pF. An S-Parameters block is placed in the schematic, configured for an SP1 simulation with a start frequency of 1.0 GHz, a stop frequency of 10.0 GHz, and a step of 0.1 GHz. A 'Tune Control' dialog box is open, showing the 'Lumped-Components' list and a plot of the filter's magnitude response. The plot shows the magnitude in dB versus frequency in GHz, with a peak at approximately 5.4 GHz. A yellow arrow points from the plot towards the right.

Also...library device simulation with template

The screenshot shows a 'Component Library/Schematic 2' window. The 'Components' list includes a 'Parameter Library' and a 'Simulation Template'. The 'Simulation Template' is selected, and its properties are shown in the 'Properties' pane. The properties include: SP_NWA, X1, Start=0.1 GHz, Stop=5 GHz, NumPoints=101, VBias1=0, VBias2=0, Port1Z=50, and Port2Z=50. The 'DisplayTemplate' section is expanded, showing 'disptemp1', 'SP_NWA_T', and 'S_21_11_wZoom'. The 'Activate for available gain and stability circles' section is also expanded, showing 'DisplayTemplate', 'disptemp2', 'Circles_Ga_Stab', and 'Circles_Stability'. A schematic diagram shows a red square component connected to two ports labeled '1' and '2'. A yellow arrow points from the schematic towards the right.

Last, example RFIC with Harmonic Balance

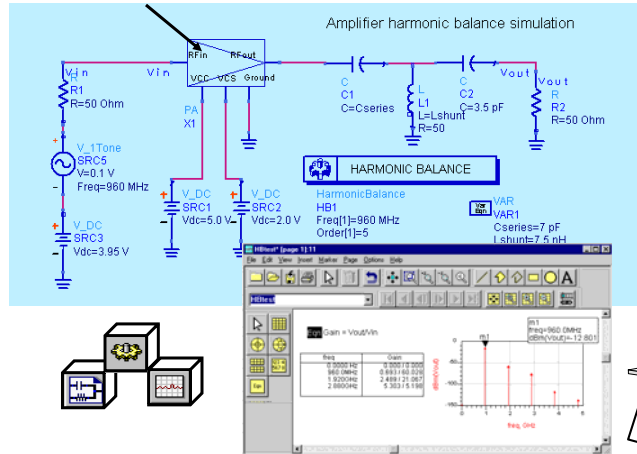You will name the node Vin, check the sub-circuit, and simulate. Then write an equation for gain in the data display.




Start the lab now!





Topic 2:

System Design Fundamentals

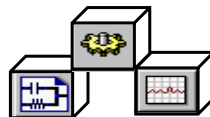

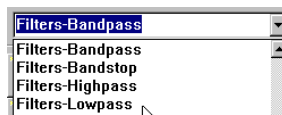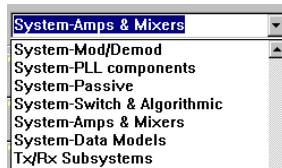
System component libraries and fundamentals:



- System design is at the higher level.
- System models are *behavioral*: equation based describing node I and V, table based, etc.
- System components can be integrated with circuit components.
- **IMPORTANT** - System simulation and data display are the same as for *circuit*.



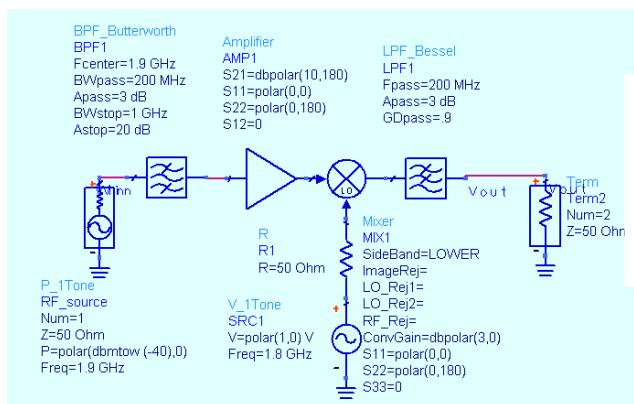Typical system design using ...behavioral models




What are behavioral models?

Behavioral models are described by equations.
 (Similar to SDD-time domain and FDD-frequency domain.)




Typical system model: Amplifier

Behavioral model

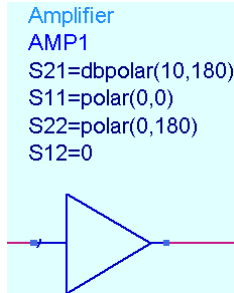

You specify the behavior:

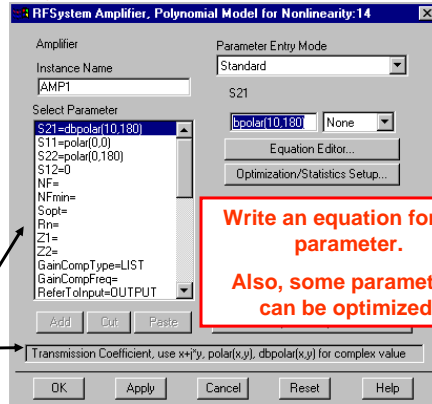Polynomial equations describe nonlinearity:




Write an equation for the parameter.

Also, some parameters can be optimized.

Simulation is the same for circuit and system (behavioral):

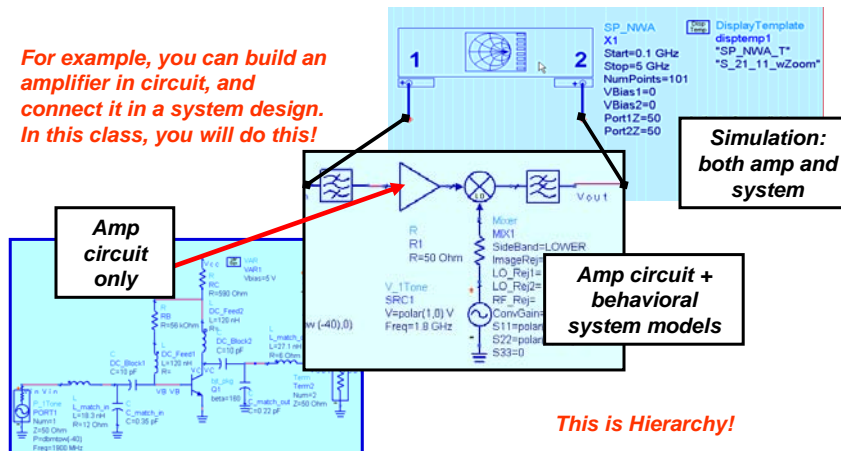For example, you can build an amplifier in circuit, and connect it in a system design. In this class, you will do this!



Simulation: both amp and system

Amp circuit only

Amp circuit + behavioral system models


This is Hierarchy!

Data Flow simulation

Data Flow simulation (Ptolemy) is 3 levels here:

- 1 - Circuit design
- 2 - System designs with Envelope or Transient
- 3 - Data Flow (Ptolemy): bits, sinks, TK plots

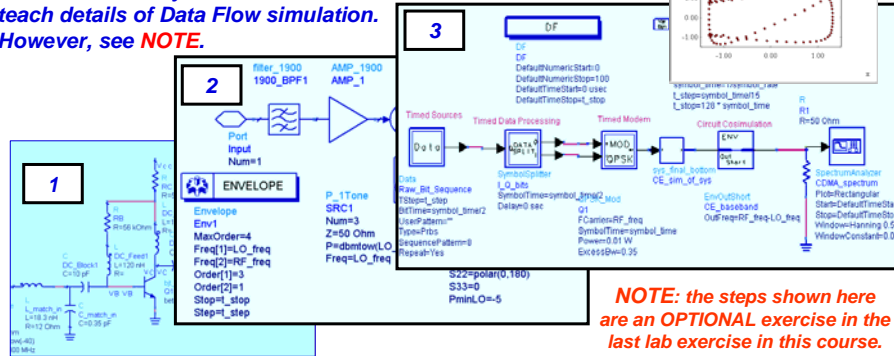DSP and CommSys courses teach details of Data Flow simulation. However, see **NOTE**.




NOTE: the steps shown here are an **OPTIONAL** exercise in the last lab exercise in this course.



What the lab is about ...

Lab 2:

System Design Fundamentals

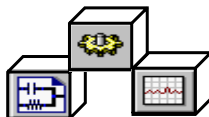


Steps in the Design Process

You are here:







- **Design the rf_sys behavioral model receiver**
- **Test conversion, budget gain, spectrum, etc.**
- Start amp_1900 design – subckt parasitics
- Simulate amp DC conditions & bias network
- Simulate amp AC response - verify gain
- Test amp noise contributions – tune parameters
- Simulate amp S-parameter response
- Define amp matching topology and tune input
- Optimize the amp in & out matching networks
- Filter design – lumped 200MHz LPF use E-Syn
- Filter design – microstrip 1900 MHz BPF
- Transient and Momentum filter analysis
- Amp spectrum, delivered power, Zin - HB
- Test amp comp, distortion, two-tone, TOI
- CE basics for spectrum and baseband
- CE for amp_1900 with GSM source
- Replace amp and filters in rf_sys receiver
- Test conversion gain, NF, swept LO power
- Final CDMA system test CE with fancy DDS
- Co-simulation of behavioral system

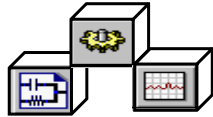

Amp and filter simulation: S-parameters

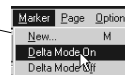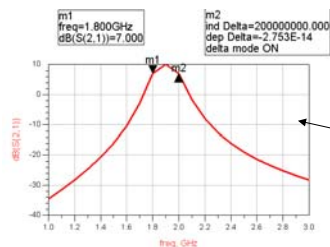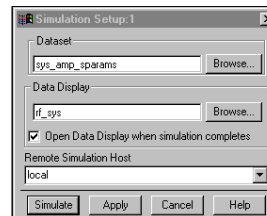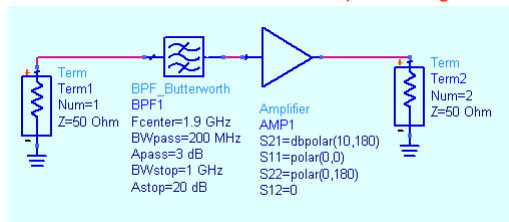S-21 measurement verifies bandpass and gain:



Receiver simulation: S-parameters

S-21 measurement tests conversion gain:

Converted Freq = 100 MHz IF

Enable is for behavioral system models only.

Simulation Setup 2

Scattering Parameter Simulation 3

Simulation Parameters:
 BPF_Butterworth: BPF1, Fcenter=1.9 GHz, BW/Pass=200 MHz, Apass=3 dB, BW/Stop=1 GHz, Astop=20 dB
 Amplifier: AMP1, S21=dbpolar(10,180), S11=polar(0,0), S22=polar(0,180), S12=0
 LPF_Bessel: LPF1, Fpass=200 MHz, Apass=3 dB, GDpass=0.9
 Term: Term1, Num=1, Z=50 Ohm
 V_1Tone: SRC1, V=polar(1,0) V, Freq=1.8 GHz
 MIX1: SideBand=LOWER, ImageRej=, LO_Rej1=, LO_Rej2=, RF_Rej=, ConvGain=dbpolar(3,0), S11=polar(0,0), S22=polar(0,180), S33=0
 R: R2, R=50 Ohm

Simulation Setup 2 (Data Display):
 Data Display: S21, S11, S22, S12, S33
 Remote Simulation Host: local

Scattering Parameter Simulation 3 (Parameters):
 Calculate: S-parameters, Y-parameters, Z-parameters, Group delay
 Frequency Conversion: Enable AC frequency conversion, S-parameter freq. conv. port: 1
 Levels: Status level: 2, Nesting level: 2
 Device operating point level: None, Bias, Detailed

Graph: Plot of $|S_{21}|$ vs. freq. GHz. The plot shows a peak at 1.9 GHz, corresponding to the converted frequency of 100 MHz IF.

AC simulation with Budget Gain

Budget measurement verifies gain in each stage:

AC
 AC1
 FreqConversion=yes
 OutputBudgetV=yes
 Freq=1.9 GHz

Simulation Parameters:
 P_1Tone: RF_source, Num=1, Z=50 Ohm, P=polar(dBm/1000,0), Freq=1.9 GHz
 V_1Tone: SRC1, V=polar(1,0) V, Freq=1.8 GHz

Generate Budget Path 1


MeasEqn
 BudPath
 budget_path = ["RF_source.t1", "BPF1.i2", "AMP1.i2", "MIX1.i2", "LPF1.i2", "Term2.t1"]

Budget Gain
 BudGain1
 BudGain1=bud_gain(1, 50.0, budget_path)

Graph: Plot of Budget Gain [dB] vs. Component. The plot shows the budget gain for each component: RF_source.t1, BPF1.i2, AMP1.i2, MIX1.i2, LPF1.i2, and Term2.t1. The gain for AMP1.i2 is highlighted as 10.000 dB.

HB simulation with Noise Controller

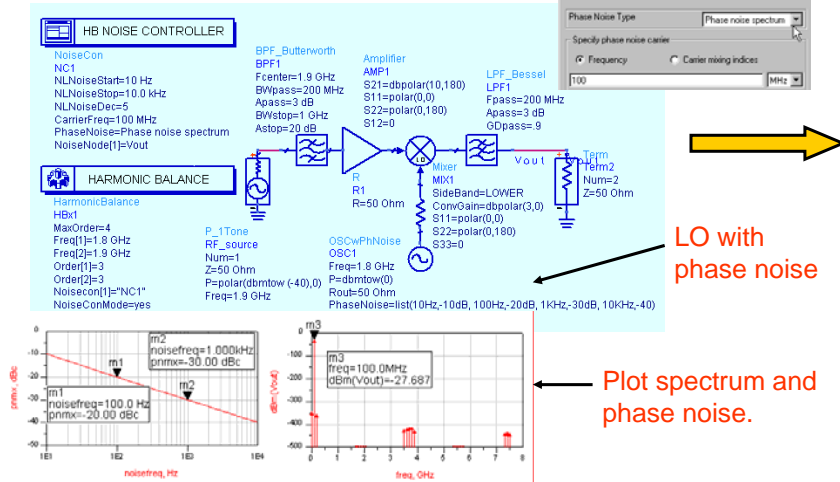
HB simulation tests phase noise and spectrum of IF:





Phase Noise NOTE: HB FFT oversample parameter can be increased until answer is constant!

Transient simulation of an SDD

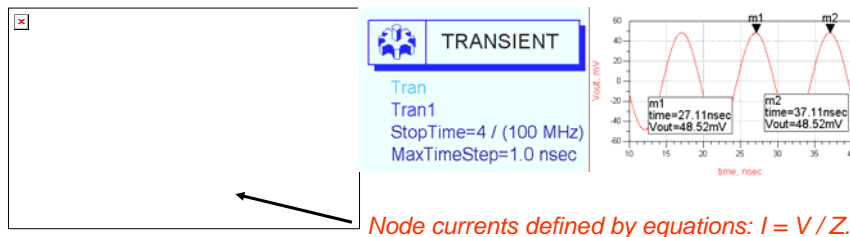Time domain signal displayed and transformed into the frequency domain:



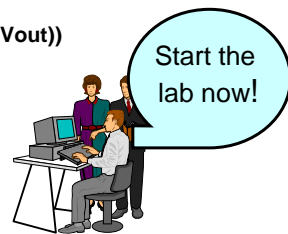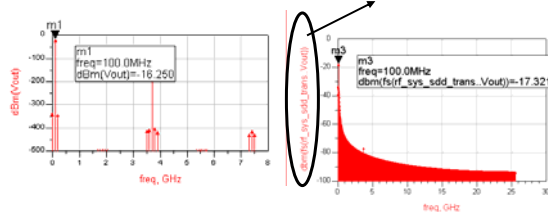Compare to HB using fs function: `dbm(fs(rf_sys_trans..Vout))`





Class Exercise

(after lab 2)



HOT KEYS and Schematic Preferences



Efficient ADS Techniques

Would you like to customize the system to be more efficient for the way you work?

Here are some things you can do:


- Moveable Toolbar: PC only - put it below
- Tear Off Menus: UNIX only - keep some on screen
- Options > Preferences: set these to your liking
- Templates - learn to use them or set up your own
- Examples - familiarize yourself with them
- ⇒ • HOT KEYS - Options > Menu / Toolbar Configuration



Pre-set schematic **Hot Keys**


Pre-configured keys:

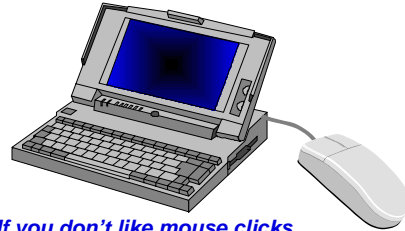F7 = Simulate
F5 = Move Component Text
 Ctrl+R = Rotate 90
 Ctrl+M = Move
 Ctrl+C = Copy
 Ctrl+Z = Undo
 plus more...




*If you don't like mouse clicks,
HOT KEY your keyboard.
 Its global for all projects*

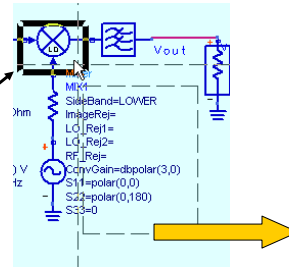Try this now: click the **F5** key,
 select the Mixer component, move
 the cursor and the text will follow!



Set the **View > Zoom** schematic **HOT KEY**

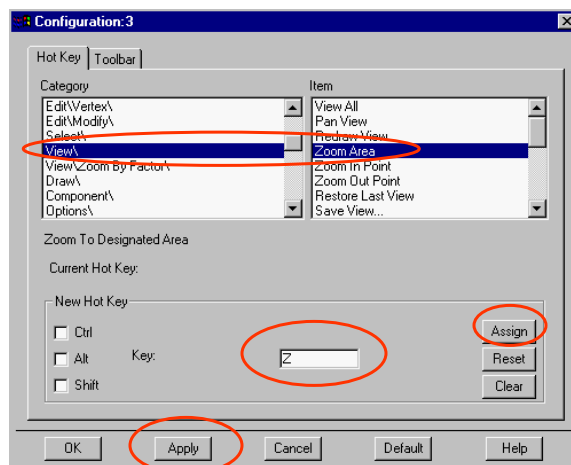Click: **Options > Hot Key / Toolbar Configurations...**




*Follow these steps to set
 Zoom Area command:*

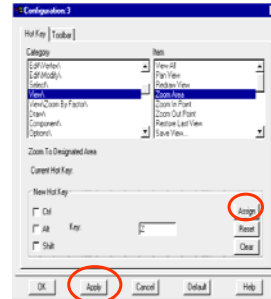1. Select the command
2. Type in a letter: z
 (not case sensitive)
3. Click: **Assign**
4. Click: **Apply**
5. Now, try the Z hot key
 to verify it works.

Next, set these **Hot Keys**
Options > Hot Key / Toolbar Configurations...

S = Simulate > Setup
 A = Activate
 D = Deactivate
 X = Edit > Move > Move & Disconnect
 and any others you want ...




You will be able to use these hotkeys for all the labs in this project.

When everyone has finished, continue →

If desired, set Schematic Preferences


Click: **Options > Preferences**

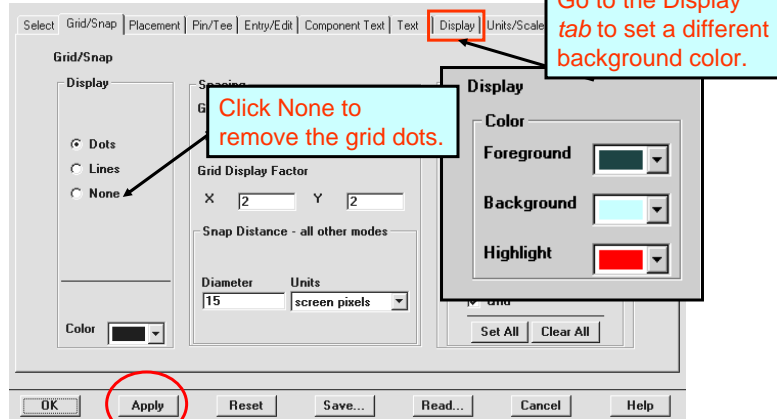

NOTE: Set wire color in - Options > Layers. →

Save the schematic preferences

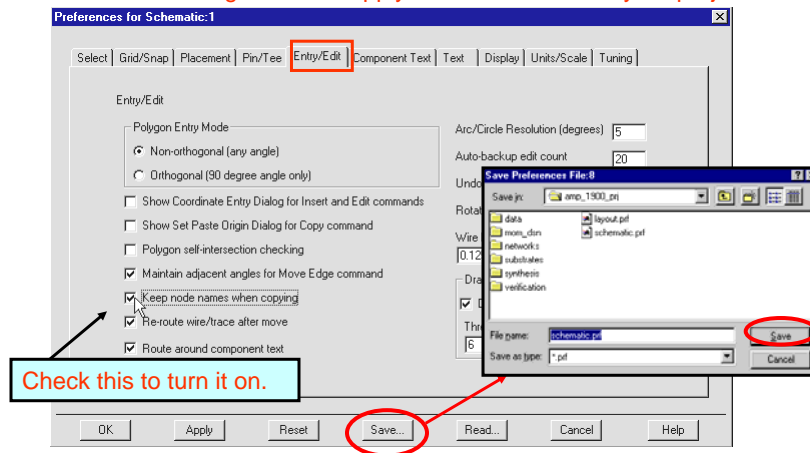...and the settings will then apply to all schematics in your project.




You can also **Read** the **.prf** file into other projects.

★ End of class exercise.



Topic 3:

DC Simulations and sub-circuit modeling

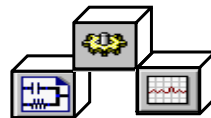


DC Simulation

You get steady-state DC voltages and currents according to Ohm's Law: $V=IR$



- Capacitors = treated as ideal open circuits
- Inductors = treated as ideal short circuits
- Topology check: dc path to ground (if not => error message)
- Kirchoff's Law satisfied: sum of node current = 0
- Convergence simulator algorithms (modes) can be set

DC simulation controller

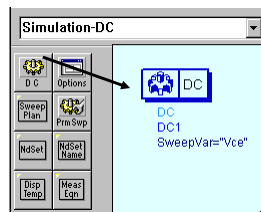
Simulation Controller and Editor (dialog box)



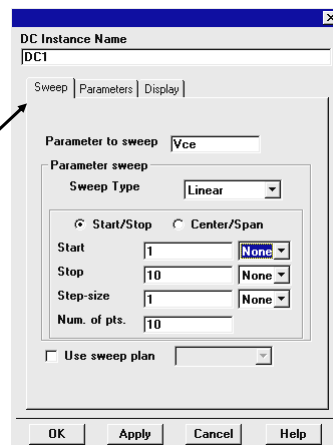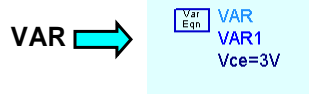Sweep: allows you to sweep a parameter but it must be defined as a variable. Note the dialog entry automatically puts quotes on the controller (screen) entry.





...more on DC

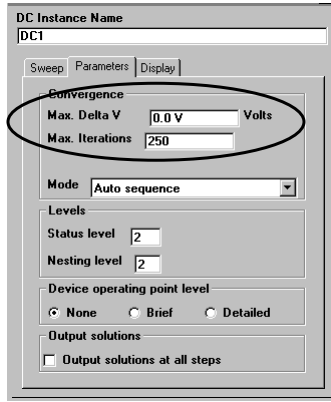

Convergence: increase V or iterations or change mode if you don't converge.

Example: device operating point

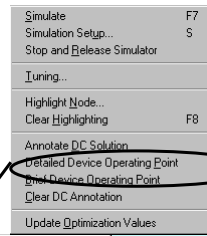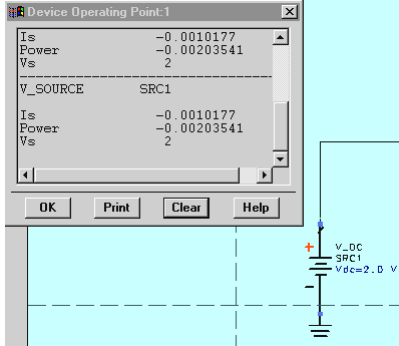


Back Annotation



No settings necessary!



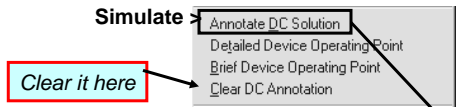Immediately after DC simulation, currents and voltages are available. Click: **Simulate > Annotate DC Solution**.



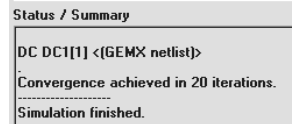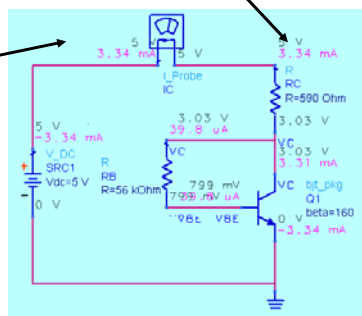Current Probe = use values of current in the dataset.



Minus sign used for current flowing out of a connection. Otherwise, current flows into a connection or device.


DC Simulation Controller is required in all simulations if you want DC annotation.



What the lab is about ...


Lab 3:

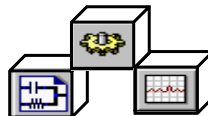DC Simulations and modeling the sub-circuit



Steps in the Design Process

You are here: 

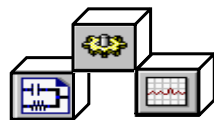

- Design the *rf_sys* behavioral model receiver
- Test conversion, budget gain, spectrum, etc.
- **Start amp_1900 design – subckt parasitics**
- **Simulate amp DC conditions & bias network**
- Simulate amp AC response - verify gain
- Test amp noise contributions – tune parameters
- Simulate amp S-parameter response
- Define amp matching topology and tune input
- Optimize the amp in & out matching networks
- Filter design – lumped 200MHz LPF - use E-Syn
- Filter design – microstrip 1900 MHz BPF
- Transient and Momentum filter analysis
- Amp spectrum, delivered power, Z_{in} - HB
- Test amp comp, distortion, two-tone, TOI
- CE basics for spectrum and baseband
- CE for amp_1900 with GSM source
- Replace amp and filters in *rf_sys* receiver
- Test conversion gain, NF, swept LO power
- Final CDMA system test CE with fancy DDS
- Co-simulation of behavioral system

Start with some specifications...

AMP with max gain & low noise:

Available voltage: 5 volts
Device: Generic BJT (Gummel-Poon)
Collector current: 3.25 mA
Frequency: RF = 1900 MHz
Gain: >10 dB (or much more with this model)
50 ohm match input/output

Filters: also, build 1900 MHz BPF for the input and a LPF for the IF output


Later on, test the AMP for TOI, distortion, noise, compression,
GSM & CDMA modulation response, and more in labs 3 through 9.

YOUR JOB: Build, test, and refine the circuits to meet specifications.


Start with a sub-circuit model... 

Model the device with package parasitics

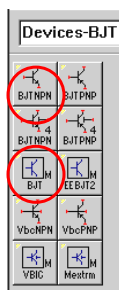Create a sub-circuit to model your components:



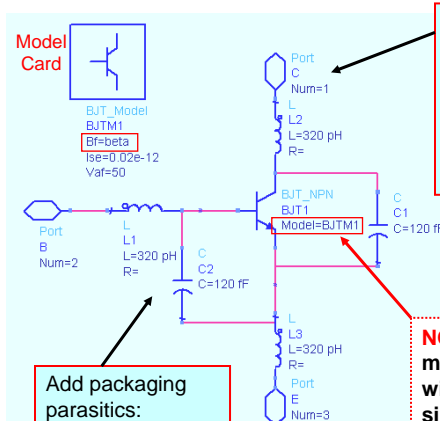Insert a device and a model: Gummel-Poon BJTM1. Bf will be a passed parameter. Vaf is changed as shown.




Add packaging parasitics:
L in pico: pH
C in femto: fF

Port connector numbers: **Num=** must be set in specific order as shown - this is necessary to use ADS built in transistor symbol.

NOTE: BJTM1 is the model card name that will be used for simulation. Library devices do not require this mapping.


Select a symbol for your sub-circuit

View Create/Edit Schematic Symbol

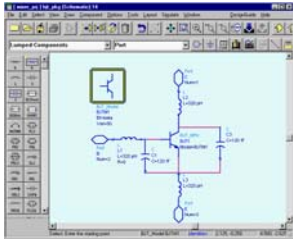

Schematic view


View Create/Edit Schematic

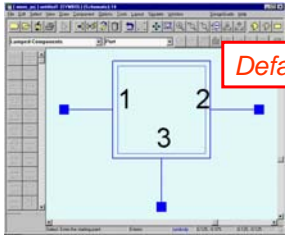


Symbol view

Default Symbol

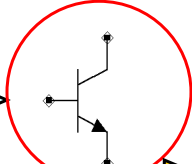To use a built-in ADS symbol that looks like an NPN BJT use **File > Design Parameters**. Or, draw your own symbol!




It's easy to use a built-in symbol:




Define the sub-circuit parameters: 2 tabs

Click: File > Design / Parameters

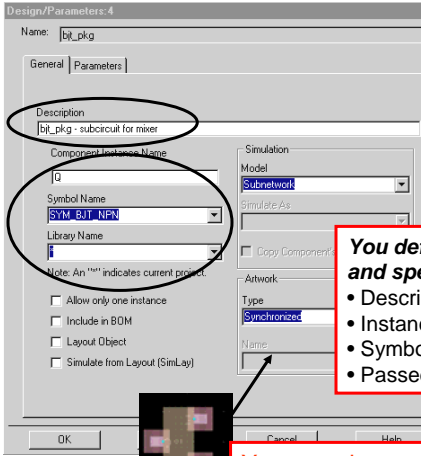

You can also specify the layout: sot23

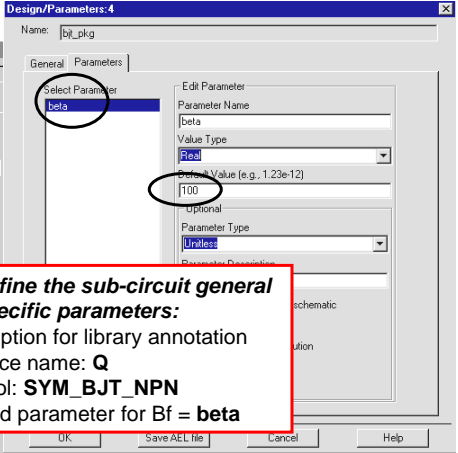

You define the sub-circuit general and specific parameters:

- Description for library annotation
- Instance name: **Q**
- Symbol: **SYM_BJT_NPN**
- Passed parameter for Bf = **beta**

Insert the model in a new schematic



Insert the sub-circuit from the library.

Design parameters follow the sub-circuit: Q1, beta, etc.

ICONS: Push into and Pop out of the hierarchy.

Set up a DC curve sweep with a template

Schematic template also has the data display template:

Your model (**bjt_pkg**) with annotation and passed parameter: beta.

Data display template:

Use with BJT_curve_tracer Schematic Template

IC1, mA

VCE

Initialized VARs:
VCE = 0 V
IBB = 0 A



NOTE: DC controller sweeps the X-axis and the Parameter Sweep, sweeps the Y-axis.

Finally, calculate and test the bias network

Calculate resistor values, verify the DC specs for I_b and I_c , and sweep temperature!


Datasets and Equations

Bias Resistor Calculations		
	Rb[3]	Rc[3]
Equations	55029.037	594.350
Rb		
Rc		

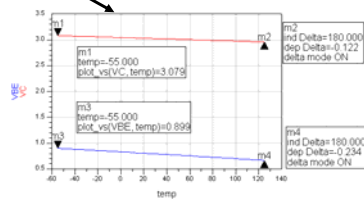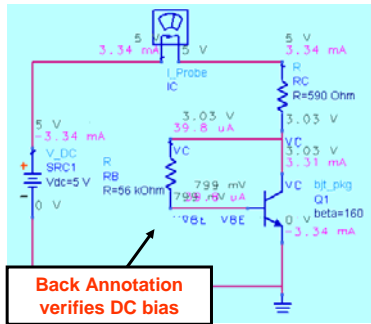

Topic 4:

AC Simulation and Tuning Parameters

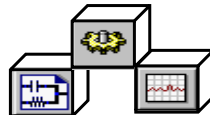

AC Simulation

*You get linear small-signal response
and you get Noise values:*


- DC analysis performed (unseen)
- Nonlinear devices are linearized
- Kirchoff's Law satisfied: sum of node current = 0
- Noise contributors defined and listed
- Budget analysis available (for named nodes)
- Signal voltages are peak - noise voltages are RMS

AC Simulation Controller

```
AC
AC1
SweepVar="freq"
Start=100 MHz
Stop=4 GHz
Step=10 MHz
CalcNoise=no
NoiseNode[1]="Vout"
```

AC is a linear or small signal simulation and **freq** is usually set in the controller not the source.

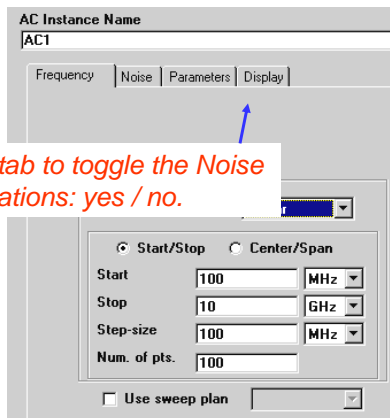Use Display tab to toggle the Noise calculations: yes / no.



Turn on and set up Noise calculation

Click here:

NOTE: Port Noise can be included in the simulation, but it does not apply to NF. Also, Port noise is turned on/off in the sources.

AC Instance Name: AC1

Frequency Noise Parameters Display

Calculate noise

Nodes for noise parameter calculation

Select	Edit
"Vout"	Vout

Add Cut Paste

Noise contributors

Mode: Sort by name

Dynamic range to display: dB

Include port noise in node noise voltages

Bandwidth: 1 Hz

OK Apply Cancel Help


Your Node Names

Sort by name or by value: in the dataset

Blank gives you all contributors

Use specific sources for specific simulations

Use AC sources for AC simulations!

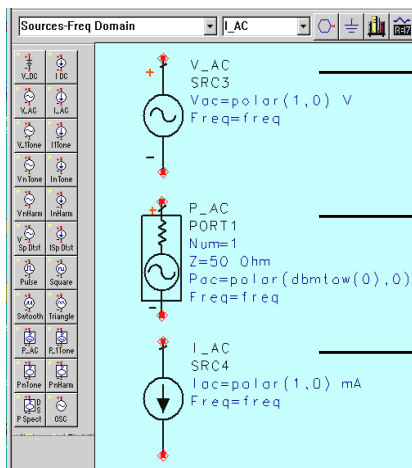

Source parameter definitions:

- **V_AC** is the component name
- **SRC3** is the instance name (you can change this)
- **Vac = polar (1,0)V** is the default
- **Freq = freq** is a global variable - you set the start & stop values in the simulation controller
- **P_AC** is the component name
- **PORT1** is the instance name (OK to change)
- **Num=1** is the port number (use for S-parameters)
- **Pac = polar (dbmtoW(0),0)** dbmtoW is a function - you enter the dbm value (*see note)
- **I_AC** is the component
- **Iac=polar (1,0) mA** is the default
- Arrow is the direction of current flow.

More on AC source settings... →


Setting AC source values

POWER SETTINGS: The dbmtow function converts power in dbm to watts for the simulator.

PHASE: The polar function specifies phase. By default, all sources are cosine waves. Use -90 for a sinewave.


NOISE and Vdc: By default, noise is turned on for the P_AC source. Use Display tab/settings to make visible. Vdc 10 mV is an offset (superposition).

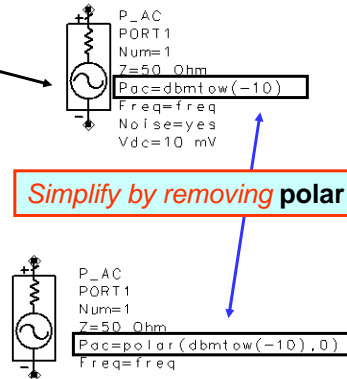Equations can also be used: $P=1W$, $P=1+j*1W$, $P=complex(1,0)$, etc.




Review of ADS Equations

- **VAR:** pre-simulation - Use for initializing sweep variables or other settings. VARs are not available in the dataset unless the OutVar function is used (later labs).
- **MeasEqn:** pre-simulation - Use for calculations to be available in the dataset (can use node names and functions).
- **Eqn:** post-simulation - Use for calculations in the data display (can include node voltages, functions, and any other dataset data).

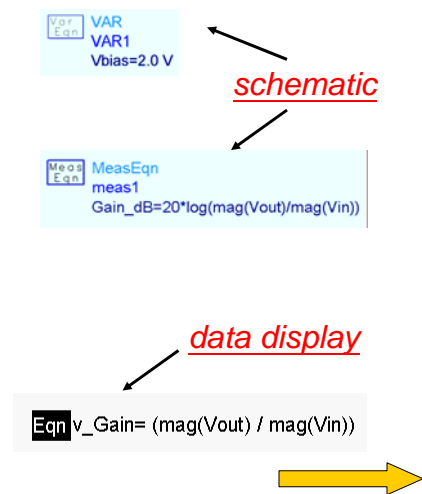

Review the Data Display equation editor

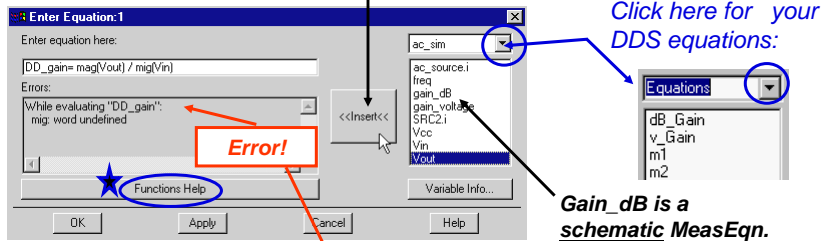Insert button gives full path (dataset..) if not the default.




Invalid equations are red:

EqnDD_gain= mag(Vout) / m1g(Vin)

Valid equations are black:


EqnDD_gain= mag(Vout) / mag(Vin)

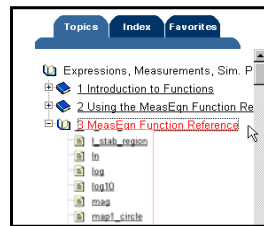★ Click **Functions Help** for on-line manuals:



TIP for copy/paste in the Data Display

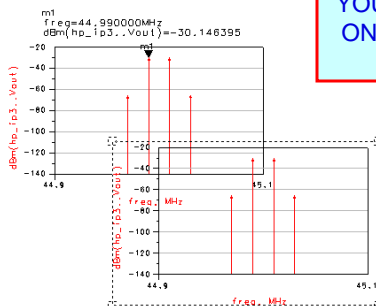- Keyboard keys: **Ctrl C** copies to the buffer
- Keyboard keys: **Ctrl V** pastes from the buffer



YOU CAN COPY A PLOT FROM ONE DATA DISPLAY WINDOW TO ANOTHER ALSO!


UNIX users probably know this but it works for ADS on the PC also. Try copying a plot or equation now!



What the lab is about ...


Lab 4:

AC Simulations and Tuning Parameters

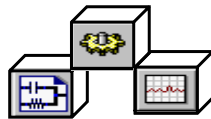


Steps in the Design Process

You are here: 

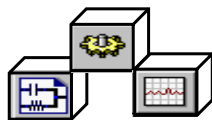

- Design the *rf_sys* behavioral model receiver
- Test conversion, budget gain, spectrum, etc.
- Start *amp_1900* design – subckt parasitics
- Simulate amp DC conditions & bias network
- **Simulate amp AC response - verify gain**
- **Test amp noise contributions – tune parameters**
- Simulate amp S-parameter response
- Define amp matching topology and tune input
- Optimize the amp in & out matching networks
- Filter design – lumped 200MHz LPF - use E-Syn
- Filter design – microstrip 1900 MHz BPF
- Transient and Momentum filter analysis
- Amp spectrum, delivered power, Z_{in} - HB
- Test amp comp, distortion, two-tone, TOI
- CE basics for spectrum and baseband
- CE for *amp_1900* with GSM source
- Replace amp and filters in *rf_sys* receiver
- Test conversion gain, NF, swept LO power
- Final CDMA system test CE with fancy DDS
- Co-simulation of behavioral system

Set up the circuit & simulate with Noise

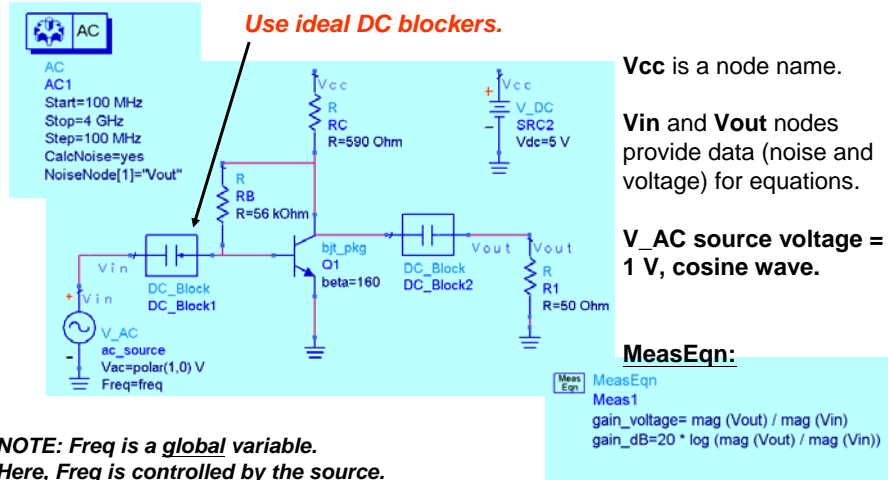

NOTE: *Freq* is a global variable.
 Here, *Freq* is controlled by the source.
 Use *freq=freq*, *freq=10 MHz*, or a variable: *freq=F_RF*.

Simulation results...



Two schematic MeasEqns: One Data Display eqn:

freq	gain_dB	gain_voltage	DD_gain
1.500GHz	14.736	5.455	5.455
1.600GHz	14.649	5.401	5.401
1.700GHz	14.559	5.345	5.345
1.800GHz	14.465	5.287	5.287
1.900GHz	14.368	5.229	5.229
2.000GHz	14.268	5.169	5.169
2.100GHz	14.165	5.108	5.108
2.200GHz	14.061	5.047	5.047


Write the same equation in Data Display as you did in schematic. Then put it in a list.

Eqn $dB_Gain=20*\log(\text{mag}(Vout) / \text{mag}(Vin))$

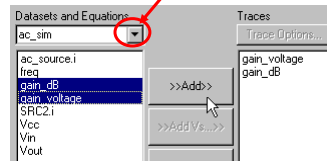
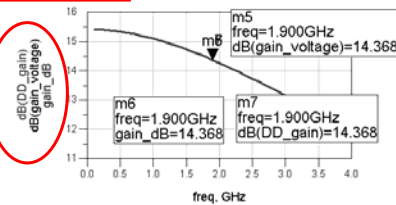
Edit the traces on-screen: all are equal.






More AC results...

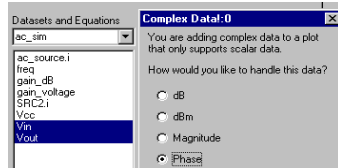

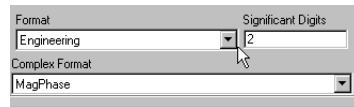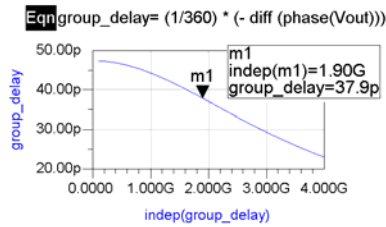Calculate group delay with an equation using Phase data. Also, control marker readout formats.



Use the *what* function... *what*?

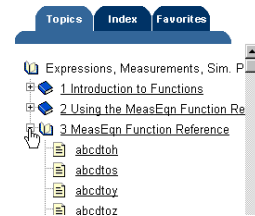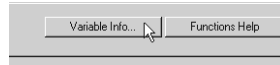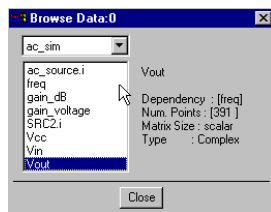

Examine the data using the *what* function and the **Variable Info**.

what (Vout)	
Dependency :	[freq]
Num. Points :	[391]
Matrix Size :	scalar
Type :	Complex

freq	what (Vout)
100.0MHz	5.901 / 178.294
200.0MHz	5.895 / 176.598
300.0MHz	5.883 / 174.891
400.0MHz	5.868 / 173.199



Sweep battery voltage




For an AC simulation, use a **parameter sweep** of a dc value which is assigned to a **VAR**.

PARAMETER SWEEP


```

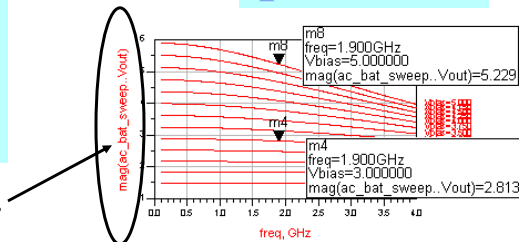ParamSweep
Sweep1
SweepVar="Vbias"
SimInstanceName[1]="AC1"
SimInstanceName[2]=
SimInstanceName[3]=
SimInstanceName[4]=
SimInstanceName[5]=
SimInstanceName[6]=
Start=2
Stop=5
Step=0.25
        
```




Note the explicit dataset path..

OPTIONAL - tune sub-circuit parameters

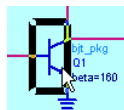

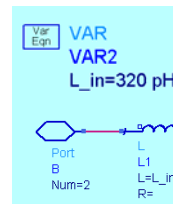Set up a **variable** in the sub-circuit and tune several parameters from the top level.



Tune Control:9

Select a parameter to tune by clicking on it

Simulate: After each change


Trace History: 7 Time

ac_sim.VAR2.L_in (pH) 390.40

ac_sim.R1.R (Ohm) 36.900

ac_sim.Q1.beta 172.800

Update Details Reset Cancel Help

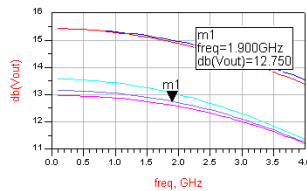


Start the lab now!





Topic 5:

S-parameter Simulation and Optimization

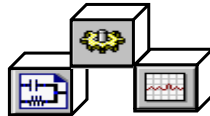

S-parameters are Power Ratios

(voltage ratios squared)

S-parameter ratios: S_{out} / S_{in}

- S11 - Forward Reflection (input match - impedance)
- S22 - Reverse Reflection (output match - impedance)
- S21 - Forward Transmission (gain or loss)
- S12 - Reverse Transmission (isolation)

These are best viewed on a Smith chart (next slides).




These are easier to understand and simply plotted.

Results of an S-Parameter Simulation in ADS


- Read the complex reflection coefficient (Gamma)
- Change the marker readout for Z_0
- Read all four S-parameters
- Smith chart plot: use for impedance matching (S11 and S22)
- Similar to Network Analyzer measurements

The Impedance Smith Chart simplified...

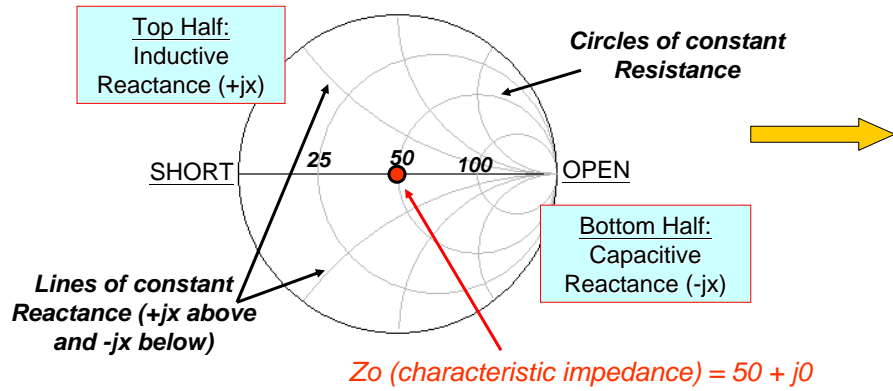This is an impedance chart transformed from rectangular Z .
 Normalized to 50 ohms, the center = $R50+J0$ or Z_0 (perfect match).
 For S_{11} or S_{22} (two-port), you get the **complex impedance**.



The Smith chart in ADS Data Display

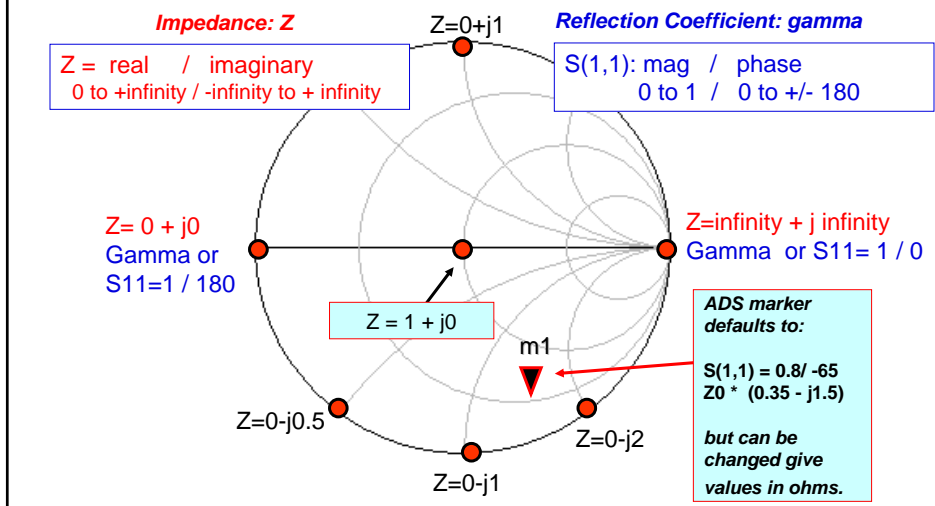

S-Parameter Simulation Controller

Default sweep = Freq

The simulator requires port termination: Num = 1

S-PARAMETERS

S_Param
SP1
Start=100 MHz
Stop=4 GHz
Step=100 MHz

Term
Term1
Num=1
Z=50 Ohm

Scattering-Parameter Simulation:2

S_Param Instance Name
SP1

Frequency Parameters Noise Display

Frequency

Sweep Type: Linear

Start/Stop Center/Span

Start: 100 MHz
Stop: 4 GHz
Step-size: 100 MHz
Num. of pts.: 40

Use sweep plan

OK Apply Cancel Help

Sweep plan can also be used (see next slide). Either way, simulation data (S matrix) will be for the specified range and points.



Other S-Parameter controller tabs

Parameters

S_Param Instance Name
SP1

Frequency Parameters Noise Display

Calculate

- S-parameters
- Y-parameters
- Z-parameters
- Group delay

Group delay aperture: 1e-4

Frequency Conversion

- Enable AC frequency conversion
- S-parameter freq. conv. port: 1

Levels

Status level: 2 Nesting level: 2

Device operating point level

None Brief Detailed

Calculate other parameters.

Enable Frequency Conversion for a mixer.

Calculate SS noise - same as in the AC simulation.

NOTE: Insert the Options controller for a noise simulation = no error message on temperature.

Noise

S_Param Instance Name
SP1

Frequency Parameters Noise Display

Calculate noise

Noise contributors

Mode: Off

Dynamic range to display: dB

Bandwidth: 1.0 Hz

OPTIONS

- Options1
- Temp=25
- TopologyCheck=yes
- V_RefTol=1e-6
- I_RefTol=1e-6
- GiveAWarnings=yes
- MaxWarnings=10

Yellow arrow pointing right.

Sweep Plan with S-parameter simulations

Sweep Plan is for sweeping **FREQ.**
Otherwise, use a **Parameter Sweep**
for variables (Vcc, pwr, etc.)

S-PARAMETERS

S_Param
SP1
SweepPlan="SwpPlan1"
Start=100 MHz
Stop=4 GHz
Step=100 MHz

These are ignored if Sweep plan is selected!

SWEEP PLAN

SweepPlan
SwpPlan1
Start=100 MHz Stop=4 GHz Step=100 MHz Lin=
Start=1.8 GHz Stop=2.0 GHz Step=2 MHz Lin=
UseSweepPlan=
SweepPlan=

Sweep Plan:2

Sweep Plan
SweepPlan Instance Name
SwpPlan1

Parameter
Pl=100 MHz
Pl=1800 MHz
Pl=1900 MHz

Sweep Type
Single point

Start/Stop Center/Span
Start/Stop

Parameter
100 MHz

Stop
None

Step-size
None

Num. of pts.
None

Add Cut Paste Next Sweep Plan

OK Apply Cancel Help


Mixer designers:
Here is a plan for an
RF, LO, and IF.

Here is a sweep within a sweep.




Typical S-parameter plots: ADS data display

Plotted S21 in dB vs frequency

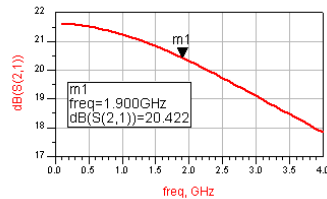

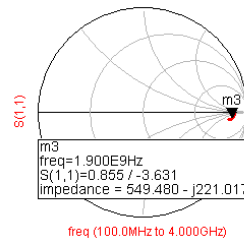Plotted S11 on a Smith Chart:
note marker readout.




Complete S-matrix with port impedance

freq	S				freq	PortZ	
	S(1,1)	S(1,2)	S(2,1)	S(2,2)		PortZ(1)	PortZ(2)
100.0M...	0.8787 / ...	2.392E-...	12.038 / ...	0.9947 / ...	100.0M...	50.000 / ...	50.000 / ...
200.0M...	0.878 / ...	7.976E-...	12.020 / ...	0.993 / ...	200.0M...	50.000 / ...	50.000 / ...
300.0M...	0.878 / ...	1.729E-...	11.894 / ...	0.992 / ...	300.0M...	50.000 / ...	50.000 / ...
400.0M...	0.877 / ...	2.556E-...	10.019 / ...	0.994 / ...	400.0M...	50.000 / ...	35.000 / ...
500.0M...	0.877 / ...	4.007E-...	9.982 / ...	0.993 / ...	500.0M...	50.000 / ...	35.000 / ...
600.0M...	0.876 / ...	5.816E-...	9.938 / ...	0.991 / ...	600.0M...	50.000 / ...	35.000 / ...
700.0M...	0.875 / ...	8.013E-...	9.888 / ...	0.990 / ...	700.0M...	50.000 / ...	35.000 / ...

Note marker readout is x50.




S-Parameter measurement equations

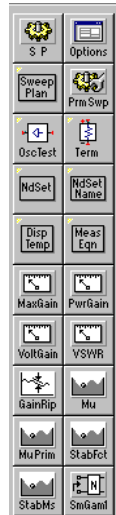


All simulation palettes have specific measurement equations. You insert the measurement equation and set the arguments if necessary. Here, S is the matrix, 30 is the value in dB, and 51 points used to draw the circle.

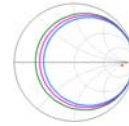Example: 3 circles for 3 different values of gain.




Arguments explained briefly here.

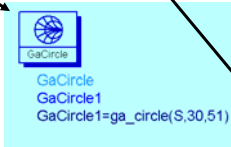

You will use some of these in the labs...

Creating Matching Networks

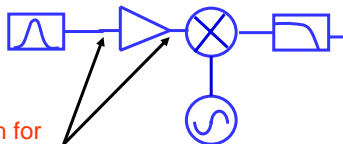- Various topologies can be used: L, C, R
- Avoid unwanted oscillations (L-C series/parallel)
- Yield can be a factor in topology (sensitivity)
- Use the fewest components (cost + efficient)
- Sweep or tune component values to see S-parameters
- Optimization: use to meet S-parameter specs (goals)



In the lab, you will optimize the match for the amplifier.

NOTE: For a mixer, match S11 @ RF and S22 @ IF.


Matching means:

Moving toward the center of the Smith Chart!

Add Series or Parallel (shunt) components.

You will do this in the lab.

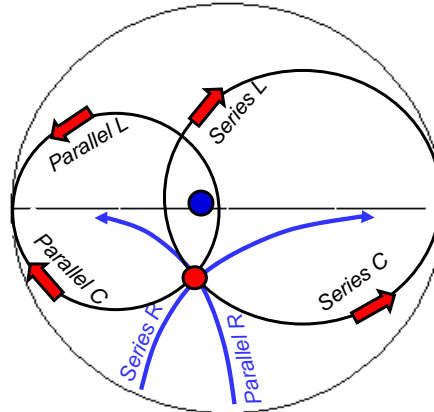Adjust the value to move toward open, short, L, C, or center of chart.



ADS Optimization Basics

DEFINITION: Optimization is a simulation that tries to achieve a performance goal.


- ➔ Start with a simulation that gives you results.
- ➔ Set up the optimization which includes:
 - 1. A search method.
 - 1. A specific goal or specification to be met.
 - 1. Enabled components or parameters to be adjusted.

NOTE: ADS has both continuous and discrete optimization. Yield analysis or a yield optimization is also available.




Optimization palette: Controller and Goals


Four steps for optimization:

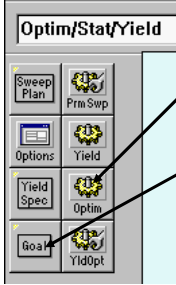


Optim controller: set the type, etc.

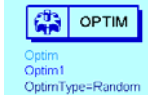


Goal statement: use valid measurement equation or dataset expression.



Enable component (opt).



Simulation controller.

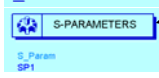

Type of Optimization:
In general, we recommend using Random first, then using Gradient. Also, first tune and then optimize.

Many Types are Available

Random & Gradient are often used together...

Optimizer	Description
Random	Random search method with least-squares error function
Random Minimax	Random search method with minimax error function
Gradient	Gradient search method with least-squares error function
Gradient Minimax	Gradient search method with minimax error function
Quasi-Newton	Quasi-Newton search method with least-squares error function
Least P th	Quasi-Newton search method with least P th error function
Minimax	Two-stage, Gauss-Newton/Quasi-Newton method with minimax error function
Random Max	Random search method with procedure to internally negate the error functions to get error function maximization (worst case analysis)
Discrete	Discrete optimization, provided there is at least one discrete valued optimization parameter in the design.
Genetic	Direct search method using evolving parameter sets

NOTE: See manual for details (*minimax* function works well for filters).

Goals and Error Function

- The goals are minimum or maximum target values.
- The error function is based on the goal(s).
- The weighting factor prioritizes multiple goals.


Error function is defined as a summation of residuals.
A residual r_i may be defined as:

$$\longrightarrow r_i = W_i | m_i - s_i | \quad \longrightarrow$$

- s_i is the simulated i th response (example: $S_{21} = 9.5\text{dB}$)
- m_i is the desired response for the i th measurement (example: $S_{21} = 10\text{dB}$)
- W_i is the weighting factor for multiple goals: higher number is greater.

Simulations continue until the maximum iterations is reached or the error function (summation of the residuals) reaches zero (same as 10 dB).

More about the Error Function...

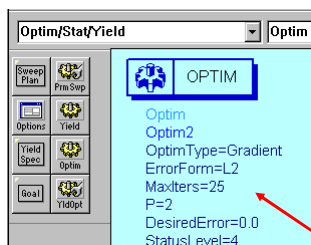

Least Squares: Each residual is squared and all terms are then summed. The sum of the squares is averaged over frequency.

Choice of optimizer determines these settings.


Least Pth: The Least Pth error function formulation is similar to the previous one, except that instead of squaring the residuals, it raises them to the Pth power with $P=2, 4, 6$ etc.

Minimax: attempts to minimize the largest of the residuals. This tends to result in equal ripple responses .


Worst case: minimizes the reciprocal of the least squares error function. This has the effect of maximizing the error function. The goal is to find a worst typical response for a given set of parameters. →

Using a combined approach...

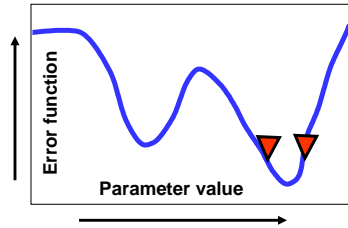Random analysis often gets you close to the goal (minimum error function).



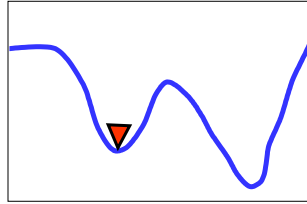
Gradient analysis may get stuck in a local minimum (not optimal error function).



Using both **RANDOM** and **GRADIENT** can reach the desired goal - others work similar (genetic, etc.).



NOTE: Random is not totally random. It uses an adaptation that helps it move closer to the goal.

You will do this in the lab!

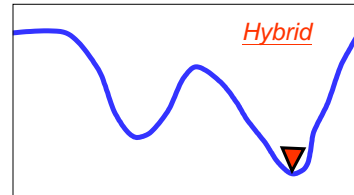

ADS Optimization Setup

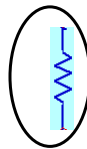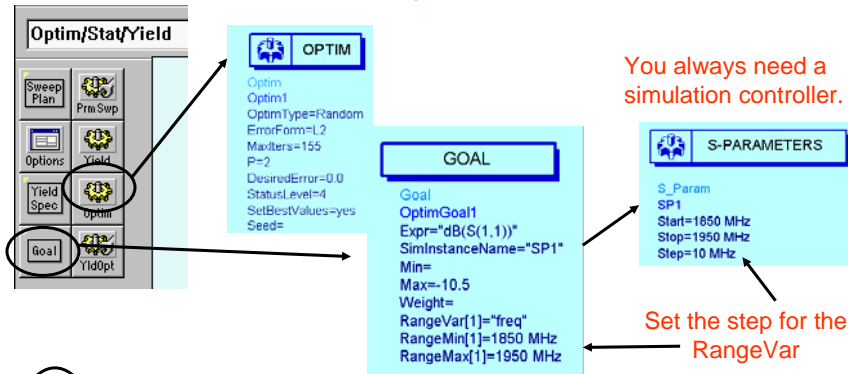Optim palette: insert controller and goal (more on this later)



Edit the component, then click to **enable** for optimization.

Optimization/Statistics Setup...



Details on next slide:

Enabling components for opt or stats (yield)

PPT is an optimization within a Yield Analysis only. Allows value to be shifted to achieve goal.

Once enabled, you can specify a continuous or discrete (stepped) variation..

Gaussian, Uniform, or discrete. Results will be viewable in the data display.

NOTE: If discrete values are not realistic, use file based: DAC



R=100 kOhm opt{ discrete 80 kOhm to 100 kOhm by 10 kOhm }

noopt = disabled (after optimization):

R=96.527 kOhm noopt{ discrete 80 kOhm to 100 kOhm by 10 kOhm }


Discrete Optimization for Library Parts

Inserted library part with listed range of values (like a DAC)

Yield Analysis: % meeting specs!

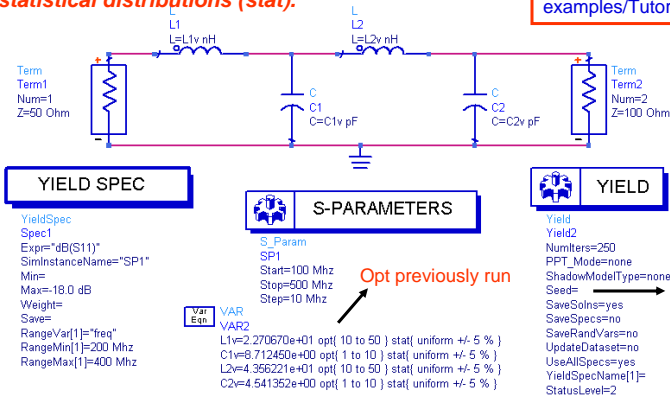Example: 200-400 MHz (50-to-100 ohm) Impedance Transformer. Simulation tests the % of circuits to meet spec using component values with defined statistical distributions (stat).

NOTE: Optimize yield results by changing the nominal values until you get maximum (near 100%). See: examples/Tutorial/yldoptex1_prj




★ **As an extra exercise:** Step 1- Copy: [examples / Tutorial / yldex1_prj](#)

Yield Analysis Results (data)


Step 2 - Run the simulation once. Then change the specs and resimulate. Or, try it on your own circuit!

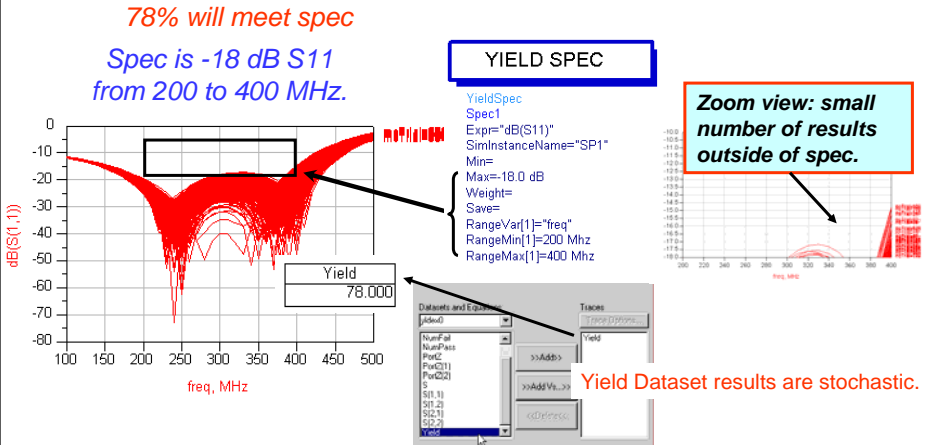Refer to this and the previous slide to setup your own Yield analysis after the class.



Additional information: *frequency sensitive components!*

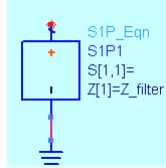Z-PORT: equation describes changing Z with changing freq





Note the ADS syntax for Z increasing as
freq (global variable in ADS) decreases:

if then elseif then elseif then else endif

```

VAR
VAR1
Z_filter=if freq < 1 GHz then 100 elseif freq < 500 MHz then 1K elseif freq < 1MHz then 10K else 1M endif
    
```

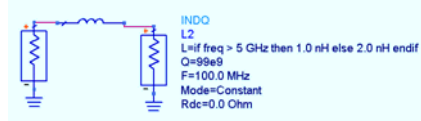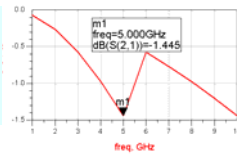
CAPQ and INDQ: equation describes changing L or C with freq



What the lab is about ...


Lab 5:

S-parameter Simulation and Optimization

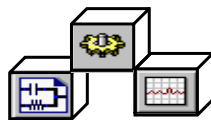


Steps in the Design Process

You are here:

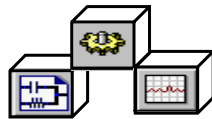


- Design the *rf_sys* behavioral model receiver
- Test conversion, budget gain, spectrum, etc.
- Start *amp_1900* design – subckt parasitics
- Simulate amp DC conditions & bias network
- Simulate amp AC response - verify gain
- Test amp noise contributions – tune parameters
- **Simulate amp S-parameter response**
- **Define amp matching topology and tune input**
- **Optimize the amp in & out matching networks**
- Filter design – lumped 200MHz LPF - use E-Syn
- Filter design – microstrip 1900 MHz BPF
- Transient and Momentum filter analysis
- Amp spectrum, delivered power, Z_{in} - HB
- Test amp comp, distortion, two-tone, TOI
- CE basics for spectrum and baseband
- CE for *amp_1900* with GSM source
- Replace amp and filters in *rf_sys* receiver
- Test conversion gain, NF, swept LO power
- Final CDMA system test CE with fancy DDS
- Co-simulation of behavioral system

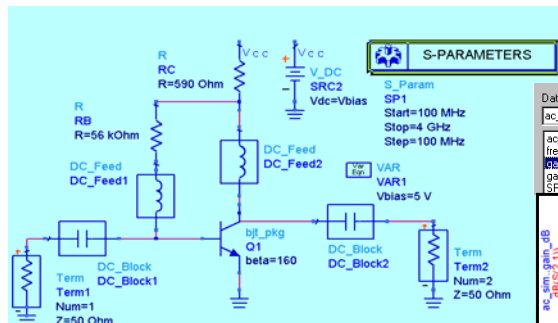First Step: Simulate with ideal components



2 different datasets

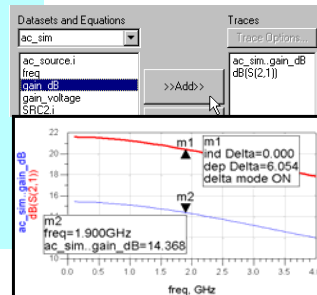

- Plot the data and compare to *ac_sim* data.
- Change Term Z and list the S matrix.

freq	S				freq	PortZ	
	S(1,1)	S(1,2)	S(2,1)	S(2,2)		PortZ(1)	PortZ(2)
100.0M...	0.879 / ...	2.392E-...	12.036 /...	0.994 / ...	100.0M...	50.000 /...	50.000 /...
200.0M...	0.879 / ...	7.978E-...	12.020 /...	0.993 / ...	200.0M...	50.000 /...	50.000 /...
300.0M...	0.878 / ...	1.729E-...	11.994 /...	0.992 / ...	300.0M...	50.000 /...	50.000 /...
400.0M...	0.877 / ...	2.559E-...	10.019 /...	0.994 / ...	400.0M...	50.000 /...	35.000 /...
500.0M...	0.877 / ...	4.007E-...	9.982 / ...	0.993 / ...	500.0M...	50.000 /...	35.000 /...
600.0M...	0.876 / ...	5.818E-...	9.939 / ...	0.991 / ...	600.0M...	50.000 /...	35.000 /...
700.0M...	0.875 / ...	8.013E-...	9.888 / ...	0.990 / ...	700.0M...	50.000 /...	35.000 /...



Calculate C and L values and re-simulate

Reactance of 10 pF at 1.9 GHz and a list of L values:

$$\text{Eqn } X_c = -1 / (2 * \pi * 1900\text{M} * 10\text{e-}12)$$




Cap value: reactance at 1900 MHz

Xc	-8.377
----	--------

$$\text{Eqn } X_L = 2 * \pi * 1900\text{M} * L_val$$




$$\text{Eqn } L_val = [1\text{n} :: 10\text{n} :: 200\text{n}]$$

L_val	XL
7.100E-8	847.602
8.100E-8	968.392
9.100E-8	1088.383
1.010E-7	1205.743
1.110E-7	1325.124
1.210E-7	1444.504
1.310E-7	1563.885

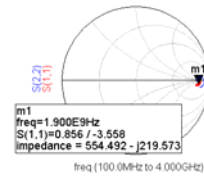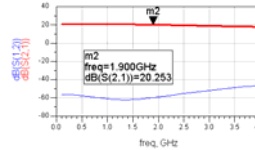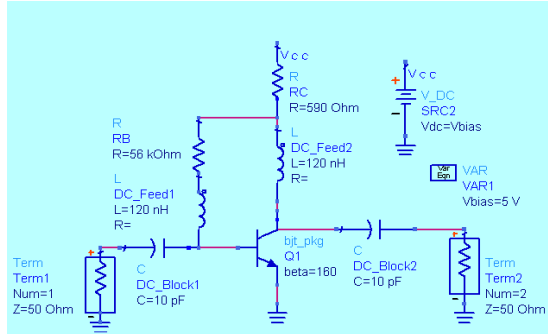

Tune the input match

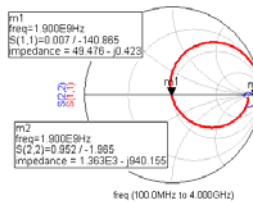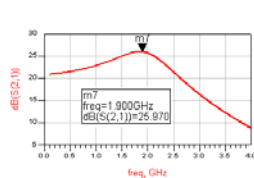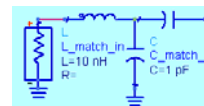Use detailed Tune control with small increments!



Optimize the output & input match

The screenshot shows the Optimizer software interface with the following components:

- OPTIM Panel:**
 - Optim Type=Random
 - Error Form=L2
 - Maxiters=125
 - P=2
 - DestiredError=0.0
 - StatusLevel=4
 - SetBestValues=yes
 - Seed=
 - SaveSols=yes
 - SaveGoals=no
 - SaveOptimVars=no
 - UpdateDataset=yes
 - UseAllGoals=yes
- GOAL Panel 1:**
 - Goal: OptimGoal1
 - Expr="dB(S(1,1))"
 - SimInstanceName="SP1"
 - Min=
 - Max=-10
 - Weight=
 - RangeVar[1]="freq"
 - RangeMin[1]=1850 Mhz
 - RangeMax[1]=1950 Mhz
- GOAL Panel 2:**
 - Goal: OptimGoal2
 - Expr="dB(S(2,2))"
 - SimInstanceName="SP1"
 - Min=
 - Max=-10
 - Weight=
 - RangeVar[1]="freq"
 - RangeMin[1]=1850 Mhz
 - RangeMax[1]=1950 Mhz
- Optimization Settings Panel:**
 - Optimization Status: Enabled
 - Type: Continuous
 - Format: min/max
 - Nominal Value: 14.3 nH
 - Minimum Value: 1 nH
 - Maximum Value: 40 nH
 - Post Production Tuning:
- Circuit Diagrams:**
 - Top: L-match_out circuit with L=10 nH, R, and C-match_out C=0.5 pF.
 - Bottom: L-match_in circuit with L=14.3 nH opt{ 1 nH to 40 nH } and R.

Optimization Goals:

- Random with 2 goals
- S11: -10 dB
- S22: -10 dB

REVIEW of 4 steps:

- Set up the OPTIM controller
- Set up the GOALS
- Enable the components
- Setup the simulation

Display opt data, update and simulate

The screenshot displays the optimization results and updated circuit parameters:

Status / Summary:

```

Iteration/Trial #45:
CurrentEF: 0
Optimization variables:
C_match_in.C = 339.738e-15
C_match_out.C = 216.617e-15
L_match_out.L = 27.1488e-09
L_match_in.L = 18.4433e-09
Simulation finished: dataset 's_
    
```

Updated Circuit Parameters:

- L-match_in: L=18.5 nH noopt{ 1 nH to 40 nH }, R=
- C-match_in: C=0.34 pF noopt{ 0.01 pF to 1 pF }
- L-match_out: L=27.1 nH noopt{ 1 nH to 40 nH }, R=
- C-match_out: C=0.22 pF noopt{ 0.01 pF to 1 pF }

Simulation Results:

- Plot 1 (dB(S(2,2)) vs freq):** Shows a peak at 1.900 GHz with a value of 38.853 dB. Parameters: m1, freq=1.900GHz, optIter=45, dB(S(2,2))=38.853.
- Plot 2 (dB(S(1,1)) vs freq):** Shows a peak at 1.900 GHz with a value of 35.168 dB. Parameters: m1, freq=1.900GHz, dB(S(1,1))=35.168.
- Plot 3 (dB(S(1,1)) vs freq):** Shows a peak at 1.900 GHz with a value of 33.824 dB. Parameters: m4, freq=1.900GHz, dB(S(1,1))=33.824.
- Plot 4 (dB(S(2,2)) vs freq):** Shows a peak at 1.900 GHz with a value of 12.196 dB. Parameters: m3, freq=1.900GHz, S(2,2)=0.011 / -12.196, impedance=51.037 - j0.227.
- Plot 5 (dB(S(2,2)) vs freq):** Shows a peak at 1.900 GHz with a value of 43.767 dB. Parameters: m2, freq=1.900GHz, S(1,1)=0.204 / -97.480, optIter=23, impedance=43.767 - j18.486.
- Plot 6 (dB(S(2,2)) vs freq):** Shows a peak at 1.900 GHz with a value of 40.979 dB. Parameters: m3, freq=1.900GHz, S(2,2)=0.035 / -105.276, optIter=40, impedance=20 * (0.979 - j0.067).

Final values look good!

Next, use built-in measurements

S-parameter simulation with gain and noise circles, and stability. These are built-in measurement equations from the simulation palette.

GaCircle
GaCircle1
GaCircle1=ga_circle(S,30,51)

NsCircle
NsCircle1
NsCircle1=ns_circle(nf2,NFmin,Sopt,Rn/50,51)

Mu
Mu1
Mu1=mu(S)

MuPrime
MuPrime1
MuPrime1=mu_prime(S)



You set the arguments if necessary!

OPTIONS

Options
Options1
Temp=16.85
TopologyCheck=yes
V_Rat=1e-6
I_Rat=1e-6
GiveAllWarnings=yes
MaxWarnings=10

NOTE: Listed results from noise turned on in the simulation controller.

freq	NFmin	nf(2)	Sopt
1.900GHz	1.075	3.264	0.793 / -20.468

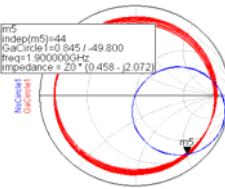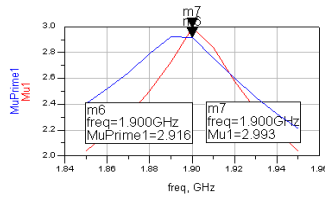

Last step: Read / Write data files

Write an ADS "S" dataset as a Touchstone file, then Read it back in... as if it came from a Network Analyzer!

S-PARAMETERS

S_Param
SP1
SweepPlan="SwpPlan1"

SWEEP PLAN


SweepPlan
SwpPlan1
Start=100 MHz Stop=3 GHz Step=100 MHz
UseSweepPlan=
SweepPlan=

Use a Sweep Plan and compare the data.



Topic 6:

E-Syn, Momentum, Transient and the DAC

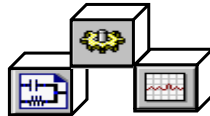


Using *E-Syn* Quick S-parameter simulation

What does E-Syn do?

It makes it easy to create FILTERS and Matching Networks.

E-Syn user interface is a little different than the ADS interface. Also, you could use a Filter Design Guide instead of E-Syn. This may appear in future releases of ADS!

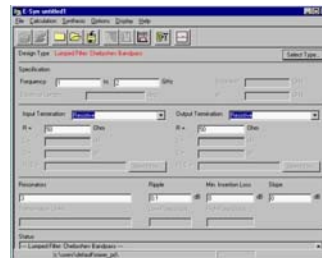- You specify the TYPE of design, the RESPONSE, and the BAND.
- SYNTHESIZE the design and you get a selection of topologies and values.
- ANALYZE the design and plot the response in the ADS data display. Optimize if desired.



Using **Momentum**


**MOM engine gives
S-parameter results**

What is Momentum? E-M (electro-magnetic) solver using Method of Moments technique and Green's functions to compute the current in planar structures, including vias and the coupling between surfaces.

Why use Momentum?


- You have no accurate model for a passive layout.
- You want to know the coupling effects between structures.
- You want to optimize the layout real-estate, performance, etc.
- Your other structure simulator takes too long to simulate!
- You want to use the results in ADS simulations.

Antenna patterns!

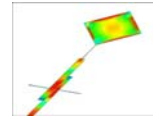

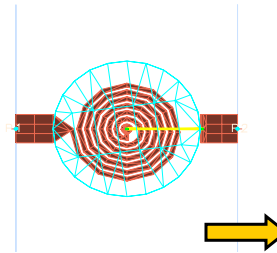Example spiral meshed as a "strip" geometry.

Hole in ground plane is meshed as a "slot", which is more efficient than meshing the entire ground plane.



Transient simulation

- *Analysis performed in the Time Domain*
- *Use any Source*
- *Solutions use Newton_Raphson iterations*
- *You get Amplitude vs. Time*
- *Time Domain data can be transformed: FS*



NOTE on Convolution:

Frequency domain models (microstrip) can be brought into the time domain and converted to the time domain - then convolved with the time-domain input signal to obtain the time-domain output signal. The convolution tab in the transient simulator allows you to define methods and settings.



Transient simulation controller

Integration: step control & error (default:Fixed)

Time Setup | Integration | Convolution | Convergence | Optic

Output Times

Start time: 0.0 nsec

Stop time: 2 / (100 MHz) None

Max time step: 1.0 nsec

Min time step: None

Limit timestep for Transmission Line

Time Step is critical !


Ignored if no TL's

TRANSIENT

Tran Tran1
StopTime=2 / (100 MHz)
MaxTimeStep=1.0 nsec

Setting the Transient Time Step

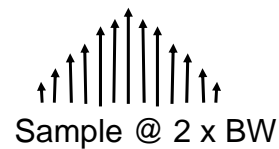Start time: sampling begins
 Stop time: sampling ends
Time step: sampling rate



Use the Nyquist rule: Sample at 2 x or more the rate of the highest frequency of interest:

To sample the fundamental (1900 MHz) plus harmonics, you must calculate @ 2 x (rate of highest harmonic desired).

$$1 / (2 \times 15 \times 1900\text{MHz}) = 17.54 \text{ picoseconds.} \longrightarrow$$


TRANSIENT

Tran Tran1
StopTime=15(1900e6)
MaxTimeStep=1/(2*15*1900e6)



Setting the Transient Stop Time


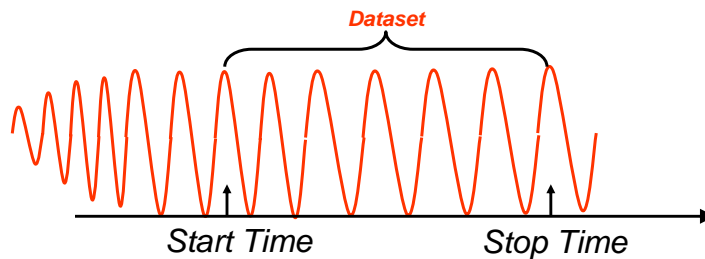
For many circuits: stop time should allow for **periodic - settling**.



NOTE: Transient analysis can be tricky. Sampling before a circuit reaches steady state will not give correct results when transformed into the frequency domain. Also, you must use a time step that is a multiple of the frequencies of interest or the results will not be correct.

Using a **DAC** (data access component)

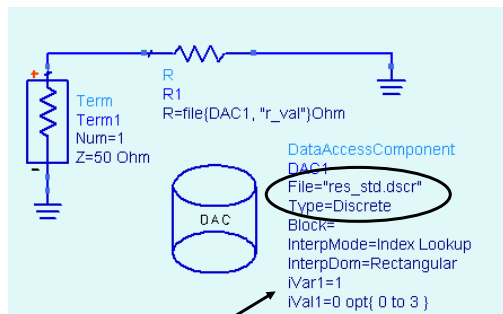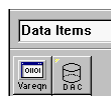For optimization, R1 is assigned to a file which is read by the DAC. "res_std.dscr" contains an index and a list of values (r_val). In the DAC, variable iVal1 is enabled over the range of indexed values beginning with iVar1 which is the first index point in the file.



```
res_std.dscr - Notepad
File Edit Search Help
BEGIN DSCRDATA
% INDEX r_val
1 56
2 68
3 82
4 100
END DSCRDATA
```

The file must be in the DATA directory and must be in correct format. The circuit simulation manual has information on file formats such as DSCR..

NOTE: iVar1 always = 1 (index at first column). However, iVal1 always starts at 0 (same as ADS data).

DAC Optimization: setup and results

GOAL

Goal
OptimGoal1
Expr="my_dbs11"
SimInstanceName="SP1"
Min=
Max=-23
Weights=
RangeVar[1]=
RangeMin[1]=
RangeMax[1]=

MeasEqn
meas1
my_dbs11= db(S(1,1))

NOMINAL OPTIMIZATION

Optim
Optim1
OptimType=Discrete
ErrorForm=L2
MaxIters=
P=2
DesiredError=0.0
StatusLevel=4
SetBestValues=yes
Seed=
SaveSols=no
SaveOptmVars=no
SaveGoals=no
GoalName[1]=

res_std.dscr - Notepad

```

BEGIN DSCRDATA
% INDEX r_val
1 56
2 68
3 82
4 100
END DSCRDATA
        
```

Save values = no. Only the MeasEqn is sent to the dataset with the final iVal1 which is 0 = 56 ohms which gives the least reflection. Also, click Simulate > Update Optimization Values to update the iVal in the DAC.


freq	my_dbs11	iVal1
1.000GHz	-24.943	0.000

DataAccessComponent
 DAC1
 File="res_std.dscr"
 Type=Discrete
 Block=
 InterpMode=Index Lookup
 InterpDom=Rectangular
 IVar1=1
 iVal1=0.000000e+000 opt{ discrete 0 to 3 by 1 }

EXTRA NOTE: TDR Setup

REFERENCE SLIDE ONLY

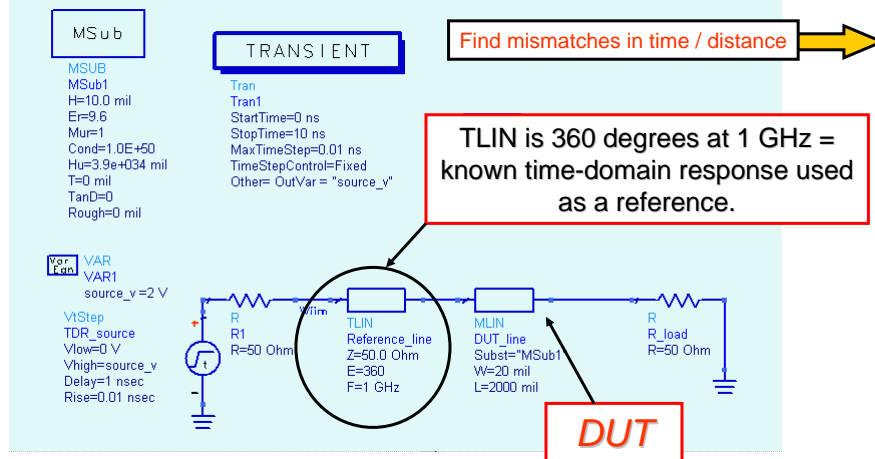After the class, you can use this slide as a reference if you need it!



EXTRA NOTE: TDR Data Displa

REFERENCE SLIDE ONLY

Eqn Er = 9.6
 Eqn Velocity = 3e8 / sqrt(Er)
 Eqn distance_mtrs = (indep(m2) - indep(m1)) / 2
 Eqn distance_mils = distance_mtrs * (1e5/2.54)

Eqn bw = 0.35/0.1e-9



bw	3.500E9
----	---------

Eqn z_line = Zo * ((1 + rho) / (1 - rho))
 Eqn Zo = 50
 Eqn rho = (m3 - ref_v) / (ref_v)
 Eqn ref_v = source_v [1] / 2

rho	z_line	ref_v
-0.192	83.916	1.000

After the class, you can use this slide as a reference if you need it!

distance_mtrs	distance_mils
0.006	29.11214

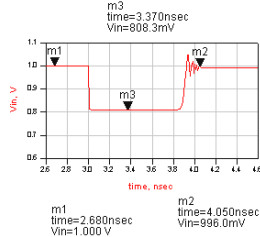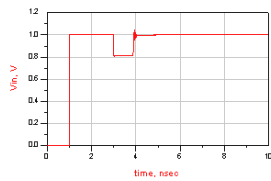

Results:
 mismatch
 delay time
 rho
 BW
 VSWR
 mtrs to mils


Eqn VSWR = (1 + mag(rho)) / (1 - mag(rho))

VSWR	1.474
------	-------

EXTRA NOTE on LineCalc and Model Composer


After the class, you can use this slide as a reference if you need it!

REFERENCE SLIDE ONLY

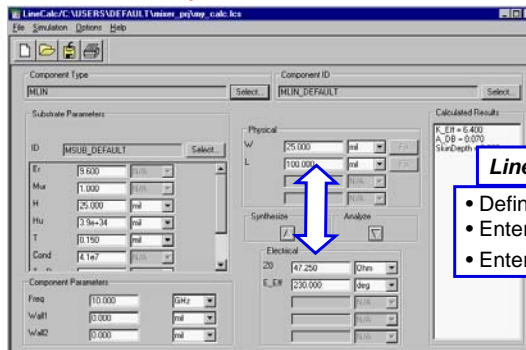

LineCalc is still available!

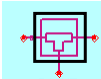- Define the substrate
- Enter L & W to get electrical
- Enter electrical to get L & W




ALSO - New add-on for ADS 1.5: MODEL COMPOSER. Generate your own passive library models (parameterized) for simulation. You get circuit simulation speed with EM simulation accuracy (Momentum) for microstrip components - more types in the future!



What the lab is about ...

Lab 6:

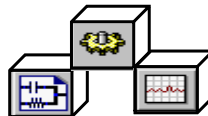Filters: E-Syn, Momentum,
Transient Simulation
and the *DAC*




Steps in the Design Process


You are here:



- Design the *rf_sys* behavioral model receiver
- Test conversion, budget gain, spectrum, etc.
- Start *amp_1900* design – subckt parasitics
- Simulate amp DC conditions & bias network
- Simulate amp AC response - verify gain
- Test amp noise contributions – tune parameters
- Simulate amp S-parameter response
- Define amp matching topology and tune input
- Optimize the amp in & out matching networks
- **Filter design – lumped 200MHz LPF - use E-Syn**
- **Filter design – microstrip 1900 MHz BPF**
- **Transient and Momentum filter analysis**
- Amp spectrum, delivered power, *Zin* - HB
- Test amp comp, distortion, two-tone, TOI
- CE basics for spectrum and baseband
- CE for *amp_1900* with GSM source
- Replace amp and filters in *rf_sys* receiver
- Test conversion gain, NF, swept LO power
- Final CDMA system test CE with fancy DDS
- Co-simulation of behavioral system

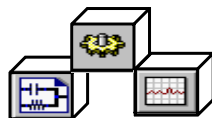

E-Syn - 200 MHz LPF design

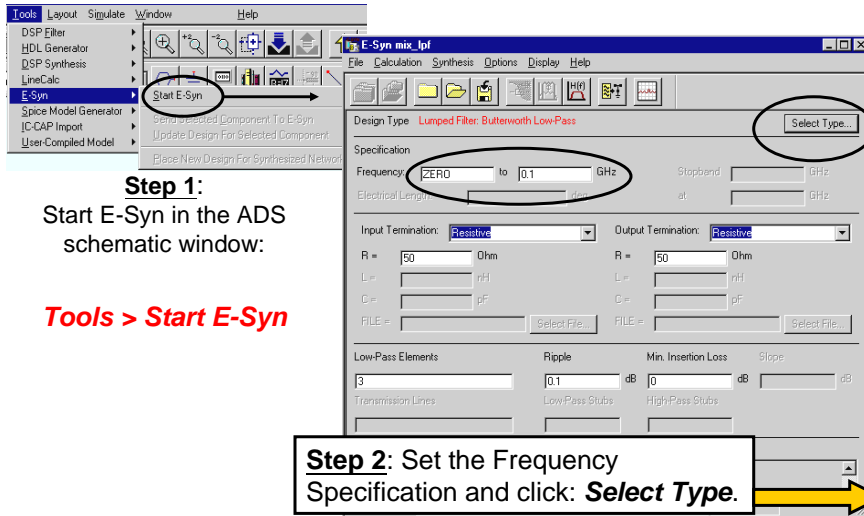


Step 1:
Start E-Syn in the ADS schematic window:

Tools > Start E-Syn

Step 2: Set the Frequency Specification and click: **Select Type.**


E-Syn - 200 MHz LPF (continued)

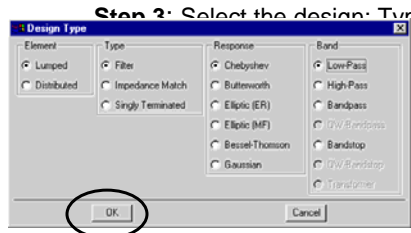Step 3: Select the design: Type, Response, and Band.




At first, window will be blank. Therefore, click the **Synthesize** button to calculate topology & component values as shown here.

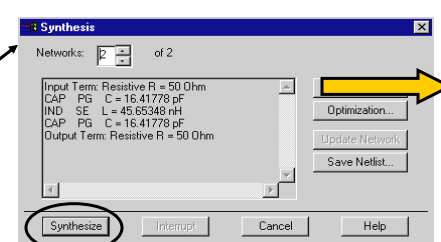Step 4: Go back to E-Syn main menu and click the **Synthesis** icon:





E-Syn - 200 MHz LPF (continued)

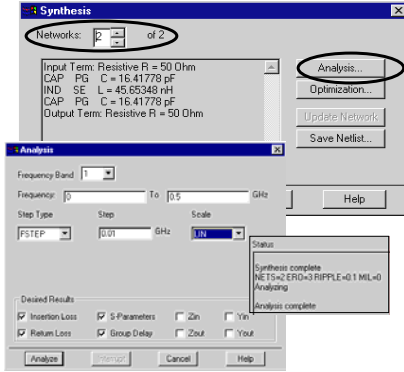

Step 5: Select the Network you want to use and then click **Analysis**.


Step 6: Set up the simulation and **Analyze**. The results will appear in the ADS Data Display window.

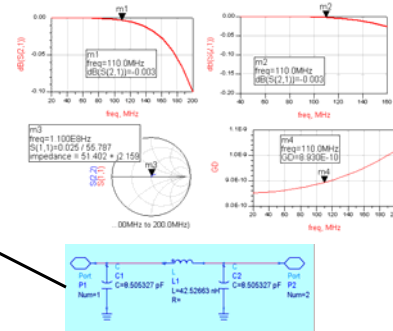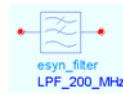Result of design (Butterworth) to be used in Final simulation.



Transient simulation of 1900 MHz BPF

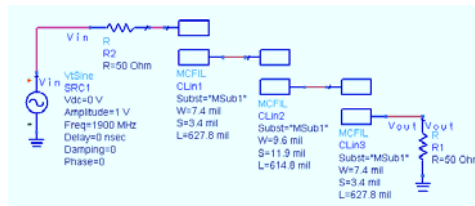Microstrip coupled line filter with substrate and VtSine source.




MSUB

MSUB
MSUB1
H=10.0 mil
Er=9.6
Mur=1
Cond=1.0E+50
Hus=3.9e+034 mil
T=0 mil
TanD=0
Rough=0 mil

TRANSIENT


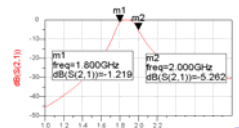
Tran
Tran1
StopTime=15/(1900e6)
MaxTimeStep=1/(2*15*1900e6)



$Eqn\ marker_val = indep(m2) - indep(m1)$
 $Eqn\ marker_freq = 1 / marker_val$

Also calculate delay:

marker_val
6.772E-11

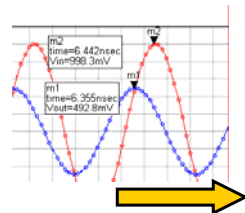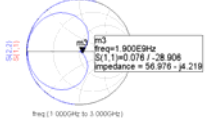

Generate the Layout of 1900 MHz BPF

Remove controllers and Terms - insert Port connectors

Layout Simulate Window Design
Generate/Update Layout...
Place Components From Schem To Layout

Use MOM menus

MOM: substrate, mesh, simulation

Substrate Layers Metalization Layers

Name: DA_CLFilter1_filter_mom_lay

Select a substrate layer to edit OR define a new layer:

Substrate Layers: FreeSpace, Alumina, GND

Thickness: 10 mil

Substrate: Alumina

Permeab: Permeab

Re, Loss: Real

Permittivity (E): Re, Loss Tangent, Real: 9.6

Mesh Setup Controls: Mesh

Global Layer Primitive Primitive Send

Define here the mesh values for the entire circuit

Mesh Frequency: GHz

Number of Cells per Wavelength: 30

Arc Facet Angle (max 45 deg): 45 degrees

Simulation Control

Compare to circuit S21:

m1 freq=1.790GHz dB(filter_mom_S(2,1))=-4.398

m2 freq=1.790GHz dB(filter_ckt_S(2,1))=-1.939


MOM - calculate coupling effects

Use the same setup and add a rectangle:

Coupled Line Filter



...draw a trace in close proximity

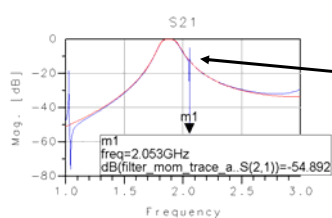

Momentum simulation shows resonance from coupling.

OPTIONAL - DAC exercise

Write the file

S-PARAMETERS

S_Param
SP1
Start=10 MHz
Stop=200 MHz
Step=10 MHz



DataAccessComponent

DAC1

File="Z_DAC.mdf"

Type=Generalized Multi-dimensional Data

InterpMode=Linear

InterpDom=Rectangular

iVar1="my_freq"

iVal1=freq


Z1P_Eqn

Z1P1

Z[1,1]=file{DAC1, "my_z"}

After setting S-parameter controller to calculate Z, results show results.
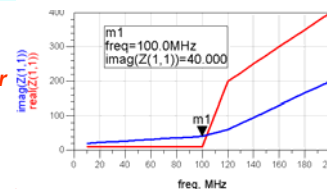
```
z_dac.mdf - Notepad
File Edit Search Help
BEGIN my_DATA
% my_freq(real) my_z(complex)
10e6 10 20
10e7 10 40
12e7 200 60
20e7 400 200
END
```




Start the lab now!





Topic 7:

Harmonic Balance


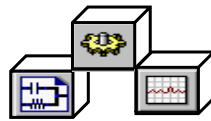


Harmonic Balance Simulation

Analyze circuits with Linear and Non-linear components:

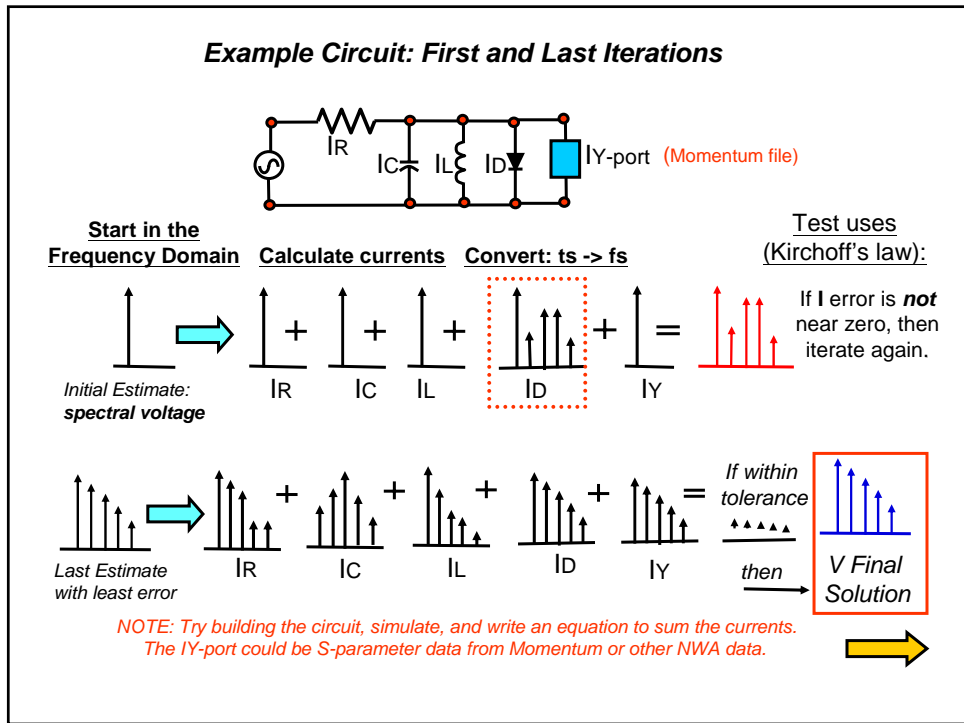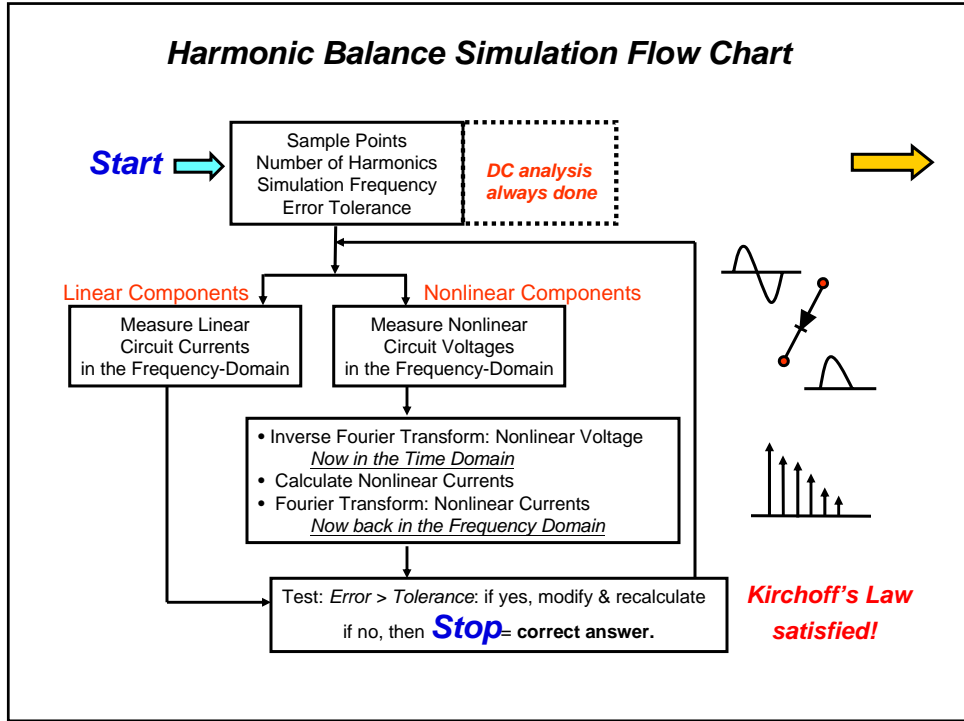- You define the tones, harmonics, and power levels
- You get the spectrum: Amplitude vs. Frequency
- Data can be transformed to time domain (ts function)
- Solutions use Newton-Raphson technique
- Krylov subspace method also available (large circuits)
- Use only Frequency domain sources
- Similar to Spectrum Analyzer





Basic 1 Tone HB simulation setup

Basic HB controller and source setup gives you spectral tones:

HARMONIC BALANCE

HarmonicBalance
HB1
Freq[1]=1900 MHz
Order[1]=3

Freq[1] is the fundamental tone you want HB to calculate. Freq[1] must match a tone in the circuit or you get a warning message.

Order [1] = 3 means HB calculates 3 harmonics of Freq [1]

HB gives you a Mix table:

freq	Vout	Mix
0.0000 Hz	0.000 / 0.000	0
1.900GHz	0.180 / -14.199	1
3.800GHz	0.001 / -170.939	2
5.700GHz	1.963E-5 / 46.135	3

Numerous built-in sources and measurement equations.

Swept variables in Harmonic Balance

HB Freq tab: specify tones (Freq), harmonics (Order), and mixing products (Max Order).

- 1) Initialize the VAR to sweep.
- 2) Specify the variable and range.

HARMONIC BALANCE

HarmonicBalance
HB1
Freq[1]=1900 MHz
Order[1]=3
SweepVar="RF_pwr"
Start=-50
Stop=-20
Step=1
Other=

VAR
VAR2
RF_pwr=-40

Fundamental Frequencies

Max Harmonic Order: 3

Frequency: 1900 MHz Order: 3

Parameter to sweep: RF_pwr

Parameter sweep

Sweep Type: Linear

Start/Stop: Start=-50 Stop=-20

Step-size: 1

Num. of pts.: 31

3) Be sure the VAR, the source, and simulation controller all have the same information.

NOTE: Swept variables always go to the dataset.

Other settings (tabs) in Harmonic Balance

Params

NOTE: Oversample: Set status level to 4, see number of samples for non-linear. Then set oversample for convergence or more accuracy.

ADS 1.5: Save (final solution) and re-use (initial guess). HB binary data file.

Noise (1 and 2) or use Noise Controller

Osc Use with Oscport

Nonlinear noise Oscillator

Nonlinear noise Oscillator

Related harmonic balance controllers ...

Transform HB spectrum into the time domain with ts function: $ts(V_{out})$.

Calculated S-params for harmonics.

XDB simulation results: 1 dB compression


input_pwr	LSSP1...S(2,1)
1.000	-3.005 + j3.258
2.000	-3.003 + j3.243
3.000	-3.000 + j3.230
4.000	-2.999 + j3.220
5.000	-2.999 + j3.213
6.000	-2.999 + j3.208
7.000	-2.999 + j3.205
8.000	-2.999 + j3.203
9.000	-2.999 + j3.202
10.000	-2.989 + j3.199

inpwr[1]	outpwr[1]
-31.251	-21.268

You will use HB and XDB in the lab!


Types of Power Sources for HB

Default power function for these sources is **polar**,
 but you can simplify it on the screen as: `dbmtow(0)`
 Therefore, `dbmtow(0)` is the same as `polar(dbmtow(0),0)`




P_1Tone
 PORT1
 Num=1
 Z=50 Ohm
 P=`polar(dbmtow(0),0)`
 Freq=1 GHz

Notice that these sources are also **ports** (OK for S-param analysis).
 Also, they can be considered **noiseless** like sources in a measurement system.



P_nTone
 PORT2
 Num=2
 Z=50 Ohm
 Freq[1]=1 GHz
 P[1]=`polar(dbmtow(0),0)`



P_nHarm
 PORT3
 Num=3
 Z=50 Ohm
 Freq=1 GHz
 P[1]=`polar(dbmtow(0),0)`


P_nTone and P_nHarm can have multiple Freqs and Power.

Example: HB simulation setup for mixer with swept LO power

Mixer example:

Freq [1] fundamental tone (most power: LO for mixer)
Freq [2] fundamental tone (RF for mixer)
Order [1] number of harmonics for Freq [1]: LO.
Order [2] number of harmonics for Freq [2]: RF.
MaxOrder = mixing products, depends on Order[n].
 NOTE: Here if MaxOrder = 9, you won't get 9th order product because Order[1] and [2] only go up to the 8th order.

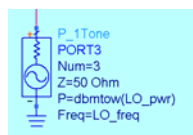Other settings: for status info, noise, and Krylov simulator (used in lab).



Do not do this: Freq = LO_freq MHz or MHz units will multiply.

To get any other VAR to the dataset (RF_pwr) requires using this syntax: OutVar = "variable name"

HARMONIC BALANCE

HarmonicBalance
 HB1
 MaxOrder=8
 Freq[1]=LO_freq
 Freq[2]=RF_freq
 Order[1]=5
 Order[2]=3
 StatusLevel=4
 NLNoiseMode=yes
 FreqForNoise=100 MHz
 UseKrylov=yes
 SweepVar="LO_pwr"
 Start=-30
 Stop=10
 Step=1
 Other=OutVar = "RF_pwr"

VAR
 mixer_vars
 LO_freq=1800 MHz
 RF_freq=1900 MHz
 LO_pwr=-40
 RF_pwr=-10

LO_pwr goes to the dataset automatically.



Example data: use mix function on Mix table

DC term=0. Freq, harmonics [order], and products [max order] are indexed:

Mixer example: Max order=8
LO order=5 RF order=3

freq	LO	Mix	RF
	Mix(1)	Mix(2)	Mix(2)
0.0000 Hz	0	0	0
100.0MHz	-1	1	1
200.0MHz	-2	2	2
300.0MHz	-3	3	3
1.500GHz	4	-3	-3
1.600GHz	3	-2	-2
1.700GHz	2	-1	-1
1.800GHz	1	0	0
1.900GHz	0	1	1
2.000GHz	-1	2	2
2.100GHz	-2	3	3
3.300GHz	5	-3	-3

LO: Freq[1]=1800 MHz RF: Freq[2]=1900 MHz

To get dBm of IF (100 MHz) at Vout, use the mix function:

```
MeasEqn
IF_100MHz_output
dbm_out=dBm(mix(Vout,{-1,1}))
```

Arguments in parentheses () and curly braces {generate the matrix }, required for Mix table.


8th order term uses +5th & -3th, but not -3th & +5th (+5th of RF does not exist).

QUIZ: Can you use this equation $\text{dBm}(\text{Vout}[1])$ for this data? Is it valid?

Answer: YES - if no other dependencies exist - it's the same as: $\text{dBm}(\text{mix}(\text{Vout},\{-1,1\}))$

Harmonic Balance convergence & errors

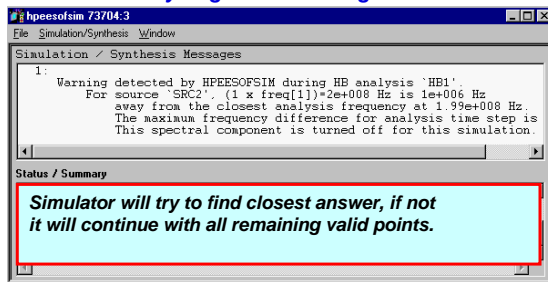Freq [x] in each source must match Freq [x] in the controller or you get this message:



HB convergence error message:


“cannot sweep to desired level”
or **“arc length continuation error”**

To solve these problems, either loosen the V and I tolerances in the options controller by ten times (for example, set: $_L_AbsTol= e-11$), or reduce the step size for power or frequency sweeps.

NOISE TEMP error for all noise simulations: Set Temp=16.85 to eliminate any error message.



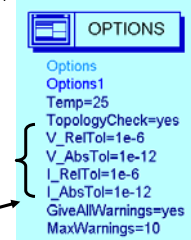
OPTIONS controller is in all simulation palettes.



TIP about “quotes”, brackets, braces, etc.

QUOTES:

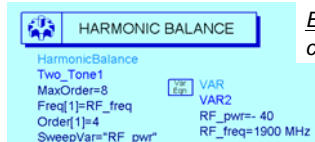- Only when editing on the screen for string value parameters, if necessary.
- When in doubt, double click and use the dialog boxes.



Exceptions - Swept variables are always in quotes and controller names (“HB1”) in opt goals.

In dialog only: @ stops quotes when not needed.



If you see 2 quotes “X”, remove one set!

Parentheses, Brackets, Curly braces:

- (parentheses for function arguments)
- [brackets for one, two, or three dimensional data]:
- {curly braces for vectors and the mix function}:

Double colon is a wildcard in ADS:




Examples: dBm(Vout [1]) dBm(mix(Vout,{-1,1})) mag(Vout [1:: 6])




What the lab is about ...

Lab 7:

Harmonic Balance Simulations

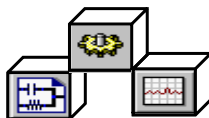


Steps in the Design Process

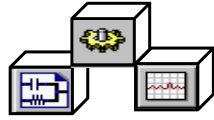

You are here:


- Design the rf_sys behavioral model receiver
- Test conversion, budget gain, spectrum, etc.
- Start amp_1900 design – subckt parasitics
- Simulate amp DC conditions & bias network
- Simulate amp AC response - verify gain
- Test amp noise contributions – tune parameters
- Simulate amp S-parameter response
- Define amp matching topology and tune input
- Optimize the amp in & out matching networks
- Filter design – lumped 200MHz LPF - use E-Syn
- Filter design – microstrip 1900 MHz BPF
- Transient and Momentum filter analysis
- Amp spectrum, delivered power, Zin - HB
- Test amp comp, distortion, two-tone, TOI
- CE basics for spectrum and baseband
- CE for amp_1900 with GSM source
- Replace amp and filters in rf_sys receiver
- Test conversion gain, NF, swept LO power
- **Final CDMA system test CE with fancy DDS**
- **Co-simulation of behavioral system**

First, HB for spectrum and Meas Eqn

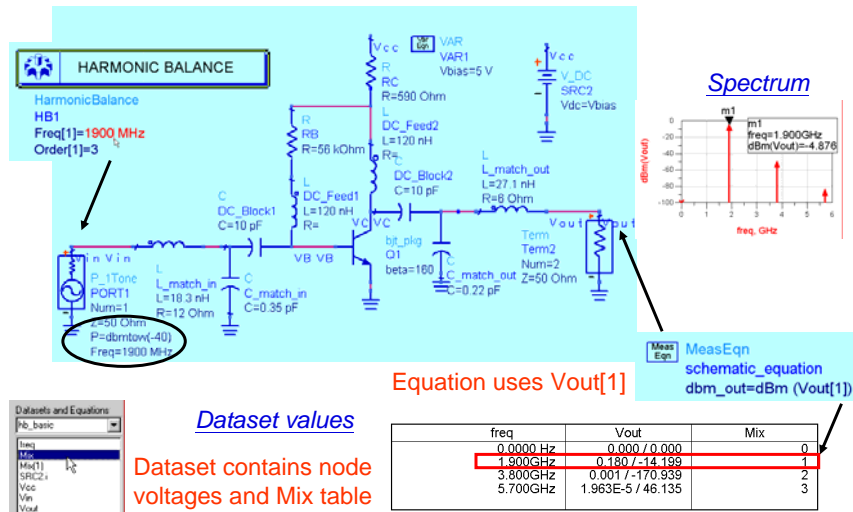


Next, simulate Power Delivered and Zin

Probe Components palette

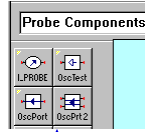

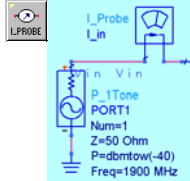NOTE for Oscillator testing: Use OscTest to determine if oscillation exists (S-param). Use OscPort to determine the frequency of oscillation (HB). See examples!



Rename the probe: I_in

Data display equations calculate power using voltage Vin and current I_in.

$$\text{Eqn } P_del_dBm = 10 * \log (0.5 * \text{real} (Vin[1] * \text{conj}(I_in.i[1]))) + 30$$

NOTE: 0.5 is for 1/2 peak value and +30 give dBm (ref to 0.001 W)

Z_in is calculated at 1900 MHz which is index value [1]. Also, Z_in is used in dBm argument instead of default of 50.


$$\text{Eqn } Z_in = Vin[1] / I_in.i[1]$$

Z_in	47.819 / 0.688
------	----------------


dBm(Vin[1],Z_in)	dBm(Vin[1])	P_del_dBm
-40.003	-40.214	-40.003

HB Phase, ts, and Gain Compression

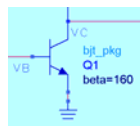Use ts function on HB data at device nodes



Verify inversion of signal:

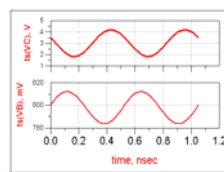

2 ways to simulate gain compression XDB and HB with swept power:

GAIN COMPRESSION

XDB
HB2
Freq[1]=1900 MHz
Order[1]=3
GC_XdB=1
GC_InputPort=1
GC_OutputPort=2
GC_InputFreq=1900 MHz
GC_OutputFreq=1900 MHz

Gain Compression at 1900 MHz

inpwr[1]	outpwr[1]
-30.159	3.189

HARMONIC BALANCE


HarmonicBalance
HB1
Freq[1]=1900 MHz
Order[1]=3
SweepVar="RF_pwr"
Start=-50
Stop=-20
Step=1




HB swept power compression data

Eqn dB_gain = hb_comp.dbm_out - hb_comp.RF_pwr

Plot_vs function

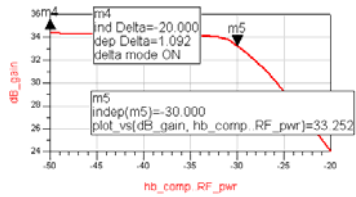


Plot_vs(dB_gain, hb_comp.dbm_out)

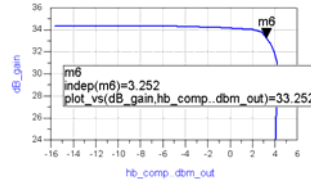


Creating a line: nonlinear to linear

Eqn line = hb_comp.RF_pwr + dB_gain [0]

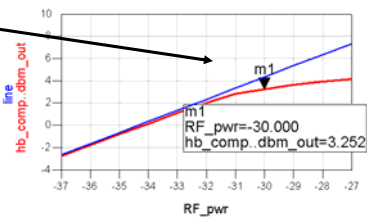


Simulating closely spaced tones...

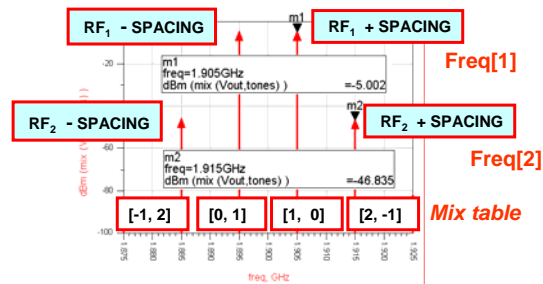
AMPS use 2 tones, such as RF +/- spacing (VAR)



Lab setup and data

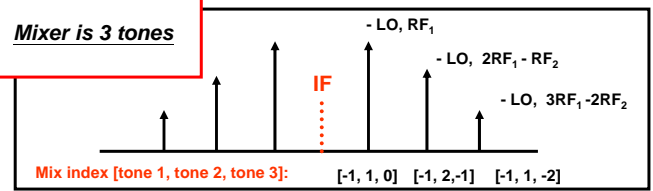


Two-tone HB simulation and data

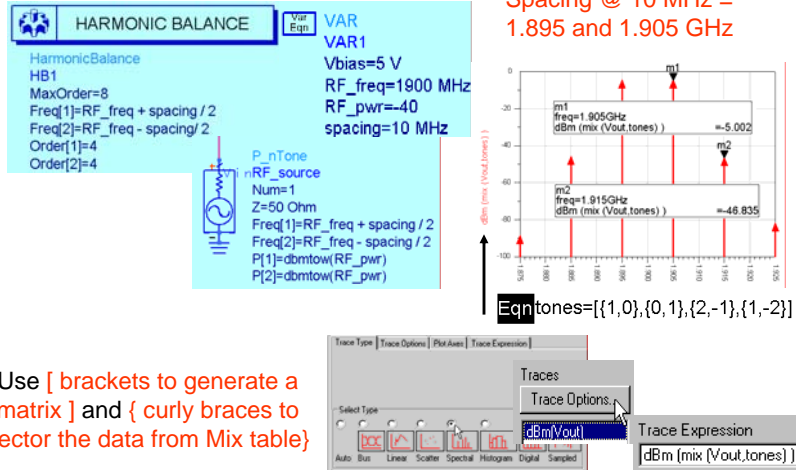

TOI or IP3 Measurement

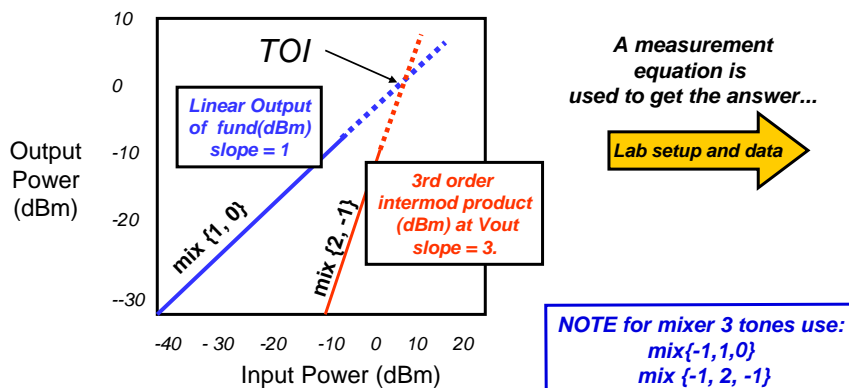When the input power drives the non-linear device into saturation or distortion, third order products near the desired frequency can become large. The point at which 3rd order products intercept the linear rise in output power is the intercept point TOI or IP3.



IP3 or TOI's

Built-in measurements use functions you set the arguments.

1.885GHz	-1	2
1.895GHz	0	1
1.905GHz	1	0
1.915GHz	2	-1

IP3out
upper_toi=ip3_out(Vout,{1,0},{2,-1},50)

IP3out
lower_toi=ip3_out(Vout,{0,1},{-1,2},50)

```

HarmonicBalance
HB1
MaxOrder=10
Freq[1]=LO_freq
Freq[2]=RF_freq + L_spacing / 2
Freq[3]=RF_freq - f_spacing / 2
Order[1]=7
Order[2]=3
Order[3]=3
          
```

NOTE: Mixers use this setup for 3 tone TOI.

HARMONIC BALANCE

```

Two_Tone
MaxOrder=8
Freq[1]=RF_freq + spacing / 2
Freq[2]=RF_freq - spacing / 2
Order[1]=4
Order[2]=4
SweepVar=
Start=
Stop=
Step=
          
```

Result of IP3 eqns in DDS:

lower_toi	upper_toi
15.679	15.914

Compare swept values to values in the TOI measurement range:

OPTIONAL: Sweep RF pwr vs TOI

HARMONIC BALANCE

```

HarmonicBalance
Two_Tone
MaxOrder=8
Freq[1]=RF_freq + spacing / 2
Freq[2]=RF_freq - spacing / 2
Order[1]=4
Order[2]=4
SweepVar='RF_pwr'
Start=-45
Stop=-30
Step=1
          
```

Swept values used for IP3

Eqn my_toi = ip3_out(Vout,{1,0},{2,-1},50)


The Eqn, **my_toi**, is on the right Y axis.
When RF_pwr is greater than 39dBm, RF and third order slopes are no longer 1:3, so IP3 Eqn becomes invalid.

Start the lab now!





Topic 8:

Circuit Envelope Simulation

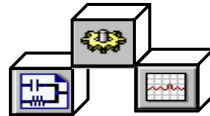

What is Circuit Envelope ?

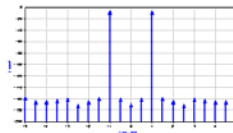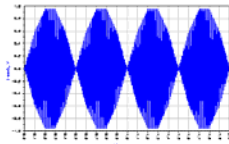- *Time samples the modulation envelope (not carrier)*
- ***Compute the spectrum at each time sample***
- ***Output a time-varying spectrum***
- ***Use equations on the data***
- ***Faster than HB or Spice in many cases***
- ***Integrates with System Simulation & HP Ptolemy***




Use realistic Signals with CE

GSM, CDMA, GMSK, pi/4DQPSK, QPSK, etc.

Simulations include:

- Adjacent Channel Power Ratio
- Noise Power Ratio
- Error Vector Magnitude
- Power Added Efficiency
- Bit Error Rate

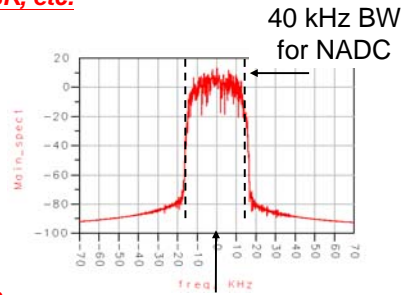
2-tone tests and linearized models do not predict this behavior as easily!



890 MHz carrier



Circuit Envelope Technology:

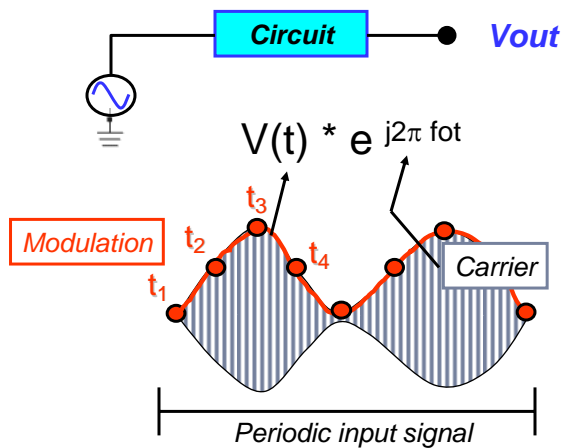

Time sample the envelope and then




performs Harmonic Balance on the samples!

NOTE: $V(t)$ can be complex - am or fm or pm


...more on CE Technology

Captures time and frequency impairments:

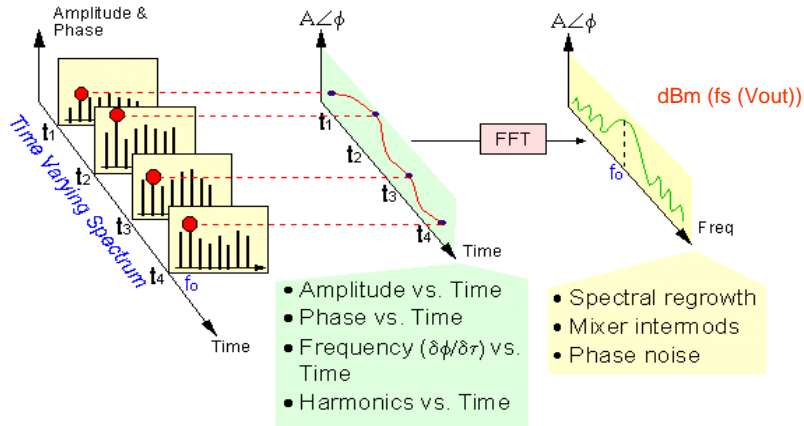

CE example: AMP with RF pulse


ONE TONE

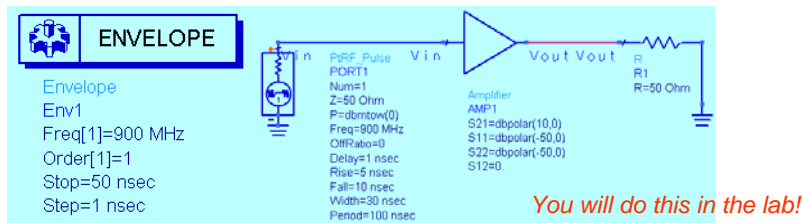

Step time is critical for sampling the envelope: rise, fall, and modulation rate. Therefore, Step (sample time) is NOT the same as Transient.

- mag of Vin [1]: envelope
- ts of Vout: signal
- mag of Vout [1]: envelope

...where [1] is the carrier Freq[1].

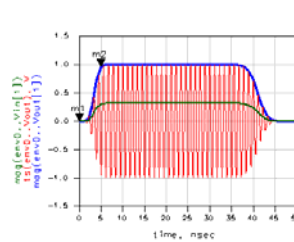

Env Setup tab in dialog



(Reference slide for one tone with 3 harmonics)

Stop time

- Determines resolution bandwidth of output spectrum
- Large enough to resolve spectral components of interest

Time step

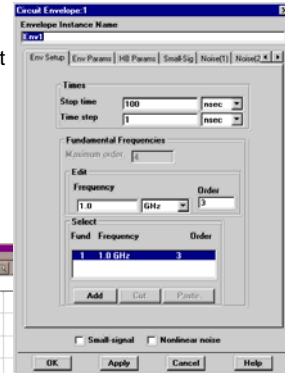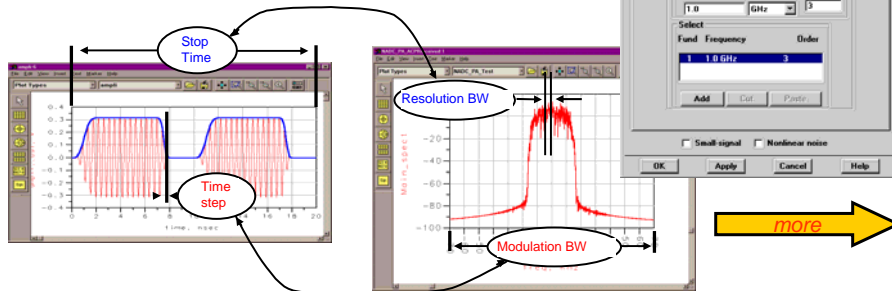
- Determines bandwidth of Circuit Envelope simulation
- Small enough to capture highest modulation frequency




ENV Steup tab (continued)

(Reference slide for multiple tones: mixer)

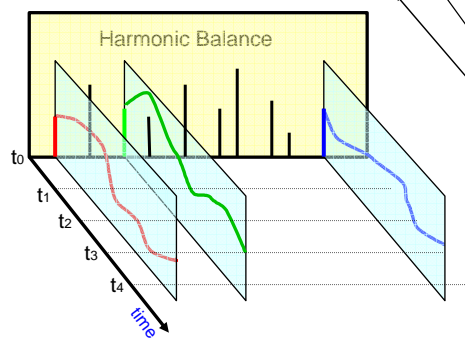7 Harmonics of Fundamental: Freq [1]
3 Harmonics of Fundamental: Freq [2]



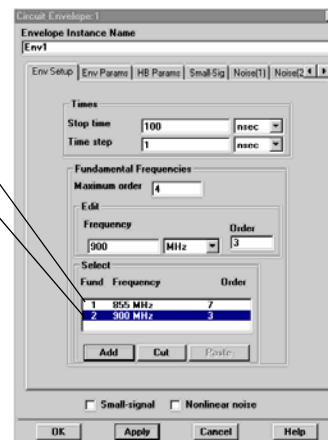Multiple tone simulation requires more data display







What the lab is about ...

Lab 8:

Circuit Envelope Simulations

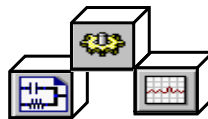

Steps in the Design Process


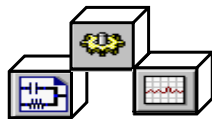


You are here:



- Design the *rf_sys* behavioral model receiver
- Test conversion, budget gain, spectrum, etc.
- Start *amp_1900* design – subckt parasitics
- Simulate amp DC conditions & bias network
- Simulate amp AC response - verify gain
- Test amp noise contributions – tune parameters
- Simulate amp S-parameter response
- Define amp matching topology and tune input
- Optimize the amp in & out matching networks
- Filter design – lumped 200MHz LPF - use E-Syn
- Filter design – microstrip 1900 MHz BPF
- Transient and Momentum filter analysis
- Amp spectrum, delivered power, Z_{in} - HB
- Test amp comp, distortion, two-tone, TOI
- **CE basics for spectrum and baseband**
- **CE for amp_1900 with GSM source**
- Replace amp and filters in *rf_sys* receiver
- Test conversion gain, NF, swept LO power
- Final CDMA system test CE with fancy DDS
- Co-simulation of behavioral system

First, simulate an RF pulse

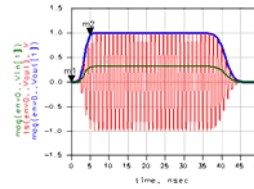
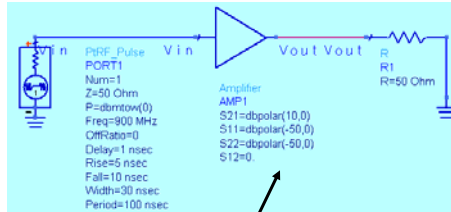
Use a behavioral amp and different time steps:



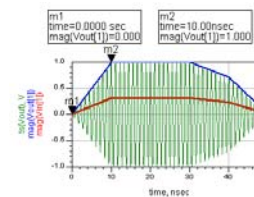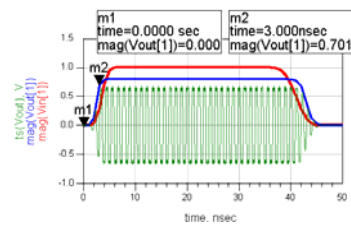Add distortion: get odd harmonics out-of-phase!




Next, phase distortion bits (baseband)

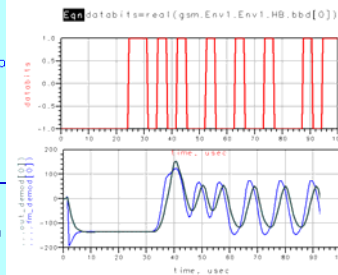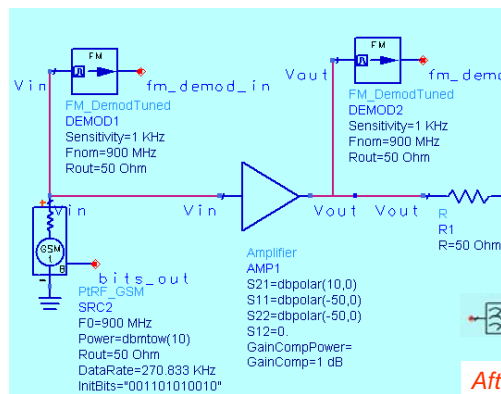

Look at the bit stream: **bits_out** node and **Vout**.

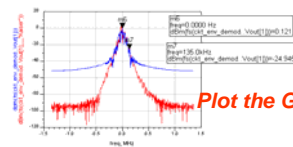
After simulating the response of the amplifier, insert a filter at **Vin** to alter the phase response.



Plot the GSM BW spectrum with windowing.



GSM source on your amp_1900

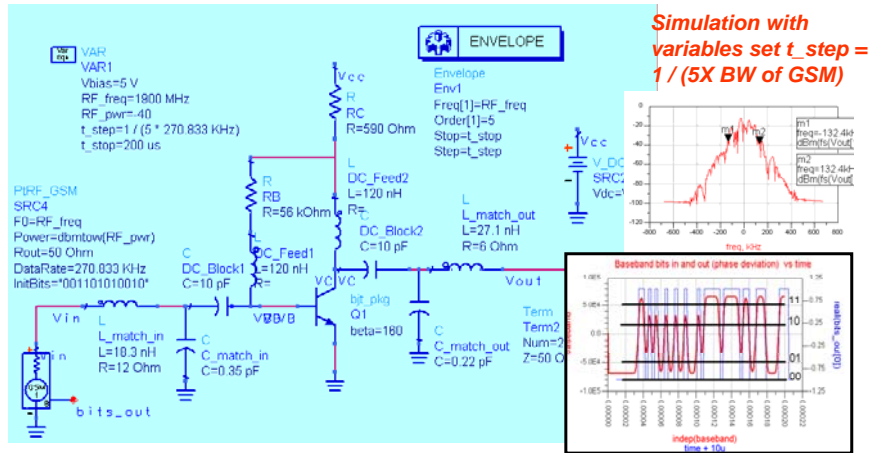


$$\text{Eqn baseband} = \text{diff}(\text{unwrap}(\text{phase}(\text{Vout}[1]))) / 360$$

Optional - channel power calculation

On a new page in DDS, write two equations:
limits defines the bandwidth and
channel_pwr calculates power in the channel.

$$\text{Eqn limits} = \{-(270\text{kHz} / 2), (270\text{kHz} / 2)\}$$


$$\text{Eqn channel_pwr} = 10 * \log(\text{channel_power_vr}(\text{Vout}[1], 50, \text{limits}, \text{"Kaiser"})) + 30$$

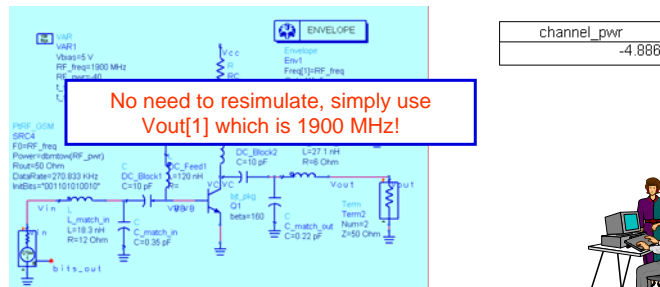




Topic 9:

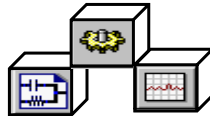Final Circuit / System Simulation and Co-Simulation



What is the final topic in this class?

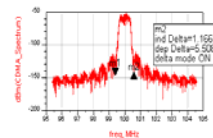
- Simulation of your amp_1900 and filters in the receiver system to verify analog performance.



Gain (S-21), HB with swept LO, and CE with a CDMA source

The co-simulation is optional if you have time - otherwise, take the CommSys class.

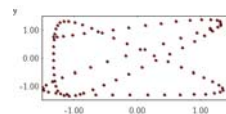- Co-simulation: simulation of the entire system using digital circuits and analog circuits together.



Constellation, spectrum, etc...


A little on co-simulation before starting the lab...



What is a co-simulation?

It is your amp_1900 and filters in the receiver system at the bottom level.
On the top level is a Data Flow simulation.

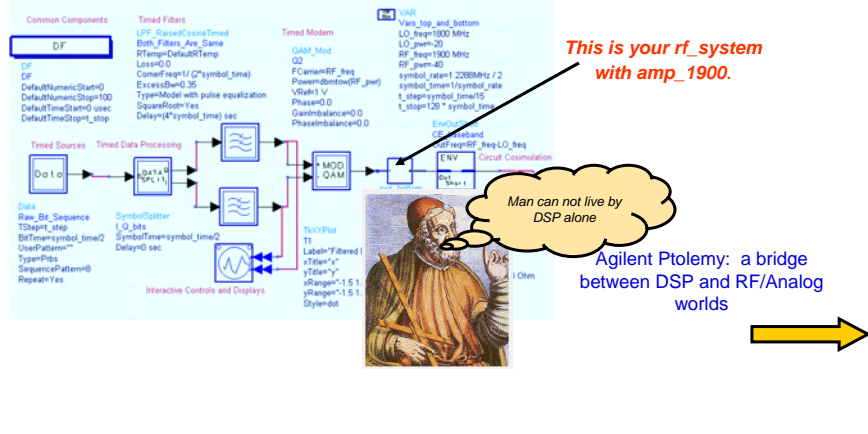Co-simulation is digital & RF/analog circuits simulating together.




What is Ptolemy ?

Agilent Ptolemy is a Timed Synchronous Data Flow Simulator

- TSDF is a unique Agilent EEs of Innovation
- Agilent Ptolemy adds timed elements
 - parameters on signals are t, I, Q, Fc (rf carrier)
- Benefits:
 - easy to add real RF effects on signals
 - more efficient simulations
 - more accurate modeling of RF effects

A key advantage for real world

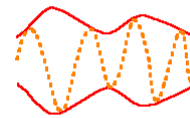


mixed signal design
(DSP / analog / RF)

Agilent Ptolemy is the data flow simulator used in the DSP schematic window...



What is Data Flow?

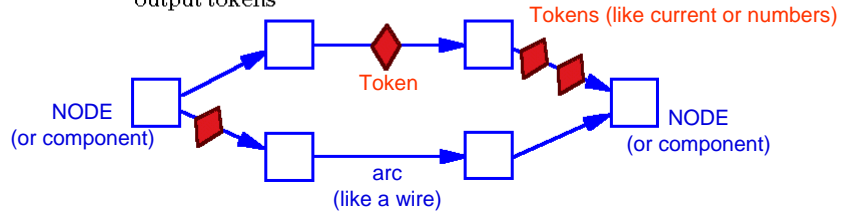- Dataflow is
 - Each arc has FIFOs
 - A node maps input tokens onto output tokens
 - A set of firing rules specify when a node runs
 - A firing consumes input tokens and produces output tokens




Tokens can also be "time stamped" - then they become samples.
 Now you can simulate time and frequency domain impairments
 such as multi-path and fading ...



What is Co-simulation?

- **Integrated Circuit, System Simulation & HP Ptolemy**

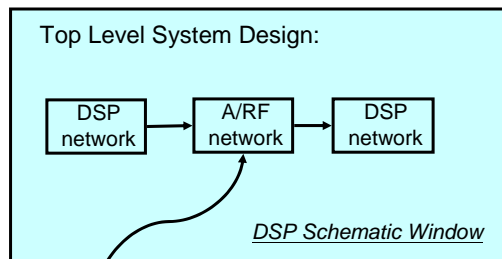Co-simulation is simulating an A/RF schematic design with a DSP schematic design.




The simulator in the A/RF design must use either **Transient** or **Circuit Envelope**

The A/RF schematic can be **any** kind of design: amplifier, mixer, PLL, etc...



The DSP components library...

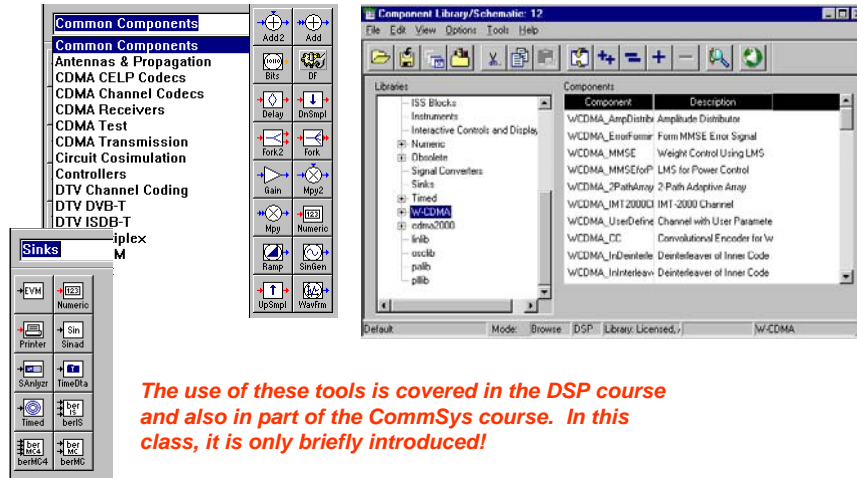Many palette selections and additional libraries:



The image displays the DSP components library interface. On the left, there are several palettes: 'Common Components' (listing Antennas & Propagation, CDMA Channel Codecs, CDMA Receivers, CDMA Test, CDMA Transmission, Circuit Cosimulation, Controllers, DTV Channel Coding, DTV DVB-T, DTV ISDB-T), 'Sinks' (listing EVM, Numeric, Printer, Sin, Sinad, SAnalyzer, TimeDta, Time, berTS, berM4, berM6), and a 'Mux' palette. In the center, there is a 'Component Library/Schematic: 12' window showing a list of components with columns for 'Component' and 'Description'. The list includes: WCDMA_AmpDistrib (Amplitude Distributor), WCDMA_ErrorForm (Form MMSE Error Signal), WCDMA_MMSE (Weight Control Using LMS), WCDMA_MMSELoP (LMS for Power Control), WCDMA_3PathArray (2-Path Adaptive Array), WCDMA_IMT2000 (IMT-2000 Channel), WCDMA_UserDefine (Channel with User Parameters), WCDMA_EC (Convolutional Encoder for WCDMA), WCDMA_InDeinterleav (Deinterleaver of Inner Code), and WCDMA_InInterleav (Deinterleaver of Inner Code).


The use of these tools is covered in the DSP course and also in part of the CommSys course. In this class, it is only briefly introduced!




What the lab is about ...

Lab 9:

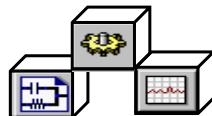Final System Simulation using:
amp_1900 and filters



Steps in the Design Process

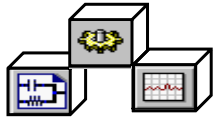


- Design the *rf_sys* behavioral model receiver
- Test conversion, budget gain, spectrum, etc.
- Start *amp_1900* design – subckt parasitics
- Simulate amp DC conditions & bias network
- Simulate amp AC response - verify gain
- Test amp noise contributions – tune parameters
- Simulate amp S-parameter response
- Define amp matching topology and tune input
- Optimize the amp in & out matching networks
- Filter design – lumped 200MHz LPF use E-Syn
- Filter design – microstrip 1900 MHz BPF
- Transient and Momentum filter analysis
- Amp spectrum, delivered power, Z_{in} - HB
- Test amp comp, distortion, two-tone, TOI
- CE basics for spectrum and baseband
- CE for *amp_1900* with GSM source
- Replace amp and filters in *rf_sys* receiver
- Test conversion gain, NF, swept LO power
- **Final CDMA system test CE with fancy DDS**
- **Co-simulation of behavioral system**

You are here:


First, system setup with S-params

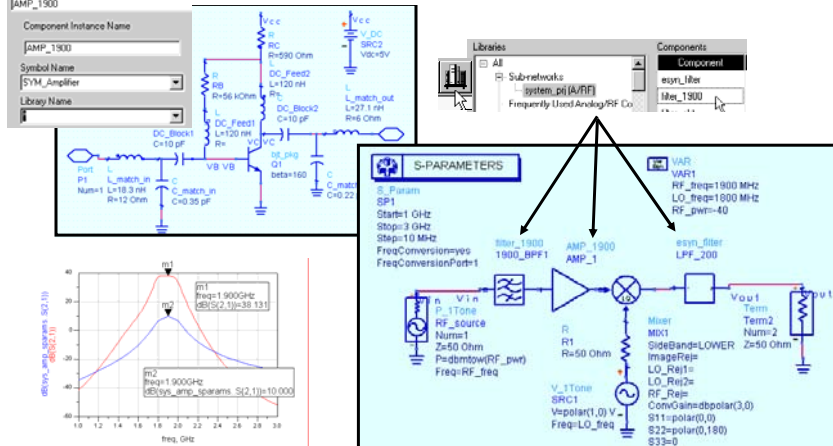Setup sub-circuit using: File > Design Parameters



First, simulate system S21 with frequency conversion to see gain!


Next, HB simulation with swept LO

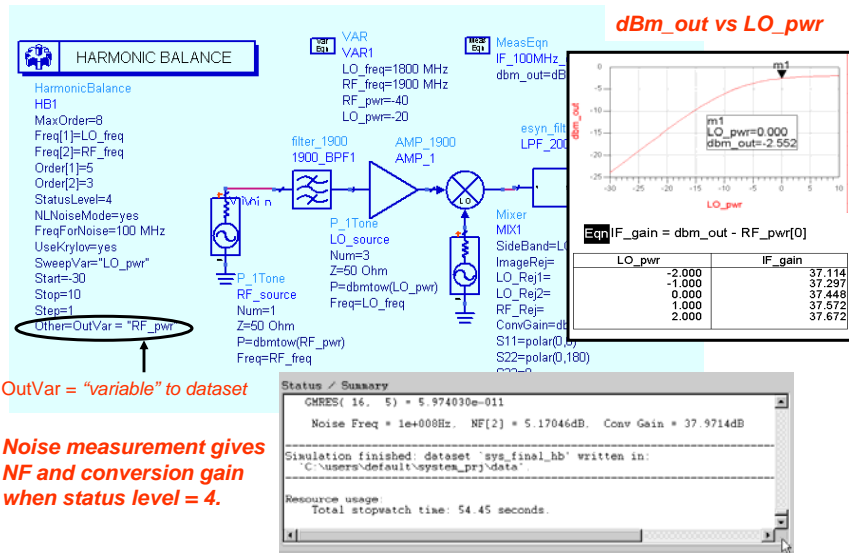

OutVar = "variable" to dataset

Noise measurement gives NF and conversion gain when status level = 4.

Final system CE simulation with CDMA

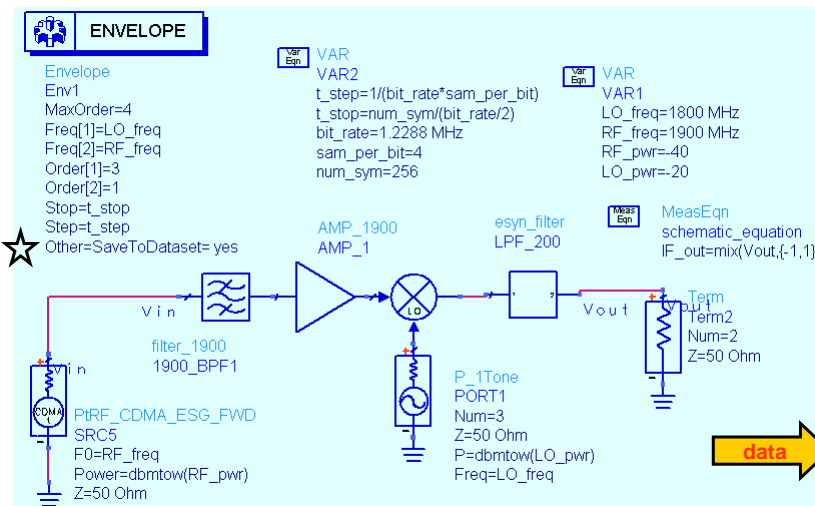


★ **NOTE: Other = SaveToDataset = no** It means only the MeasEqn IF_out goes to dataset.


Power calculations from an example DDS

Use your CE data:

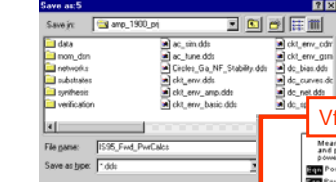1. Open the example DDS file from the Tutorials/ModSources /IS95_Fwd_PwrCalcs
2. Save it in your system .prj.
3. Change the dataset and MeasEqn



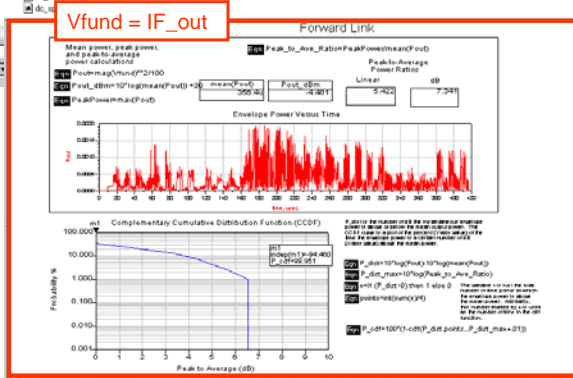
Simply change the eqn name to Vfund=IF_out and all the data fills in the plots and equations values!




Fancy Data Display for CDMA spectrum

Set up a marker slider using equations: m1 slides to a frequency and the spectrum of that carrier frequency is displayed: RF, LO, IF, etc.

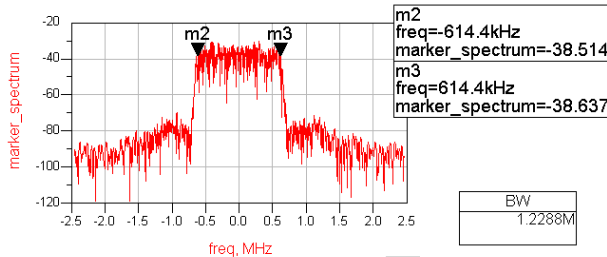Eqn marker_spectrum = dBm(fs(Vout[:,freq_index],,,,,"Kaiser"))



BW
1.2288M

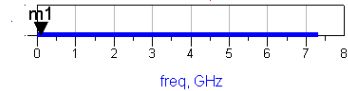

Eqn BW = indep (m3) - indep (m2)

m1 is at the IF

Eqn marker_freq = freq [0,:]

Eqn freq_index=find_index (marker_freq,m1)

m1
freq=100.0MHz
marker_freq=10.000E7


NOTE: If you finish this step in the lab, you have achieved all the goals for this class!

OPTIONAL - Co-simulation of *rf_sys*

This process requires several steps:

First step: Modify the system to become a sub-circuit (bottom CE simulation level) as shown here. Co-simulation requires a Transient or CE simulation setup.

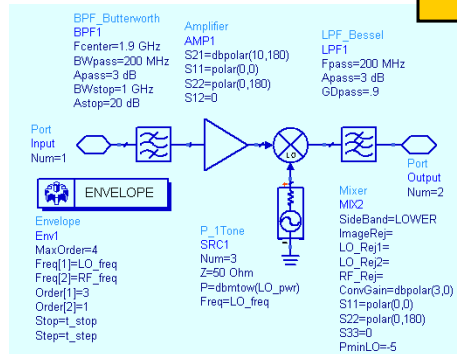
In this class, it is easier and faster to set up and run co-simulation using the behavioral system. The Extra exercise shows even more co-simulations you can try after the course!



Co-simulation continued...


Next step: Open a top level DSP network so that the Ptolemy / DSP palettes become available in schematic.

Then build the system shown here:

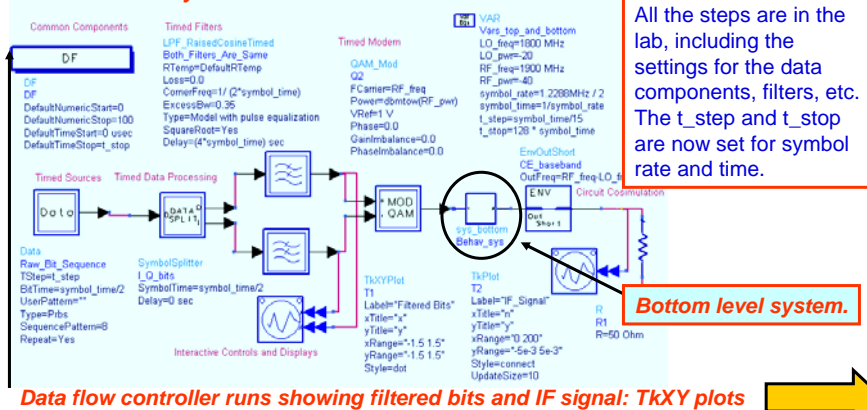

Data flow controller runs showing filtered bits and IF signal: TkXY plots


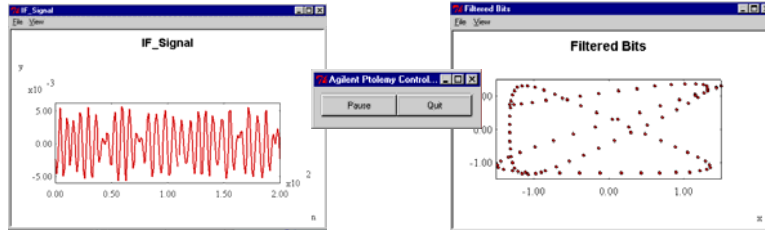
Data Flow simulation - TK plots are active!



Quit the DF simulation and connect a SpectrumAnalyzer sink to collect the data. Results of this co-simulation show spectrum of the behavioral system. To use amp_1900 and your filters, replace them in the system and setup a new simulation (requires more time).

Start the lab now!

Spectrum Analyzer sink:

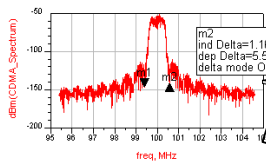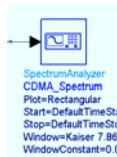

By the way...RF Board and RFIC Design Flow Integration Solutions from Agilent EEsof EDA

- Software and Services available to integrate ADS into existing design flow based on:
 - Schematic transfer via IFF
 - Layout transfer via IFF
 - Schematic sharing via Dynamic Link
- For more info, contact your Agilent EEsof Sales Representative, or visit:



RFIC Design Flow:

<http://www.tm.agilent.com/tmo/hpeesof/products/ads/prod600a.html>

ml

RF Board Design Flow:

<http://www.tm.agilent.com/tmo/hpeesof/products/ads/prod600b.html>

ml

End of the Course



Before you leave, please fill-out the course evaluation...thanks!

Look for us on the WWW for more ADS training and applications.

Goodbye and see you next time!
www.agilent.com
Agilent EEs of EDA - Customer Education