




Receiver architectures



Introduction




Example of a complete transceiver

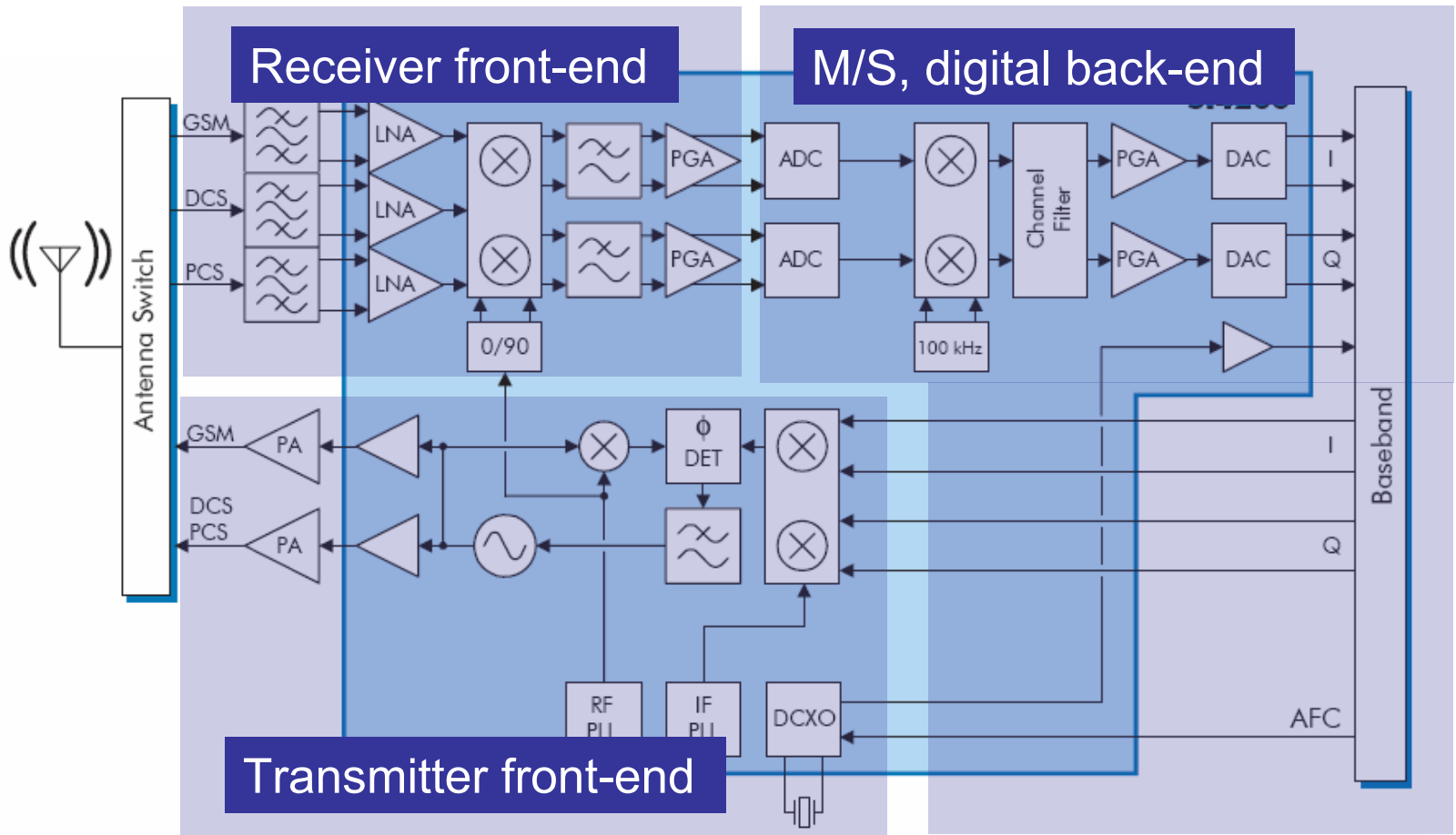

RX (Receiver) / TX (transmitter) building blocks


Low Noise Amplifier (LNA)

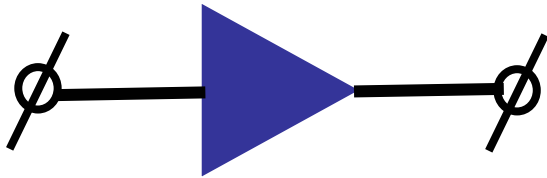


Filter




Mixer

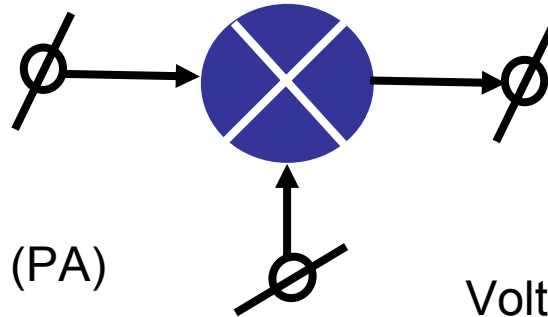


Variable gain amplifier (VGA)

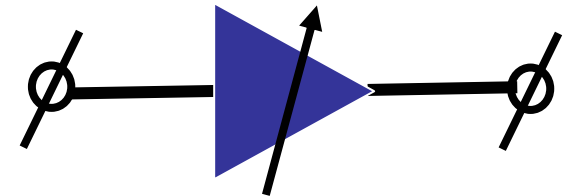

Power amplifier (PA)

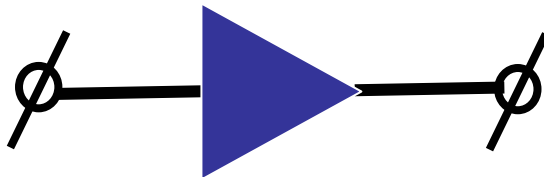


Voltage controlled oscillator (VCO)

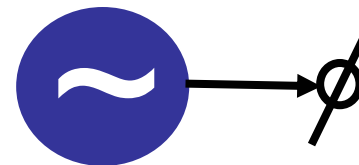

Not a complete list

RF transceiver design parameters

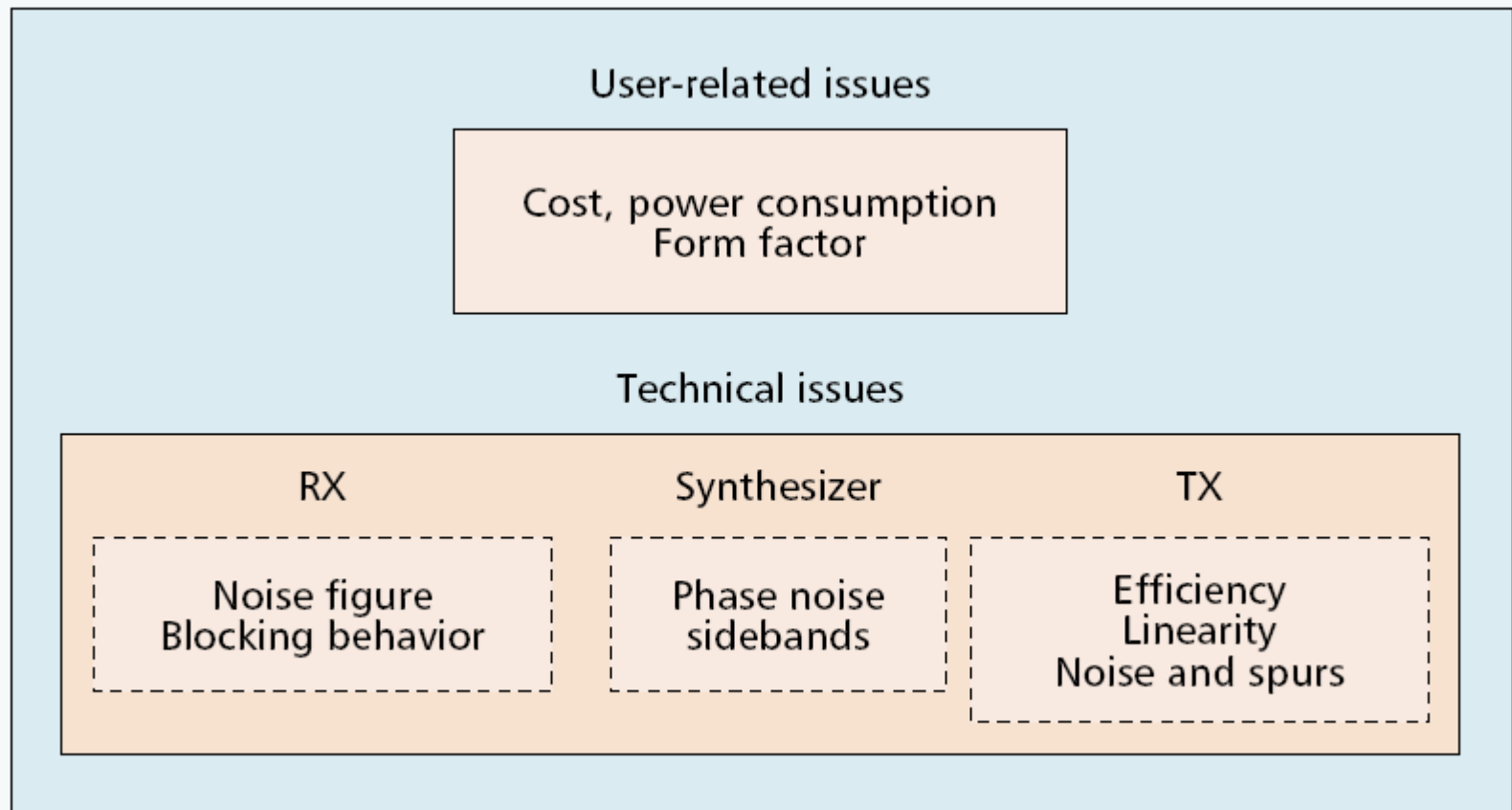


Basic function of a receiver front-end

What do we want of a receiver front-end:



Select and receive a small desired channel or signal among many interferers: we need **gain**, **selectivity** and **frequency-conversion** (for digital-processing at low frequencies).

Generic receiver architecture

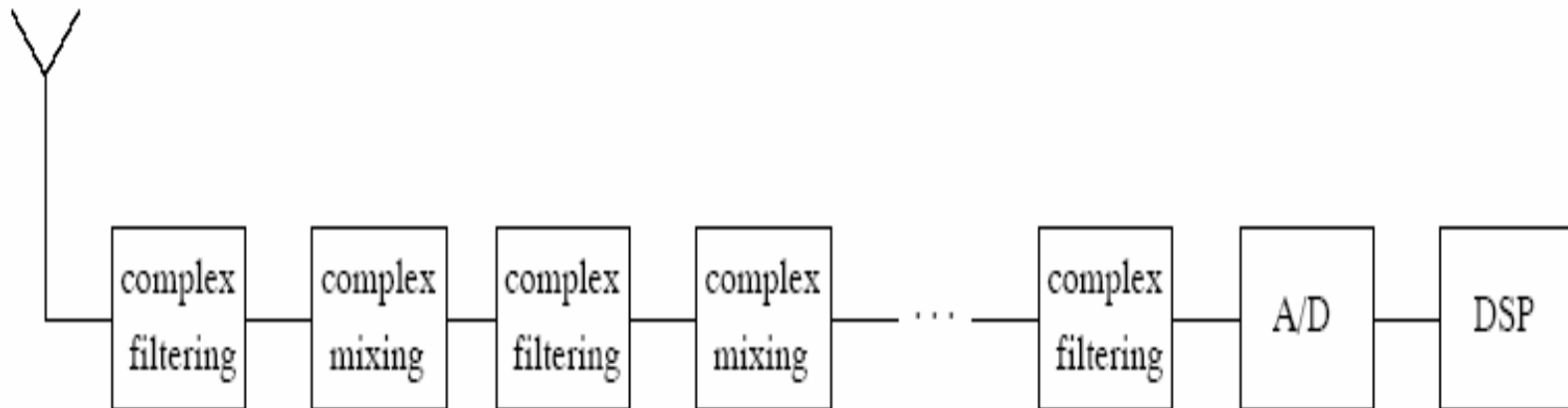



Practically the basis for every receiver architecture



General RX aspects

Quadrature signals: complete signal description
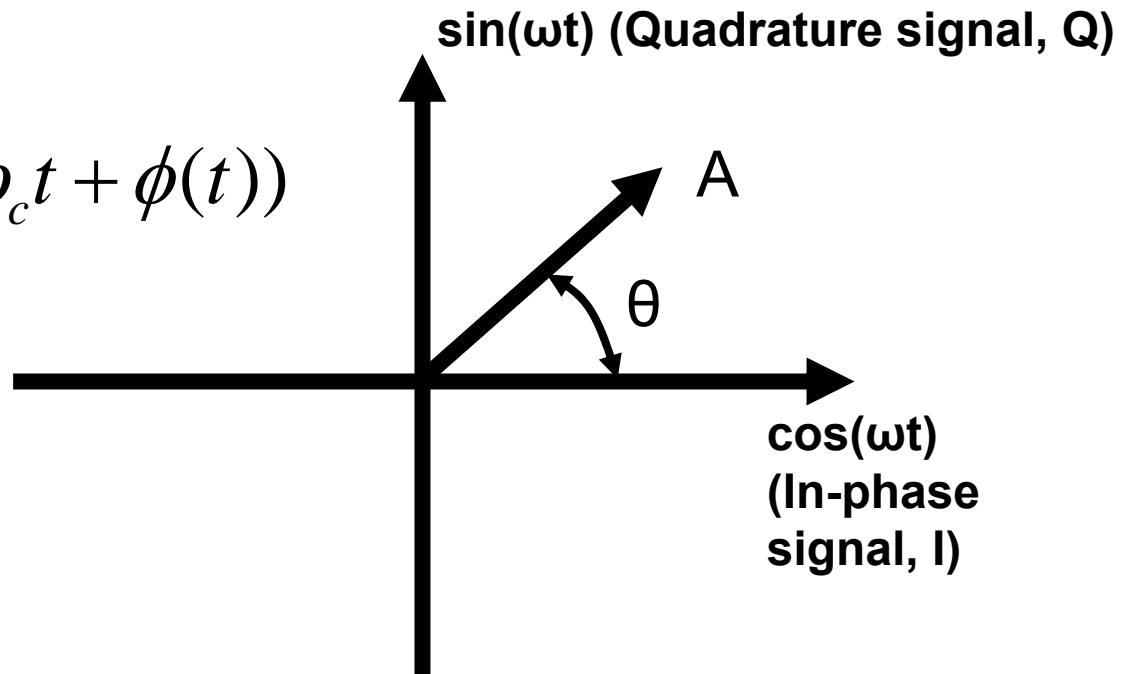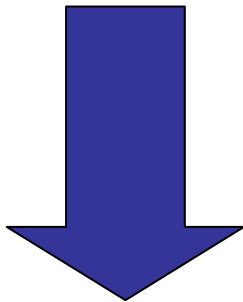
$$s(t) = A_c \cos(\omega_c t + \phi(t))$$



$$s(t) = A_c \cos(\phi(t)) \cos(\omega_c t) - A_c \sin(\phi(t)) \sin(\omega_c t)$$

Complex signal processing

“Cosine-channel”




“Sine-channel”

Quadrature signals needed for complete signal description

Frequency conversion: mixing frequencies

Radio frequency (RF) input

Intermediate frequency (IF) output

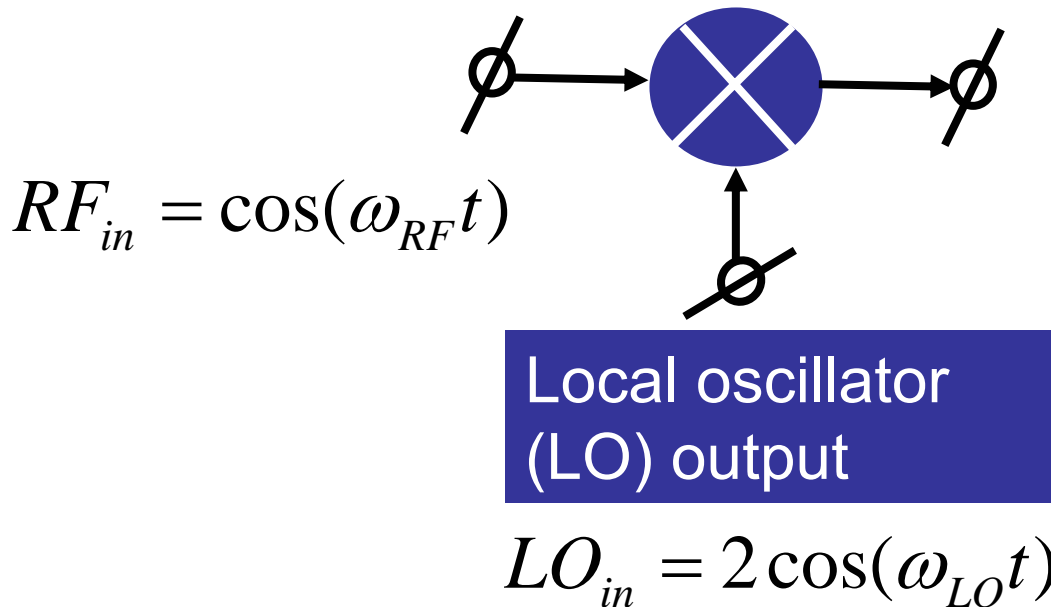

$$IF_{out} = \cos((\omega_{RF} - \omega_{LO})t) + \cancel{\cos((\omega_{RF} + \omega_{LO})t)}$$


Filter



RF Sampling

RF sampling (I)

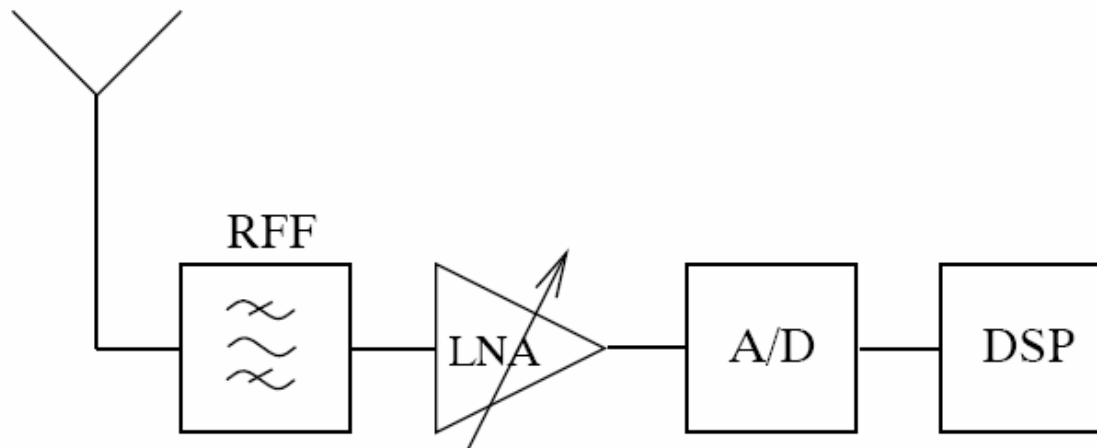Digitization almost directly at the antenna



Currently, still not feasible / cost-effective given normal constraints for power consumption and cost.



RF sampling (II)


- For example, for a Digital European Cordless Telephone (DECT) system, which is working at 1.9 GHz:
 - An A/D converter is needed with at least a sampling rate of the nyquist frequency (3.8 GHz) and 14 bits resolution.

When RF sampling becomes cost-effective it will be the most flexible “software-defined” receiver implementation




Super- heterodyne receiver

Super-heterodyne receiver (I)

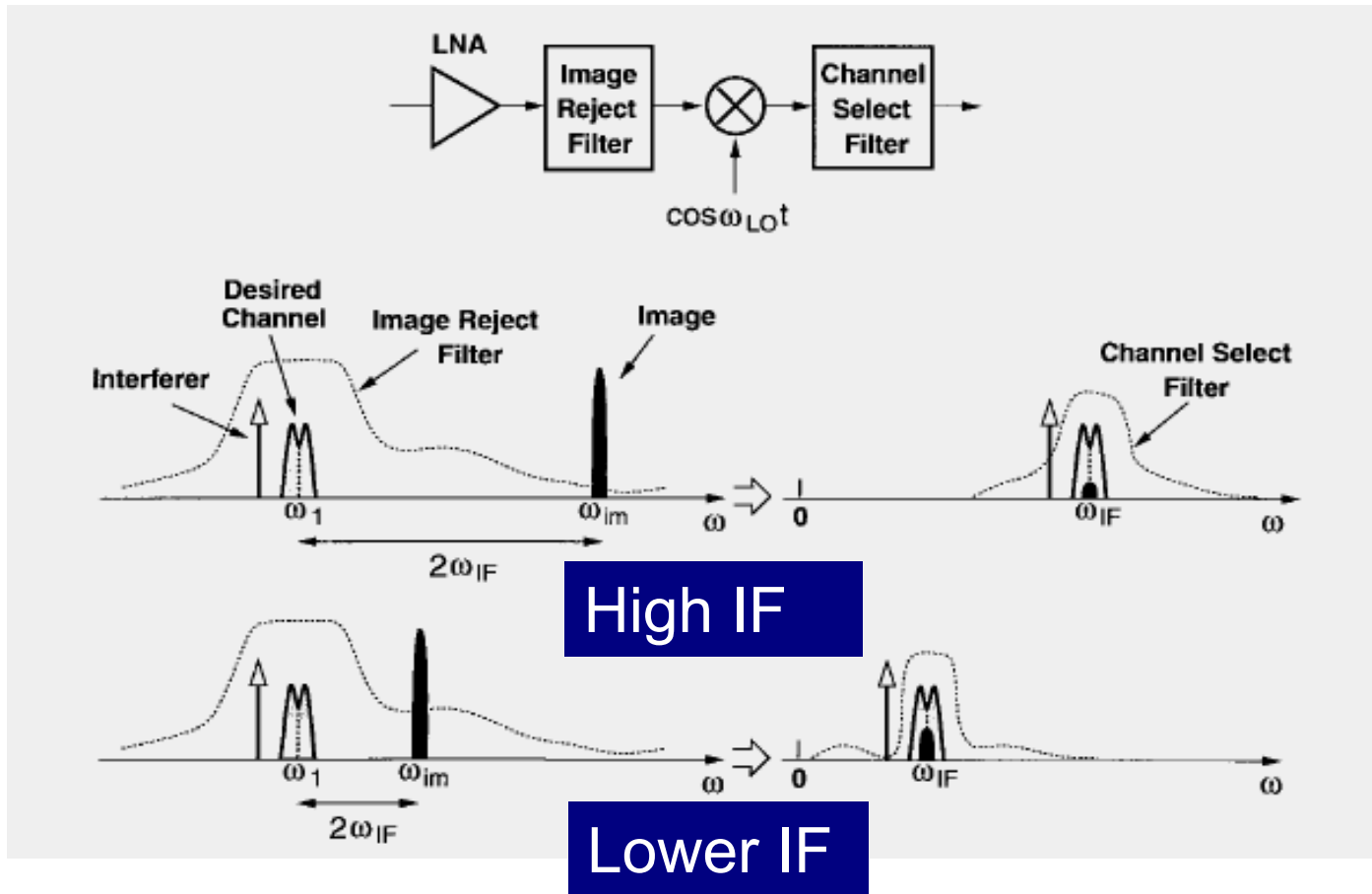

Super-heterodyne receiver (II)

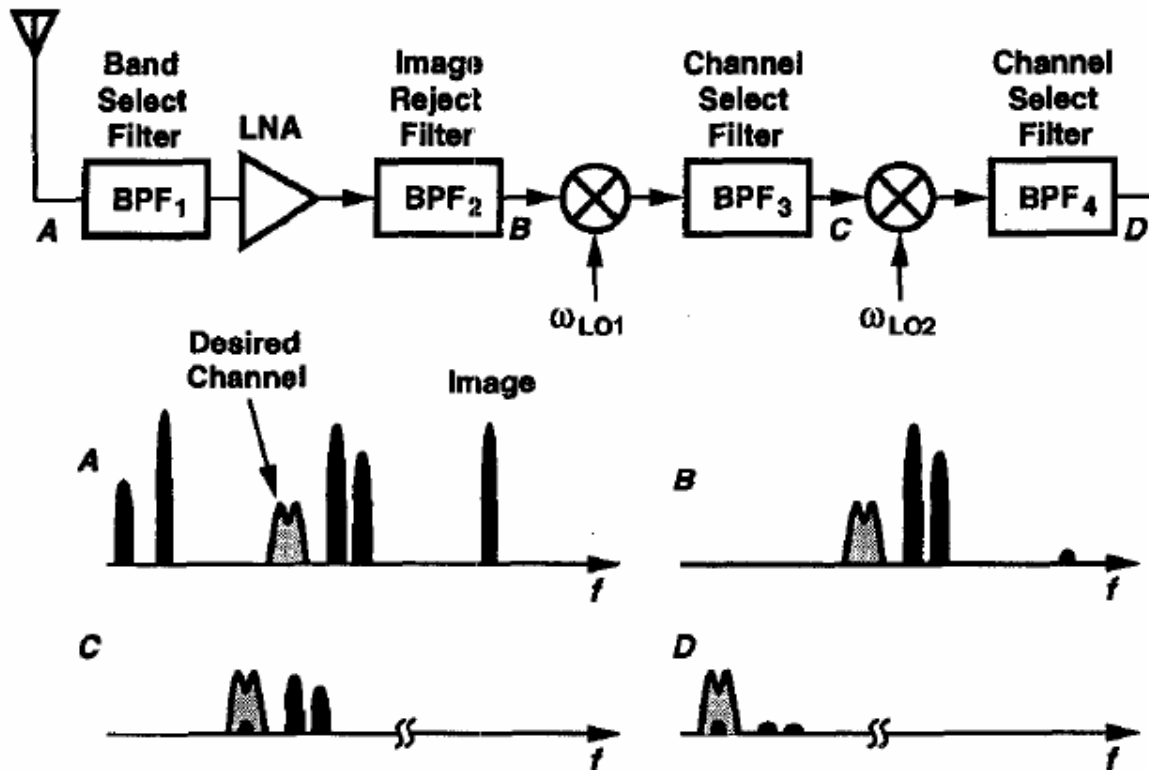

An example of a double-conversion receiver (two IFs)



Advantages & Disadvantages Super-heterodyne receiver

Advantages:

- Excellent selectivity: selection of small signals in the presence of strong interfering signals (interferers).



Disadvantages:

- Bulky external RF and IF filters normally needed: expensive, pin-count, power-hungry (50 Ohm interface)
- Several spurious frequency components due to the frequency conversions: good frequency planning needed.

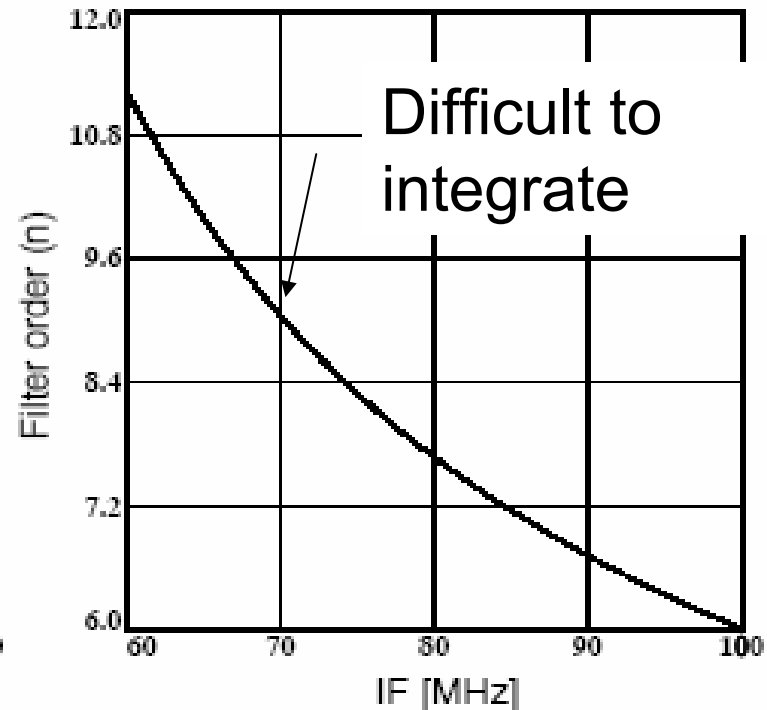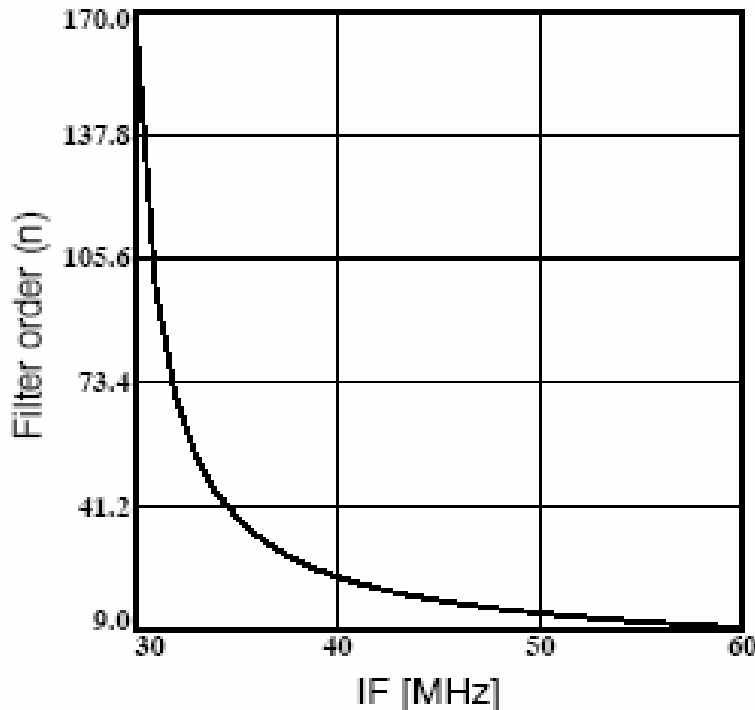Example of requirements of a DECT RF filter versus IF

$$f_{image} = f_{wanted} - 2IF$$


DECT works at 1.9 GHz
 Assume 20 dB image suppression, and B=100 MHz





Direct- Conversion receiver

Direct-conversion receiver

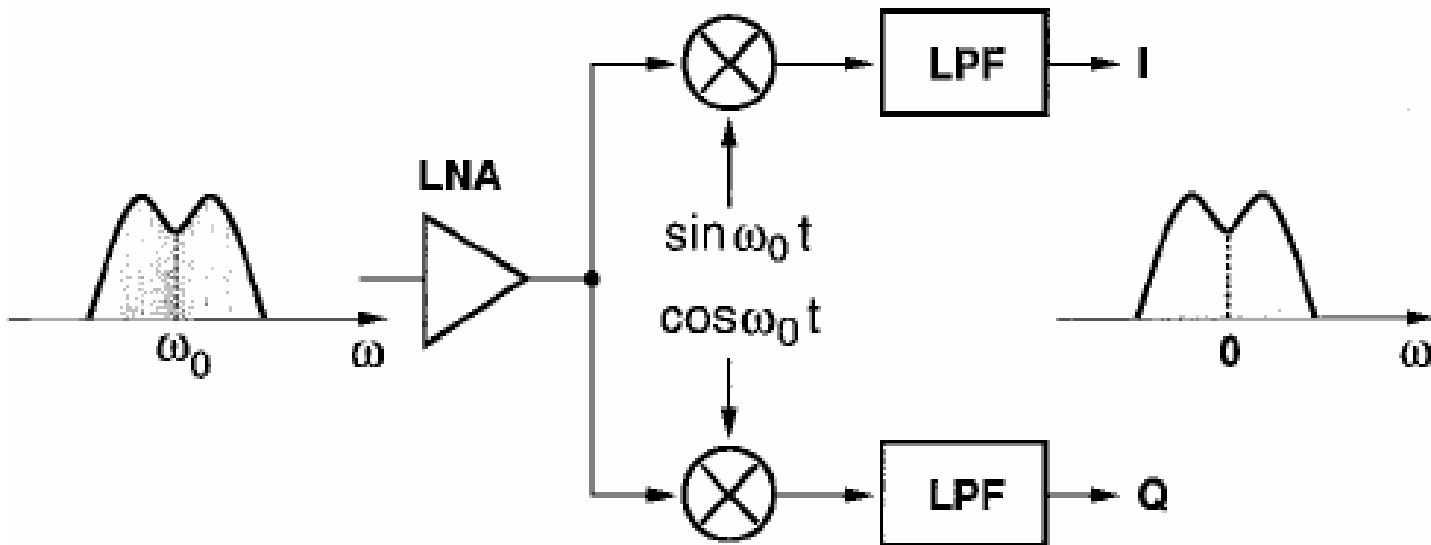

Wanted channel directly converted to baseband (“0 Hz”)



Advantages of direct-conversion


For phase and frequency modulated signals, direct-conversion requires I/Q signals.

Advantages:



- No image, since the wanted signal is its image ($\omega_{IF}=0$)
- The IF filter in a super-heterodyne receiver is replaced by low-pass filters
- Low-pass filters are easy to integrate; in general direct-conversion (Zero-IF) receivers allow a high level of integration.

Disadvantages / design issues of direct-conversion

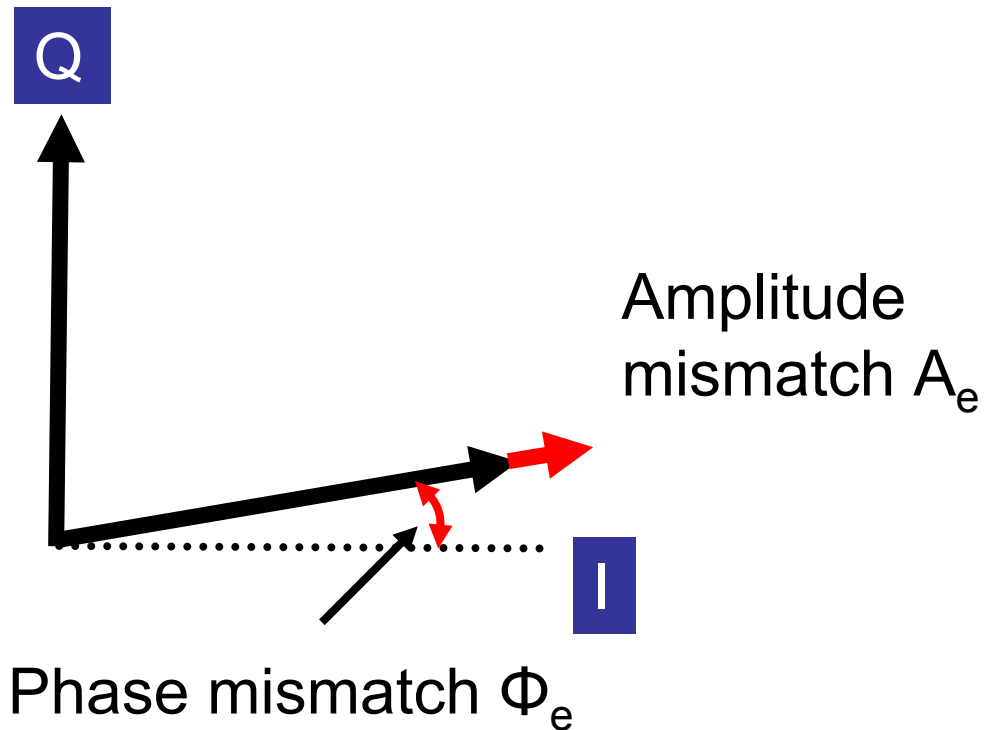- Cross-talk (image-problem) when there is amplitude or phase mismatch between I and Q channel.



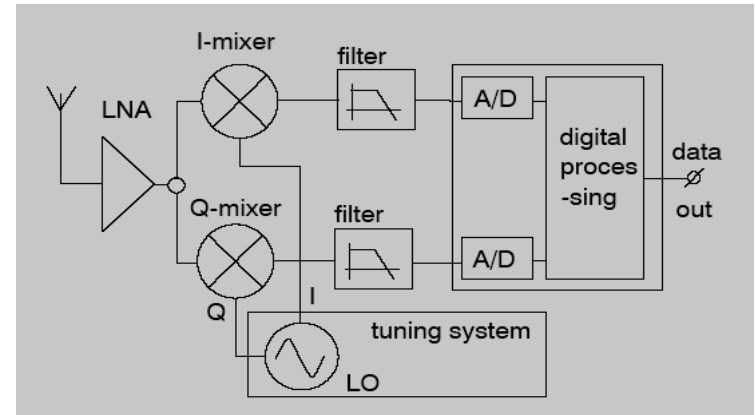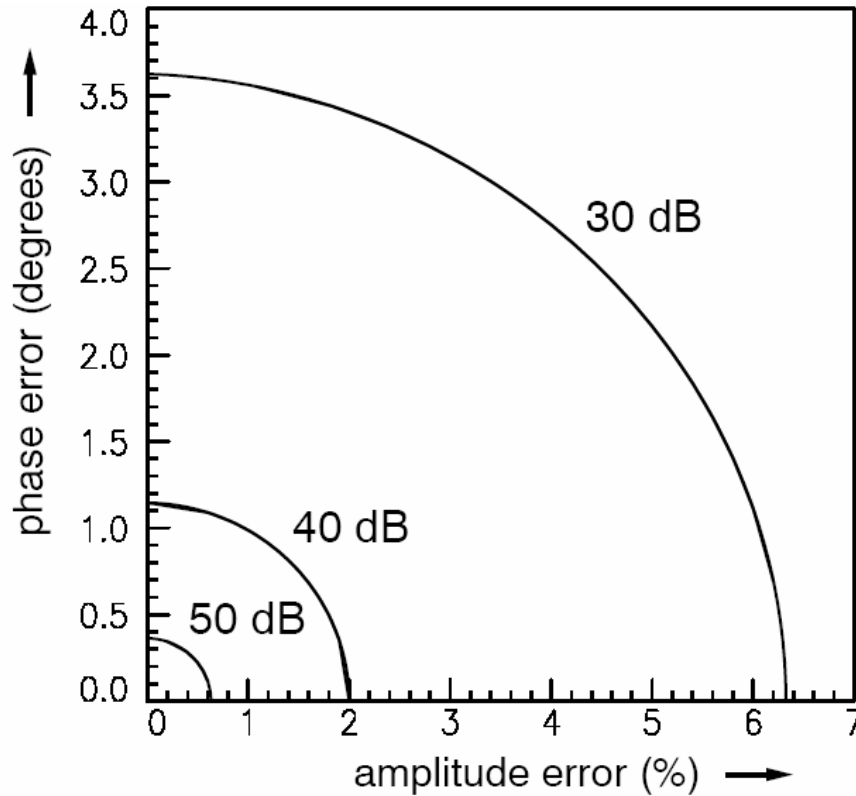Disadvantages / design issues of direct-conversion: I/Q mismatch




$$IRR \approx 10 \log \left(\frac{4}{A_e^2 + \phi_e^2} \right)$$

Amplitude error

Phase error


Effect of I/Q mismatch

Demodulated QPSK data

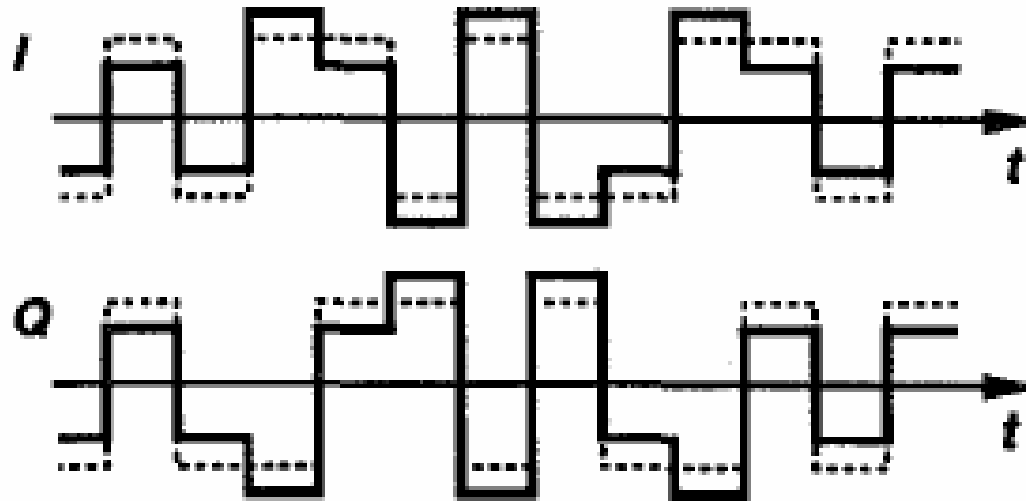

For example, phase imbalance yields cross-talk in the demodulated quadrature signal, thus lowering the SNR (BER) of the received signal.

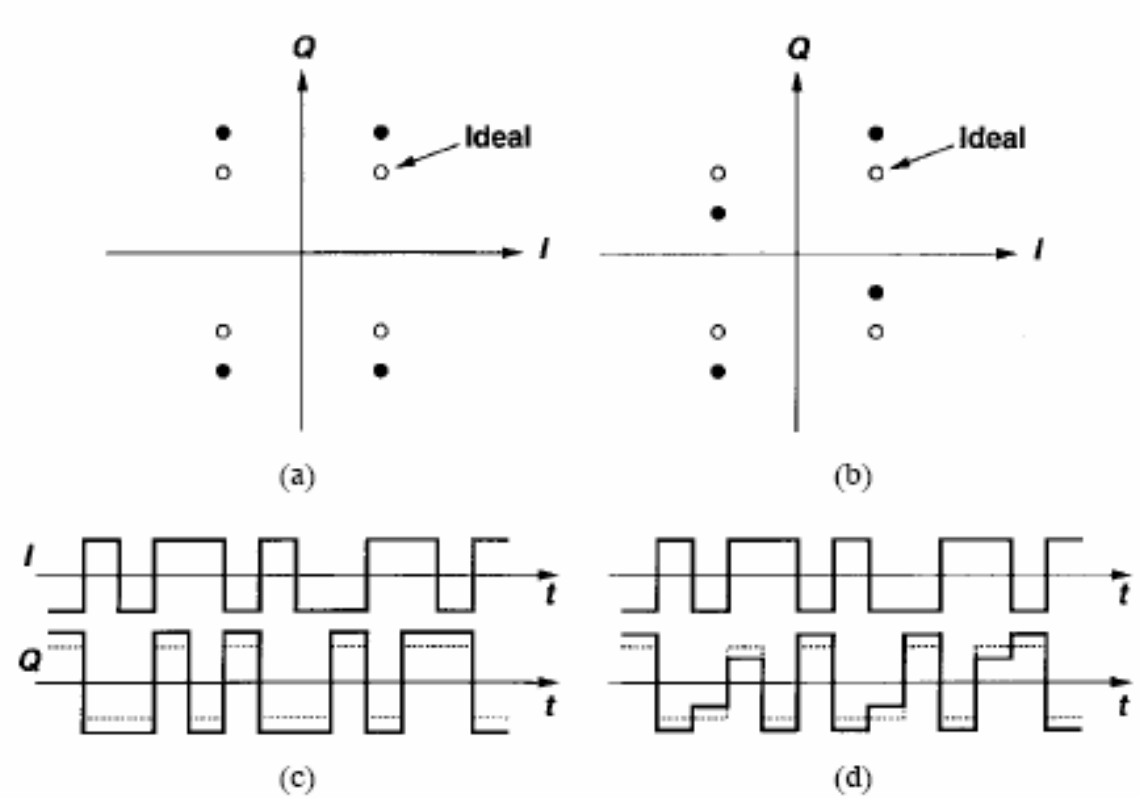
Effect of I/Q mismatch on constellation diagram for QPSK modulation



Effect of gain mismatch


Effect of phase mismatch

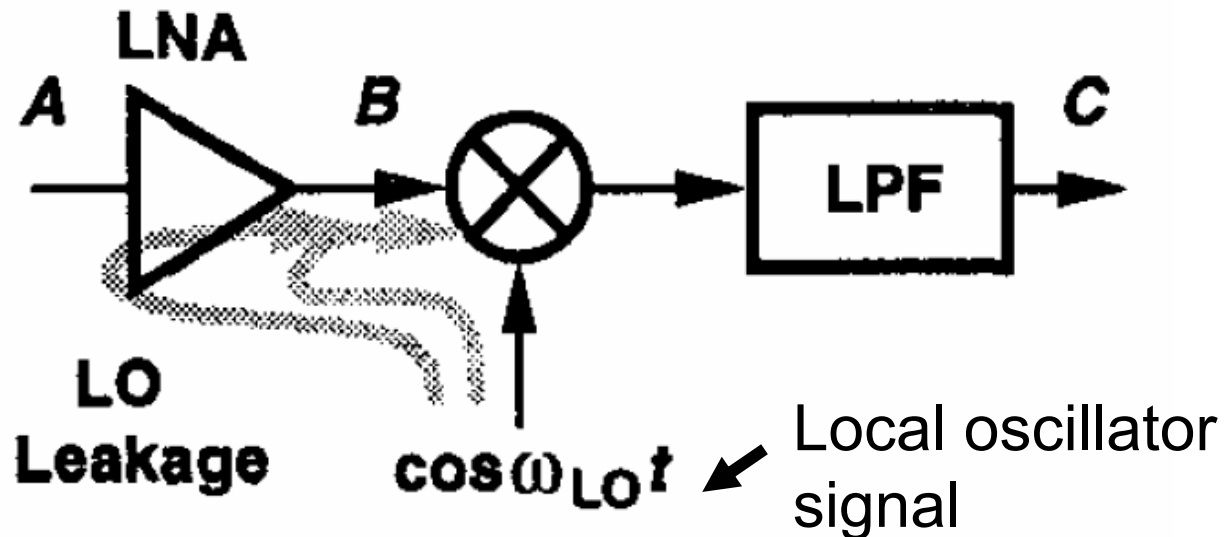Disadvantages / design issues of direct-conversion: LO leakage




The local oscillator signal leaks to RF input port of the mixer (LO leakage), which causes self-mixing. This results in (modulated) DC components (that cannot be removed by AC-coupling if there is a lot signal content (energy) located around DC).

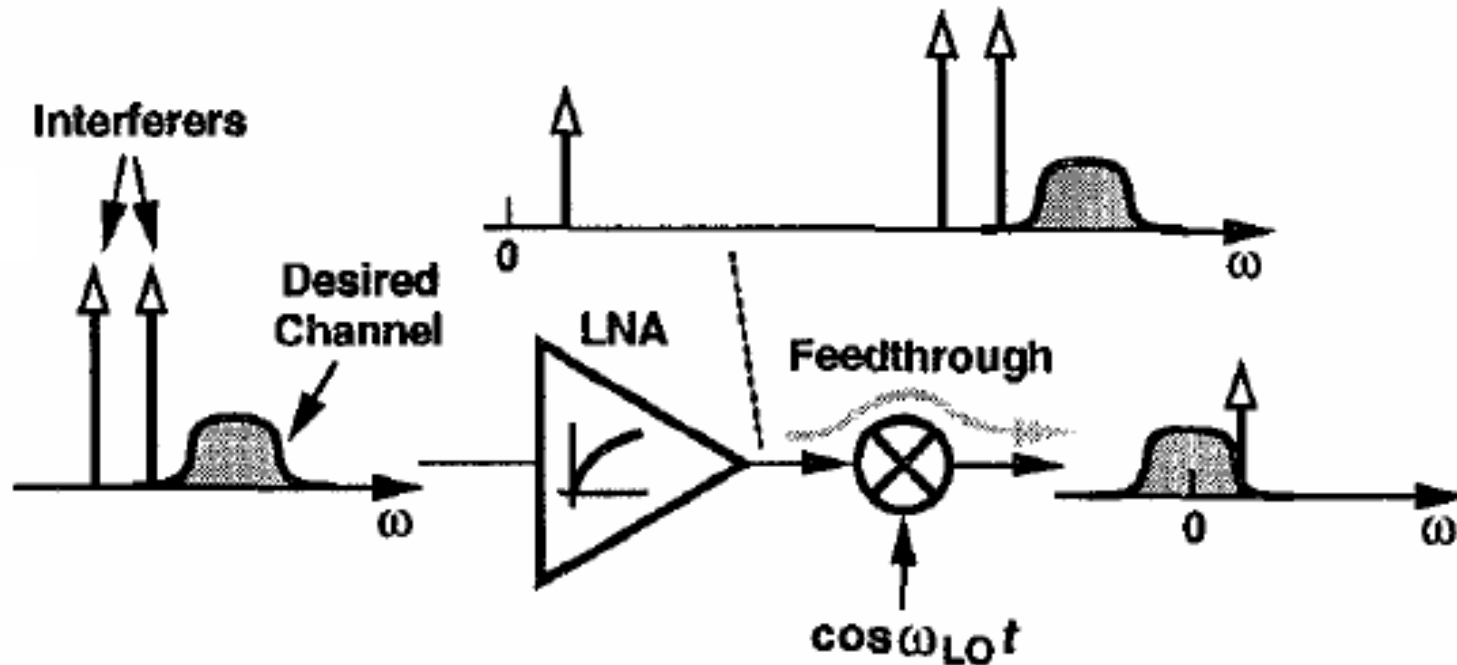Disadvantages / design issues of direct-conversion: IM2 products



Even-order distortion creates low-frequency beat notes that can be passed on by the mixer in case of mismatch

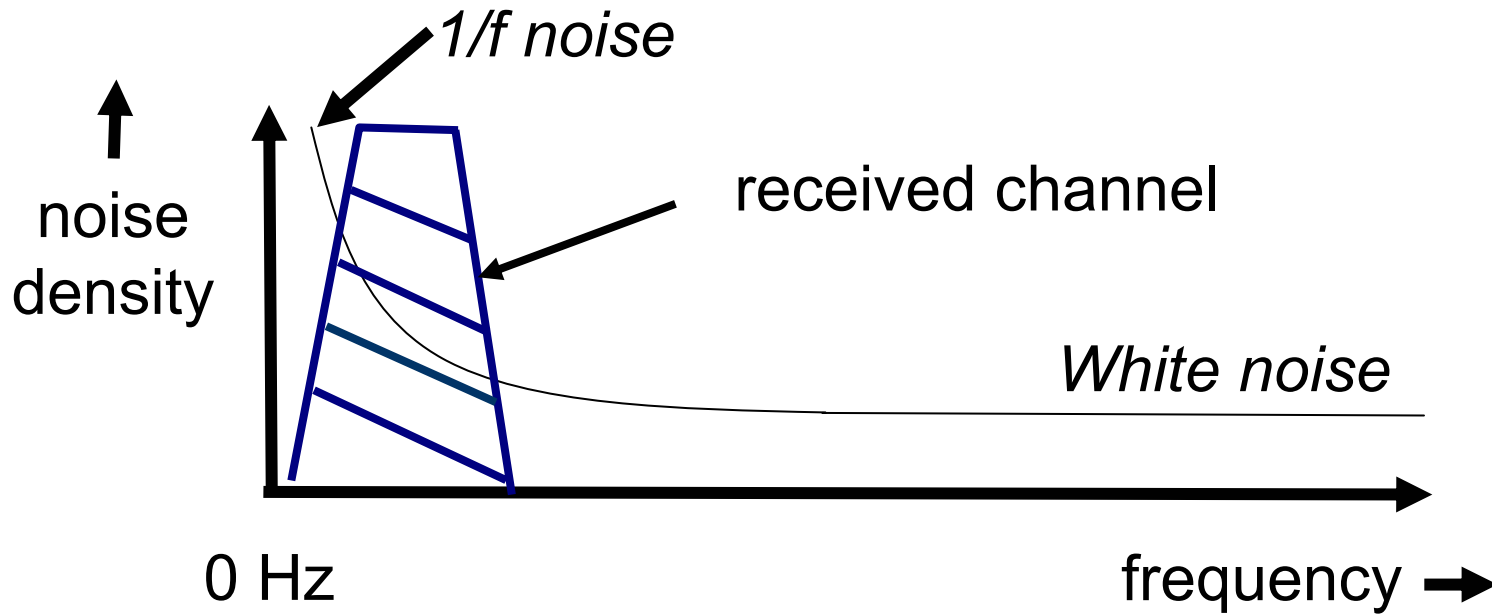Disadvantages / design issues of direct-conversion: 1/f noise



Especially, for CMOS transceivers, 1/f noise can pose big problems for the received channel that is down-converted in the middle of the 1/f noise.




Direct-conversion: frequently used

- Despite the many design challenges direct-conversion receivers face, they are used in many products.
- The high level of integration it allows is one of the main driving forces behind its use.
- Especially in consumer electronics, costs are a dominant factor; external components are very expensive and influence the bill-of-material (BOM) in a negative sense.




Low-IF receivers

Low-IF receiver

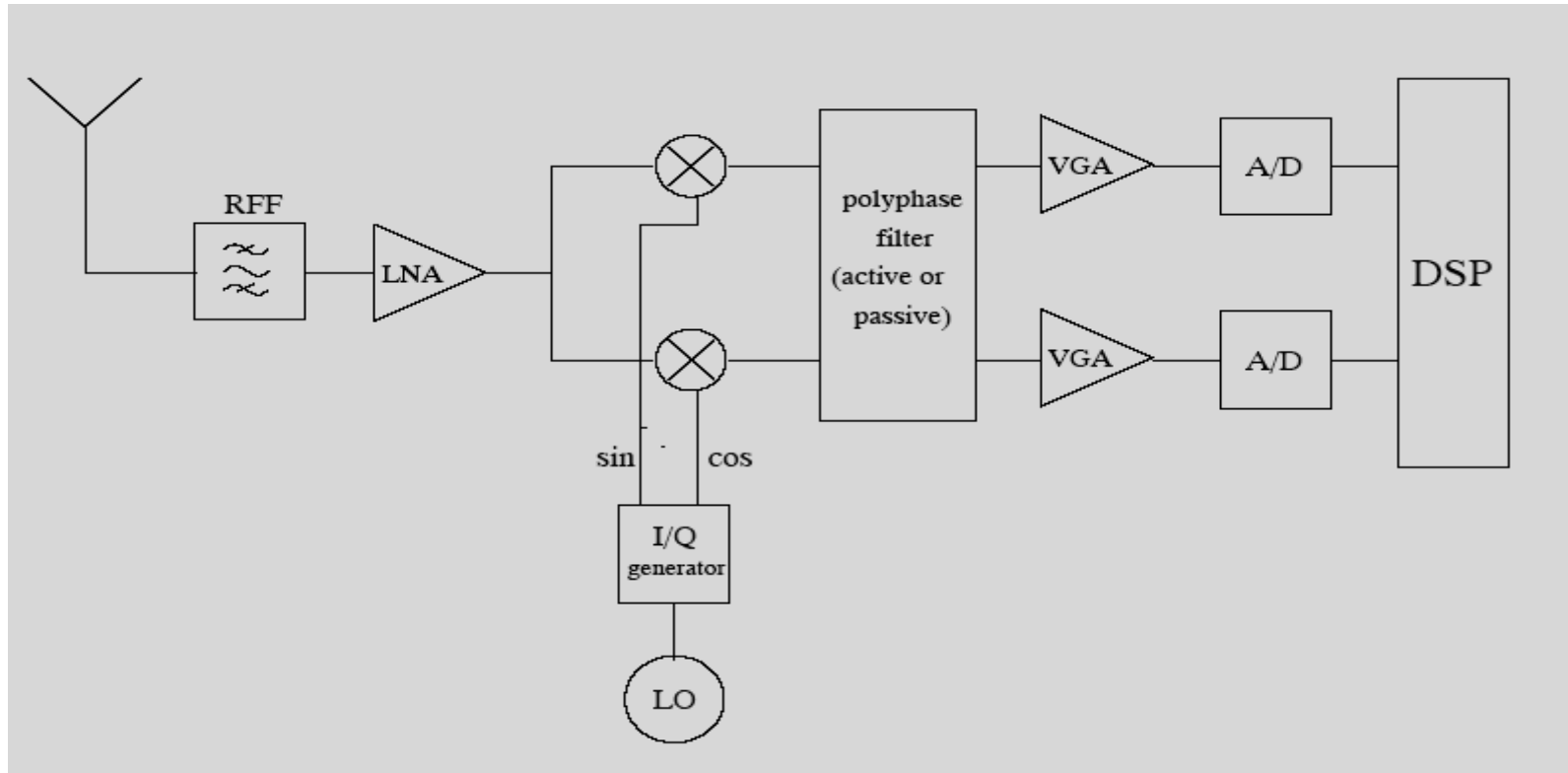

Wanted channel is converted to a low, non-zero IF.

Image is suppressed in a Low-IF receiver by a poly-phase filter

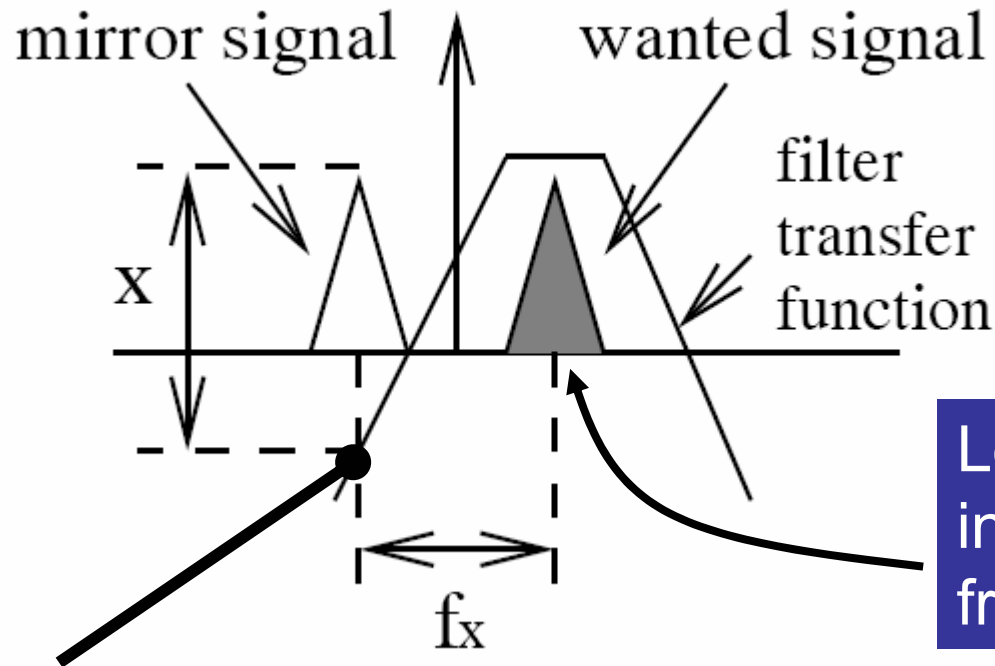

A poly-phase filter (normally I- and Q-phase) can have an asymmetric transfer function with respect to 0 Hz.



Advantages Low-IF receiver

Advantages:

- Image is suppressed by a poly-phase filter, which can be integrated. Because of matching, 30-35 dB image suppression is typical.
- The IF-frequency is not 0 Hz, hence the influence of $1/f$ noise in the receiver chain is less.
- A high-pass filter may be used after the mixer to remove unwanted DC components, assuming the used modulation allows removal of part of the energy in the spectrum around DC.



Disadvantages/ design issues of a low-IF receiver


disadvantages:

- Image suppression is limited by I/Q matching (same problem as direct-conversion architectures).
- Poly-phase filters may be power-hungry (relative compared to low-pass filters)
- Poly-phase filters may require a lot of chip area (large capacitors, because of the low-IF).
- Even-order distortion components may still produce unwanted beat notes in the wanted channel, after down-conversion

Image-reject architectures

Hartley image-reject receiver

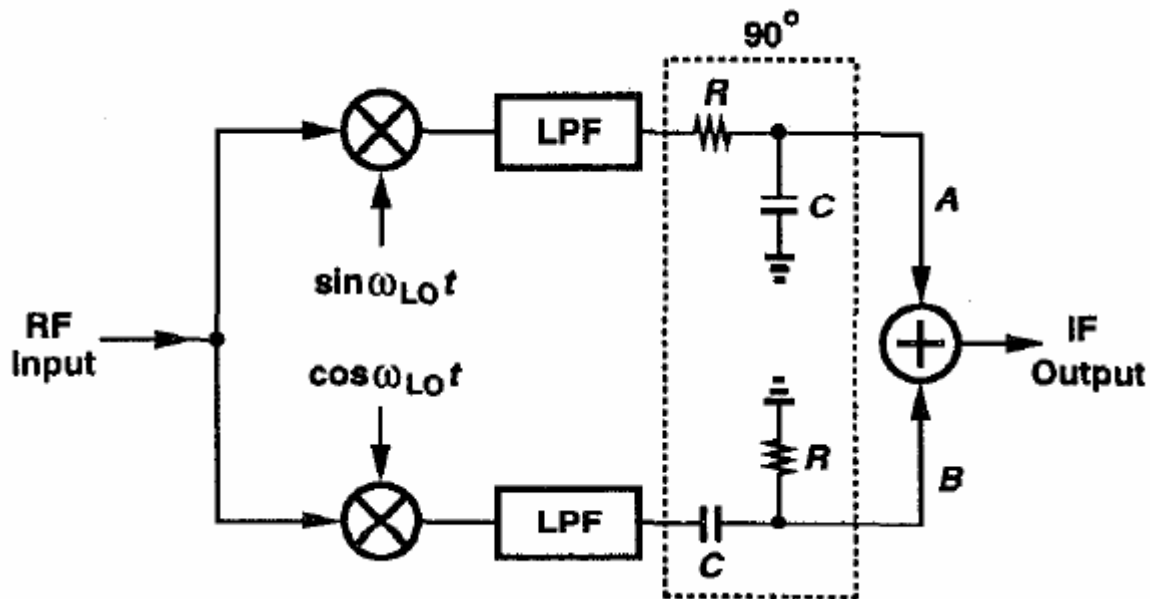Summed signal is free from image under perfect matching conditions.



The main draw-back is its high sensitivity to mismatches between the two signal paths.

Spectra in Hartley architecture


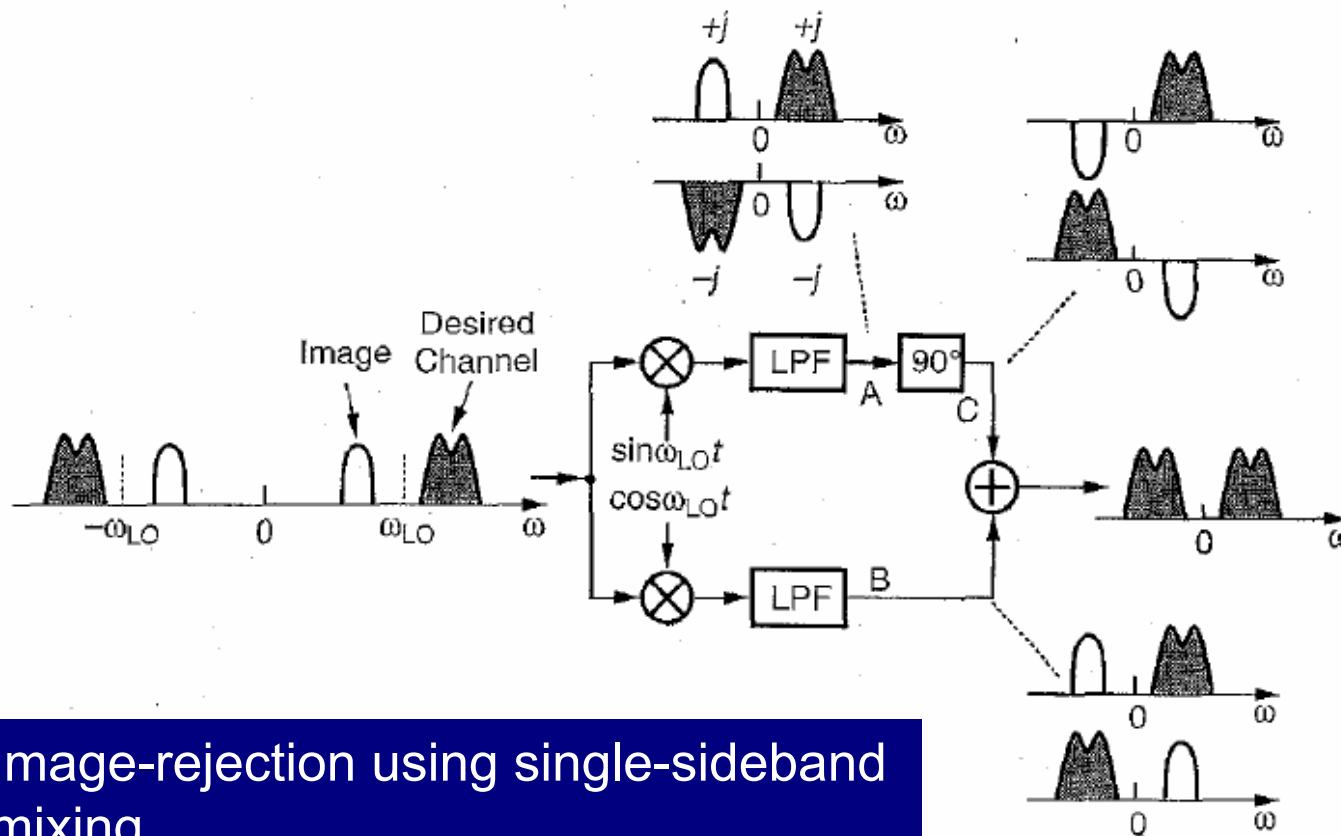


Image-rejection using single-sideband mixing.


Weaver image-reject receiver

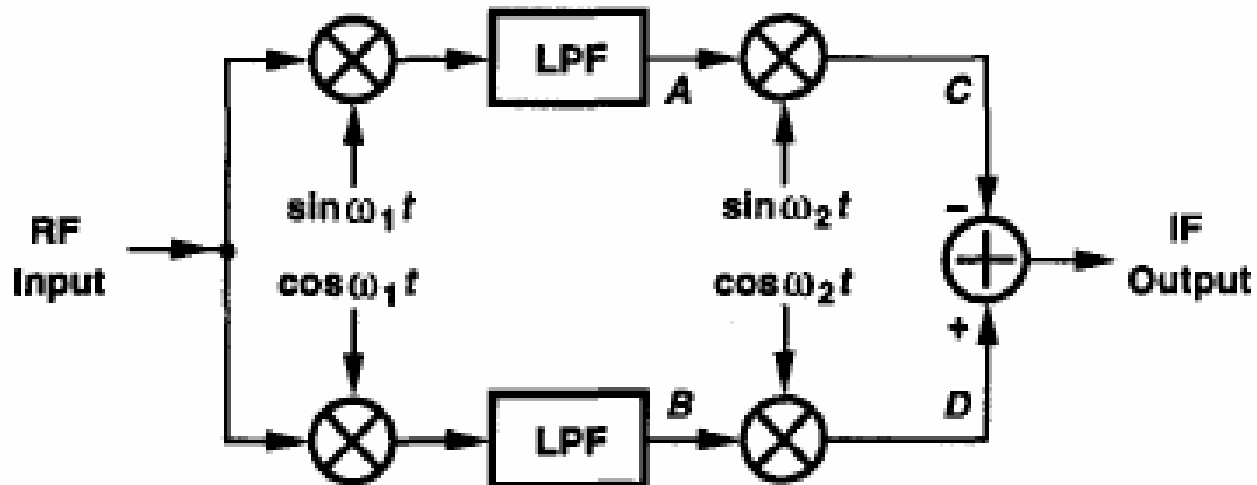RC-CR network which is present in the Hartley receiver architecture is avoided by a second time quadrature mixing.



The architecture is still sensitive to I/Q mismatch and requires two LOs.

Spectra in Weaver architecture

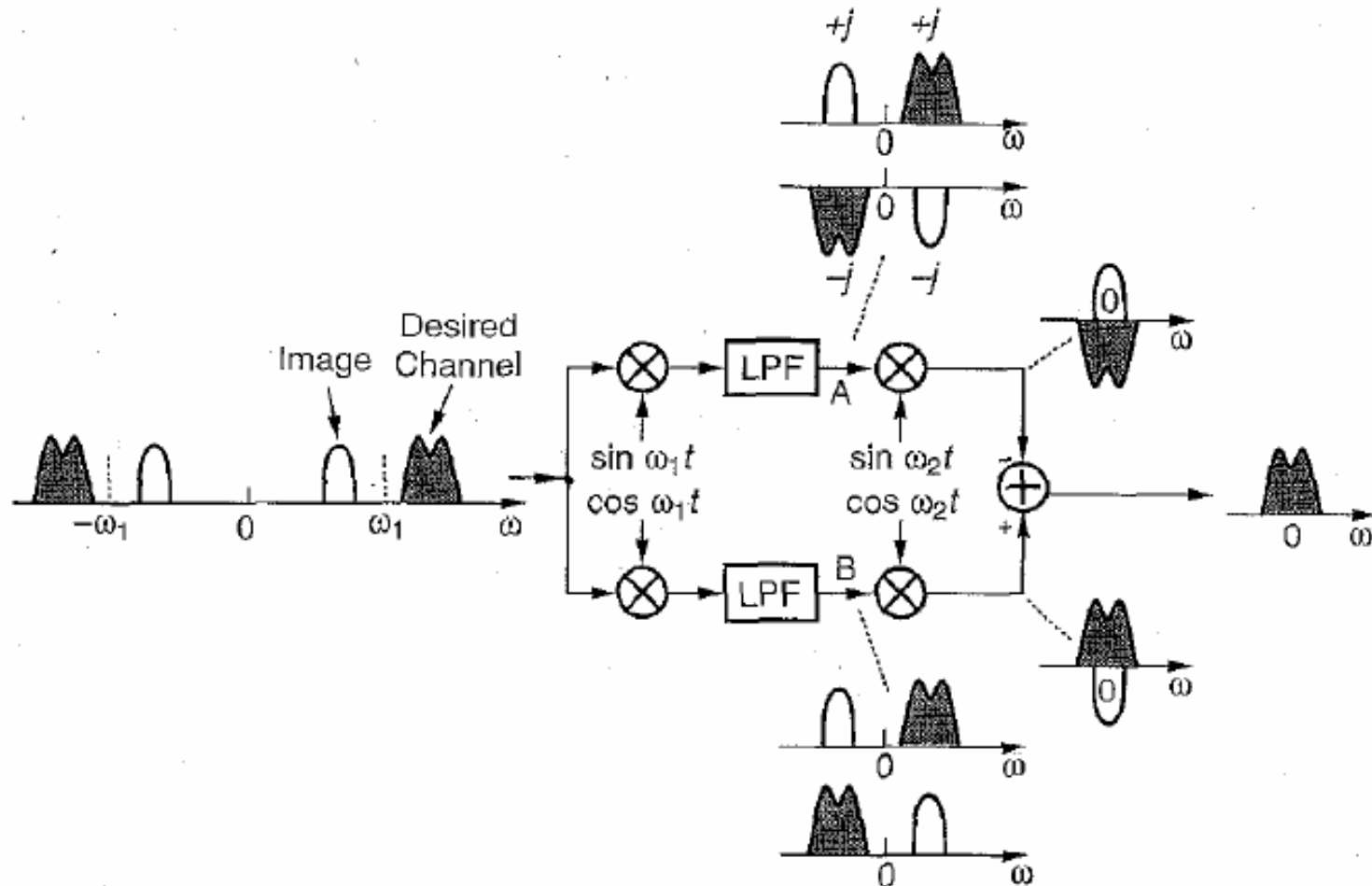




Digital-IF Receiver

Digital-IF Receiver

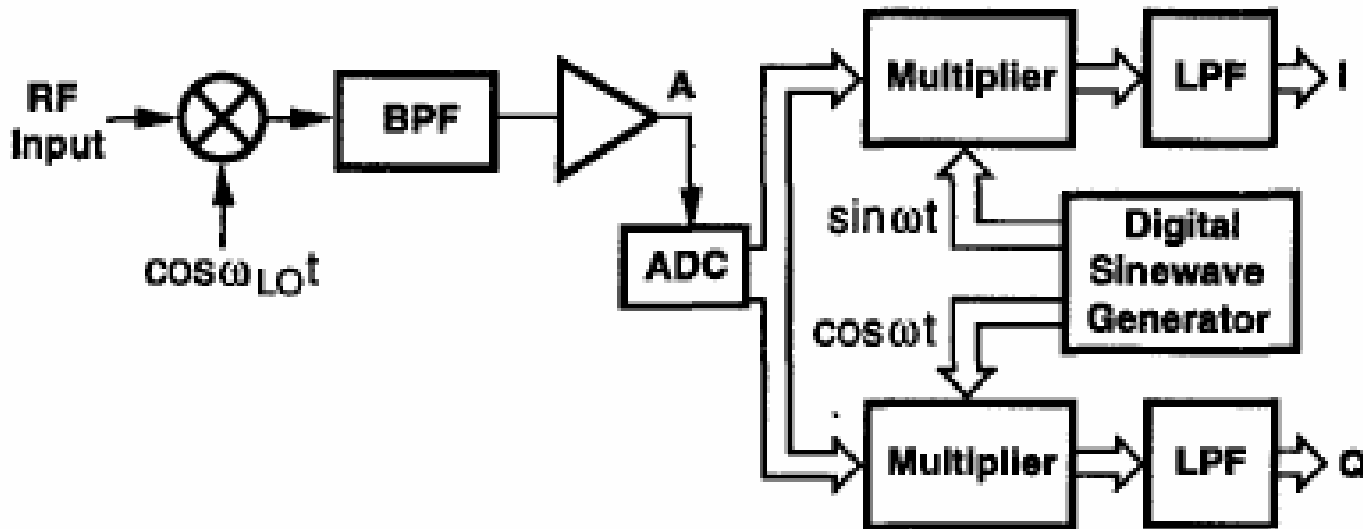Received signal is digitized at the IF: high A/D requirements, but e.g. possible for FM radio.




I/Q matching no issue: transferred to the digital domain



Examples of derivative receiver architectures


Six-mixer Low-IF architecture

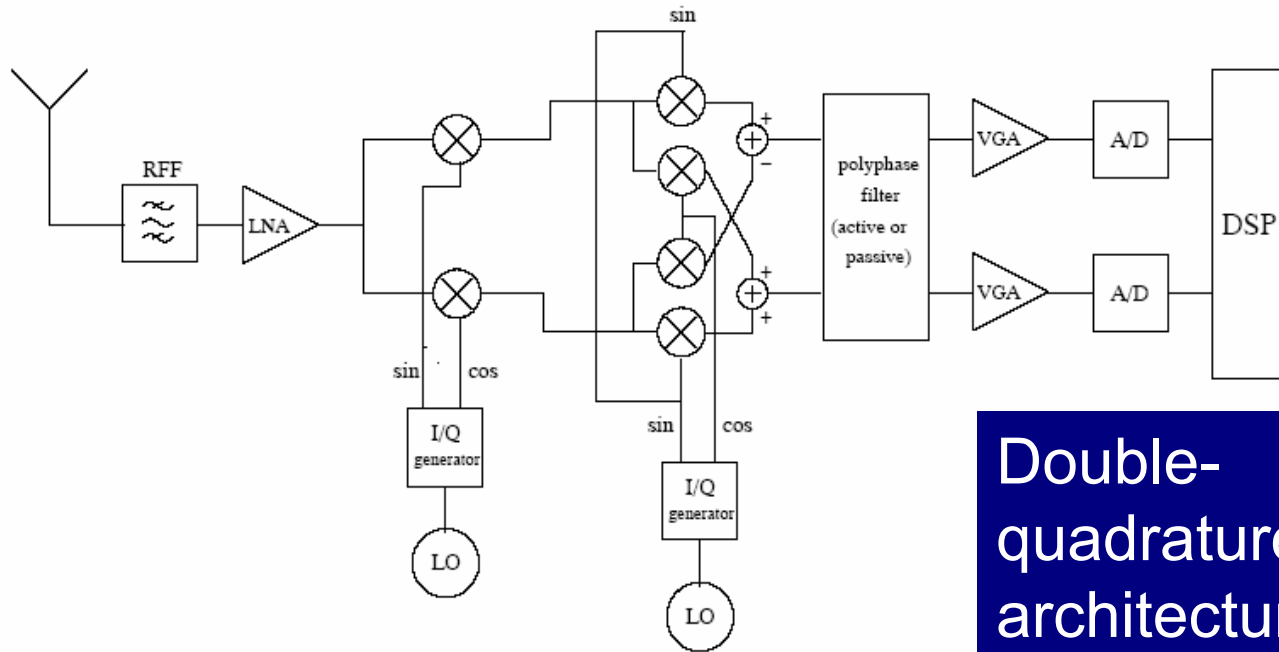

Double-quadrature architecture


IRR can be significant higher than 40 dB at the cost of more power dissipation (six mixers) and a higher complexity.

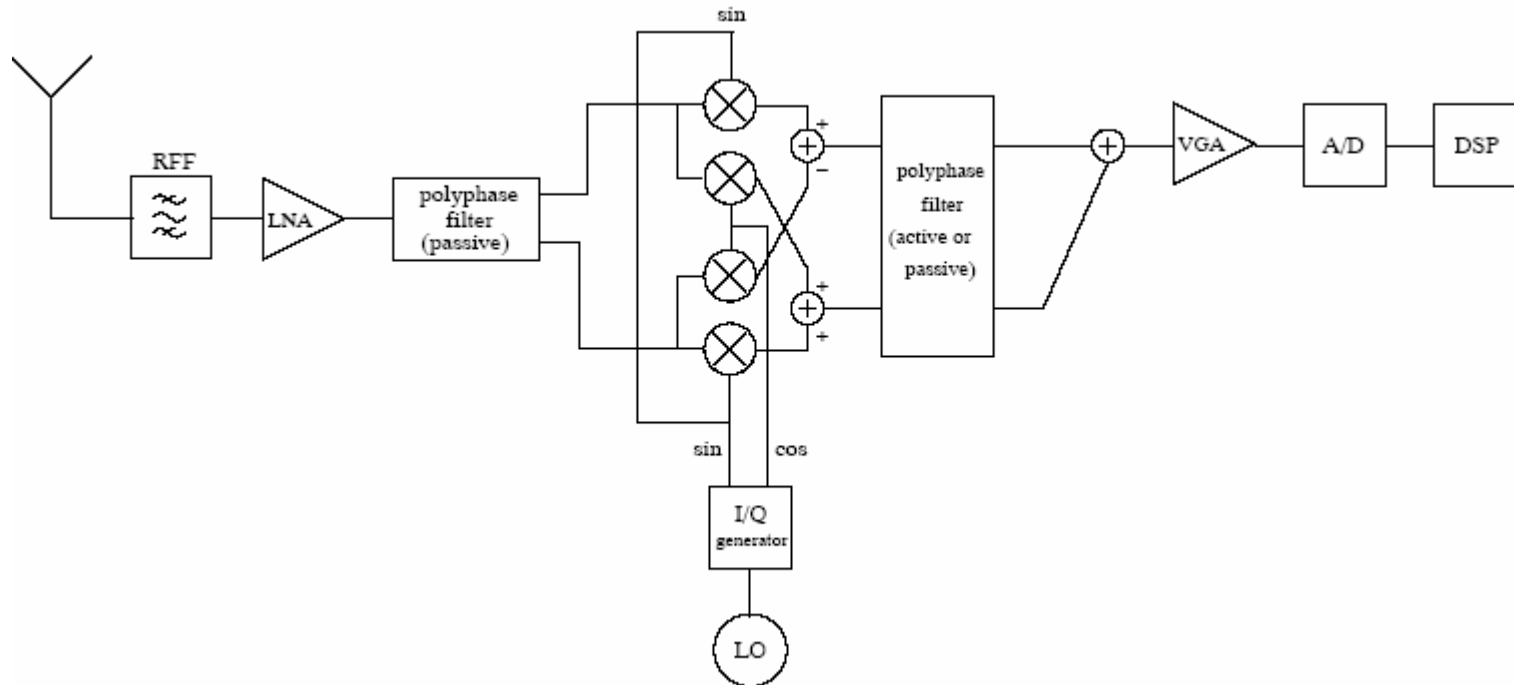Double-quadrature receiver with poly-phase filter in the receive path




IRR can be significant higher than 40 dB at the cost of more power dissipation and a lower sensitivity (RF poly-phase filter) and higher complexity.

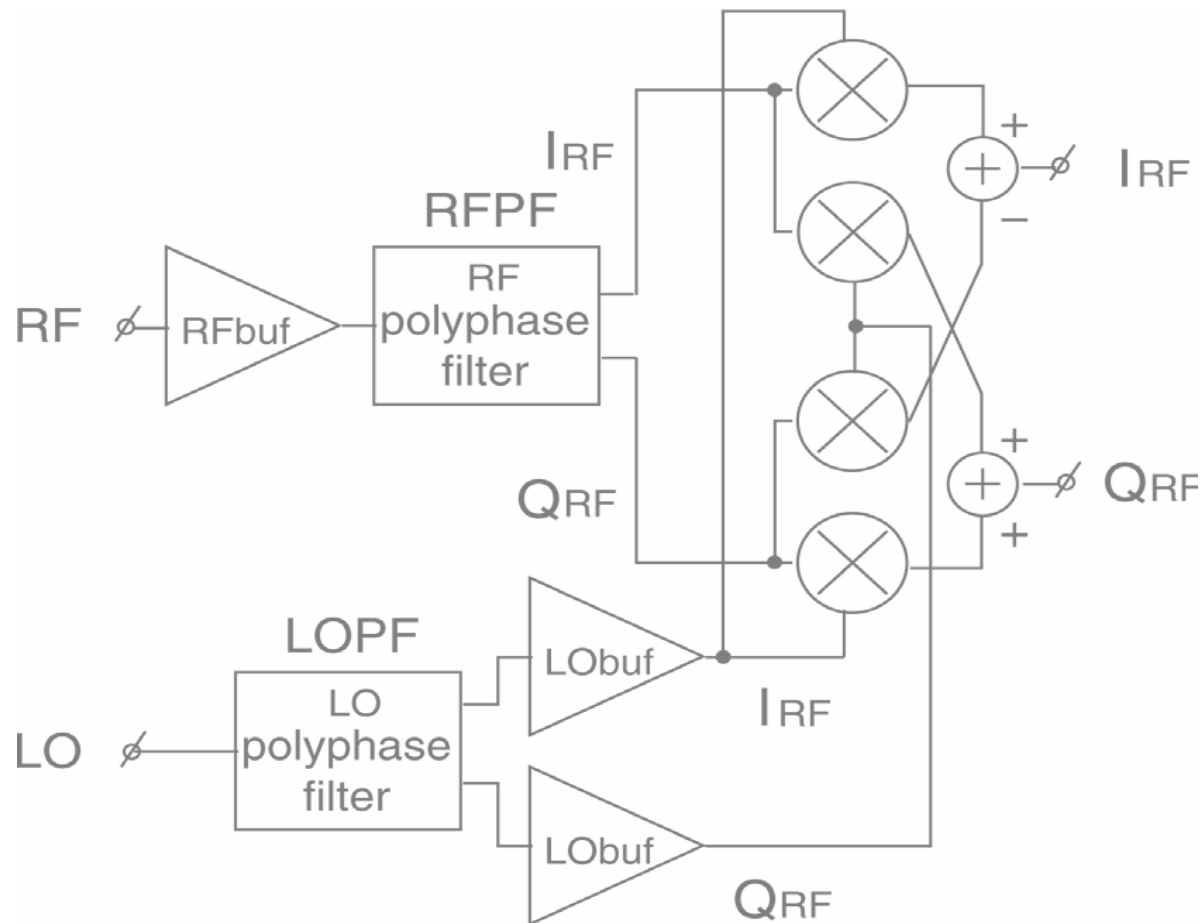Example of architecture realized in the Mixed-signal Microelectronics group




Layout of realized chip

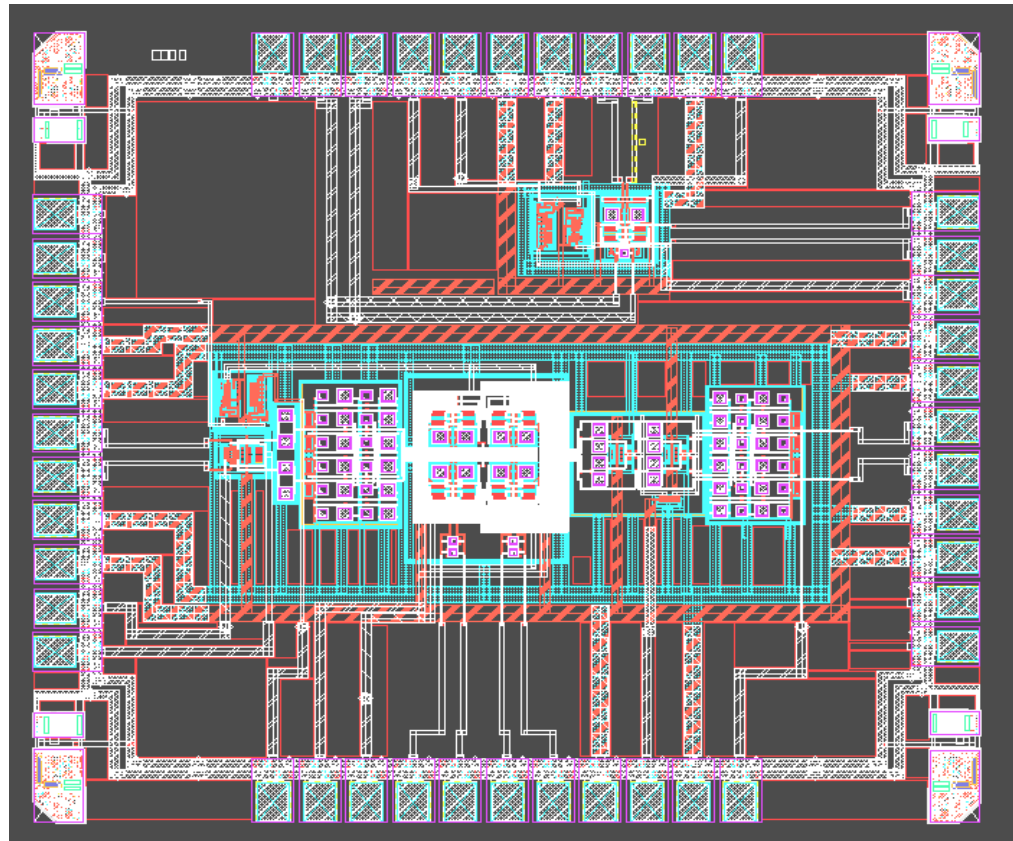



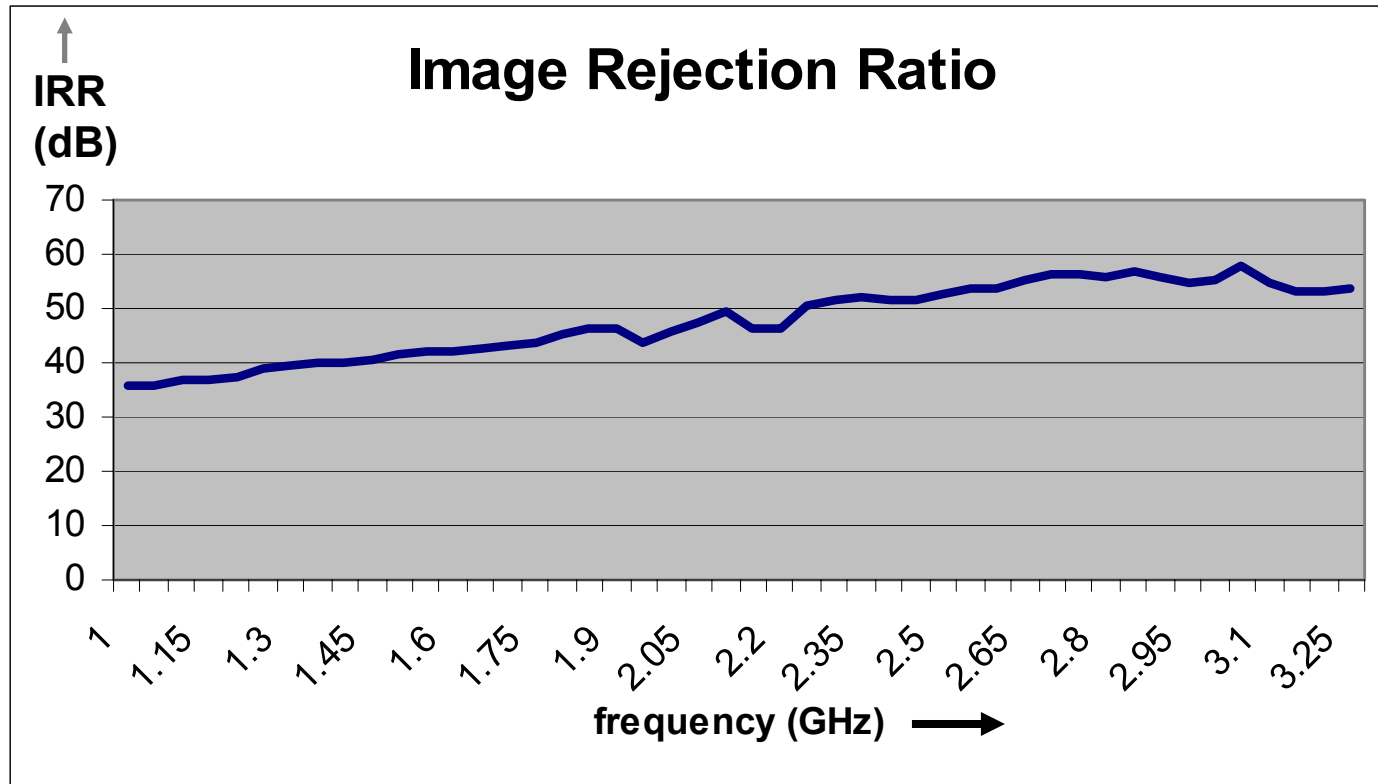Measured IRR of realized receiver front-end




Broadband High Image Rejection




Quadrature generation

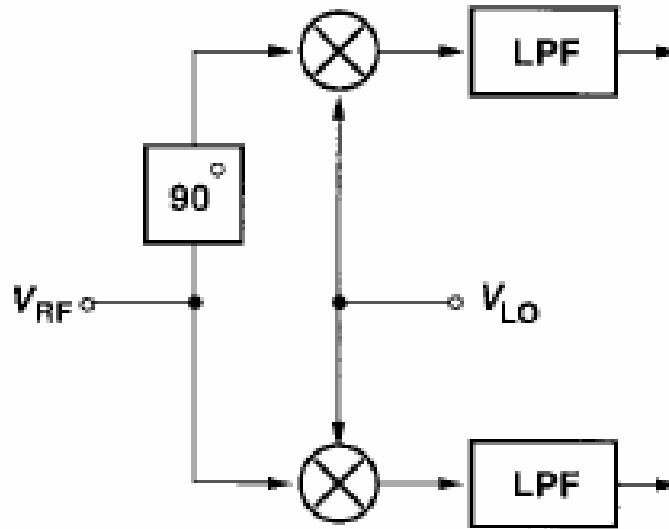Most often I/Q generation is done in the LO path




I/Q generation in RF path

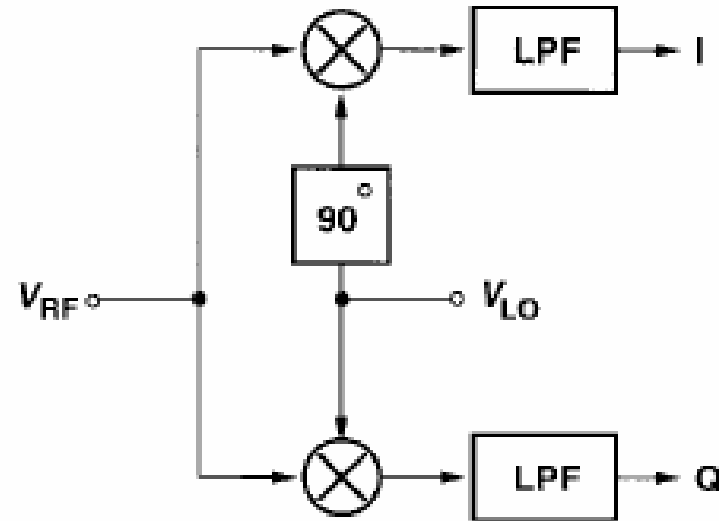

I/Q generation in LO path

I/Q generation (1)

RC-CR network

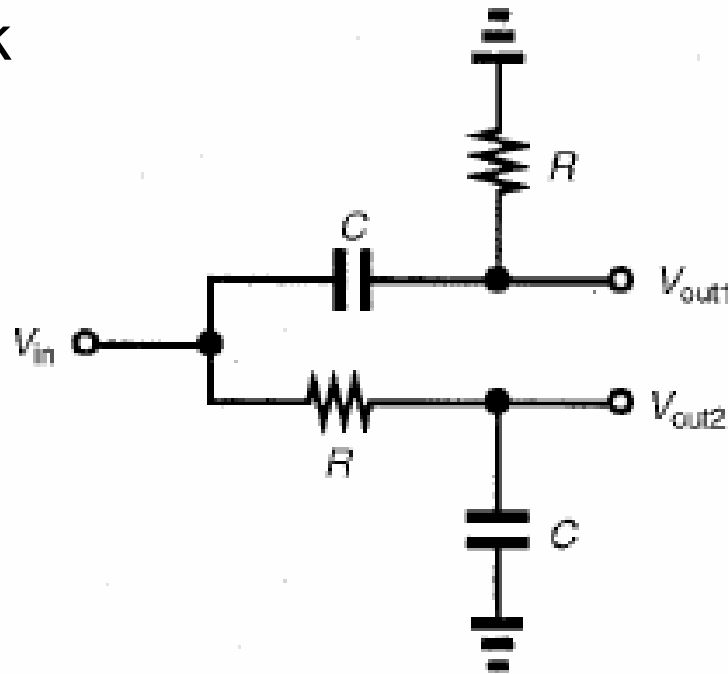


In-phase
signal

Quadrature
signal

Phase-shift always 90 degrees between outputs. Amplitudes only equal for $\omega=1/(RC)$. But clipping (limiter) may be used, for example in LO path.

I/Q generation (2)

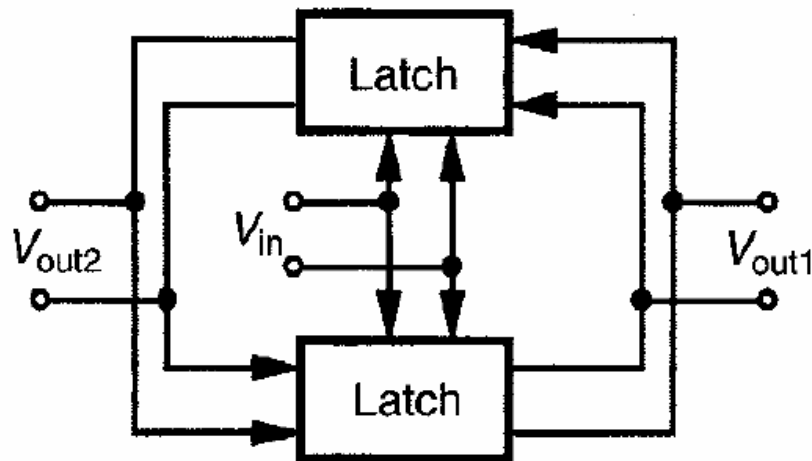
Using a divider-by-two and driving it at $2 f_{osc}$



Outputs in quadrature when the input signal has a duty cycle of 50%. Two dividers can be used to improve the I/Q matching (but input signal must then be at $4 f_{osc}$).

I/Q generation (3)


Even-stage multi-phase LC oscillators:

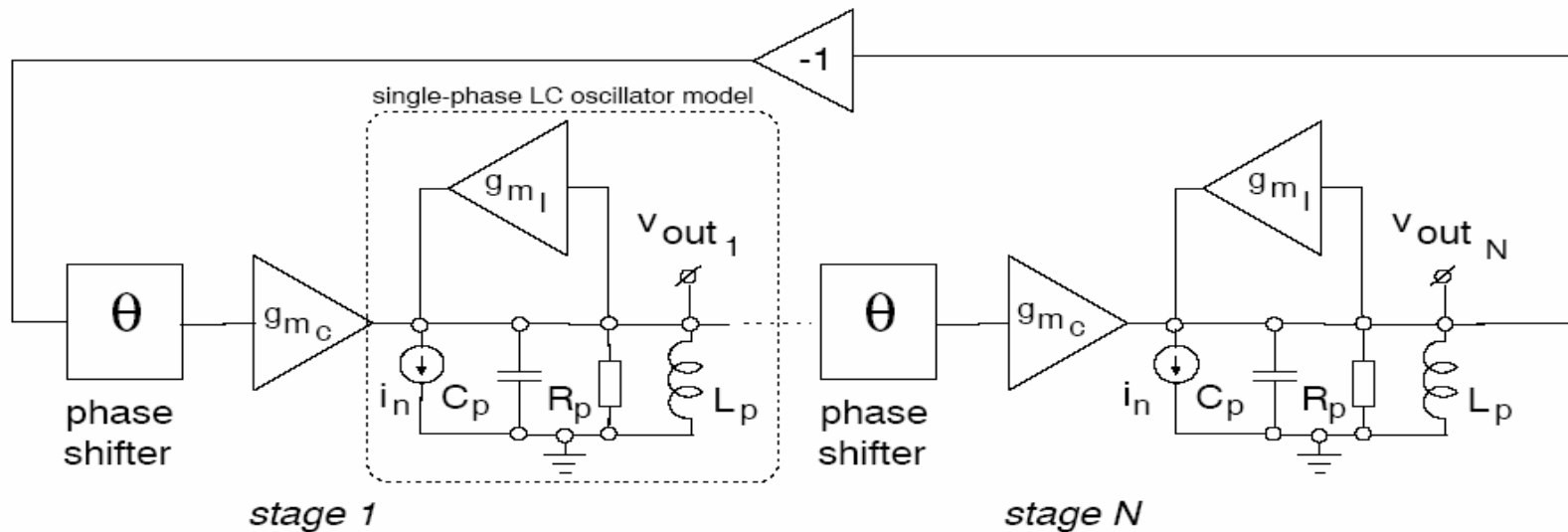

Inductors (2, balanced or 4 single) may require a lot chip area. Power should be compared to other solutions.

I/Q generation (4)

Even-stage ring oscillators oscillators:

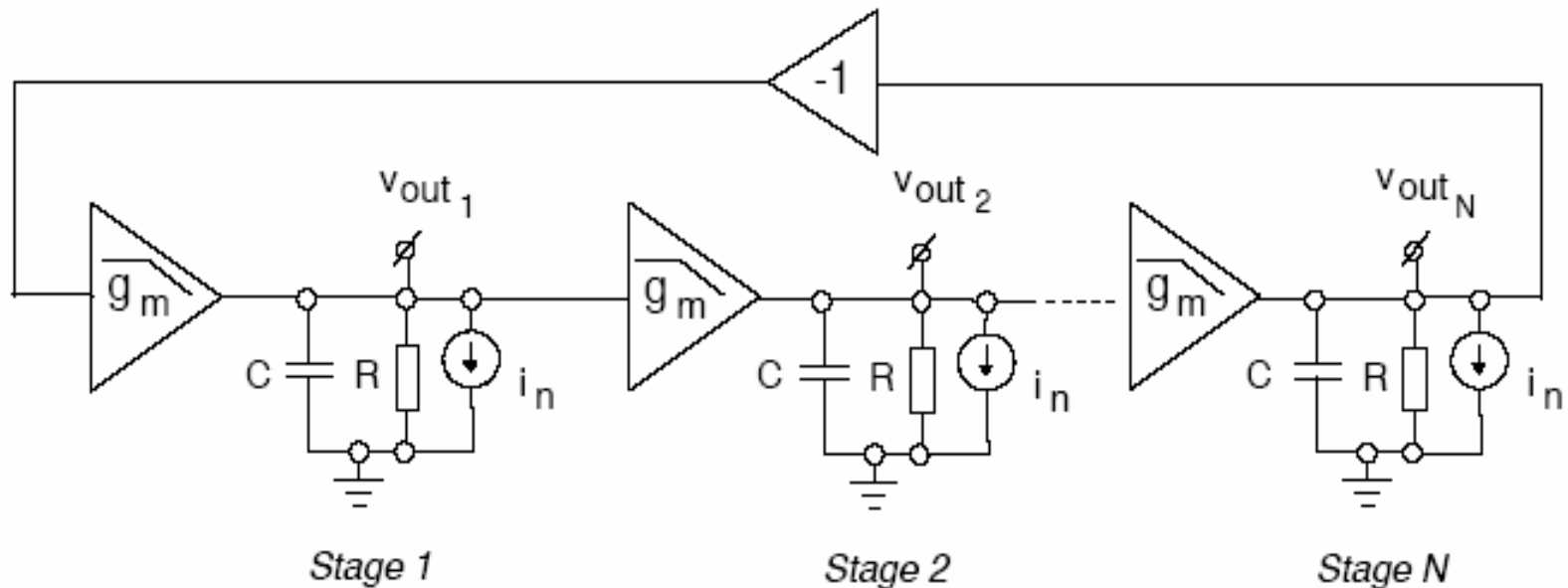

Ring oscillators are relatively very noisy compared to LC oscillators given the same power budget.



Some other I/Q generation methods

Oscillator at f_{osc} and poly-phase filter	+ good $\mathcal{L}(f_m)$ in combination with LC oscillator, - high noise floor, - high insertion loss, - bandwidth limited.
Oscillator at 2 (or 4) $\times f_{osc}$ with divider	+ good $\mathcal{L}(f_m)$ in combination with LC oscillator, - In case of division by 2 , 50% duty cycle of oscillator required, - oscillator must be constructed at 2 or $4 \times f_{osc}$ resulting in more power dissipation.
Double PLL loop: ring oscillator at f_{osc} locked to LC oscillator	+ good $\mathcal{L}(f_m)$, + wide-band, - high complexity, - high power dissipation.
Four-stage oscillator at $1/2 \cdot f_{osc}$ with mixers or addition of phases	+ oscillator required at half the desired frequency, + wide-band if a ring oscillator is used, - large chip area if a (four-stage) LC oscillator is used, - poor $\mathcal{L}(f_m)$ if a ring oscillator is used.
One of above techniques with calibration technique added	properties of one of above methods, + improved amplitude and phase matching, + can have improved bandwidth, - high complexity, - high power dissipation (depending on technique).
Digital implementation, for example utilizing lookup table and reference clock	+ accurate, + wide-band, - A/D-converter needed if signals are needed in analog domain - low frequency.



Transmitter architectures

Basic function of a transmitter

What do we want of a transmitter front-end:




A transmitter converts a baseband signal to a higher frequency (i.e. to a specific channel) and amplifies the signal to a specified power level that can drive the antenna.



Baseband TX considerations


Constant envelope signals

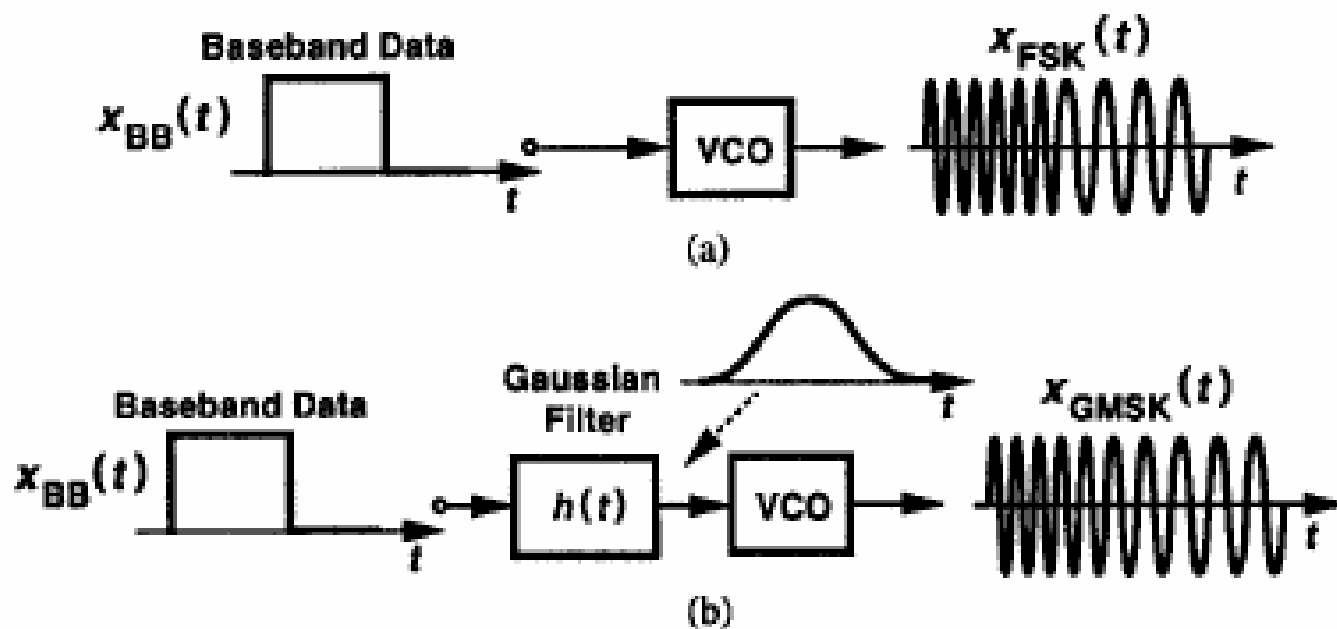


The amplitude of the baseband modulated signal does not vary in time: only info in the phase. This allows the use of a high-efficient switching and non-linear (limiting) power amplifier.

Pulse shaping can be used to limit spectral content of constant envelope signals

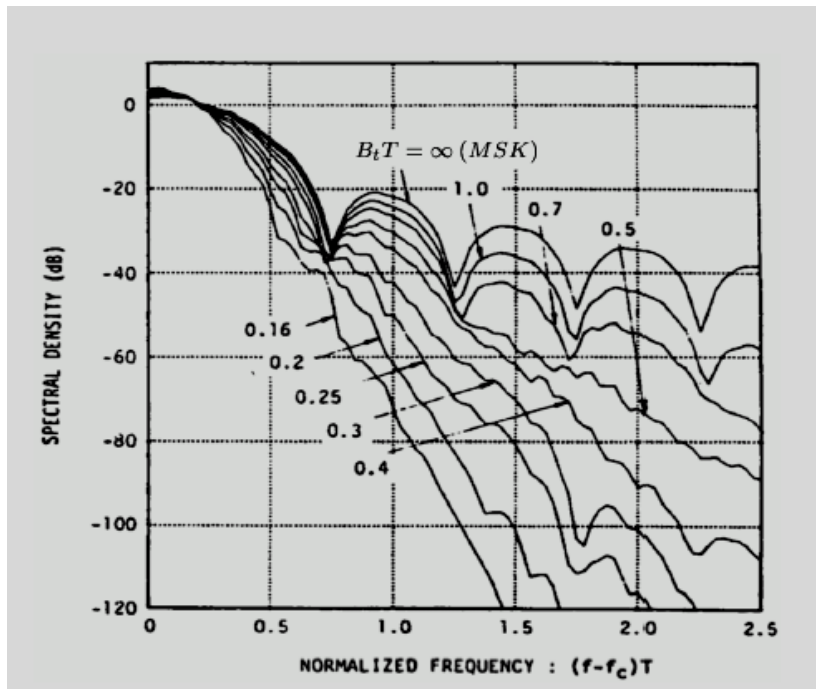- For example, BPSK occupies a relatively large spectrum.



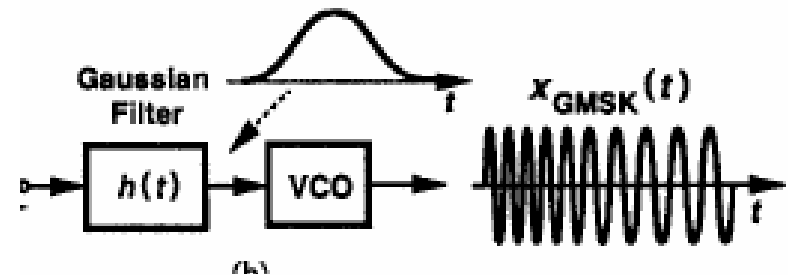GMSK (Gaussian minimum shift keying) makes use of a pulse shaping filter to limit the spectral content.



$$h_G(t) = B_t \frac{2\pi}{\ln 2} e^{-\frac{2\pi^2 B_t^2}{\ln 2} t^2}$$

3 dB bandwidth of Gaussian LPF filter.




Gaussian minimum shift keying widely used


- Examples of standards
 - Digital European Cordless Telephone (DECT)
 - GSM
 - Hyper-lan
 - Frequency hopping part of IEEE 802.11

Key advantages is that GSMK (as an example) allows the use of a non-linear, efficient power amplifier while occupying a moderate part of the spectrum. Negative point is that the pulse shaping causes inter-symbol interference (ISI). Using Matched filters in RX and TX helps to minimize ISI.

QPSK modulation

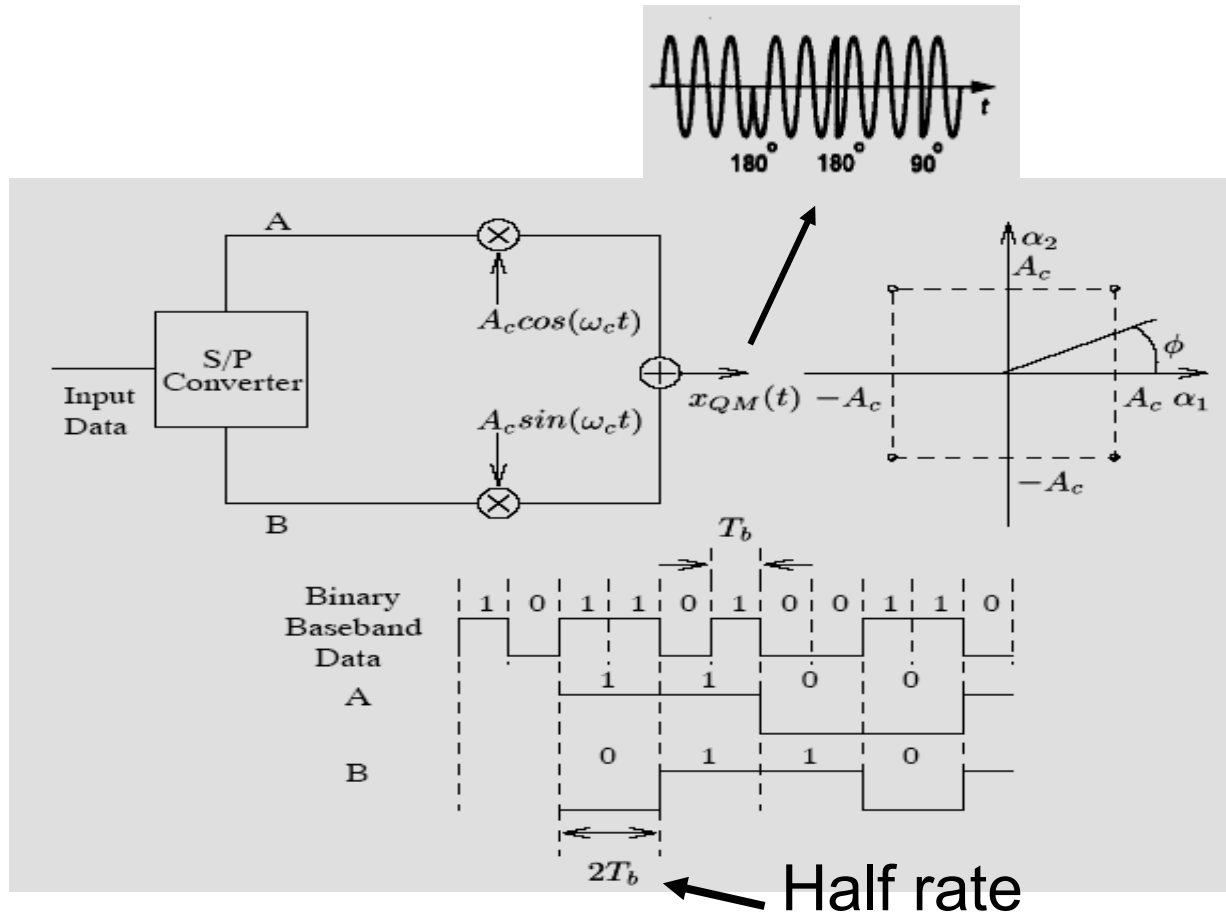

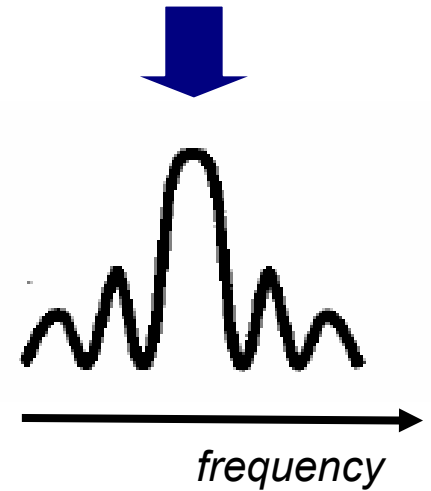
QPSK modulation gives, without pulse shaping a lot of spectral content



Phase changes in QPSK

$$x_{QPSK}(t) = \sqrt{2}A_c \cos\left(\omega_c t + \frac{k\pi}{4}\right)$$


With $k=1,3,5$ and 7

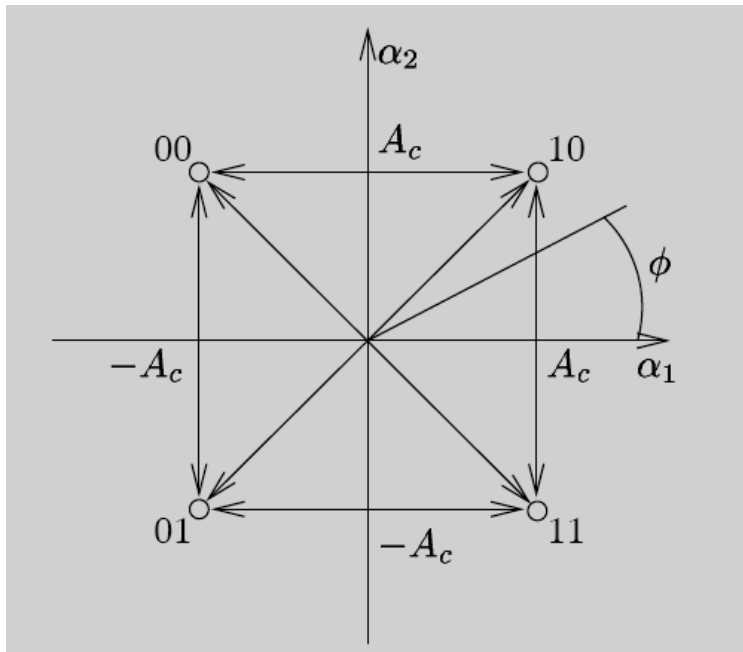


Phase transitions in QPSK signal: worst case 00 to 11 (or vice versa) and 10 to 01 (i.e. π). Abrupt phase-changes implies large spectral content.



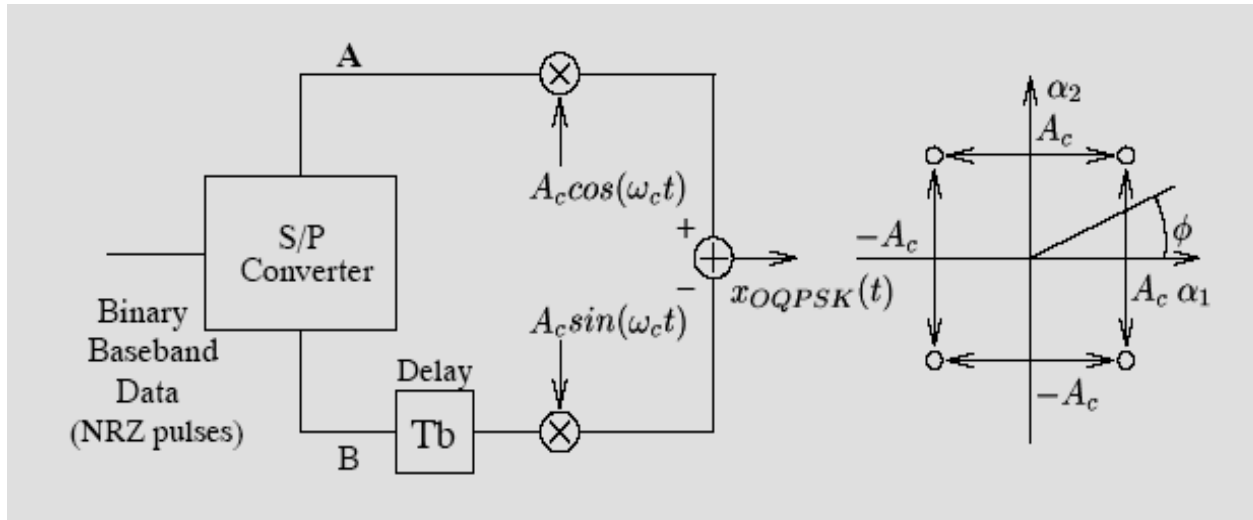Offset QPSK and $\pi/4$ QPSK more spectral efficient due to less abrupt phase changes



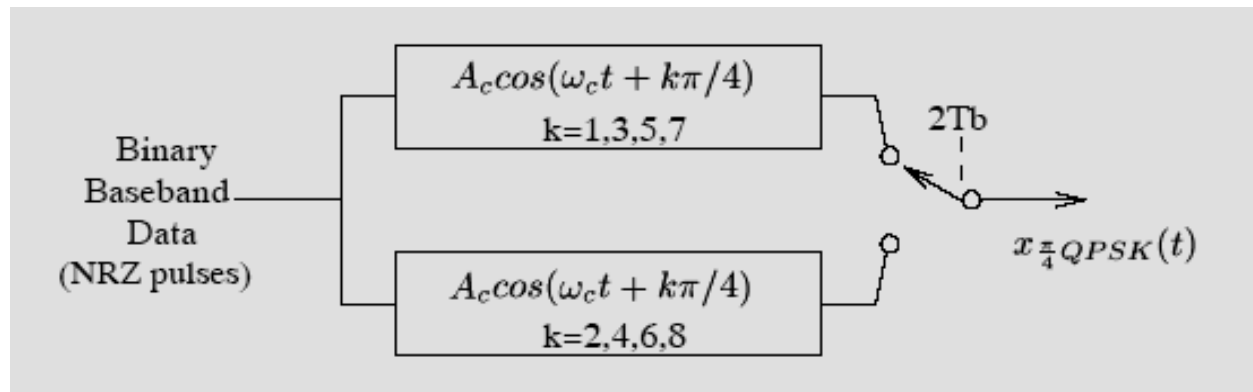
Offset QPSK, the maximum phase change is $\pi/2$.




$\pi/4$ QPSK, the maximum phase change is $3\pi/2$.

QPSK with pulse shaping gives a high spectral efficiency at the cost of a non-constant envelope

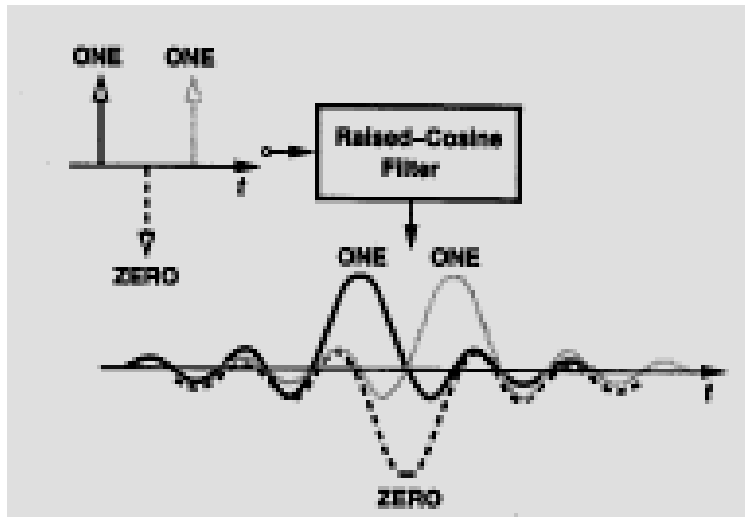- Is used in standards like IS-94, IS95 and the spread-spectrum variant of IEEE 802.11




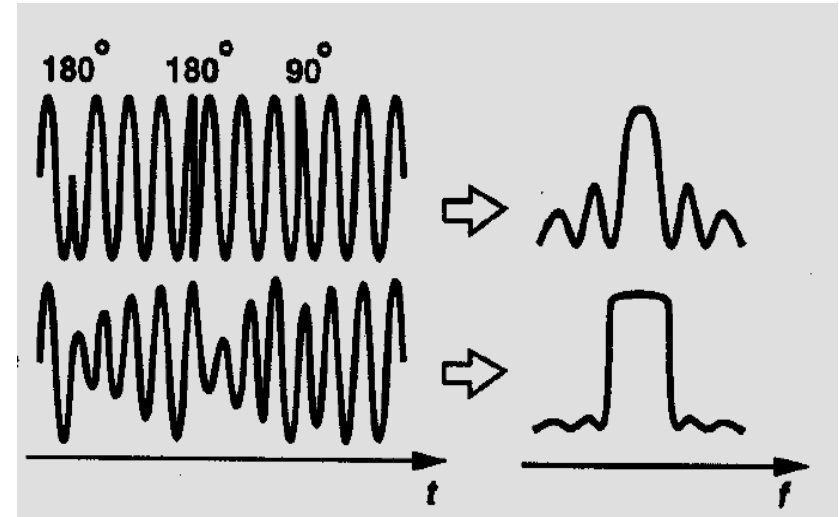Each bit is represented by a sinc-function.



This yields a block-like spectrum in the frequency domain.

Example of baseband/RF interface

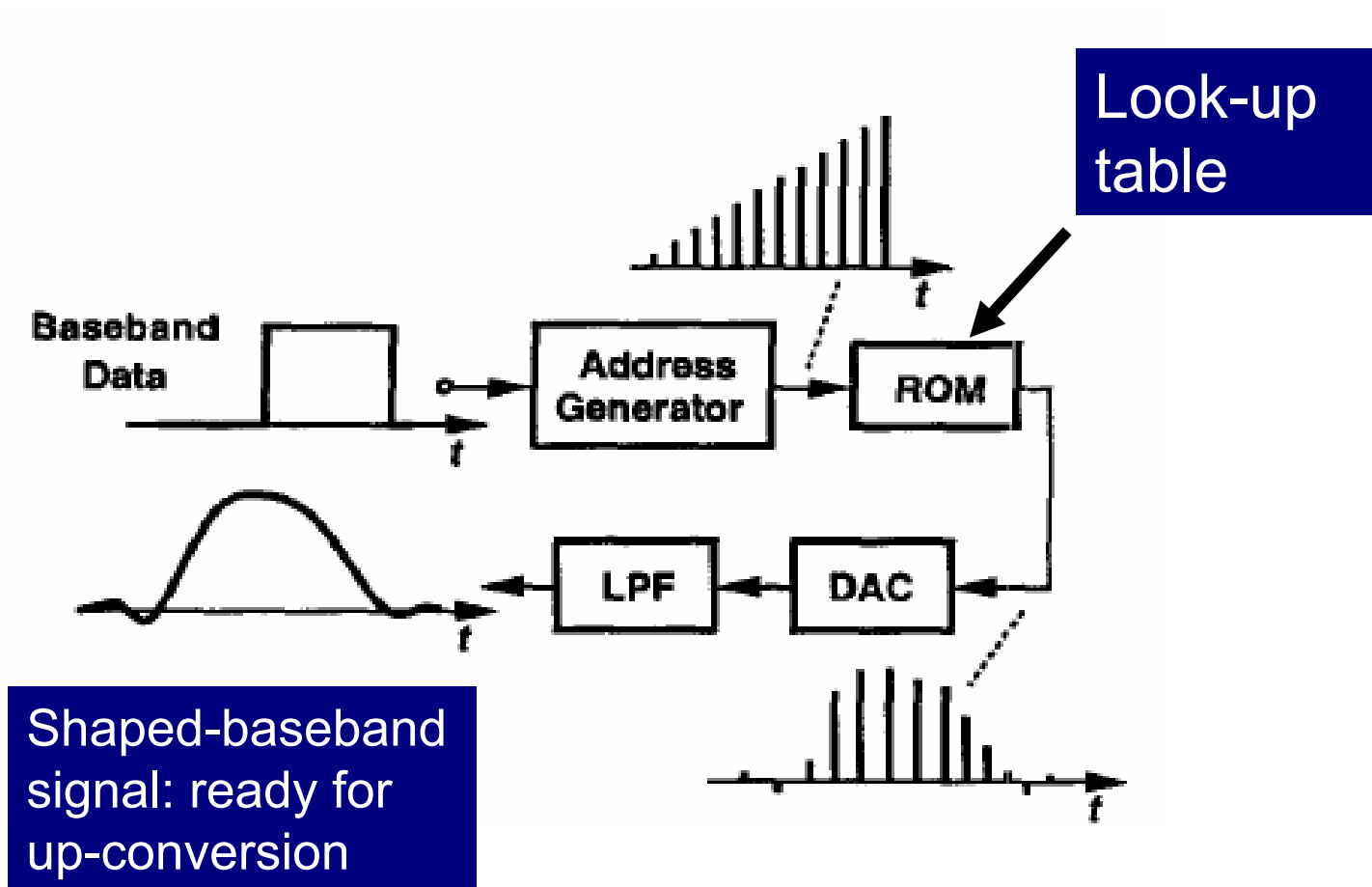





TX specifications

Non-constant envelope modulation & non-linear amplifier gives spectral regrowth

**Variable-Envelope
Signal**



**Nonlinear
PA**

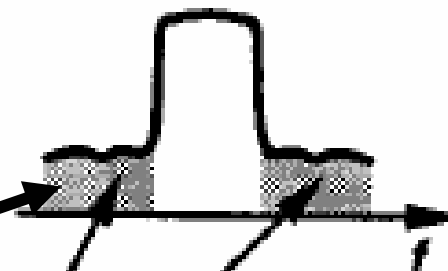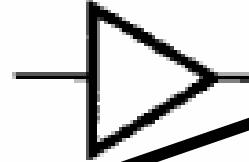


Adjacent Channel Power

ACPR: channel power over adjacent channel power (dBc).


ACPR: Adjacent channel power ratio, sometimes referred to as ACLR, adjacent channel leakage ratio. If the ACPR is too high: an adjacent channel sees a high interfering signal.

TX spectral emission masks

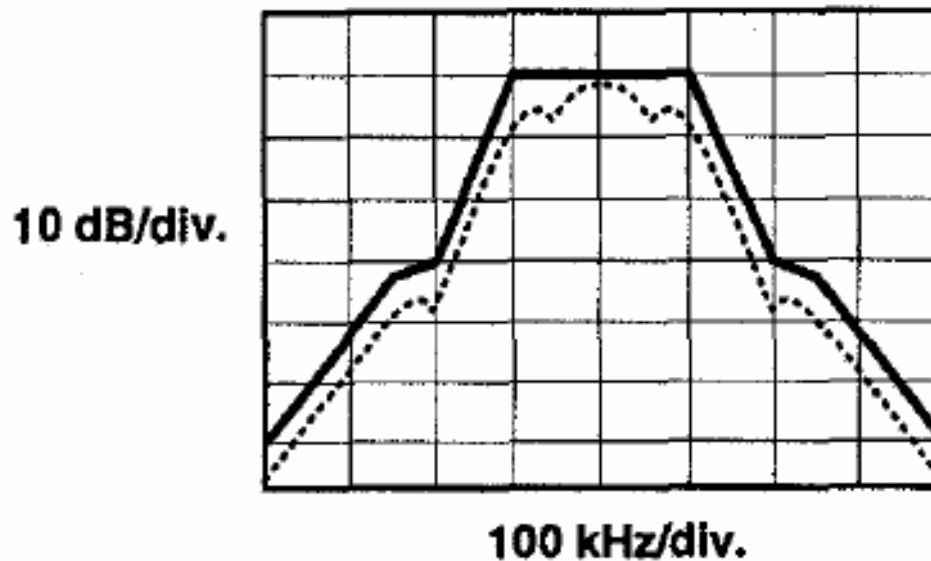

TX spectral content is specified by TX emission masks. This example shows an emission mask for GSM.

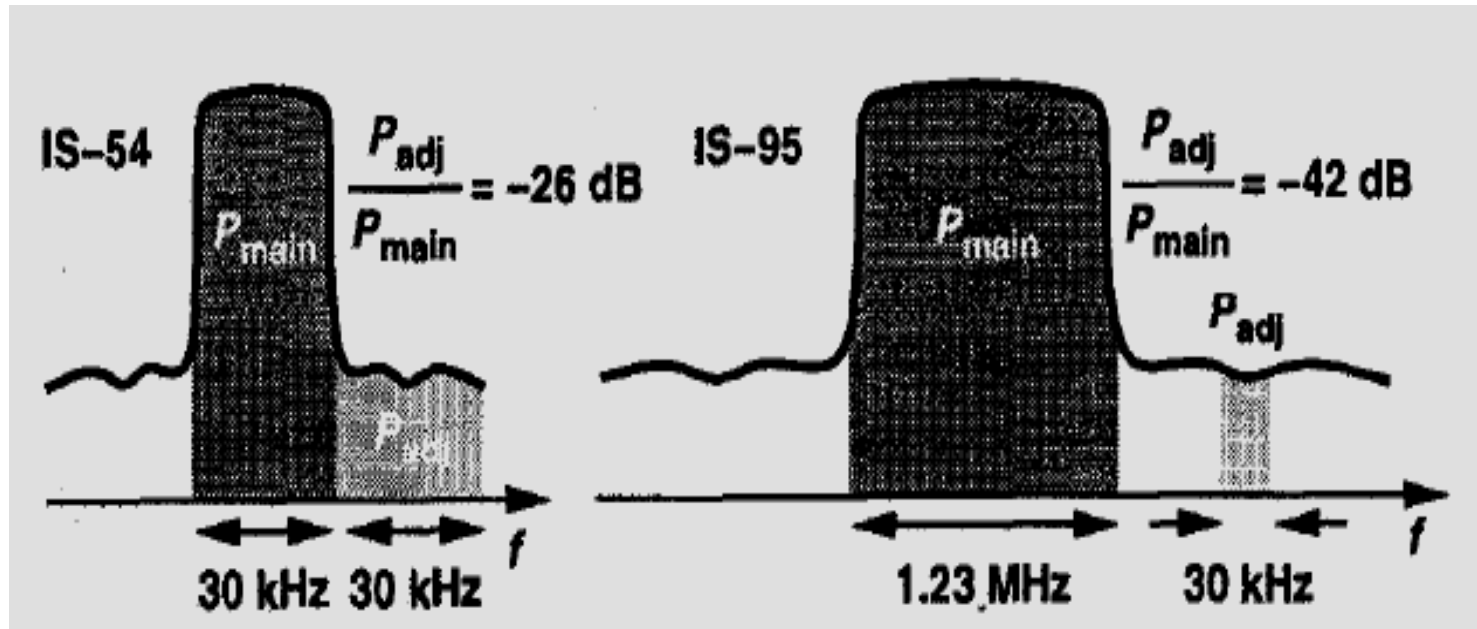In standards with non-constant envelope modulation, ACPR is specified




IS-94 standard (USA)

IS-95 standard (USA)

The ACPR spec. enforces sufficient linearity in up-conversion mixers and power amplifiers of the TX.

Transmitted noise

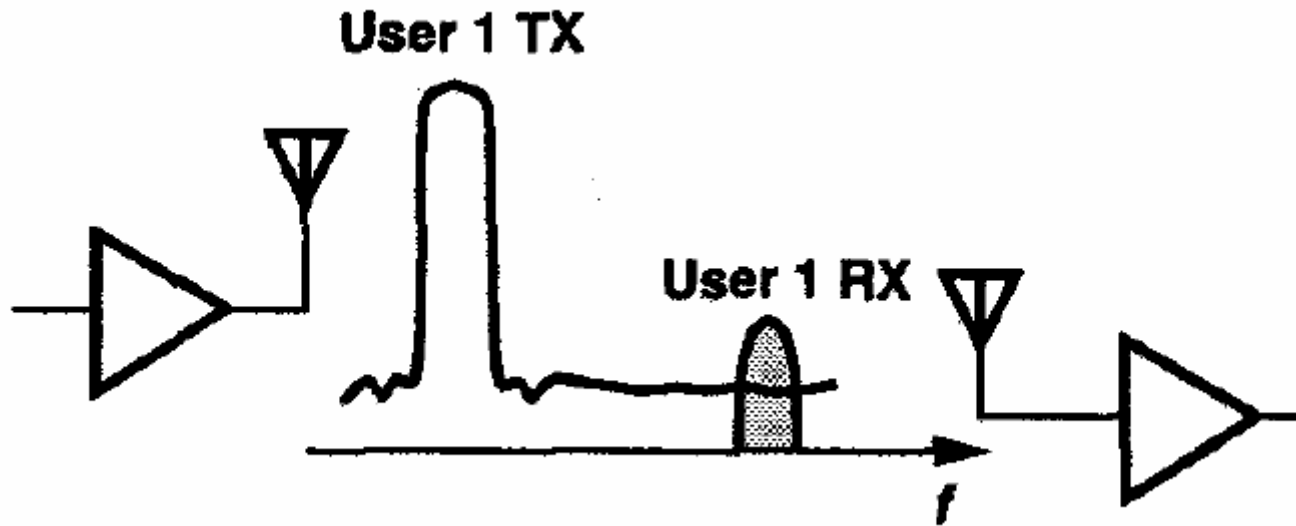


The transmitter noise in the RX band must be very low for a standard like GSM: if two users are near each other the noise in the RX band may corrupt the desired signal.



General RF TX issues

PA-antenna interface

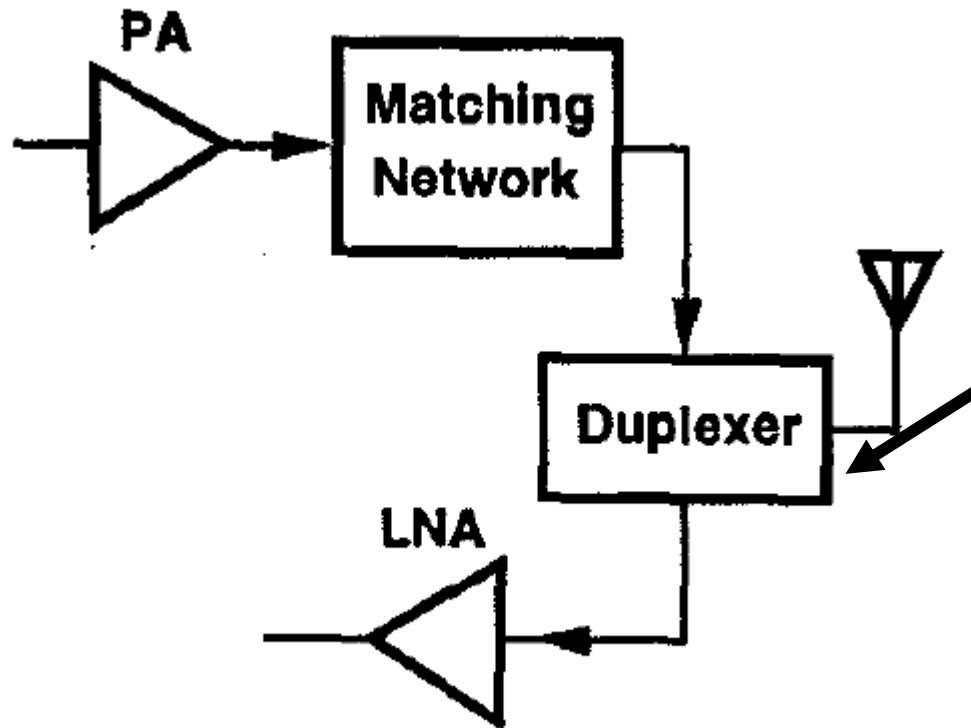


Separates the RX frequency and the TX frequency in case of FDD.

The duplexer is replaced by an RF switch in case of TDD

Duplexer only offers finite isolation

Feed-through from TX to RX path

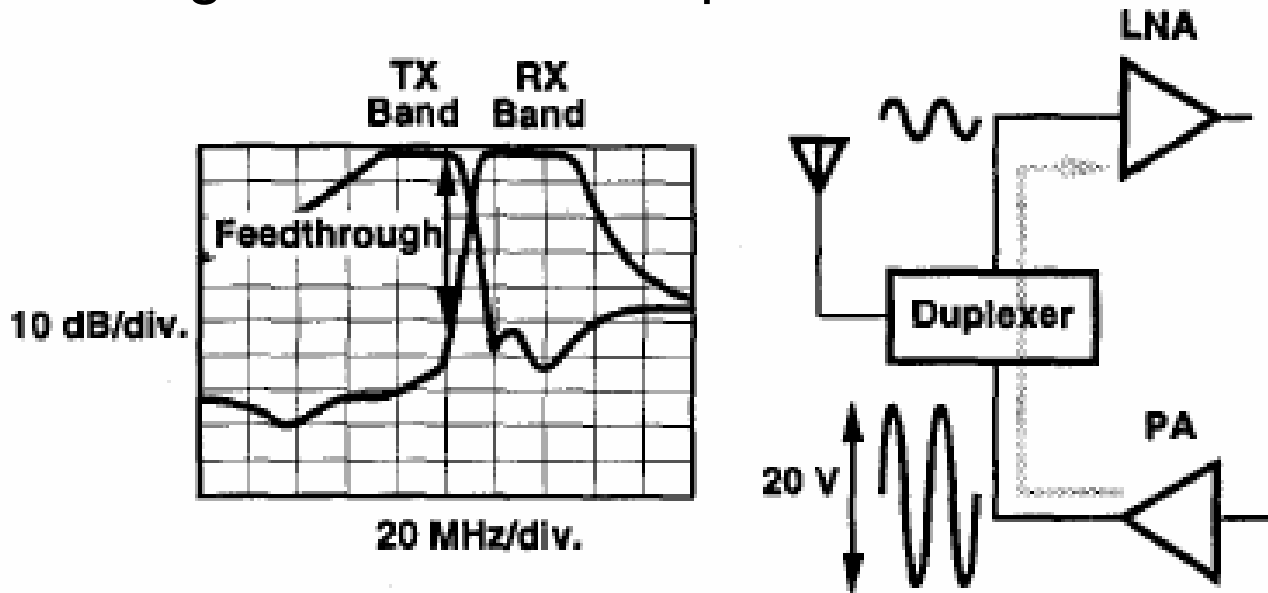


Duplexer may have 2-3 dB insertion loss. Solution (used in GSM) for feed-through is to use non-overlapping time slots for RX and TX.



Direct- conversion transmitters


Direct-conversion TX

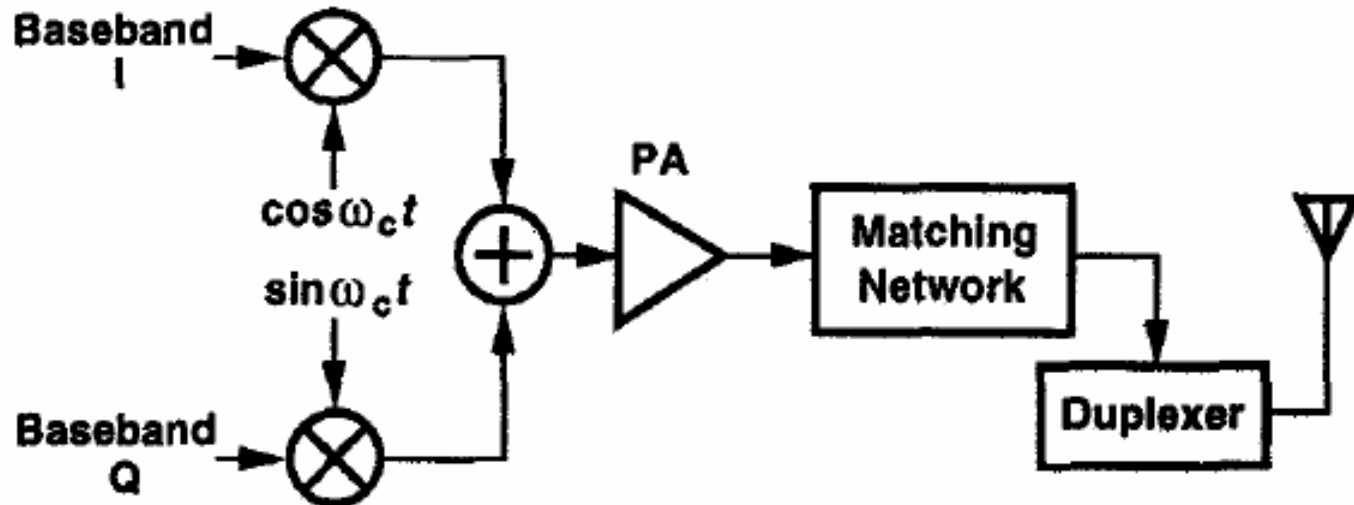

Simple architecture. LO frequency is the same as the output frequency, and up-conversion and quadrature modulation are combined in the same circuitry.

Major disadvantage of direct-conversion TX

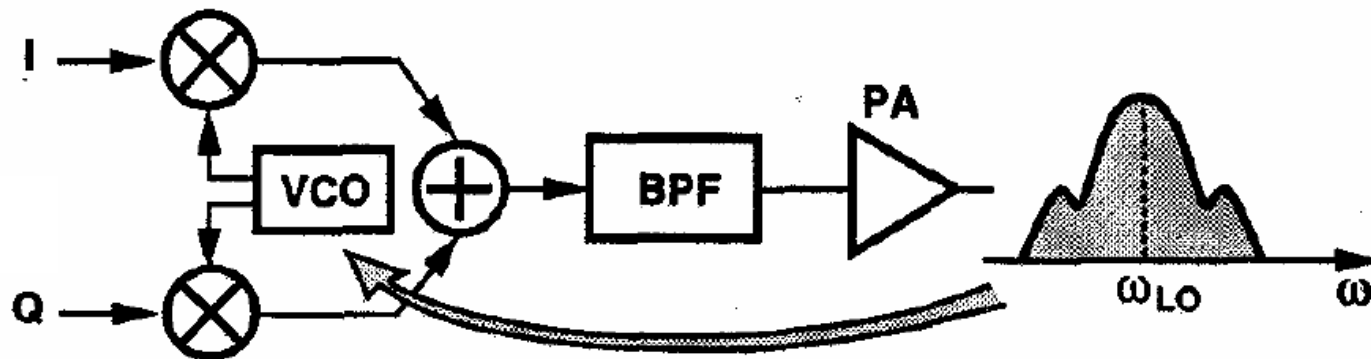Output signal of PA modulates local oscillator: LO pulling




Depending on the level of the injected signal into the oscillator the oscillator may be modulated in a noisy fashion or even “pulled” away from its intended frequency.



Direct-conversion transmitters with offset LO

Direct-conversion with offset LO

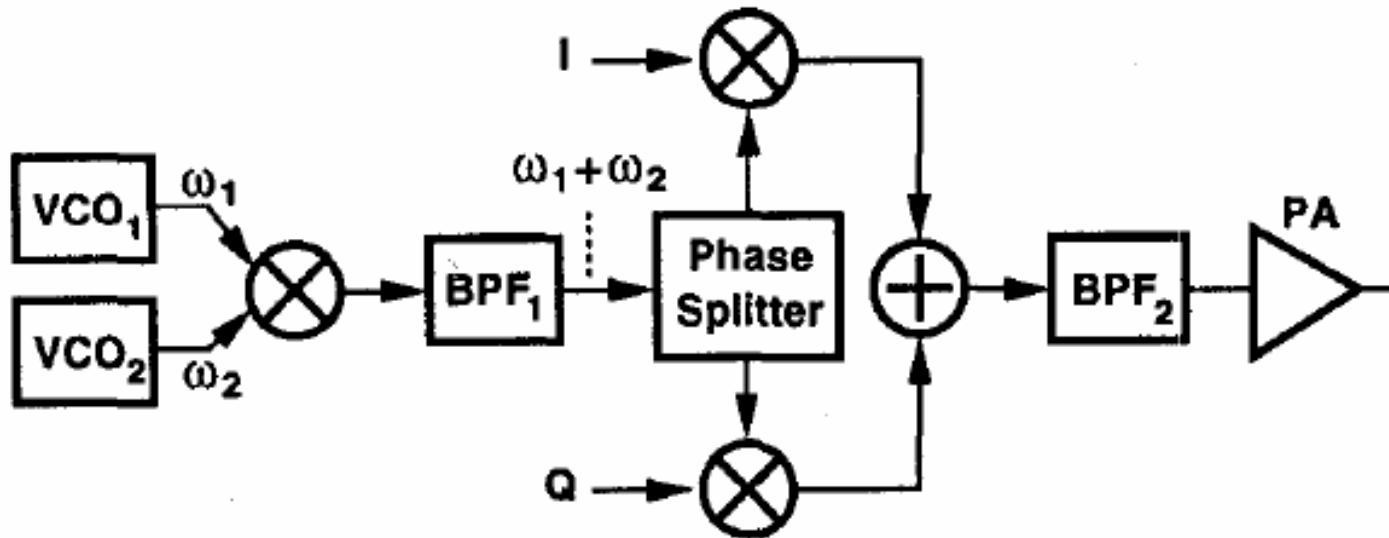


LO frequencies unequal to output frequency, hence pulling problem is alleviated. BPF must be good enough to suppress all unwanted mixing products sufficiently.



Two-step transmitter architecture

Two-step transmitter architecture

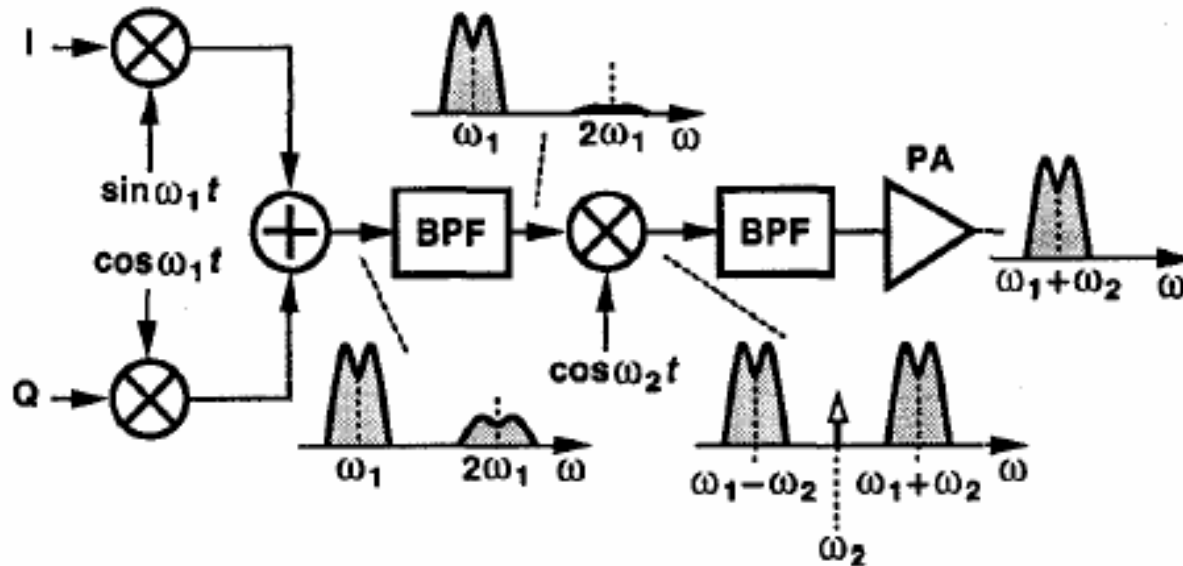- Two up-conversions to remove LO pulling problem




Bandpass filters are difficult to make on-chip and may require 50-60 dB suppression of unwanted conversion product.



Offset-PLL transmitter architecture


Offset PLL architectures

Only for constant envelope systems

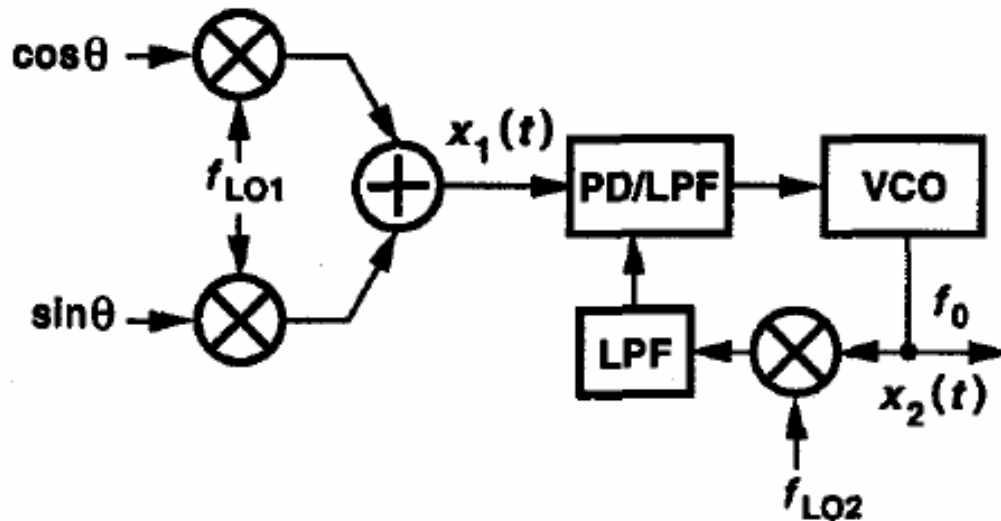


Second LO, f_{LO2} , reduces input frequency of phase detector: $f_0 = f_{LO1} + f_{LO2}$. The architecture is relatively complex but offers excellent out-of-band noise performance.

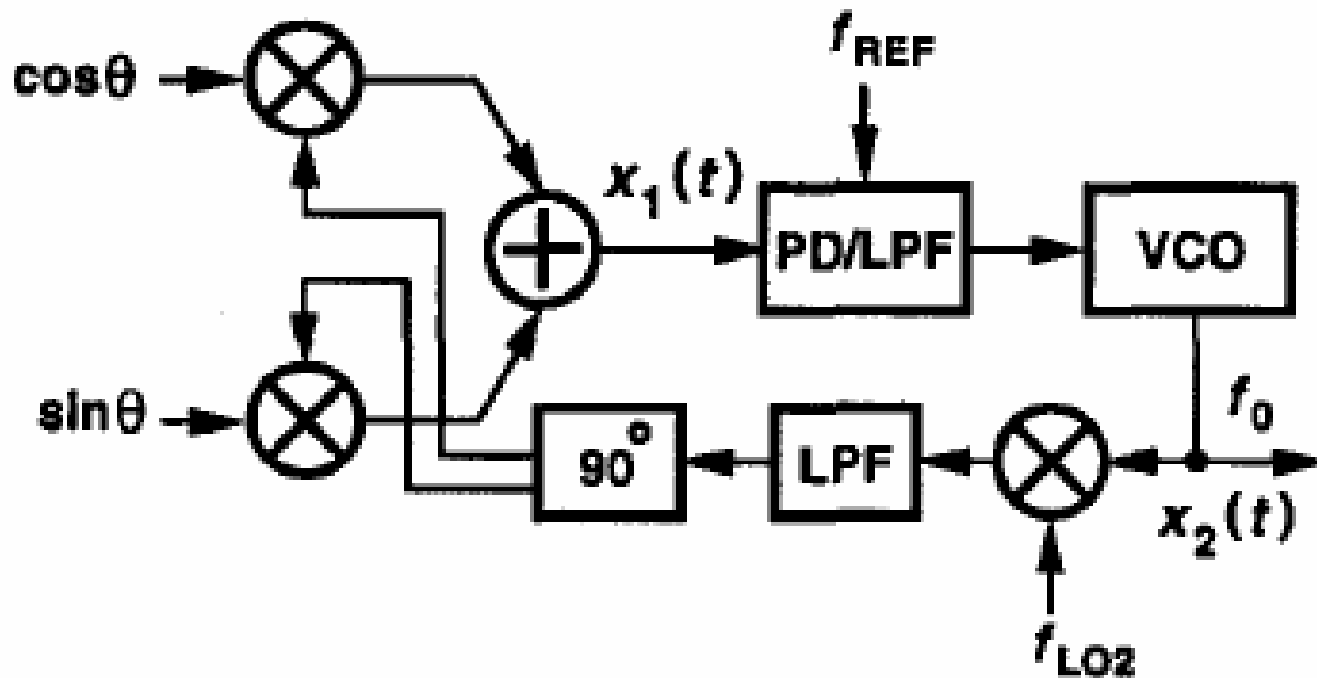Offset PLL architecture can be combined with quadrature up-conversion



The phase lock loop uses a fixed reference frequency f_{ref} , in order to have an accurate translation of $X_1(t)$ to $X_2(t)$.

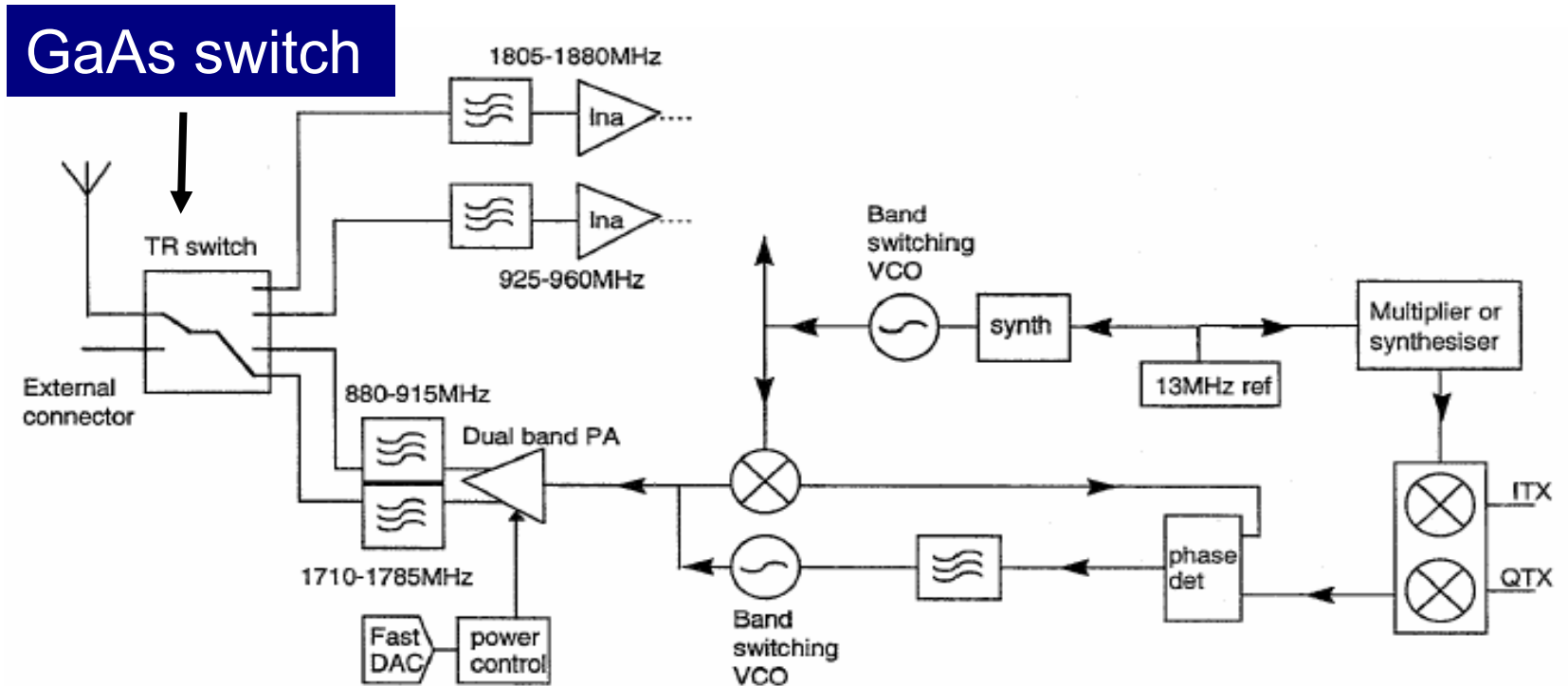Example of dual band PLL offset architecture




Dual-band PA removes the need for a bulky transmit duplex filter.





Digital transmitter concept example

Digital transmitter concept

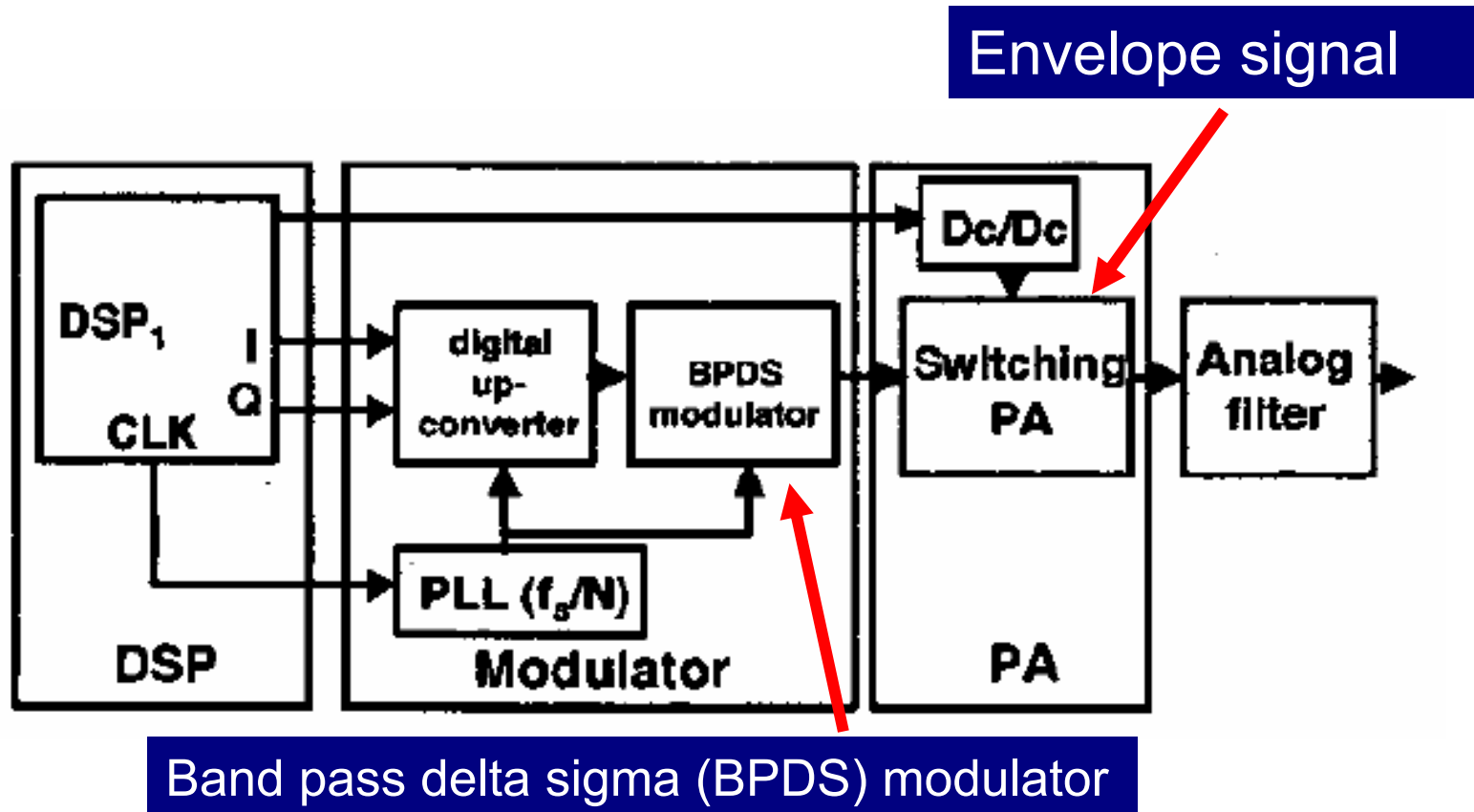

Source:Rode,
Hinrich,Asbeck

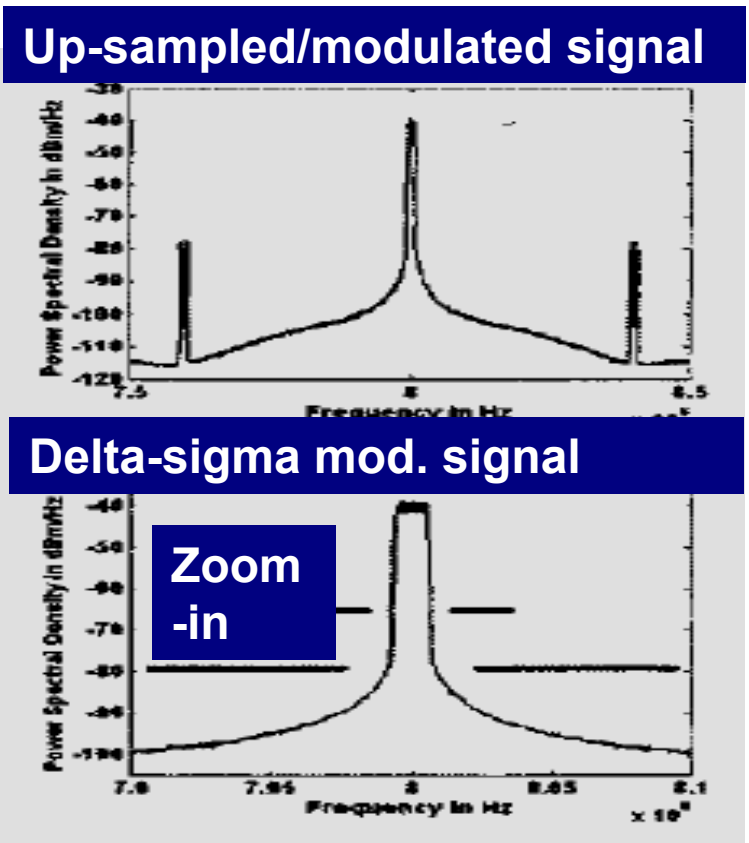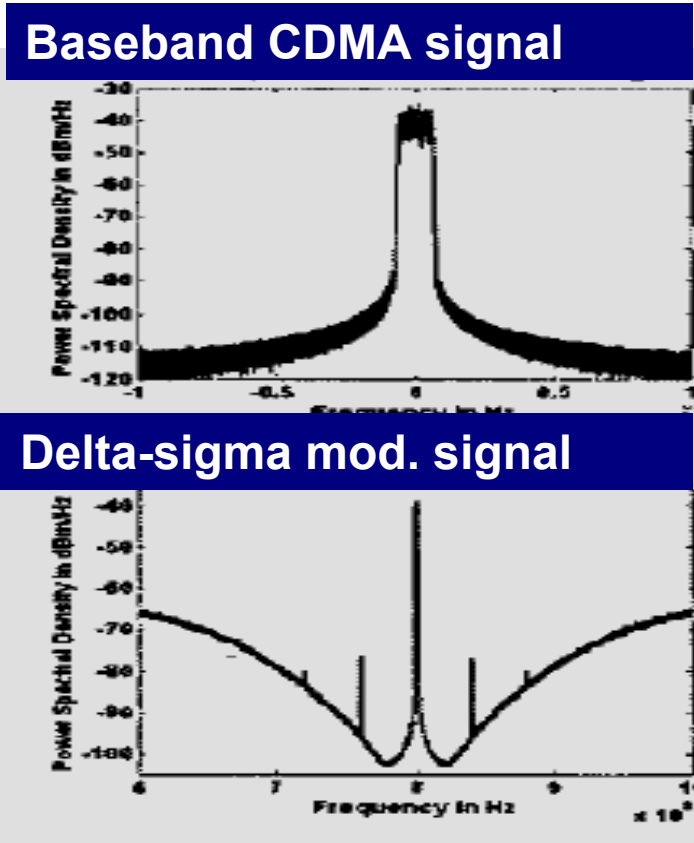Simulated spectra of digital transmitter concept



Source:Rode,
Hinrich,Asbeck