

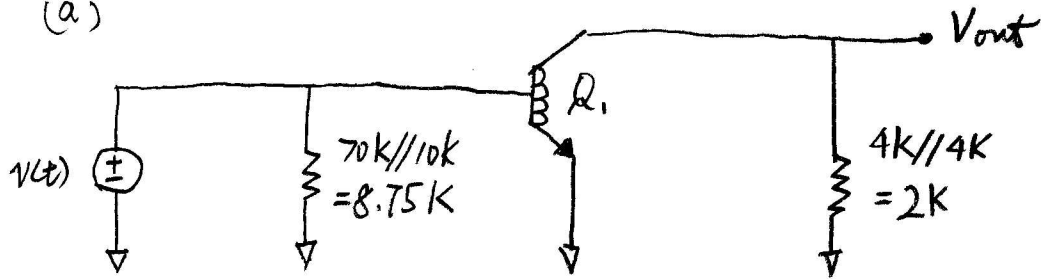


P1 (a)

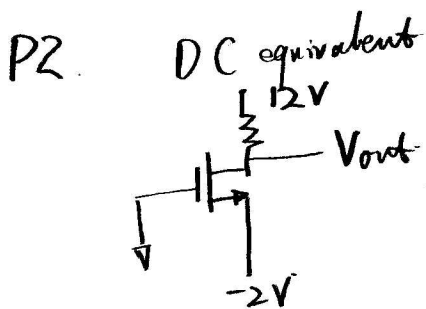

(b)

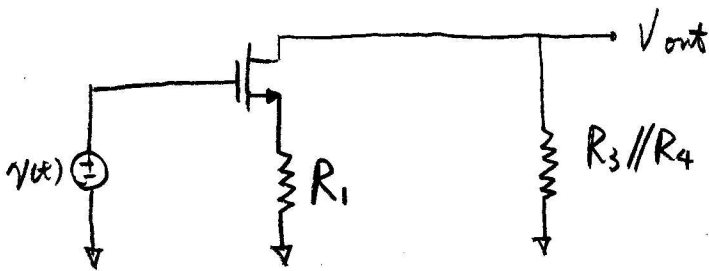

Assume in Saturation.


$$I_{DQ} = \frac{\mu C_{ox} W}{2L} (V_{GSQ} - V_T)^2$$

$$= 0.2 \text{ mA}$$

$$V_{outQ} = 12 - 20\text{k} \cdot 0.2 \text{ mA} = 12 - 4 = 8 \text{ V}$$

Hence $V_{DS} = 8 - (-2) = 10 \text{ V} > V_{GS} - V_T$, assumption holds

Small signal model

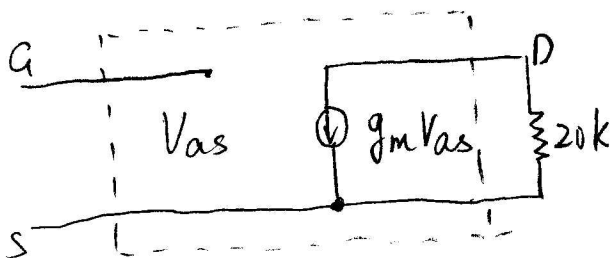


$$g_m = \mu C_{ox} \frac{W}{L} (V_{GSQ} - V_T)$$


$$= 4 \times 10^{-4}$$

$$g_{am} = \frac{V_{out}}{V_{in}} = -g_m \cdot 20\text{k} = -8$$

P3 DC equivalent:

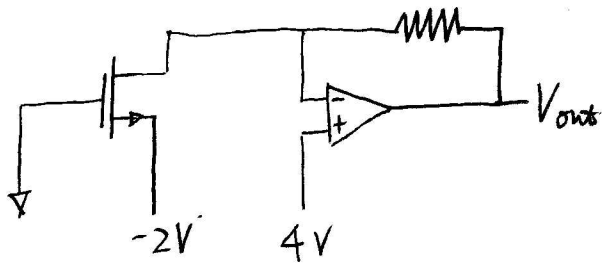

Small Signal:

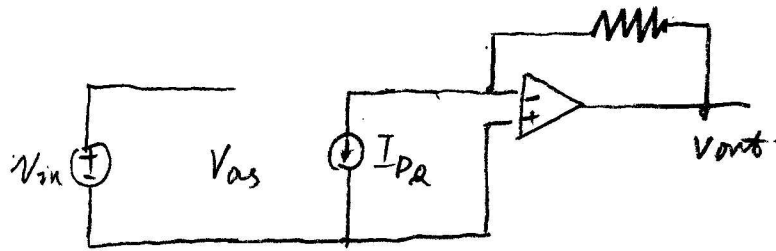

assume saturation

$$I_{DR} = \frac{\mu C_{ox} W}{2L} (V_{asR} - V_T)^2$$

$$= 0.2 \text{ mA}$$

$$V_{out} = 4V + 0.2 \cdot 20k = 8V$$

assumption holds

$$\text{gain} = \frac{I_{DR} \cdot R}{V_{as}} = 8$$

$$\Rightarrow V_{out} = V_{outR} + 8 \cdot V_{in}(t)$$

$$= 8 + 0.8 \sin(2000\pi t)$$

P4. (a) $I_{DR} = \frac{\mu C_{ox} W}{2L} (V_{asR} - V_T)^2 = 1 \text{ mA}$

$$\Rightarrow V_{asR} - V_T = \sqrt{2} \text{ V}$$

$$\therefore R = \frac{\partial V_{DS}}{\partial I_D} = \frac{1}{\left(\frac{\partial I_D}{\partial V_{DS}}\right)} = \frac{1}{g_m}$$

$$g_m = \frac{\partial I_D}{\partial V_{DS}} = \mu C_{ox} \frac{W}{L} (V_{asR} - V_T) = \frac{\mu C_{ox} W}{2L} (V_{as} - V_T)^2 \cdot \frac{2}{V_{as} - V_T} = \frac{2m}{\sqrt{2}}$$

$$\therefore R = \frac{\sqrt{2}}{2} \cdot 1000 \approx 707 \Omega$$

$$(b) \quad R = \frac{V_{CE}}{i_B + i_C} \quad \because V_{CE} = V_{BE} \quad g_{\pi} = \frac{I_{CQ}}{\beta V_T}, \quad g_m = \frac{I_{CQ}}{V_T}$$

$$\Rightarrow R = \frac{V_{BE}}{g_{\pi} V_{BE} + g_m V_{BE}} = \frac{1}{g_{\pi} + g_m} = \frac{1}{\left(\frac{1\text{m}}{100} + 1\text{m}\right)} \approx 990 \Omega$$

(a)

$$P5 \quad i_1 = y_{11} v_1 + y_{12} v_2 \quad \text{where } v_1 = V_1 - V_{1R}$$

$$i_2 = y_{21} v_1 + y_{22} v_2 \quad v_2 = V_2 - V_{2R}$$

$$y_{11} = \left. \frac{\partial I_1}{\partial V_1} \right|_{\substack{V_1=V_{1R} \\ V_2=V_{2R}}} = V_{2R}^3 \quad y_{12} = \left. \frac{\partial I_1}{\partial V_2} \right|_{\substack{V_1=V_{1R} \\ V_2=V_{2R}}} = 3V_{1R}V_{2R}^2$$

$$y_{21} = \left. \frac{\partial I_2}{\partial V_1} \right|_{\substack{V_1=V_{1R} \\ V_2=V_{2R}}} = 0 \quad y_{22} = \left. \frac{\partial I_2}{\partial V_2} \right|_{\substack{V_1=V_{1R} \\ V_2=V_{2R}}} = 0.02 e^{0.2V_{2R}}$$

$$\therefore i_1 = V_{2R}^3 (V_1 - V_{1R}) + 3V_{1R}V_{2R}^2 (V_2 - V_{2R})$$

$$i_2 = 0.02 e^{0.2V_{2R}} (V_2 - V_{2R})$$

$$(b) \quad y_{11} = 1, \quad y_{12} = 15$$

$$y_{21} = 0, \quad y_{22} = 0.02 e^{0.2}$$

$$(c) \quad I_1 = V_{1R}V_{2R}^3 = 5\text{A}, \quad I_2 = 0.1 \cdot e^{0.2V_{2R}} = 0.1 \cdot e^{0.2} \approx 122\text{mA}$$

$$(d) \quad i_1 = 1 \cdot 1 + 15 \cdot 2 = 31\text{mA}$$

$$i_2 = 0.02 e^{0.2 \cdot 0.002} \approx 48.9 \mu\text{A}$$

P6 (a) $V_{GS} = 2V$
 $V_{DS} = 0 < V_{GS} - V_T$ } in triode region

$$R_{FET} = \frac{L}{\mu C_{ox} W (V_{GS} - V_T)} = \frac{1 \mu}{100 \mu \cdot 16 \mu} = 625$$

$$\text{gain} = \frac{V_{out}}{V_{in}} = -1 + \frac{R_F}{R_{FET}} = 1 + \frac{R_F}{625}$$

(b) $V_{DS} < V_{GS} - V_T$ for $1.5V \leq V_{xx} \leq 4$
 So transistor is always in triode region.

as $V_{xx} \uparrow$, $R_{FET} \downarrow$, gain \uparrow .

P7. (a) $V_{DS} < V_{GS} - V_T$... in triode region

$$R_{FET} = \frac{L}{\mu C_{ox} W (V_{GS} - V_T)} = 2500 \Omega$$

$$A(s) = 1 + \frac{R_F // C_F}{R_{FET}} = \frac{s + 5000}{s + 1000}$$

$$\therefore |A(j1000)| = \frac{\sqrt{1000^2 + 5000^2}}{\sqrt{2 \times 1000^2}} = \sqrt{13} \approx 3.61$$

$$\angle A(j1000) = \tan^{-1}\left(\frac{1}{5}\right) - \tan^{-1}(1) = -33.69^\circ$$


$$\therefore V_{out} = |A(j1000)| \cdot 0.02 \sin(1000t - \angle A(j1000))$$


$$= 0.0722 \cdot \sin(1000t - 33.69^\circ)$$

(c) $A(s) = \frac{s + 8000V_{xx} - 7000}{s + 1000}$

poles $s = -1000$

zeros $s = 7000 - 8000V_{xx}$

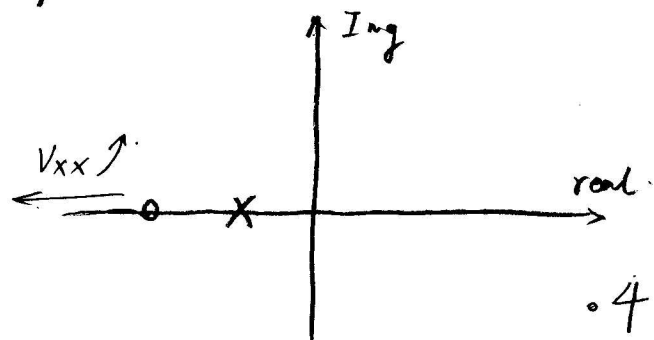

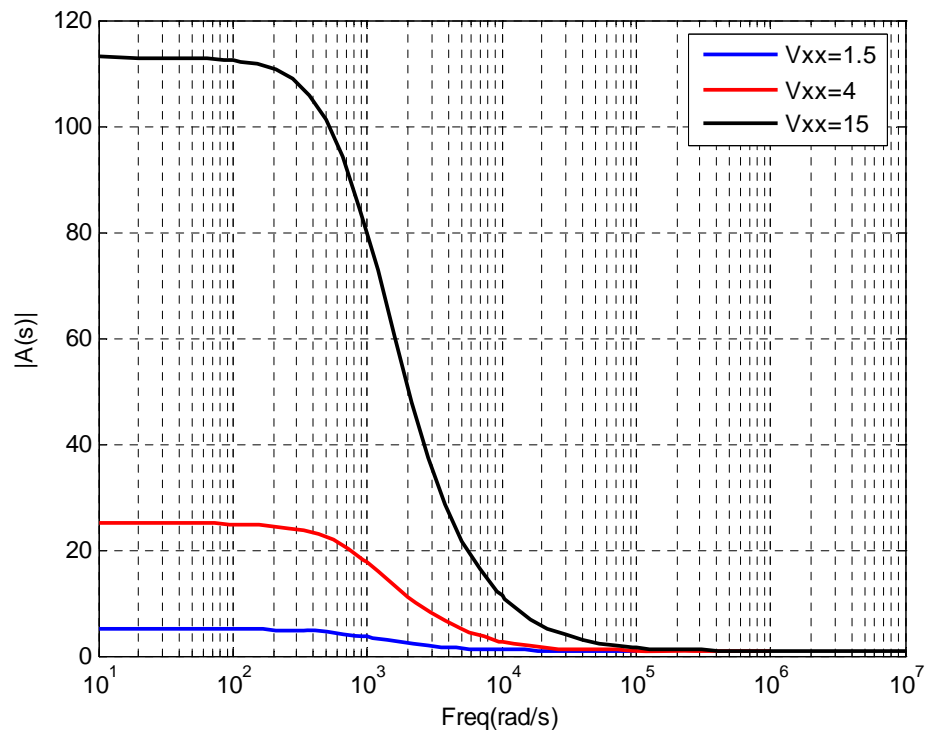

P8 (a) $P_R = \frac{KAR}{1+R^2} \Big|_{R=1} = \frac{KA}{2}$


(b) $P = \frac{KA(H + 0.1 \sin \omega t)}{1 + (1 + 0.1 \sin \omega t)^2}$

$\omega = \frac{2\pi}{30 \text{ year}}$


(c) $\frac{\partial P}{\partial R} \Big|_{R=1} = \frac{KA(HR^2) - KAR \cdot 2R}{(1+R^2)^2} = \frac{KA(R-1)^2}{(1+R^2)^2} = 0$

$P = P_a + \frac{\partial P}{\partial R} \cdot (R - R_a) = \frac{KA}{2}$

(d) the gain obtained in c is zero, while the gain in b is not zero, they are close, though. This is due to the fact that the small signal model is based on first-order Taylor expansion only.

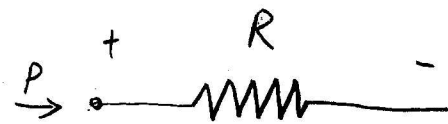(e) 
 $\frac{\partial P}{\partial R} = \frac{KA(R-1)^2}{(1+R)^2}$



P9. DC equivalent

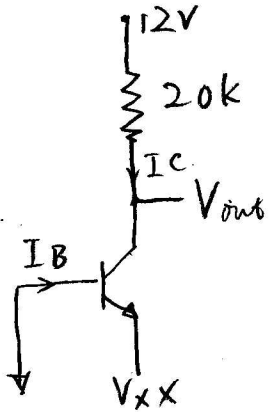

$$V_{out} = 12V - I_{CQ} \cdot 20k$$

$$= 12 - 4 = 8V$$

Small Signal

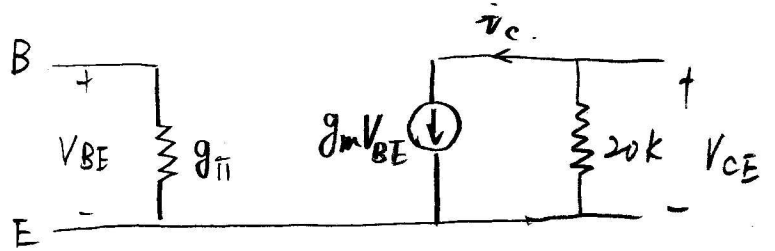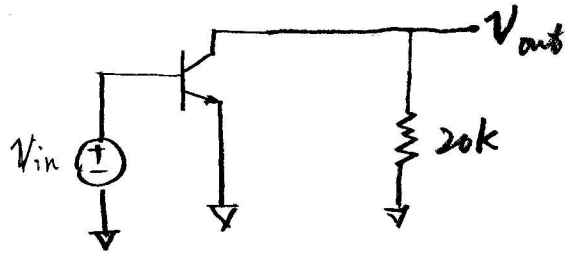

$$\frac{V_{out}}{V_{in}} = \frac{-i_c \cdot R}{V_{BE}} = -g_m R$$

$$= -\frac{I_{CQ}}{V_T} \cdot R$$

$$= -160$$