

## EE 230


### HW2 Solutions

#### Problem 1

1. A square wave can be represented a sum of an infinite number of sine waves as follows:

$$x_{square} = \left(\frac{4}{\pi}\right) \sum_{k=1}^{\infty} \frac{\sin 2\pi f t 2k-1}{2k-1}$$

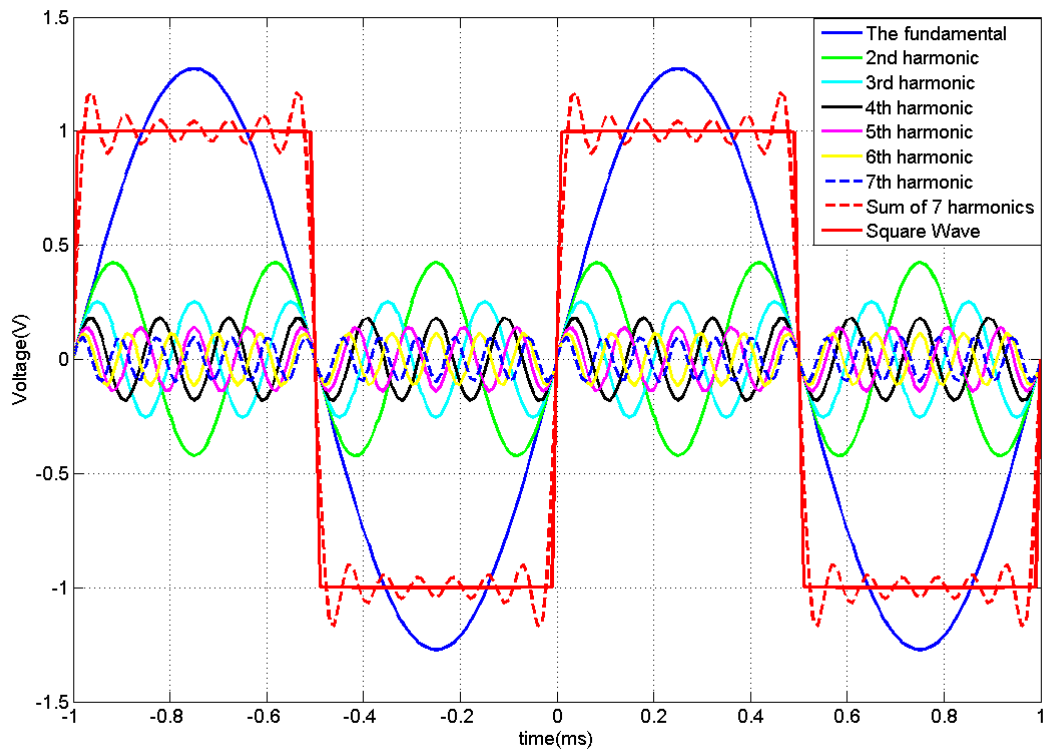- a. When  $K=1$ , we obtain the fundamental
- b. When  $K=2, \dots, 7$ , we obtain the 2<sup>nd</sup>, 3<sup>rd</sup>,  $\dots$ , 7<sup>th</sup> harmonics respectively
- c. Sum up the 1<sup>st</sup> 7 harmonics



#### Matlab code for problem 1:

```
clear all
close all

f=1000;           % frequency
t=-1e-3:1e-5:1e-3; % time

x_out=0;
for i=1:1000
    x = (4/pi)*sin((2*i-1)*2*pi*f.*t)/(2*i-1); % One harmonic at a time
```

```


x_out = x_out + x; % Add up the harmonics
if i==1
    plot(t*1e3,x,'b','linewidth',2.5),
    xlabel('time(ms)','fontsize',14),ylabel('Voltage(V)','fontsize',14)
    hold on
end
if i==2
    plot(t*1e3,x,'g','linewidth',2.5),
    xlabel('time(ms)','fontsize',14),ylabel('Voltage(V)','fontsize',14)
    hold on
end
if i==3
    plot(t*1e3,x,'c','linewidth',2.5),
    xlabel('time(ms)','fontsize',14),ylabel('Voltage(V)','fontsize',14)
    hold on
end
if i==4
    plot(t*1e3,x,'k','linewidth',2.5),
    xlabel('time(ms)','fontsize',14),ylabel('Voltage(V)','fontsize',14)
    hold on
end
if i==5
    plot(t*1e3,x,'m','linewidth',2.5),
    xlabel('time(ms)','fontsize',14),ylabel('Voltage(V)','fontsize',14)
    hold on
end
if i==6
    plot(t*1e3,x,'y','linewidth',2.5),
    xlabel('time(ms)','fontsize',14),ylabel('Voltage(V)','fontsize',14)
    hold on
end
if i==7
    plot(t*1e3,x,'b--','linewidth',2.5),
    xlabel('time(ms)','fontsize',14),ylabel('Voltage(V)','fontsize',14)
    hold on
    plot(t*1e3,x_out,'r--','linewidth',2.5),
    hold on
end
if i==1000
    plot(t*1e3,x_out,'r','linewidth',2.5),
    xlabel('time(ms)','fontsize',14),ylabel('Voltage(V)','fontsize',14)
    hold on
end
end
set(gcf,'CurrentAxes'),'FontSize',14)
grid on
legend('The fundamental','2nd harmonic','3rd harmonic','4th harmonic','5th
harmonic','6th harmonic','7th harmonic','Sum of 7 harmonics','Square Wave')

```

## Problem 2

- THD = 0.02%
- Operating Range = 20Hz-40KHz
- Gain deviation = the gain is flat to within -3dB. That means they are only guaranteeing the gain to be within 3dB over the entire frequency range

## Problem 3

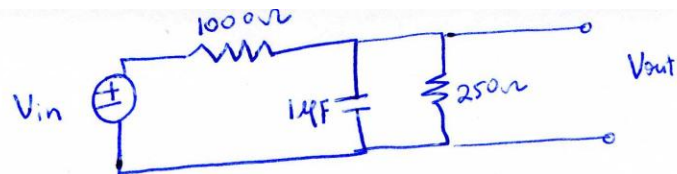

$$a) \quad Z_1 = R_1 \quad Z_2 = R_2 \quad ; \quad Z_3 = \frac{1}{j\omega C}$$

$$Z = Z_2 // Z_3 = \frac{Z_2 Z_3}{Z_2 + Z_3} = \frac{R_2 / j\omega C}{R_2 + \frac{1}{j\omega C}} = \frac{R_2}{1 + j\omega R_2 C}$$

$$\Rightarrow V_{out} = V_{in} \cdot \frac{Z}{Z_1 + Z} \Rightarrow \frac{V_{out}}{V_{in}} = \frac{Z}{R_1 + Z} = \frac{R_2 / (1 + j\omega R_2 C)}{R_1 + R_2 / (1 + j\omega R_2 C)}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{R_2}{(1 + j\omega R_2 C)R_1 + R_2} = \frac{R_2}{(R_1 + R_2) + j\omega R_1 R_2 C}$$

$$T(j\omega) = \frac{V_{out}}{V_{in}} = \frac{250}{1250 + 0.25j\omega}$$

$$b) \quad T(s) = \frac{250}{1250 + 0.25s} \quad s = j\omega$$

$$c) \quad V_{in} = 0.5 \sin 1000t \quad \Rightarrow \quad \omega = 1000 \text{ rad/s}$$


$$\text{at } \omega = 1000 \text{ rad/s, we have } T(j\omega) = \frac{250}{1250 + j250} = \frac{1}{5 + j} = \frac{5 - j}{(5 + j)(5 - j)} = \frac{5 - j}{25 + 1}$$

$$\Rightarrow T(j\omega)|_{\omega=1000} = \frac{5}{26} - \frac{1}{26}j = 0.196 \angle -0.196 \text{ rad}$$

$$V_{out}(t) = 0.5 \times 0.196 \times \sin(1000t - 0.196)$$

$$V_{out}(t) = 0.098 \sin(1000t - 0.196)$$

Problem 4

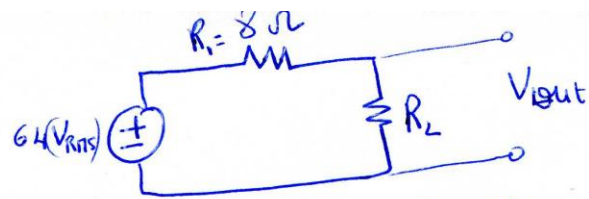

a) \*  $R_L = 4 \Omega \Rightarrow V_{out} = \frac{4 \times 64}{4 + 8} = \left(\frac{128}{3}\right) V$

Power =  $P_L = \frac{V_{out}^2}{R_L} = \frac{(128/3)^2}{4} = \boxed{113.78 W}$

\*  $R_L = 8 \Omega \Rightarrow P_L = \frac{(8 \times 64)^2}{8^3} = \boxed{128 W}$


\*  $R_L = 1000 \Omega \Rightarrow P_L = \frac{(64 \times 1000)^2}{1000^3} = \boxed{4.03 W}$

b)  $P_L = \frac{V_{out}^2}{R_L} = \frac{(R_L V_{in})^2}{R_L (R_1 + R_L)^2} \quad V_{in} ?$

$\Rightarrow P_L \cdot R_L = \left(\frac{R_L}{R_1 + R_L}\right)^2 V_{in}^2$

$\Rightarrow V_{in} = \sqrt{\frac{P_L \cdot R_L}{\left(\frac{R_L}{R_1 + R_L}\right)}} = \sqrt{\frac{128 \times 1000}{\left(\frac{1000}{1008}\right)}} = \boxed{360 V}$

## Problem 5

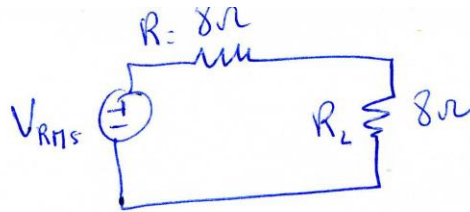

Assume: 100W at  $8\Omega$  load

$$\Rightarrow P_L = \frac{V_L^2}{R_L} = \frac{(V_{RMS} R_L)}{R_L + R}^2$$

$$\Rightarrow 100 = \frac{V_{RMS}^2 \left(\frac{8}{10}\right)^2}{8}$$

$$\Rightarrow V_{RMS} = \sqrt{\frac{100 \times 8}{(0.5)^2}} = 56.56V$$

$$V_p = \text{Voltage (peak)} = \sqrt{2} \cdot V_{RMS} = \sqrt{2} \times 56.56V = 80V$$

$$V_p = 80V$$

Now 100W at  $1000\Omega$  load

$$V_p = V_{RMS} \cdot \sqrt{2} = \sqrt{2} \cdot \sqrt{\frac{100 \times 1000}{\left(\frac{1000}{1008}\right)}} = 448.9V$$

- To achieve the same power at  $1000\Omega$  load, the power amplifier will require a very high voltage
- AC outlet doesn't provide this voltage
- This high voltage is hazardous.

## Problem 6

### Problem 6

$$T(s) = 20 \frac{s+1}{s^2+5s+6}$$

$$a) T(j\omega) = 20 \frac{j\omega+1}{(j\omega)^2+5j\omega+6} = \frac{20+20j\omega}{(6-\omega^2)+5j\omega}$$

$$|T(j\omega)| = \frac{\sqrt{20^2+20^2\omega^2}}{\sqrt{(6-\omega^2)^2+25\omega^2}} = \frac{20\sqrt{1+\omega^2}}{\sqrt{\omega^4+13\omega^2+36}}$$

b) The maximum gain is 4.38 at  $\omega = 2$  rad

c) System is linear  $\Rightarrow$  THD = 0

$$d) T_1(j3) = 20 \frac{j3+1}{15j-3} = 4.13 \angle -0.519$$

$$T_2(j6) = 20 \frac{j6+1}{30j-30} = 2.86 \angle -0.951$$

$$V_{out1} = 0.4 \times 4.13 \sin(3t - 0.519) = 1.654 \sin(3t - 0.519)$$

$$V_{out2} = 0.2 \times 2.86 \sin(6t - 0.951) = 0.57 \sin(6t - 0.951)$$

$$P = \frac{(1.654)^2 + (0.57)^2}{2} = 1.532 \text{ W}$$

```
clear all
close all
w=0:0.01:20;
```

```
T = (20*sqrt(1+w.^2))./sqrt(w.^4 + 13*w.^2 + 36);
plot(w,T,'linewidth',2.5)
grid on
xlabel('Angular
frequency (rad)', 'fontsize',14), ylabel('Magnitude', 'fontsize',14)
set(get(gcf, 'CurrentAxes'), 'FontSize',14)
```

