

HW 3 Solutions
EE 230


Problem 1

a) 1 pole at $s = -6 \Rightarrow T(s) = \frac{A}{s+6}$

DC gain of 9 $\Rightarrow T(j\omega=0) = T(s) = 9 \Rightarrow T(0) = \frac{A}{6} = 9 \Rightarrow A = 54$

Therefore $T(s) = \frac{54}{s+6}$

b) Step response to $5u(t)$

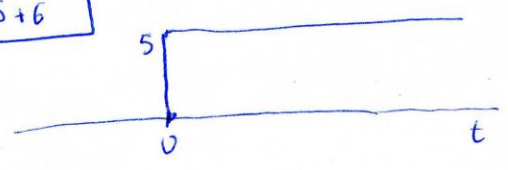

$x(t) = 5u(t) \Rightarrow X_{in}(s) = \frac{5}{s}$

$X_{out}(s) = X_{in}(s) \cdot T(s) = \frac{5}{s} \cdot \frac{54}{s+6} = \frac{270}{s(s+6)} = \frac{A}{s} + \frac{B}{s+6}$

$\begin{cases} As + 6A + Bs = 270 \\ \quad \quad \quad \downarrow \\ \quad \quad \quad As + Bs = 0 \end{cases}$

$\Rightarrow \begin{cases} 6A = 270 \\ A = -B \end{cases} \Rightarrow \begin{cases} A = 45 \\ B = -45 \end{cases}$

\Rightarrow $X_{out}(s) = \frac{45}{s} - \frac{45}{s+6}$

Take inverse Laplace Transform:

$X_{out}(t) = \mathcal{L}^{-1}\left(\frac{45}{s} - \frac{45}{s+6}\right) = \mathcal{L}^{-1}\left(\frac{45}{s}\right) - \mathcal{L}^{-1}\left(\frac{45}{s+6}\right)$

$X_{out}(t) = 45u(t) - 45e^{-6t}u(t)$

Problem 2


$$T(s) = 20 \frac{s+2}{s^2+3s+9}$$

$$\begin{aligned} \text{a) } s^2+3s+9 &\Rightarrow P_1 = \frac{-3 - \sqrt{3^2 - 4 \cdot 9 \cdot 1}}{2 \cdot 1} & ; P_2 = \frac{-3 + \sqrt{3^2 - 4 \cdot 9 \cdot 1}}{2} \\ &\Rightarrow P_1 = -\frac{3}{2} - \frac{\sqrt{-27}}{2} & ; P_2 = -\frac{3}{2} + \frac{\sqrt{-27}}{2} \\ &\Rightarrow P_1 = -\frac{3}{2} - \frac{j3\sqrt{3}}{2} & ; P_2 = -\frac{3}{2} + \frac{j3\sqrt{3}}{2} \end{aligned}$$

$$\Rightarrow T(s) = 20 \frac{(s+2)}{\left(s + \frac{3}{2} + j\frac{3\sqrt{3}}{2}\right)\left(s + \frac{3}{2} - j\frac{3\sqrt{3}}{2}\right)}$$

$$\begin{array}{l} \text{Zero at } s = -2 \\ \text{Poles at } s = -\frac{3}{2} - j\frac{3\sqrt{3}}{2} \text{ and } s = -\frac{3}{2} + j\frac{3\sqrt{3}}{2} \end{array}$$

b)

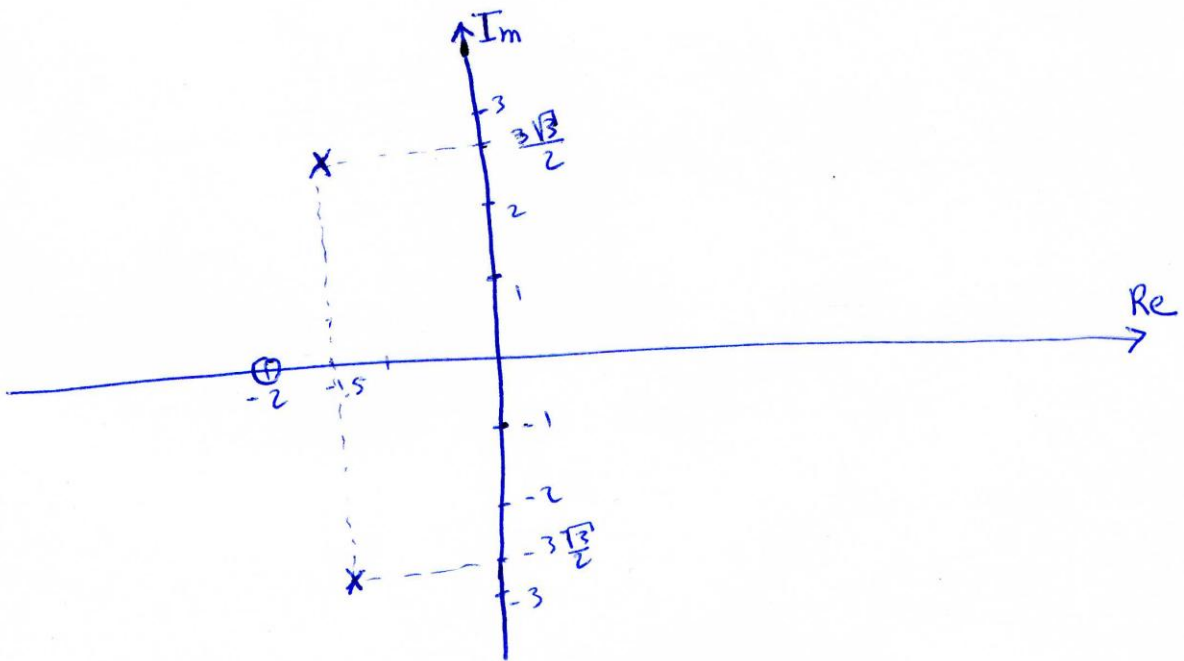

Problem 3

$$a) T(s) = 10 \frac{(s+1)(s-1)}{(s+8)(s-2+2j)(s-2-2j)}$$

Poles at $s = 2 - 2j$ and $s = 2 + 2j \Rightarrow$ **unstable**
These two poles are in the Right half of the s plane

$$b) T(s) = 10 \frac{s^2 + 3s + 18}{s^3 + s^2 + s + 6}$$

$$s^3 + s^2 + s + 6 = (s+2)(s^2 - s + 3) = (s+2) \left[s - \left(\frac{1+j\sqrt{11}}{2} \right) \right] \left[s - \left(\frac{1-j\sqrt{11}}{2} \right) \right]$$

The system is unstable because the poles $s = \frac{1+j\sqrt{11}}{2}$ and $s = \frac{1-j\sqrt{11}}{2}$ are in the Right half of the s -plane



$$c) T(s) = \frac{3}{s+3} + \frac{9}{s+20} - \frac{4}{s+1} = \frac{3(s+20)(s+1) + 9(s+3)(s+1) - 4(s+3)(s+2)}{(s+3)(s+20)(s+1)}$$

All the poles are in the Left Half of the plane \Rightarrow **stable**

$$d) T(s) = \frac{10}{s+10}$$

stable

Problem 4

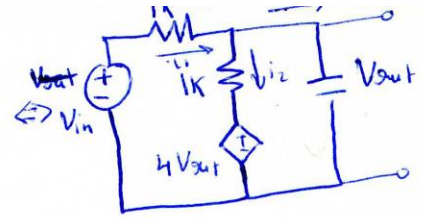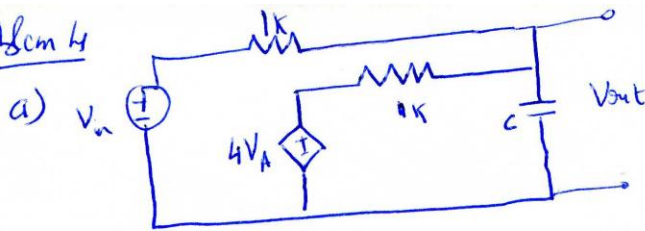

Use KCL

$$i_3 = i_1 - i_2$$


$$(S.C) \cdot \frac{V_{out}}{1} = \left(\frac{V_{in} - V_{out}}{1R} \right) - \left(\frac{V_{out} - 4V_{out}}{1R} \right)$$

$$\Rightarrow V_{out} \left(SC + \frac{1}{1R} + \frac{1}{1R} - \frac{4}{1R} \right) = \frac{V_{in}}{1R}$$

$$\Rightarrow T(s) = \frac{V_{out}}{V_{in}} = \frac{1}{1R \left(SC - \frac{2}{1R} \right)} = \frac{1}{1000s - 2}$$

$C = 1\mu F \Rightarrow T(s) = \frac{1}{10^{-3}s - 2} = \frac{10^3}{s - 2000}$

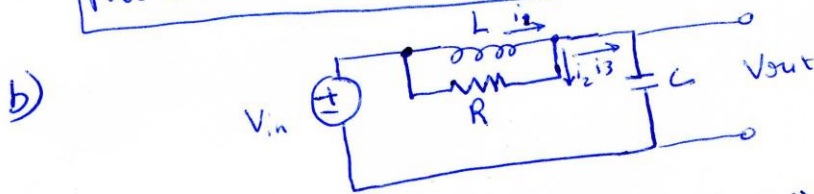Pole at $s = 2000$ in RHP \Rightarrow System unstable



Use KCL $i_3 = -i_2 + i_1 = \left(\frac{V_{in} - V_{out}}{sL} \right) + \left(\frac{V_{in} - V_{out}}{R} \right) = (S.C) V_{out}$

$$\Rightarrow V_{out} \left(sC + \frac{1}{sL} + \frac{1}{R} \right) = V_{in} \left(\frac{1}{sL} + \frac{1}{R} \right)$$

$$T(s) = \frac{V_{out}}{V_{in}} = \frac{\frac{1}{sL} + \frac{1}{R}}{sC + \frac{1}{sL} + \frac{1}{R}} = \frac{1 + \frac{sL}{R}}{s^2LC + 1 + \frac{sL}{R}} = \frac{R + sL}{s^2RLC + R + sL}$$


$$T(s) = \frac{2000 + 10^3 s}{s^2 \times 2 \times 10^{-3} \times 10^{-3} \times 5 \times 10^{-9} + 2 \times 10^3 + 10^3 s} = \frac{2 \times 10^{11} + 10^5 s}{10^{-8} s^2 + 10^{-3} s + 2 \times 10^3} = \frac{2 \times 10^{11} + 10^5 s}{s^2 + 10^5 s + 2 \times 10^8}$$

$$s^2 + 10^5 s + 2 \times 10^8 = \left[s - (-5 \times 10^4 + j 4.44 \times 10^5) \right] \left[s - (-5 \times 10^4 - j 4.44 \times 10^5) \right]$$

All poles in LHP \Rightarrow Stable

Problem 4

c)

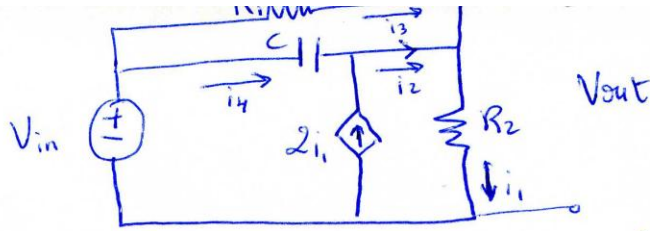

Use KCL $\begin{cases} i_3 = i_2 + i_1 \\ i_2 = 2i_1 + i_4 = 2i_1 + \left(\frac{V_{in} - V_{out}}{1}\right) s \cdot C \end{cases}$ (1) (2)

replace (2) in (1) $\Rightarrow i_1 = 2i_1 + (V_{in} - V_{out}) s C + i_3$
 $\Rightarrow \frac{V_{out}}{R_2} = \frac{2V_{out}}{R_2} + (V_{in} - V_{out}) s C + \frac{(V_{in} - V_{out})}{R_1}$

$\Rightarrow V_{out} \left(s C + \frac{1}{R_1} - \frac{1}{R_2} \right) = V_{in} \left(s C + \frac{1}{R_1} \right)$

$\Rightarrow T(s) = \frac{s C + 1/R_1}{s C + \frac{1}{R_1} - \frac{1}{R_2}} = \frac{s C R_1 + 1}{s C R_1 + 1 - \frac{R_1}{R_2}} = \frac{s C R_1 R_2 + R_2}{s C R_1 R_2 + R_2 - R_1}$

$s C R_1 R_2 + R_2 - R_1 = 0 \Rightarrow s = \frac{R_1 - R_2}{C R_1 R_2}$

$R_1 = 1k$ and $R_2 = 5k \Rightarrow s < 0$

system unstable

Problem 5

a)

$$T(s) = \frac{5}{s+2}$$

$$X_{in}(t) = 4u(t)$$

$$X_{in}(s) = \frac{4}{s}$$

$$X_{out}(s) = T(s) X_{in}(s) = \frac{20}{s(s+2)} = \frac{10}{s} - \frac{10}{s+2}$$

$$X_{out}(t) = \mathcal{L}^{-1}(X_{out}(s)) = 10u(t) - 10e^{-2t}u(t)$$

b) $|T(s)| = |T(s)|_{s=j\omega} = \left| \frac{5}{j\omega+2} \right| = \frac{5}{\sqrt{4+\omega^2}}$

$$|T(j\omega)| = \frac{1}{\sqrt{2}} \Rightarrow \frac{5}{\sqrt{4+\omega^2}} = \frac{1}{\sqrt{2}} \Rightarrow 50 = 4 + \omega^2$$

$$\Rightarrow \omega = \sqrt{46} \text{ rad}$$

Problem 6

$$T(s) = \frac{A}{s+5} = \frac{V_{out}}{V_{in}}$$

$$\Rightarrow V_{out}(s+5) = A V_{in}$$

$$\Rightarrow s V_{out} = A V_{in} - 5 V_{out}$$

let $A=5 \Rightarrow$ $s V_{out} = 5(V_{in} - V_{out})$ (1)



Based on this circuit $s C V_{out} = \frac{(V_{in} - V_{out})}{R}$

or $s V_{out} = \frac{(V_{in} - V_{out})}{R C}$ (2)

compare (1) and (2) $\Rightarrow RC = \frac{1}{5}$

Choose $R = 2k\Omega$ $C = 100\mu F$

Problem 7

Pole at $s = -10$ and DC gain of $1/3$

$$T(s) = \frac{A}{s+10}$$


$$T(0) = \frac{1}{3} \Rightarrow \frac{A}{10} = \frac{1}{3} \Rightarrow A = 10/3$$

$$\boxed{T(s) = \frac{10/3}{s+10}} \quad (1)$$

$$\frac{V_{out}}{V_{in}} = \frac{(10/3)}{s+10} \Rightarrow V_{out}(s+10) = \frac{10}{3} V_{in}$$

$$\Rightarrow s \cdot V_{out} = \frac{10}{3} V_{in} - 10 V_{out} = \frac{10}{3} (V_{in} - V_{out}) = \frac{20 V_{out}}{3}$$
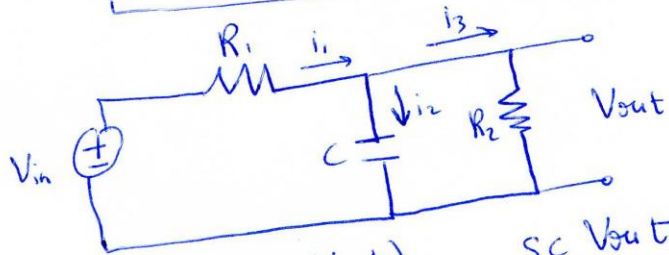
$$\boxed{s \cdot V_{out} = \frac{10}{3} (V_{in} - V_{out}) = \frac{20 V_{out}}{3}} \quad (1)$$



KCL

$$\frac{V_{out}}{R_2} = \frac{(V_{in} - V_{out})}{R_1} - sC V_{out}$$

$$V_{out} \left(sC + \frac{1}{R_2} + \frac{1}{R_1} \right) = \frac{V_{in}}{R_1}$$


$$T(s) = \frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 \left(sC + \frac{1}{R_2} + \frac{1}{R_1} \right)} = \frac{R_2}{R_1 R_2 sC + R_1 + R_2} = \frac{\left(\frac{1}{R_1 C} \right)}{s + \left(\frac{R_1 + R_2}{R_1 R_2 C} \right)}$$

Compare to (1) \Rightarrow

$$\begin{cases} \frac{1}{R_1 C} = \frac{10}{3} \Rightarrow R_1 C = 0.3 \\ \frac{R_1 + R_2}{R_1 R_2 C} = 10 \Rightarrow \frac{R_1 + R_2}{0.3 R_2} = 10 \Rightarrow 2R_2 = R_1 \end{cases}$$

$$\boxed{\text{Choose } C = 100 \mu\text{F} \Rightarrow R_1 = 3 \text{ k}\Omega \text{ and } R_2 = 1.5 \text{ k}\Omega}$$

Problem 8

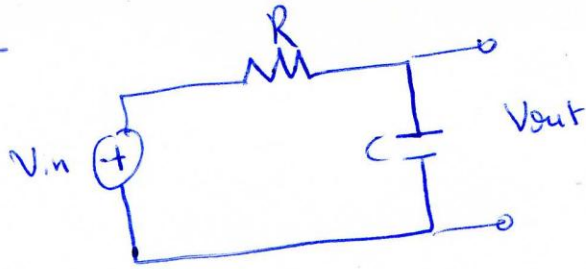

$$T(s) = \frac{1}{RCs + 1}$$

$$V_{out} = \frac{V_{sc}}{R + \frac{1}{sC}} V_{in} \Rightarrow T(s) = \frac{V_{out}}{V_{in}} = \frac{1}{RCs + 1}$$

$$\omega_c = \frac{1}{\sqrt{RC}} = 60\pi \text{ rad/s} \Rightarrow RC = 28 \times 10^{-6}$$

$$\text{let } C = 10 \text{ nF} \Rightarrow R = \frac{28 \times 10^{-6}}{10 \times 10^{-9}} = 2.8 \text{ k}\Omega$$

$$1.39 \text{ (a) } A_v = \frac{v_o}{v_i} = \frac{10 \text{ V}}{100 \text{ mV}} = 100 \text{ V/V}$$

$$\text{or, } 20 \log 100 = 40 \text{ dB}$$

$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_L}{i_i} = \frac{10 \text{ V}/100 \Omega}{100 \mu\text{A}} = \frac{0.1 \text{ A}}{100 \mu\text{A}} \\ = 1000 \text{ A/A}$$

$$\text{or, } 20 \log 1000 = 60 \text{ dB}$$

$$A_p = \frac{v_o i_o}{v_i i_i} = \frac{v_o}{v_i} \times \frac{i_o}{i_i} = 100 \times 1000 \\ = 10^5 \text{ W/W}$$

$$\text{or } 10 \log 10^5 = 50 \text{ dB}$$

$$\text{(b) } A_v = \frac{v_o}{v_i} = \frac{2 \text{ V}}{10 \mu\text{V}} = 2 \times 10^5 \text{ V/V}$$

$$\text{or, } 20 \log 2 \times 10^5 = 106 \text{ dB}$$

$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_L}{i_i} = \frac{2 \text{ V}/10 \text{ k}\Omega}{100 \text{ nA}} \\ = \frac{0.2 \text{ mA}}{100 \text{ nA}} = \frac{0.2 \times 10^{-3}}{100 \times 10^{-9}} = 2000 \text{ A/A}$$

$$\text{or } 20 \log A_i = 66 \text{ dB}$$

$$A_p = \frac{v_o i_o}{v_i i_i} = \frac{v_o}{v_i} \times \frac{i_o}{i_i} \\ = 2 \times 10^5 \times 2000 \\ = 4 \times 10^8 \text{ W/W}$$

$$\text{or } 10 \log A_p = 86 \text{ dB}$$

$$\text{(c) } A_v = \frac{v_o}{v_i} = \frac{10 \text{ V}}{1 \text{ V}} = 10 \text{ V/V}$$

$$\text{or, } 20 \log 10 = 20 \text{ dB}$$

$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_L}{i_i} = \frac{10 \text{ V}/10 \Omega}{1 \text{ mA}} \\ = \frac{1 \text{ A}}{1 \text{ mA}} = 1000 \text{ A/A}$$

or, $20 \log 1000 = 60 \text{ dB}$


$$\begin{aligned} A_p &= \frac{v_o i_o}{v_i i_i} = \frac{v_o}{v_i} \times \frac{i_o}{i_i} \\ &= 10 \times 1000 = 10^4 \text{ W/W} \end{aligned}$$

or $10 \log_{10} A_p = 40 \text{ dB}$

1.41 For $V_{DD} = 5 \text{ V}$:

The largest undistorted sine-wave output is of 3.8-V peak amplitude or $3.8/\sqrt{2} = 2.7 \text{ V}_{\text{rms}}$. Input needed is $5.4 \text{ mV}_{\text{rms}}$.

Supplies are V_{DD} and $-V_{DD}$

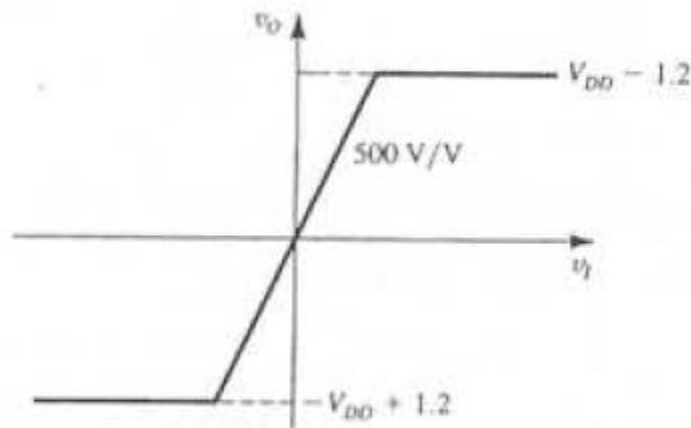

For $V_{DD} = 10 \text{ V}$, the largest undistorted sine-wave output is of 8.8-V peak amplitude or $6.2 \text{ V}_{\text{rms}}$. Input needed is $12.4 \text{ mV}_{\text{rms}}$.

For $V_{DD} = 15 \text{ V}$, the largest undistorted sine-wave output is of 13.8-V peak amplitude or $9.8 \text{ V}_{\text{rms}}$. The input needed is $9.8 \text{ V}/500 = 19.6 \text{ mV}_{\text{rms}}$.