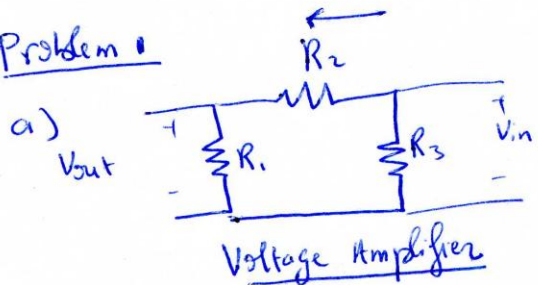



EE 230
HW 4 Solutions

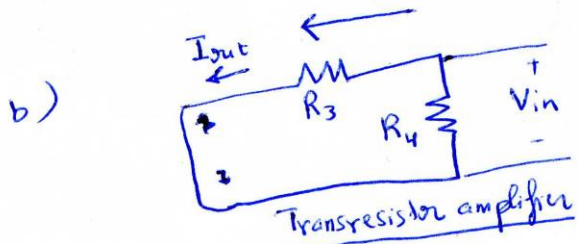Problem 1




$$\beta = \frac{V_{out}}{V_{in}}$$

$$V_{out} = \frac{R_1}{R_1 + R_2} V_{in} \Rightarrow \beta = \frac{R_1}{R_1 + R_2}$$



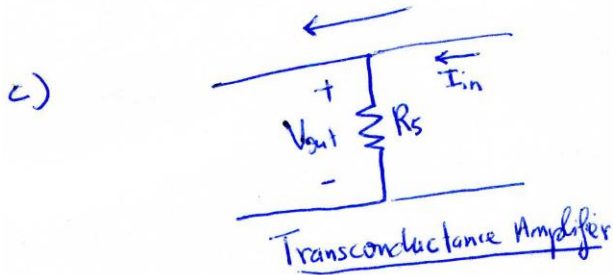
$$\beta = \frac{V_{out}}{V_{in}} \frac{I_{out}}{V_{in}} \Rightarrow \beta = \frac{\left(\frac{V_{in}}{R_3}\right)}{V_{in}} = \frac{1}{R_3}$$



$$\beta = \frac{V_{out}}{I_{in}} \Rightarrow \beta = \frac{R_5 I_{in}}{I_{in}} = R_5$$

Problem 2

$$V_{in} = 0.5 \sin(500t + 30^\circ)$$

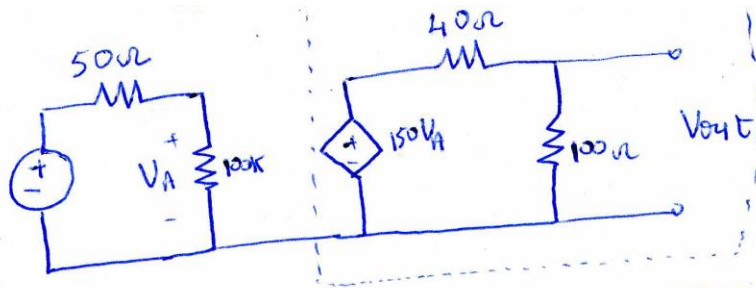

From the second part (dotted box) : $V_{out} = \frac{150 \Omega \times 100}{40 + 100} = \frac{15000 \Omega}{140} = \frac{1500}{14}$ (2)


From the first part

$$V_A = \frac{100 \times 10^3 \times V_{in}}{100 \times 10^3 + 50}$$

Replace (2) in (1) $\Rightarrow V_{out} = \frac{1500 \left(\frac{10^5 V_{in}}{10^5 + 50} \right)}{14} = 107.089 V_{in}$

$$\Rightarrow \boxed{V_{out} = 53.54 \sin(500t + 30^\circ)}$$

Problem 3

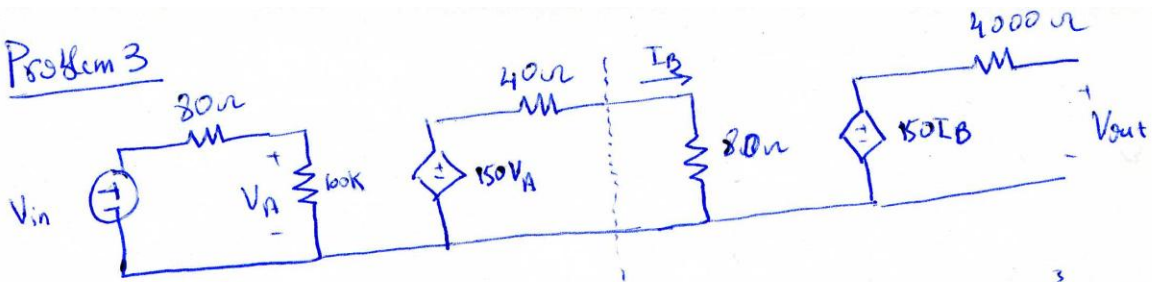


$$\begin{cases} V_{out} = 150 I_B \\ I_B = \frac{150 V_A}{40 + 80} \\ V_A = \frac{100 \times 10^3 \times V_{in}}{80 + 100 \times 10^3} \end{cases} \Rightarrow V_{out} = 150 \times \frac{150}{40 + 80} \times \frac{100 \times 10^3}{80 + 100 \times 10^3} V_{in}$$


$$\Rightarrow \boxed{\text{Gain} = \frac{V_{out}}{V_{in}} = 187.35}$$

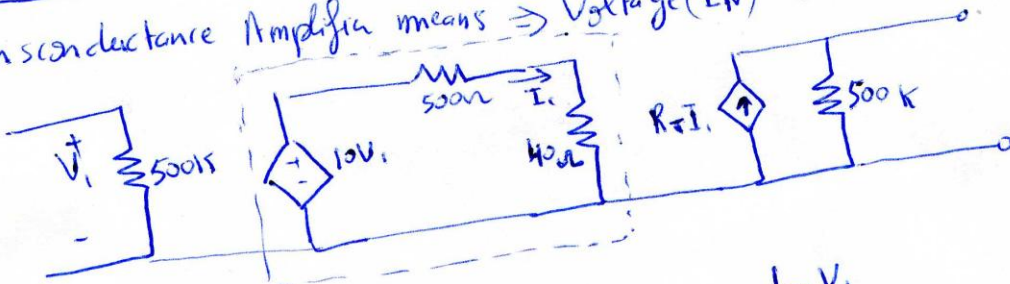Problem 4


Transconductance Amplifier means \Rightarrow Voltage (IN) and Current (OUT)



Based on the dotted box : $I_1 = \frac{10V_i}{500 + 40} = \frac{1}{54} V_i$

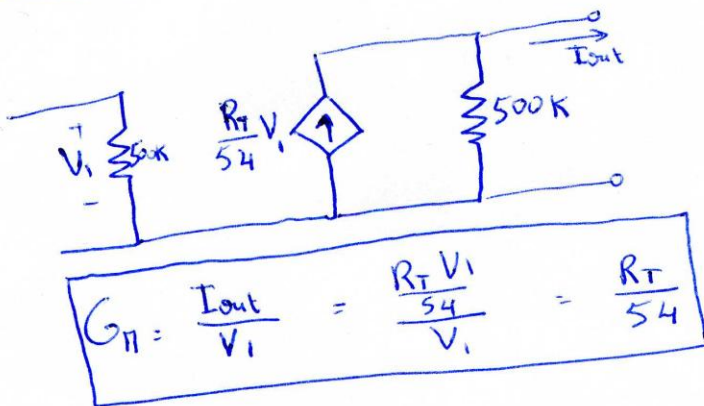

Problem 5

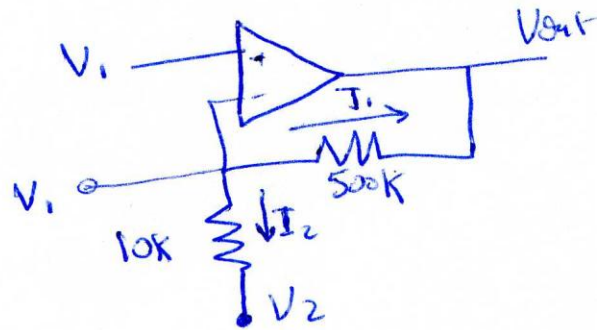

$$\underline{V^+ = V^- = V_1}$$


KCL $I_1 + I_2 = 0$

$$\left(\frac{V_1 - V_{out}}{500K} \right) + \left(\frac{V_1 - V_2}{10K} \right) = 0$$

$$\Rightarrow V_{out} = V_1 + 50(V_1 - V_2)$$

$$\boxed{V_{out} = 51V_1 - 50V_2}$$

Problem 6

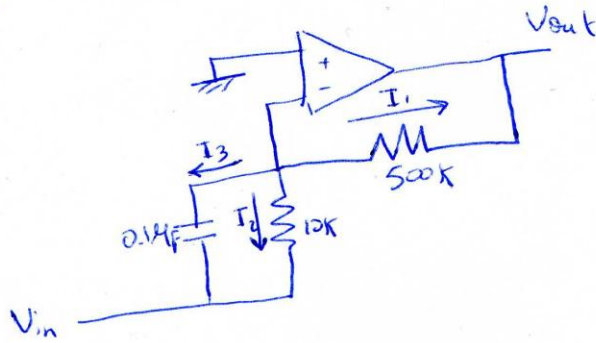

$$V^+ = V^- = 0V$$

$$* \text{ KCL } I_1 + I_2 + I_3 = 0$$

$$\left(-\frac{V_{out}}{500k}\right) + \left(-\frac{V_{in}}{10k}\right) + (-V_{in} s C) = 0$$

$$\Rightarrow V_{out} = -50V_{in} - 500 \times 10^3 s C V_{in}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = -50 - 500 \times 10^3 \times 0.1 \times 10^{-6} \cdot s$$

$$\Rightarrow \boxed{T(s) = \frac{V_{out}}{V_{in}} = -50 - 0.05s}$$


$$* V_{in} = 2u(t) \Rightarrow V_{in}(s) = \frac{2}{s}$$

$$V_{out}(s) = V_{in}(s) \cdot T(s) = \frac{2}{s} (-50 - 0.05s) = \frac{-100}{s} - 0.05x$$

$$V_{out}(t) = \mathcal{L}^{-1}(V_{out}(s)) = -100u(t) - 0.1\delta(t)$$


$$\boxed{V_{out}(t) = -(0.1\delta(t) + 100u(t))}$$

Problem 7

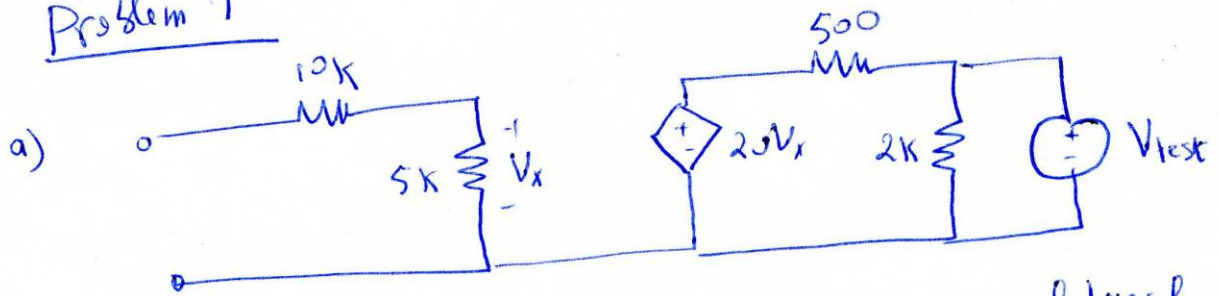

$V_x = 0$
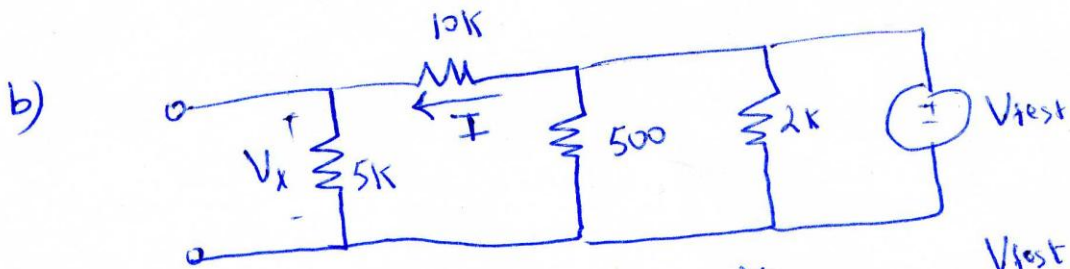
$$A_{VR} = \frac{V_x}{V_{test}} = \frac{0}{V_{test}} = 0 \Rightarrow \text{unilateral}$$



we have




$$I = \frac{V_{test}}{10K + 5K} = \frac{V_{test}}{15K}$$

and


$$V_x = 5K \cdot I = \frac{5K V_{test}}{15K} = \frac{1}{3} V_{test}$$

$$\Rightarrow \boxed{\frac{V_x}{V_{test}} = \frac{1}{3} \Rightarrow \text{Not unilateral}}$$

Problem 8

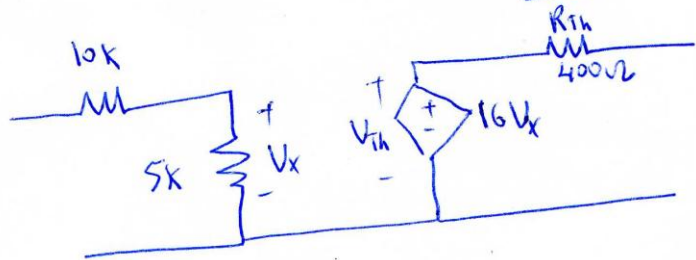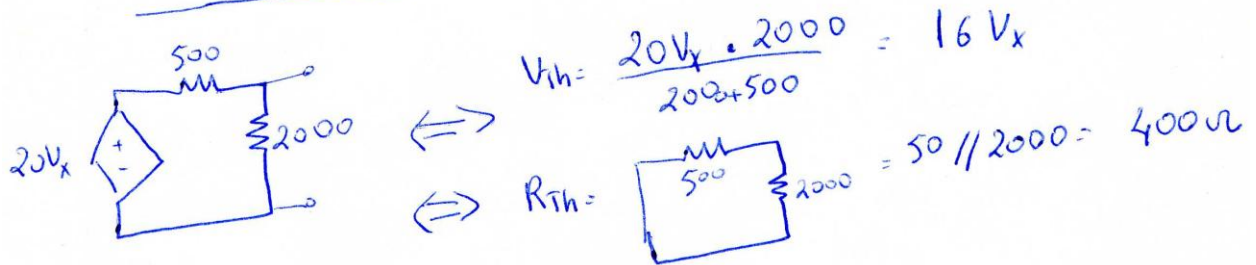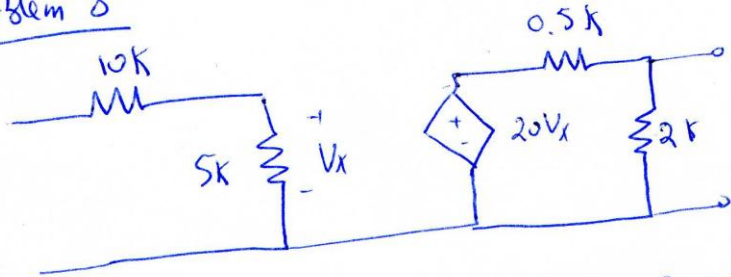

Problem 9

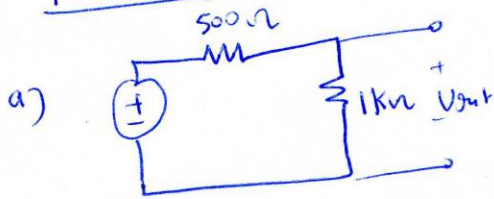


$$V_{out} = \frac{V_{in} \cdot 1K}{1K + 0.5K} = \frac{2}{3} V_{in}$$

$$P_L = \frac{V_{out}^2}{R_L} = \frac{\left(\frac{2}{3} V_{in}\right)^2}{R_L} = \frac{4}{9} \frac{V_{in}^2}{R_L}$$

$$P_{source} = \frac{V_{in}^2}{1K + 0.5K} = \left(\frac{2}{3K}\right) V_{in}^2$$
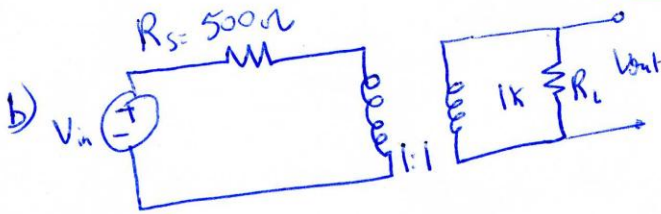
$$\eta = \frac{P_L}{P_{source}} = \frac{\left(\frac{4}{9K}\right) V_{in}^2}{\left(\frac{2}{3K}\right) V_{in}^2} = \frac{4}{9} \cdot \frac{3}{2} = \frac{2}{3} = 66\%$$




$$\eta = \frac{P_{load}}{P_{in}} = \frac{R_L / r^2}{R_s + R_L / r^2}$$

$r = 1 \quad R_s = 500 \Omega \quad R_L = 1000 \Omega$

$$\eta = \frac{1000}{1500} = \frac{2}{3} = 66\%$$


See lecture 8 pg 24

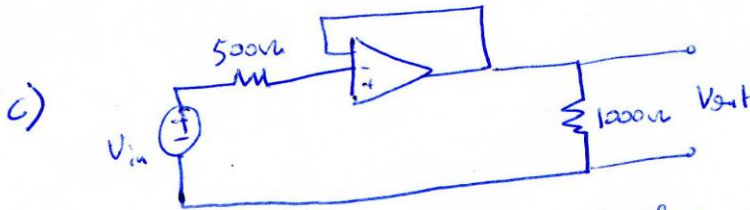

The op-amp acts as a buffer $\Rightarrow V_{in} = V_{out} \Rightarrow \eta = 100\%$

$$P_L = \frac{V_{out}^2}{1000 \Omega} = \frac{V_{in}^2}{1000} = \frac{1}{1000} = 1 \text{ mW}$$

Problem 10

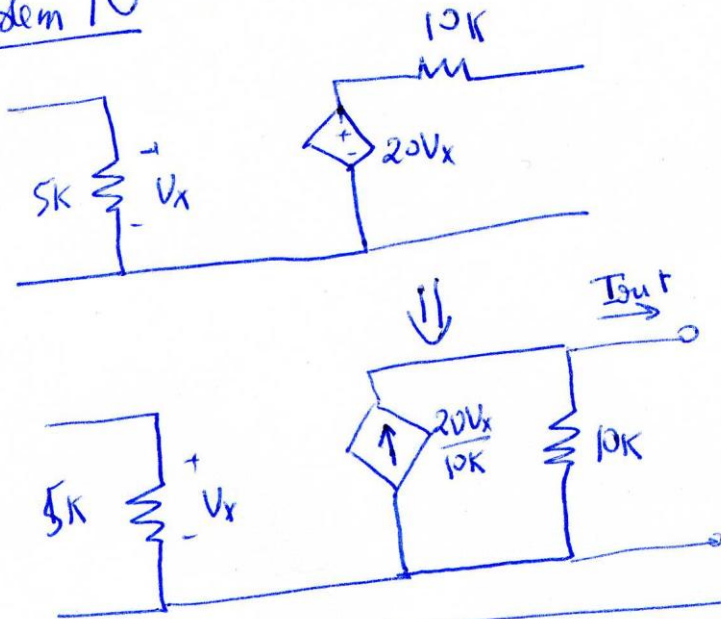

$$G_m = \frac{20}{10 \times 1000} = 0.002$$