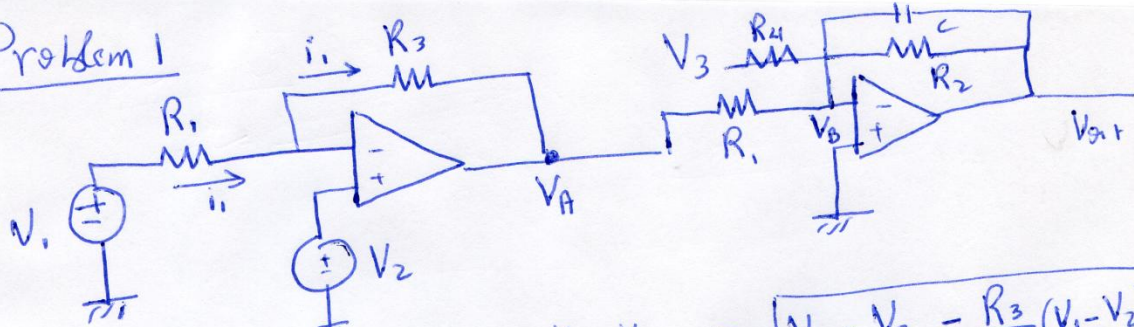


Problem 1



* USE KCL

$$i_1 = \frac{V_1 - V_2}{R_1} = \frac{V_2 - V_A}{R_3} \Rightarrow \boxed{V_A = V_2 - \frac{R_3}{R_1}(V_1 - V_2)}$$

* In second stage, we have inverting amp with $Z = R_2 \parallel \frac{1}{sC}$ and $V_B = 0$

$$\text{KCL} \Rightarrow \frac{V_A - V_B}{R_1} + \frac{V_3 - V_B}{R_4} = \frac{V_B - V_{out}}{Z} \quad \left(Z = R_2 \parallel \left(\frac{1}{sC} \right) \right)$$

$$\Rightarrow \frac{V_A}{R_1} + \frac{V_3}{R_4} = \frac{-V_{out}}{\left(\frac{R_2}{R_2 sC + 1} \right)}$$

$$\Rightarrow \boxed{V_{out} = \frac{-R_2}{R_1 R_2 sC + R_1} V_A - \frac{R_2}{R_2 R_4 sC + R_4} V_3} \quad (2)$$


Combine (1) and (2)

$$V_{out} = \frac{-R_2}{R_1 R_2 sC + R_1} V_2 + \frac{R_2 R_3}{R_1^2 R_2 sC + R_1^2} (V_1 - V_2) - \frac{R_2}{R_2 R_4 sC + R_4} V_3$$

$$V_{out} = \frac{R_2 R_3}{R_1^2 R_2 sC + R_1^2} V_1 - \left(\frac{R_2}{R_1 R_2 sC + R_1} + \frac{R_2 R_3}{R_1^2 R_2 sC + R_1^2} \right) V_2 - \frac{R_2}{R_2 R_4 sC + R_4} V_3$$

$$\boxed{V_{out} = \left(\frac{R_2 R_3}{R_1^2 R_2 sC + R_1^2} \right) V_1 - \left(\frac{R_1 R_2 + R_2 R_3}{R_1^2 R_2 sC + R_1^2} \right) V_2 - \left(\frac{R_2}{R_2 R_4 sC + R_4} \right) V_3}$$

Problem 2

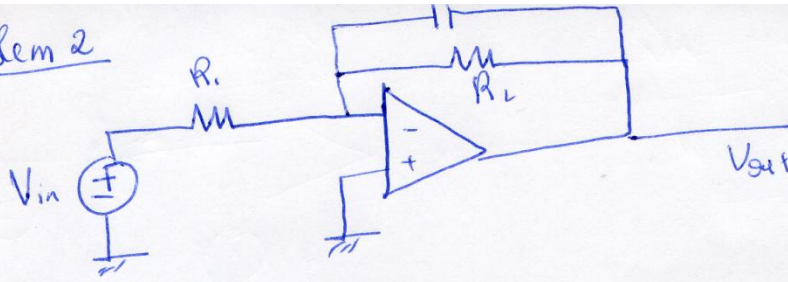

From Lecture 12 page 17

$$T(s) = -\left(\frac{R_2}{R_1}\right) \cdot \frac{1}{1 + sCR_2}$$

$$R_2 = 10 \times 10^3 \Omega, \quad R_1 = 2 \times 10^3, \quad C = 100 \times 10^{-9} \text{ F} = 10^{-7} \text{ F}$$

$$T(s) = -5 \cdot \frac{1}{1 + s \times 10^{-4}} = \frac{-5000}{s + 1000}$$

Pole at $s = -1000$


\Rightarrow

$$\omega_0 = -p = 1000 \text{ rad/s}$$

$$\left|T(s)\right|_{\omega=\omega_0} = \frac{5000}{\sqrt{\omega^2 + 10^6}} \Big|_{\omega=1000} = \frac{5000}{\sqrt{2 \times 10^6}} = \frac{5000}{\sqrt{2} \times 10^3} = \frac{5}{\sqrt{2}}$$

Matlab code

```
clear all
close all
f = -2:.01:5;
f = 10.^f;
w = 2*pi*f;
T = 5000./sqrt(w.^2 + 10^6);
semilogx(f,T,'linewidth',2.5)
grid on
xlabel('Frequency(Hz)','fontsize',14),ylabel('Magnitude','fontsize',14)
set(get(gcf,'CurrentAxes'),'FontSize',14)
title('Magnitude versus frequency','fontsize',14)
```

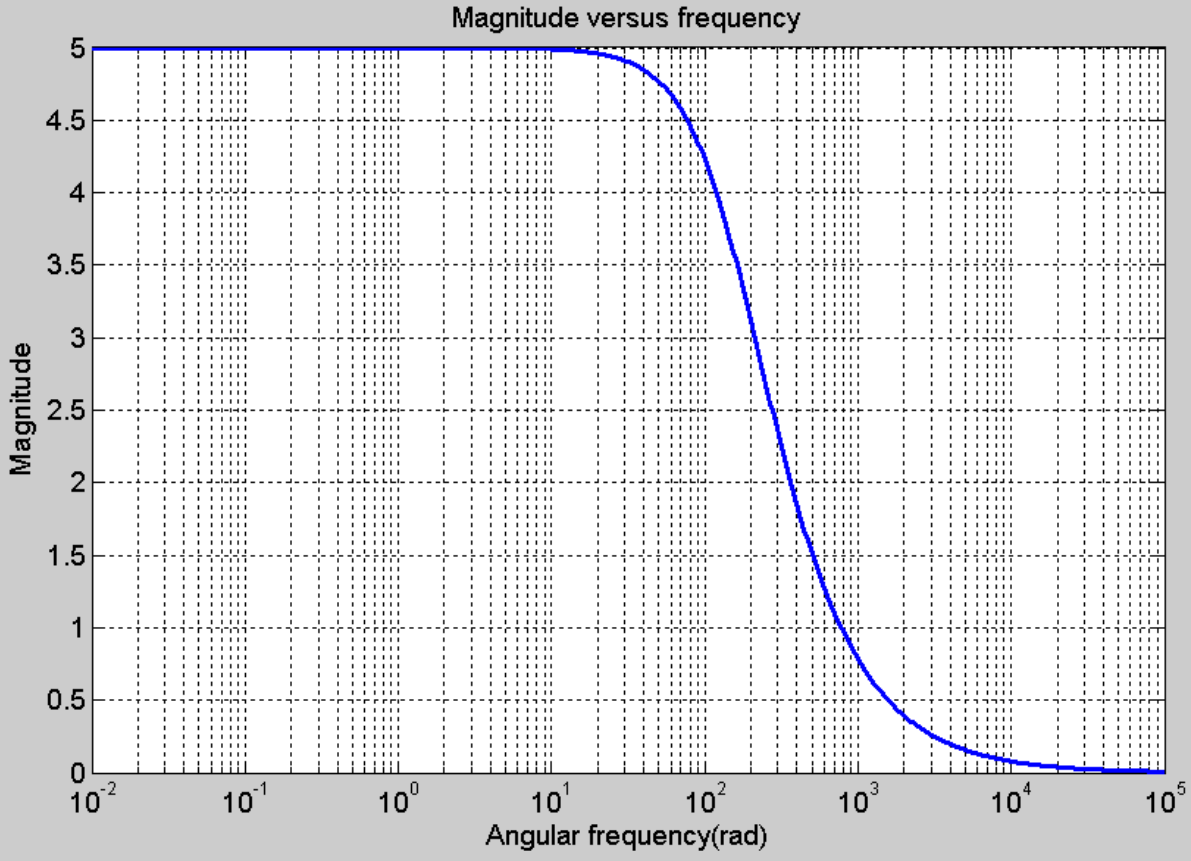

Problem 3


Similar to problem (2)

$$T(s) = -\left(\frac{R_2}{R_1}\right) \cdot \frac{1}{1+sCR_2}$$


Given $A(s) = \frac{A_0}{\frac{s}{P} + 1} \Rightarrow -\frac{R_2}{R_1} = A_0$ and $CR_2 = \frac{1}{P}$

or $A_0 = -\frac{R_2}{R_1}$, $P = \frac{1}{R_2C}$

Pole at $s = -\frac{1}{R_2C}$

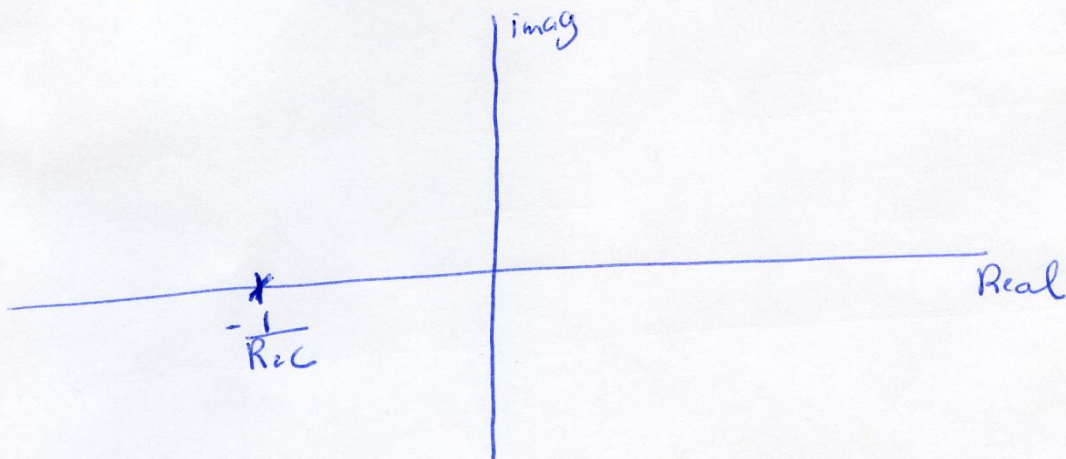

Problem 4

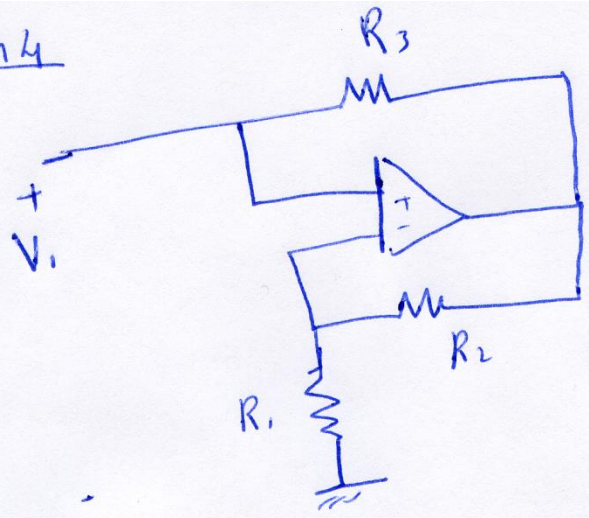


from Lecture 15 pg 20

$$Z_{in} = -\frac{R_1 R_3}{R_2}$$

Choose

$R_1 = 2\text{ k}\Omega$	$R_2 = 1\text{ k}\Omega$	$R_3 = 10\text{ k}\Omega$
--------------------------	--------------------------	---------------------------

Problem 5

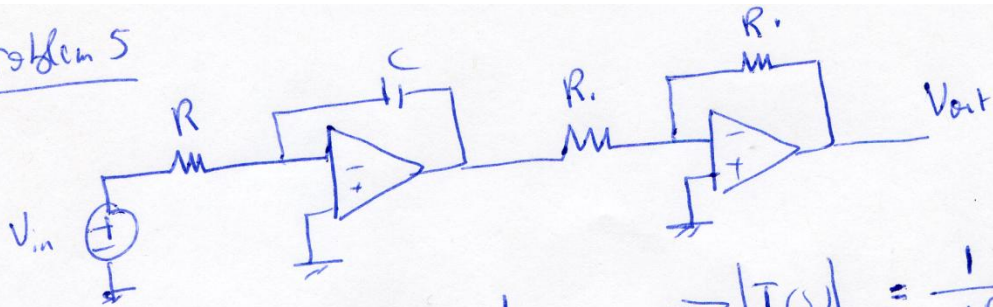

$$T(s) = \frac{1}{sRC} \Rightarrow |T(s)| = \frac{1}{\omega RC}$$


$$f = 10 \text{ kHz} \Rightarrow |T(s)| = 1 \Rightarrow \omega = \frac{1}{RC}$$

$$\text{or } RC = \frac{1}{\omega} = \frac{1}{2\pi \times 10^4} \approx$$

$$\text{Choose } C = 10 \text{ nF} \Rightarrow R = \frac{1}{2\pi \times 10^4} \cdot \frac{1}{10 \times 10^{-9}} = \frac{1}{2\pi} \times 10^4$$

$$R = 1.59 \text{ k}\Omega$$

Problem 6

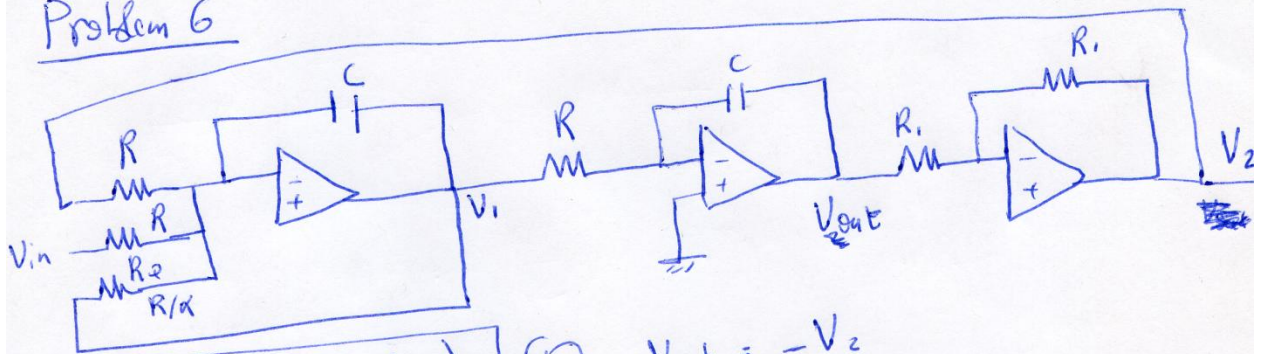

$$V_{out} = -V_1 \left(\frac{1}{sR_1C} \right) \quad (1) \quad V_{out} = -V_2$$

$$V_1 = \left(\frac{-1}{sR_1C} \right) V_2 + \left(\frac{-1}{sR_1C} \right) V_{in} + \left(\frac{1}{sR_1C} \right) V_1$$

$$\Rightarrow V_1 \left(1 + \frac{1}{sR_1C} \right) = \frac{V_{out}}{sR_1C} - \frac{1}{sR_1C} V_{in} \quad (2)$$

Replace (2) in (1)

$$V_{out} = \left(\frac{-1}{sR_1C} \right) \frac{sR_1C}{1+sR_1C} \left(\frac{V_{out} - V_{in}}{sR_1C} \right)$$

$$V_{out} = -\frac{R_1}{R_1 + sR_1R_1C} \left(\frac{V_{out} - V_{in}}{sR_1C} \right)$$

$$V_{out} \left(1 + \frac{R_1}{sR_1^2C + s^2R_1^2R_1C^2} \right) = \frac{R_1}{R_1^2sC + s^2R_1^2R_1C^2} V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_1}{R_1^2sC + s^2R_1^2R_1C^2} \times \frac{sR_1^2C + s^2R_1^2R_1C^2}{R_1 + sR_1^2C + s^2R_1^2R_1C^2}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_1}{(R_1^2R_1C^2)s^2 + (R_1^2C)s + R_1} = \frac{\left(\frac{1}{RC} \right)^2}{s^2 + s \left(\frac{R}{R_1C} \right) + \left(\frac{1}{RC} \right)^2}$$


$$BW = \frac{1}{R_1C} = \left| \frac{\alpha}{RC} \right| \quad \omega_p = \sqrt{\left(\frac{1}{RC} \right)^2} = \left| \frac{1}{RC} \right|$$

No Zeros

poles @

$$s = \frac{-\frac{\alpha}{RC} \pm \sqrt{\frac{\alpha^2 - 4}{(RC)^2}}}{2}$$

Problem 7

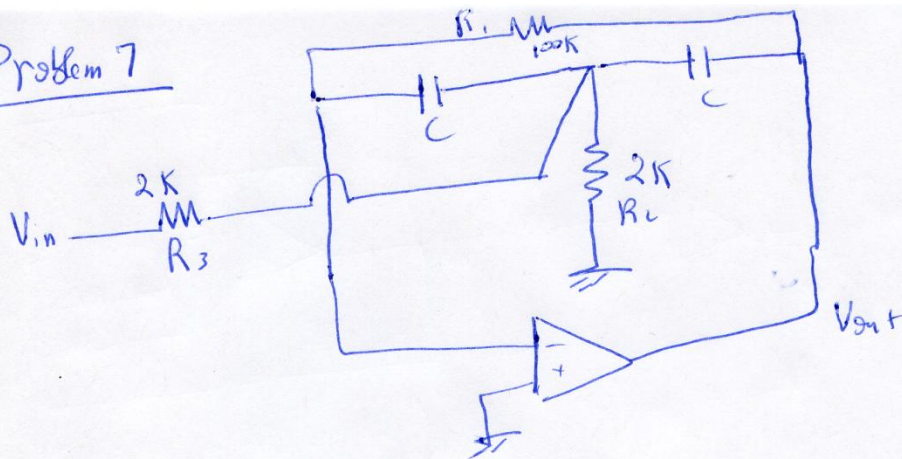

Lecture (12) pg 32

$$T(s) = - \frac{\frac{s}{R_3 C}}{s^2 + s \left(\frac{2}{R_1 C} \right) + \frac{1}{(R_1 // R_3) R_1 C^2}}$$

$$\omega_p = \frac{1}{\sqrt{R_1 (R_1 // R_3) C}} \quad BW = \frac{2}{R_1 C} \quad K = \frac{R_1}{2R_3}$$

$$BW = \frac{2}{R_1 C} = \boxed{2000 \text{ rad/s}}$$

$$\omega_p = \boxed{10,000 \text{ rad/s}}$$

$$K = \boxed{25}$$

$$\omega_L = \omega_p - \frac{BW}{2} = \boxed{9000 \text{ rad/s}}$$

$$\omega_H = \omega_p + \frac{BW}{2} = \boxed{11,000 \text{ rad/s}}$$

$$\text{Poles } \omega = -9,000 \text{ rad/s} \quad \text{and} \quad -11,000 \text{ rad/s}$$

Problem 8

Use circuit from problem 7

$$BW = 500 \text{ Hz}$$

$$\omega_p = 5 \text{ kHz}$$

$$\text{or } BW = 1000\pi \text{ rad/s}$$

$$\text{a } \omega_p = 10,000\pi \text{ rad/s}$$


$$\text{let } C = 10 \text{ nF} \Rightarrow R_1 = \frac{2}{BW \cdot C} = 63.7 \text{ k}\Omega$$

$$\text{let } k = 10 \Rightarrow R_3 = \frac{R_1}{2k} = 3.18 \text{ k}\Omega$$


$$\omega_p = 10,000\pi = \frac{1}{C} \sqrt{\frac{1}{R_1} \left(\frac{1}{R_2} + \frac{1}{R_3} \right)}$$

$$\Rightarrow R_2 = 167.5 \text{ }\Omega$$

Problem 9

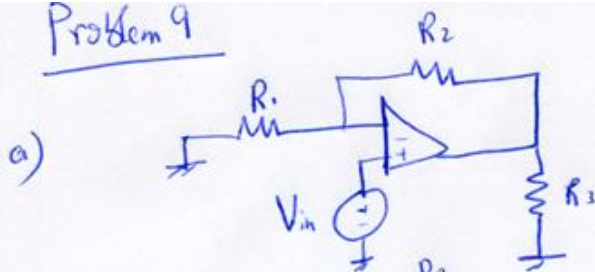

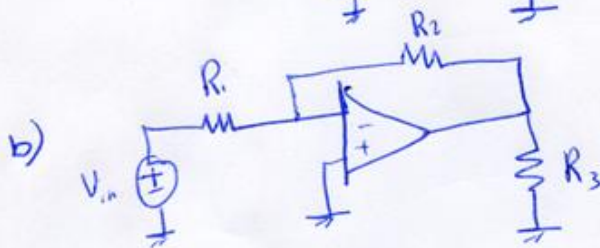
$$\Rightarrow \text{Noninverting amp}$$
$$BW = \frac{GB}{K_0} = \frac{2\pi \text{ Hz}}{1 + \frac{R_2}{R_1}} = 1400 \text{ kHz}$$



$$\Rightarrow \text{Inverting amp}$$
$$BW = \frac{GB}{1 + |K_0|} = \frac{2\pi \text{ Hz}}{1 + 8} = 222 \text{ kHz}$$

Problem 9

c)

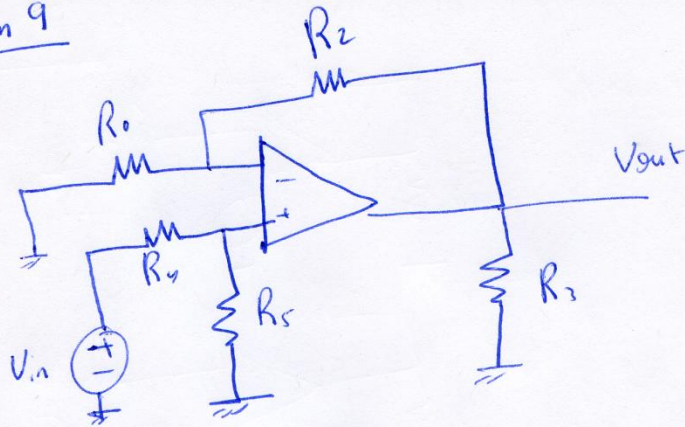

$$V^- = \frac{V_{out} R_1}{R_1 + R_2} = \frac{V_{out}}{9} \Rightarrow V_{out} = (V^+ - V^-) A_o(s)$$


$$V^+ = \frac{V_{in} R_5}{R_4 + R_5} = \frac{V_{in}}{2}$$

$$V_{out} = \frac{GB}{s} \left(\frac{V_{in}}{2} - \frac{V_{out}}{9} \right) \quad (1)$$

from (1) $\frac{V_{out}}{V_{in}} = \frac{9/2}{1 + \frac{9s}{GB}} \Rightarrow BW = \frac{GB}{9}$

$$BW = \frac{2\pi \text{MHz}}{9} = 222 \text{ kHz}$$

Problem 10

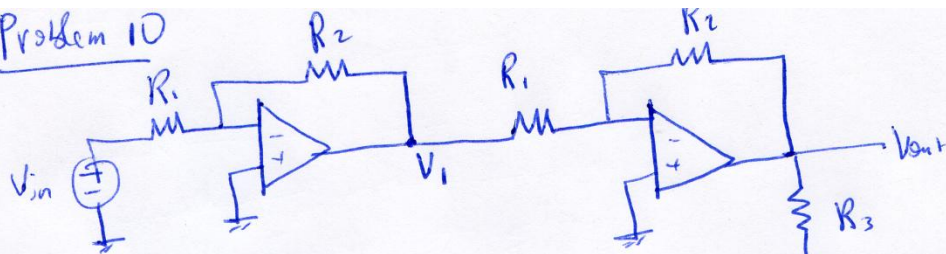

1st stage

$$V_1 = \frac{GB}{s} (V^+ - V^-) = -\frac{GB}{s} V^- = -\frac{GB}{s} \left(V_{in} + \frac{R_1(V_1 - V_{in})}{R_1 + R_2} \right)$$

$$\text{or } V_1 = -\frac{GB}{s} \left(V_{in} + \frac{1}{s} V_1 - \frac{1}{s} V_{in} \right)$$

$$\text{or } V_1 \left(1 + \frac{GB}{5s} \right) = \frac{-4 GB}{5s} V_{in}$$

$$\text{or } V_1 = \frac{-4 GB}{5s + GB} V_{in}$$

$$\Rightarrow BW = \frac{GB}{1.7k} = \frac{750}{1.4} = 500KHz$$

2nd stage

$$V_{out} = \frac{-4 GB}{5s + GB} V_1$$

$$V_{out} = \frac{16 GB^2}{25s^2 + 10GBs + GB^2} V_{in}$$

$$|T(j\omega)| = \frac{16 GB^2}{|(5s + GB)^2|} = \frac{16 GB^2}{25\omega^2 + GB^2}$$

$$\omega = 0 \Rightarrow |T(j\omega)| = 16$$

$$\Rightarrow K_0 = 16$$

$$|T(j\omega)| = \frac{16}{\sqrt{2}} \Rightarrow 16\sqrt{2} GB^2 = 16(25\omega_B^2 + GB^2) \Rightarrow \omega_B^2 = \frac{GB^2(\sqrt{2}-1)}{25}$$

$$\omega_B = GB \sqrt{\frac{\sqrt{2}-1}{25}} = 606.57 \text{ rad/s} = BW$$

$$f_B = 96.5 \text{ KHz}$$

$$BW = \frac{GB}{K_0} = \frac{750KHz}{16} = 46.87 \text{ KHz}$$

single stage

For a 1st stage amplifier with gain 16, we have

$$BW = \frac{GB}{K_2} = \frac{750 \text{ KHZ}}{16} = \boxed{46 \text{ KHZ}}$$

Therefore, there is a significant improvement when we cascade 2 stages.