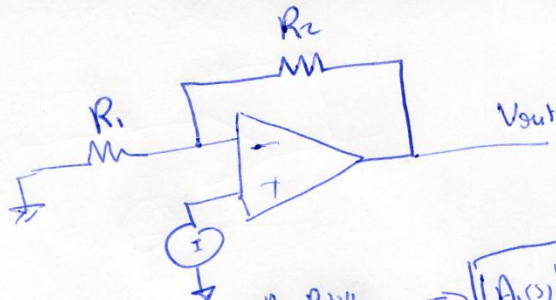


# Problem 1

g)



\* Open Loop

$$A_i(s) = \frac{GB}{s + BW_A}$$

$$= \frac{A_0 BW_A}{s + BW_A}$$

$$\Rightarrow |A_i(s)| = \frac{A_0 BW_A}{\sqrt{\omega^2 + BW_A^2}}$$

At  $\omega=0$

$$|A_i(s)| = A_0$$

\* Closed Loop

$$V_{out} = (V^+ - V^-) A_i(s) = \left( V_{in} - \frac{R_1 V_{out}}{R_1 + R_2} \right) \frac{A_0 BW_A}{s + BW_A}$$

$$V_{out} \left( 1 + \frac{A_0 BW_A}{K_0 (s + BW_A)} \right) = \frac{A_0 BW_A}{s + BW_A} V_{in}$$

$$A_{FB}(s) = \frac{\frac{A_0 BW_A}{s + BW_A}}{\left( \frac{K_0 (s + BW_A) + A_0 BW_A}{K_0 (s + BW_A)} \right)} = \frac{K_0 A_0 BW_A}{K_0 (s + BW_A) + A_0 BW_A}$$

$$|A_{FB}(s)| = \left| \frac{\frac{A_0 BW_A}{s + BW_A + \frac{A_0 BW_A}{K_0}}}{\frac{A_0 BW_A}{s + BW_A + \frac{A_0 BW_A}{K_0}}} \right| = \frac{A_0 BW_A}{\sqrt{\omega^2 + \left( BW_A + \frac{A_0 BW_A}{K_0} \right)^2}}$$

At  $\omega=0$

$$A_{FB}(s) = \frac{A_0 BW_A}{K_0 + A_0}$$

$$= \frac{A_0}{\frac{K_0 + A_0}{K_0}} = \frac{A_0 K_0}{A_0 + K_0} \approx K_0$$

$$\frac{|A_i(s)|}{|A_{FB}(s)|} = \frac{\sqrt{\omega^2 + \left( BW_A + \frac{A_0 BW_A}{K_0} \right)^2}}{\sqrt{\omega^2 + BW_A^2}} = \frac{\sqrt{\omega^2 + \left( BW_A + \frac{GB}{K_0} \right)^2}}{\sqrt{\omega^2 + BW_A^2}}$$

$$GB = BW \cdot K_0 \Rightarrow \frac{GB}{K_0} = BW$$

At  $\omega \gg BW$

$$\begin{cases} \omega^2 + \left( BW_A + \frac{GB}{K_0} \right)^2 \approx \omega^2 \\ \omega^2 + BW_A^2 \approx \omega^2 \end{cases}$$

$$\Rightarrow \left| \frac{A_i(s)}{A_{FB}(s)} \right| = 1 \quad \underline{\underline{\omega \gg BW}}$$

$$b) \quad V_{out} = (V^+ - V^-) A(s) = \left( V_{in} - \frac{R_1 V_{out}}{R_1 + R_2} \right) \frac{GB}{s}$$

$$V_{out} \left( 1 + \frac{GB}{K_0 s} \right) = \frac{GB}{s} V_{in}$$


$$A(s) = \frac{V_{out}}{V_{in}} = \frac{GB/s}{\left( \frac{K_0 s + GB}{K_0 s} \right)} = \frac{K_0 GB}{K_0 s + GB} = \frac{GB}{s + \left( \frac{GB}{K_0} \right)}$$

$$\boxed{|A(s)| = \frac{GB}{\sqrt{\omega^2 + \left( \frac{GB}{K_0} \right)^2}}}$$

$$\text{Compare to } A_{FB}(s) = \frac{GB}{\sqrt{\omega^2 + \left( BW_A + \frac{GB}{K_0} \right)^2}}$$

$$\boxed{\text{At frequencies } \omega \gg BW_A \quad |A(s)| \approx A_{FB}(s)}$$



## Problem 2

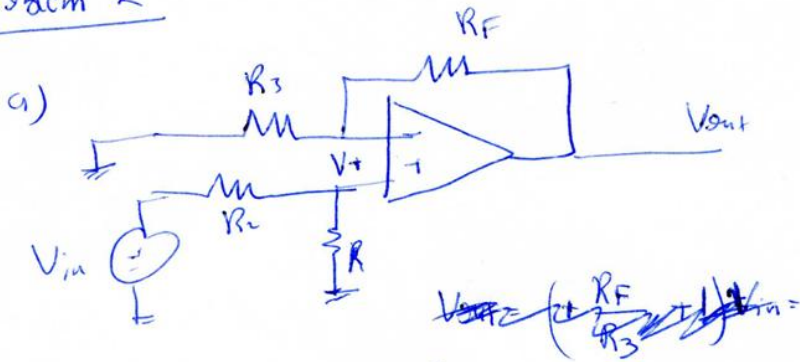


$$V_{out} = \left(1 + \frac{R_F}{R_3}\right) V^+ = 2 V^+$$

$$K_o = \frac{V_{out}}{V^+} = 2$$
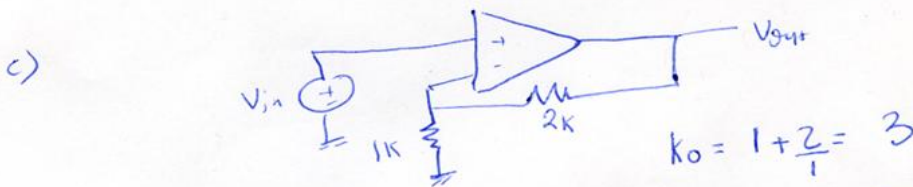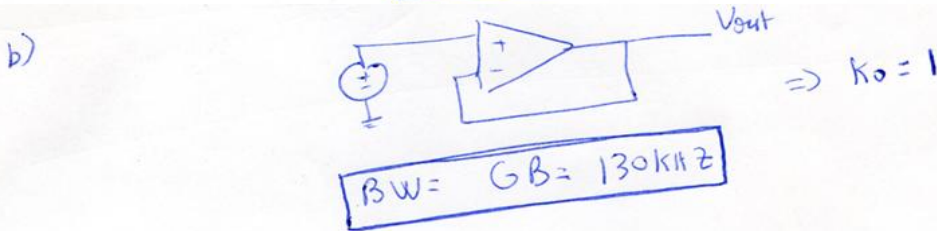
$$BW = \frac{GB}{K_o} = \frac{130 \text{ kHz}}{2} = 65 \text{ kHz}$$



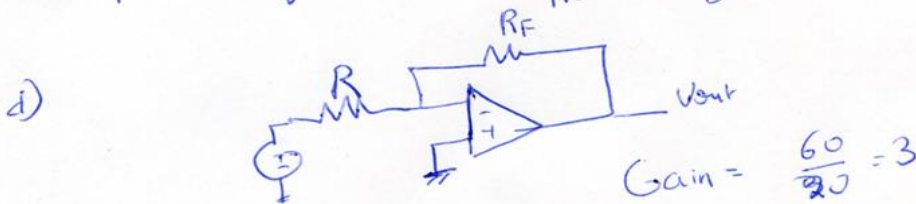
Non-inverting  $\Rightarrow BW = \frac{GB}{K_o} = \frac{130}{3} = 43 \text{ kHz}$



Inverting  $BW = \frac{GB}{1 \times 3} = \frac{130}{4} = 32.5 \text{ kHz}$



Problem 3

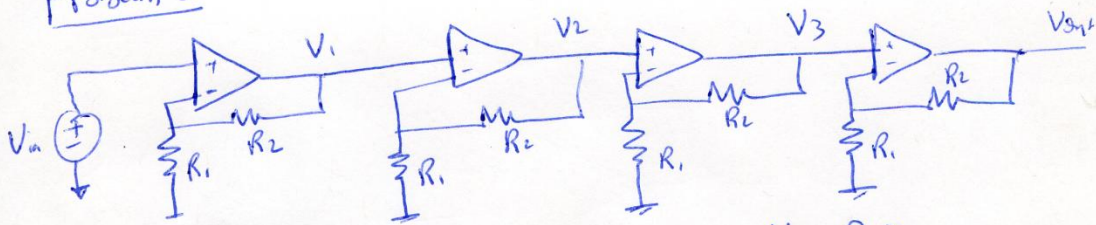

$$V_1 = \frac{GB}{s} (V^+ - V^-) = \frac{GB}{s} (V_{in} - \frac{V_1 \cdot R_1}{R_1 + R_2})$$

$$V_1 \left( 1 + \frac{GB R_1}{s(R_1 + R_2)} \right) = \frac{GB}{s} V_{in} \Rightarrow V_1 = \frac{GB/s}{\left( \frac{s(R_1 + R_2) + GB R_1}{s(R_1 + R_2)} \right)} V_{in}$$

$$\text{or } V_1 = \frac{(R_1 + R_2) GB}{s(R_1 + R_2) + GB R_1} = \frac{GB}{s + GB \left( \frac{R_1}{R_1 + R_2} \right)} V_{in}$$

Similarly

$$V_2 = \frac{GB}{s + GB \left( \frac{R_1}{R_1 + R_2} \right)} V_1$$

"

$$V_3 = \frac{GB}{s + GB \left( \frac{R_1}{R_1 + R_2} \right)} V_2$$

$$V_{out} = \frac{GB}{s + GB \left( \frac{R_1}{R_1 + R_2} \right)} V_3 = \frac{GB^4}{\left[ s + GB \left( \frac{R_1}{R_1 + R_2} \right) \right]^4} V_{in} \Rightarrow T(j\omega) = \frac{GB^4}{\left[ j\omega + \frac{GB R_1}{R_1 + R_2} \right]^4}$$

$$K_0 = \left| \frac{V_{out}}{V_{in}} \right|_{\omega=0} = \frac{1}{\left( \frac{R_1}{R_1 + R_2} \right)^4} = \left( \frac{R_1 + R_2}{R_1} \right)^4$$

$$|T(j\omega)| = \frac{K_0}{\sqrt{2}} \Rightarrow \frac{GB^4}{\left( \omega_B^2 + \left( \frac{GB R_1}{R_1 + R_2} \right)^2 \right)^2} = \frac{\left( \frac{R_1 + R_2}{R_1} \right)^4}{\sqrt{2}}$$

$$\Rightarrow \frac{R_1 + R_2}{R_1} \left( \omega_B^2 + \left( \frac{GB R_1}{R_1 + R_2} \right)^2 \right) = 2^{1/4} GB^2$$


$$\Rightarrow \omega_B^2 = GB^2 \left( 2^{1/4} \left( \frac{R_1 + R_2}{R_1} \right)^2 - 1 \right)$$

$$\omega_B^2 = \frac{2^{1/4} GB^2}{\left(\frac{R_1+R_2}{R_1}\right)^2} - GB^2 \left(\frac{R_1}{R_1+R_2}\right)^2$$

$$\omega_B = \sqrt{GB^2 \left(\frac{R_1}{R_1+R_2}\right)^2 2^{1/4} - \left(\frac{R_1}{R_1+R_2}\right)^2}$$

$$\omega_B = GB \left(\frac{R_1}{R_1+R_2}\right) (2^{1/4} - 1)$$
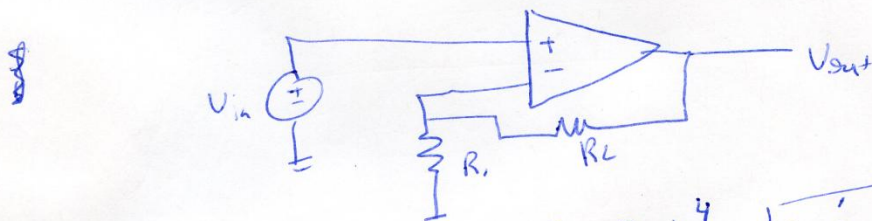
$$\boxed{\omega_B = 0.18 GB \left(\frac{R_1}{R_1+R_2}\right)} = BW \quad (1)$$




for a gain of  $\left(\frac{R_1+R_2}{R_1}\right)^4$   $\boxed{BW' = \frac{GB}{\left(\frac{R_1+R_2}{R_1}\right)^4}} \quad (2)$

$$\boxed{\frac{BW}{BW'} = 0.18 \left(\frac{R_1+R_2}{R_1}\right)^3}$$

Therefore the bandwidth is much larger when we cascade 4 stages.



Problem 5

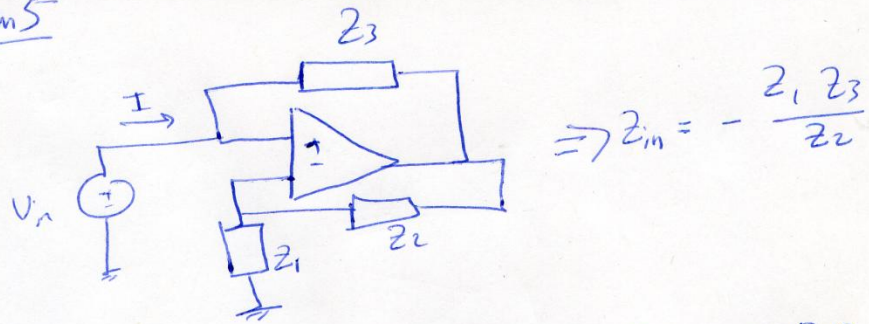

$$\Rightarrow Z_{in} = -\frac{Z_1 Z_3}{Z_2}$$

Choose  $Z_2 = \frac{1}{sC}$ ,  $Z_1 = R_1$ ,  $Z_3 = R_3 \Rightarrow Z_{in} = -sCR_1R_3$


Let  $C = 1\text{nF}$ ,  $R_1 = 3\text{k}\Omega$ ,  $R_3 = 1\text{k}\Omega \Rightarrow Z'_{in} = -3 \times 10^{-3} \text{ S}$

For a 3mH inductor  $Z = 3 \times 10^{-3} \text{ S}$


We need to invert  $Z'_{in}$

$$Z_{in} = -\frac{Z'_{in} Z_3}{Z_2} \quad \text{by letting}$$
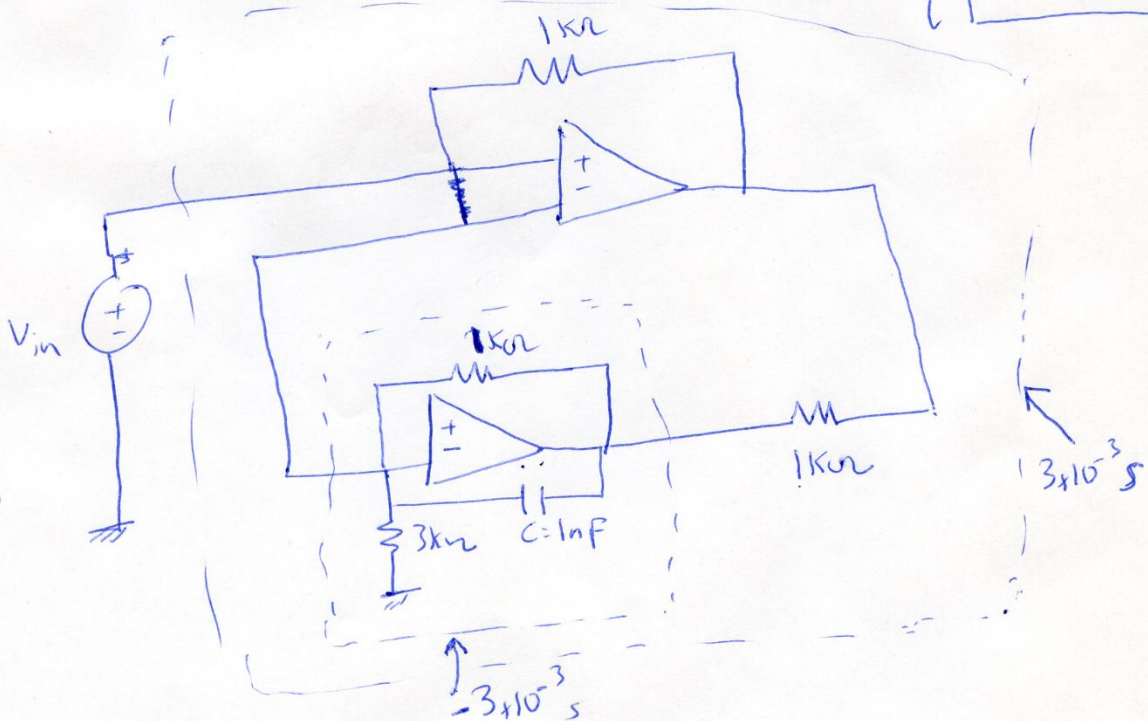
$$\begin{cases} Z'_{in} = Z_1 \\ Z_3 = 1\text{k}\Omega \\ Z_2 = 1\text{k}\Omega \end{cases}$$



## Problem 6

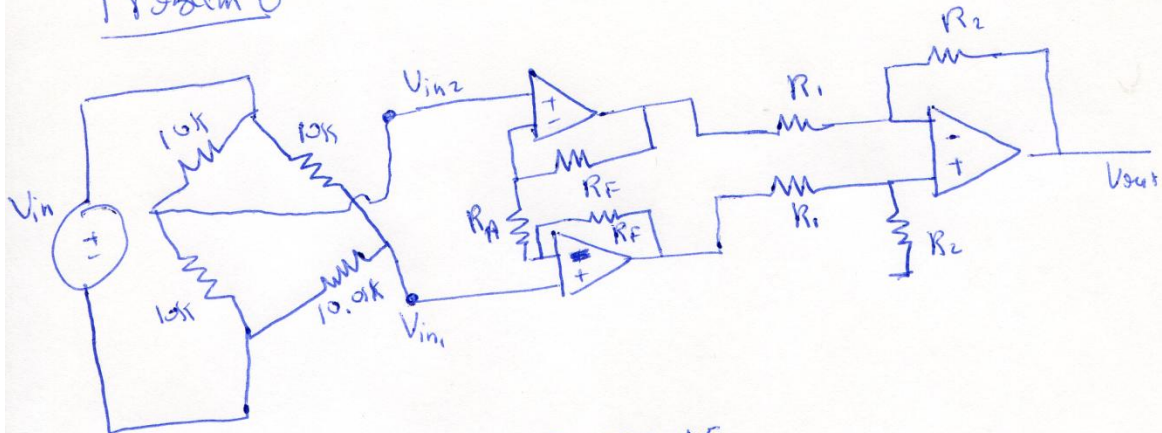

From Lecture 15 pg 15

$$V_{out} = (V_{in2} - V_{in1}) \left( 1 + \frac{2R_F}{R_A} \right) \left( \frac{R_2}{R_i} \right)$$

$$\boxed{V_{out} = (V_{in2} - V_{in1}) = 450(V_{in2} - V_{in1})}$$

$$V_{in2} = V_{in} \left( \frac{10k}{10k + 10k} \right) = \frac{1}{2} V_{in}$$


$$V_{in1} = V_{in} \left( \frac{10.01k}{10.01 + 10} \right) = 0.50025 V_{in}$$

$$V_{out} = 450 V_{in} (0.5 - 0.50025)$$

$$V_{out} = 0.1124 V_{in}$$

$$\boxed{V_{out} = 0.56 \sin 500t}$$

Problem 7

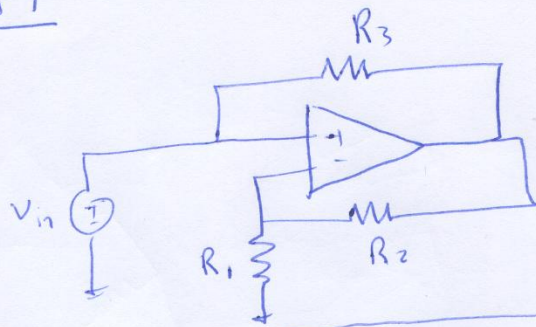

$$R_{in} = - \frac{R_1 R_3}{R_2}$$

Choose

$R_1 = 10 \text{ k}\Omega$	$R_3 = 1 \text{ k}\Omega$	$R_2 = 1 \text{ k}\Omega$
----------------------------	---------------------------	---------------------------



Problem 8

$$\epsilon = \frac{\Delta L}{L} = \frac{GFL}{YWh^2}$$

$$\frac{\Delta R}{R} = \frac{\epsilon}{K}$$

$$L = 1 \text{ m}$$

$$W = 1 \text{ inch} = 0.0254 \text{ m}$$

$$H = 0.2 \text{ inch} = 0.00508 \text{ m} \quad Y = 6.9 \times 10^{10} \frac{\text{N}}{\text{m}^2}$$


$$1 \text{ pound} = 4.448 \text{ N}$$

$$\epsilon = F \frac{GL}{YWh^2} = \frac{FG}{45228.3} = 1.327 \times 10^{-4} \text{ F}$$

$$\frac{\Delta R}{R} = \frac{\epsilon}{K} \Rightarrow \Delta R = \frac{R\epsilon}{K} = \frac{300 \times 1.327 \times 10^{-4}}{1.5} \text{ F}$$

$$\boxed{\Delta R = 0.0265 \text{ F}}$$
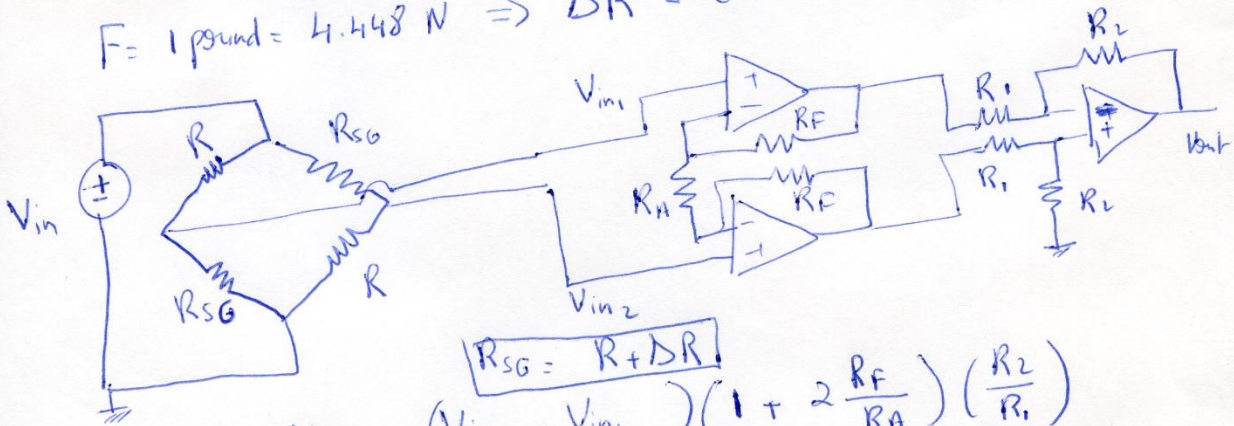
$$F = 1 \text{ pound} = 4.448 \text{ N} \Rightarrow \Delta R = 0.117872 \Omega$$



$$\boxed{R_{SG} = R + \Delta R}$$

$$V_{out} = (V_{in2} - V_{in1}) \left(1 + 2 \frac{R_F}{R_A}\right) \left(\frac{R_2}{R_1}\right)$$

$$V_{out} = \left(V_{in} \frac{R_{SG}}{R_{SG}+R} - V_{in} \frac{R}{R_{SG}+R}\right) \left(1 + 2 \frac{R_F}{R_A}\right) \left(\frac{R_2}{R_1}\right)$$

$$V_{out} = \frac{V_{in}}{R_{SG}+R} (-R + R_{SG}) \left(1 + 2 \frac{R_F}{R_A}\right) \left(\frac{R_2}{R_1}\right)$$

$$V_{out} = 5V \quad \text{and} \quad \Delta R = 0.117872 \Omega \Rightarrow 5 = \frac{V_{in}}{600 + 0.117872} (0.117872) \left(1 + 2 \frac{R_F}{R_A}\right) \left(\frac{R_2}{R_1}\right)$$

$$\Rightarrow 25456.33 = \left(1 + 2 \frac{R_F}{R_A}\right) \left(\frac{R_2}{R_1}\right) V_{in}$$

Choose	$R_2 = 100 \text{ k}\Omega$	$R_1 = 1 \text{ k}\Omega$	$R_F = 250 \text{ k}\Omega$	$R_A = 1 \text{ k}\Omega$
		$V_{in} = 10V$	$R_F = 1 \text{ k}\Omega$	$R_A = 13 \text{ k}\Omega$

Problem 9

$$\epsilon = 8 \times 10^{-4} \Rightarrow \Delta R = \frac{\epsilon R}{K} = \frac{8 \times 10^{-4} \times 300}{6.9 \times 10^{1.5}} = 0.16 \Omega$$


$$V_{out} = \frac{V_{in} \Delta R}{2R + \Delta R} \left( 1 + \frac{2R_F}{R_A} \right) \left( \frac{R_2}{R_1} \right) V_{in}$$

$$V_{out} = \frac{10 \times 0.16}{600.16} \left( 1 + \frac{2 \times 1}{1.3} \right) (100) \times 10$$

$$V_{out} = 6.77 \text{ V}$$

# Problem 10

a)

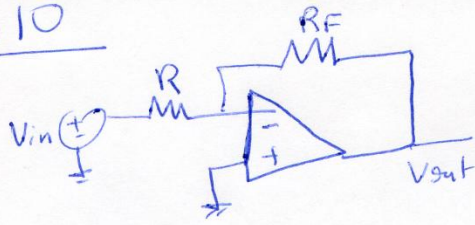


Short  $V_{in}$

$$V_{out\_offset} = \left(1 + \frac{R_F}{R}\right) V_{os} = 4 \times 3mV$$

$$V_{out\_offset} = 12mV$$


b)

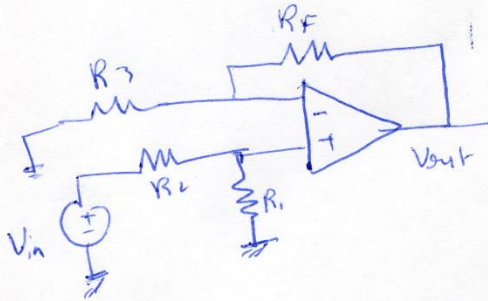

Same as above after shorting  $V_{in}$

$$V_{out\_offset} = 12mV$$

c)

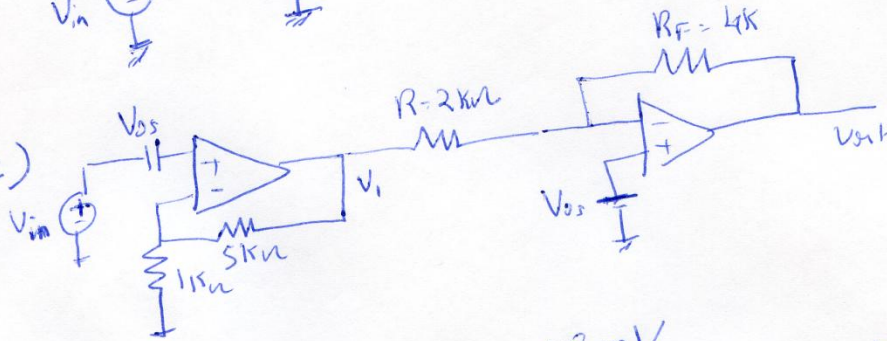

Short  $V_{in} \Rightarrow V_i = \left(1 + \frac{5}{1}\right) 3mV = 18mV$

in 2nd stage apply superposition  $\Rightarrow$


$$V_{out\_offset} = \left(-\frac{R_F}{R} V_i\right) + \left(1 + \frac{R_F}{R}\right) V_{os}$$

$$V_{out\_offset} = -2 \times 18mV + 3 \times 3mV$$

$$V_{out\_offset} = -27mV$$



d)

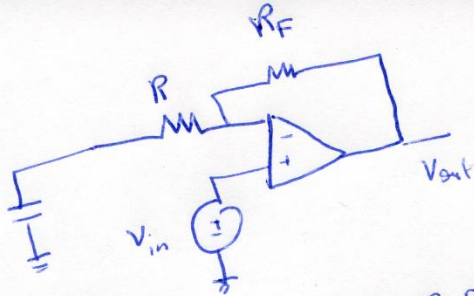

from P13 Lecture 20:  
$$V_{out-offset} = \frac{1 + sC(R+R_F)}{1 + sRC} V_{os}$$

at  $\omega=0$

$$V_{out-offset} = V_{os} = 3mV$$

e)



$$V_{out} = V_{os} = 3mV$$