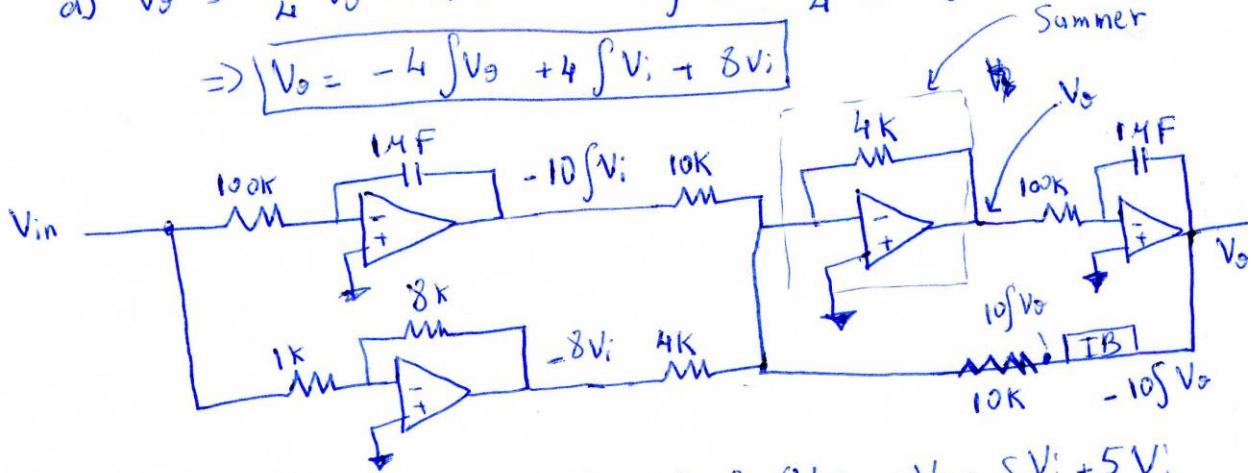


Problem 1

a) $V_o = -\frac{1}{4} V_o' + V_i + 2V_i' \Rightarrow \int V_o = -\frac{1}{4} V_o + \int V_i + 2V_i'$


$\Rightarrow V_o = -4 \int V_o + 4 \int V_i + 8V_i'$



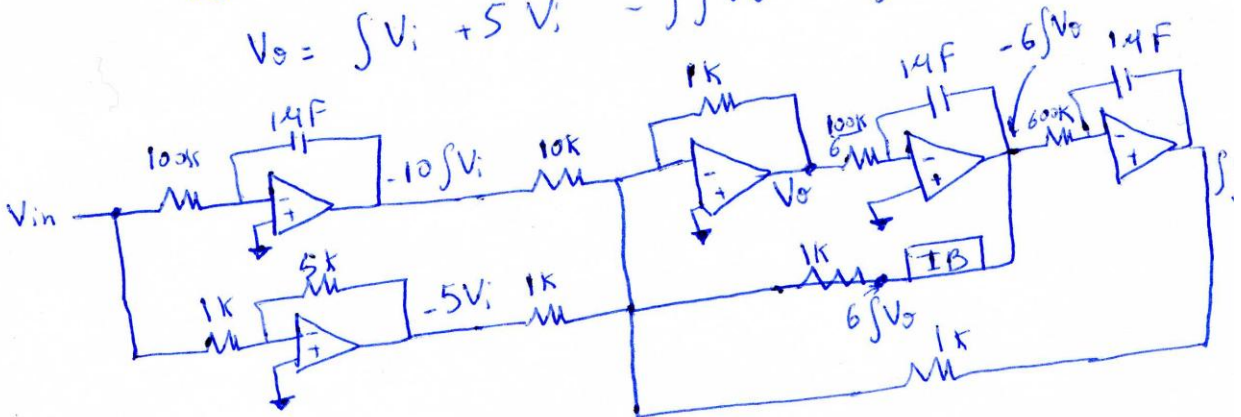b) $T(s) = \frac{s+5}{s^2+6s+1} \Rightarrow V_o(s) s^2 + 6V_o s + V_o = 5V_i + 5V_i'$

$\int \int V_o + 6 \int V_o + V_o = \int V_i + 5V_i'$


$V_o = \int V_i + 5V_i' - \int \int V_o - 6 \int V_o$



IB is an inverting Buffer

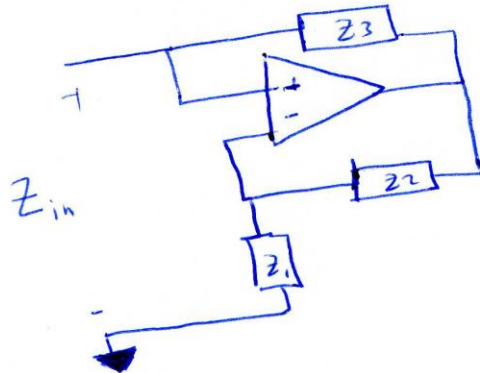Problem 2

$$C = 1\mu F \Rightarrow Z = \frac{1}{sC} = \frac{1}{s \times 10^{-6}} = \frac{10^6}{s}$$




$$Z_{in} = - \frac{Z_1 Z_3}{Z_2}$$

Choose $Z_2 = R_2$ $Z_1 = \frac{1}{sC}$ $Z_3 = R_3 \Rightarrow Z_{in} = - \frac{R_3}{sC R_2}$

choose $C = 1\mu F$ $R_2 = 1k\Omega$ $R_3 = 1k\Omega \Rightarrow Z_{in} = - \frac{10^6}{s}$

We need to invert that to obtain $Z = \frac{10^6}{s}$

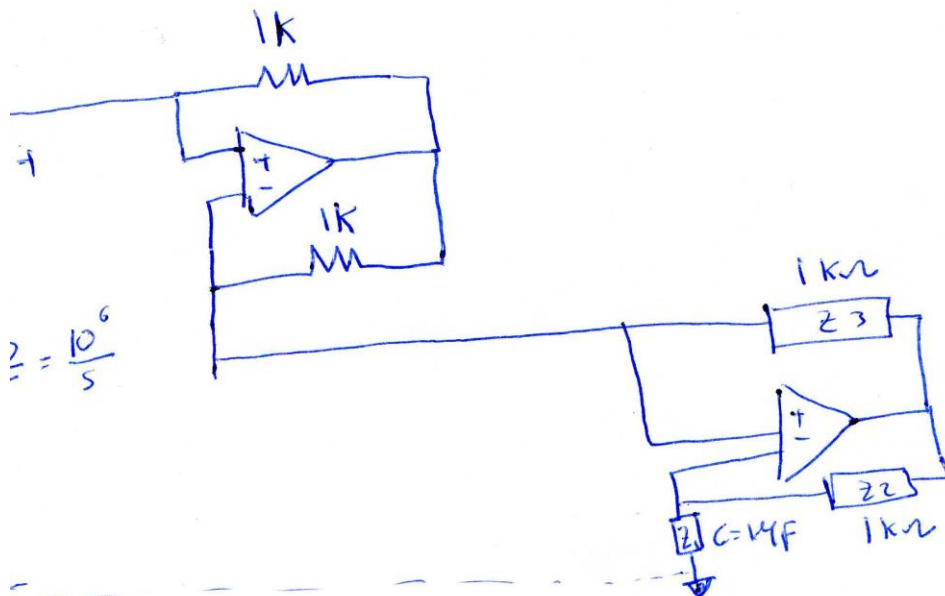

Problem 3

$$V_{in} = 2 \sin(2\pi f t)$$

$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in} = 12 \sin(2\pi f t)$$


$$\frac{dV_{out}}{dt} = 24\pi f \cos(2\pi f t)$$

$$24\pi f \text{ is } SR = 5 \text{ V}/\mu\text{s} = 5 \times 10^6 \text{ V/s}$$

$$f \text{ is } \frac{5 \times 10^6}{24\pi}$$

$$f \text{ is } 66.3 \text{ kHz}$$

Problem 4

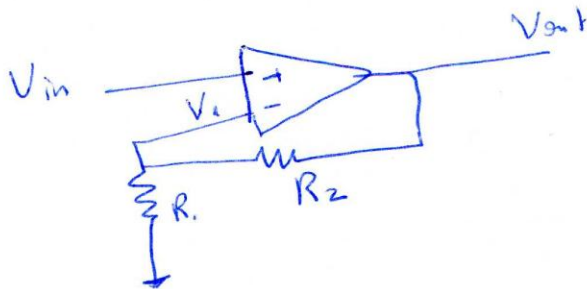

$$(V_{in} - V_i) \frac{GB}{s} = V_{out} \neq$$

$$V_i = V_{out} \frac{R_1}{R_1 + R_2} = \frac{V_{out}}{k_0}$$

$$\Rightarrow V_{out} = \frac{GB}{s} \left(V_{in} - \frac{V_{out}}{k_0} \right)$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = T(s) = \frac{k_0}{1 + s \frac{k_0}{GB}}$$

$$|T(s)| = \frac{k_0}{\sqrt{1 + \frac{\omega^2 k_0^2}{GB^2}}} \quad \angle T(s) = \theta$$


$$\S V_{out}(t) = \frac{k_0}{\sqrt{1 + \frac{\omega^2 k_0^2}{GB^2}}} V_m \sin(\omega t + \theta)$$

$$\frac{dV_{out}(t)}{dt} = \frac{k_0 \omega V_m}{\sqrt{1 + \left(\frac{\omega k_0}{GB}\right)^2}} \cos(\omega t + \theta) \quad \text{if SR}$$

$$\Rightarrow V_m \quad \text{if} \quad \frac{SR \sqrt{1 + \left(\frac{\omega k_0}{GB}\right)^2}}{k_0 \omega}$$

$$\boxed{V_m \quad \text{if} \quad SR \sqrt{\left(\frac{1}{k_0 \omega}\right)^2 + \frac{1}{GB^2}}}$$

Problem 5

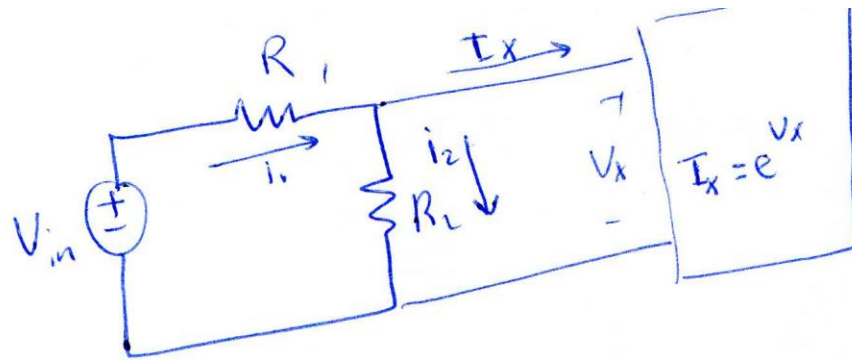


$$I_x = i_1 = i_2$$



$$e^{V_x} = \frac{(V_{in} - V_x)}{R_1} = \frac{V_x}{R_2}$$

$$V_{in} = R_1 e^{V_x} + V_x \left(\frac{R_1}{R_2} + 1 \right)$$

Problem 6

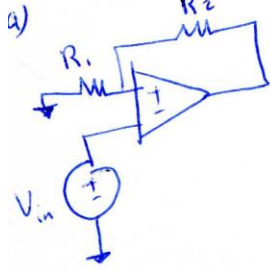
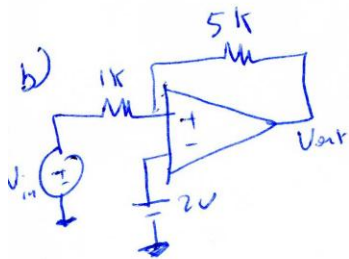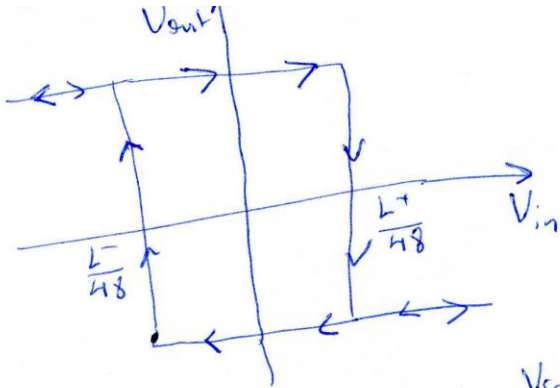
$$G = \frac{R_1}{R_1 + R_2} = \frac{1}{48}$$



Assume $V_{out} = V_{sat-H}$ Valid if $V^+ - V^- > \frac{V_{sat-H}}{A_0}$

$$V^+ = V_{out} \frac{1}{1+5} + V_{in} \frac{5}{1+5} = \frac{V_{out}}{6} + V_{in} \frac{5}{6}$$

$$V^+ = \frac{V_{sat-H}}{6} + \frac{5V_{HYH}}{6} \quad ; \quad V^- = 2V$$

$$V^+ - V^- > \frac{V_{sat-H}}{A_0} \approx 0 \Rightarrow \frac{V_{sat-H}}{6} + \frac{5V_{HYH}}{6} - 2 > 0$$

$$\Rightarrow V_{HYH} = \left(2 - \frac{V_{sat-H}}{6} \right) \frac{6}{5} = 2.4 - \frac{V_{sat-H}}{6}$$

Now Assume $V_{out} = V_{sat-L}$ Valid if $V^+ - V^- < \frac{V_{sat-L}}{A_0} \approx 0$


$$\frac{V_{sat-L}}{6} + \frac{5V_{HYL}}{6} - 2 < 0$$

$$V_{HYL} = \left(2 - \frac{V_{sat-L}}{6} \right) \frac{6}{5} = 2.4 - \frac{V_{sat-L}}{6}$$

Assume $V_{satH} = -V_{sat-L} = 12V$


$$V_{HYH} = 0.4V$$

$$V_{HYL} = 4.4V$$

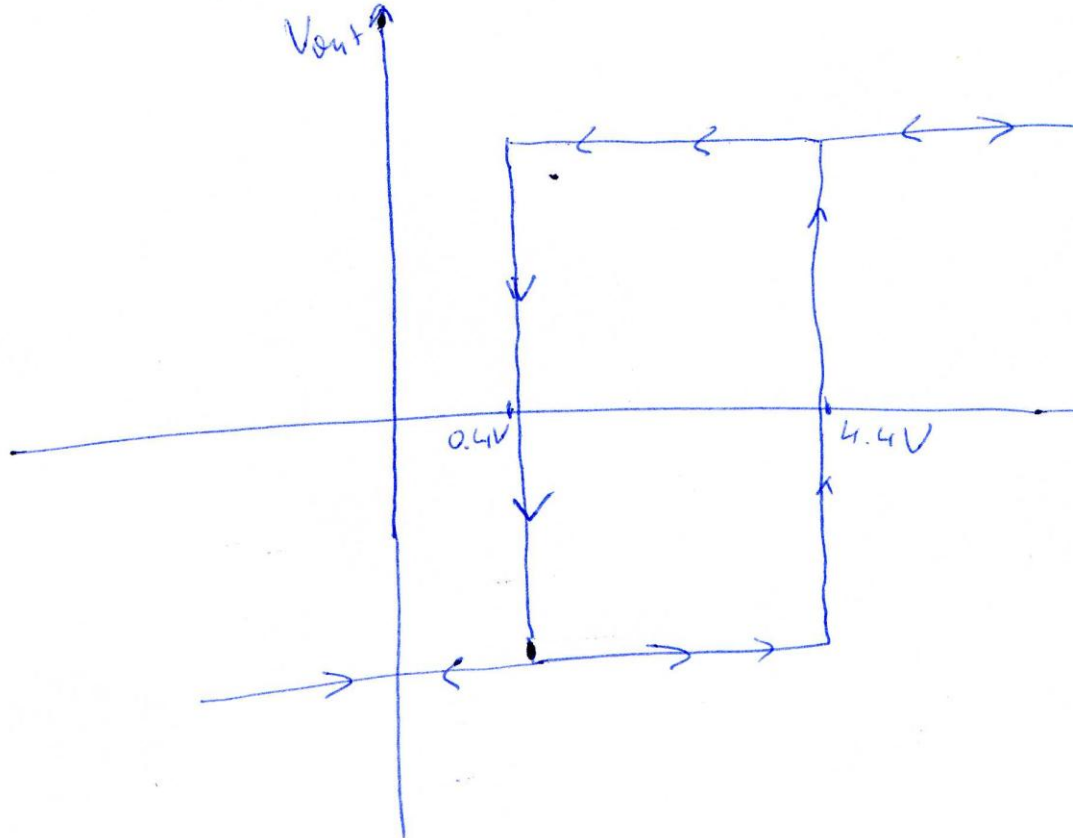

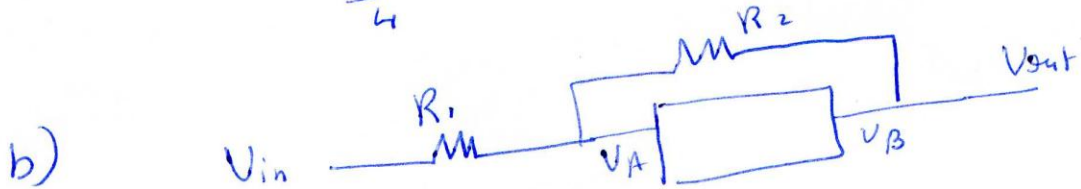Problem 1

$$a) \quad V_B = \begin{cases} -2V & V_A \leq -2V \\ V_A & -2V \leq V_A \leq 2V \\ \frac{V_A+6}{4} & V_A > 2V \end{cases}$$



Assume operation in Region 1 $\Rightarrow V_B = -2V = V_{out}$

$$V_A \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = V_B \left(\frac{1}{R_2} \right) + V_{in} \left(\frac{1}{R_1} \right)$$

$$V_A \left(\frac{1}{4} + 1 \right) = -2 \left(\frac{1}{4} \right) + 1 = \frac{1}{2}$$

$$\Rightarrow \underline{V_A = \frac{2}{5} > -2}$$

Based on this result, our assumption is wrong

No Assume operation in Region 2 $\Rightarrow V_A = V_B = V_{out}$

$$V_A \left(\frac{1}{4} + 1 \right) = \frac{V_A}{4} + 1$$

$$-1V \leq V_A = 1V \leq 2V$$


our assumption is correct $\Rightarrow V_{out} = 1V$

Problem 8

a) $B_{25/85} = 3528k$

b) $R(T) = \begin{cases} 1000 e^{(-12.0596 + \frac{3687.667}{T} - \frac{7617.15}{T^2} + \frac{5.914 \times 10^6}{T^3})} \\ 1000 e^{(-21.07 + \frac{11903.45}{T} - \frac{2504.699}{T^2} + \frac{2.4703 \times 10^8}{T^3})} \end{cases} \Big|_{T=25}^{T=75^\circ C}$

c) At $T = 50^\circ$ $R = 407.37 \Omega$

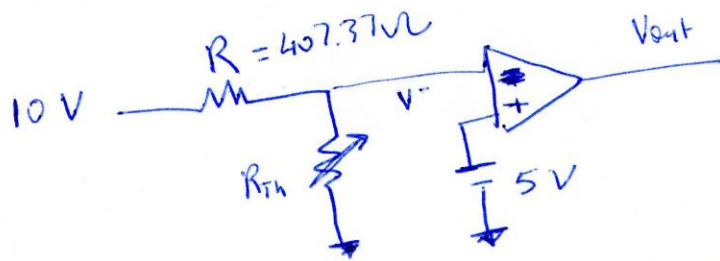




At low temperatures $\Downarrow T < 50^\circ$
 $R_{th} > R \Rightarrow V^- > 5V$
 \Downarrow
 V_{out} is Low

At temperatures $T > 50^\circ C$
 $R_{th} < R \Rightarrow V^- < 5V$
 \Downarrow
 V_{out} is high

At $T = 50^\circ$ $R_{th} = R = 407.37 \Omega$

Problem 9



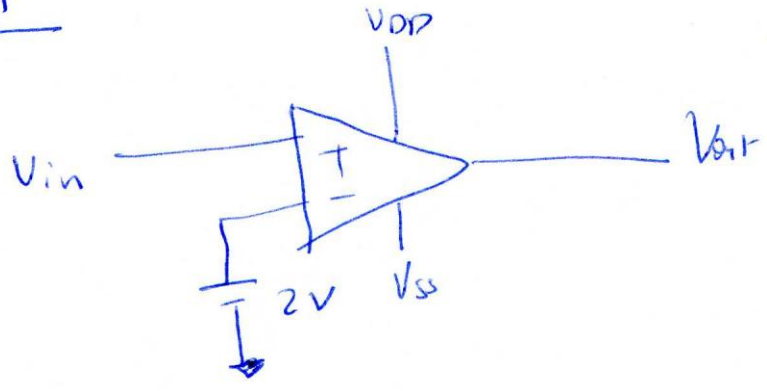


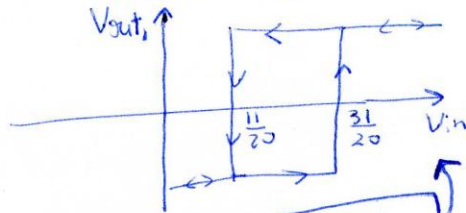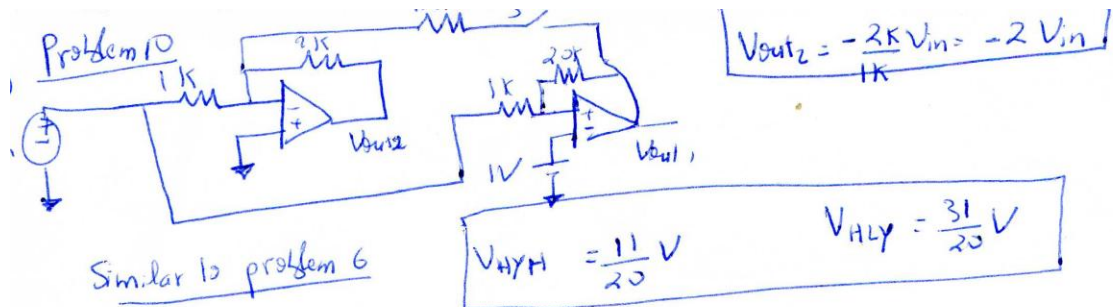

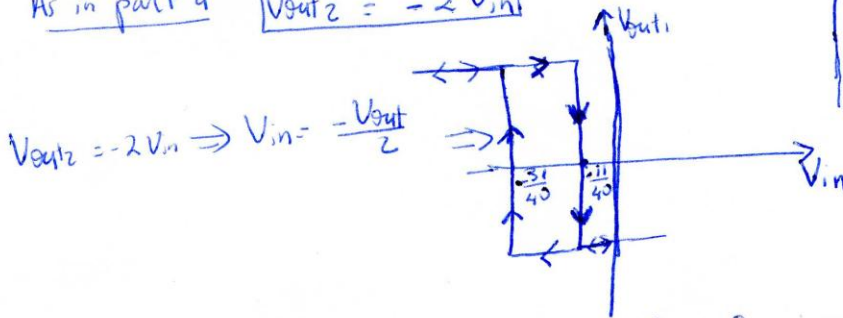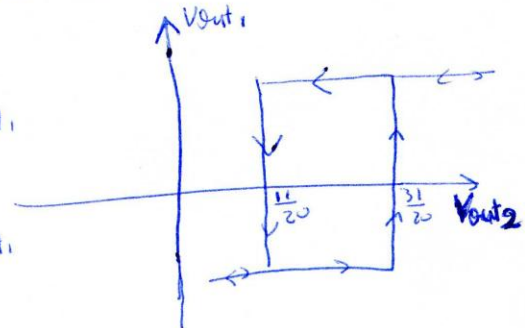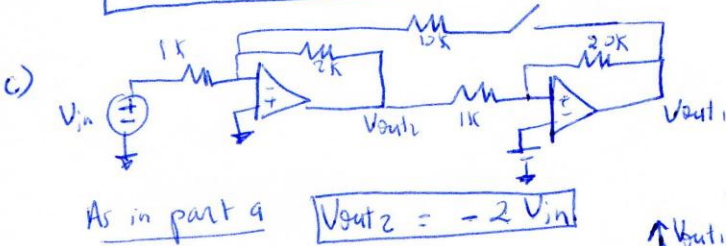b) Now close switch

V_{out1} is same as part a

$$V_{out2} = -\frac{2k}{1k} V_{in} = \frac{10k}{1k} V_{out1} = -2 V_{in} + \left(-\frac{10}{5}\right) V_{out1}$$




Below is Matlab plots for parts a, b and c

```
clear all
close all
```


```
time = -2:0.01:2; % 8 seconds gives us 8 cycles
Vin = [(4*time(1:99)+6), (4*time(100:199)+2), (4*time(200:299)-2), (4*time(300:401)-6)];
```

```
***** part a *****
Vout2 = -2*Vin;
Vout1 = 10*(Vin>31/20)-10*(Vin<31/20);
```



Problem 10 part a

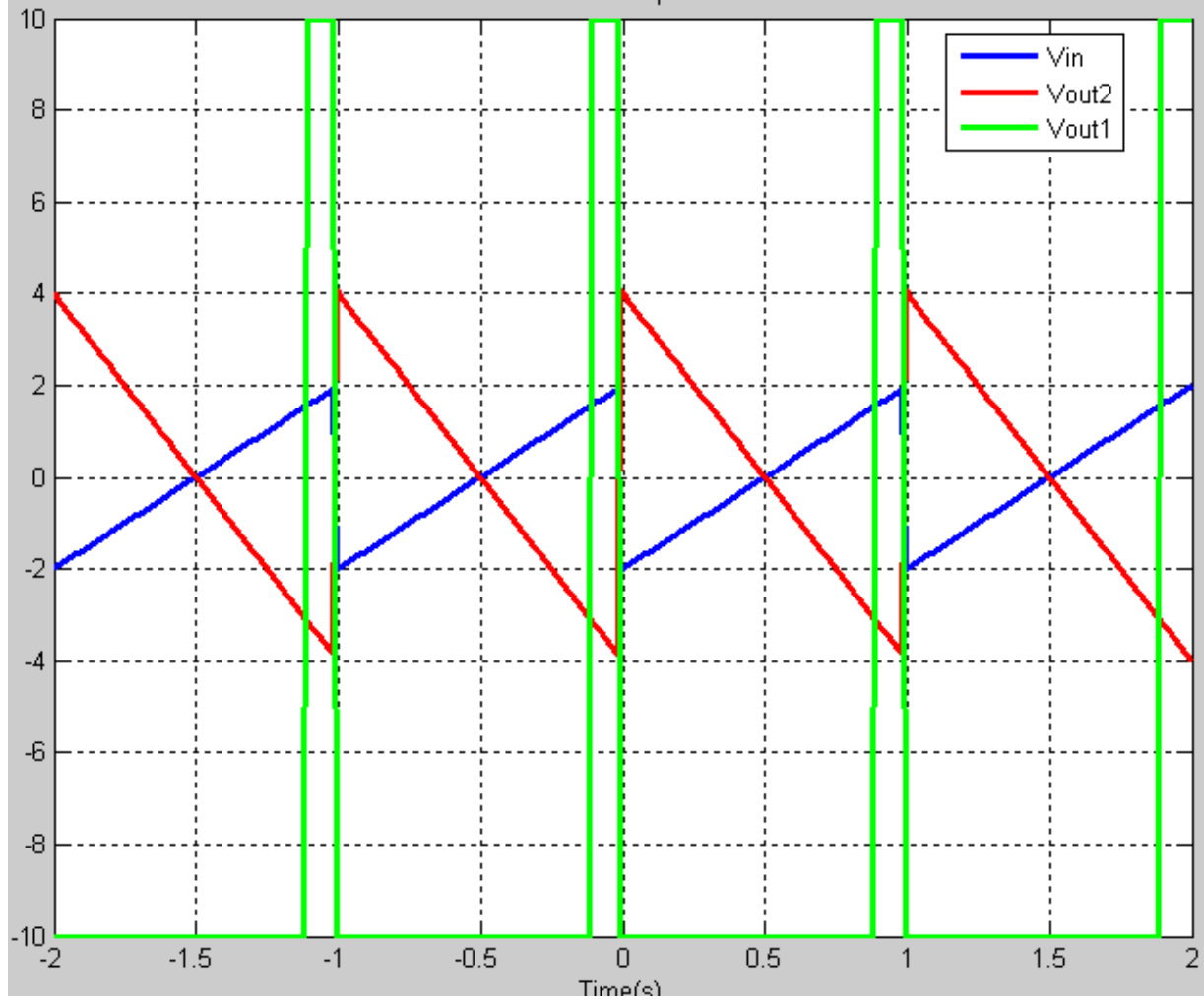


Problem 10 part b

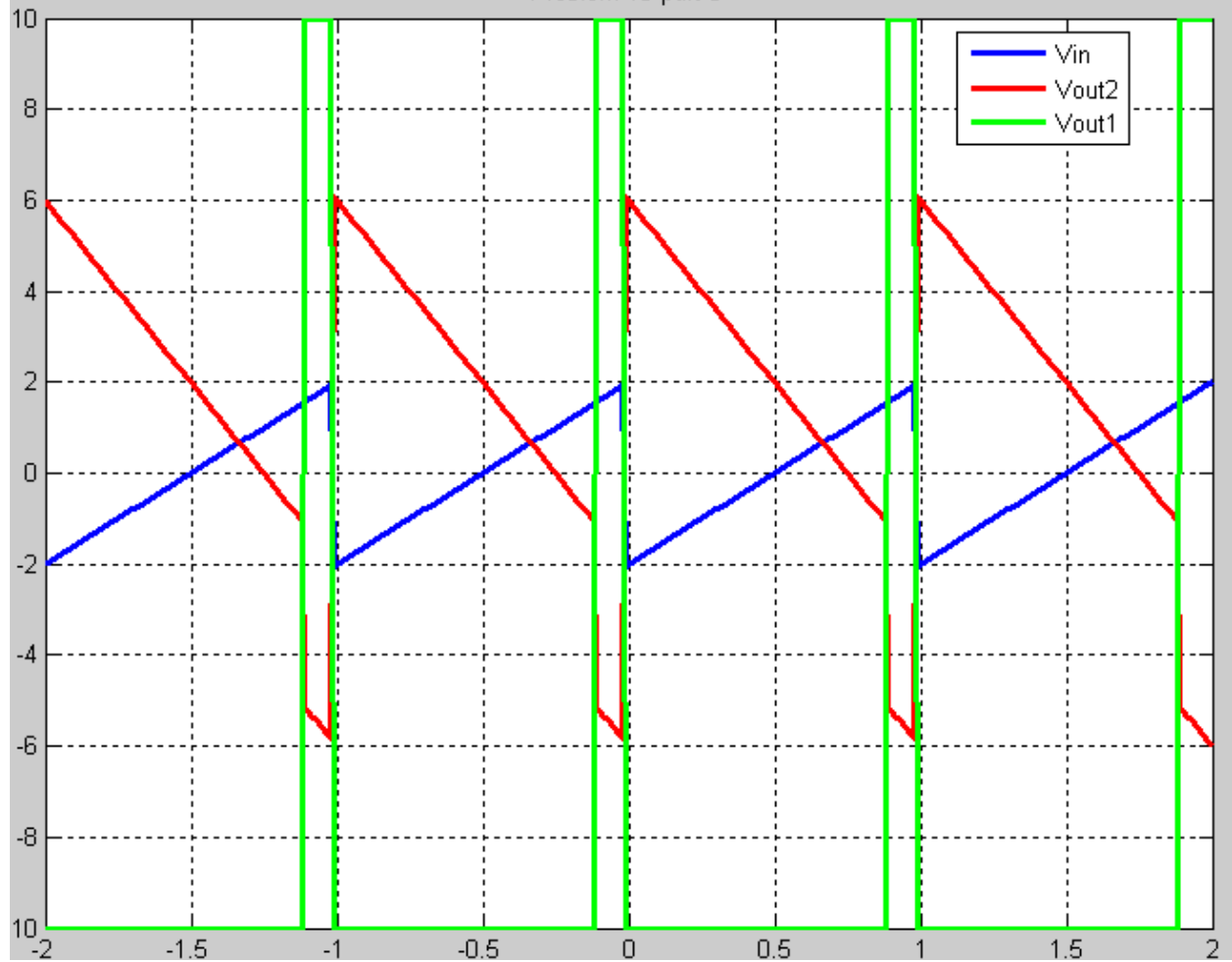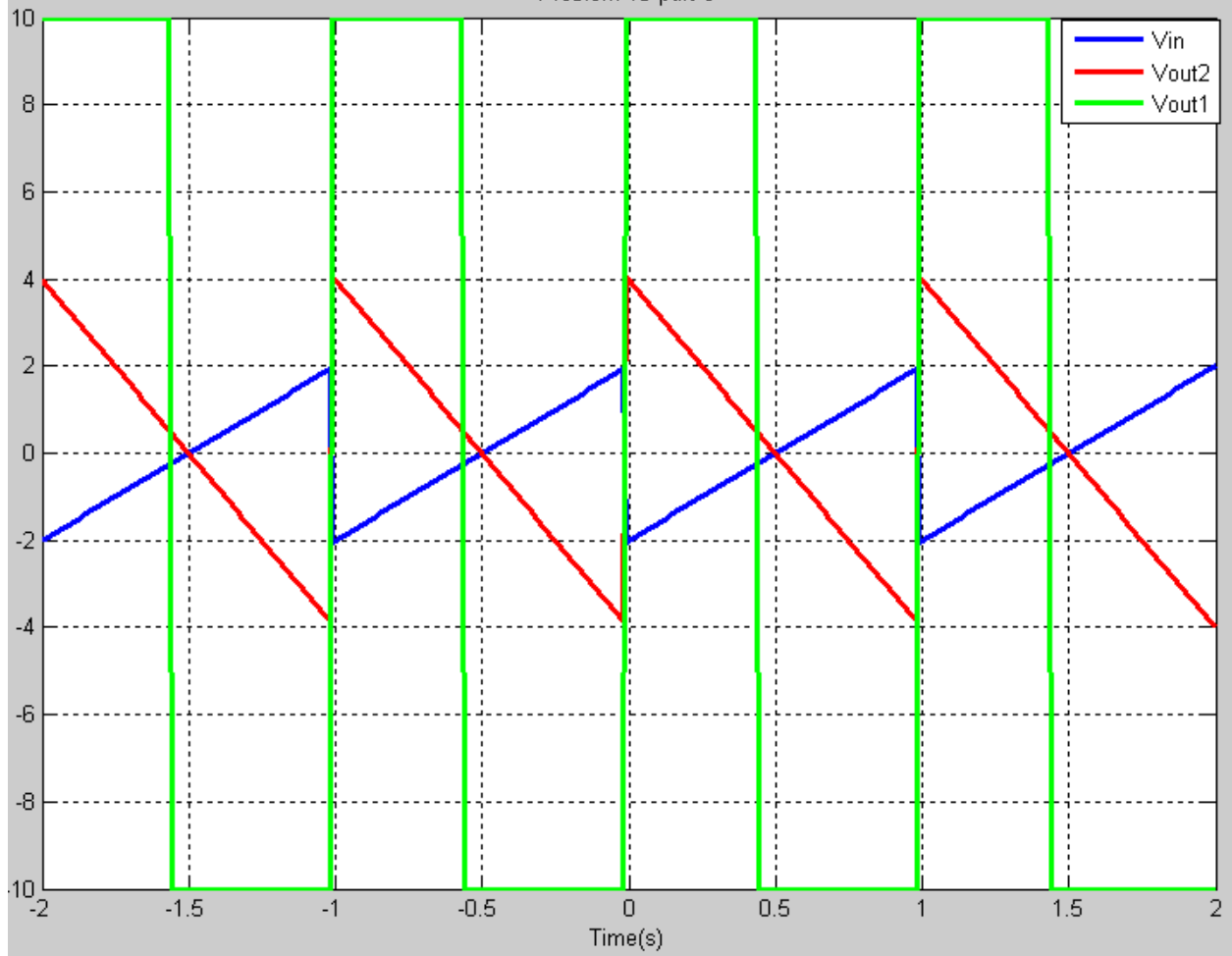


Problem 10 part c



Problem 11

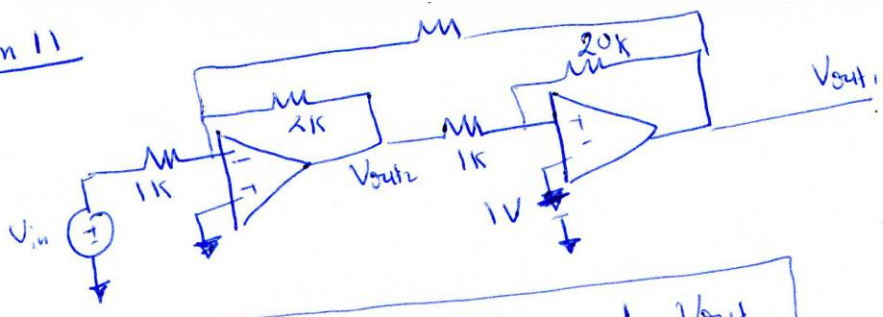
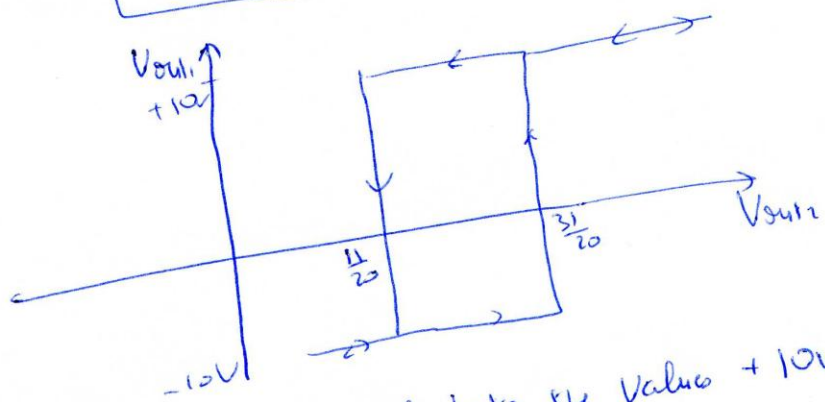
$$V_{out2} = -2V_{in} \quad -\frac{1}{5} V_{out1}$$



Based on the plot V_{out1} can only take the values $+10V$ and $-10V$

Assume $V_{out1} = 10V$

$$\Rightarrow \begin{cases} V_{out2} < \frac{11}{20} & V_{out2} < \frac{31}{20} \\ V_{out2} = -2V_{in} - 2 & V_{out1} = 10 \\ V_{out2} = -2V_{in} + 2 & V_{out1} = -10 \end{cases}$$


Assume $V_{out1} = -10V$

$$\Rightarrow \begin{cases} \frac{11}{20} < V_{out2} < \frac{31}{20} & -\frac{71}{40} < V_{in} < -\frac{51}{40} \text{ case 1} \\ V_{out2} < \frac{11}{20} & V_{in} > -\frac{51}{40} \text{ case 2} \\ V_{out2} > \frac{31}{20} & V_{in} < -\frac{71}{40} \text{ case 3} \end{cases}$$

Only case 2 is valid because $-2 < V_{in} < 2$, however if $V_{out2} < \frac{11}{20}$
 $V_{out1} = -10V \Rightarrow V_{out1}$ can never be $10V$

Therefore $V_{out1} = -10V$ always

Problem 12

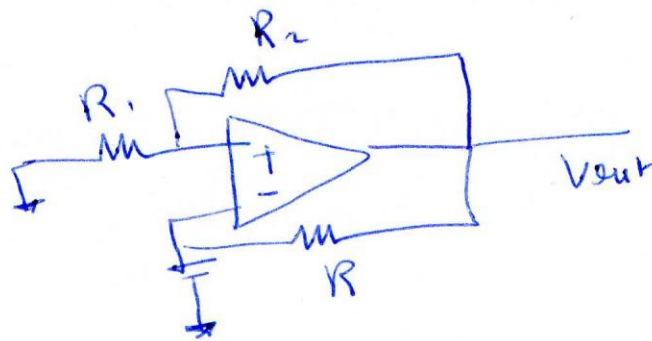

$$f = \frac{1}{2RC} \frac{1}{\ln\left(\frac{1+\phi}{1-\phi}\right)} = 4 \text{ kHz}$$

$$\phi = \frac{R_1}{R_1 + R_2}$$


$$R_1 = R_2 = 1 \text{ k} \Rightarrow \phi = \frac{1}{2}$$

$$4000 = \frac{1}{2RC} \left(\frac{1}{\ln\left(\frac{1.5}{0.5}\right)} \right)$$

$$R_C = 1.1378 \times 10^{-4}$$

Choose	$C = 10 \text{ nF}$	$R = 11.38 \text{ k}\Omega$
--------	---------------------	-----------------------------

Bias op amps at $\pm 10 \text{ V}$

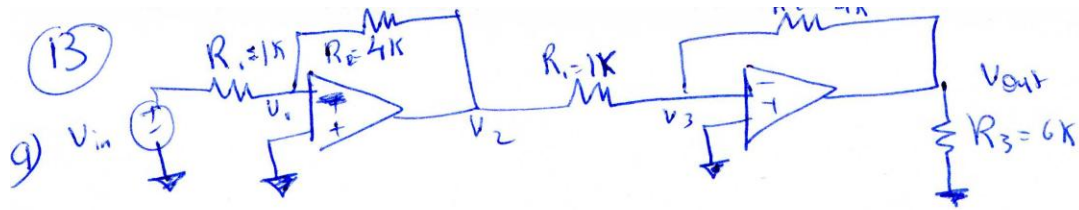


The first stage is an inverting amp $\Rightarrow \frac{V_2}{V_{in}}(s) = \frac{-4}{1 + (1+4)\frac{s}{GB}} = \frac{-\frac{4}{5} GB}{\frac{GB}{5} + s}$

pole at $(-\frac{GB}{5}) = -200\text{kHz} \Rightarrow$ Stable 1st stage

The second stage is also an inverting amp $\Rightarrow \frac{V_{out}}{V_2}(s) = \frac{-\frac{4}{5} GB}{\frac{GB}{5} + s}$ (1)

$\Rightarrow \frac{V_{out}}{V_{in}}(s) = \frac{\frac{16}{25} GB^2}{(\frac{GB}{5} + s)^2} \Rightarrow$ double pole at -200kHz

Therefore, we have a stable system

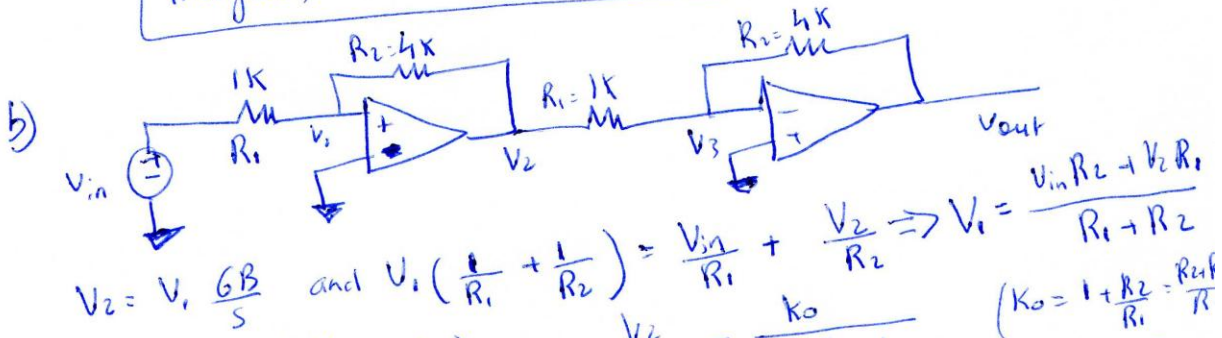


$V_2 = V_1 \frac{GB}{5}$ and $V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_{in}}{R_1} + \frac{V_2}{R_2} \Rightarrow V_1 = \frac{V_{in} R_2 + V_2 R_1}{R_1 + R_2}$

$V_2 = \frac{V_{in} R_2 + V_2 R_1}{R_1 + R_2} \left(\frac{GB}{5} \right) \Rightarrow \frac{V_2}{V_{in}} = \frac{K_0}{K_0 s - 1}$ ($K_0 = 1 + \frac{R_2}{R_1} = \frac{R_2 + R_1}{R_1}$)

$\frac{V_2}{V_{in}} = \frac{5}{\frac{5}{5}s - 1} = \frac{GB}{(s - \frac{GB}{5})}$ using (1) $\Rightarrow \frac{V_{out}}{V_{in}} = \frac{-\frac{4}{5} GB^2}{(s - \frac{GB}{5})(s + \frac{GB}{5})}$

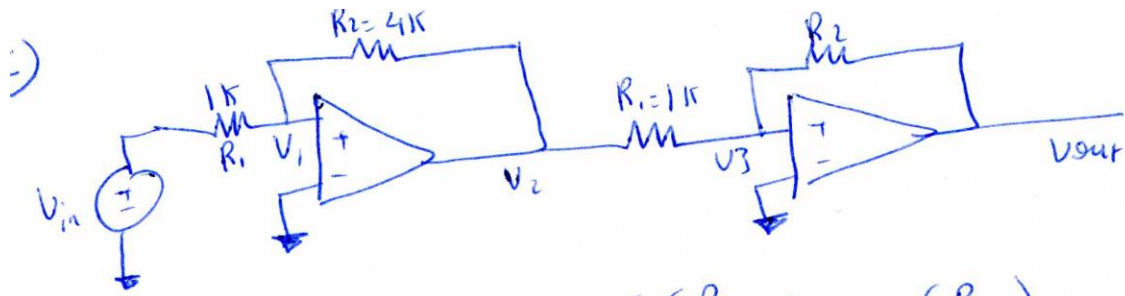1 pole at -200kHz and 1 pole at $200\text{kHz} \Rightarrow$ Unstable




from part B

$$\frac{V_{out}}{V_{in}} = \left(\frac{GB}{s - \frac{GB}{s}} \right) \left(\frac{GB}{s - \frac{GB}{s}} \right)$$

2 poles at $\frac{GB}{s} = 200 \text{ kHz} \Rightarrow$ not stable

problem 4

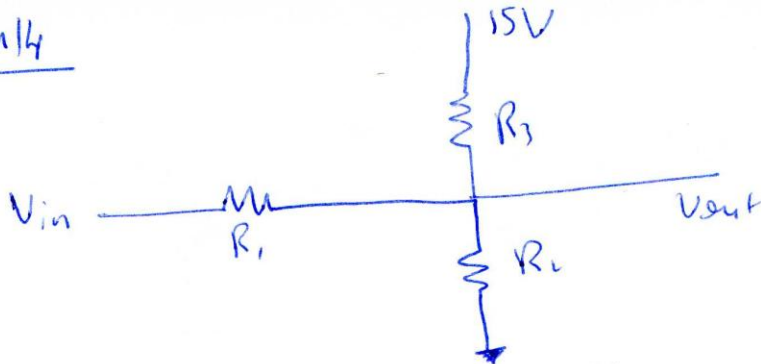

$$\frac{V_{out} - 15}{R_3} + \frac{V_{out} - V_{in}}{R_1} + \frac{V_{out}}{R_2} = 0 \quad (\text{KCL})$$

$$\textcircled{1} \left\{ \begin{aligned} \frac{-10}{R_3} + \frac{-10}{R_1} + \frac{5}{R_2} &= 0 \\ \frac{-15}{R_3} + \frac{15}{R_1} &= 0 \end{aligned} \right.$$

$$V_{out} = 5V \quad V_{in} = 15$$

$$V_{out} = 0V \quad V_{in} =$$

let $R_1 = R_3$

solve ① $\Rightarrow R_2 = 1k\Omega \quad R_1 = 4k\Omega \quad R_3 = 4k\Omega$