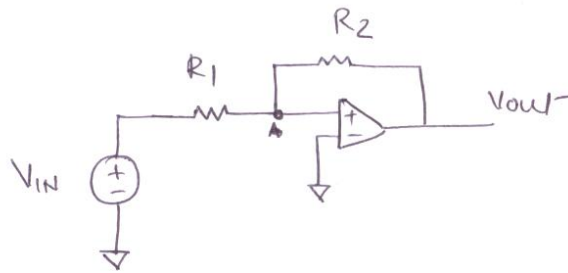


1.



$$R_2 = 10k \quad R_1 = 100\Omega$$

$$V_t = V_{IN} \frac{R_2}{R_1 + R_2} + V_{out} \frac{R_1}{R_1 + R_2} \quad \text{--- (1)}$$

If circuit is in positive stable state ( $V_{out} = L_+$ ),  $V_{in}$  must be made negative to trigger it to ( $V_{out} = L_-$ ) state. For such value of  $V_{in}$ ;  $V_t = 0$ . Thus putting  $V_{out} = L_+ = 15$  in eqn (1)

$$0 = V_{in} \frac{10000}{10100} + 15 \cdot \frac{100}{10100}$$

$$\Rightarrow V_{in} = -\frac{1500}{10000} = -0.15 \text{ V} = V_{TL} \quad \text{--- (2)}$$


similarly for getting  $V_{TH}$ , we put  $V_{out} = L_- = -15$  V in eqn (1)

$$0 = V_{in} \cdot \frac{10000}{10100} - 15 \cdot \frac{100}{10100}$$


$$\Rightarrow V_{in} = +0.15 \text{ V} = V_{TH} \quad \text{--- (3)}$$

Hence

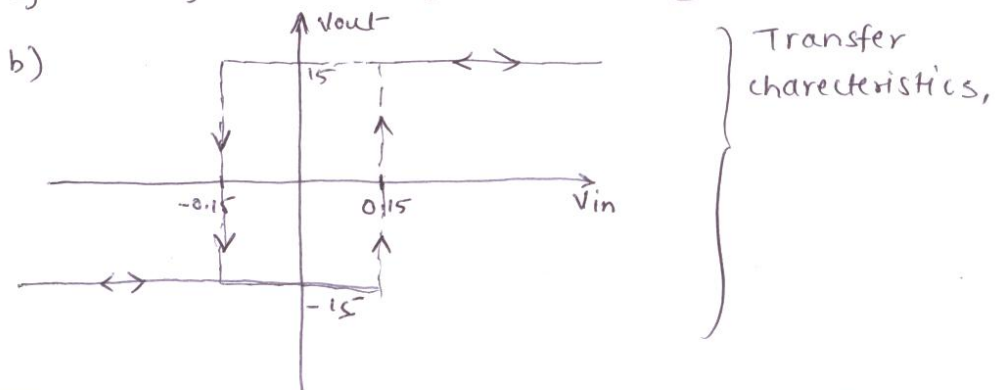
a) width of hysteresis region =  $V_{TH} + V_{TL} = 0.3 \text{ V}$



2.

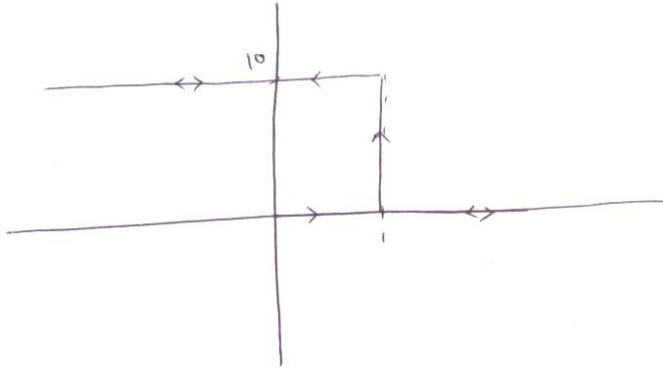

It is an inverting comparator

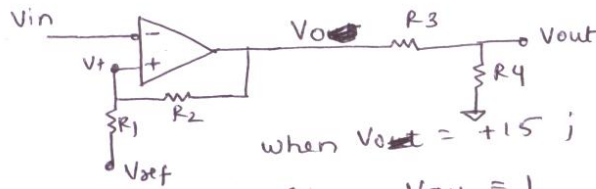

when  $V_{out} = +15$ ;  $V_{in} = V_{TH}$  will flip it to  $-15$   
Given  $V_{TH} = 1$

$\Rightarrow$   ~~$V_{in} = V_{TH}$~~   $\frac{V_0 - V_+}{R_2} = \frac{V_+ - V_{ref}}{R_1}$

$$\Rightarrow \frac{15 - 1}{R_2} = \frac{1 - V_{ref}}{R_1} \Rightarrow \frac{14}{1 - V_{ref}} = \frac{R_2}{R_1} \quad \dots 1)$$

when  $V_{out} = -15$ ;  $V_{in} = V_{TL}$  will flip it to  $+15$

Given  $V_{TL} = 0$

$$\frac{-15 - 0}{R_2} = \frac{0 - V_{ref}}{R_1} \Rightarrow \frac{15}{R_2} = \frac{V_{ref}}{R_1}$$

$$\Rightarrow \frac{R_2}{R_1} = \frac{15}{V_{ref}} \quad \dots 2)$$

from 1) and 2)

$$\frac{14}{1 - V_{ref}} = \frac{15}{V_{ref}} \Rightarrow 14 V_{ref} = 15 - 15 V_{ref}$$
$$V_{ref} = \frac{15}{29} \text{ Volts}$$

2 cont'd


$$\Rightarrow \frac{R_2}{R_1} = 29$$

$\Rightarrow R_2 = 29 \text{ K}$  and  $R_1 = 1 \text{ K}$  should work.

Now final output is 10V which can be obtained by a voltage divider with


$$\frac{R_4}{R_3 + R_4} = \frac{10}{15}$$

3.

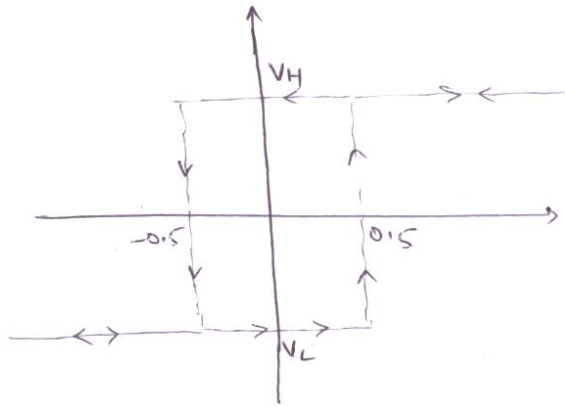

Given:-  $V_{TH} = 0.5 \text{ V}$      $V_{TL} = -0.5 \text{ V}$

The comparator is non-inverting,

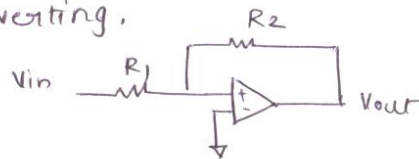

$$V_{TL} = -V_H \cdot \frac{R_1}{R_2}$$

Assume  $V_H = 15 \text{ V}$

$V_L = +15 \text{ V}$

$$\Rightarrow -0.5 = -15 \cdot \frac{R_1}{R_2} \Rightarrow \frac{R_1}{R_2} = \frac{0.5}{15} = \frac{1}{30}$$


Hence  $R_1 = 100 \Omega$      $R_2 = 3000 \Omega$  is a solution,

Let us check if this value works for  $V_{TH} = 0.5$

$$V_{TH} = -V_L \left( \frac{R_1}{R_2} \right)$$

$$0.5 = 15 \cdot \frac{100}{3000} = 0.5 \quad (\text{Thus verified})$$

4.

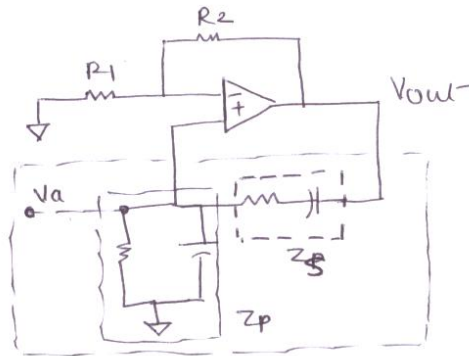

The loop gain for the above circuit can be obtained by multiplying  $\frac{V_a(s)}{V_o(s)}$  by amplifier gain which is  $1 + \frac{R_2}{R_1}$

$$L(s) = \left[ 1 + \frac{R_2}{R_1} \right] \frac{Z_P}{Z_P + Z_S}$$

On simplifying

$$L(s) = \frac{1 + R_2/R_1}{3 + sCR + 1/sCR} = \frac{(1 + R_2/R_1) sCR}{s^2 R^2 C^2 + 3sCR + 1}$$

characteristic eqn is  $s^2 R^2 C^2 + 3sCR + 1 = 0$  ~~+~~  $\left( \frac{1 + R_2}{R_1} \right) sCR$

~~poles~~;


$$\Rightarrow s^2 R^2 C^2 + sRC \left[ 3 - \left( 1 + \frac{R_2}{R_1} \right) \right] + 1 = 0$$

but  $\frac{R_2}{R_1} = 2$  (Given)

$$\Rightarrow s^2 R^2 C^2 + 1 = 0 \quad \left. \vphantom{s^2 R^2 C^2 + 1 = 0} \right\} \text{characteristic equation}$$

$$s = \pm \frac{1}{RC} \quad (\text{poles})$$

5.

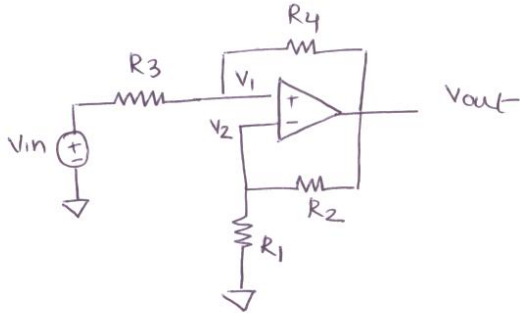

$$V_1 \left( \frac{1}{R_3} + \frac{1}{R_4} \right) = \frac{V_{in}}{R_3} + \frac{V_{out}}{R_4} \quad \text{--- 1)}$$

$$V_2 = \frac{R_1}{R_1 + R_2} \cdot V_{out} \quad \text{--- 2)}$$

$$V_{out} = \frac{G_B}{s} (V_1 - V_2) \quad \text{--- 3)}$$

from 2 and 3

$$V_{out} \left( 1 + \frac{G_B}{s} \frac{R_1}{R_1 + R_2} \right) = \frac{G_B}{s} V_1$$

from 1)

$$V_{out} \left( 1 + \frac{G_B}{s} \frac{R_1}{R_1 + R_2} \right) = \frac{G_B}{s} \left( \frac{\frac{V_{in}}{R_3} + \frac{V_{out}}{R_4}}{\frac{1}{R_3} + \frac{1}{R_4}} \right)$$

$$\Rightarrow V_{out} \left[ \frac{s}{G_B} + \frac{R_1}{R_1 + R_2} \right] = \frac{R_4 V_{in} + R_3 V_{out}}{R_3 + R_4}$$

putting given values for  $R_1, R_2, R_3$

$$V_{out} \left[ \frac{s}{G_B} + \frac{1}{6} \right] = \frac{R_4 V_{in}}{1 + R_4} + \frac{V_{out}}{1 + R_4}$$

$$V_{out} = \left[ \frac{R_4 / (1 + R_4)}{\frac{s}{G_B} + \frac{1}{6} - \frac{1}{1 + R_4}} \right] V_{in} \quad \text{--- ans a)}$$

For stability pole  $< 0$

$$2) \quad \frac{1}{6} - \frac{1}{1+R_4} > 0$$

$$\Rightarrow 1+R_4 > 6$$

$$R_4 > 5 \text{ K}, \quad \text{--- ans b)}$$


$$\text{if } R_4 = 0.5 R_{4\text{min}}$$

$$R_4 = 2.5 \text{ K}$$


$$\Rightarrow V_{\text{out}} = \frac{2.5/3.5}{\frac{s}{6} + \frac{1}{6}} V_{\text{in}}$$

o

Transfer characteristics.

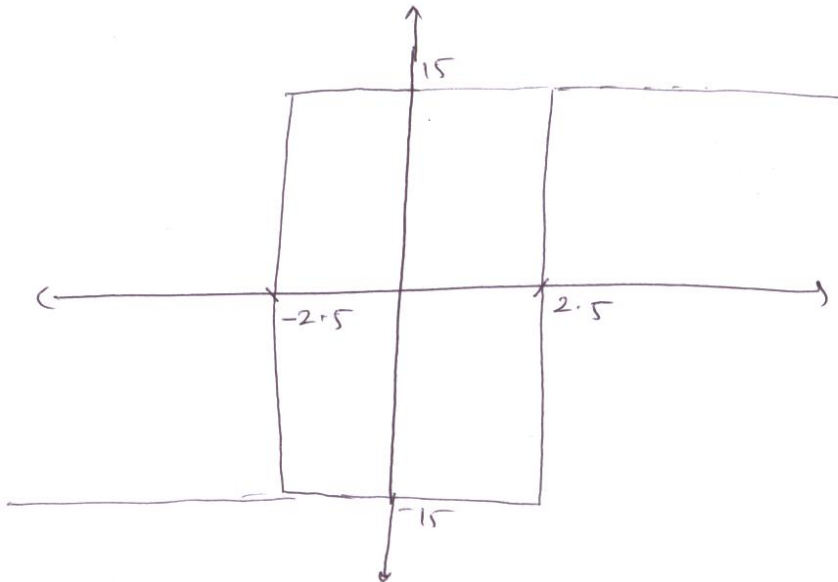

6. a)

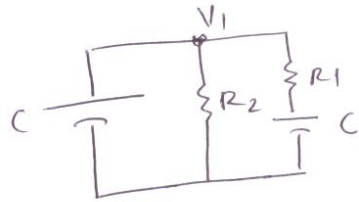

Applying KCL

$$V_1 \left( sC + \frac{1}{R_2} + \frac{1}{R_1 + \frac{1}{sC}} \right) = 0$$

$$\Rightarrow sCR_2 \left( R_1 + \frac{1}{sC} \right) + R_1 + \frac{1}{sC} + R_2 = 0$$


$$\Rightarrow sCR_1R_2 + R_2 + R_1 + \frac{1}{sC} + R_2 = 0$$

$$\Rightarrow s^2 C^2 R_1 R_2 + (R_1 + 2R_2)Cs + 1 = 0$$

$$s = \frac{-(R_1 + 2R_2) \pm C \sqrt{R_1^2 + 4R_2^2}}{2C^2 R_1 R_2}$$

both poles in LHP, hence stable.

b)

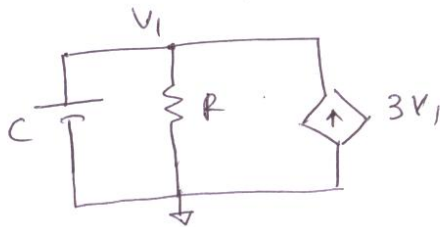

Applying KCL.


$$3V_1 = V_1 \left( \frac{1}{R} + sC \right)$$

$$3 = sC + \frac{1}{R} \Rightarrow s = \frac{1}{C} \left( 3 - \frac{1}{R} \right)$$

Can be stable or unstable depending on R.



(c)

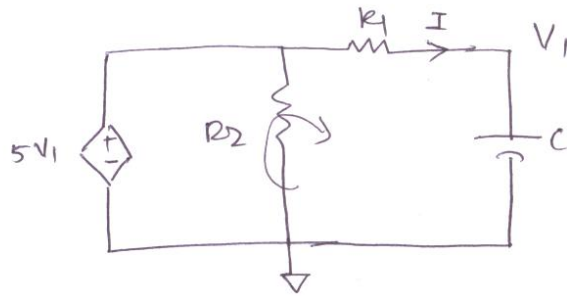

Applying KVL in outer loop

$$5V_1 - IR_1 - \frac{I}{sC} = 0$$

$$I = \frac{5V_1}{R_1 + \frac{1}{sC}}$$


$$V_1 = 0 + \frac{I}{sC} = \frac{5V_1}{sC(R_1 + \frac{1}{sC})} = \frac{5}{sRC + 1} V_1$$

$$2) \quad sRC + 1 = 5$$

$$s = \frac{4}{RC}$$

Pole in RHP  $\Rightarrow$  unstable.

d)

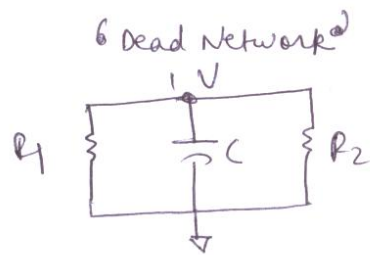


KCL at Node 1

$$\frac{V}{R_1} + \frac{V}{R_2} + V s C = 0$$

$$V \left[ s C + \frac{1}{R_1} + \frac{1}{R_2} \right] = 0$$

- stable.

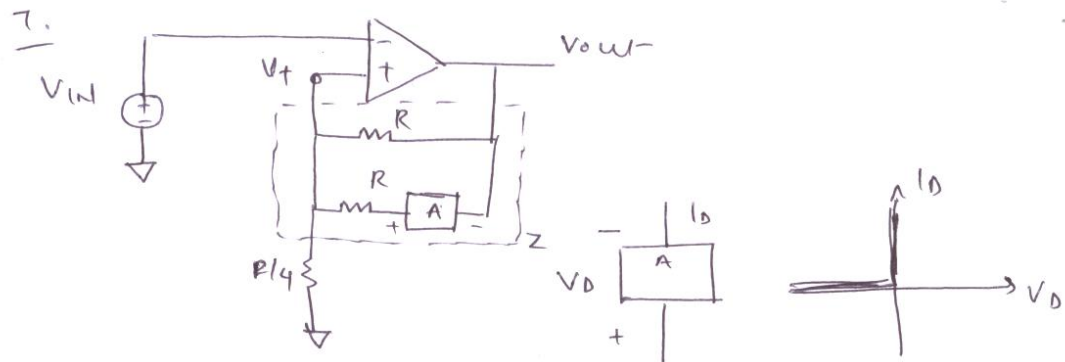

The component is open-ckt for  $V_D < 0$  while it is short ckt for  $V_D \geq 0$ .

clearly, above circuit is inverting comparator

for  $V_{out} = V_{SAT H}$

$$V_+ = \frac{R_{14}}{R_{14} + Z} V_{out} < V_{out} \quad (V_{out} > 0)$$

$\Rightarrow V_D$  across component  $A$  is negative  
 $\Rightarrow Z = R$

$$V_+ = \frac{R_{14} V_{out}}{R_{14} + R} = \frac{R}{5R} V_{out} = \frac{V_{out}}{5} = \frac{V_{SAT H}}{5}$$

$\Rightarrow V_{in} > \frac{V_{SAT H}}{5}$  will flip  $V_{out}$  to  $V_{SAT L}$

$$\Rightarrow V_{TH} = \frac{V_{SAT H}}{5}$$

for  $V_{out} = V_{SAT L}$

$$V_+ = \frac{R_{14}}{R_{14} + Z} V_{out} > V_{out} \quad (V_{out} < 0)$$

$\Rightarrow V_D$  across component  $A$  is +ve

$$2) z = R \parallel R = R/2$$


$$\Rightarrow V_T = \frac{R/4 \cdot V_{out}}{R/4 + R/2} = \frac{R}{3R} \cdot V_{out}$$


$$V_T = \frac{V_{out}}{3} = \frac{V_{SATL}}{3}$$

2) for  $V_{in} < \frac{V_{SATL}}{3}$ , output will flip to  $V_{SATH}$

$$\Rightarrow V_{TL} = \frac{V_{SATL}}{3}$$

Hence Transfer characteristics

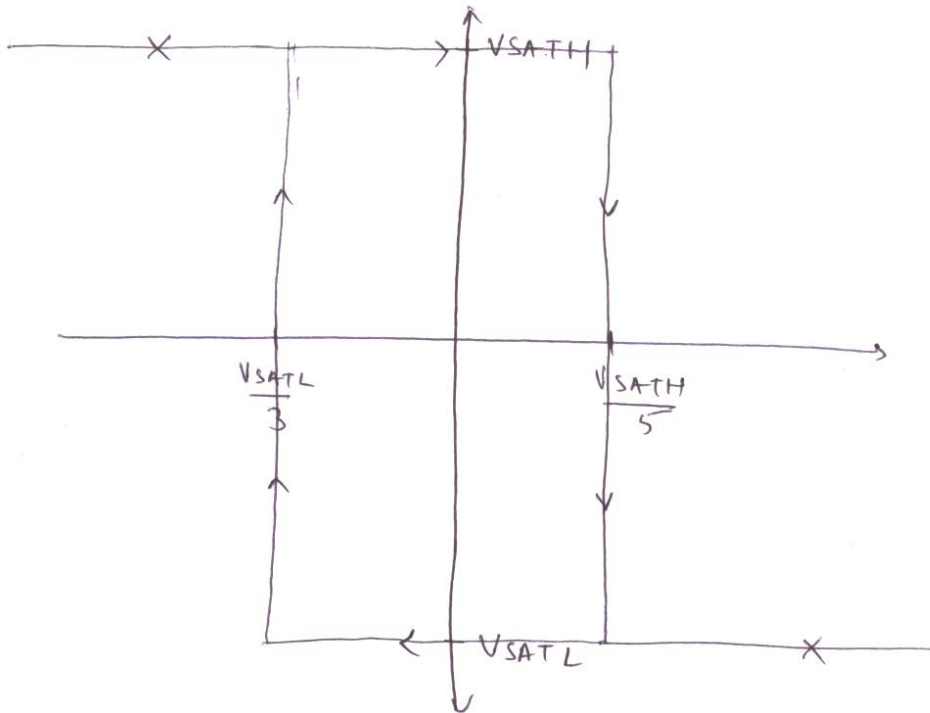

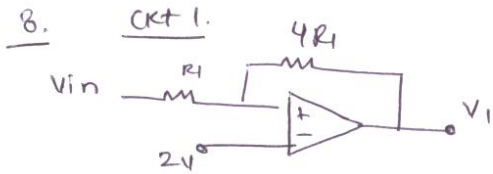

It is a non inverting comparator.


$$V_{TH} = \frac{-V_{SATL} + V_{ref}}{R_2} + V_{out}$$

$$= 5.5 \text{ V}$$


$$V_{TL} = -\left(\frac{V_{SATLH} - V_{ref}}{R_2}\right) + V_{out}$$

$$= -0.5 \text{ V}$$

characteristic

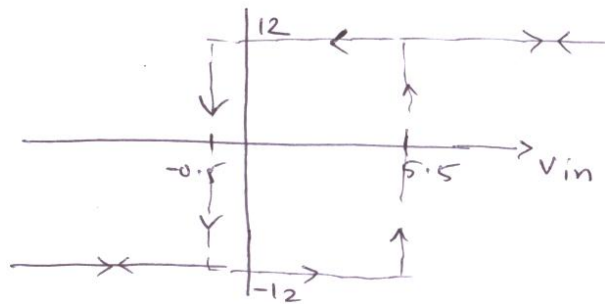

Ckt 2. (Inverting Comparator)

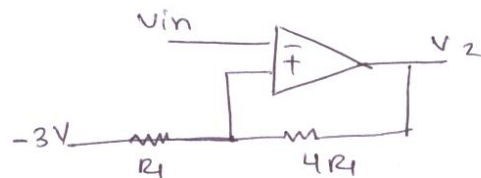


$$V_+ = \frac{R_1}{5R_1} (V_2 + 3) - 3$$

$$= \frac{V_2 + 3}{5} - 3$$


$$V_+ = \frac{V_2 - 12}{5}$$

$$\Rightarrow V_{TH} = 0 ; V_{TL} = -\frac{24}{5} = -4.8 \text{ V}$$

⇒ Transfer characteristics for ckt 2

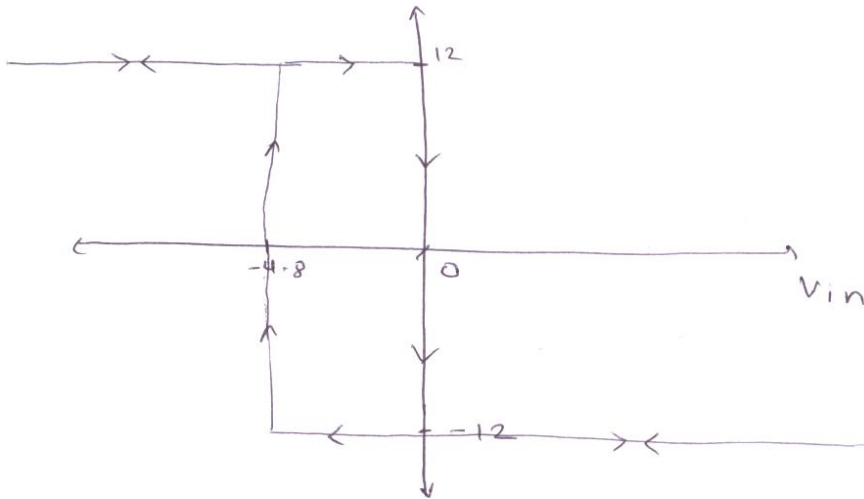

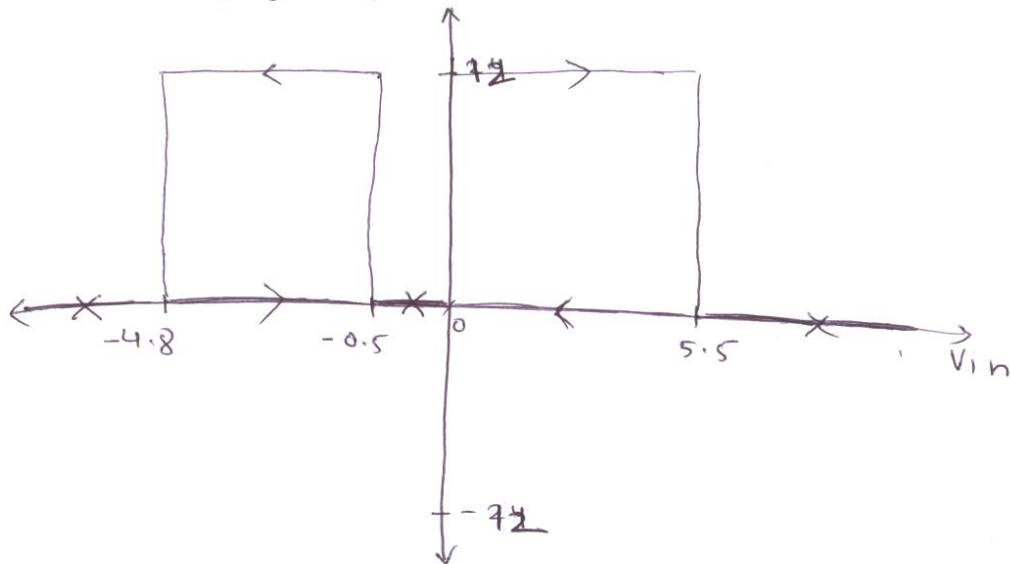Third opamp is just a <sup>inverting</sup> summer. Thus overall transfer characteristics can be obtained by adding 2 curves, and multiplying by (-1)




9.

Errata:

~~V<sub>sat</sub> = 15V~~

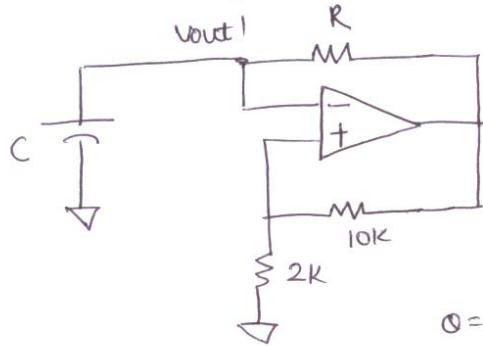Required P-P Value of V<sub>out</sub> = 4V.



$$\theta = \frac{2}{12} = \frac{1}{6}$$

$$f = \frac{1}{2RC} \cdot \frac{1}{\ln\left(\frac{1+\theta}{1-\theta}\right)}$$

$$2000 = \frac{1}{2RC} \cdot \frac{1}{\ln\left(\frac{7}{5}\right)}$$

$$RC = 7.43 \times 10^{-4}$$

take C = 1μf

$$R = 7.43 \times 10^2 \Omega$$