

P1. Case I, assume  $I_D = 0$ ,  $\Rightarrow V_D \leq 0$

$$\begin{cases} V_{out} = \left(1 + \frac{20k}{2k}\right) \cdot V_{in} \\ V_D = V_{out} - V_{in} \end{cases} \Rightarrow \begin{aligned} V_{out} &= 11V_{in} \\ V_D &= 10V_{in} \end{aligned}$$

$$\begin{cases} V_D \leq 0 \\ V_D = 10V_{in} \end{cases} \Rightarrow V_{in} \leq 0$$


$$\therefore \text{When } V_{in} \leq 0 \quad \frac{V_{out}}{V_{in}} = 11$$

Case II. assume  $V_D = 0 \Rightarrow I_D > 0$

$$\begin{cases} V_{out} = \left(1 + \frac{20k \parallel 5k}{2k}\right) \cdot V_{in} \\ I_D = \frac{V_{out} - V_{in}}{5k} \end{cases} \Rightarrow V_{out} = 3V_{in}$$

$$I_D = \frac{V_{out} - V_{in}}{5k} > 0 \Rightarrow \frac{2V_{in}}{5k} > 0 \Rightarrow V_{in} > 0$$
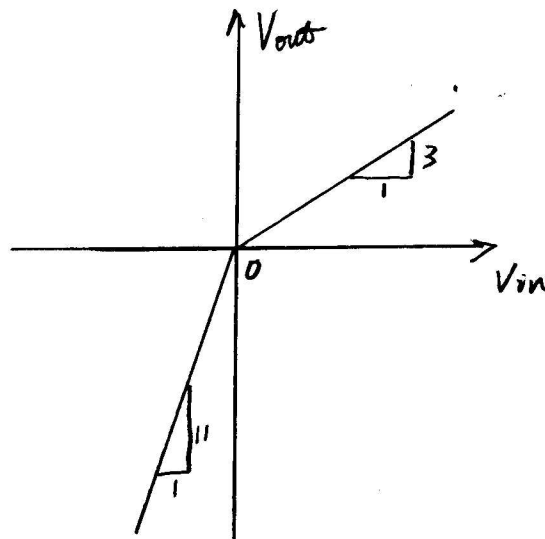
$$\therefore \text{When } V_{in} > 0 \quad \frac{V_{out}}{V_{in}} = 3$$



P2. Case I, assume  $I_D = 0 \Rightarrow V_D \leq 0$

$$\begin{cases} V_{out} = \left(1 + \frac{20k}{2k}\right) \cdot V_{in} \\ V_D = V_{in} - V_{out} \end{cases} \Rightarrow \begin{aligned} V_{out} &= 11 V_{in} \\ V_D &= -10 V_{in} \end{aligned}$$

$$\begin{cases} V_D = -10 V_{in} \\ V_D \leq 0 \end{cases} \Rightarrow V_{in} \geq 0$$


$$\therefore \text{when } V_{in} \geq 0, \frac{V_{out}}{V_{in}} = 11$$

Case II, assume  $V_D = 0 \Rightarrow I_D > 0$

$$\begin{cases} V_{out} = \left(1 + \frac{20k // 5k}{2k}\right) \cdot V_{in} \\ I_D = \frac{V_{in} - V_{out}}{5k} \end{cases} \Rightarrow V_{out} = 3 V_{in}$$

$$I_D = -\frac{2 V_{in}}{5k} > 0 \Rightarrow V_{in} < 0$$
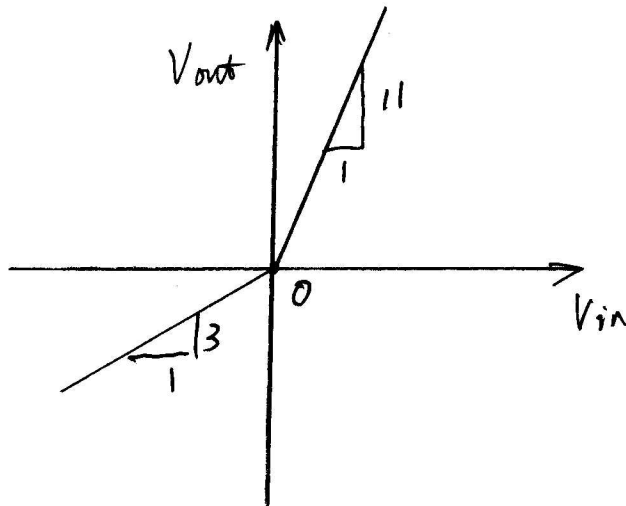
$$\therefore \text{when } V_{in} < 0, \frac{V_{out}}{V_{in}} = 3$$



P3, Case I assume  $D_1$  On  $D_2$  Off

$$I_{D_1} \geq 0 \quad V_{D_1} = 0 \quad I_{D_2} = 0 \quad V_{D_2} \leq 0$$

Hence  $V_{out} = V_{sath}$ ,  $V_+ > 0$

$$\frac{V_{in} - V_+}{R_1} + \frac{V_{out} - V_+}{R_2} = \frac{V_+ + V_{xx}}{R_2 + R_3}$$

----- KCL at point A.

$$\Rightarrow \frac{V_{in}}{R_1} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_2 + R_3} \right) V_+ + \frac{V_{xx}}{R_2 + R_3} - \frac{V_{sath}}{R_2}$$

$$V_+ > 0 \Rightarrow V_{in} > \left( \frac{V_{xx}}{R_2 + R_3} - \frac{V_{sath}}{R_2} \right) R_1$$

Case II


assume  $D_1$  off  $D_2$  On  $\therefore I_{D_1} = 0 \quad V_{D_1} \leq 0, \quad I_{D_2} \geq 0 \quad V_{D_2} = 0$

Hence  $V_{out} = -V_{sath}$ ,  $V_+ < 0$

$$\frac{V_{in} - V_+}{R_1} + \frac{V_{xx} - V_+}{R_2 + R_3} = \frac{V_+ - V_{out}}{R_2} \quad \text{----- KCL at A}$$

$$\Rightarrow \frac{V_{in}}{R_1} = \left( \frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{R_2 + R_3} \right) V_+ + \frac{V_{sath}}{R_2} - \frac{V_{xx}}{R_2 + R_3}$$
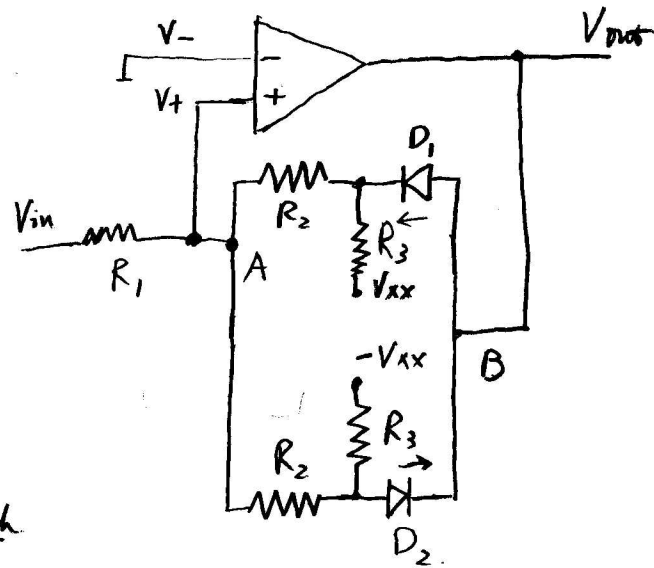
$$V_+ < 0 \Rightarrow V_{in} < - \left( \frac{V_{xx}}{R_2 + R_3} - \frac{V_{sath}}{R_2} \right) \cdot R_1$$



Case III assume both  $D_1$  and  $D_2$  are On


$$\frac{V_{in} - V_+}{R_1} + \frac{V_{out} - V_+}{R_2} + \frac{V_{out} - V_+}{R_2} = 0$$

$$\Rightarrow V_{out} = -\frac{R_2}{2} \left( \frac{V_{in}}{R_1} + \left( \frac{1}{R_1} + \frac{2}{R_2} \right) V_+ \right)$$

from case I and II, in Case III

$$-\left( \frac{V_{xx}}{R_2 + R_3} - \frac{V_{sath}}{R_2} \right) R_1 < V_{in} < \left( \frac{V_{xx}}{R_2 + R_3} - \frac{V_{sath}}{R_2} \right) R_1$$

Hence (a)

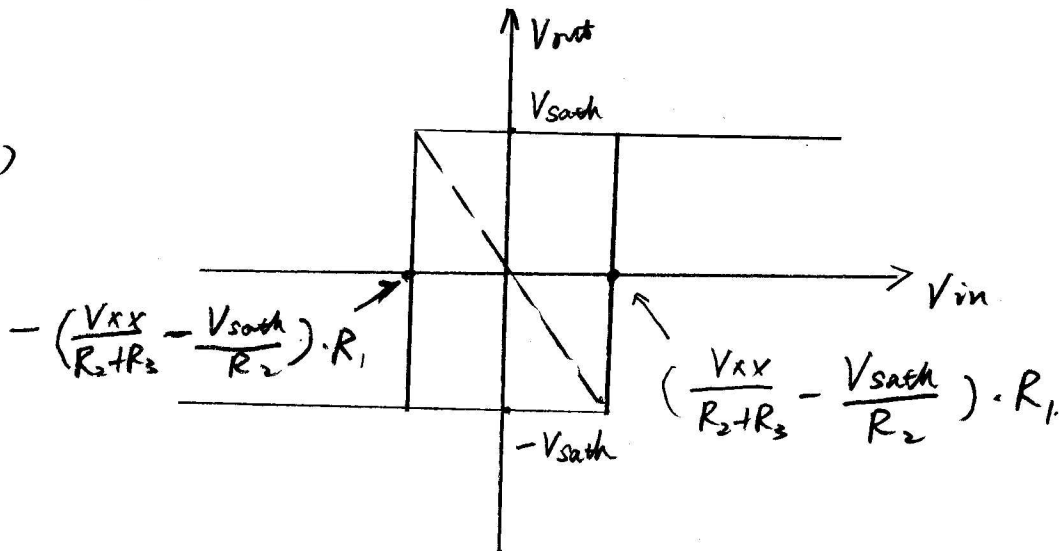

(b)

$$\text{Width} = \left( \frac{V_{xx}}{R_2 + R_3} - \frac{V_{sath}}{R_2} \right) \cdot 2R_1$$

$$\text{Center} = 0$$

P4 Case I assume  $D_1$  &  $D_2$  both off

$$-0.6 < V_1 - V_{out} < 0.6 \text{ must hold}$$


$$\therefore V_1 = \frac{1}{2} (V_{out} + V_{in})$$

$$\Rightarrow -0.6 < \frac{V_{in}}{2} - \frac{V_{out}}{2} < 0.6$$

$\therefore D_1$  &  $D_2$  are off

$$V_{out} = V_{in} \left( 1 + \frac{20k}{1k} \right) = 21 V_{in}$$

$$\Rightarrow \text{when } |V_{in}| < 0.06V, \quad V_{out} = 21 V_{in}$$

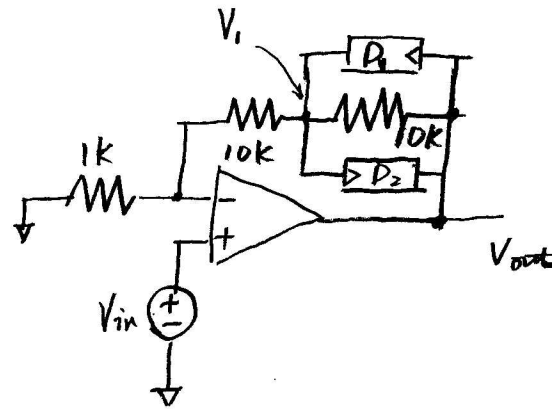

Case II

$D_1$  is On,  $D_2$  is off

$$V_{out} - V_1 = 0.6 \quad \text{and} \quad V_{out \max} = 15V$$

$$\therefore \frac{V_{out} - 0.6}{10k} = V_{in} \left( \frac{1}{10k} + \frac{1}{1k} \right)$$

$$\Rightarrow V_{out} = 11 V_{in} + 0.6 \quad \text{if } V_{out} \leq 15V \text{ and } V_{out} - V_1 \geq 0.6$$

$$\Rightarrow V_{out} = \begin{cases} 11 V_{in} + 0.6 & 0.06 < V_{in} \leq 1.309 \\ 15 & V_{in} \geq 1.309 \end{cases}$$

Case III

$D_1$  is off,  $D_2$  is on.


$$V_1 - V_{out} = 0.6 \quad \text{and} \quad V_{out \min} = -15V$$

$$\frac{V_{out} + 0.6}{10k} = V_{in} \left( \frac{1}{10k} + \frac{1}{1k} \right)$$

$$\Rightarrow V_{out} = 11 V_{in} - 0.6 \quad \text{if } V_{out} > -15V \text{ and } V_1 - V_{out} \geq 0.6$$

$$\Rightarrow V_{out} = \begin{cases} 11 V_{in} - 0.6 & -1.309 \leq V_{in} < -0.06 \\ -15 & V_{in} \leq -1.309 \end{cases}$$

P5

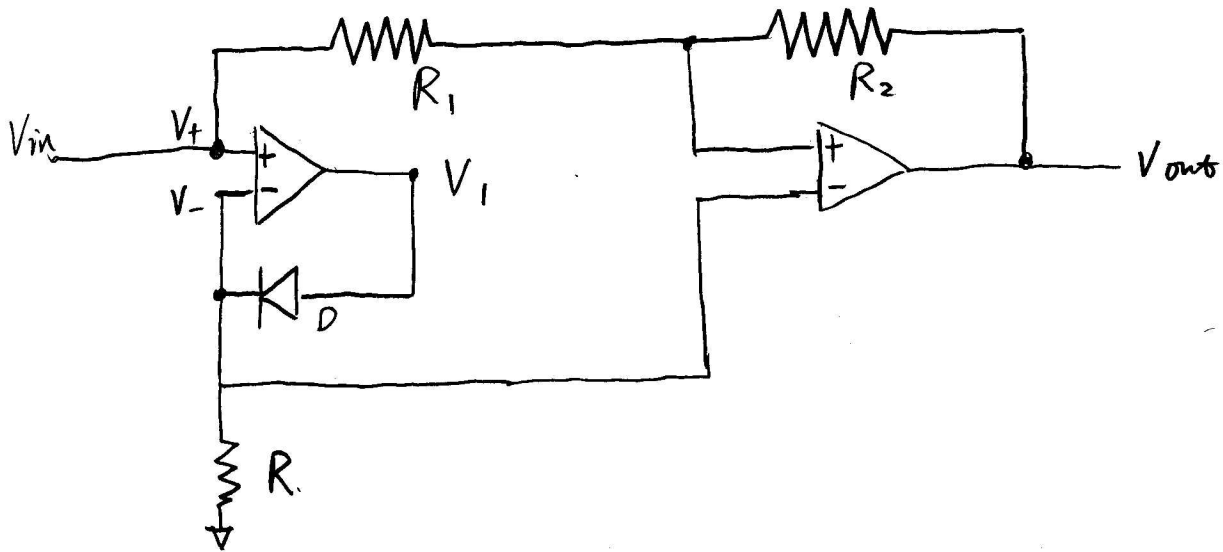

**Case I**, assume diode is on,  $I_D > 0$

$$V_1 - V_- = V_1 - V_{in} = V_{on} = 0.6 \text{ V}$$

$$\Rightarrow V_1 = V_{in} + 0.6$$

$$\therefore V_1 \text{ max} = 15 \text{ V when } V_{in} \geq 0$$

$$\therefore \begin{cases} V_1 = V_{in} + 0.6 & \text{if } 0 \leq V_{in} \leq 14.4 \text{ V} \\ V_1 = +15 & \text{if } V_{in} \geq 14.4 \text{ V} \end{cases}$$

**Case II** assume diode is off

then  $V_- = 0$ , because no current go through R.

We need  $V_+ - V_- < 0.6$  as diode is off

which holds when  $V_{in} < 0$  and  $V_1 = -15$

$$\therefore V_1 = -15 \text{ if } V_{in} < 0$$

$$V_{out} = V_- \left(1 + \frac{R_2}{R_1}\right) - V_{in} \left(\frac{R_2}{R_1}\right) \quad \text{when } V_{in} > 0 \quad V_- = V_{in}$$

$$\Rightarrow V_{out} = V_{in}$$

$$\text{when } V_{in} < 0 \quad V_- = 0$$

$$\Rightarrow V_{out} = -3V_{in}$$

$$\therefore V_{out} = \begin{cases} 2 \sin 1000t & 0 < V_{in} < 14.4 \\ -6 \sin 1000t & V_{in} < 0 \end{cases}$$

P 6 When diode is ideal.

Case I. diode is On.

$$\frac{V_{out}}{V_{in}} = \frac{1}{2} \quad V_{in} \geq 0$$

Case II diode is off

$$V_{out} = 0, \quad V_{in} < 0$$

When diode is not ideal.

Case I diode is on.


$$\frac{V_{out}}{1k} = \frac{V_{in} - (V_{out} + 0.6)}{1k} \Rightarrow V_{out} = \frac{V_{in} - 0.6}{2}$$

$$\text{and } I_d > 0 \text{ if } \frac{V_{in} - (V_{out} + 0.6)}{1k} > 0 \Rightarrow V_{in} > 0.6V$$

Case II diode is off



$$V_{out} = 0 \quad \text{and} \quad V_{in} - V_{out} \leq 0.6V \Rightarrow V_{in} \leq 0.6V$$

The plot when diode is ideal is omitted.

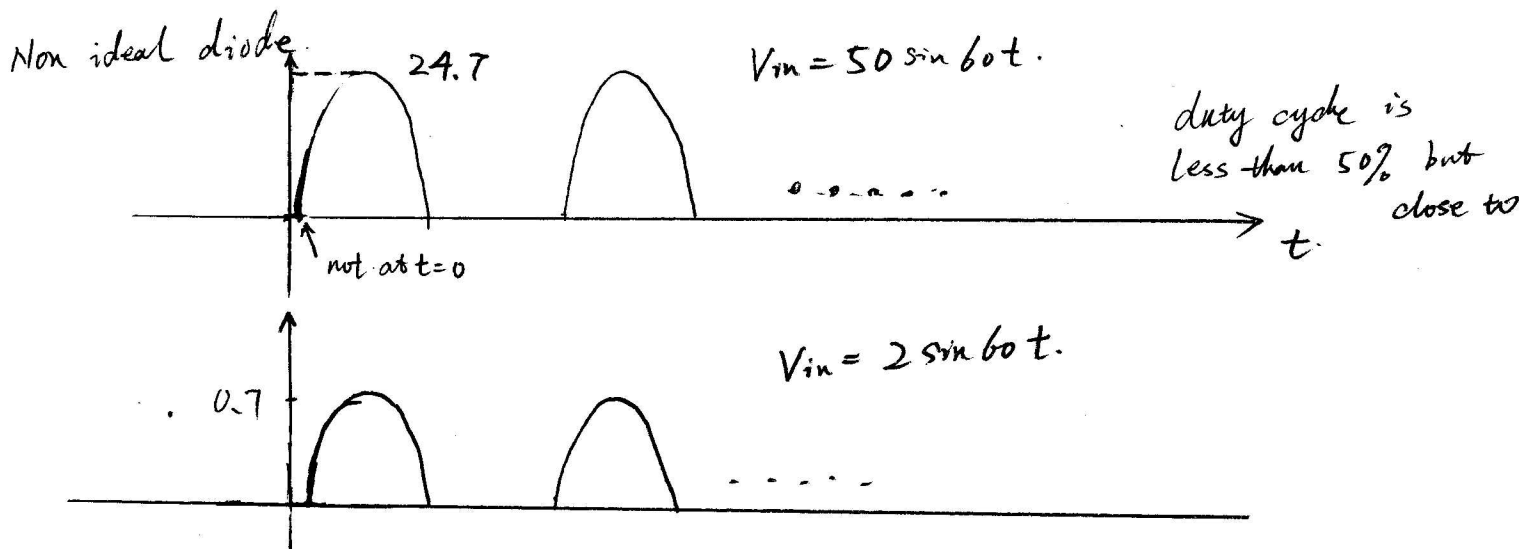

$$V_{out} = 0 \quad \text{if} \quad V_{in} = 0.5 \sin 60t$$

P7

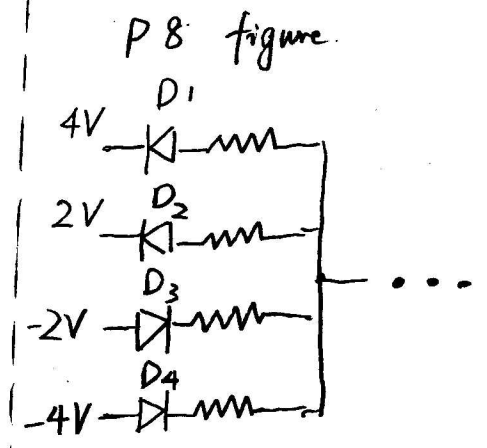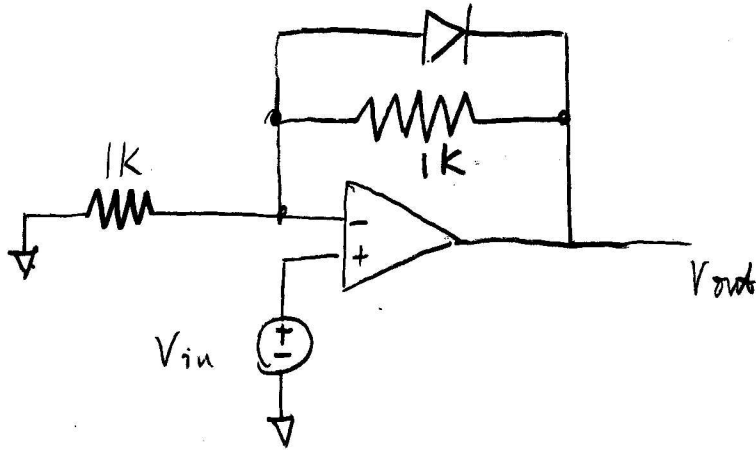

P8 case 1. when  $\frac{1}{5}V_{in} \geq 4V$   $D_1, D_2$  on,  $D_3, D_4$  off

$$V_{out} = \frac{1}{5}V_{in} \left( 1 + \frac{10k}{10k // 10k} \right) - 4 \cdot \frac{10k}{10k} - 2 \cdot \frac{10k}{10k}$$

$$= \frac{3}{5}V_{in} - 6$$

case 2, when  $2V \leq \frac{1}{5}V_{in} < 4V$   $D_2$  on,  $D_1, D_3, D_4$  off

$$V_{out} = \frac{1}{5}V_{in} \left( 1 + \frac{10k}{10k} \right) - 2 \cdot \frac{10k}{10k}$$

$$= \frac{2}{5}V_{in} - 2$$

case 3 when  $-2V \leq \frac{1}{5}V_{in} < 2V$  all diodes are off

$$V_{out} = \frac{1}{5}V_{in}$$

case 4 when  $-4V \leq \frac{1}{5}V_{in} < -2V$   $D_1, D_2, D_4$  off  $D_3$  on.

$$V_{out} = \frac{1}{5}V_{in} \left( 1 + \frac{10k}{5k} \right) - (-2) \cdot \frac{10k}{5k}$$

$$= \frac{3}{5}V_{in} + 4$$

case 5 when  $\frac{1}{5}V_{in} < -4$   $D_1, D_2$  off,  $D_3, D_4$  on.




$$V_{out} = \frac{1}{5} V_{in} \left( 1 + \frac{10k}{5k // 5k} \right) - (-4) \frac{10k}{5k} - (-2) \frac{10k}{5k}$$

$$= V_{in} + 12$$

Hence
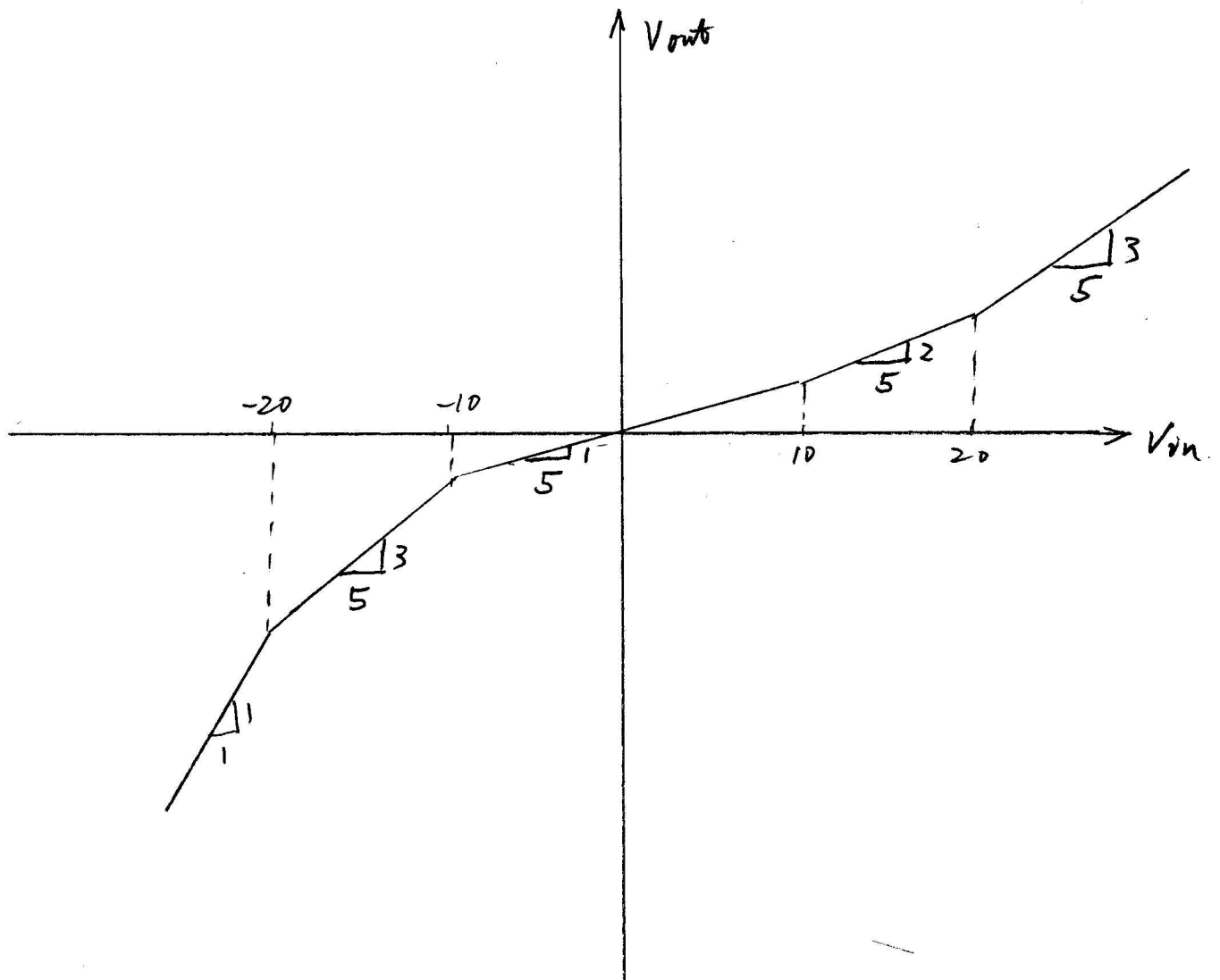
$$V_{out} = \begin{cases} \frac{3}{5} V_{in} - 6 & V_{in} \geq 20V \\ \frac{2}{5} V_{in} - 2 & 10V \leq V_{in} < 20V \\ \frac{1}{5} V_{in} & -10V \leq V_{in} < 10V \\ \frac{3}{5} V_{in} + 4 & -20V \leq V_{in} < -10V \\ V_{in} + 12 & V_{in} < -20V \end{cases}$$



P9. Case I assume both diodes are on.

$$V_{out} = 2V, \quad \frac{V_{in} - V_{out}}{4K} - \frac{V_{out}}{1K} = I_{D2} > 0$$

$$\Rightarrow V_{in} > 10V$$

Case II assume  $D_1$  on  $D_2$  off

$$V_{out} < 2V \quad \frac{V_{in} - V_{out}}{4K} = \frac{V_{out}}{1K} \Rightarrow V_{out} = \frac{1}{5} V_{in}$$

$$I_{D1} > 0 \Rightarrow V_{in} = V_{out} > 0 \Rightarrow V_{in} > 0$$

$$\therefore V_{out} = \frac{1}{5} V_{in} \quad \text{if } 0 < V_{in} < 10V$$

Case III both off

$$V_{out} = 0, \quad \text{valid when } V_{in} < 0$$

(a) When  $V_{in} = 5V$   $V_{out} = 1V$

$$(b) \quad V_{out} = \begin{cases} 0 & V_{in} < 0V \\ \frac{1}{5} V_{in} & 0V < V_{in} < 10V \\ 2 & V_{in} > 10V \end{cases}$$

P10 case I assume both are on.

$$V_{out} = 2.6V \quad \frac{V_{in} - 2.6}{4k} - \frac{2.6}{1k} = I_{D_2} > 0 \Rightarrow V_{in} > 13.6V$$

Case II assume  $D_1$  on  $D_2$  off

$$V_{out} < 2.6V \quad \frac{V_{in} - V_{out} - 0.6}{4k} = \frac{V_{out}}{1k} \Rightarrow V_{out} = \frac{1}{5}(V_{in} - 0.6)$$

$$I_{D_1} > 0 \Rightarrow V_{in} - 0.6 - V_{out} > 0 \Rightarrow V_{in} > 0.6$$

$$\text{SO } V_{out} = \frac{1}{5}(V_{in} - 0.6) \quad \text{if } 0.6 < V_{in} < 13.6$$

Case III assume both off

$$V_{out} = 0, \quad \text{valid when } V_{in} - 0.6 < 0$$

$$(a) \quad \text{when } V_{in} = 5V \quad V_{out} = 0.88V$$

$$(b) \quad V_{out} = \begin{cases} 0 & V_{in} < 0.6V \\ \frac{1}{5}(V_{in} - 0.6) & 0.6V < V_{in} < 13.6V \\ 2.6V & V_{in} > 13.6V \end{cases}$$