

EE 230

Lecture 5


Linear Systems

- Poles/Zeros/Stability
- Stability

Quiz 4

Obtain the transfer function $T(s)$ for the circuit shown.

$$T(s) = \frac{V_{OUT}(s)}{V_{IN}(s)}$$

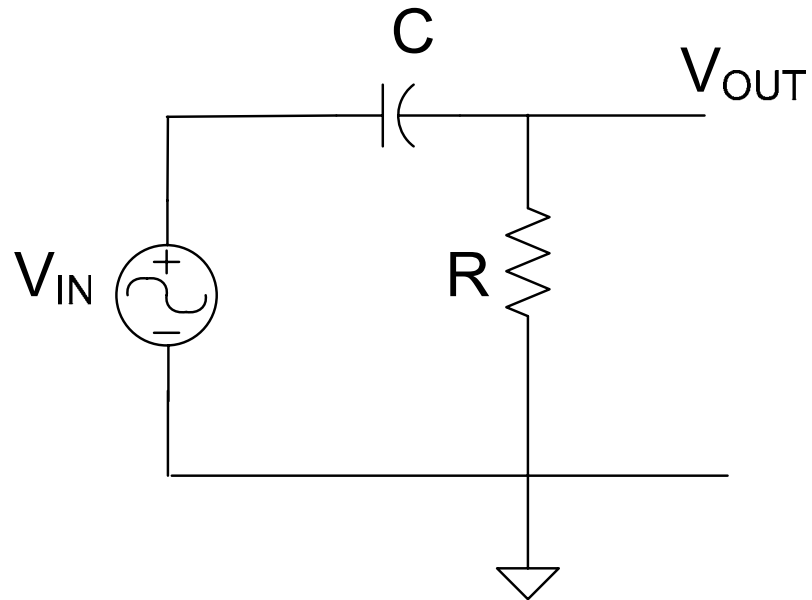

And the number is ?

1

3

8

5

4

2

6

9

7

And the number is ?

1

3

8

5

4

2

3

6


9

7

Quiz 4

Obtain the transfer function $T(s)$ for the circuit shown.

$$T(s) = \frac{V_{OUT}(s)}{V_{IN}(s)}$$

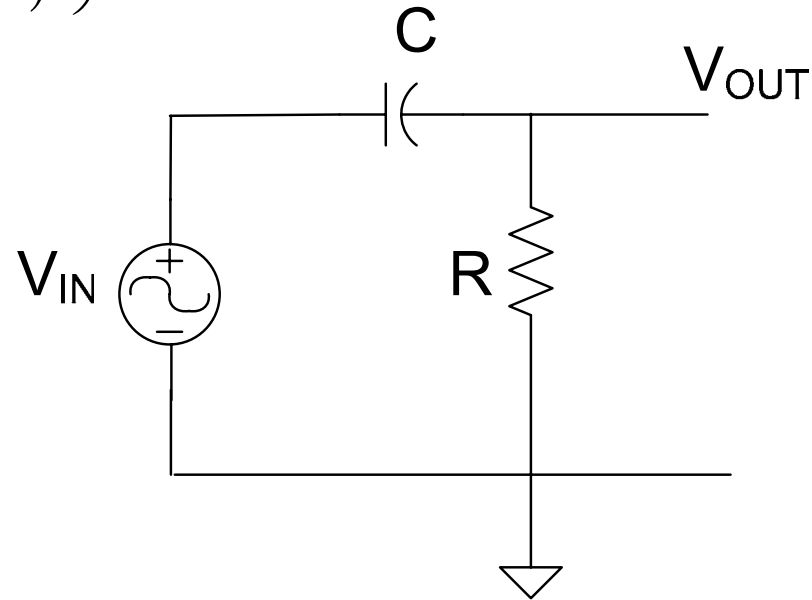

Solution:

$$T(s) = \frac{R}{R + \frac{1}{sC}} = \frac{RCs}{1 + RCs}$$

Review from Last Time

$T(s)$ is often used instead of $T_P(j\omega)$ in the electronics and systems communities when characterizing the frequency response of linear circuits or systems

$$T(s)\Big|_{s=j\omega} = T_P(j\omega)$$


For linear system with excitation $V_m \sin(\omega t + \theta)$ and transfer function $T(s)$

$$V_{OSS} = V_M |T_P(j\omega)| \sin(\omega t + \theta + \angle T_P(j\omega))$$

$$V_{OSS} = V_M |T(s)\Big|_{s=j\omega}| \sin(\omega t + \theta + \angle T(s)\Big|_{s=j\omega})$$


Review from Last Time

Time, Phasor, and s- Domain Analysis

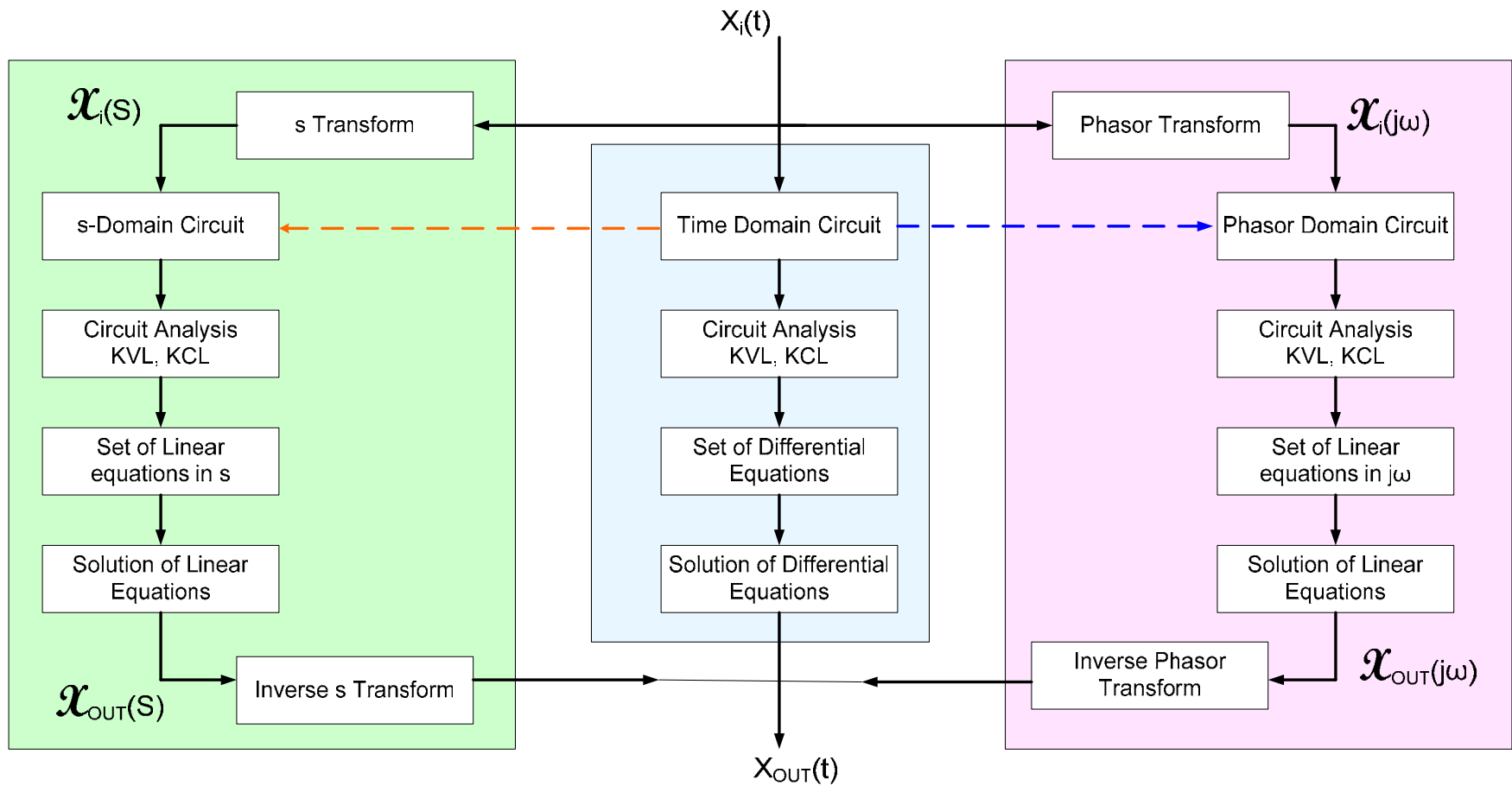


Review from Last Time

s- Domain Analysis

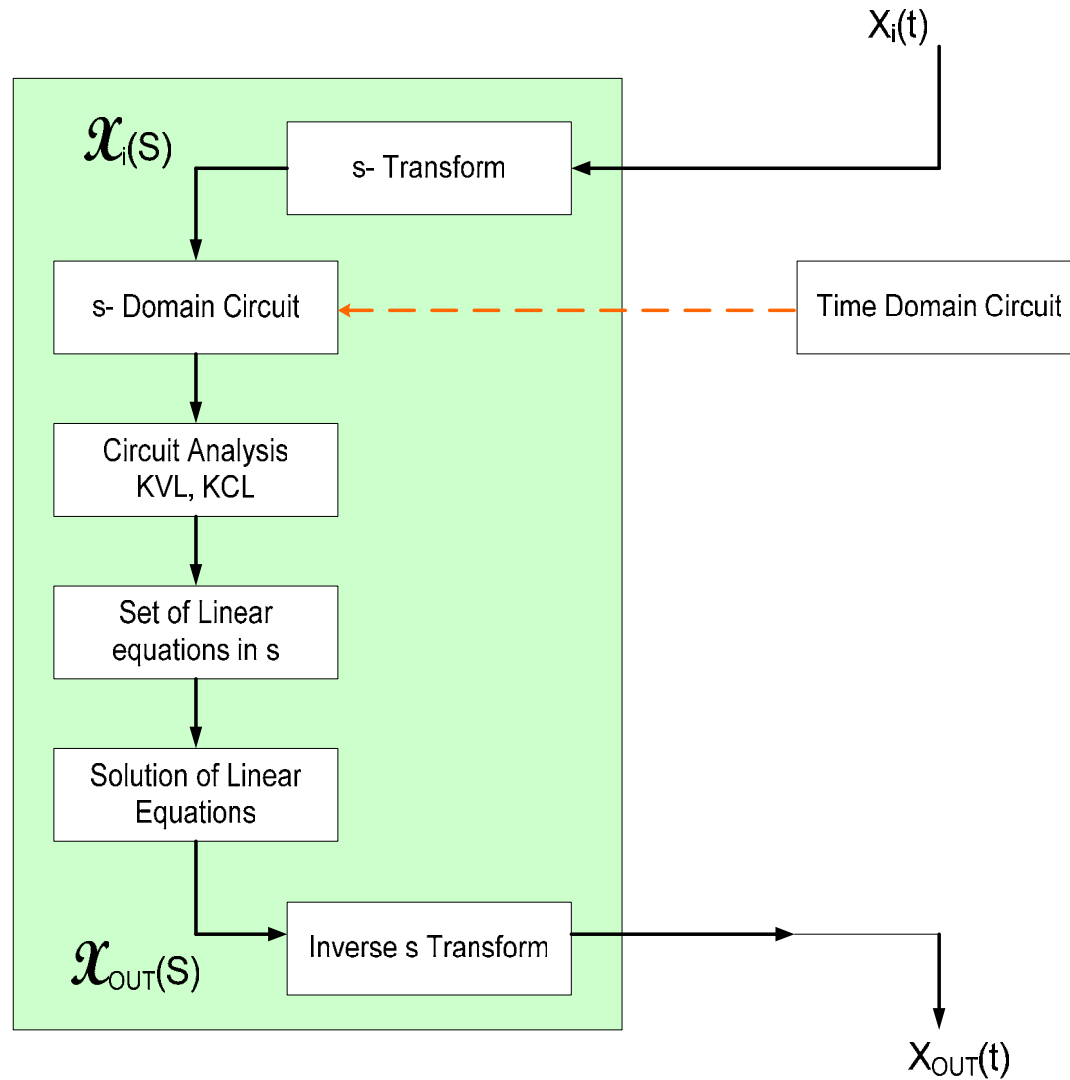


Sinusoidal Steady State Analysis of Linear Networks - A Review

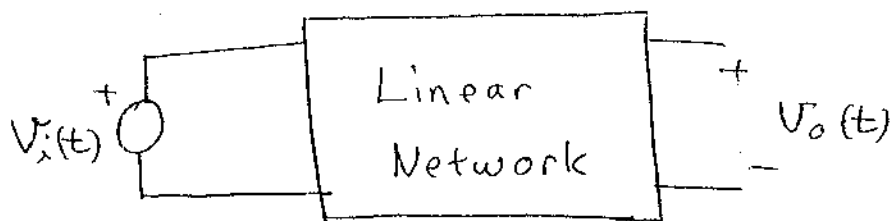Consider a linear network with input $V_i(t)$ and output $V_o(t)$



$$\text{Assume } V_i(t) = V_m \sin(\omega t + \theta) \quad (1)$$

Phasor Analysis

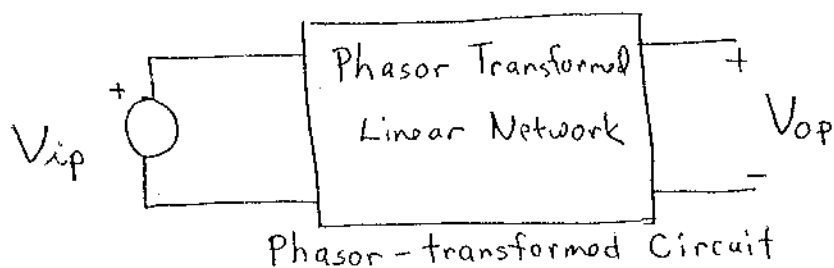

Note: V_{ip} and V_{op} are the phasor transforms of $V_i(t)$ and $V_o(t)$ respectively

The phasor transformed linear network is obtained by making the following element transformations

$$- \quad C \rightarrow \frac{1}{j\omega C} \quad (2)$$

$$- \quad L \rightarrow j\omega L \quad (3)$$

- All other elements unchanged

Analyzing the phasor-domain network, we obtain the output phasor as the product of the input phasor and a complex function, $T_p(j\omega)$, determined by the network. This can be written as

$$V_{op} = T_p(j\omega) \cdot V_{ip} \quad (4)$$

$T_p(j\omega)$ can be written in polar form as

$$T_p(j\omega) = |T_p(j\omega)| \angle \arg(T(j\omega)) \quad (5)$$

where $\arg(T(j\omega))$ is the angle of the function $T_p(j\omega)$

The input phasor, from (1), can be written as

$$V_{ip} = V_m \angle \theta \quad (6)$$

Substituting (5) and (6) into (4), we obtain the output phasor

$$V_{op} = (V_m \angle \theta) (|T_p(j\omega)| \angle \arg(T(j\omega))) \quad (7)$$

which can be rewritten in standard polar form as


$$V_{op} = [V_m \cdot |T(j\omega)|] \angle (\theta + \arg(T(j\omega))) \quad (8)$$

The sinusoidal steady state output can be obtained from the inverse phasor transform of V_{op} in (8)

$$V_o(t) = V_m |T_p(j\omega)| \sin(\omega t + \theta + \arg(T(j\omega))) \quad (9)$$

Equation (9) is a key result!

s-domain analysis

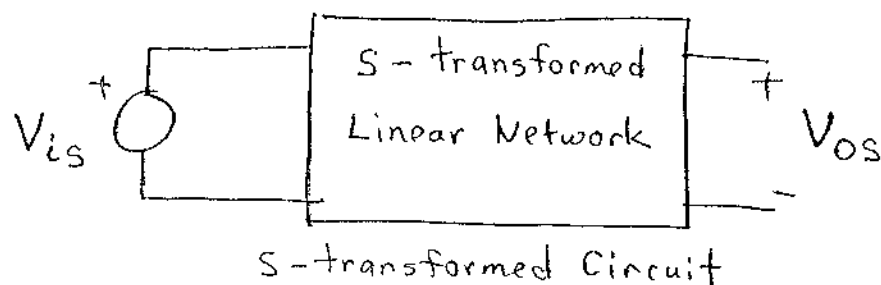

- Note
- V_{is} and V_{os} are the s-transforms of $V_i(t)$ and $V_o(t)$ respectively
 - The s-transformed linear network is obtained by making the following element transformations

$$- \quad C \rightarrow \frac{1}{sC} \quad (2')$$

$$- \quad L \rightarrow sL \quad (3')$$

- All other elements unchanged

Analyzing the s-domain network, we obtain the s-domain output as the product of the s-domain input and an s-domain function, $T(s)$, determined by the network. This can be written as

$$V_{os} = T(s) \cdot V_{is} \quad (4')$$

The sinusoidal steady state response can be obtained from the inverse-s transform of V_{os} which becomes, after transient response terms are neglected,

$$V_o(t) = V_m |T(j\omega)| \sin(\omega t + \theta + \arg(T(j\omega))) \quad (9)$$

where $T(j\omega) = T(s) \Big|_{s=j\omega}$

Equation (9') is a key result!

Note : $T(s)$ is called the system transfer function


Note : $T_p(j\omega) = T(s) \Big|_{s=j\omega}$

Note : $T_p(s) = T(j\omega) \Big|_{\omega = \frac{s}{j}}$


Note : $T_p(s) = T(s)$

Note : Equations (9) and (9') are identical

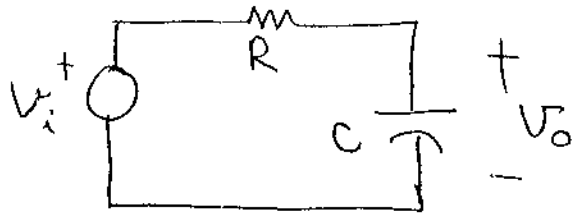Example: Obtain the transfer function and the sinusoidal steady state response of the following circuit using a) phasor analysis ; b) s-domain analysis and c) differential equations. Assume $V_i = V_m \sin(\omega t + \theta)$



a) Phasor analysis

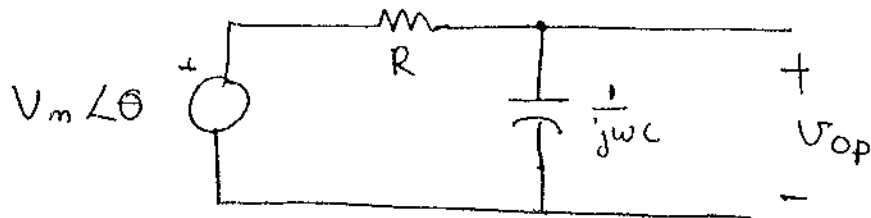

Phasor-transformed circuit

By voltage divider

$$V_{op} = \left(\frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \right) V_m \angle \theta \quad (1)$$

$$V_{op} = \left(\frac{1}{1 + RC\omega j} \right) V_m \angle \theta \quad (2)$$

$$\text{From (2), } T_p(j\omega) = \frac{V_{op}}{V_{ip}} = \frac{V_{op}}{V_m \angle \theta} = \frac{1}{1 + RC\omega j} \quad (3)$$

$$\therefore T(s) = \frac{1}{1 + RCs} \quad (4)$$

Converting $T_p(j\omega)$ in (2) from rectangular to polar form, we obtain


$$V_{op} = \left(\frac{1}{\sqrt{1+R^2C^2\omega^2}} \angle -\tan^{-1}\omega RC \right) V_m \angle \Theta \quad (5)$$

$$V_{op} = \frac{V_m}{\sqrt{1+R^2C^2\omega^2}} \angle (\Theta - \tan^{-1}\omega RC) \quad (6)$$

Taking the inverse phasor transform of (6) we obtain the sinusoidal steady state response

$$V_o(t) = \frac{V_m}{\sqrt{1+R^2C^2\omega^2}} \sin(\omega t + \Theta - \tan^{-1}(\omega RC)) \quad (7)$$

b) s-domain Analysis

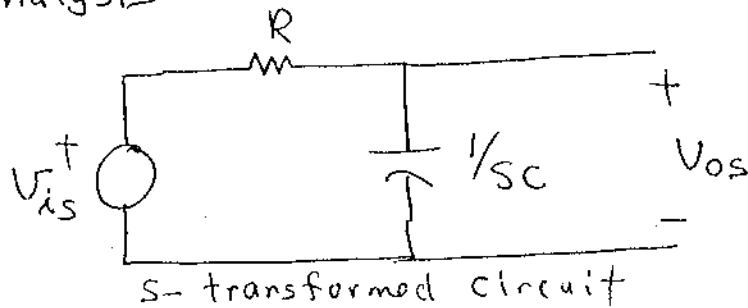

By voltage divider

$$V_{os} = \left[\frac{\frac{1}{sC}}{R + \frac{1}{sC}} \right] V_{is} \quad (8)$$

$$V_{os} = \left[\frac{1}{1+RCs} \right] V_{is} \quad (9)$$

It follows from (9) that the transfer function is

$$T(s) = \frac{1}{1+RCs} \quad (10)$$

From (10),

$$T(j\omega) = \frac{1}{1+RC\omega j} \quad (11)$$


Thus the sinusoidal steady state output is given by

$$V_o(t) = V_m |T(j\omega)| \sin(\omega t + \theta + \angle T(j\omega)) \quad (12)$$

from (12), this becomes

$$V_o(t) = \frac{V_m}{\sqrt{1+R^2C^2\omega^2}} \sin(\omega t + \theta - \tan^{-1}(\omega RC)) \quad (13)$$

c) using differential equations

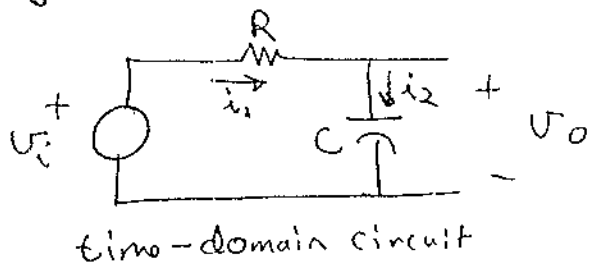

$$i_1 = \frac{V_i - V_o}{R} \quad (14)$$

$$i_2 = C \frac{dV_0}{dt} \quad (15)$$

equating i_1 and i_2 , we obtain the differential equation

$$\frac{V_i - V_0}{R} = C \frac{dV_0}{dt} \quad (16)$$

I will use Laplace transforms to solve. Taking the Laplace transform of (16)

$$\frac{V_{is} - V_{os}}{R} = C s V_{os} \quad (17)$$

Simplifying (17), we obtain

$$V_{os} = \frac{1}{1 + RCs} \cdot V_{is} \quad (18)$$

If $V_{is} = V_m \sin(\omega t + \theta)$, taking the inverse Laplace transform and neglecting the transient response, we obtain

$$V_0(t) = \frac{V_m}{|T(j\omega)|} \sin(\omega t + \theta - \arg(T(j\omega))) \quad (19)$$


where

$$T(j\omega) = \frac{1}{1 + RCj\omega} \quad (20)$$

Thus,


$$V_0(t) = \frac{V_m}{\sqrt{1 + R^2 C^2 \omega^2}} \sin(\omega t + \theta - \tan^{-1} \omega RC) \quad (21)$$

Step Response of First-Order Networks

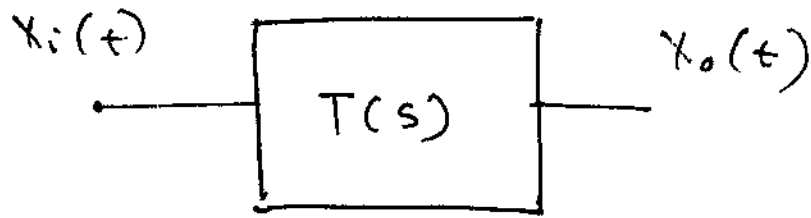


$$T(s) = \frac{N(s)}{S + P}$$

If $x_i = x_m u(t)$

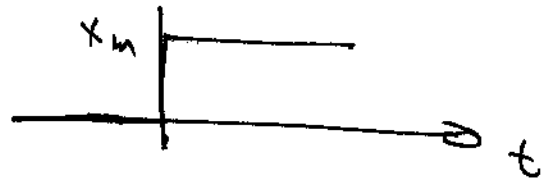

$$x_o(t) = F + (I - F) e^{-t/\tau}$$

$$\tau = P^{-1}$$

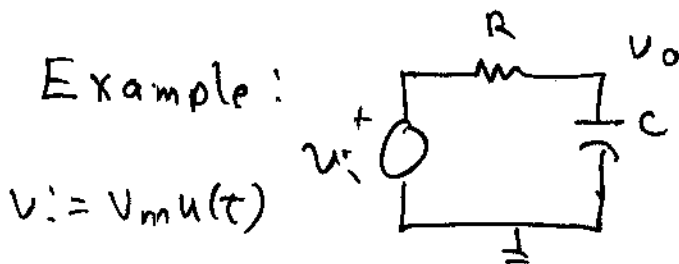



$$\frac{v_o}{v_i} = \frac{1}{1 + RCs} \rightarrow P = \frac{1}{RC}$$

$$v_o(t) = V_m + -V_m e^{-\frac{t}{RC}} = V_m (1 - e^{-t/RC})$$


"Gain" of linear networks

- $T(j\omega)$ represents the gain of a linear network with a sinusoidal input
- $T(j\omega)$ is frequency dependent
- $|T(j\omega)|$ is termed the magnitude of the gain
- $\angle T(j\omega)$ is termed the phase or angle of the gain
- Plots of $|T(j\omega)|$ and $\angle(T(j\omega))$ often used to characterize the network
- These plots characterize the "frequency response" of the network


Example :

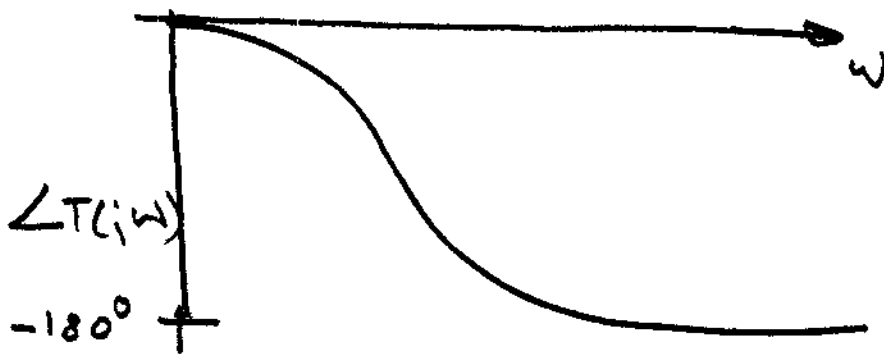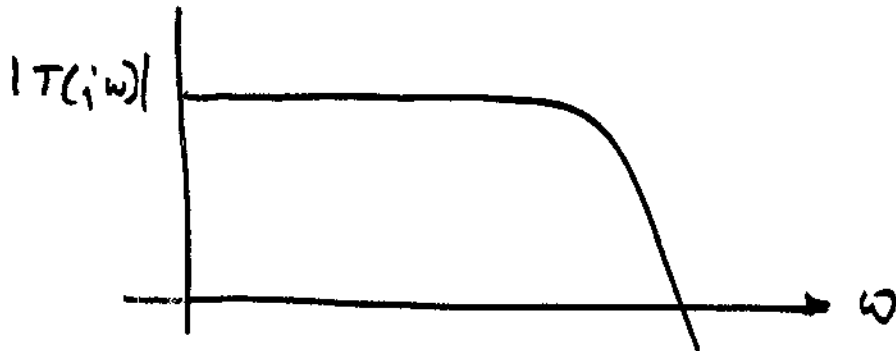


Nomenclature

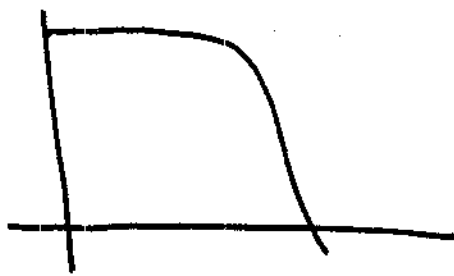


Lowpass

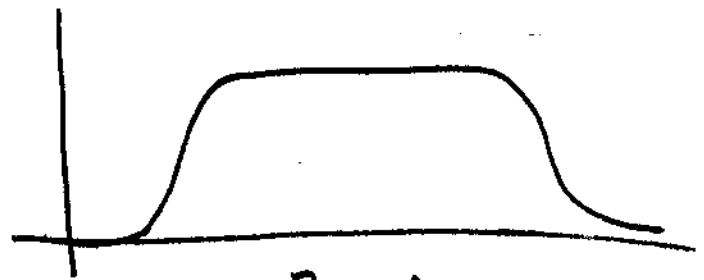

Bandpass

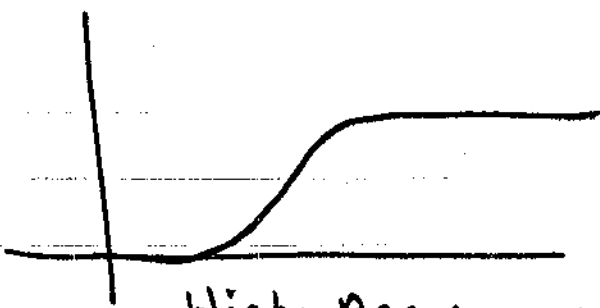


High-pass

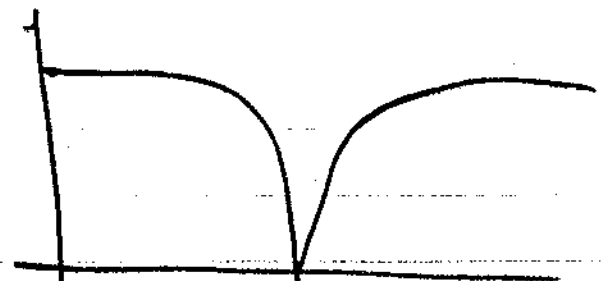

Notch

Recall:

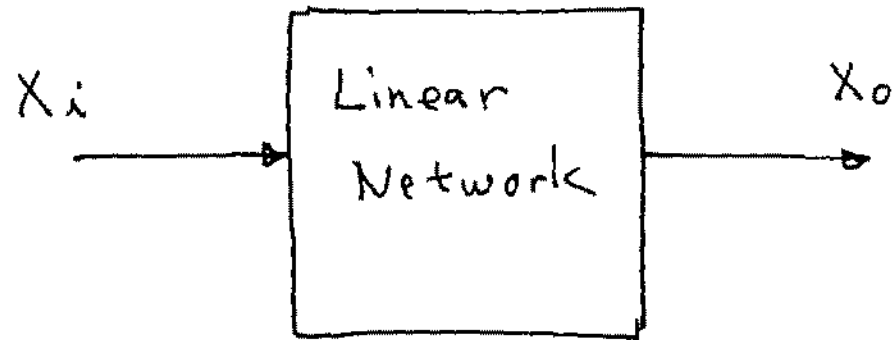

$$T(s) = \frac{\vec{X}_o(s)}{\vec{X}_i(s)}$$

Claim: $T(s)$ can always be expressed as a rational fraction in S if the network has a finite number of lumped components

will only be interested in networks with finite number of lumped components in this course

$$T(s) = \frac{N(s)}{D(s)}$$


where $N(s) = \sum_{k=0}^M a_k s^k$

$$D(s) = \sum_{k=0}^n b_k s^k$$


The roots of $D(s)$ are the poles of the network

The roots of $N(s)$ are the zeros of the network

Example:

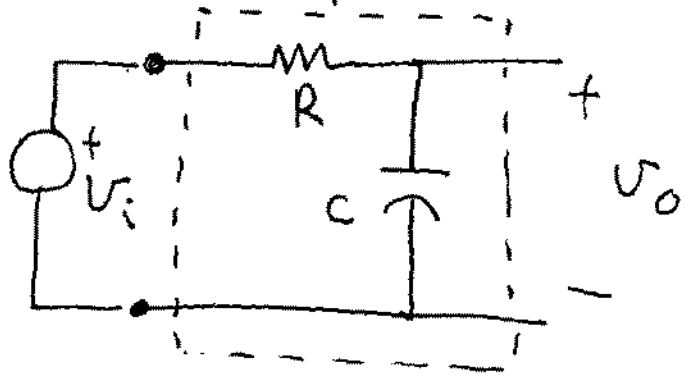

$$\frac{V_o}{V_i} = \frac{1}{1+RCs}$$

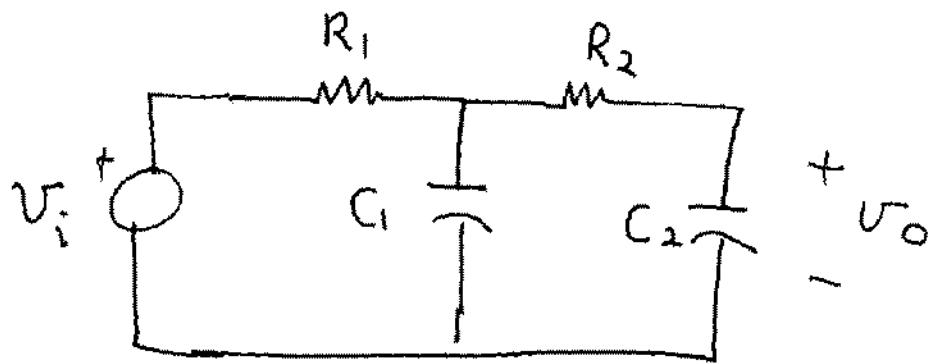

$$\frac{V_o}{V_i} = \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + s \left[\frac{1}{C_1} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + \frac{1}{C_2 R_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

Example: $T(s) = \frac{s+4}{s^2+9s+8}$

$$= \frac{s+4}{(s+1)(s+8)}$$

Zeros: $\{s = -4\}$

Poles: $\{s = -1, s = -8\}$

Often designated as

$$z = -4$$

$$p_1 = -1, p_2 = -8$$

Claim: A system with a 1st order lowpass transfer function with a pole p and dc gain K has a unit step response of

$$r(t) = F + (I - F) e^{pt}$$

I : Initial Value

F : Final Value

$\therefore p^{-1}$ is the time constant of the system

Alternate representations of Transfer Functions

$$T(s) = \frac{N(s)}{D(s)} = \frac{\prod_{i=1}^m a_i s^i}{\prod_{i=1}^n b_i s^i}$$

$$T(s) = \frac{A_1 \prod_{i=1}^m (s - z_i)}{B_1 \prod_{i=1}^n (s - p_i)}$$

If $X(s)$ is the input

$$X_0(s) = X(s) \frac{A_1 \prod_{i=1}^m (s - z_i)}{B_1 \prod_{i=1}^n (s - p_i)}$$

$$X_0(s) = \frac{\theta_1}{s - p_1} + \frac{\theta_2}{s - p_2} + \dots + \frac{\theta_n}{s - p_n} + \frac{\beta_1}{(s - \hat{p}_1)^{\hat{p}_1}} + \dots + \frac{\beta_k}{(s - \hat{p}_k)^{\hat{p}_k}}$$

$$\mathcal{L}^{-1}(X_0(s)) = \theta_1 e^{p_1 t} + \theta_2 e^{p_2 t} + \dots + \theta_n e^{p_n t} + \beta_1 e^{\hat{p}_1 t} + \dots + \beta_k e^{\hat{p}_k t}$$

Theorem: Any network comprised of R_s, L_s, C_s , will have all poles in the L.H.P.


Note: This theorem is not true, in general, if amplifiers (dependent sources) are included.

End of Lecture 5

Pole-Zero Plots

- Plots of the poles and zeros in the complex plane ($\times \rightsquigarrow$ poles, $\circ \rightsquigarrow$ zeros)

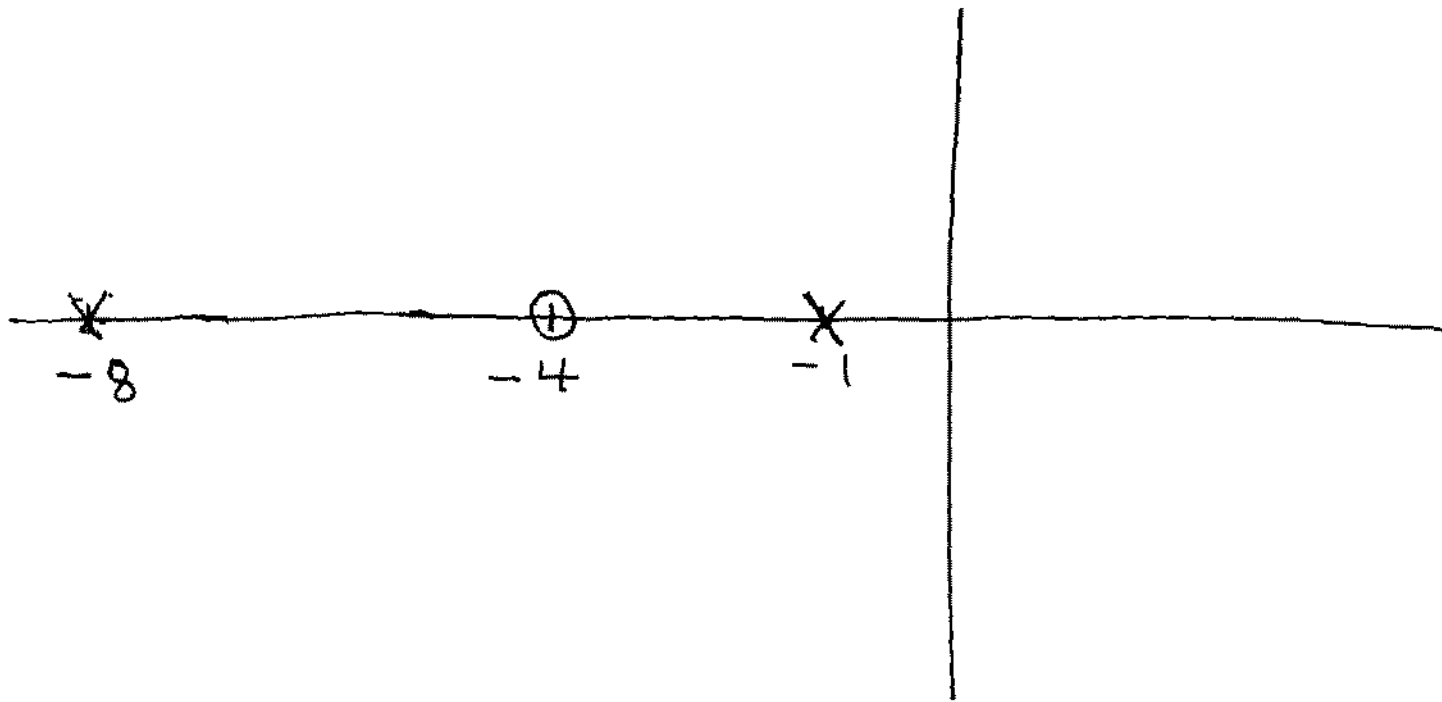Example: $Z = -4$, $P_1 = -1$, $P_2 = -8$



Example $T(s) = \frac{s-1}{s^2+2s+2}$

Determine poles and zeros and plot in complex plane

$$z_1 = 1$$

$$p = ?$$

$$s^2 + 2s + 2 = 0 \Rightarrow s = \frac{-2 \pm \sqrt{2^2 - (4)(2)}}{2}$$

$$s = \frac{-2 \pm \sqrt{-4}}{2}$$


$$s = -1 \pm j$$

$$S = -1 \pm j$$

$$P_1 = -1 + j$$

$$P_2 = -1 - j$$

$$Z_1 = 1$$

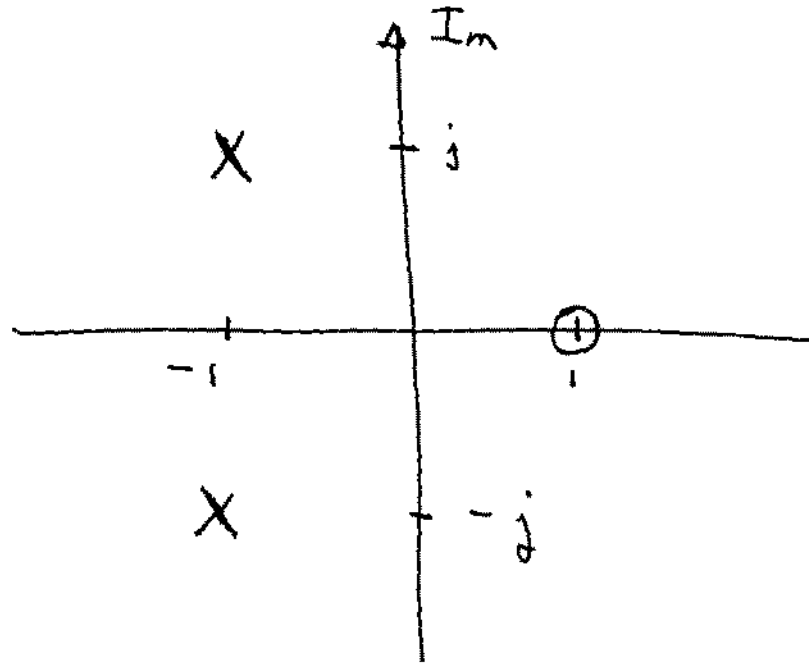

Example: $T(s) = \frac{4s+1}{s^5 + s^4 + 2s^3 + 3s^2 + 2s + 1}$

Zeros: $\left\{-\frac{1}{4}\right\}$

poles: - 5 in number

- closed form expression does not exist for polynomials of order 5 or higher

Theorem: A system is stable iff
all poles lie in the left half-plane

What is "stable" ?

- A linear system is stable iff any bounded input will result in a bounded output
- A system is stable iff the output due to any appropriately small input does not cause the output to go to $\pm \infty$ and does not create an output that persists indefinitely

Examples:

$$T(s) = \frac{1}{s+1}$$

pole at $p = -1$

\therefore system is stable

step response : $r(t) = F + (I - F)e^{-t/\tau} = e^{-t}$

$$T(s) = \frac{1}{s-1}$$

pole at $p = 1$

\therefore system is unstable


It can be shown that the step response is

$$r(t) = e^t$$

$r(t)$ diverges to ∞ !


Example: $T(s) = \frac{4}{s^2 + 9}$

Poles: $\{-j3, +j3\}$

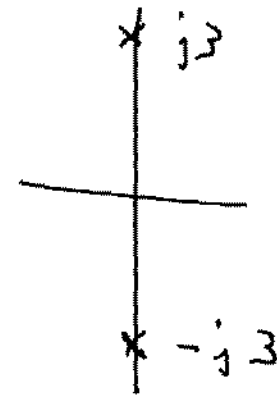

It can be shown that the step response will include a term

$$r(t) = H \sin 3t$$

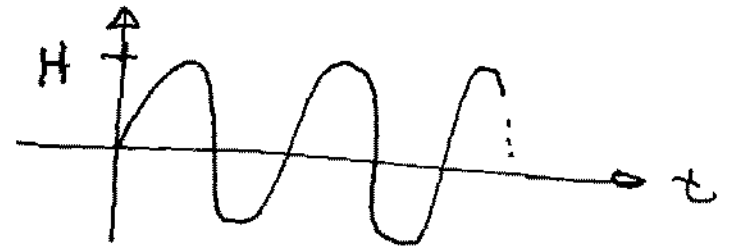

\therefore Output persists indefinitely

Is stability good or bad?

- depends on what is desired

Is instability good or bad?

- depends upon what is desired