

EE 230


Lecture 11

Basic Applications of
Operational Amplifiers

Quiz 8

Although high gain amplifiers are often needed, the operational amplifier, which is a high gain amplifier, is almost never used as an open-loop voltage amplifier.

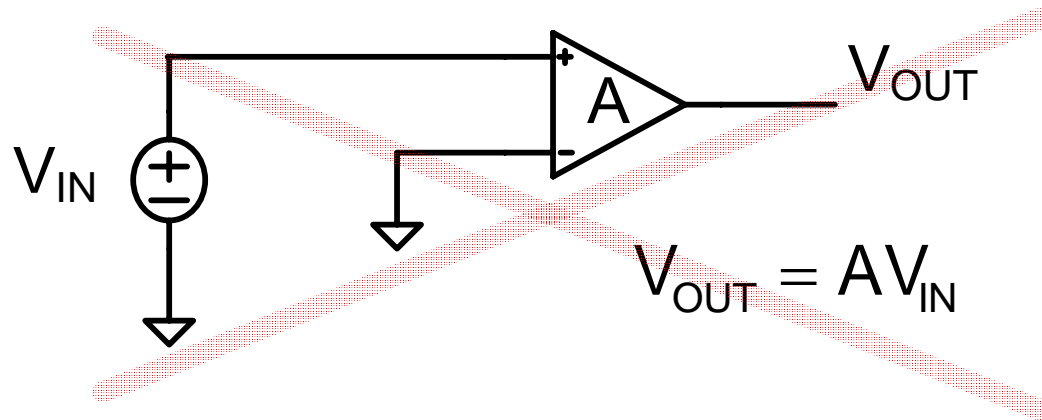- Give two major reasons that the op amp is almost never used as an open-loop voltage amplifier
- How are large voltage gains practically realized?



And the number is ?

1

3

8

5

4

2

6

9

7

And the number is ?

1

3

8

5

4

8

2

6

9

7

Quiz 8

a) Give two major reasons that the op amp is almost never used as an open-loop voltage amplifier


Gain of op amp is nonlinear

Gain of op amp is too variable

Other issues (such as offset voltage) render circuits not usable in most applications

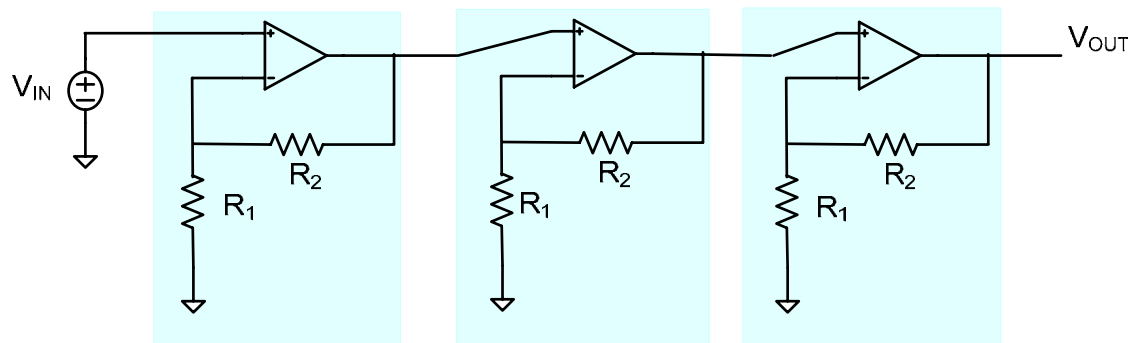a) How are large voltage gains practically realized?

By a cascade of a larger number of finite gain feedback amplifiers



Review from Last Time


Op Amp input port is termed a “null port”

Virtual short exists between input terminals of op amp when operating as an amplifier

Op Amp is almost never used as an open-loop voltage amplifier


Op Amp is basic high-gain amplifier used to build feedback networks

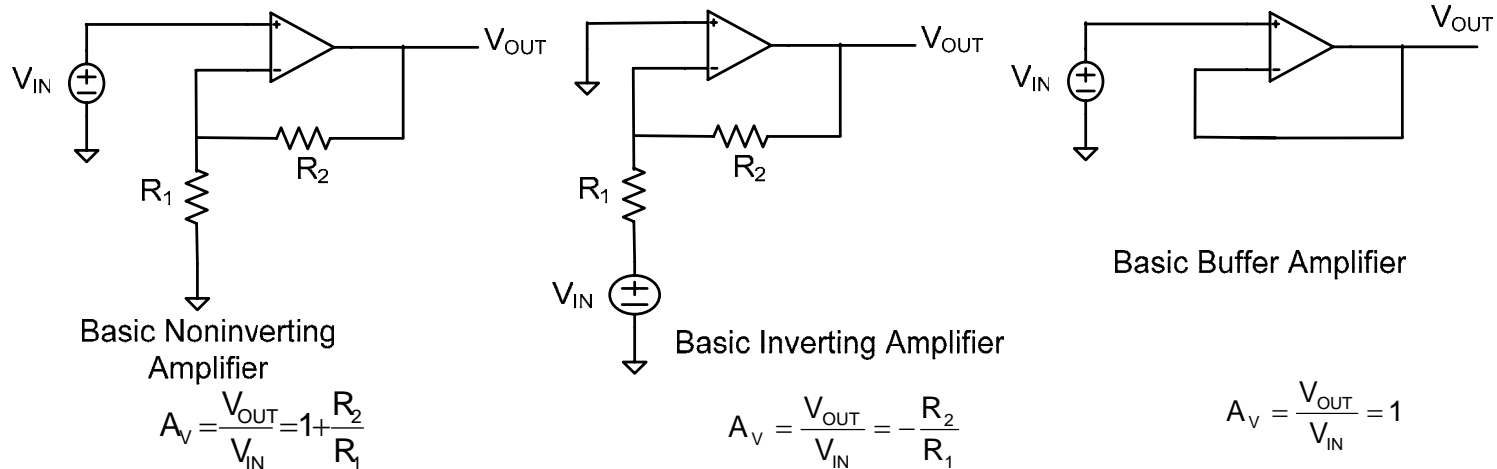Although feedback is used in almost all linear applications of op amps, feedback analysis is seldom used to analyze such circuits



$$U_0 = -\frac{R_f}{R_1} U_1 - \frac{R_f}{R_2} U_2 - \frac{R_f}{R_3} U_3$$

- All weights are negative

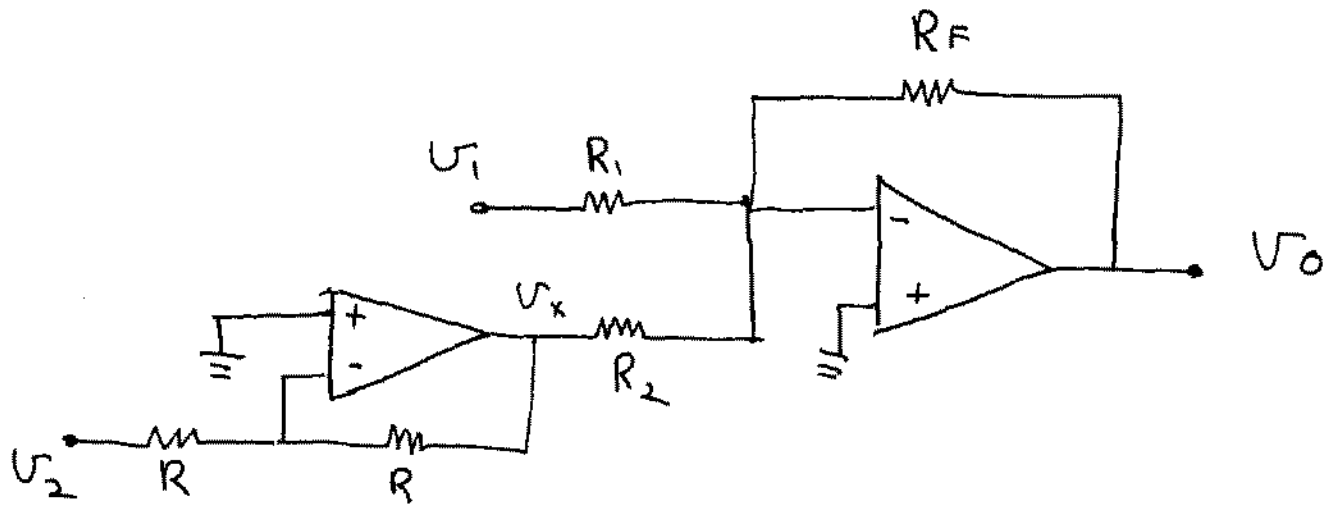


$$\left. \begin{aligned} V_o &= -\frac{R_F}{R_1} V_1 - \frac{R_F}{R_2} V_x \\ V_x &= -V_2 \end{aligned} \right\}$$

$$\therefore V_o = \frac{R_F}{R_2} V_2 - \frac{R_F}{R_1} V_1$$

Any number of inverting and noninverting inputs can be added.


Generalized Inverting Amplifier

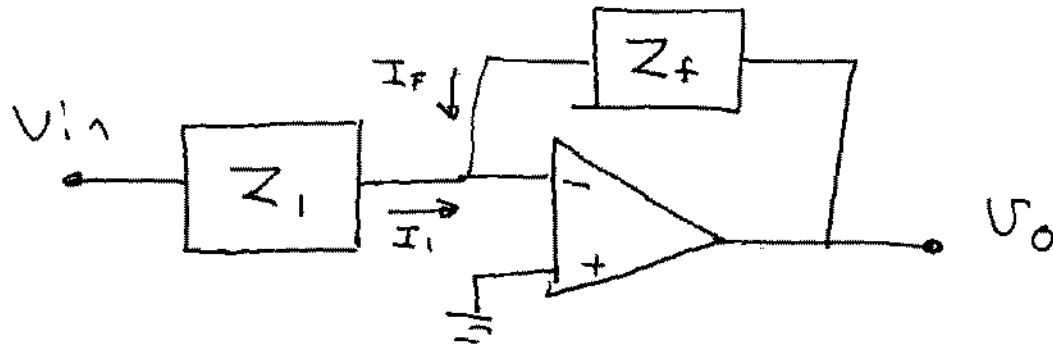

s-domain
impedances

$$\left. \begin{aligned} I_i &= \frac{V_{in}}{Z_1} \\ I_f &= \frac{V_o}{Z_f} \\ I_i &= -I_f \end{aligned} \right\} \frac{V_o}{V_{in}} = -\frac{Z_f}{Z_1}$$

What if $Z_F = 1/sC$, $Z_i = R$

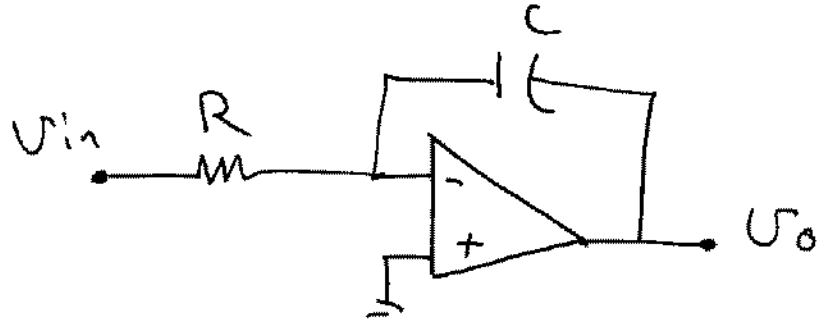

$$\frac{v_o}{v_i} = - \frac{1}{RCs}$$



What is this?


$$T(s) = -\frac{1}{RCs}$$

$$T(j\omega) = -\frac{1}{j\omega RC}$$

$$|T(j\omega)| = \frac{1}{\omega RC}$$

Integrator Gain

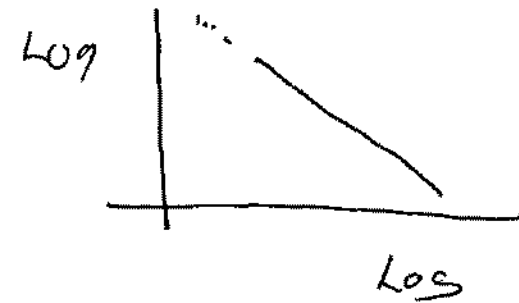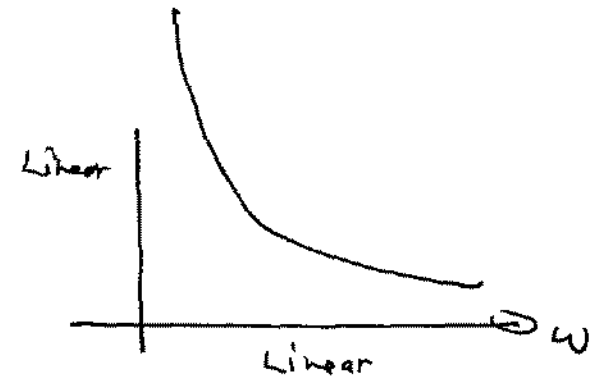

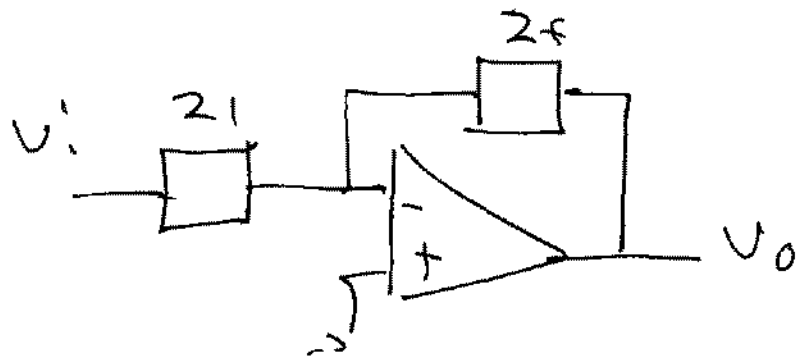

$$\frac{v_o}{v_i} = -\frac{Z_f}{Z_1}$$

$$\text{Let } Z_1 = \frac{1}{sC}$$


$$Z_f = R$$

$$\therefore \frac{v_o}{v_i} = -\frac{sCR}{1}$$

Differentiator (Inverting)

- Not widely used
- Noise relentlessly amplified
- stability problems with implementation

Summing Amplifier

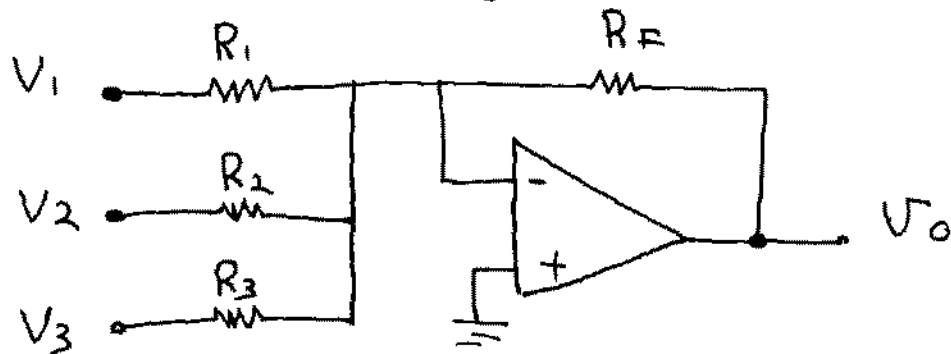

$$\frac{V_0}{R_F} + \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = 0$$


$$\therefore V_0 = -\frac{R_F}{R_1} V_1 - \frac{R_F}{R_2} V_2 - \frac{R_F}{R_3} V_3$$

- Termed a "mixer" in the audio community,
- Any number of inputs can be used
- R_F can adjust all gains together
- Individual gains can be independently adjusted




The following pages were
in response to questions
from students,

Example:

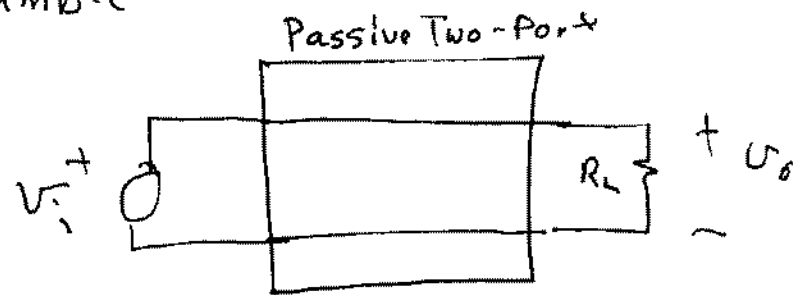

$$\frac{v_o}{v_i} = 1 \quad \text{Why will this not serve as a buffer since } A_v = 1 \text{ ?}$$


• No power gain

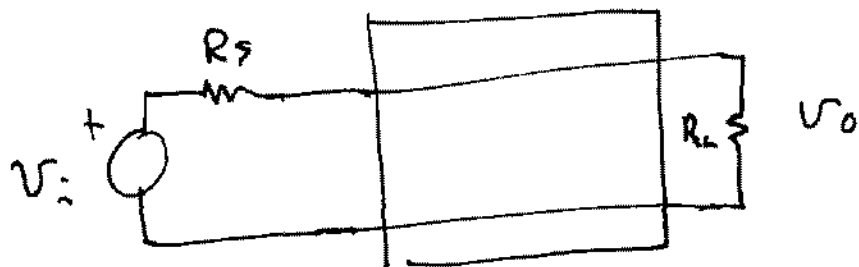

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_s}$$

• Gain dependent upon R_s

Power Gain of Buffer

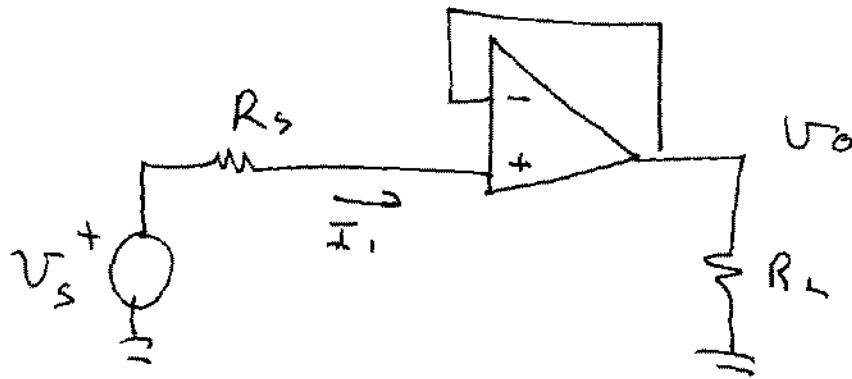

$$I_i = 0 \quad \therefore \quad P_s = (V_s)(I_i) = 0$$

$$P_L = \frac{V_o^2}{R_L} = \frac{V_s^2}{R_L}$$

\therefore Power gain is infinite

When is input impedance not a problem?

a) If $R_s = 0$


b) If R_s is a known constant
(Not versatile)

c) When accuracy not a problem

1) $R_s \ll R_i$

2) Audio to end user

Inverting Integrator

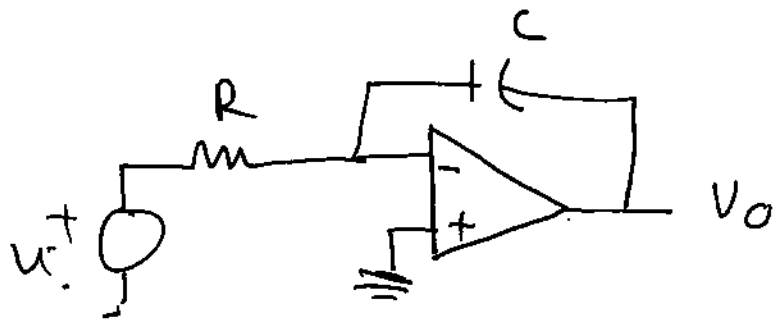


$$\frac{V_o}{V_i} = -\frac{1}{RCs}$$

Inverting because gain is negative

$$R_o = 0$$

$$R_{in} = R$$

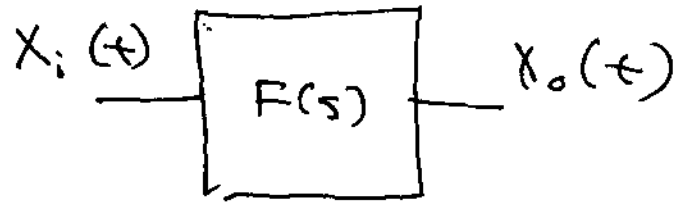- Seldom used in open-loop application
- widely used in feedback application




If $X_i(t)$ has any dc component

$$F(s) = 1/s$$

$$\begin{aligned}
 X_o(t) &= \int_0^{\infty} X_i(t) dt = \int_0^{\infty} \left(A_0 + A_1 \sin(\omega t + \theta_1) + \dots \right) dt \\
 &= \int_0^{\infty} A_0 dt + A_1 \int_0^{\infty} \sin(\omega t + \theta_1) dt + A_2 \int_0^{\infty} \sin(2\omega t + \theta_2) dt + \dots \\
 &\quad \left. \begin{array}{l} \int_0^{\infty} A_0 dt \\ \lim_{t \rightarrow \infty} A_0(t) \end{array} \right\} \text{diverge to } \infty
 \end{aligned}$$


- Integrator function is ill-conditioned for open loop applications
-

Method for approx. open loop integration

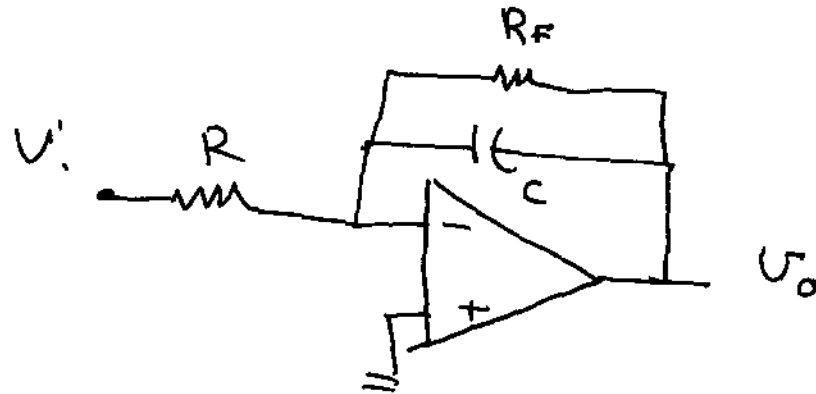


- R_F very large
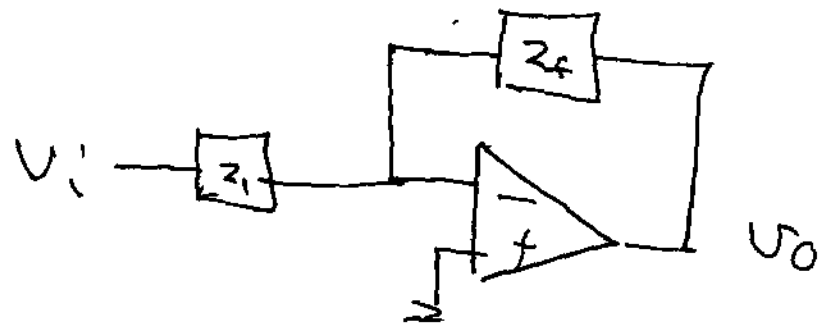
$$V_o \approx -\frac{1}{Rc} \int_0^t V_i(t) dt + V_i(0)$$



Lossy Integrator

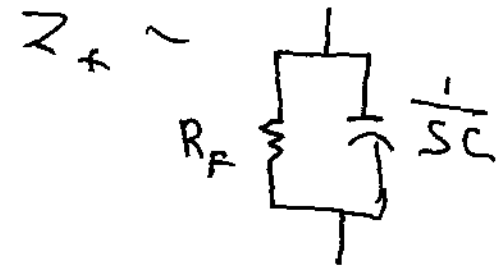


$$Z_f = \frac{(R_f) \parallel \frac{1}{sC}}{R_f + \frac{1}{sC}} = \frac{R_f}{1 + R_f C s}$$

$$\frac{v_o}{v_i} = - \frac{Z_f}{Z_1} = - \frac{R_f}{(1 + R_f C s) R}$$

Ideally $R_f = \infty$





$$\frac{v_o}{v_i} = - \frac{1}{R C s}$$

$$\left| \frac{v_o}{v_i} \right| = \frac{R_f/R}{\sqrt{1 + (R_f C \omega)^2}}$$

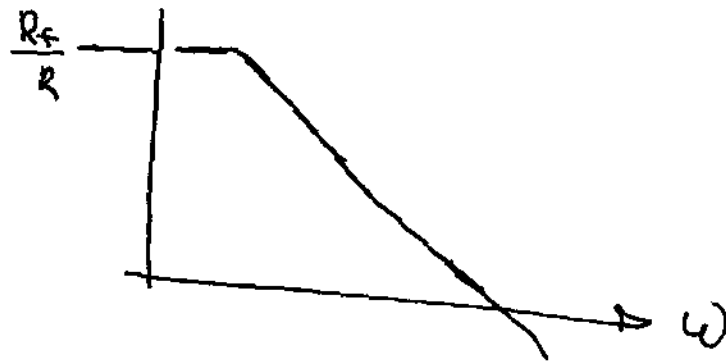

Noninverting Integrator.

Temptation

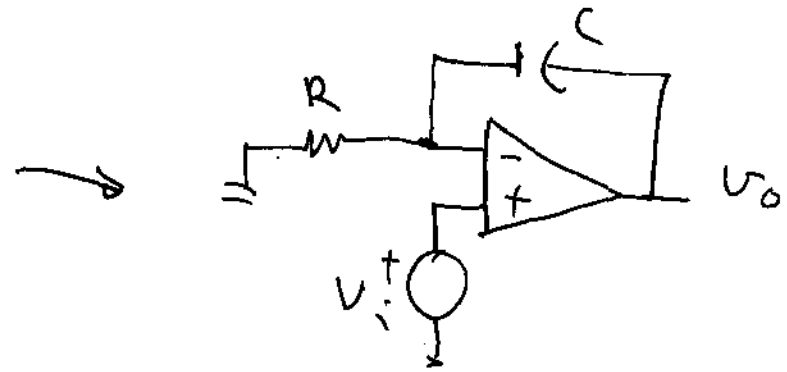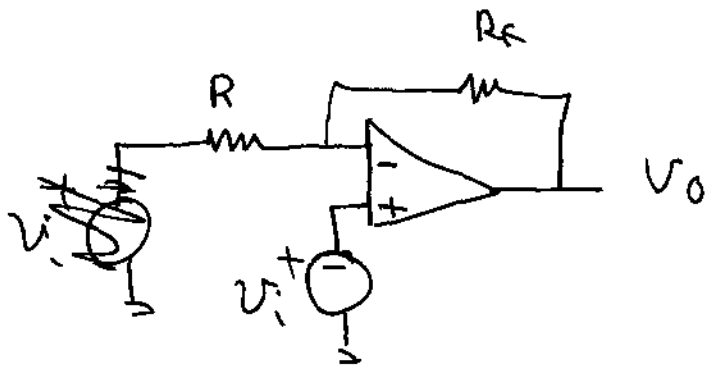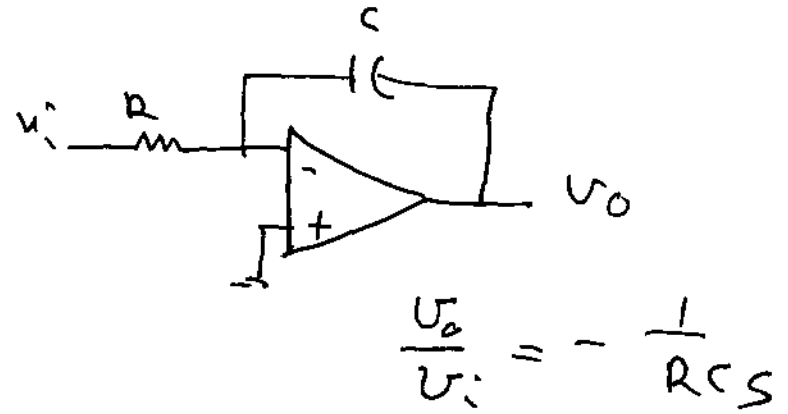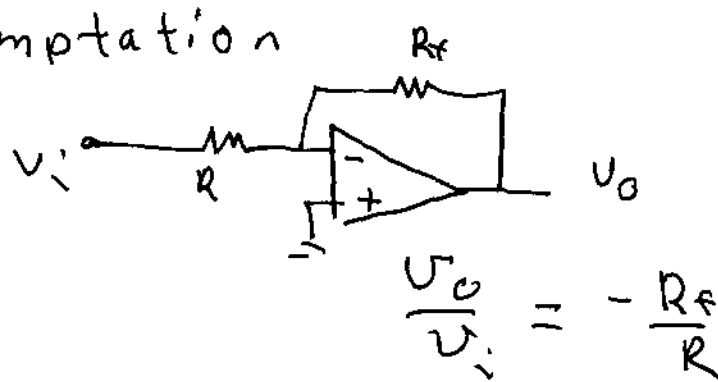


$$v_i = v_o \left(\frac{R}{R + 1/sC} \right)$$

$$v_i = v_o \frac{RCS}{1 + RCS}$$

$$\therefore \frac{v_o}{v_i} = \frac{1 + RCS}{RCS}$$

This is not a noninverting integrator

Noninverting Integrator

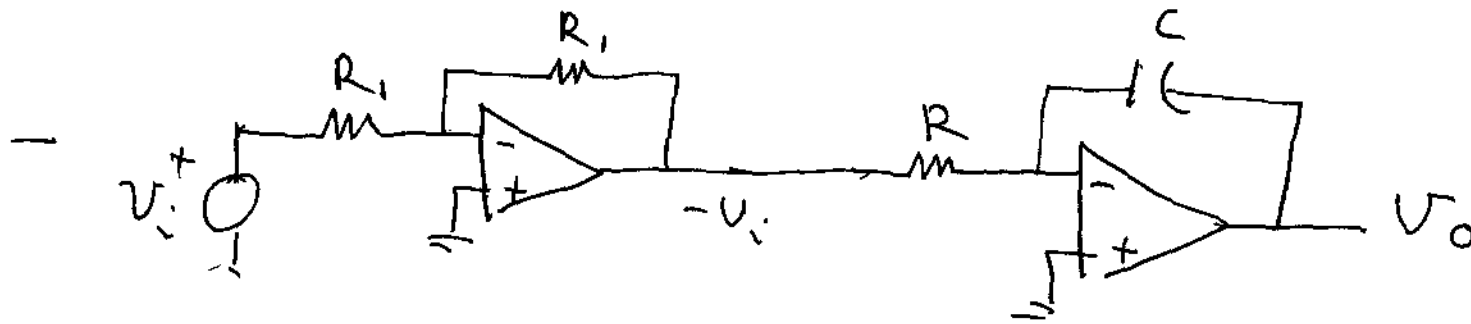


$$V_o = \frac{1}{RCS} V_i$$

— follow inverting integrator with inverter instead

- Most popular noninverting integrator structure

Noninverting Integrator

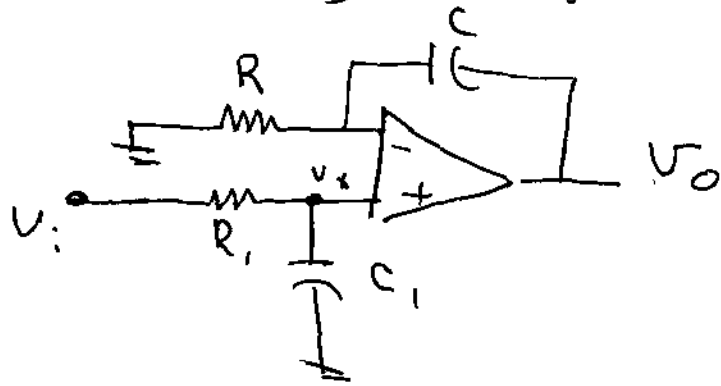

$$V_x = \frac{1}{sC_i} V_i = \frac{1}{1 + R_i C_i s} V_i$$

$$V_x = \frac{R}{R + 1/sC} V_o = \frac{RCS}{1 + RCS} V_o$$

$$\frac{V_o}{V_i} = \left(\frac{1}{1 + R_i C_i s} \right) \left(\frac{1 + RCS}{RCS} \right)$$

IF $R_i C_i = RC$ (pole/zero cancellation)


$$\frac{V_o}{V_i} = \frac{1}{RCS}$$

Advantage: eliminated one opamp

Disadvantage: - two capacitors

- precise relationships between $R_i C_i = RC$

Summing Inverting Integrator.

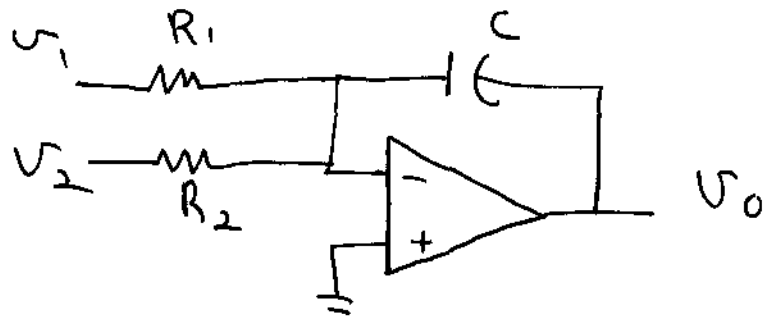

$$V_0 = -\frac{1}{R_1 C S} V_1 - \frac{1}{R_2 C S} V_2$$

Applications to solving differential equations.

Example:

$$\underline{V_0 = K_1 \int V_0 + K_2 \iint V_0 + K_3 V_i}$$

standard
integral form


$$V_0' = K_1 V_0 + K_2 \int V_0 + K_3 V_i'$$



$$V_0'' = K_1 V_0' + K_2 V_0 + K_3 V_i''$$

$$\underline{V_0 = a_1 V_0' + a_2 V_0'' + a_3 V_i''}$$

standard
differential
form

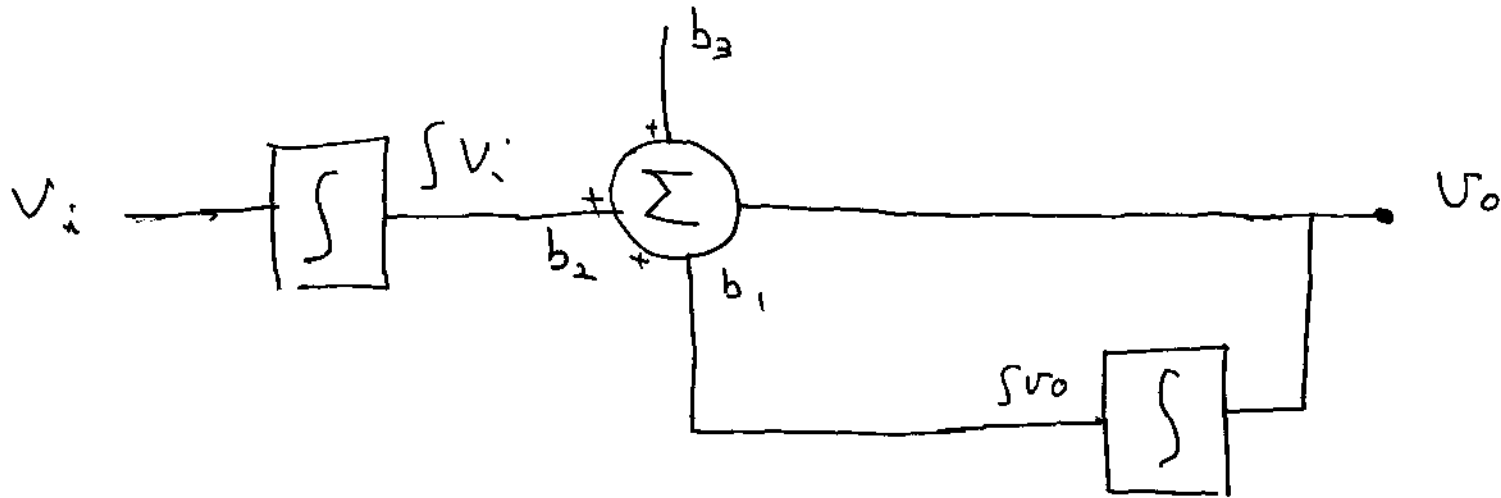
$$v_o = b_1 \int v_o + b_2 \int v_i + b_3$$



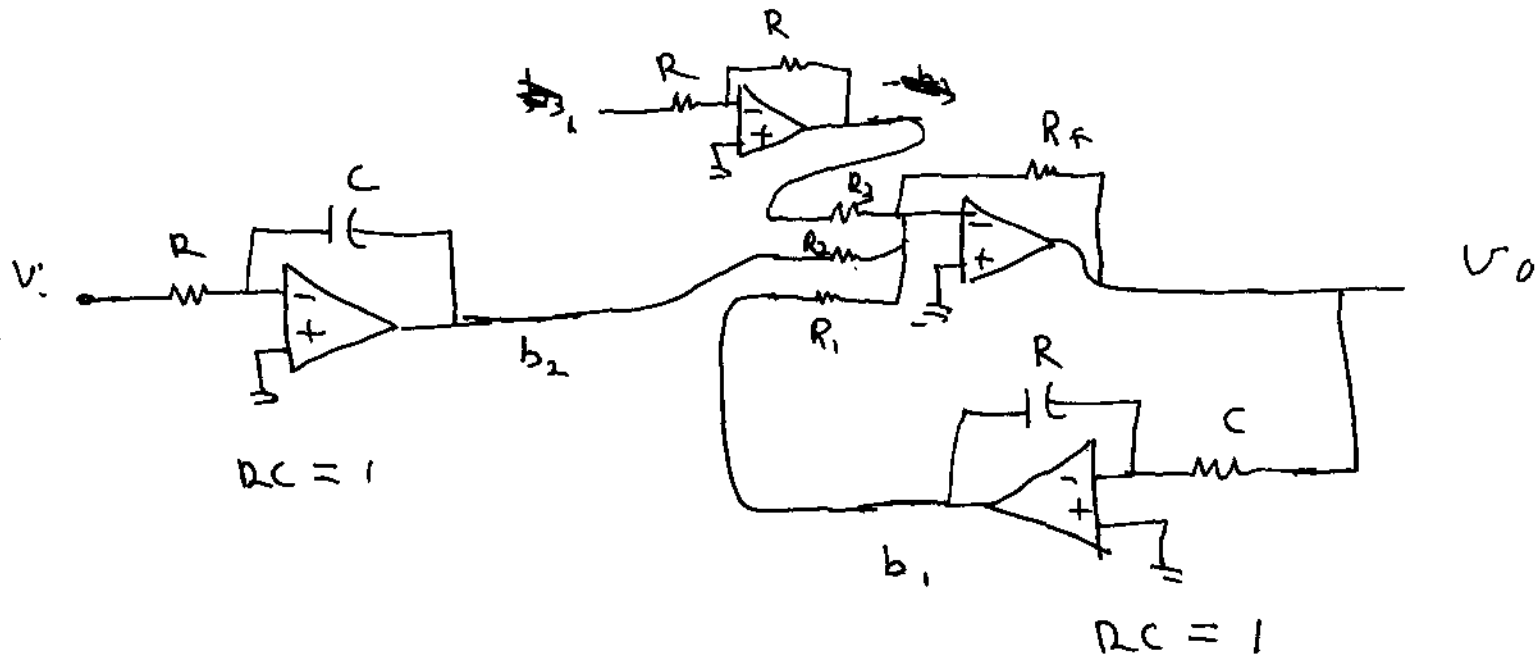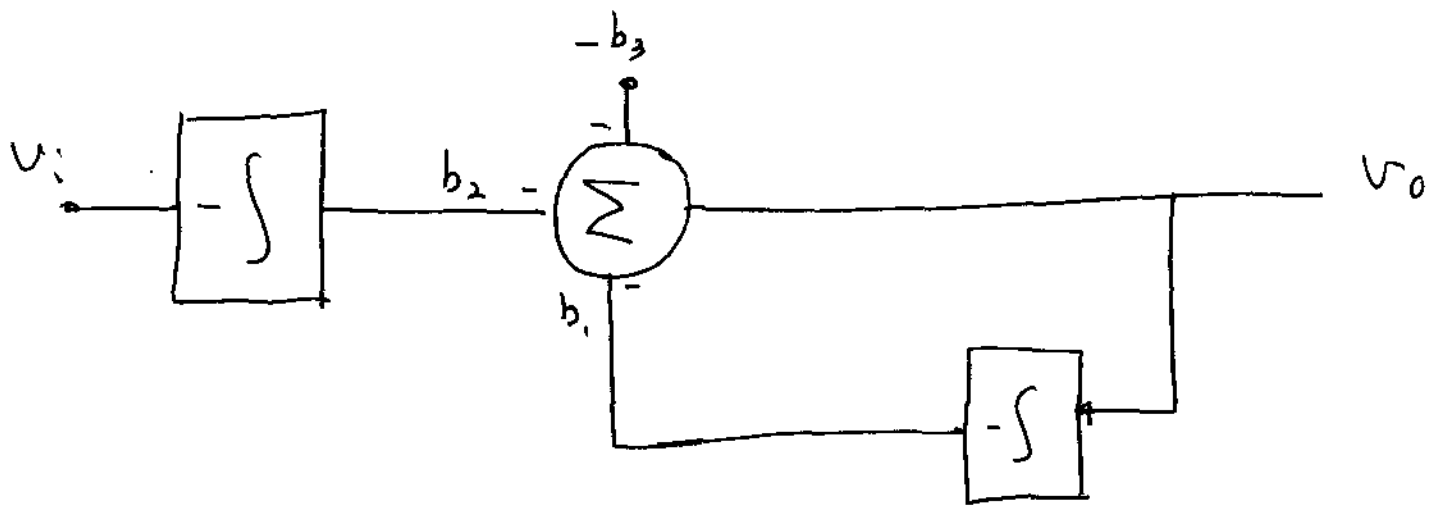

$$\frac{R_f}{R_1} = b_1 \quad \frac{R_f}{R_2} = b_2 \quad \frac{R_f}{R_3} = b_3$$

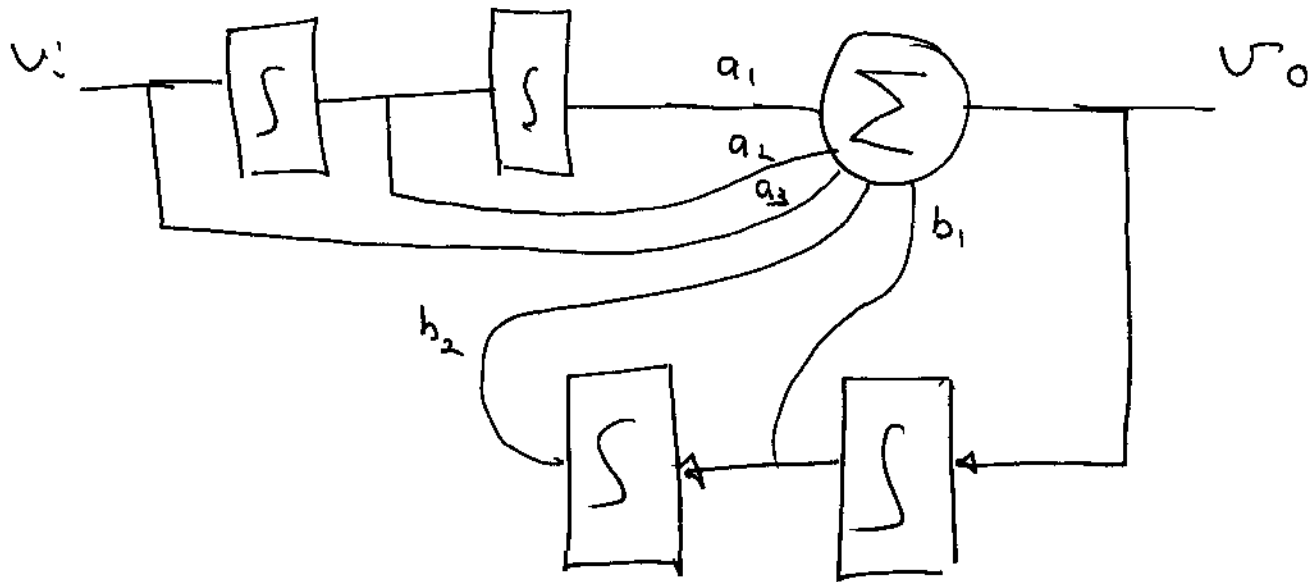- Straightforward to solve an arbitrary differential equation with inverting integrators, summing amplifiers and inverters
- Analog Computer solves differential equations



$$U_0 = \frac{a_1 U_i}{s} + \frac{a_2 U_i}{s^2} + a_3 U_i + \frac{b_1 U_0}{s} + \frac{b_2 U_0}{s^2}$$

$$\frac{U_0}{U_i} = \frac{a_3 s^2 + a_2 s + a_1}{s^2 - b_1 s - b_2}$$

any coeff can be positive or negative or zero

Arbitrary transfer function synthesis is easy to achieve.

$$U_0 = \frac{1}{b_2} U_0'' - \frac{b_1}{b_2} U_0' - \frac{a_1}{b_2} U_i - \frac{a_2}{b_2} U_i' - \frac{a_3}{b_2} U_i''$$


$$U_0 = \alpha_2 U_0'' + \alpha_1 U_0' + \beta_0 U_i + \beta_1 U_i' + \beta_2 U_i''$$

standard differential form

Differential Amplifiers.

$$V_o = K(V_2 - V_1)$$

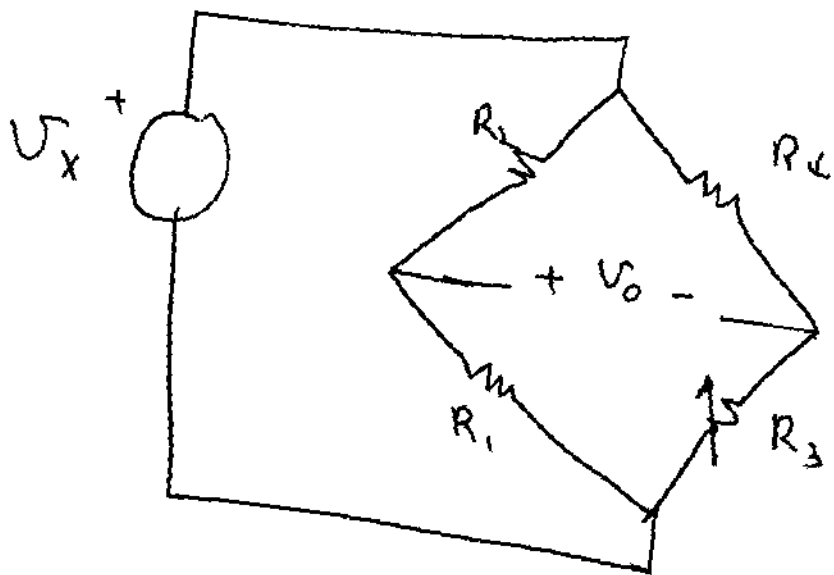Information is carried in difference of two voltages.



V_x might be large ($V_x = 10 \sin \omega t$)
 $V_o \sim (10^{-6}) \sin \omega t$