

# EE 230

## Lecture 12

Basic Applications of Operational Amplifiers


Generalized Impedances

Integrators

Analog Computation
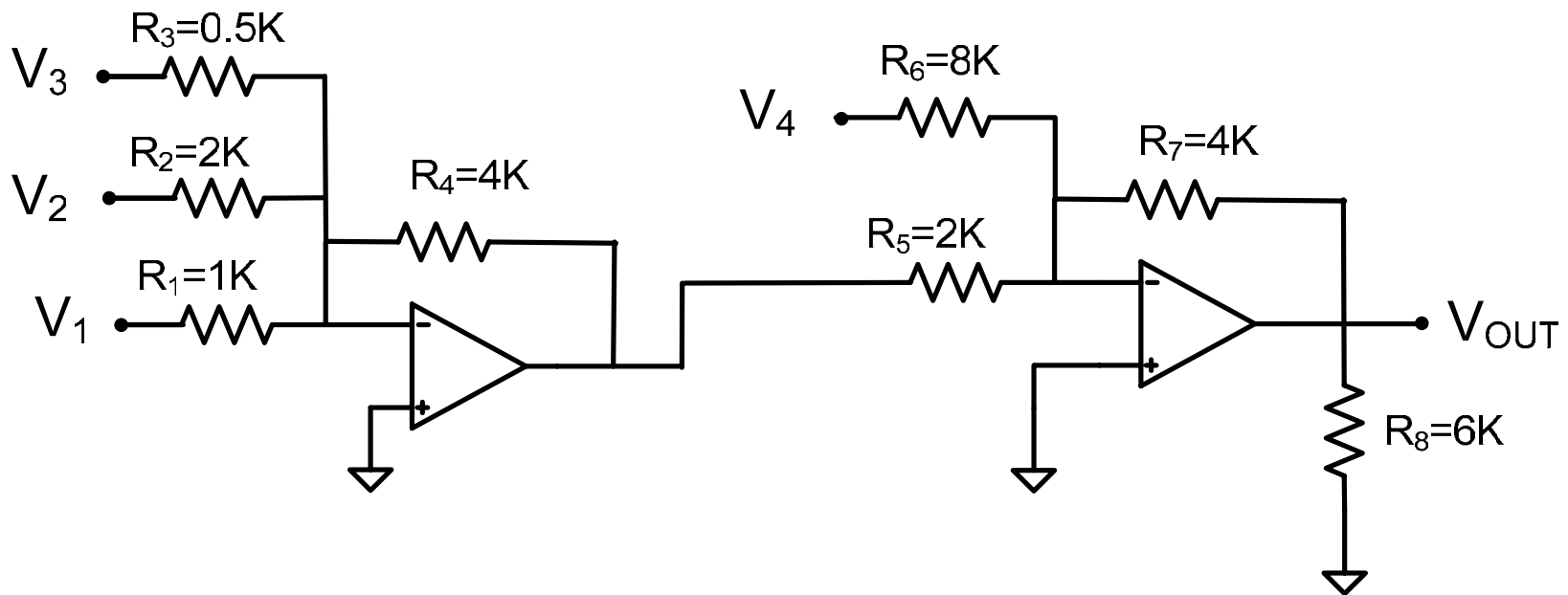
# Quiz 9

Determine the output voltage for the following circuit. Assume the op amps are ideal.



And the number is ?

1

3

8

5

4

2

6

9

7

And the number is ?

1

3

8

5

4

2

6

9


5

7

# Quiz 9
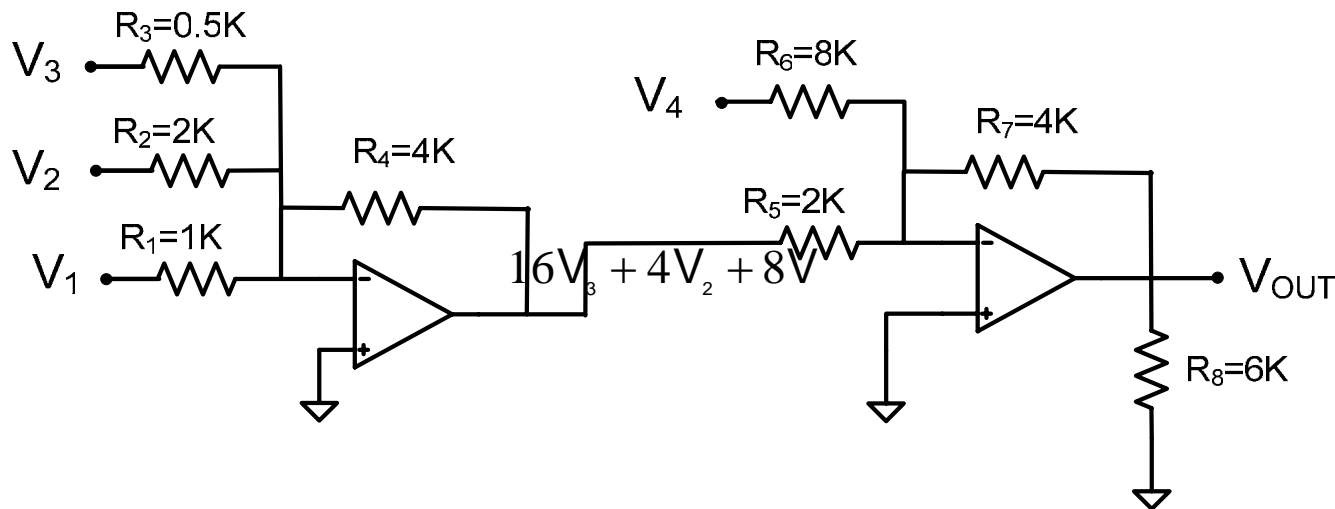
# Solution:

Determine the output voltage for the following circuit. Assume the op amps are ideal.



By superposition


$$V_{OUT} = -\frac{R_7}{R_6} V_4 - \frac{R_7}{R_5} \left( -\frac{R_4}{R_3} V_3 - \frac{R_4}{R_2} V_2 - \frac{R_4}{R_1} V_1 \right)$$

$$V_{OUT} = -0.5V_4 + 16V_3 + 4V_2 + 8V_1$$
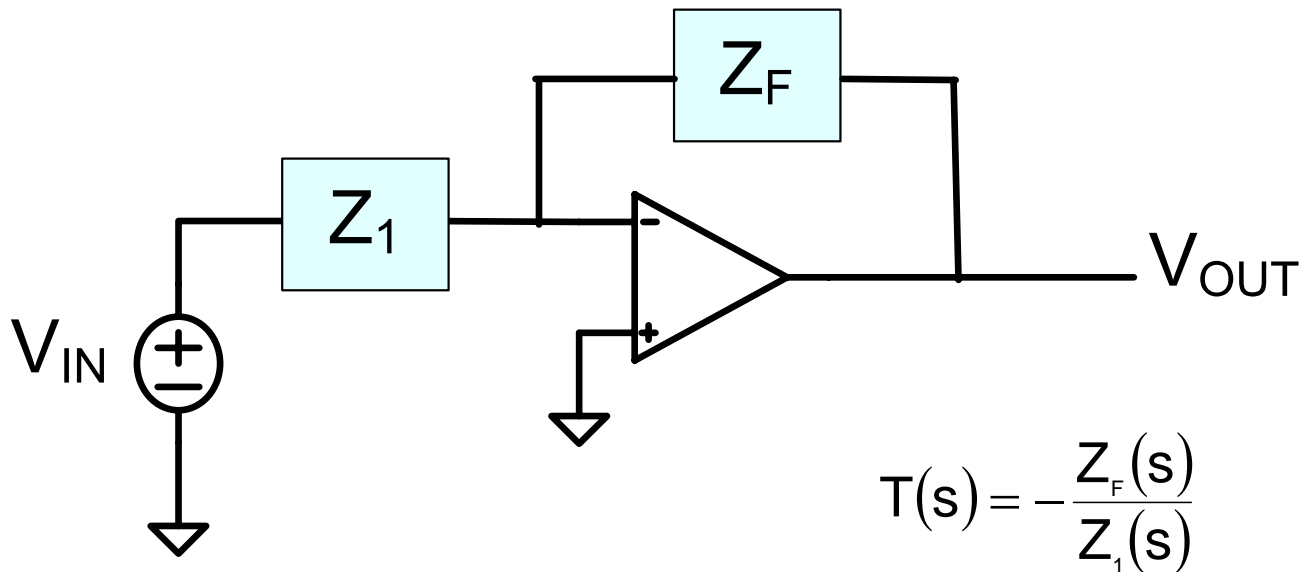
## Review from Last Time

Summing Amplifiers with mixed weights on inverting and noninverting inputs can be readily obtained

Integration and Differentiation functions can be obtained from the basic generalized feedback amplifier structure



# Integration and Differentiation

## Integration

$$y(t) = K \int_{\tau=0}^t x(\tau) d\tau$$

$$\mathcal{L}(y(t)) = \frac{K}{s} \mathcal{L}(x(t))$$

$$Y(s) = \frac{K}{s} X(s)$$

# Integration and Differentiation

## Differentiation


$$y(t) = K \frac{dx(t)}{dt}$$

$$\mathcal{L}(y(t)) = Ks\mathcal{L}(x(t)) - x(0)$$

$$Y(s) = KsX(s) - x(0)$$




# Generalized Inverting Amplifier

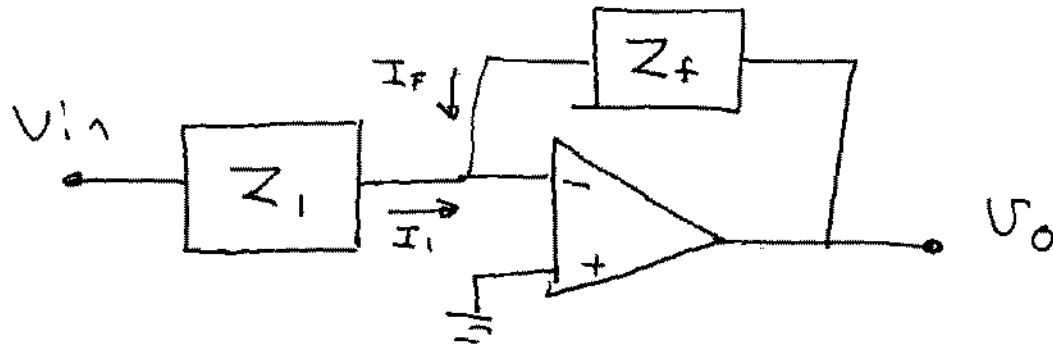

s-domain  
impedances

$$\left. \begin{aligned} I_i &= \frac{V_{in}}{Z_1} \\ I_f &= \frac{V_o}{Z_f} \\ I_i &= -I_f \end{aligned} \right\} \frac{V_o}{V_{in}} = -\frac{Z_f}{Z_1}$$

What if  $Z_F = 1/sC$  ,  $Z_i = R$

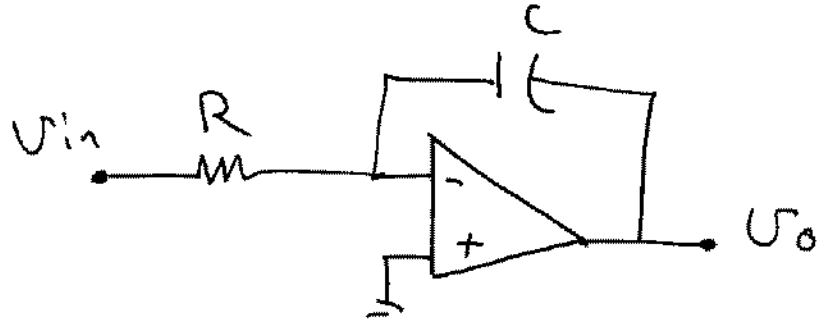

$$\frac{v_o}{v_i} = - \frac{1}{RCs}$$



What is this?


$$T(s) = -\frac{1}{RCs}$$

$$T(j\omega) = -\frac{1}{j\omega RC}$$

$$|T(j\omega)| = \frac{1}{\omega RC}$$

Integrator Gain

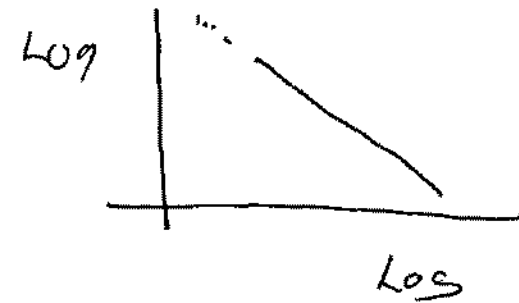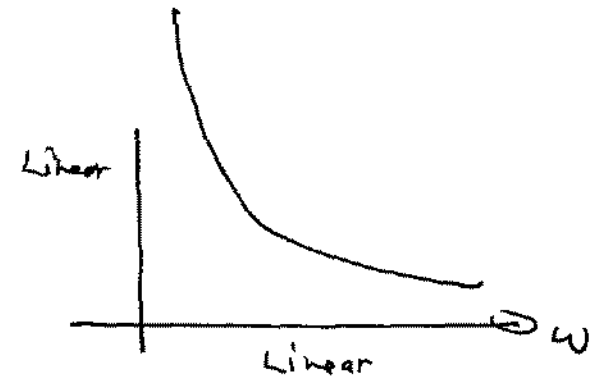

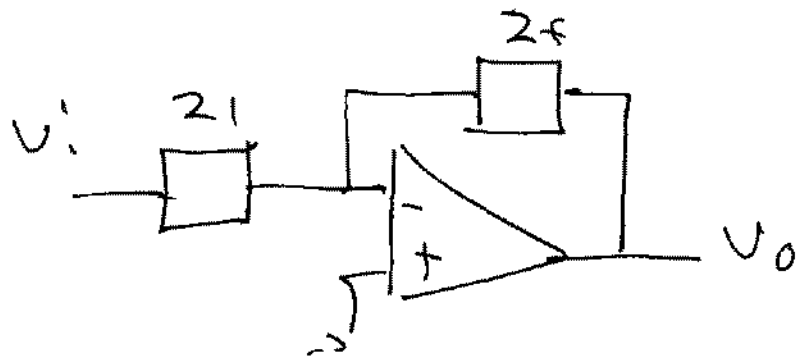

$$\frac{v_o}{v_i} = -\frac{Z_f}{Z_1}$$

$$\text{Let } Z_1 = \frac{1}{sC}$$


$$Z_f = R$$

$$\therefore \frac{v_o}{v_i} = -\frac{sCR}{1}$$

Differentiator (Inverting)

- Not widely used
- Noise relentlessly amplified
- stability problems with implementation

# Inverting Integrator

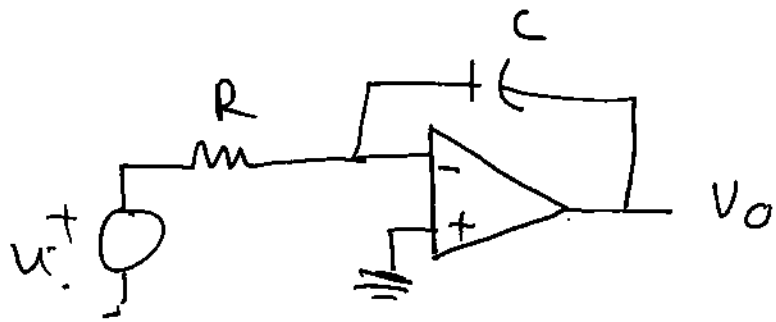


$$\frac{V_o}{V_i} = -\frac{1}{RCs}$$

Inverting because gain is negative

$$R_o = 0$$

$$R_{in} = R$$

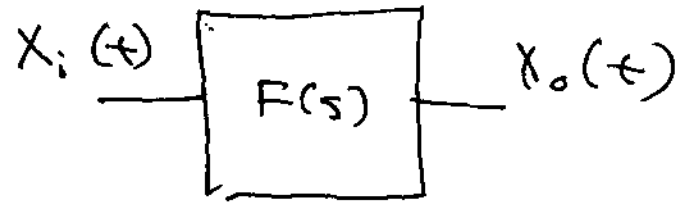- Seldom used in open-loop application
- widely used in feedback application



If  $X_i(t)$  has any dc component

$$F(s) = 1/s$$

$$X_o(t) = \int_0^{\infty} X_i(t) dt = \int_0^{\infty} (A_0 + A_1 \sin(\omega t + \theta_1) + \dots) dt$$


$$= \int_0^{\infty} A_0 dt + A_1 \int_0^{\infty} \sin(\omega t + \theta_1) dt + A_2 \int_0^{\infty} \sin(2\omega t + \theta_2) dt + \dots$$

$$\lim_{t \rightarrow \infty} A_0(t)$$

diverge to  $\infty$


- Integrator function is ill-conditioned for open loop applications
- 

Method for approx. open loop integration

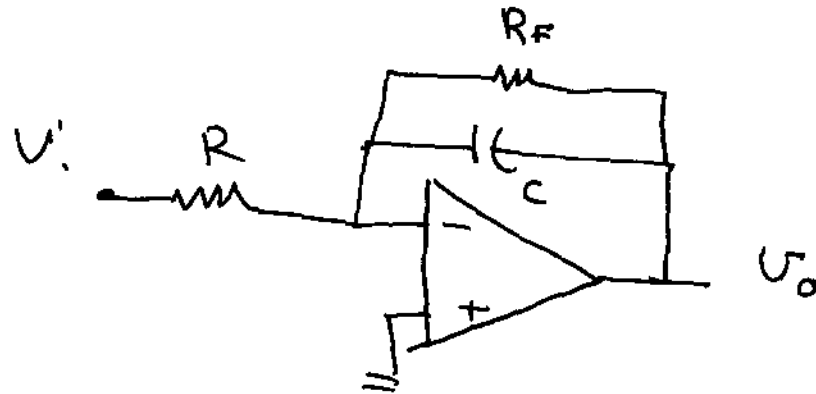


- $R_F$  very large
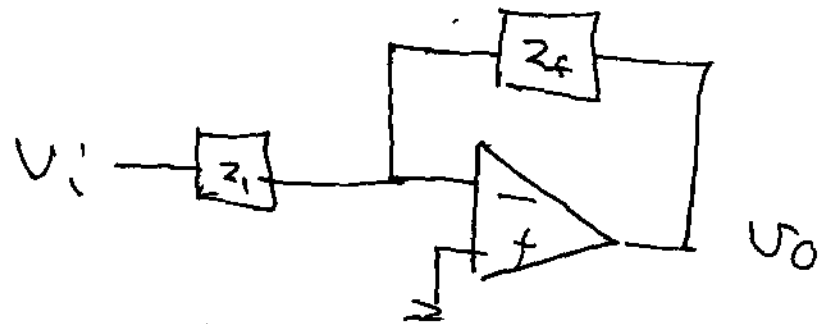
$$V_o \approx -\frac{1}{Rc} \int_0^t V_i(t) dt + V_i(0)$$



Lossy Integrator

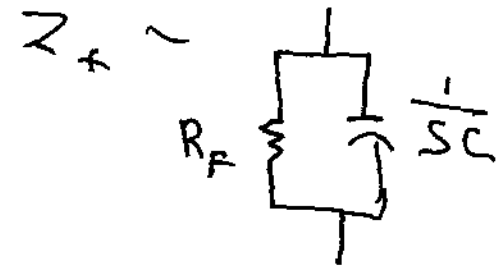


$$Z_f = \frac{(R_f) \parallel \frac{1}{sC}}{R_f + \frac{1}{sC}} = \frac{R_f}{1 + R_f C s}$$

$$\frac{v_o}{v_i} = - \frac{Z_f}{Z_1} = - \frac{R_f}{(1 + R_f C s) R}$$

Ideally  $R_f = \infty$

$$\frac{v_o}{v_i} = - \frac{1}{R C s}$$





$$\left| \frac{v_o}{v_i} \right| = \frac{R_f/R}{\sqrt{1 + (R_f C \omega)^2}}$$

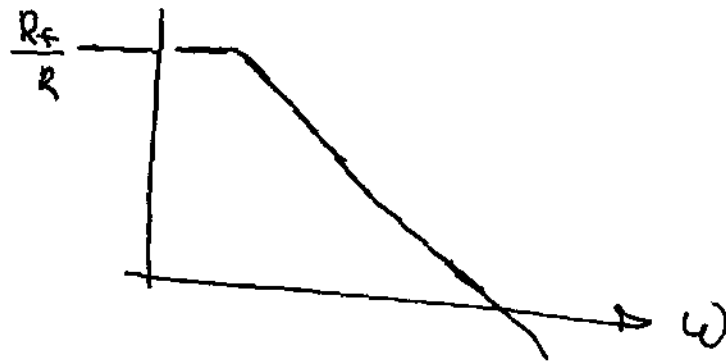



# Noninverting Integrator.

Temptation

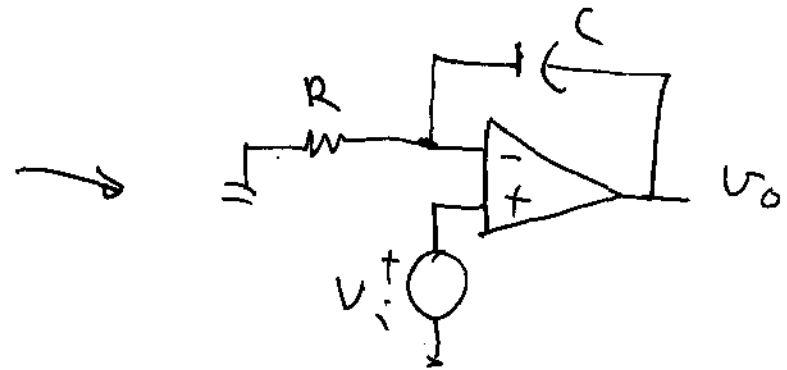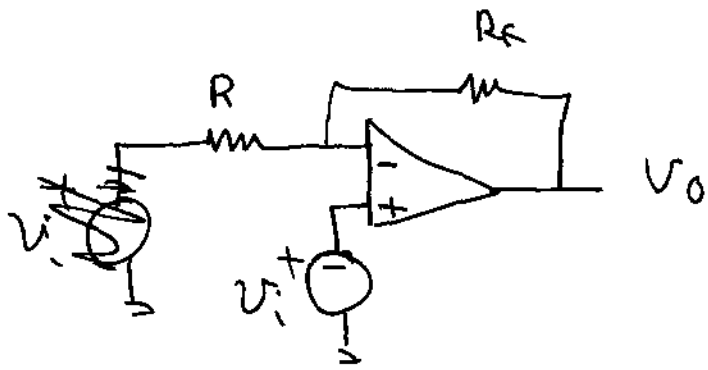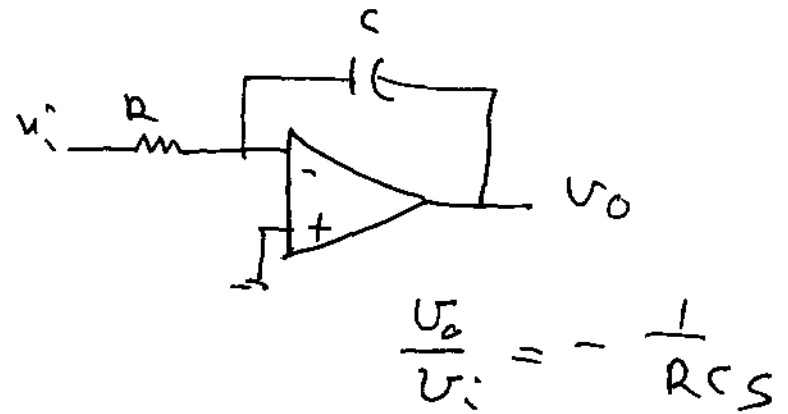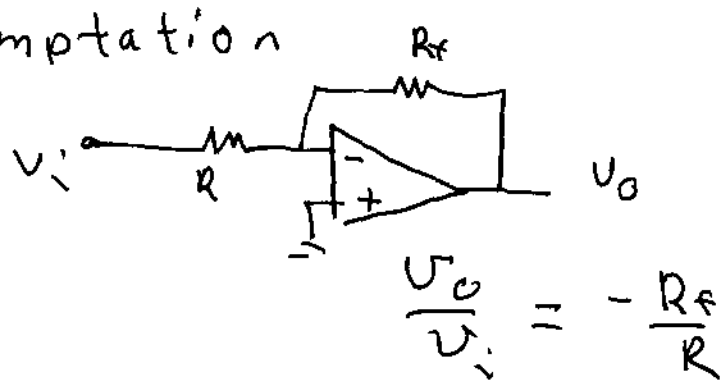


$$v_i = v_o \left( \frac{R}{R + 1/sc} \right)$$

$$v_i = v_o \frac{Rcs}{1 + Rcs}$$

$$\therefore \frac{v_o}{v_i} = \frac{1 + Rcs}{Rcs}$$

This is not a noninverting integrator

# Noninverting Integrator

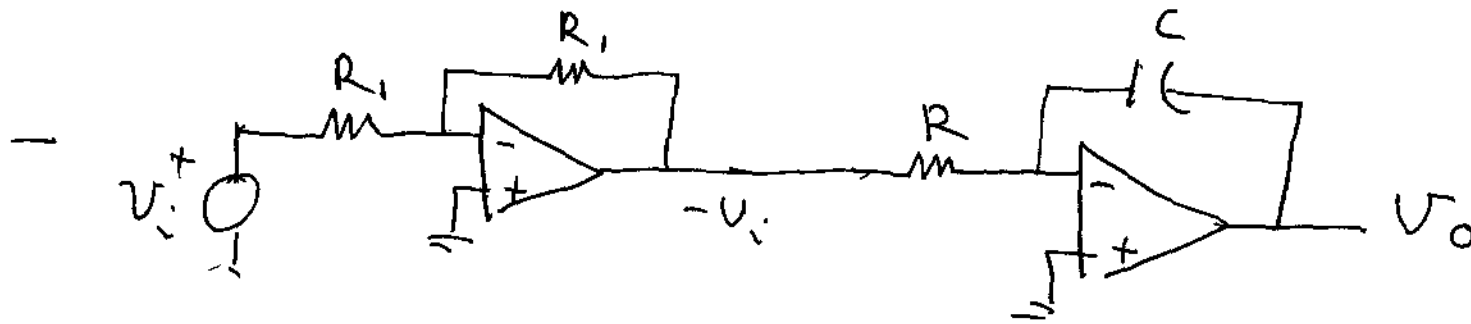


$$V_o = \frac{1}{R_1 C} V_i$$

— follow inverting integrator with inverter instead

- Most popular noninverting integrator structure

# Noninverting Integrator

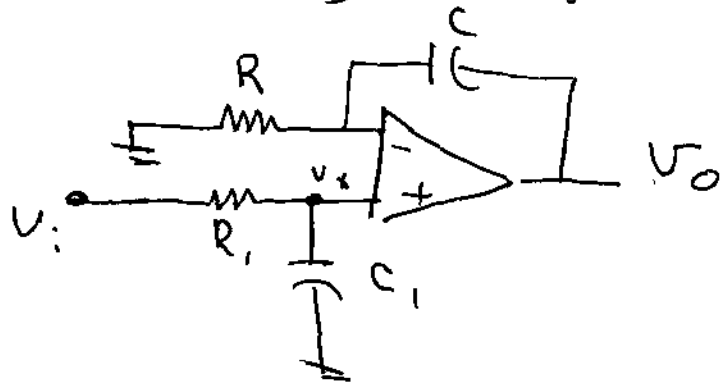

$$V_x = \frac{1}{sC_i} V_i = \frac{1}{1 + R_i C_i s} V_i$$

$$V_x = \frac{R}{R + 1/sC} V_o = \frac{RCS}{1 + RCS} V_o$$

$$\frac{V_o}{V_i} = \left( \frac{1}{1 + R_i C_i s} \right) \left( \frac{1 + RCS}{RCS} \right)$$

IF  $R_i C_i = RC$  (pole/zero cancellation)


$$\frac{V_o}{V_i} = \frac{1}{RCS}$$

Advantage: eliminated one opamp

Disadvantage: - two capacitors

- precise relationships between  $R_i C_i = RC$

Summing Inverting Integrator.

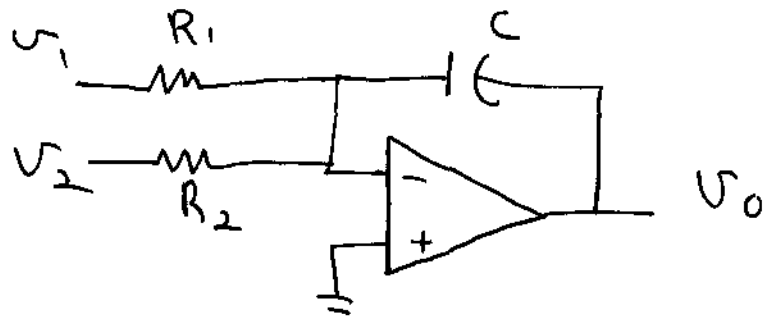

$$V_0 = -\frac{1}{R_1 C S} V_1 - \frac{1}{R_2 C S} V_2$$

# Applications to solving differential equations.

Example:

$$\underline{V_0 = K_1 \int V_0 + K_2 \iint V_0 + K_3 V_i}$$

standard  
integral form


$$V_0' = K_1 V_0 + K_2 \int V_0 + K_3 V_i'$$



$$V_0'' = K_1 V_0' + K_2 V_0 + K_3 V_i''$$

$$\underline{V_0 = a_1 V_0' + a_2 V_0'' + a_3 V_i''}$$

standard  
differential  
form
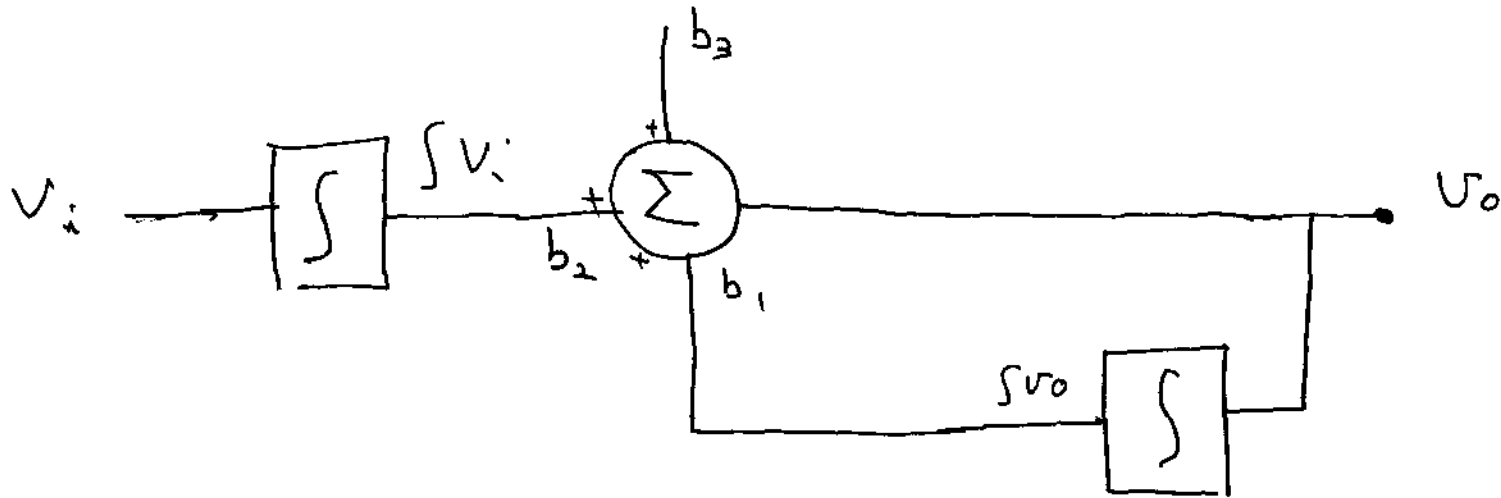
$$v_o = b_1 \int v_o + b_2 \int v_i + b_3$$



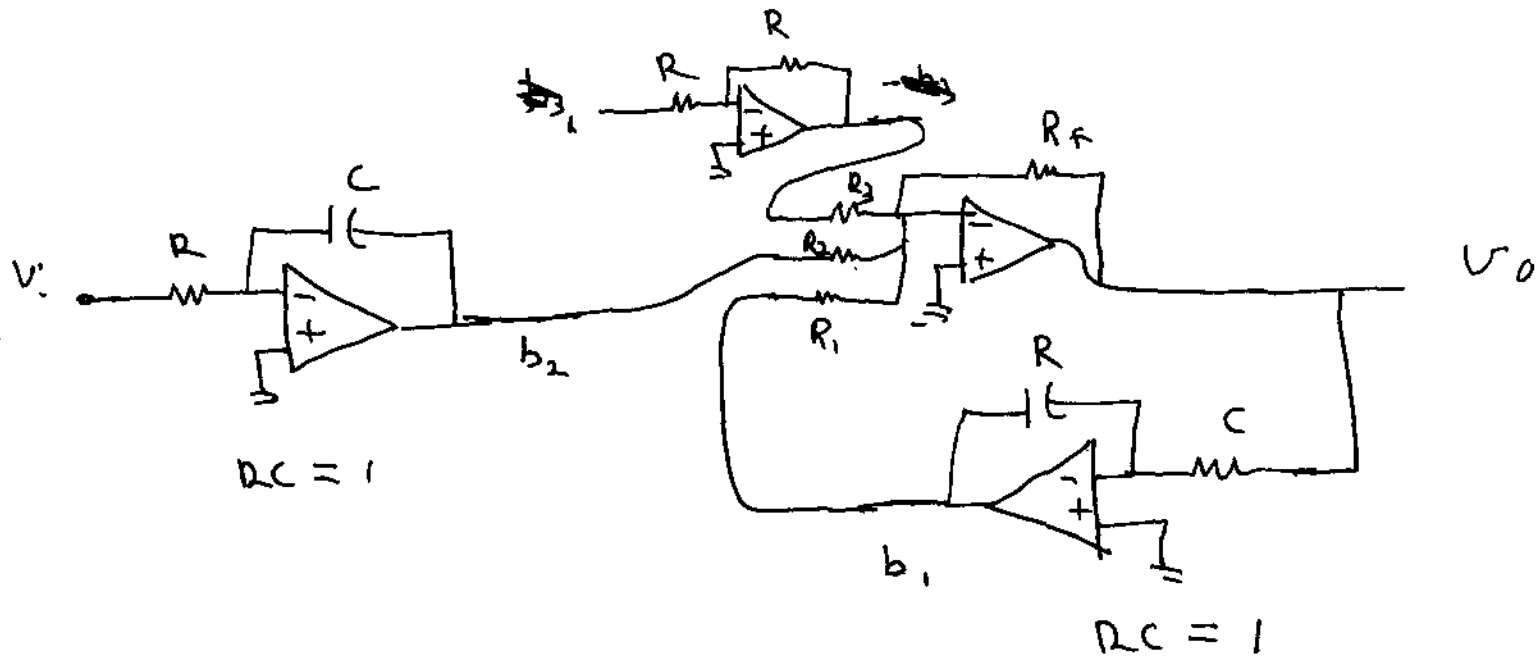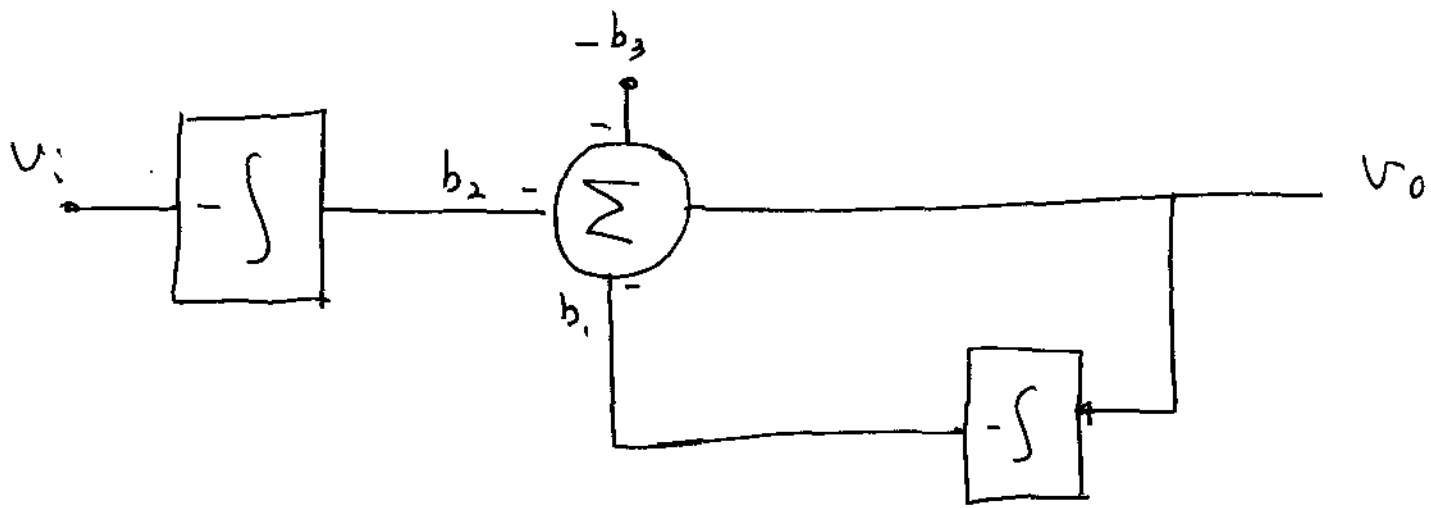


$$\frac{R_f}{R_1} = b_1 \quad \frac{R_f}{R_2} = b_2 \quad \frac{R_f}{R_3} = b_3$$

- Straightforward to solve an arbitrary differential equation with inverting integrators, summing amplifiers and inverters
- Analog Computer solves differential equations



**End of lecture**

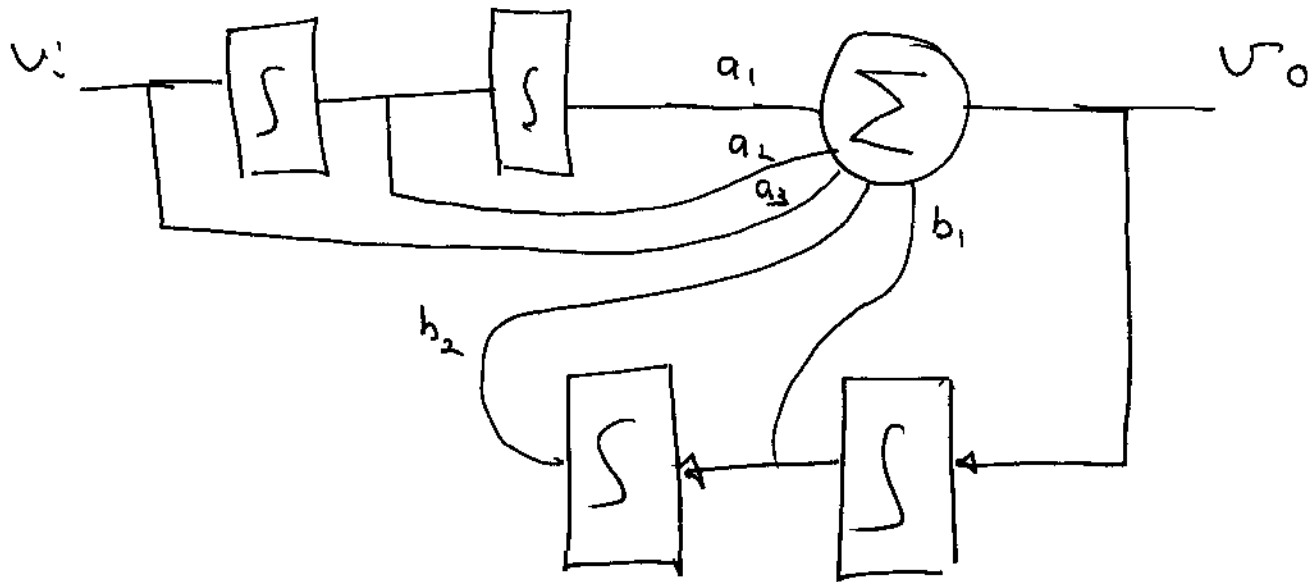

$$U_0 = \frac{a_1 U_i}{s} + \frac{a_2 U_i}{s^2} + a_3 U_i + \frac{b_1 U_0}{s} + \frac{b_2 U_0}{s^2}$$

$$\frac{U_0}{U_i} = \frac{a_3 s^2 + a_2 s + a_1}{s^2 - b_1 s - b_2}$$

any coeff can be positive or negative or zero

Arbitrary transfer function synthesis is easy to achieve.

$$U_0 = \frac{1}{b_2} U_0'' - \frac{b_1}{b_2} U_0' - \frac{a_1}{b_2} U_i - \frac{a_2}{b_2} U_i' - \frac{a_3}{b_2} U_i''$$

$$U_0 = \alpha_2 U_0'' + \alpha_1 U_0' + \beta_0 U_i + \beta_1 U_i' + \beta_2 U_i''$$

standard differential form