

# EE 230

## Lecture 14

Basic Feedback Configurations

Second-Order Filters


Difference Amplifiers

Impedance Converters

# Quiz 10

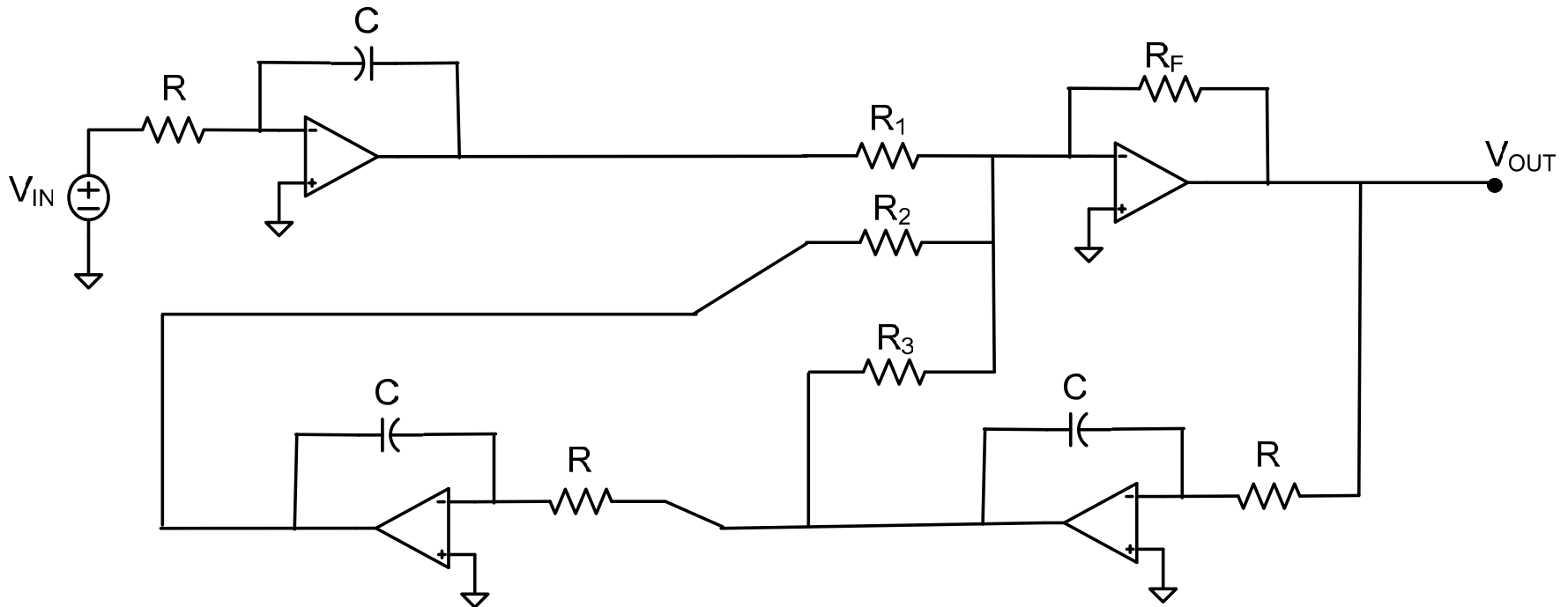- a) Determine the transfer function  $T(s)=V_{OUT}(s)/V_{IN}(s)$  for the circuit shown
- b) Is the circuit stable?

Assume the op amps are ideal and all resistors are  $1\Omega$  and all capacitors are  $1F$



And the number is ?

1

3

8

5

?

4

2

6


9

7

# Quiz 10
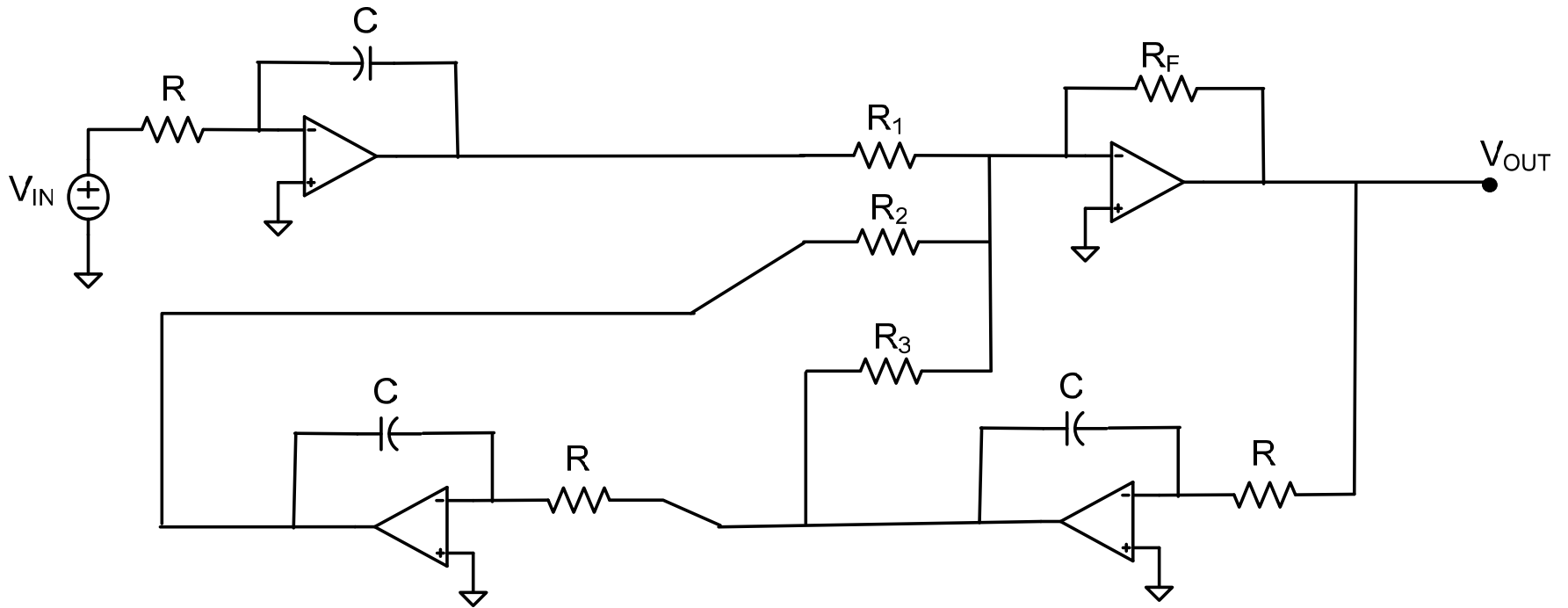
## Solution:


- Determine the transfer function  $T(s) = V_{OUT}(s)/V_{IN}(s)$  for the circuit shown
- Is the circuit stable?



# Quiz 10

## Solution:

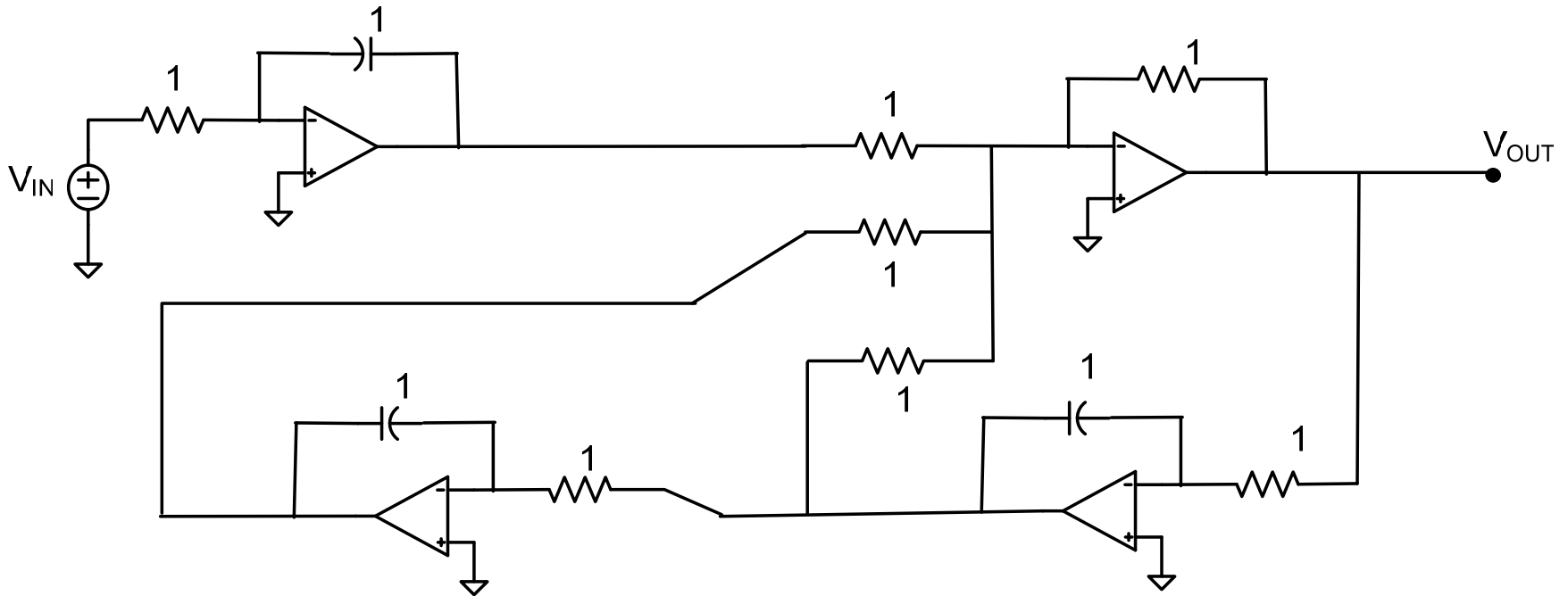
- a) Determine the transfer function  $T(s) = V_{OUT}(s)/V_{IN}(s)$  for the circuit shown
- b) Is the circuit stable?



# Quiz 10
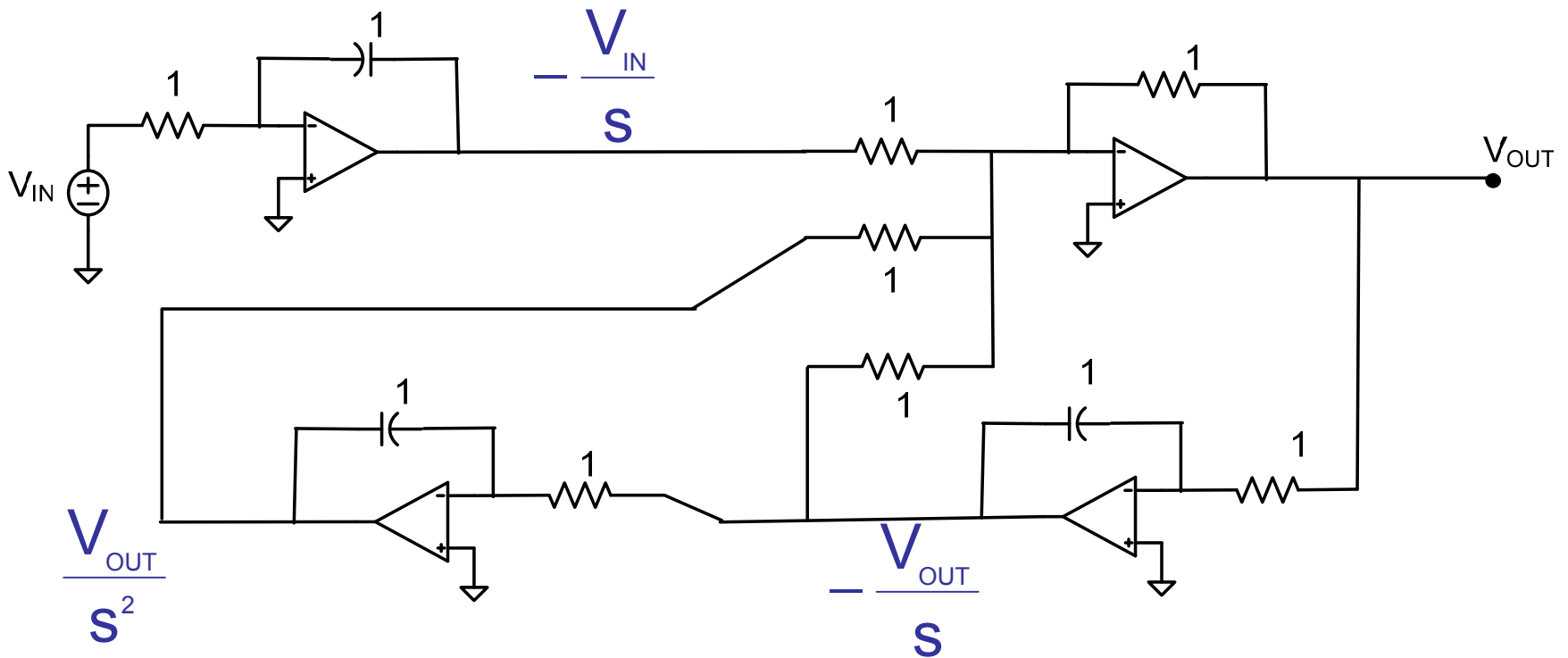
## Solution:


- Determine the transfer function  $T(s) = V_{OUT}(s)/V_{IN}(s)$  for the circuit shown
- Is the circuit stable?



# Quiz 10

## Solution:

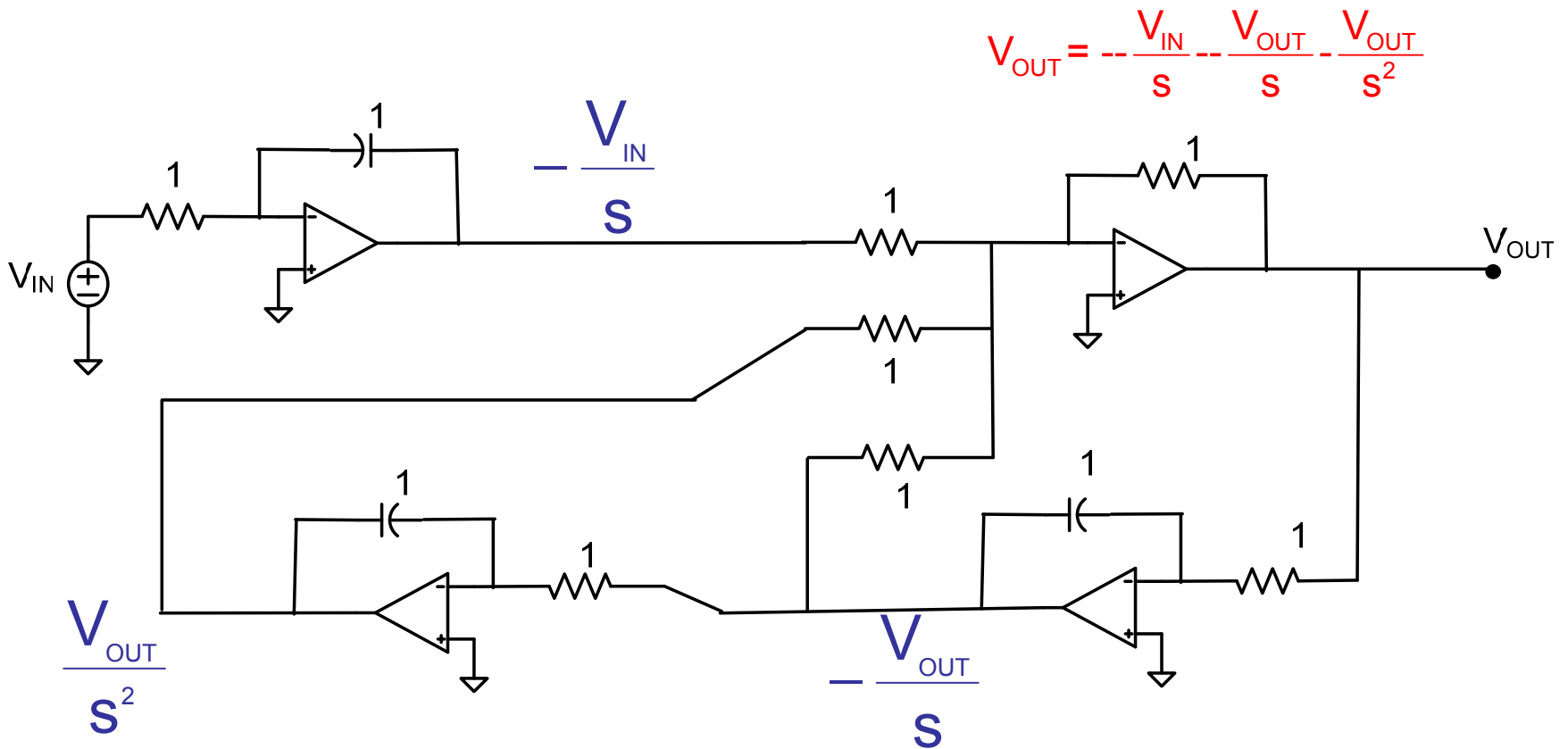- a) Determine the transfer function  $T(s) = V_{OUT}(s)/V_{IN}(s)$  for the circuit shown
- b) Is the circuit stable?



# Quiz 10

## Solution:

- a) Determine the transfer function  $T(s) = V_{OUT}(s)/V_{IN}(s)$  for the circuit shown
- b) Is the circuit stable?

$$V_{OUT} = -\frac{V_{IN}}{s} - \frac{V_{OUT}}{s} - \frac{V_{OUT}}{s^2}$$

$$s^2 V_{OUT} - s V_{OUT} + V_{OUT} = s V_{IN}$$

$$V_{OUT} (s^2 - s + 1) = s V_{IN}$$

$$T(s) = \frac{V_{OUT}}{V_{IN}} = \frac{s}{s^2 - s + 1}$$



# Quiz 10

## Solution:

- a) Determine the transfer function  $T(s) = V_{\text{OUT}}(s)/V_{\text{IN}}(s)$  for the circuit shown
- b) Is the circuit stable?

$$T(s) = \frac{V_{\text{OUT}}}{V_{\text{IN}}} = \frac{s}{s^2 - s + 1}$$

Poles at

$$s = \frac{1 + j\sqrt{3}}{2}$$

$$s = \frac{1 - j\sqrt{3}}{2}$$

# Quiz 10

## Solution:

- a) Determine the transfer function  $T(s) = V_{OUT}(s)/V_{IN}(s)$  for the circuit shown
- b) Is the circuit stable?

$$T(s) = \frac{V_{OUT}}{V_{IN}} = \frac{s}{s^2 - s + 1}$$

Poles at

$$s = \frac{1+j\sqrt{3}}{2}$$

RHP

$$s = \frac{1-j\sqrt{3}}{2}$$

RHP

# Quiz 10

## Solution:

- a) Determine the transfer function  $T(s) = V_{OUT}(s)/V_{IN}(s)$  for the circuit shown
- b) Is the circuit stable?

$$T(s) = \frac{V_{OUT}}{V_{IN}} = \frac{s}{s^2 - s + 1}$$

Poles at

$$s = \frac{1 + j\sqrt{3}}{2}$$


RHP

$$s = \frac{1 - j\sqrt{3}}{2}$$

LHP

Since there is one RHP pole, the circuit is unstable !

# Inverting Integrator

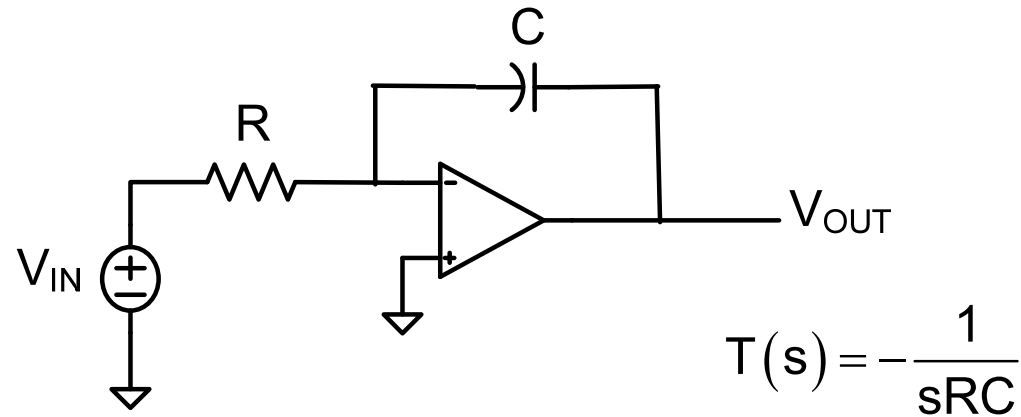

$$T(j\omega) = -\frac{1}{j\omega RC}$$


$$|T(j\omega)| = \frac{1}{\omega RC}$$

$$\angle T(j\omega) = 90^\circ$$

Unity gain frequency is  $\omega_0 = \frac{1}{RC}$

Review from Last Time

# Noninverting Integrator

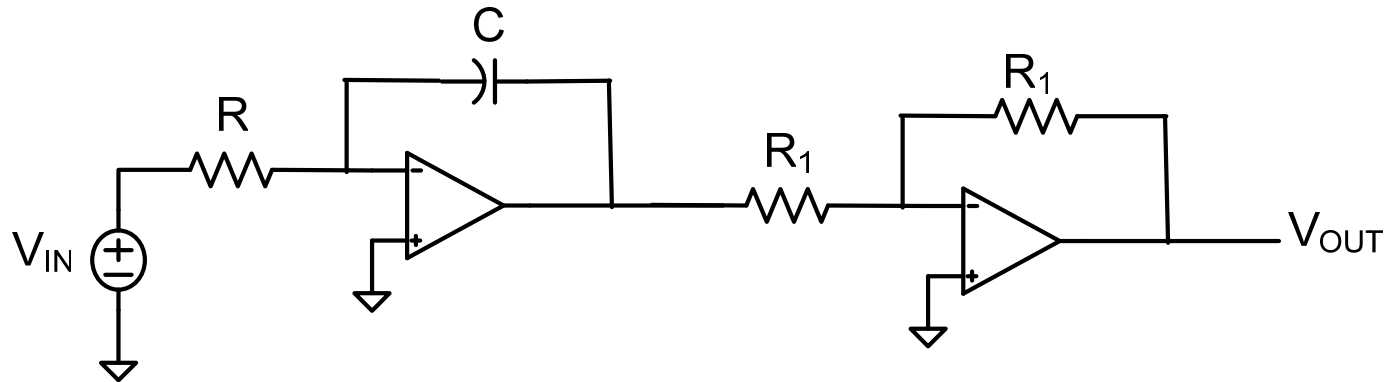

$$V_{\text{OUT}} = \frac{1}{RC} \int_0^t V_{\text{IN}}(\tau) d\tau + V_{\text{IN}}(0)$$

Obtained from inverting integrator by preceding or following with inverter


Requires more components

Also widely used


Same issues affect noninverting integrator

## Review from Last Time
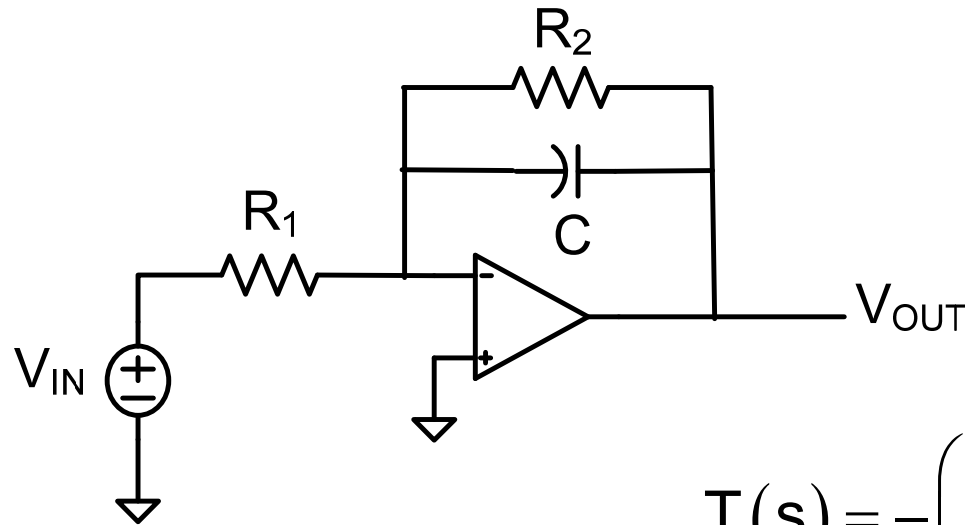
# First-order lowpass filter with a dc gain of $R_2/R_1$


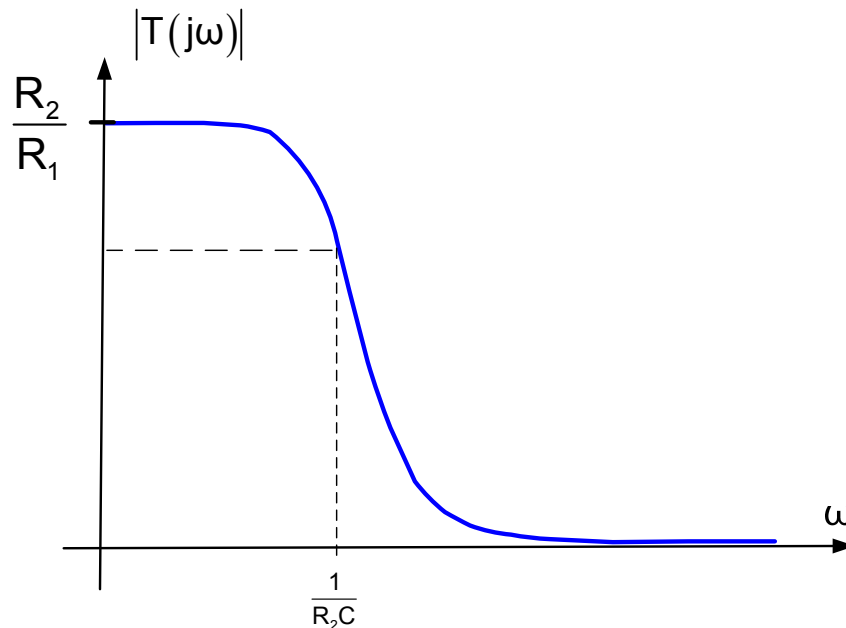
$$T(s) = -\left(\frac{R_2}{R_1}\right) \frac{1}{1+sCR_2}$$




$R_2$  controls the pole  
(and also the dc gain)



$R_1$  controls the dc gain  
(and not the pole)

Review from Last Time

# First-Order Highpass Filter


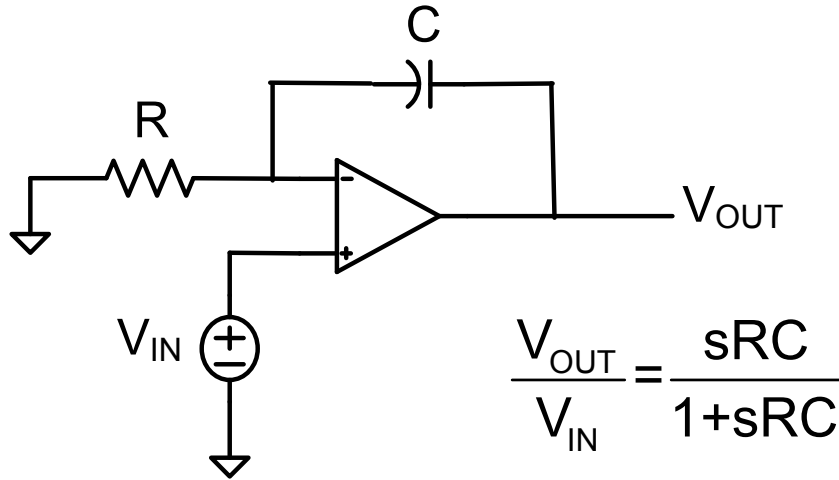


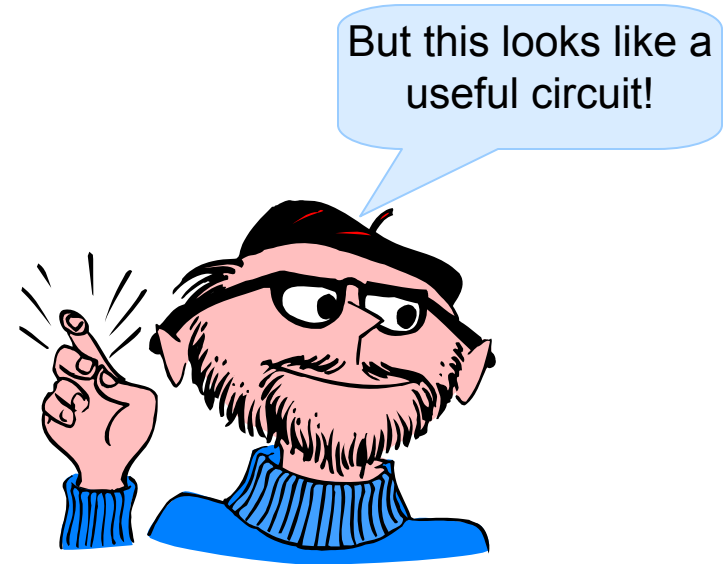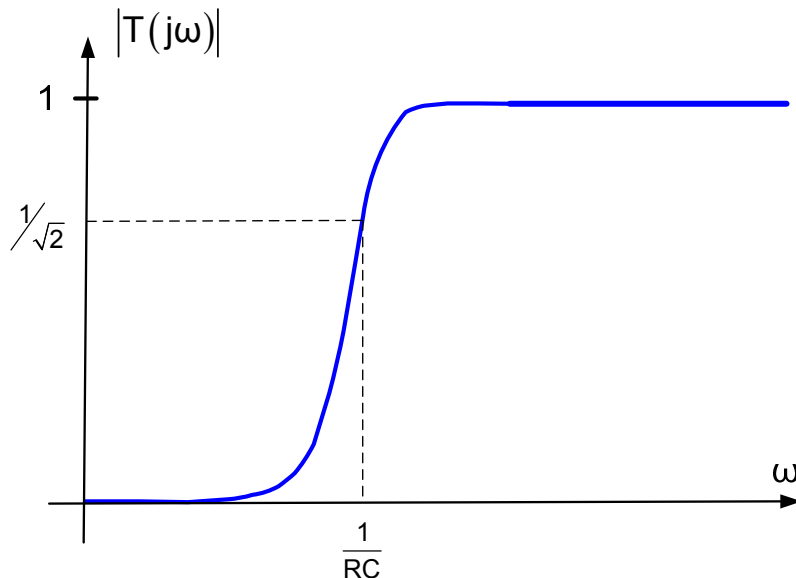This is a first-order high-pass amplifier (or filter)



3dB band edge at  $\omega=1/(RC)$

# Inverting Differentiator

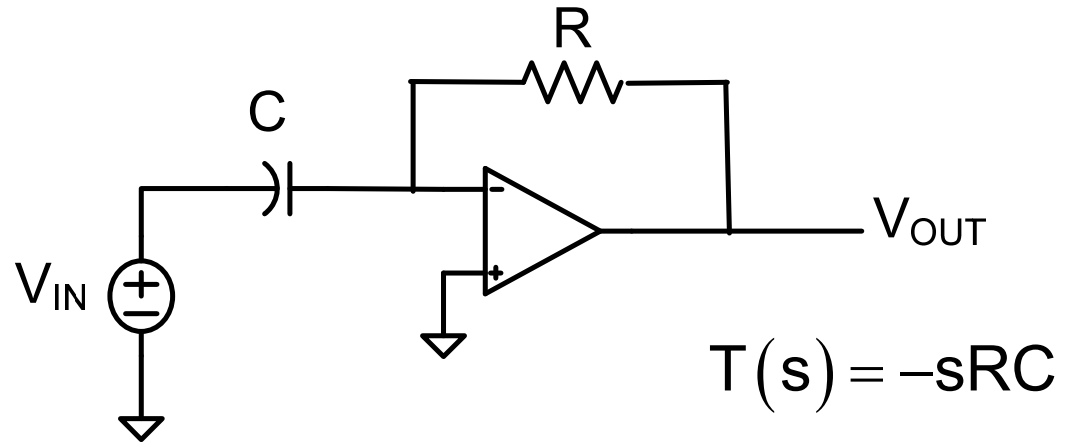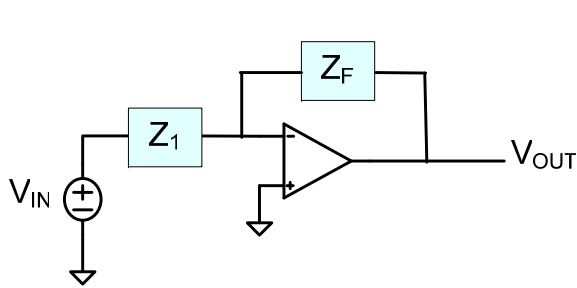

Differentiator gain ideally goes to  $\infty$  at high frequencies

Differentiator not widely used



Differentiator relentlessly amplifies noise

Stability problems with implementation (not discussed here)

Placing a resistor in series with  $C$  will result in a lossy differentiator that has some applications




# First-order High-pass Filter

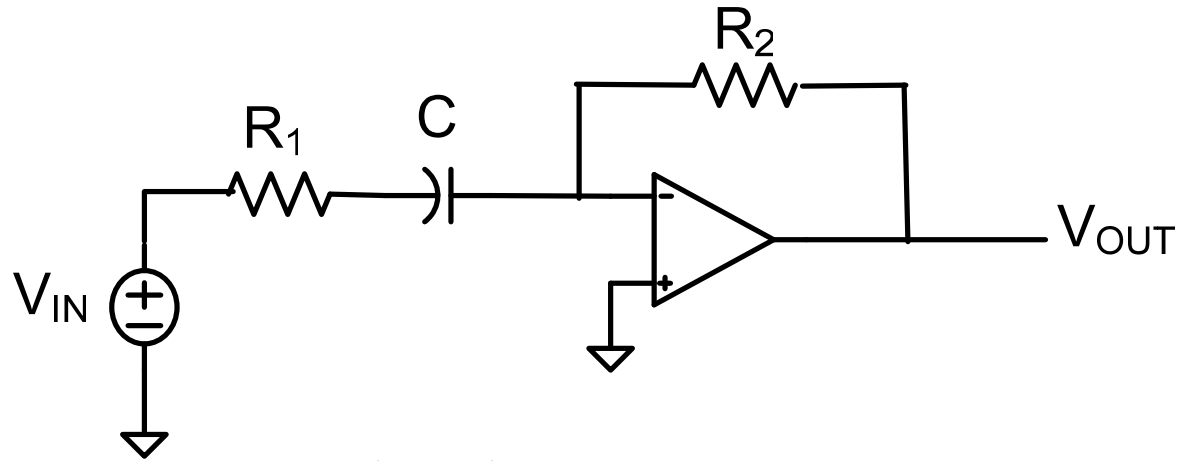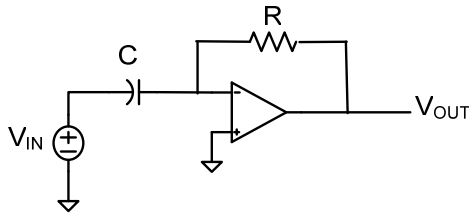


$$T(s) = -\frac{R_2}{R_1 + \frac{1}{sC}} = -\frac{sR_2C}{1 + R_1Cs}$$

$$|T(j\omega)| = \frac{\omega R_2 C}{\sqrt{1 + (\omega R_1 C)^2}}$$

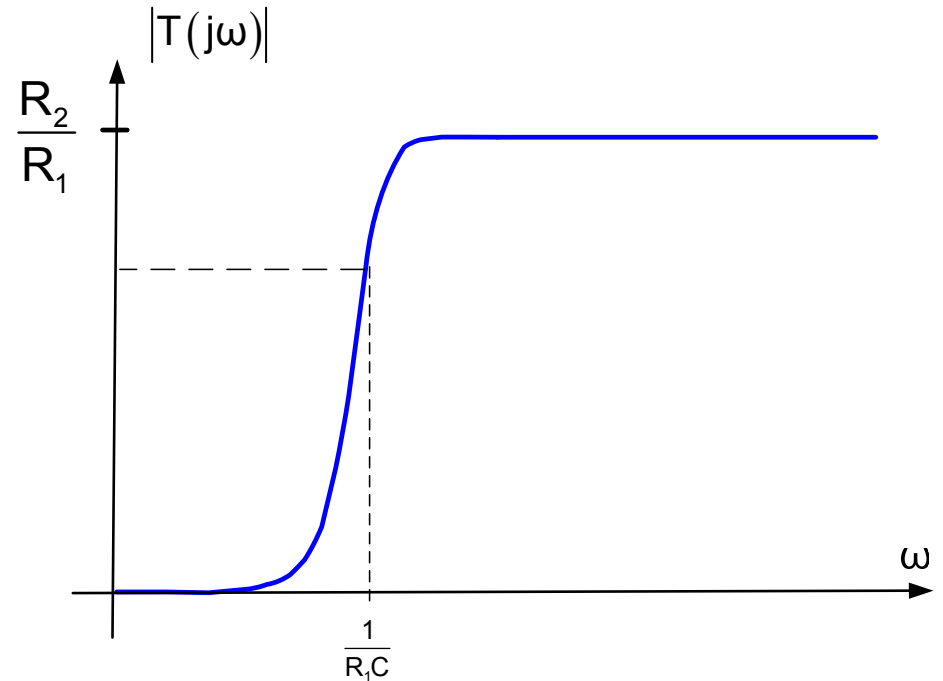

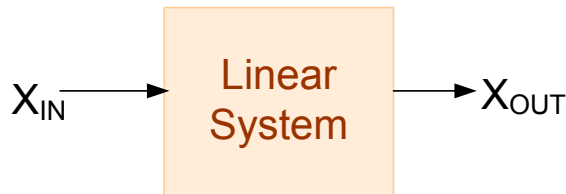
# Applications of integrators to solving differential equations




Consider the standard integral form
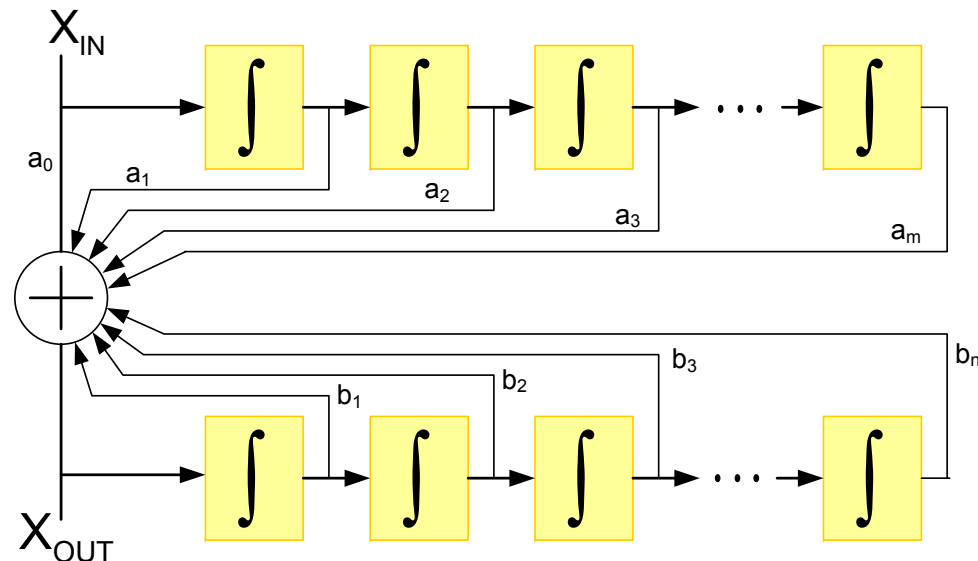
$$X_{OUT} = b_1 \int X_{OUT} + b_2 \iint X_{OUT} + b_3 \iiint X_{OUT} + \dots + a_0 X_{IN} + \int X_{IN} + \iint X_{IN} + \dots$$



This circuit is comprised of summers and integrators  
Can solve an arbitrary linear differential equation  
This concept was used in Analog Computers in the past
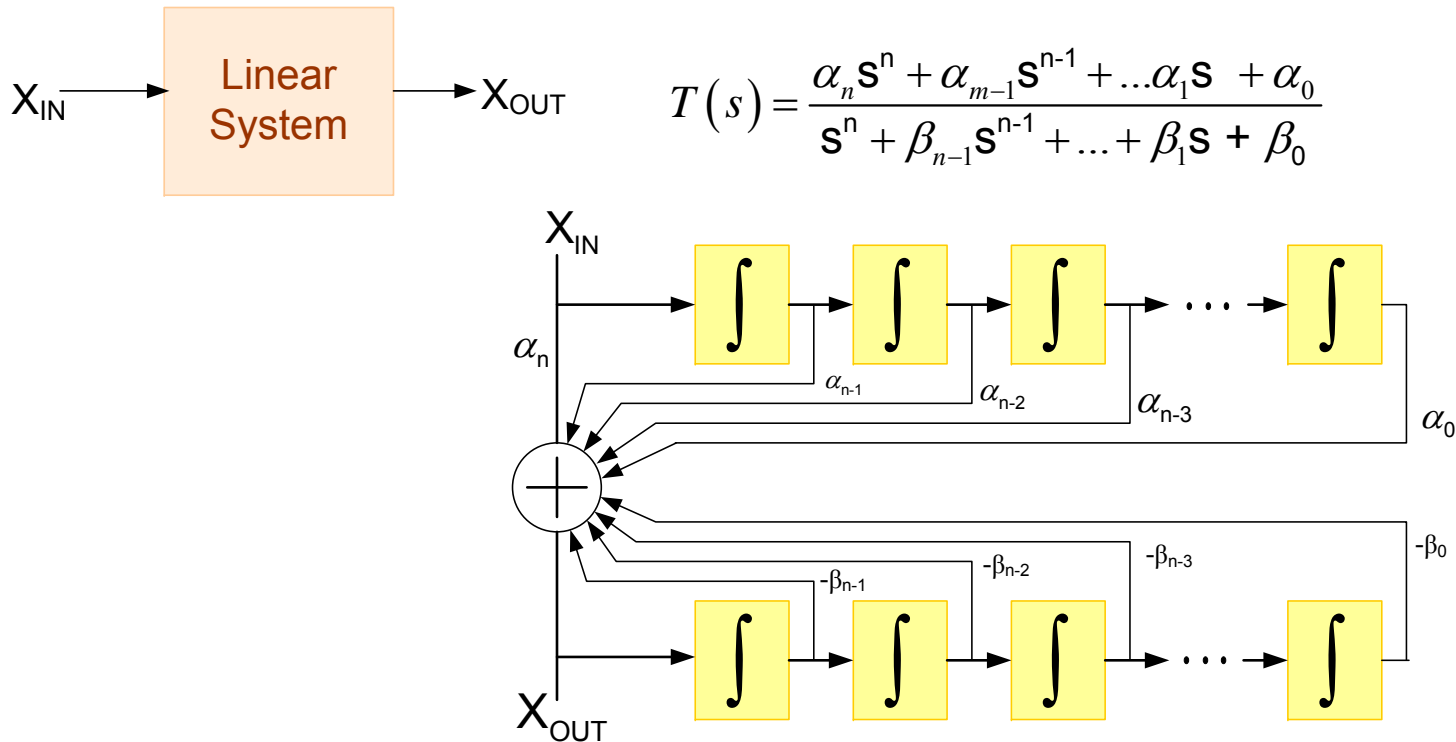
# Applications of integrators to filter design




Can design (synthesize) any  $T(s)$  with just integrators and summers !

Integrators are not used "open loop" so loss is not added

Although this approach to filter design works, often more practical methods are used
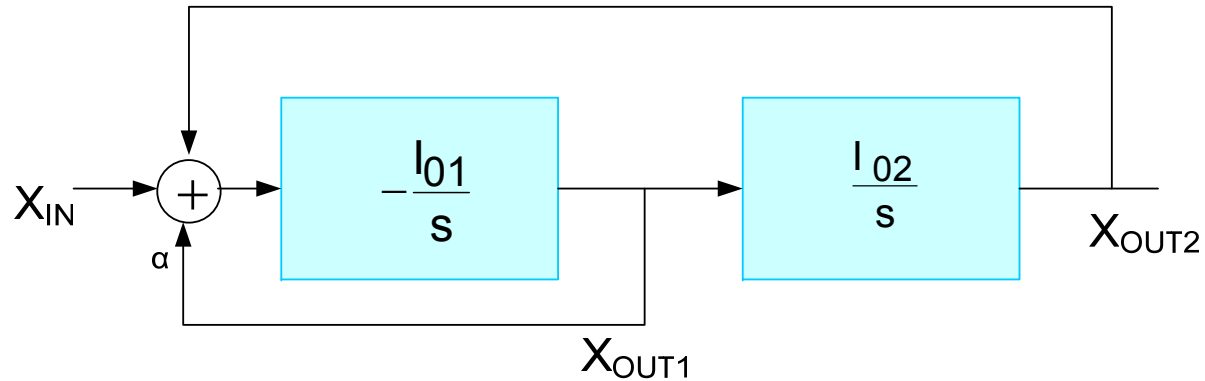
# Applications of integrators to filter design



This is a two-integrator-loop filter

$$X_{OUT1} = \left( -\frac{l_{01}}{s} \right) (X_{IN} + X_{OUT2} + \alpha X_{OUT1})$$

$$X_{OUT2} = \left( \frac{l_{02}}{s} \right) X_{OUT1}$$

$$\frac{X_{OUT1}}{X_{IN}} = T_1(s) = \frac{-l_{01}s}{s^2 + \alpha l_{01}s + l_{01}l_{02}}$$

$$\frac{X_{OUT2}}{X_{IN}} = T_2(s) = \frac{-l_{01}l_{02}}{s^2 + \alpha l_{01}s + l_{01}l_{02}}$$


These are 2-nd order filters

If  $l_{01} = l_{02} = l_0$ , these transfer functions reduce to

$$T_1(s) = \frac{-l_0 s}{s^2 + \alpha l_0 s + l_0^2}$$

$$T_2(s) = \frac{-l_0^2}{s^2 + \alpha l_0 s + l_0^2}$$
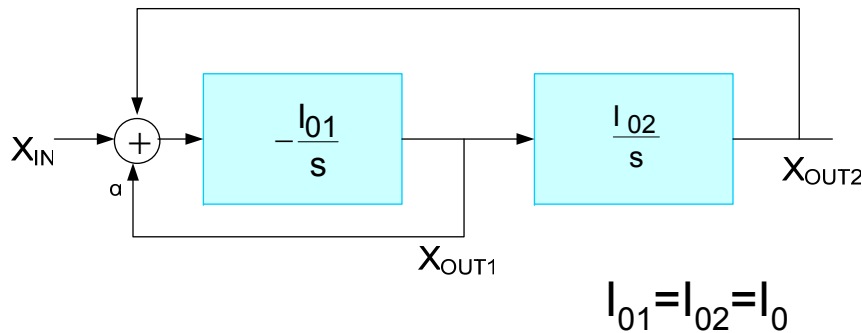
# Applications of integrators to filter design




$$T_1(s) = \frac{-l_0 s}{s^2 + \alpha l_0 s + l_0^2}$$

$$T_2(s) = \frac{-l_0^2}{s^2 + \alpha l_0 s + l_0^2}$$

Consider  $T_1(j\omega)$

$$T_1(j\omega) = \frac{-j\omega l_0}{(l_0^2 - \omega^2) + j\omega \alpha l_0}$$

$$|T_1(j\omega)| = \frac{\omega l_0}{\sqrt{(l_0^2 - \omega^2)^2 + (\omega \alpha l_0)^2}}$$

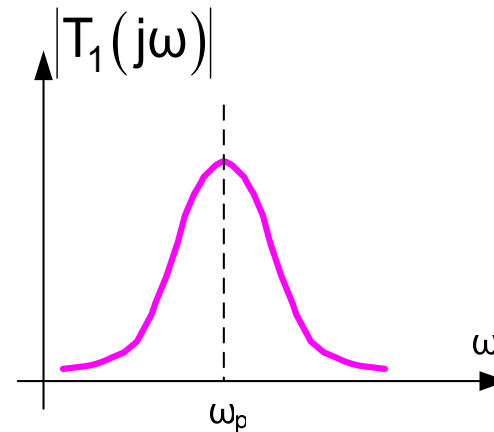

This is the standard 2<sup>nd</sup> order bandpass transfer function

Now lets determine the BW and  $\omega_p$

# Applications of integrators to filter design

Determine the BW and  $\omega_p$

$$T_1(s) = \frac{-I_0 s}{s^2 + \alpha I_0 s + I_0^2}$$

$$|T_1(j\omega)| = \frac{\omega I_0}{\sqrt{(I_0^2 - \omega^2)^2 + (\omega \alpha I_0)^2}}$$


To determine  $\omega_p$ , must set

$$\frac{d|T_1(j\omega)|}{d\omega} = 0$$

This will occur also when  $\frac{d|T_1(j\omega)|^2}{d\omega^2} = 0$  and the latter is easier to work with

$$|T_1(j\omega)|^2 = \frac{\omega^2 I_0^2}{(I_0^2 - \omega^2)^2 + (\omega \alpha I_0)^2}$$

$$\frac{d|T_1(j\omega)|^2}{d\omega^2} = \frac{\left( (I_0^2 - \omega^2)^2 + (\omega \alpha I_0)^2 \right) I_0^2 - \omega^2 I_0^2 \left( -2(I_0^2 - \omega^2) + (\alpha I_0)^2 \right)}{\left[ (I_0^2 - \omega^2)^2 + (\omega \alpha I_0)^2 \right]^2} = 0$$

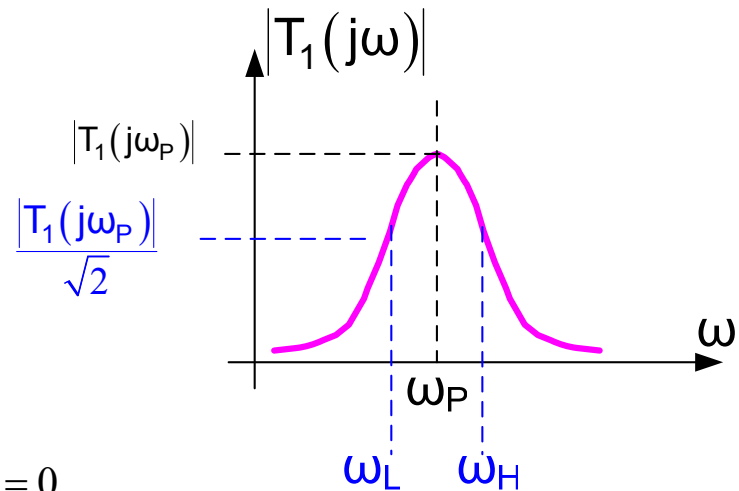

# Applications of integrators to filter design

## The 2<sup>nd</sup> order Bandpass Filter

Determine the BW and  $\omega_P$

$$T_1(s) = \frac{-I_0 s}{s^2 + \alpha I_0 s + I_0^2} \quad |T_1(j\omega)| = \frac{\omega I_0}{\sqrt{(I_0^2 - \omega^2)^2 + (\omega \alpha I_0)^2}}$$

$$\frac{d|T_1(j\omega)|^2}{d\omega^2} = \frac{\left( (I_0^2 - \omega^2)^2 + (\omega \alpha I_0)^2 \right) I_0^2 - \omega^2 I_0^2 \left( -2(I_0^2 - \omega^2) + (\alpha I_0)^2 \right)}{\left[ (I_0^2 - \omega^2)^2 + (\omega \alpha I_0)^2 \right]^2} = 0$$

It suffices to set the numerator to 0

$$\left( (I_0^2 - \omega^2)^2 + (\omega \alpha I_0)^2 \right) I_0^2 = \omega^2 I_0^2 \left( -2(I_0^2 - \omega^2) + (\alpha I_0)^2 \right)$$


Solving, we obtain

$$\omega_P = I_0$$

Substituting back into the magnitude expression, we obtain

$$|T_1(j\omega_P)| = \frac{I_0 I_0}{\sqrt{(I_0^2 - I_0^2) + (I_0 \alpha)^2}} = \frac{1}{\alpha}$$

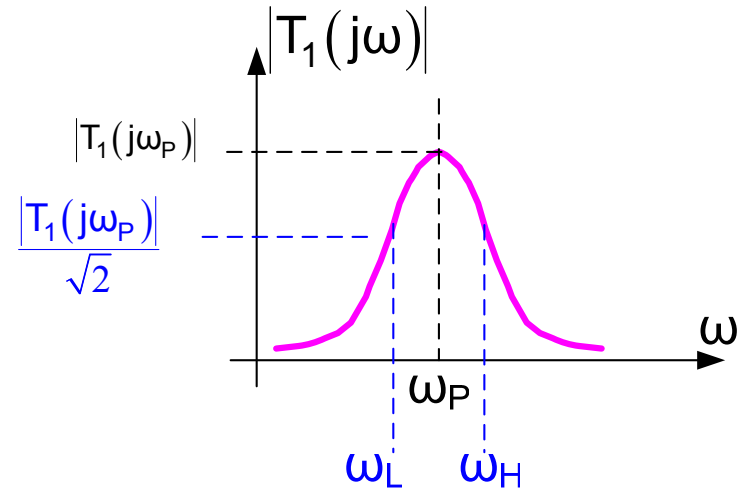Although the analysis is somewhat tedious, the results are clean



# Applications of integrators to filter design

## The 2<sup>nd</sup> order Bandpass Filter

Determine the BW and  $\omega_p$

$$T_1(s) = \frac{-I_0 s}{s^2 + \alpha I_0 s + I_0^2} \quad |T_1(j\omega)| = \frac{\omega I_0}{\sqrt{(I_0^2 - \omega^2)^2 + (\omega \alpha I_0)^2}}$$

To obtain  $\omega_L$  and  $\omega_H$ , must solve  $|T_1(j\omega)| = \frac{1}{\sqrt{2}\alpha}$


This becomes

$$\frac{1}{2\alpha^2} = \frac{\left( (I_0^2 - \omega^2)^2 + (\omega \alpha I_0)^2 \right) I_0^2 - \omega^2 I_0^2 \left( -2(I_0^2 - \omega^2) + (\alpha I_0)^2 \right)}{\left[ (I_0^2 - \omega^2)^2 + (\omega \alpha I_0)^2 \right]^2}$$

The expressions for  $\omega_L$  and  $\omega_H$  can be easily obtained but are somewhat messy, but from these expressions, we obtain the simple expressions

$$BW = \omega_H - \omega_L = \alpha I_0$$

$$\sqrt{\omega_H \omega_L} = I_0$$

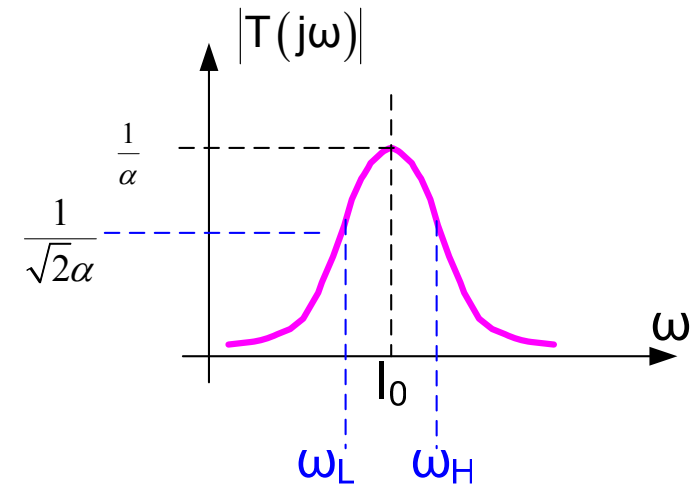



# Applications of integrators to filter design

## The 2<sup>nd</sup> order Bandpass Filter

Determine the BW and  $\omega_P$



$$T_1(s) = \frac{-I_0 s}{s^2 + \alpha I_0 s + I_0^2}$$

$$|T_1(j\omega)| = \frac{\omega I_0}{\sqrt{(I_0^2 - \omega^2)^2 + (\omega \alpha I_0)^2}}$$

$$\omega_P = I_0$$

$$BW = \alpha I_0$$

$$|T_1(j\omega_P)| = \frac{1}{\alpha}$$

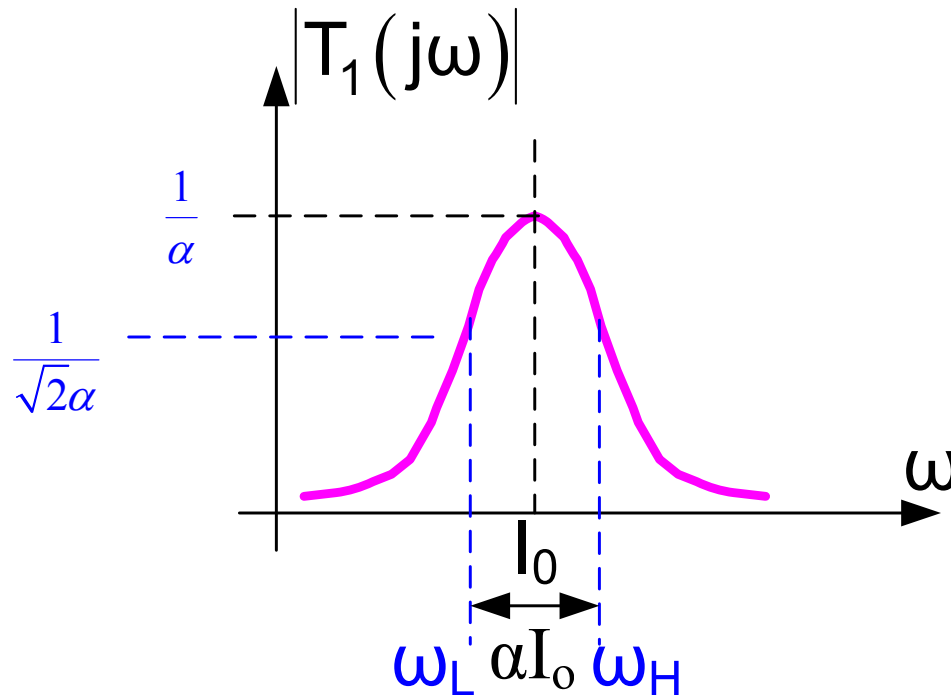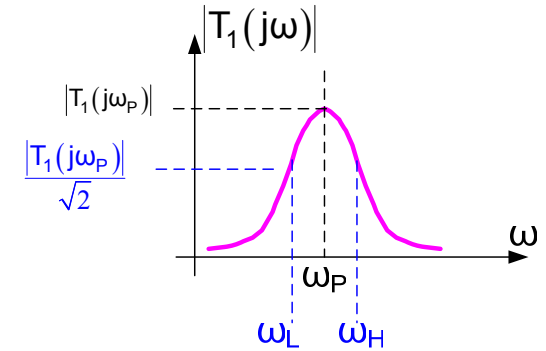


# Applications of integrators to filter design

## The 2<sup>nd</sup> order Bandpass Filter

Determine the BW and  $\omega_p$

$$T_1(s) = \frac{-I_0 s}{s^2 + \alpha I_0 s + I_0^2}$$
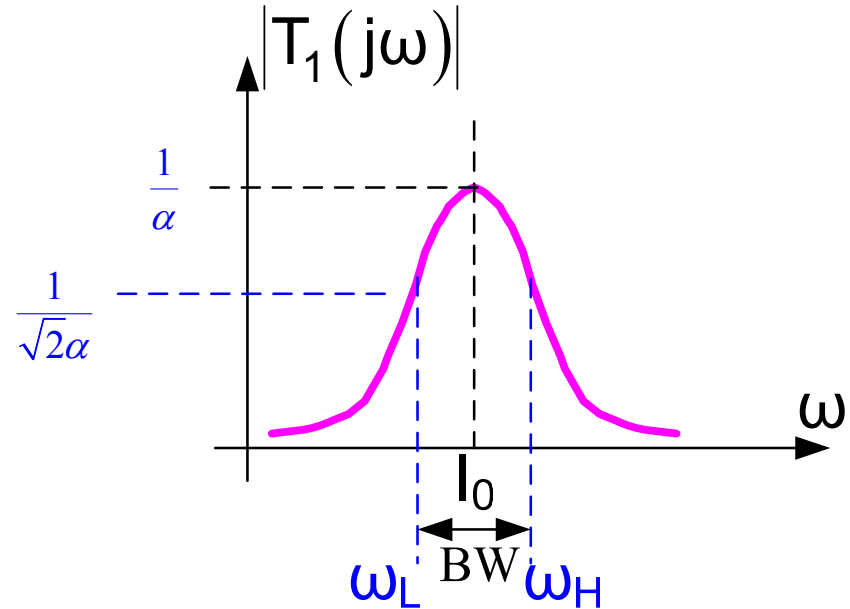
$$BW = \alpha I_0 \quad \sqrt{\omega_H \omega_L} = I_0$$



Often express the standard 2<sup>nd</sup> order bandpass transfer function as

$$T_1(s) = \frac{-I_0 s}{s^2 + BWs + I_0^2}$$

# Applications of integrators to filter design

## The 2<sup>nd</sup> order Bandpass Filter


These results can be generalized

$$T_{BP}(s) = \frac{Hs}{s^2 + as + b}$$

$$BW = a$$

$$\omega_p = \sqrt{b}$$

$$K = \frac{|H|}{a}$$

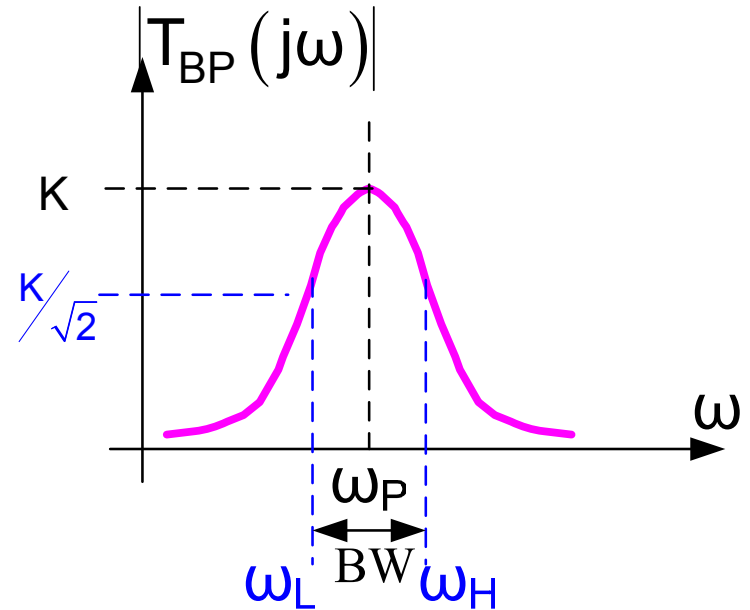



# Applications of integrators to filter design

## The 2<sup>nd</sup> order Bandpass Filter

Determine the BW and  $\omega_p$

$$T_1(s) = \frac{-I_0 s}{s^2 + \alpha I_0 s + I_0^2}$$
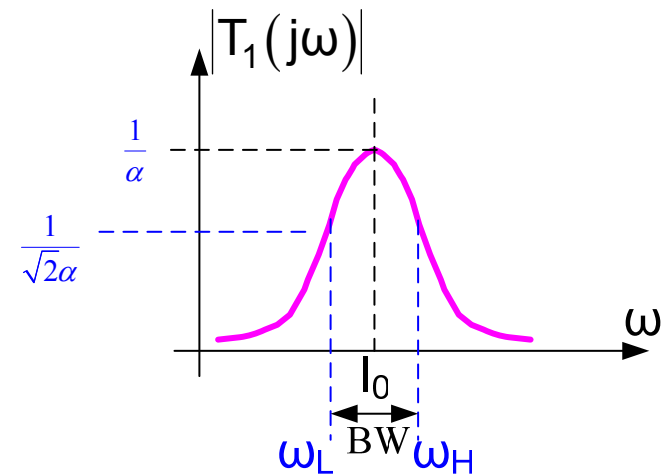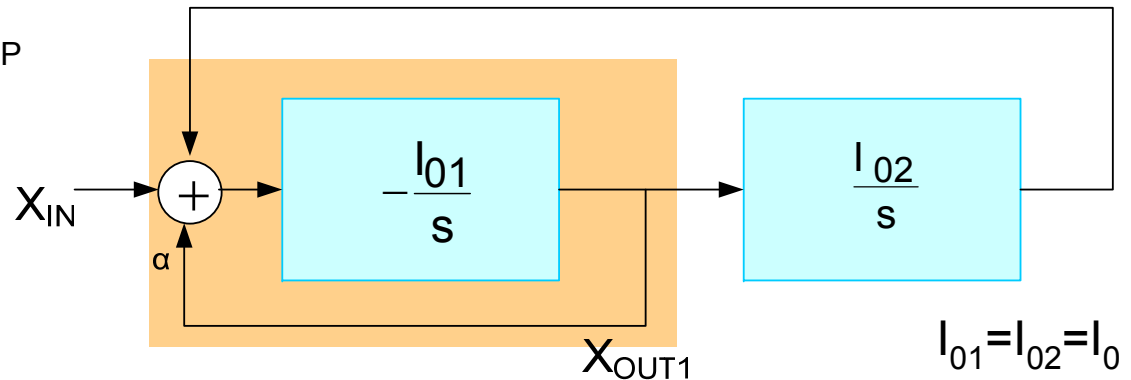
$$T_1(s) = \frac{-I_0 s}{s^2 + BW s + I_0^2}$$



Can readily be implemented with a summing inverting integrator and a noninverting integrator




# Applications of integrators to filter design

## The 2<sup>nd</sup> order Bandpass Filter

Determine the BW and  $\omega_p$

$$T_1(s) = \frac{-I_0 s}{s^2 + \alpha I_0 s + I_0^2}$$
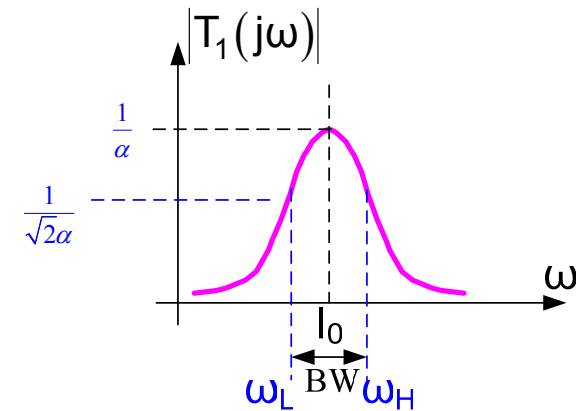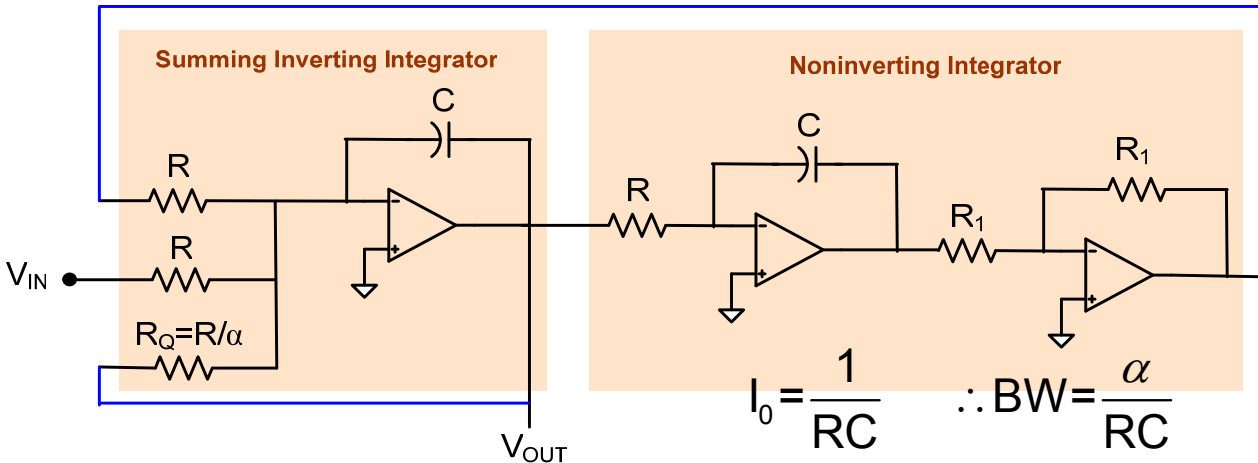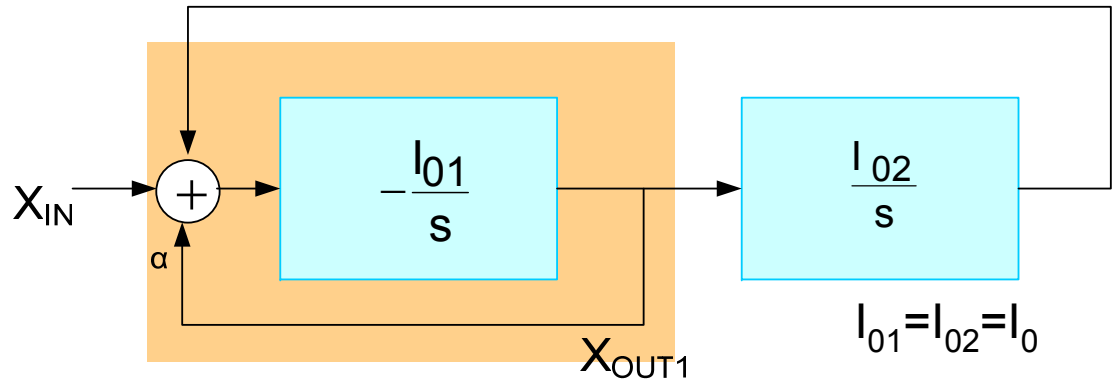
$$T_1(s) = \frac{-I_0 s}{s^2 + BW s + I_0^2}$$



- Widely used 2<sup>nd</sup> order Bandpass Filter
- BW can be adjusted with  $R_Q$
- Peak gain changes with  $R_Q$
- Note no loss is added to the integrators

$$\omega_p = I_0$$

$$BW = \alpha I_0$$




# Applications of integrators to filter design

## The 2<sup>nd</sup> order Bandpass Filter
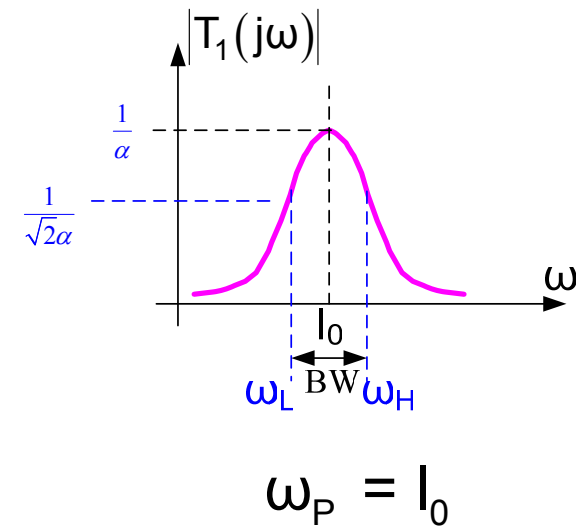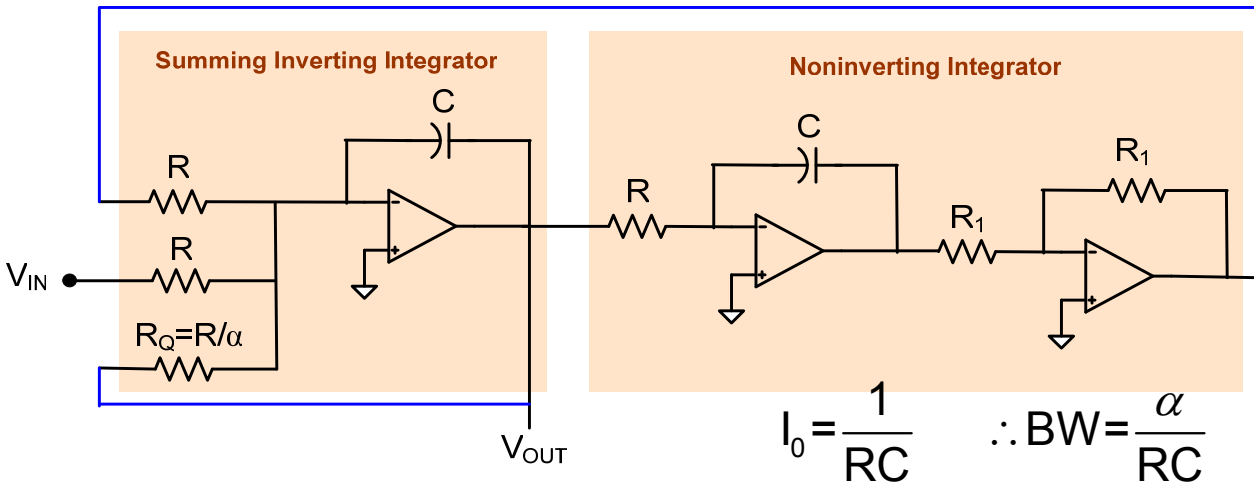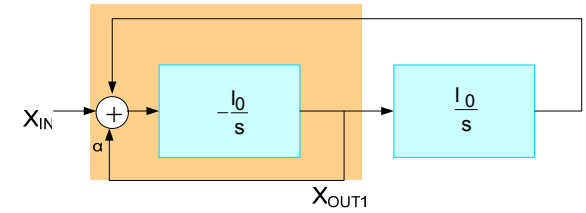
### Design Strategy

Assume BW and  $\omega_p$  are specified

$$T_{BP}(s) = \frac{-I_0 s}{s^2 + \alpha I_0 s + I_0^2}$$



1. Pick C (use some practical or convenient value)

2. Solve expression  $\omega_p = \frac{1}{RC}$  to obtain R


3. Solve expression  $BW = \frac{\alpha}{RC}$  to obtain  $\alpha$  and thus  $R_Q$





# Applications of integrators to filter design
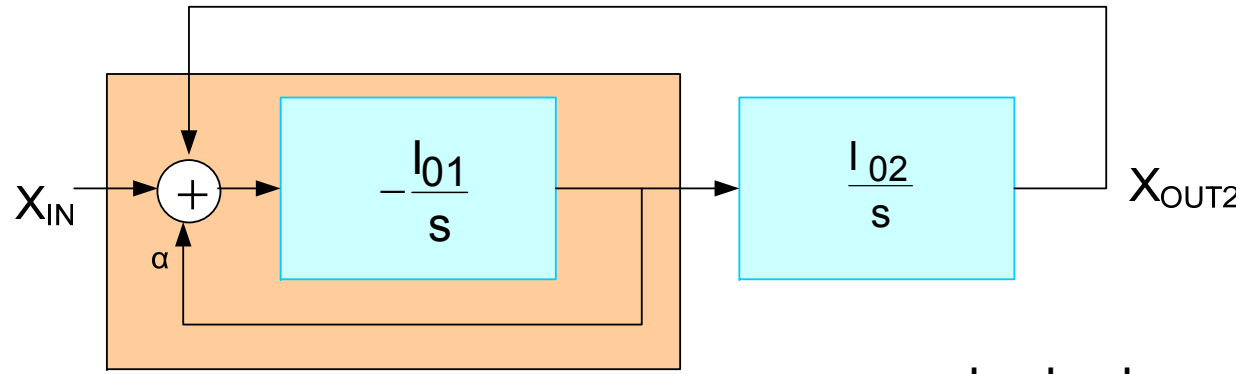
## The 2<sup>nd</sup> order Lowpass Filter

$$T_2(s) = \frac{-I_0^2}{s^2 + \alpha I_0 s + I_0^2}$$



$$I_{01} = I_{02} = I_0$$

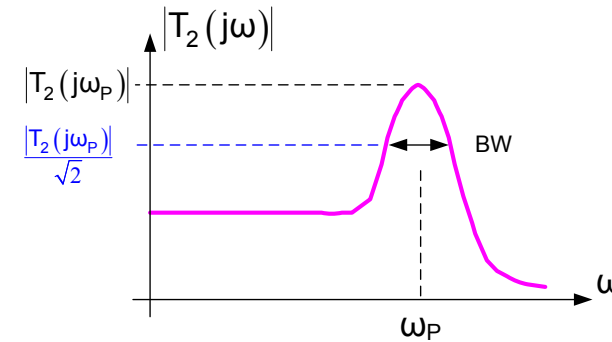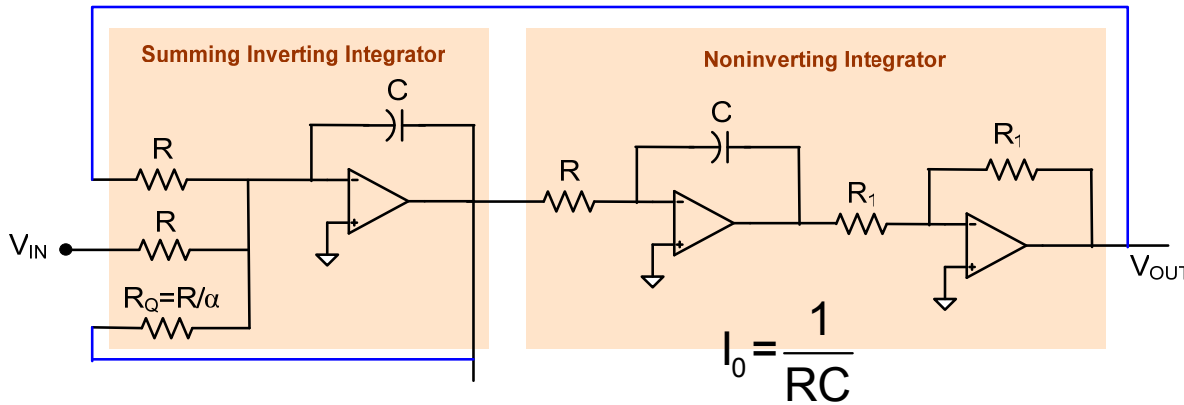

Exact expressions for BW and  $\omega_p$  are very complicated but  $\omega_p \approx I_0$




- Widely used 2<sup>nd</sup> order Lowpass Filter
- BW can be adjusted with  $R_Q$  but expression not so simple
- Peak gain changes with  $R_Q$
- Note no loss is added to the integrators

Design procedure to realize a given 2<sup>nd</sup> order lowpass function is straightforward


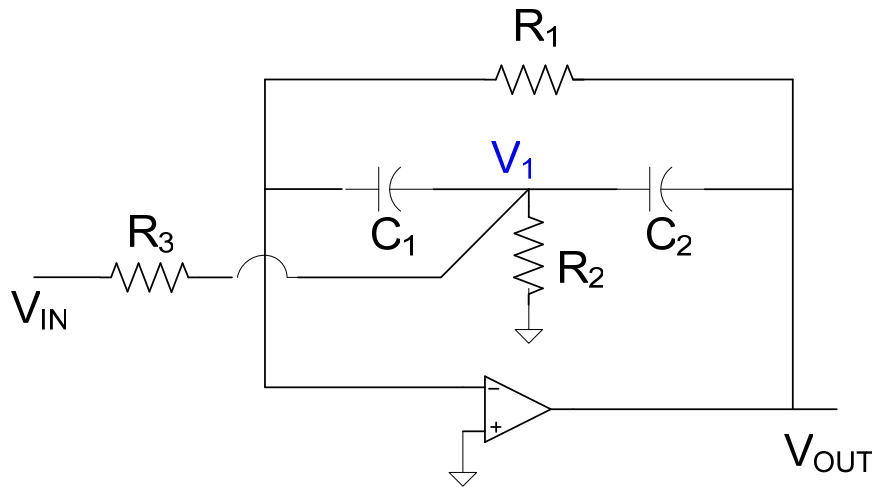
# Another 2<sup>nd</sup>-order Bandpass Filter



$$V_1(sC_1 + sC_2 + G_2 + G_3) = V_{OUT}sC_2 + V_{IN}G_3$$

$$V_1sC_1 + V_{OUT}G_1 = 0$$

$$T(s) = -\frac{\frac{s}{R_3C_2}}{s^2 + s\left(\frac{1}{R_1C_1} + \frac{1}{R_1C_2}\right) + \frac{1}{(R_2//R_3)R_1C_1C_2}}$$


If the capacitors are matched and equal to C

$$T(s) = -\frac{\frac{s}{R_3C}}{s^2 + s\left(\frac{2}{R_1C}\right) + \frac{1}{(R_2//R_3)R_1C^2}}$$

Since this is of the general form of a 2<sup>nd</sup> order BP transfer function, obtain

$$\omega_P = \frac{1}{\sqrt{R_1(R_2//R_3)C}}$$
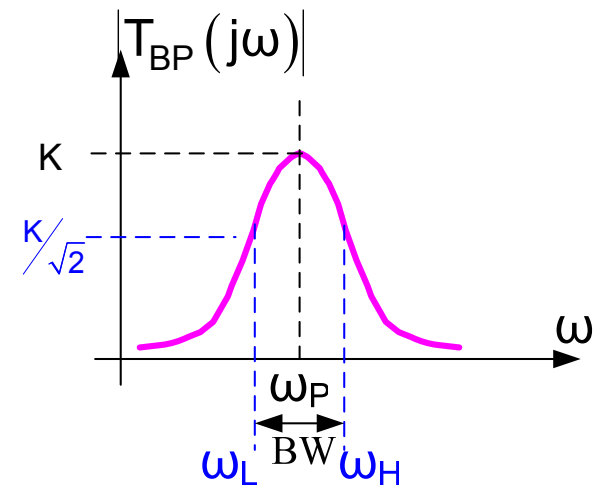
$$BW = \frac{2}{R_1C} \quad K = \frac{R_1}{2R_3}$$





# Another 2<sup>nd</sup>-order Bandpass Filter

## Design Strategy

Assume BW,  $\omega_p$ , and K are specified

$$T(s) = \frac{\frac{s}{R_3 C}}{s^2 + s \left( \frac{2}{R_1 C} \right) + \frac{1}{(R_2 // R_3) R_1 C^2}}$$

$$BW = \frac{2}{R_1 C} \quad \omega_p = \frac{1}{\sqrt{R_1 (R_2 // R_3) C}}$$



$$K = \frac{R_1}{2R_3}$$

1. Pick C to some practical or convenient value

2. Solve expression  $BW = \frac{2}{R_1 C}$  to obtain  $R_1$


3. Solve expression  $K = \frac{R_1}{2R_3}$  to obtain  $\alpha$  and thus  $R_3$

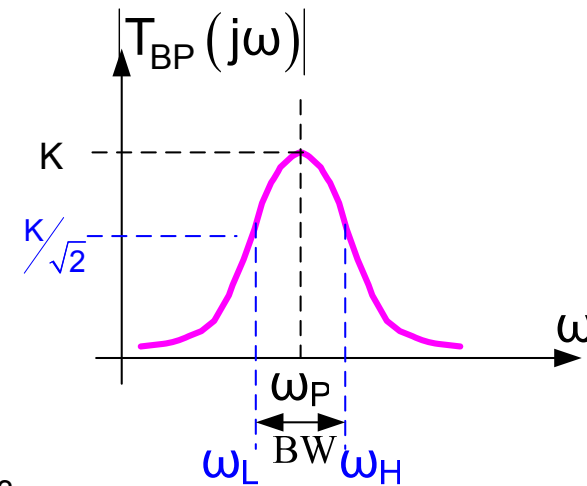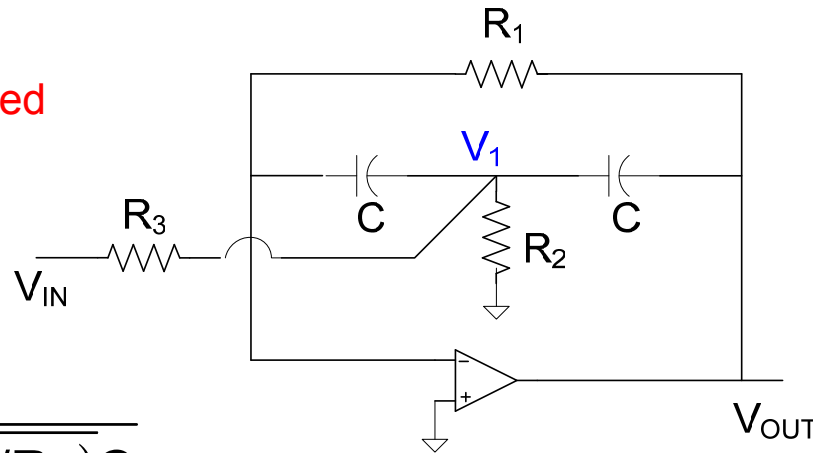4. Solve expression  $\omega_p = \frac{1}{\sqrt{R_1 (R_2 // R_3) C}}$  to obtain  $R_2$


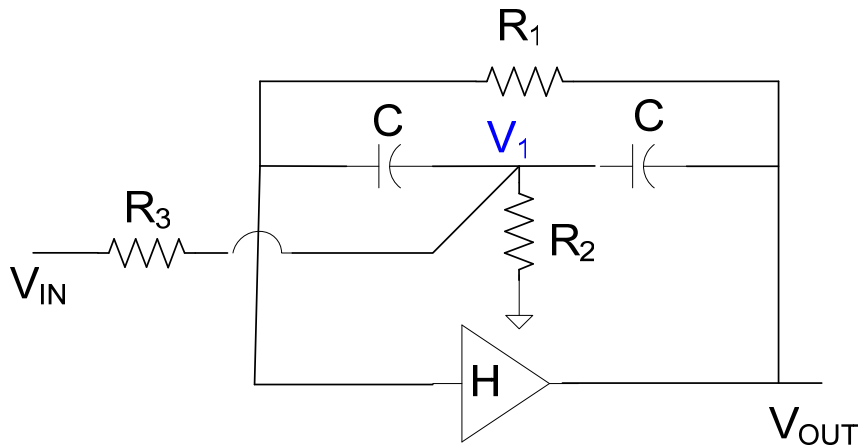
# Another 2<sup>nd</sup>-order Bandpass Filter

Termed the “STAR” biquad by inventors at Bell Labs



$$V_1(sC + sC + G_2 + G_3) = V_{OUT}sC + V_{IN}G_3 + V_{OUT} \frac{sC}{H}$$


$$\frac{V_{OUT}}{H}(sC + G_1) = V_1sC + V_{OUT}G_1$$

$$T(s) = \frac{\frac{s}{R_3C} \left( \frac{H}{H-1} \right)}{s^2 + s \left( \frac{2}{R_1C} - \frac{1}{(R_2//R_3)(H-1)} \right) + \frac{1}{(R_2//R_3)R_1C^2}}$$

$$\omega_p = \frac{1}{\sqrt{R_1(R_2//R_3)C}}$$

$$BW = \frac{2}{R_1C} - \frac{1}{(R_2//R_3)(H-1)}$$

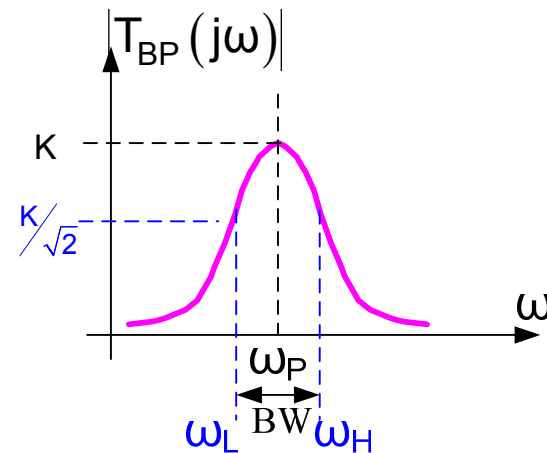
$$K = \frac{\frac{1}{R_3} \left( \frac{H}{H-1} \right)}{\left( \frac{2}{R_1} - \frac{1}{(R_2//R_3)(H-1)} \right)}$$



For the appropriate selection of component values, this is one of the best 2<sup>nd</sup> order bandpass filters that has been published




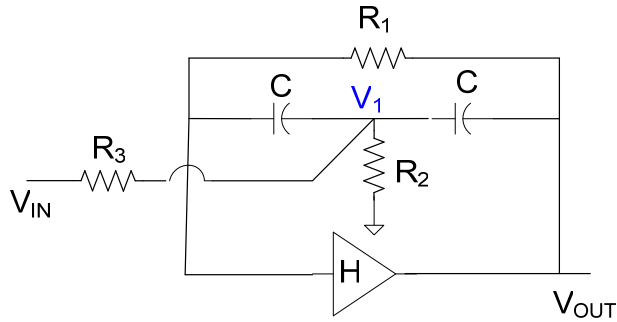
# STAR 2<sup>nd</sup>-order Bandpass Filter




$$T(s) = \frac{\frac{s}{R_3 C} \left( \frac{H}{H-1} \right)}{s^2 + s \left( \frac{2}{R_1 C} - \frac{1}{(R_2 // R_3)(H-1)} \right) + \frac{1}{(R_2 // R_3) R_1 C^2}}$$


Implementation:

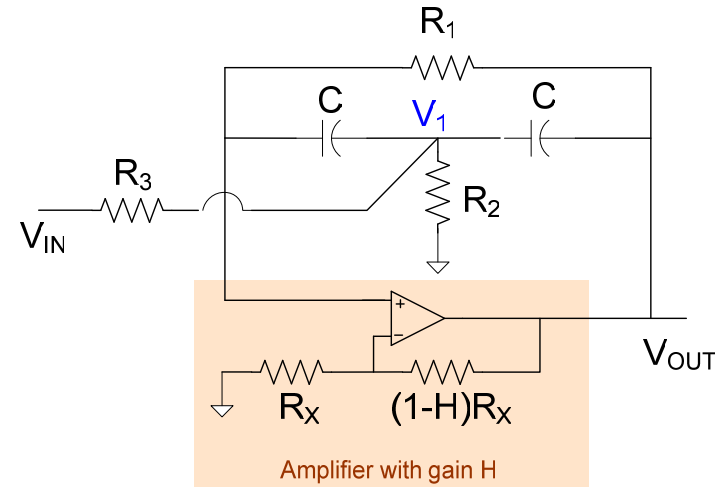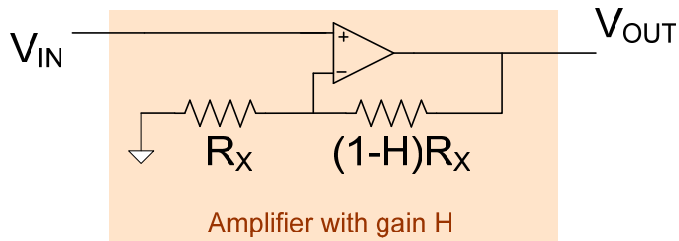

But the filter doesn't work !

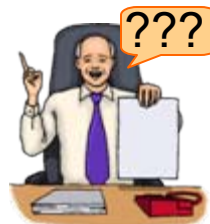

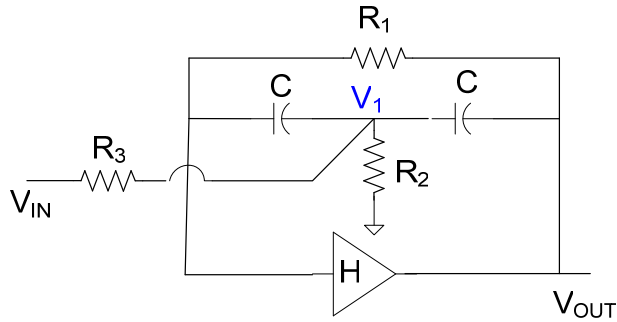
# STAR 2<sup>nd</sup>-order Bandpass Filter




$$T(s) = \frac{\frac{s}{R_3 C} \left( \frac{H}{H-1} \right)}{s^2 + s \left( \frac{2}{R_1 C} - \frac{1}{(R_2 // R_3)(H-1)} \right) + \frac{1}{(R_2 // R_3) R_1 C^2}}$$


Implementation:

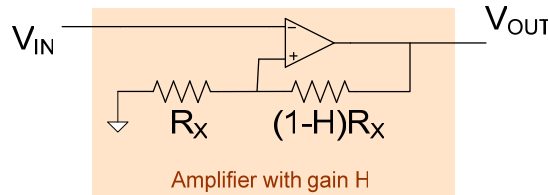

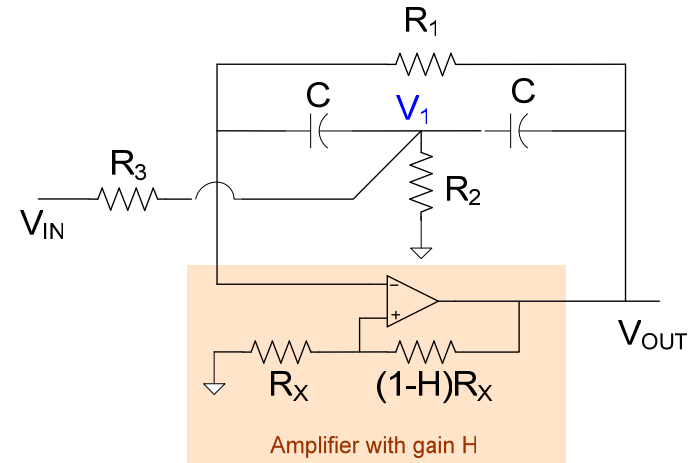If op amp ideal,  $\frac{V_{OUT}}{V_{IN}} = H$



Works fine !

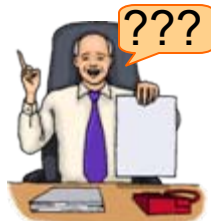

Will discuss why this happens later!

Reduces to previous bandpass filter at H gets large

Note that the "H" amplifier has feedback to positive terminal

**End of Lecture 14**