

EE 230



Lecture 15

Nonideal Op Amp Characteristics

Nonideal op amp characteristics

- Finite Gain
 - Finite BW
- > GB
- Compensation
 - Output Saturation
 - Slew Rate
 - R_{IN} & R_{OUT}
 - Offset Voltage
 - Bias Currents
-
- CMRR
 - PSRR
 - Offset Current
 - Full Power Bandwidth

Finite GB and BW

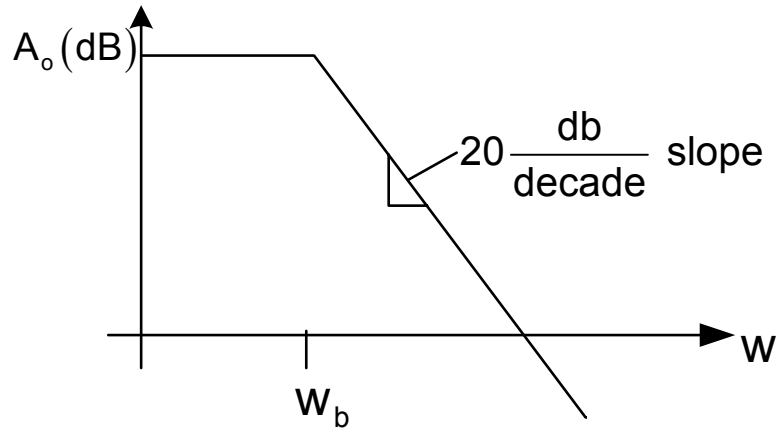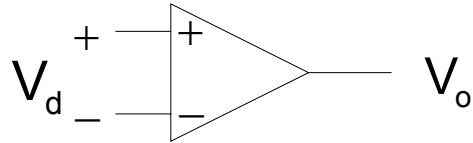

$$A(s) = \frac{V_o(s)}{V_d(s)} = \frac{A_o}{\frac{s}{\omega_b} + 1}$$

$\omega_b \sim$ BW of OA

$$|A(j\omega)| = \frac{A_o}{\sqrt{\left(\frac{\omega}{\omega_b}\right)^2 + 1}}$$

For $\omega \gg \omega_b$, $A(s) \approx \frac{A_o}{s} = \frac{A_o \omega_b}{s}$

$$|A(j\omega)| = \frac{A_o \omega_b}{\omega}$$

$$A_o \omega_b = \text{GB}$$



GB termed Gain-Bandwidth Product

$$A(s) = \frac{\text{GB}}{s} \iff A(s) = \frac{A_o}{\frac{s}{\omega_b} + 1}$$

Macromodel

- Equivalent circuit that mimics the behavior of an actual circuit
- Not necessarily (usually no) relationship between elements in macromodel and the circuit of interest

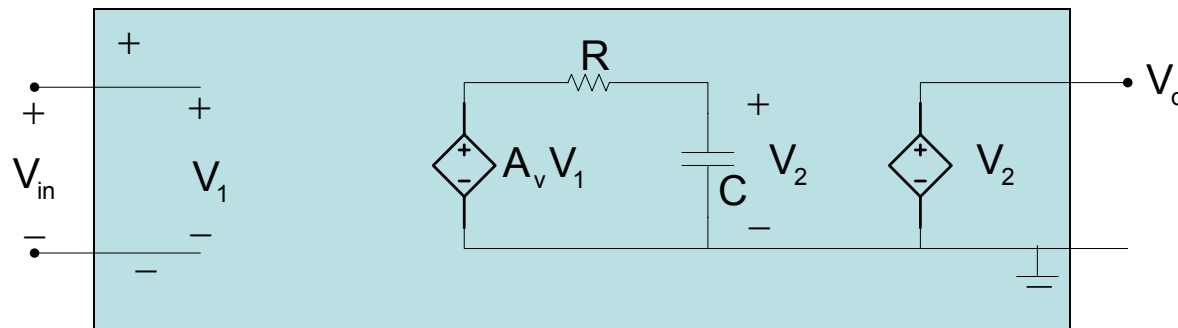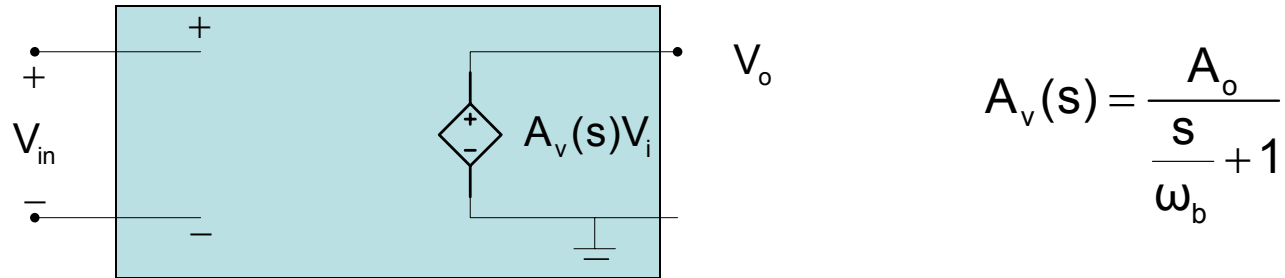Macromodel of op amp that includes effects of frequency dependent gain




$$V_o = A_o V_i \left(\frac{1}{R + \frac{1}{sC}} \right) = V_i \left[\frac{A_o}{1 + RCs} \right]$$

If $C=1F$

$$R = \frac{1}{\omega_b}$$

$$\frac{V_o}{V_i} = \frac{A_o}{1 + \frac{s}{\omega_b}}$$

Noninverting Finite Gain Amplifier

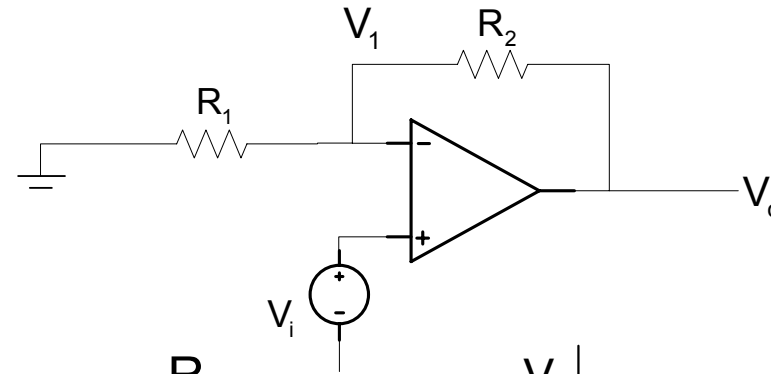

$$K_o = 1 + \frac{R_2}{R_1}$$

$$\left. \frac{V_o}{V_i} \right|_{A_o = \infty} = K_o$$

If not ideal:

$$\left. \begin{aligned} V_1 &= \frac{R_1}{R_1 + R_2} V_o \\ V_o &= A(s)(V_i - V_1) \end{aligned} \right\} \frac{V_o(s)}{V_i(s)} = \frac{K_o}{1 + \frac{K_o}{A(s)}}$$

$$A(s) = \frac{A_o}{\frac{s}{w_b} + 1}$$

$$A_{FB}(s) = \frac{K_o}{1 + \frac{K_o \left(\frac{s}{w_b} + 1 \right)}{A_o}} = \frac{K_o A_o}{A_o + K_o + \frac{s K_o}{w_b}}$$

but since $A_o \gg K_o$

$$A_{FB}(s) \approx \frac{A_o K_o}{A_o + s \frac{K_o}{w_b}} = \frac{A_o w_b K_o}{A_o w_b + s K_o} = \frac{K_o GB}{s K_o + GB}$$

$$BW = \frac{GB}{K_0}$$

$$\boxed{K_0 \bullet BW = GB}$$


Example: If an op amp has a GB of 1MHz and a dc gain of a closed loop amplifier of 10, what is the BW of the closed loop amplifier?

$$\text{Solution: } Bw = \frac{GB}{K_0} = \frac{1\text{MHz}}{10} = 100\text{kHz}$$

Example: Determine the maximum dc gain of a noninverting FB amplifier if designed with an OA with GB=1MHz, if the closed loop BW must be greater than 20 kHz.

$$\text{Solution: } K_0 BW = GB \Rightarrow K_0 = \frac{GB}{BW} = \frac{1\text{MHz}}{20\text{kHz}} = 50$$

Inverting Amplifier

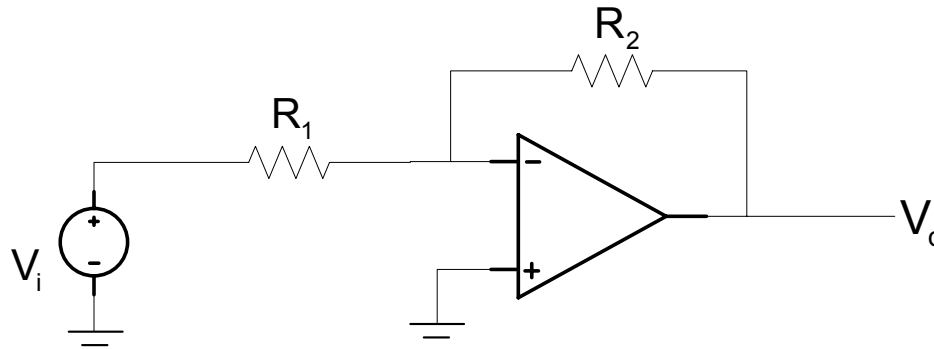

$$K_o = \frac{R_2}{R_1}$$

\therefore ideal dc gain is $-K_o$

Effects of GB of OA on closed loop amplifier

$$A_{fb}(s) = \frac{-K_o}{1 + \frac{1+K_o}{A(s)}}$$

$$A_{FB}(s) \approx \frac{-K_o}{1 + s \frac{1+K_o}{GB}}$$

$$A(s) \approx \frac{GB}{s}$$

$$BW_{CL} = \frac{GB}{1+K_o}$$

$$(1+K_o)BW = GB$$

How do bandwidths compare for inverting and noninverting amplifiers?

$$\text{Inverting: } BW = \frac{GB}{1+K_o}$$

$$\text{Noninverting: } BW = \frac{GB}{K_o}$$

$$\text{If } K_o = 1 \quad BW_{\text{INV}} = \frac{1}{2} BW_{\text{NONINV}}$$

$$K_o \text{ is large, } BW_{\text{INV}} \approx BW_{\text{NONINV}}$$

Strategy for Measuring GB

1. Build FB noninverting amplifier with gain K_0
2. Measure BW
3. $GB=(K_0)(BW)$


Review: Noninverting Amplifier

$$(BW)(K_0) = GB$$

Inverting Amplifier


$$(BW)(1+K_0) = GB$$

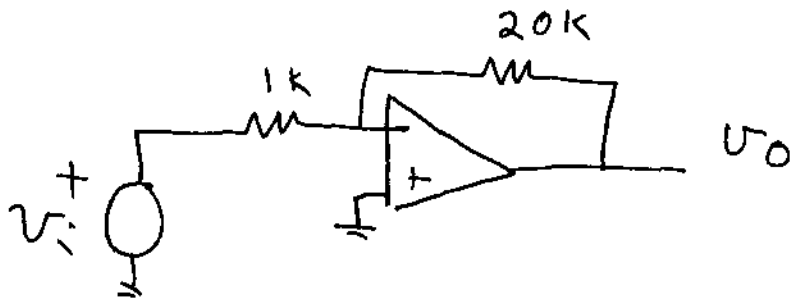Example: Determine the 3dB bandwidth of the amplifier shown if $GB = 500\text{kHz}$.




$$BW = \frac{500\text{kHz}}{1+20} = \frac{500\text{kHz}}{21}$$

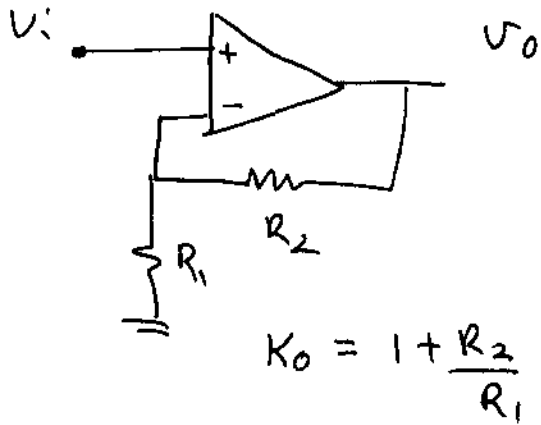Compensation provided the 1st-order roll-off characteristic



$$K_0 = 1 + \frac{R_2}{R_1}$$

Good circuit!

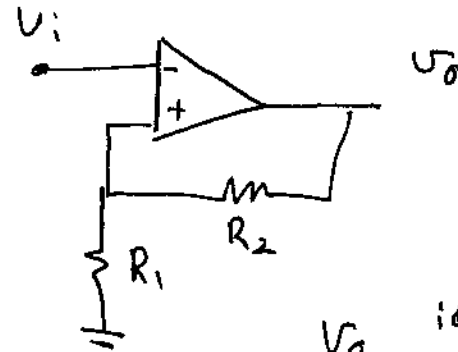


$$\frac{V_o}{V_i} \stackrel{\text{ideal}}{=} \stackrel{\text{op amp}}{=} 1 + \frac{R_2}{R_1}$$

Not a good amplifier

Recall: A system is stable iff
all poles lie in the LHP

Consider First Circuit
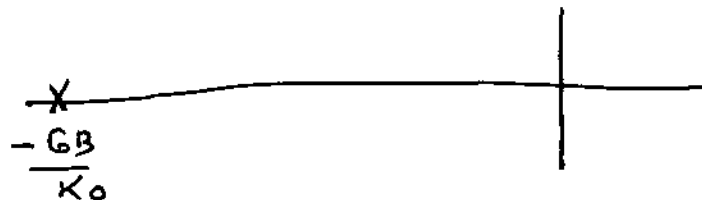
$$A_{FB}(s) = \frac{K_0}{1 + \frac{K_0}{A(s)}} = \frac{K_0}{1 + s \frac{K_0}{GB}} \Rightarrow \text{pole at } s = -\frac{GB}{K_0}$$




∴ This amplifier is stable

Consider second circuit

$$A_{FB}(s) = \frac{K_0}{1 + \frac{K_0}{-A(s)}} \quad \begin{matrix} A(s) = \frac{GB}{s} \\ \underline{\underline{\quad}} \end{matrix} \quad \frac{K_0}{1 + \frac{K_0}{-GB/s}}$$

$$= \frac{K_0}{1 - s \frac{K_0}{GB}}$$

pole at $s = +\frac{GB}{K_0}$

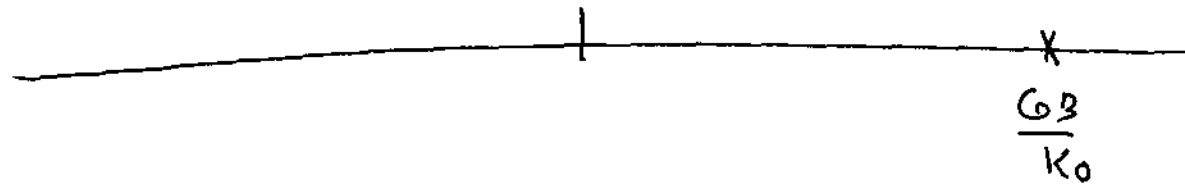


This "amplifier" is unstable

This circuit is not useful as an amplifier


Output Saturation

- Voltage Limit \rightarrow Maximum or minimum output voltages an op amp can provide
- Current Limit \rightarrow Maximum or minimum output currents an op amp can provide

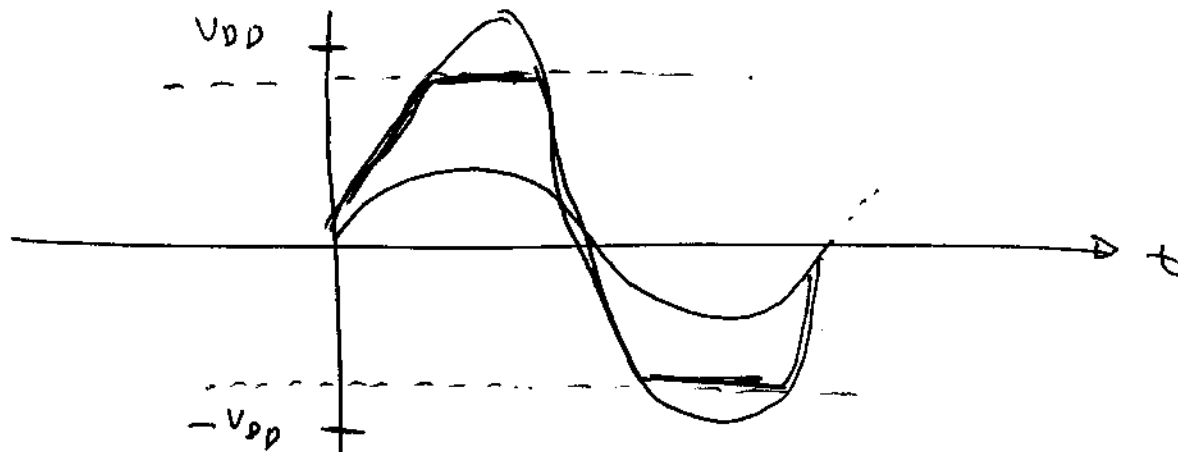
Often $V_{OMAX} \approx V_{DD} - 1.2V$
 $V_{OMIN} \approx V_{SS} + 1.2V$



Nonlinear distortion is introduced

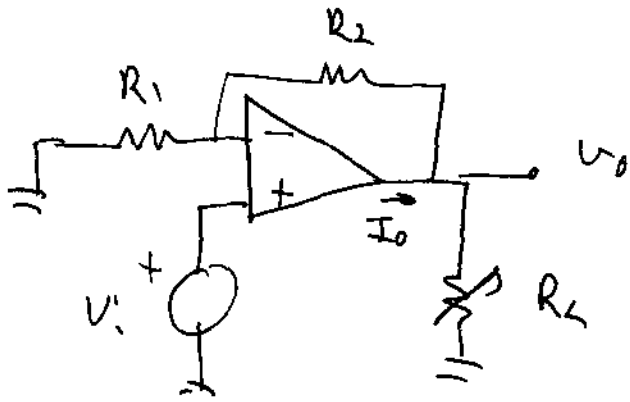
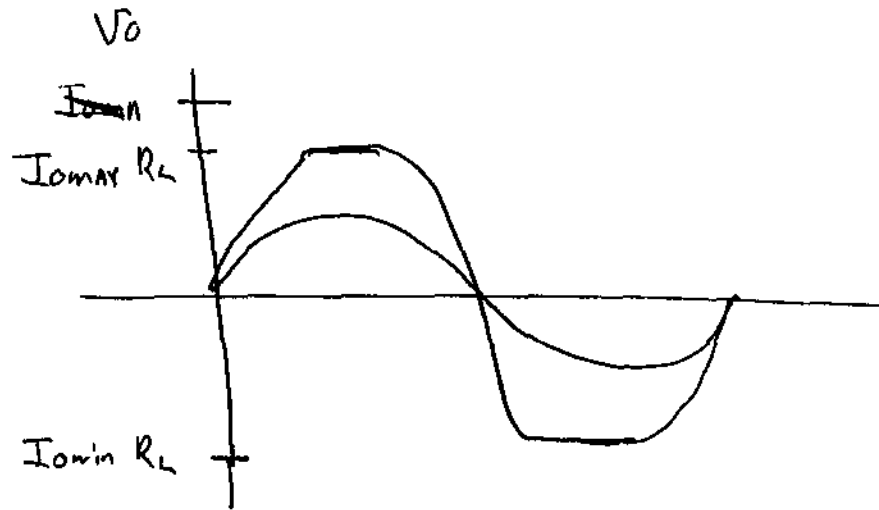
$$I_o \approx \frac{V_o - V_i}{R_2} + \frac{V_o}{R_L} \approx \frac{V_o}{R_L}$$




Output Current Saturation provides similar limits to what was seen with output voltage saturation

Usually tell difference between voltage & current saturation by looking at saturation voltage

Slew Rate

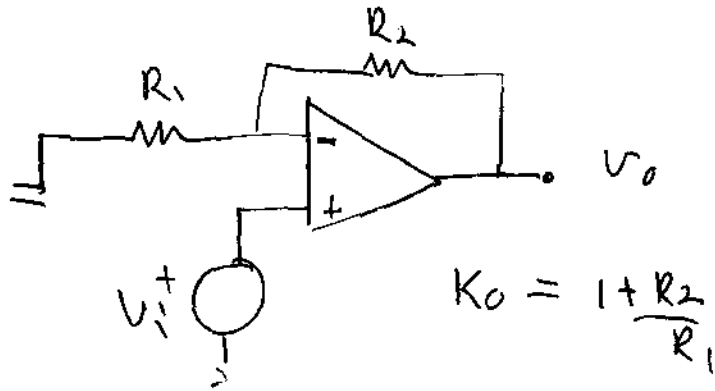Maximum Rate of Change at Output of Op Amp.



If $V_i(t)$ is a square wave of height V_m ,
 $V_o(t)$ will ^{ideally} be a square wave of height $K_o V_m$



Actual Output.



SR in $V/\mu\text{sec}$

$1V/\mu\text{sec}$ to $100V/\mu\text{sec}$

SR with sinusoidal signals

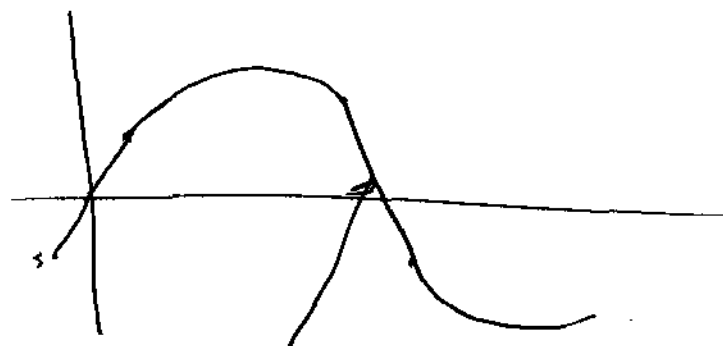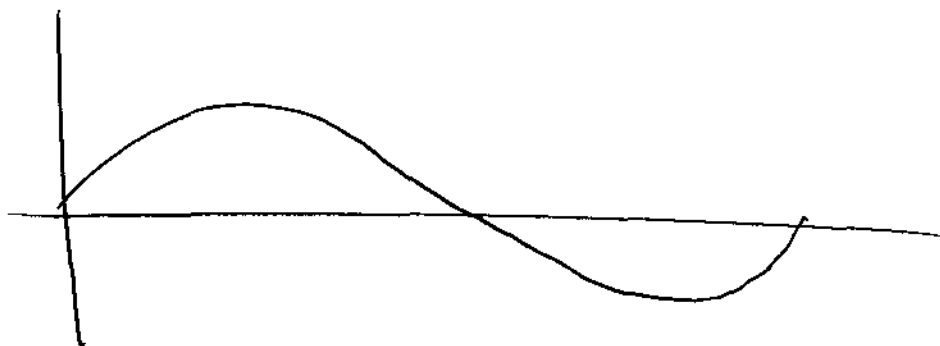


slew
rate
limits

$$V_o = V_m \sin(\omega t + \theta)$$

$$\frac{dV_o}{dt} = V_m \cos(\omega t + \theta) \omega < S R$$


To avoid slew distortion

$$V_m \omega < S R$$


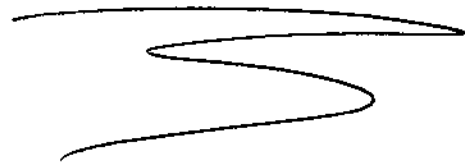


If $V_m \omega$ significantly larger than $S R$

Output will become a triangle wave

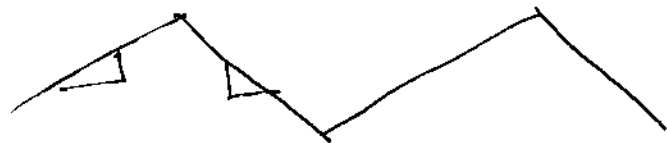

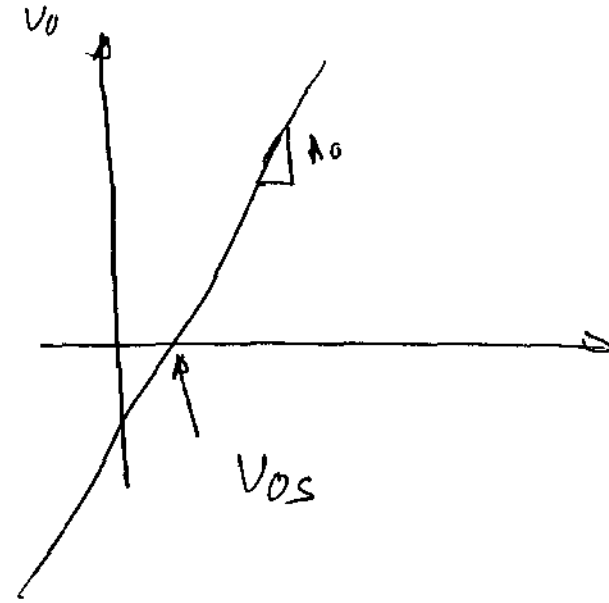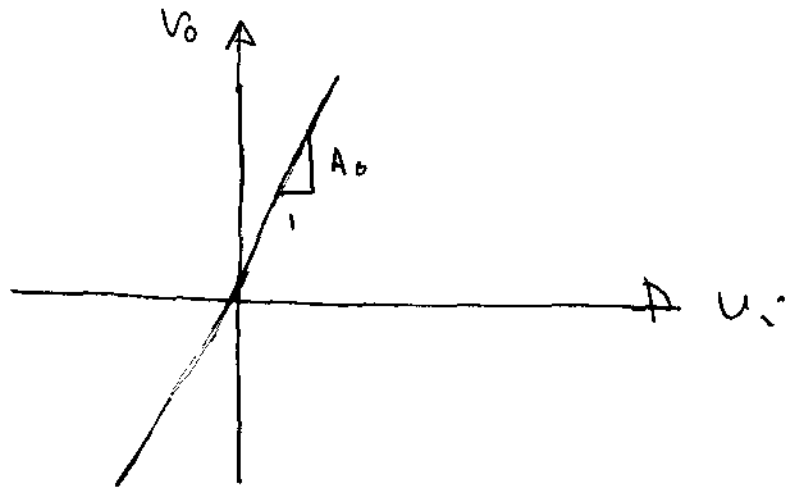
Offset voltage (Input Referred Offset Voltage)





V_{OS} can be positive or negative

V_{OS} is a random variable

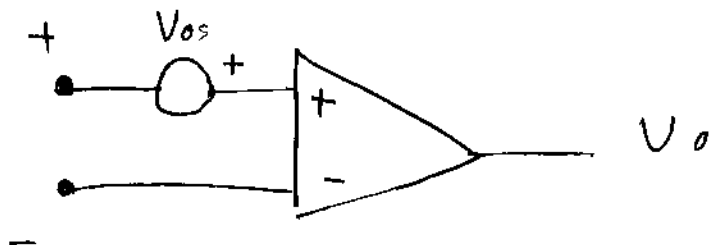V_{os} can be modeled with a dc voltage source in series with input terminal



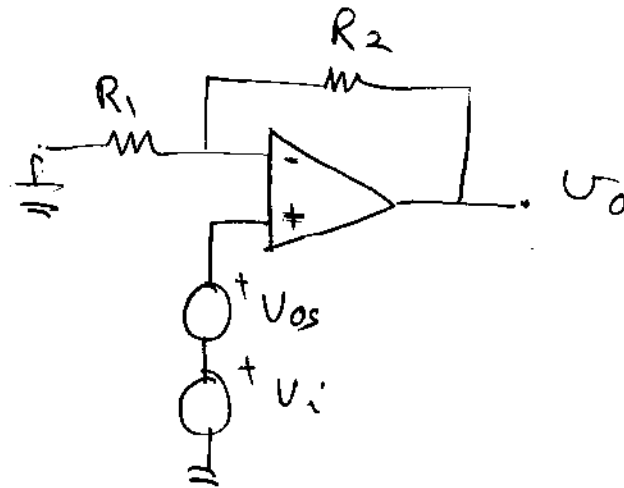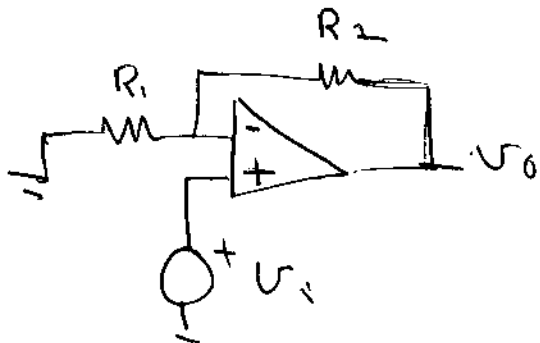Effects of V_{os} on basic noninverting amplifier



$$V_o = V_i \left(1 + \frac{R_2}{R_1} \right) + V_{os} \left(1 + \frac{R_2}{R_1} \right)$$

If $V_i \gg V_{os}$, V_{os} does not adversely affect performance

$V_i \sim V_{os}$, V_{os} presents a major problem

$V_i \ll V_{os}$, V_{os} is very difficult to manage

$$V_o = V_i \left(1 + \frac{R_2}{R_1} \right) + V_{os} \left(1 + \frac{R_2}{R_1} \right)$$

If $V_{os} = 3 \text{ mV}$

$$V_i = 3 \text{ mV}$$

$$1 + \frac{R_2}{R_1} = 1000$$


$$V_{offset} = (3 \text{ mV})(1000) = 3 \text{ V}$$

$$V_{o \text{ actual}} = (3 \text{ mV})(1000) + (3 \text{ mV})1000 = 6 \text{ V}$$

Methods of managing V_{os}

- 1) Cap. Coupling
- 2) Trimming V_{os}
- 3) use the premium OA


If $V_i = V_m \sin \omega t$

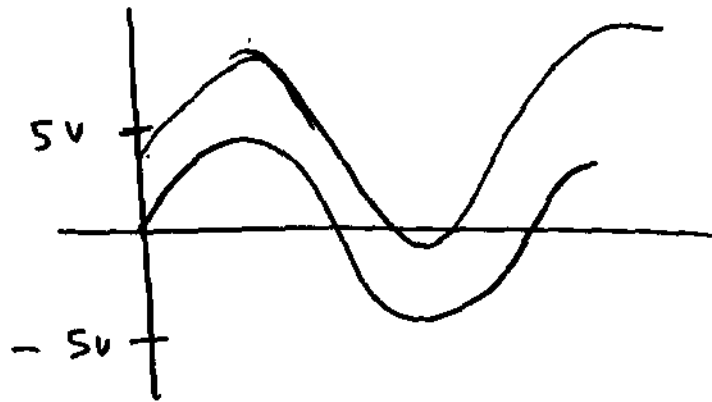

$$V_{os} = 3 \text{ mV}$$

$$A_v = 1000$$

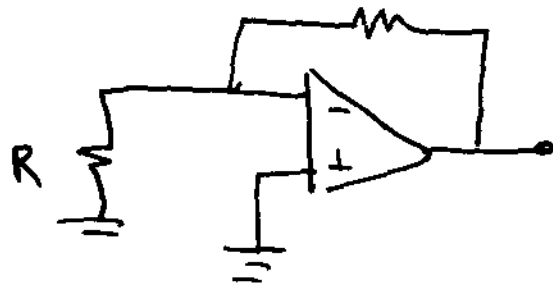Measurement of V_{os} (must be on every device if of concern)





$$V_o = V_{os}(1 + 100)$$

$$V_{os} = \frac{V_o}{101}$$

Nonlinear Op Amp Applications

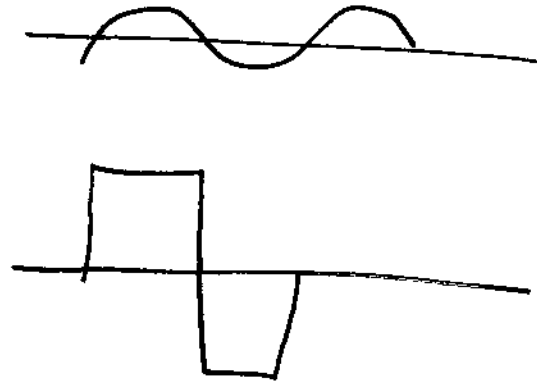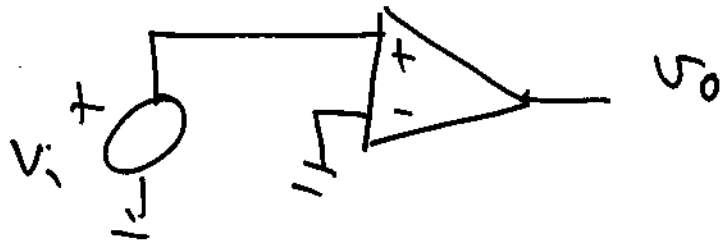Op Amp almost never used as amplifier
open loop



Comparator