

# EE 230

## Lecture 15

Basic Applications of Operational Amplifiers

Differential Amplifiers

Impedance Converters

Nonideal Op Amp Characteristics (if time permits)

Review from Last Time




# Applications of integrators to filter design

## The 2<sup>nd</sup> order Bandpass Filter
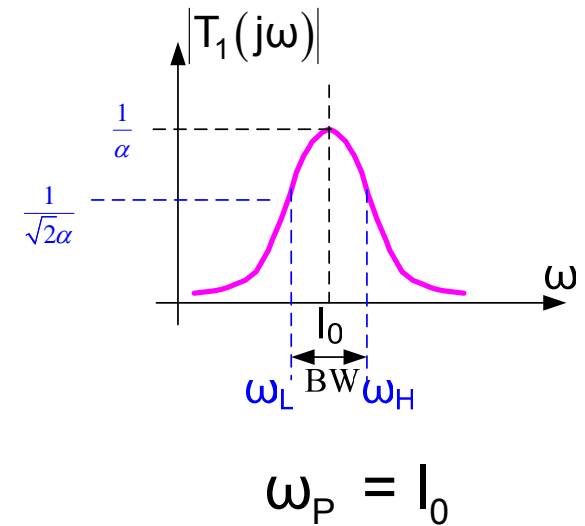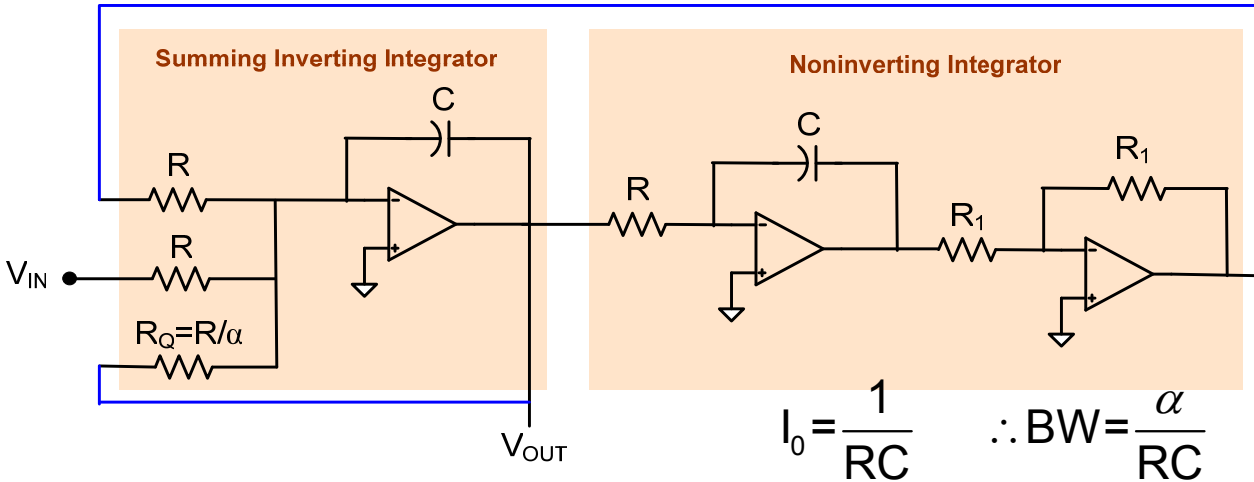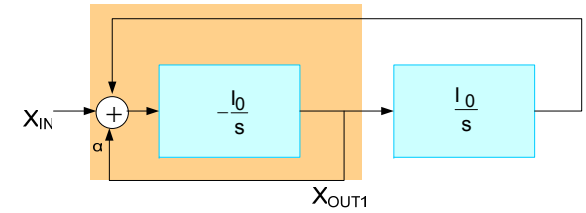
### Design Strategy

Assume BW and  $\omega_p$  are specified

$$T_{BP}(s) = \frac{-I_0 s}{s^2 + \alpha I_0 s + I_0^2}$$



1. Pick C (use some practical or convenient value)

2. Solve expression  $\omega_p = \frac{1}{RC}$  to obtain R

3. Solve expression  $BW = \frac{\alpha}{RC}$  to obtain  $\alpha$  and thus  $R_Q$




# Another 2<sup>nd</sup>-order Bandpass Filter

## Design Strategy

Assume BW,  $\omega_p$ , and K are specified

$$T(s) = -\frac{\frac{s}{R_3 C}}{s^2 + s\left(\frac{2}{R_1 C}\right) + \frac{1}{(R_2 // R_3) R_1 C^2}}$$
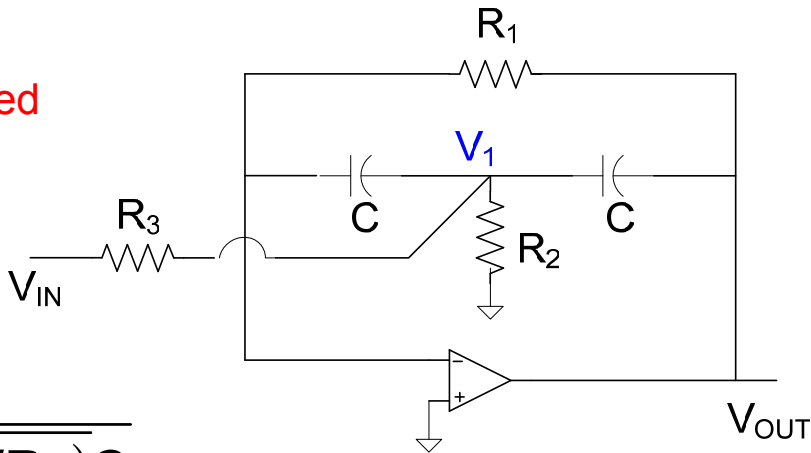
$$BW = \frac{2}{R_1 C} \quad \omega_p = \frac{1}{\sqrt{R_1 (R_2 // R_3) C}}$$




$$K = \frac{R_1}{2R_3}$$

1. Pick C to some practical or convenient value


2. Solve expression  $BW = \frac{2}{R_1 C}$  to obtain  $R_1$

3. Solve expression  $K = \frac{R_1}{2R_3}$  to obtain  $\alpha$  and thus  $R_3$

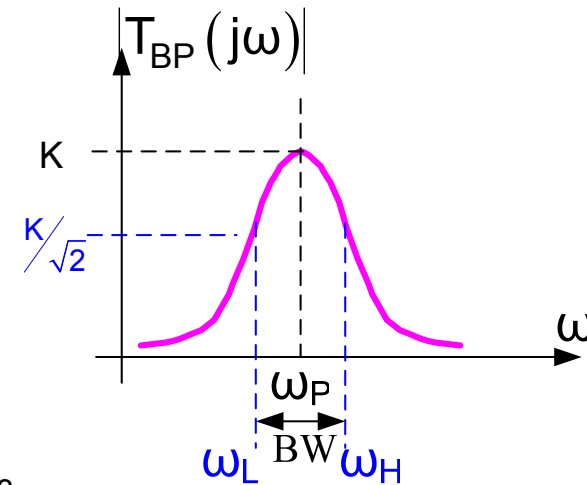4. Solve expression  $\omega_p = \frac{1}{\sqrt{R_1 (R_2 // R_3) C}}$  to obtain  $R_2$



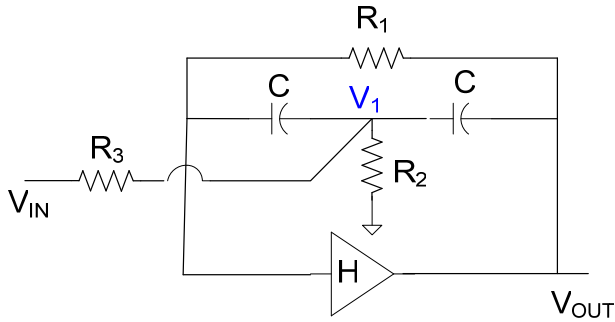
# STAR 2<sup>nd</sup>-order Bandpass Filter




$$T(s) = \frac{\frac{s}{R_3 C} \left( \frac{H}{H-1} \right)}{s^2 + s \left( \frac{2}{R_1 C} - \frac{1}{(R_2 // R_3)(H-1)} \right) + \frac{1}{(R_2 // R_3) R_1 C^2}}$$


Implementation:

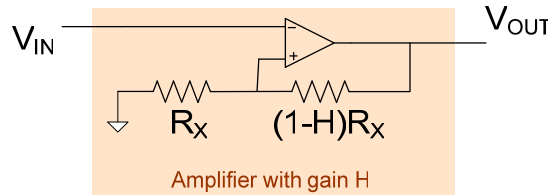

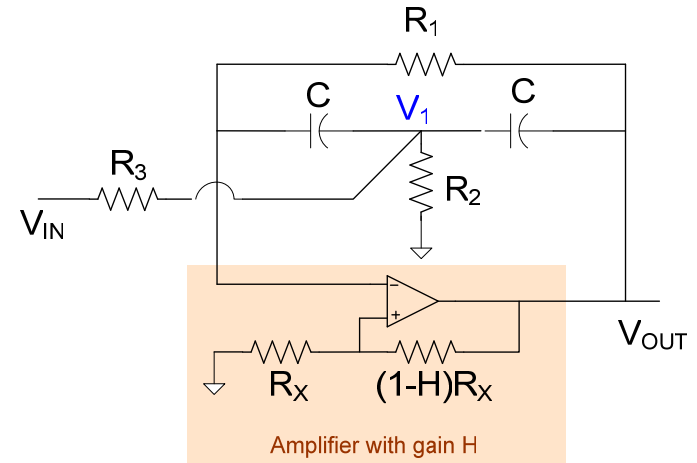If op amp ideal,  $\frac{V_{OUT}}{V_{IN}} = H$



Works fine !

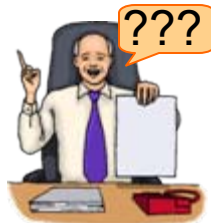

Will discuss why this happens later!

Reduces to previous bandpass filter at H gets large



Note that the “H” amplifier has feedback to positive terminal

# Differential Amplifiers


Many applications exist for difference (differential) amplifiers

Differential amplifiers are widely used

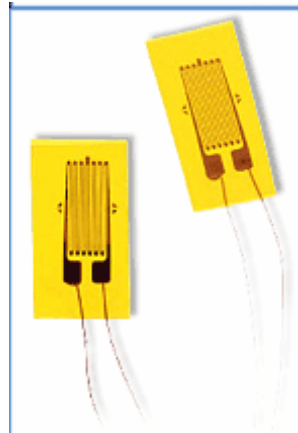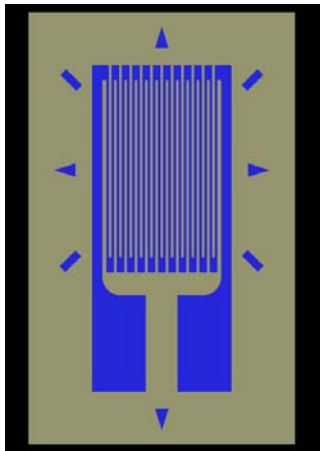Strain gage is one application that demonstrates some challenges



Metal foil strain gages

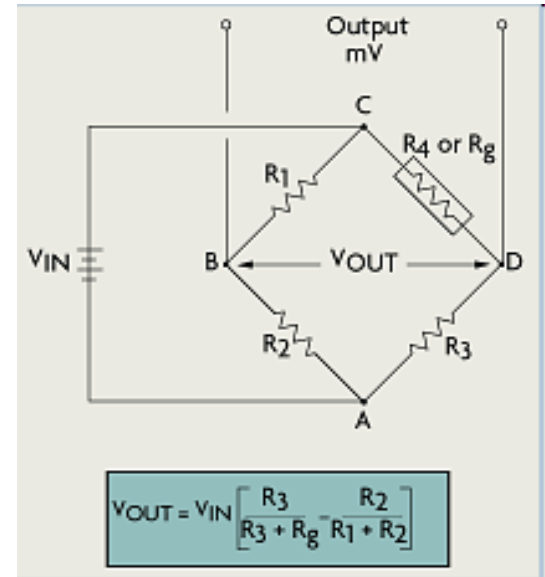

Wheatstone Bridge

<http://www.omega.com/prodinfo/straingages.html>


[http://en.wikipedia.org/wiki/Strain\\_gauge](http://en.wikipedia.org/wiki/Strain_gauge)

Assume  $V_A$  is ground

$V_{OUT}$  is very small compared to  $V_B$  and  $V_D$

# Differential Amplifiers

Ideal differential amplifier

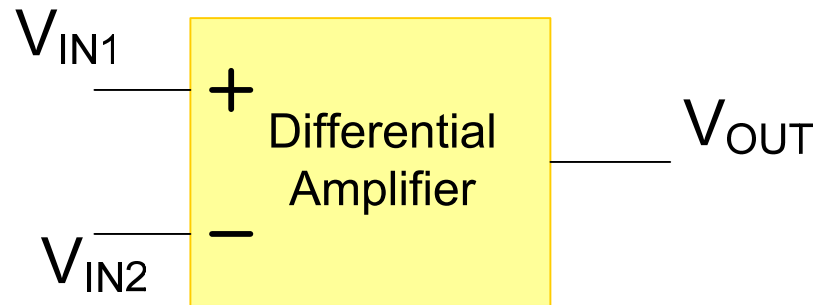

$$V_{OUT} = A(V_{IN1} - V_{IN2})$$

$$R_{OUT} = 0$$


$$\text{All } R_{IN} = \infty$$

Ideally the output is not dependent upon the size of  $V_{IN1}$  or  $V_{IN2}$  but only upon their difference

This creates a challenge when designing differential amplifiers

# Differential Amplifiers

## Differential amplifier application

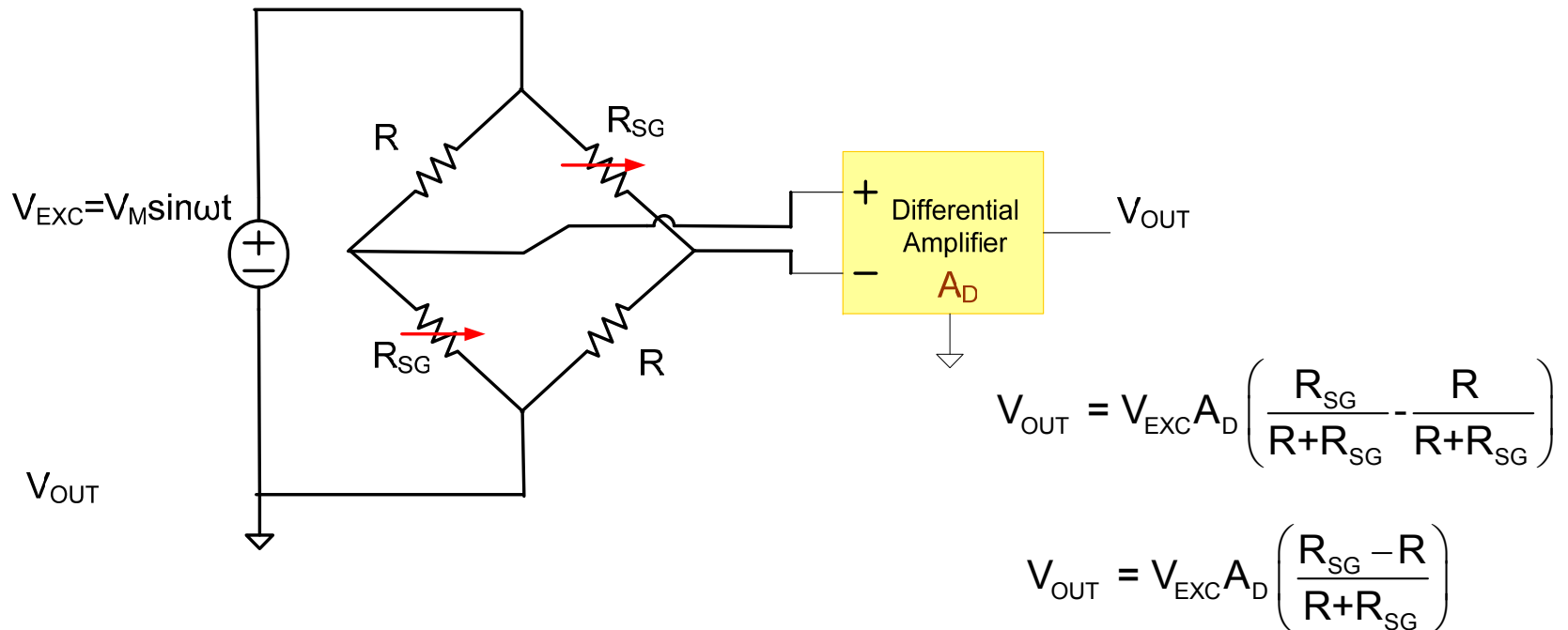


Let  $R_{SG} = R + \Delta R$

$$V_{OUT} = V_{EXC} A_D \left( \frac{\Delta R}{2R + \Delta R} \right) \approx V_{EXC} A_D \left( \frac{\Delta R}{2R} \right)$$

If  $\Delta R$  is very small and varies linearly with strain,  $V_{OUT}$  varies linearly with strain

# Differential Amplifiers

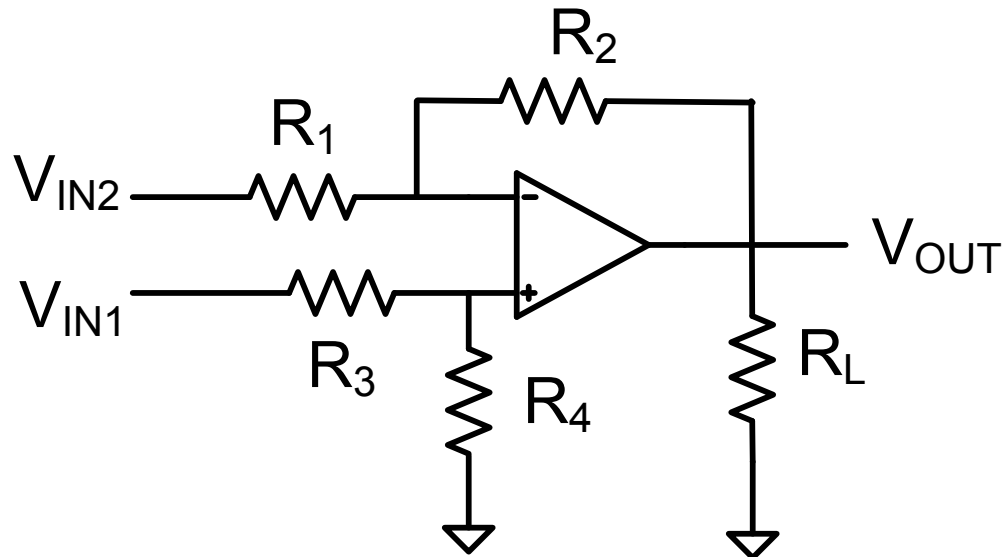

$$V_{OUT} = V_{IN1} \left( \frac{R_4}{R_3 + R_4} \left[ 1 + \frac{R_2}{R_1} \right] \right) - V_{IN2} \left( \frac{R_2}{R_1} \right)$$

$$V_{OUT} = V_{IN1} \left( \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} \right) - V_{IN2} \left( \frac{R_2}{R_1} \right)$$

If  $R_1 = R_3$  and  $R_2 = R_4$ , this becomes

$$V_{OUT} = V_{IN1} \left( \frac{R_2}{R_1} \right) - V_{IN2} \left( \frac{R_2}{R_1} \right)$$

$$V_{OUT} = \frac{R_2}{R_1} (V_{IN1} - V_{IN2})$$

Good matching is required to eliminate the dependence on  $V_{IN1}$  and  $V_{IN2}$



# Differential Amplifiers

## Common Mode and Difference Mode Gains

$$V_{OUT} = V_{IN1} \left( \frac{R_4}{R_3 + R_4} \left[ 1 + \frac{R_2}{R_1} \right] \right) - V_{IN2} \left( \frac{R_2}{R_1} \right)$$

Define

$$V_{INC} = \frac{V_{IN1} + V_{IN2}}{2} \quad V_{IND} = V_{IN1} - V_{IN2}$$

These can be expressed as

$$V_{IND} = V_{IN1} - V_{IN2} \quad V_{IN1} = V_{INC} + \frac{V_{IND}}{2}$$

$$V_{OUT} = \left( V_{INC} + \frac{V_{IND}}{2} \right) \left( \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} \right) - \left( V_{INC} - \frac{V_{IND}}{2} \right) \left( \frac{R_2}{R_1} \right)$$


$$V_{OUT} = V_{INC} \left( \left( \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} \right) - \left( \frac{R_2}{R_1} \right) \right) + V_{IND} \left( \frac{1}{2} \right) \left( \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} + \frac{R_2}{R_1} \right)$$

Define

$$A_{COM} = \left( \left( \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} \right) - \left( \frac{R_2}{R_1} \right) \right) \quad A_{DIFF} = \frac{1}{2} \left( \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} + \frac{R_2}{R_1} \right)$$

It follows that
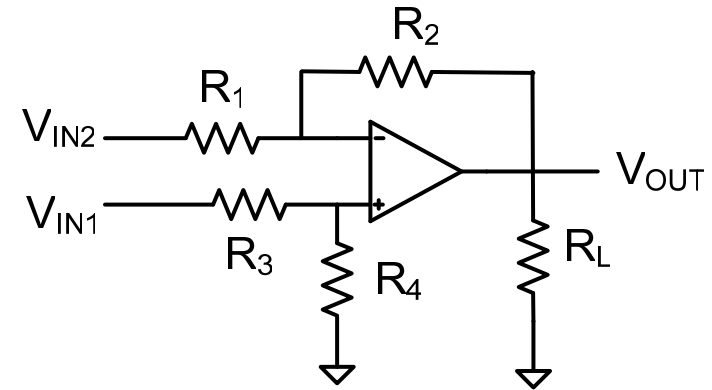
$$V_{OUT} = V_{INC} A_{COM} + V_{IND} A_D$$



$R_{IN}$  on each terminal is  $R_3 + R_4$

If  $R_1 = R_3$  and  $R_2 = R_4$

$$A_{COM} = 0 \quad A_{DIFF} = \frac{R_2}{R_1}$$

$$V_{OUT} = A_{DIFF} V_{IND}$$

Good matching is required to eliminate  $V_{INC}$   
Not easy to adjust or trim the gain

# Differential Amplifiers

Example: Consider the performance of the bridge structure driving the differential amplifier where  $A_D$  is nominally 10,000. Neglect loading of bridge with the differential amplifier

Assume  $\Delta R = .00005R$

$$V_{\text{EXC}} = 4\sin\omega t$$

$$V_{\text{IN1}} = V_{\text{EXC}} \left( \frac{R_{\text{SG}}}{R + R_{\text{SG}}} \right) \approx \frac{V_{\text{EXC}}}{2} \left( 1 + \frac{\Delta R}{R} \right)$$

$$V_{\text{IN2}} = V_{\text{EXC}} \left( \frac{R}{R + R_{\text{SG}}} \right) \approx \frac{V_{\text{EXC}}}{2} \left( 1 - \frac{\Delta R}{R} \right)$$


$$V_{\text{IN1}} = 2.0001\sin\omega t \quad V_{\text{IN2}} = 1.9999\sin\omega t$$

$$V_{\text{IND}} = V_{\text{IN1}} - V_{\text{IN2}} = .0002\sin\omega t$$

$$V_{\text{INC}} = \frac{V_{\text{IN1}} + V_{\text{IN2}}}{2} \approx 2\sin\omega t$$

All signal information is carried in the difference signal  $V_{\text{IND}}$

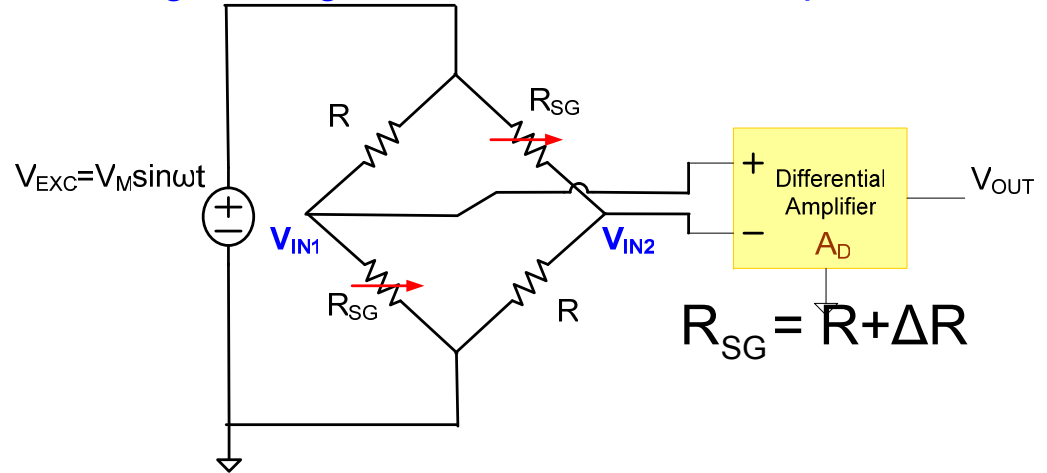But observe  $V_{\text{IND}} \ll V_{\text{INC}}$



# Differential Amplifiers

## Example (cont)

$$V_{IN1} = 2.0001 \sin \omega t \quad V_{IN2} = 1.9999 \sin \omega t$$

$$V_{INC} = 2 \sin \omega t \quad V_{IND} = .0002 \sin \omega t$$


Case 1 Matched resistors

If  $R_1 = R_3$  and  $R_2 = R_4$

$$V_{OUT} = A_{DIFF} V_{IND}$$

$$A_{DIFF} = \frac{R_2}{R_1} \quad A_{COM} = 0 \quad \frac{R_2}{R_1} = 10000$$
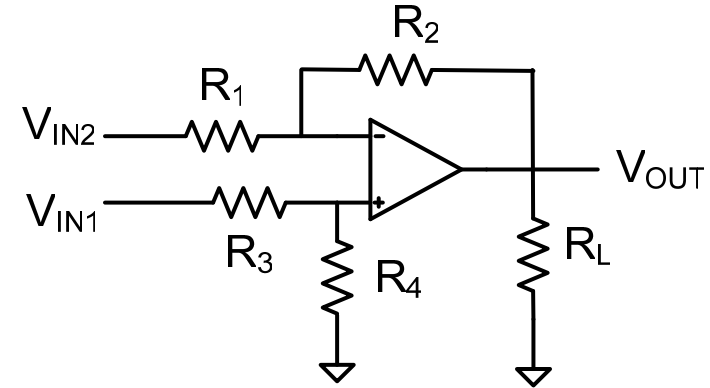
$$V_{OUT} = 10000 \cdot .0002 \sin \omega t = 2 \sin \omega t$$



$$V_{OUT} = V_{INC} \left( \left( \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} \right) - \left( \frac{R_2}{R_1} \right) \right) + V_{IND} \left( \frac{1}{2} \right) \left( \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} + \frac{R_2}{R_1} \right)$$

Ideally  $R_1 = R_3$  and  $R_2 = R_4$

# Differential Amplifiers


## Example (cont)

$$V_{IN1} = 2.0001 \sin \omega t \quad V_{IN2} = 1.9999 \sin \omega t$$

$$V_{INC} = 2 \sin \omega t \quad V_{IND} = .0002 \sin \omega t$$

Case 1 Matched resistors

$$V_{OUT} = 2 \sin \omega t$$

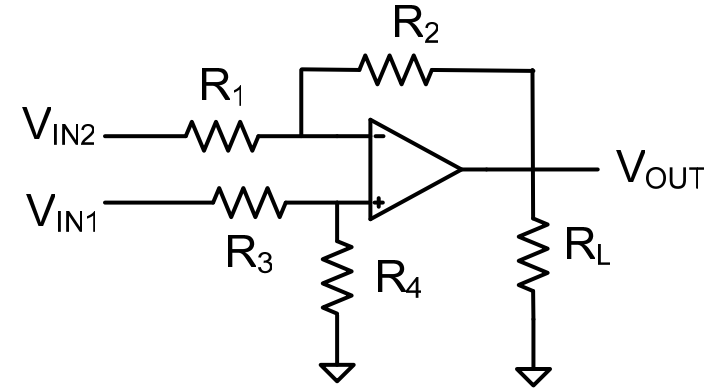

Case 2  $R_1 = R_3$ ,  $R_4 = 1.01 R_2$   $\frac{R_2}{R_1} = 10000$

$$V_{OUT} = V_{INC} \left( \left( \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} \right) - \left( \frac{R_2}{R_1} \right) \right) + V_{IND} \left( \frac{1}{2} \right) \left( \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} + \frac{R_2}{R_1} \right)$$

Ideally  $R_1 = R_3$  and  $R_2 = R_4$

$$V_{OUT} = V_{INC} \left( \left( \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} \right) - \left( \frac{R_2}{R_1} \right) \right) + V_{IND} \left( \frac{1}{2} \right) \left( \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} + \frac{R_2}{R_1} \right)$$

$$V_{OUT} = V_{INC} \left( \left( \frac{10001 R_1}{10101 R_1} \cdot \frac{1.01 \cdot 10000 R_1}{R_1} \right) - (10000) \right) + V_{IND} \left( \frac{1}{2} \right) \left( \left( \frac{10001 R_1}{10101 R_1} \cdot \frac{1.01 \cdot 10000 R_1}{R_1} \right) + 10000 \right)$$

$$V_{OUT} = V_{INC} (.0099) + V_{IND} (10000.005)$$

$$V_{OUT} = 2 \sin \omega t (.0099) + (.0002 \sin \omega t) (10000.005)$$


$$V_{OUT} = \sin \omega t (.0198) + (\sin \omega t) (2.000001)$$

$$V_{OUT} = (\sin \omega t) (2.019801)$$

Note a 1% error in a resistor causes a 2% error in output

# Differential Amplifiers

## Buffered Difference Amplifier

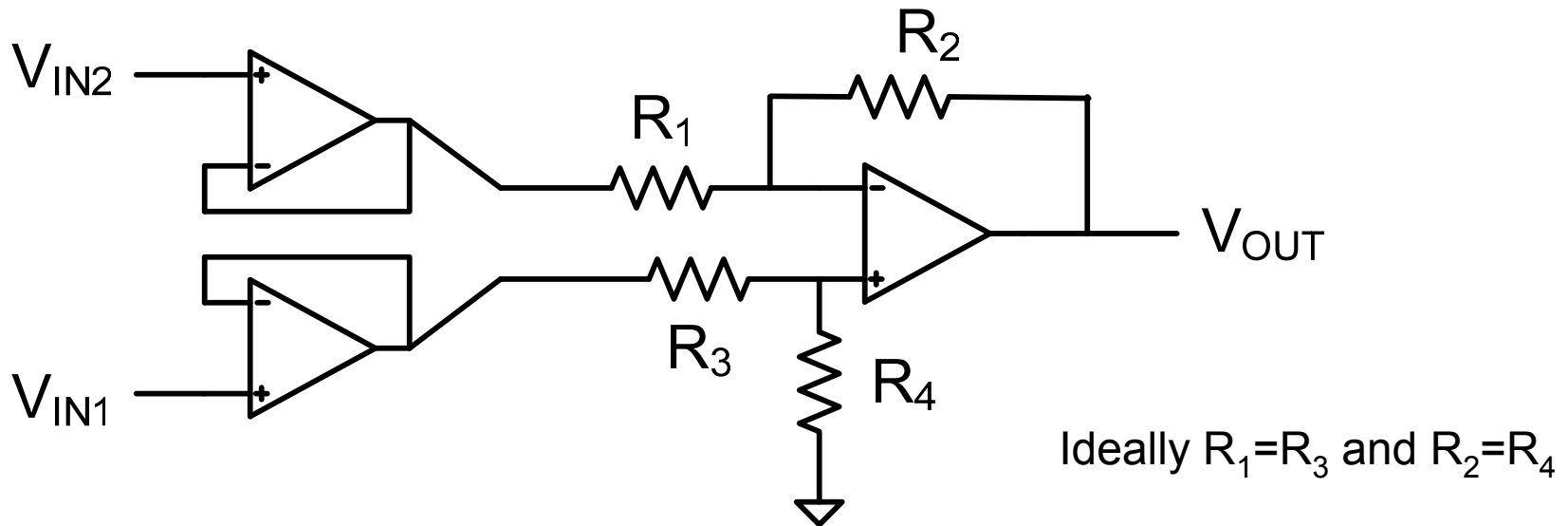


Minimizes loading effect of difference amplifier on source

Not easy to adjust or trim the gain

# Differential Amplifiers


## Buffered Difference Amplifier

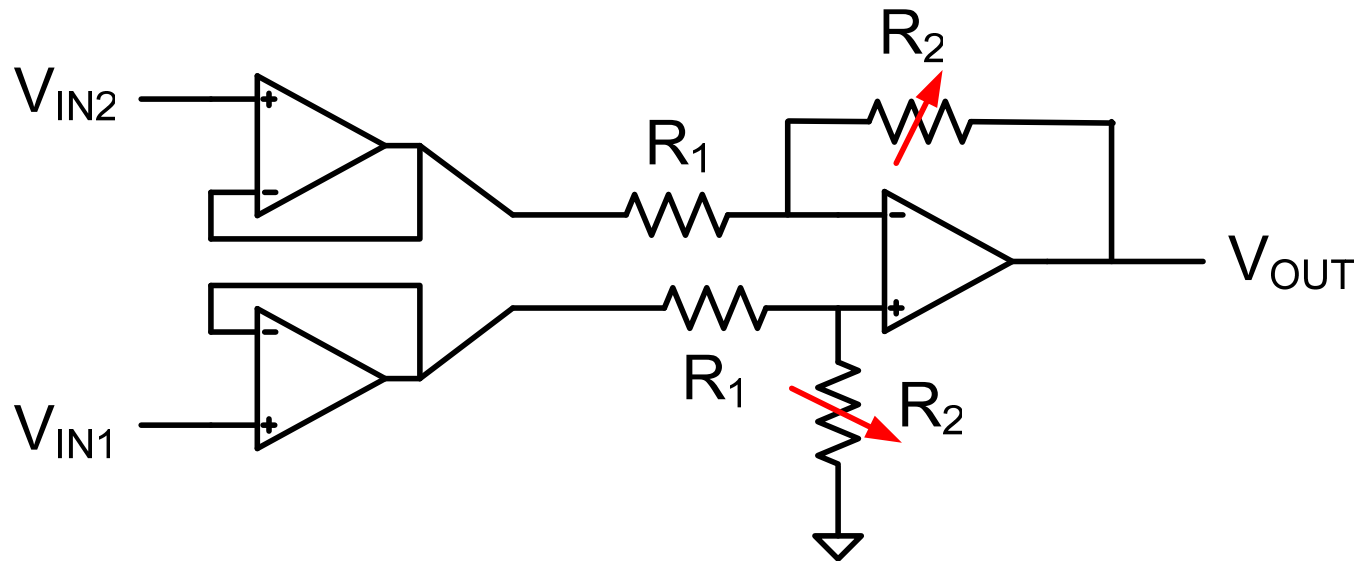

Not easy to adjust or trim the gain

# Differential Amplifiers

## Instrumentation Amplifier

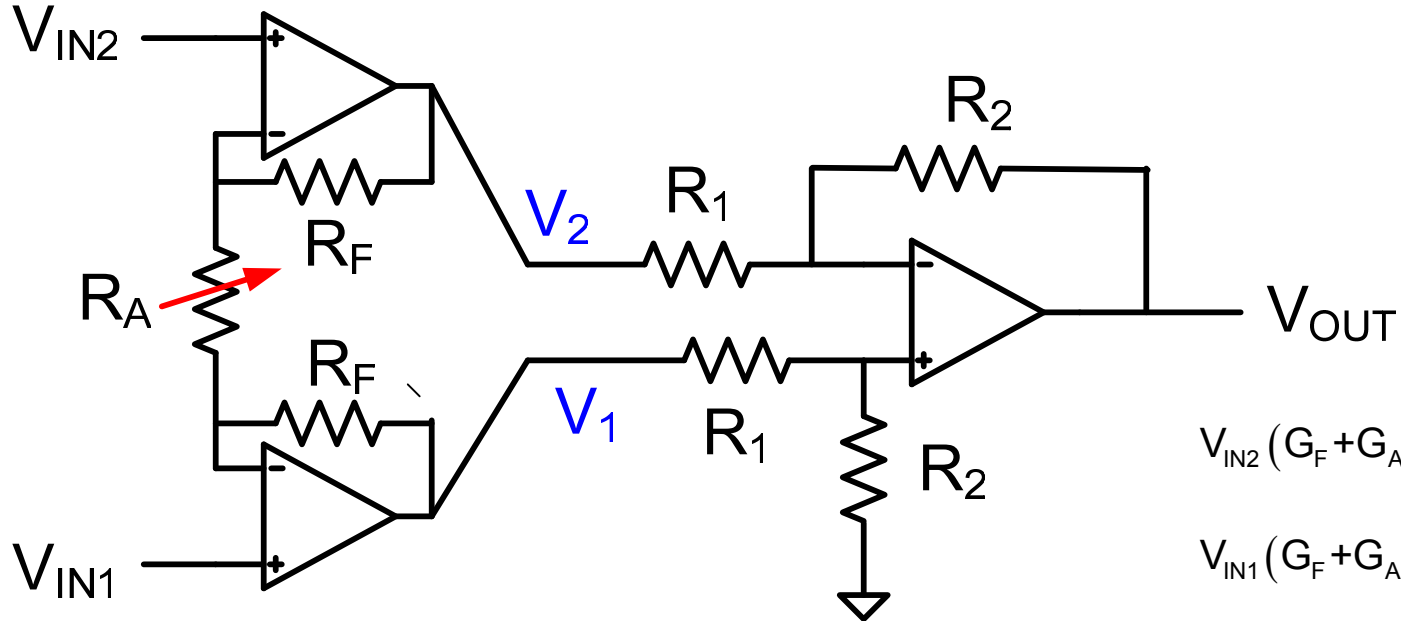

$$V_{IN2}(G_F + G_A) = G_F V_2 + G_A V_{IN1}$$

$$V_{IN1}(G_F + G_A) = G_F V_1 + G_A V_{IN2}$$

$$(V_{IN2} - V_{IN1})(G_F + G_A) = G_F (V_2 - V_1) + G_A (V_{IN1} - V_{IN2})$$

$$(V_{IN2} - V_{IN1})(G_F + 2G_A) = G_F (V_2 - V_1)$$


$$(V_{IN2} - V_{IN1}) \left( 1 + 2 \frac{R_F}{R_A} \right) = (V_2 - V_1)$$

$$V_{OUT} = (V_{IN2} - V_{IN1}) \left( 1 + 2 \frac{R_F}{R_A} \right) \left( \frac{R_2}{R_1} \right)$$

- Gain can be adjusted with the single resistor  $R_A$
- Gain adjustment does not affect trimming of  $R_1$  or  $R_2$
- Input impedance is infinite
- Can provide higher gains

# Differential Amplifiers



## Instrumentation Amplifier

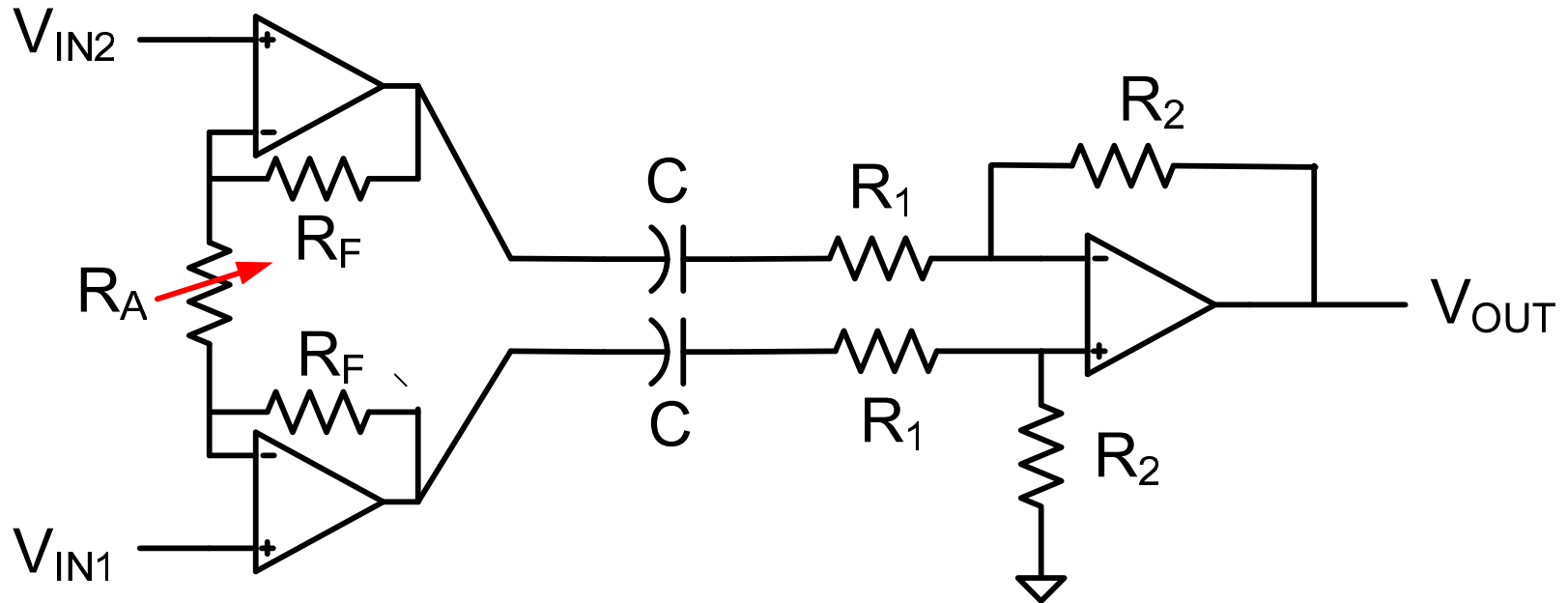

- Can reduce effects of dc offset if gain must be very large
- Must pick  $C$  to that frequencies of interest are in passband




# Impedance Converters

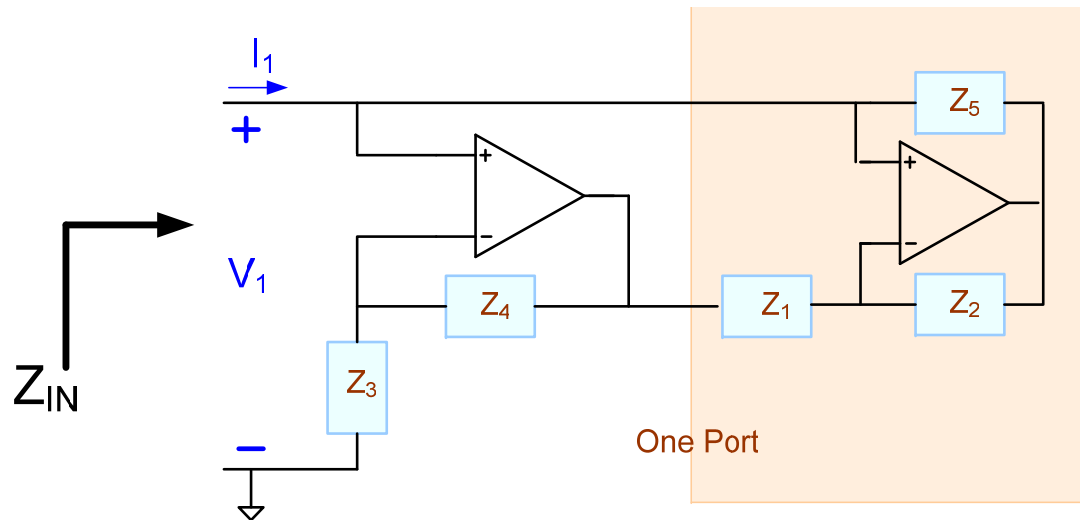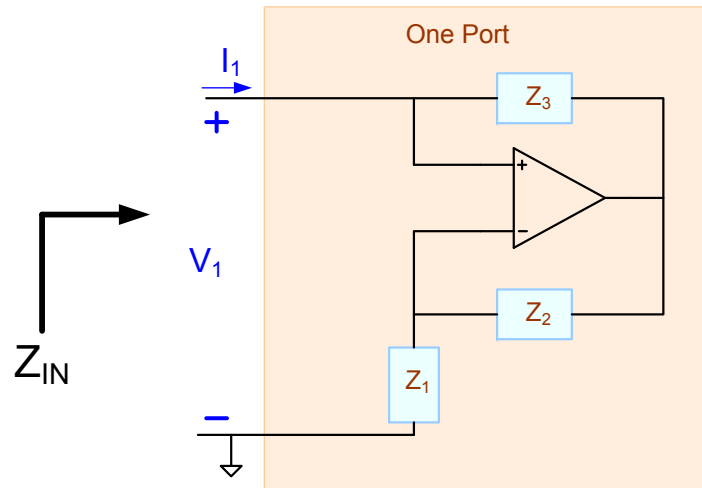

Note these circuits are strictly one-ports and have no output node

# Impedance Converters

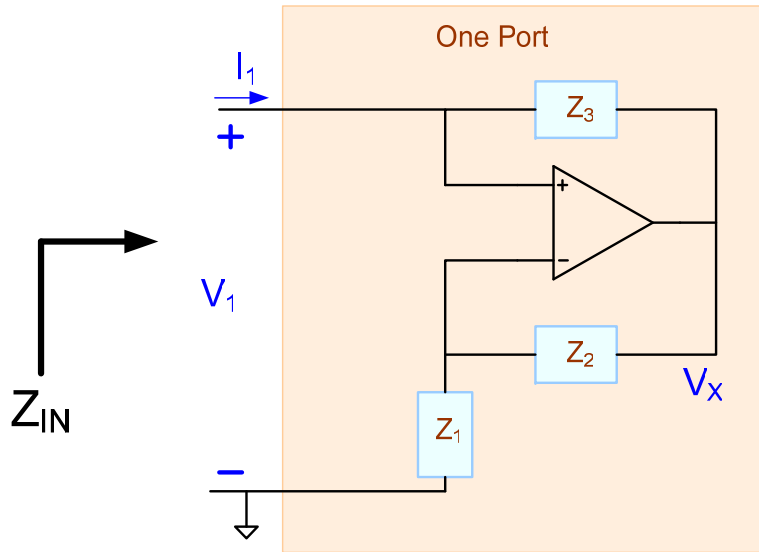


$$\left. \begin{aligned} V_1(G_1 + G_2) &= V_x G_2 \\ I_1 &= (V_1 - V_x) G_3 \end{aligned} \right\}$$

$$Z_{IN} = -\frac{Z_1 Z_3}{Z_2}$$

Observe this input impedance is negative!

# Impedance Converters

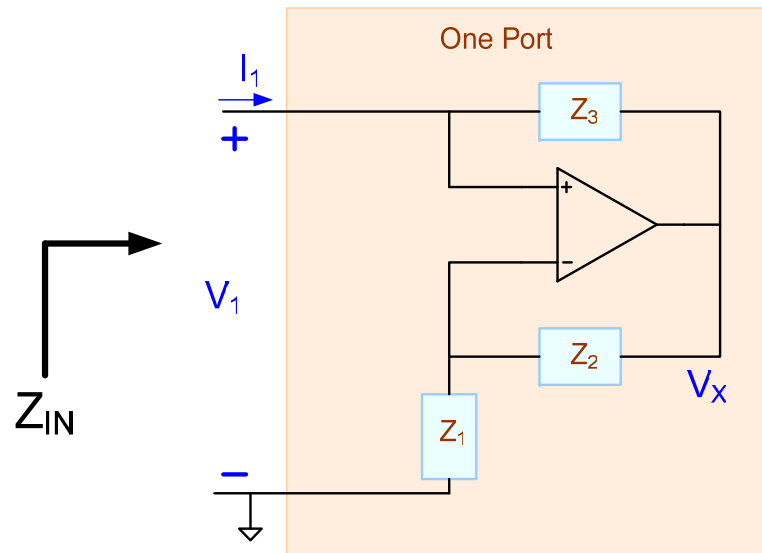

$$Z_{IN} = -\frac{Z_1 Z_3}{Z_2}$$

If  $Z_1=R_1$ ,  $Z_2=R_2$  and  $Z_3=R_3$ ,

$$Z_{IN} = -\frac{R_1 R_3}{R_2}$$

This is a negative resistor !

If  $Z_2=1/sC$ ,  $Z_1=R_1$  and  $Z_3=R_3$ ,

$$Z_{IN} = -sCR_1 R_3$$

This is a negative inductor !


If  $Z_2=R_2$ ,  $Z_1=1/sC$  and  $Z_3=R_3$ ,

$$Z_{IN} = -\frac{R_3}{sCR_2}$$

This is a negative capacitor !

**This is termed a Negative Impedance Converter**

# Impedance Converters

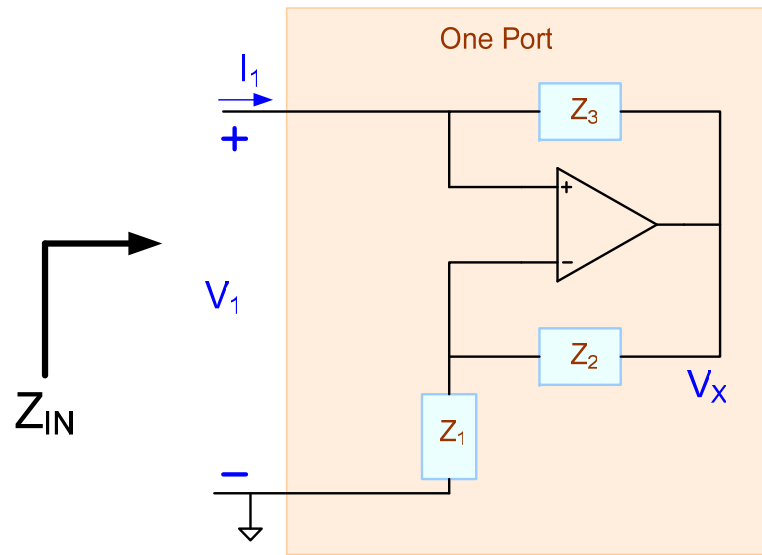



$$Z_{IN} = -\frac{Z_1 Z_3}{Z_2}$$

If  $Z_2 = 1/sC$ ,  $Z_1 = R_1$  and  $Z_3 = R_3$ ,  $Z_{IN} = -sCR_1R_3$


Modification of NIC to provide a positive inductance:

Replace  $Z_1$  itself with a second NIC that has a negative input impedance


# Negative Impedance Converter

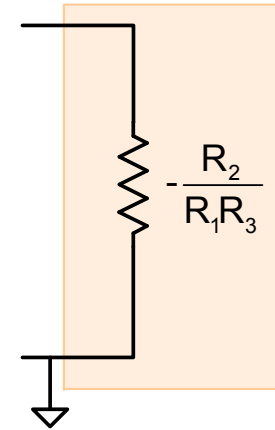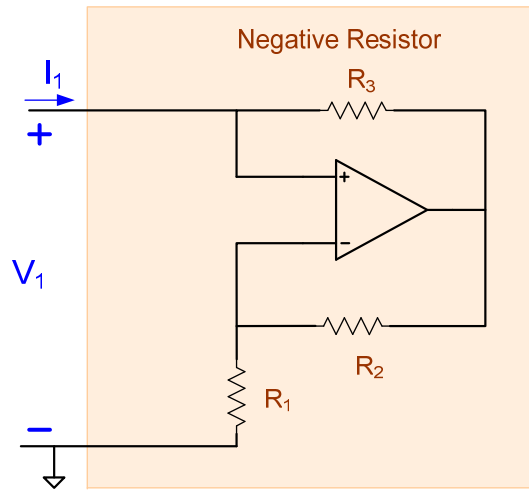

## One application of NIC

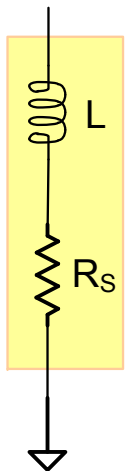


Lossy Inductor

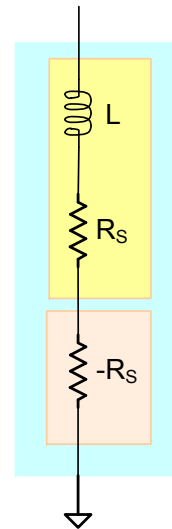

If select components so that  $R_s = \frac{R_2}{R_1 R_3}$

Lossless Inductor


# Impedance Converters

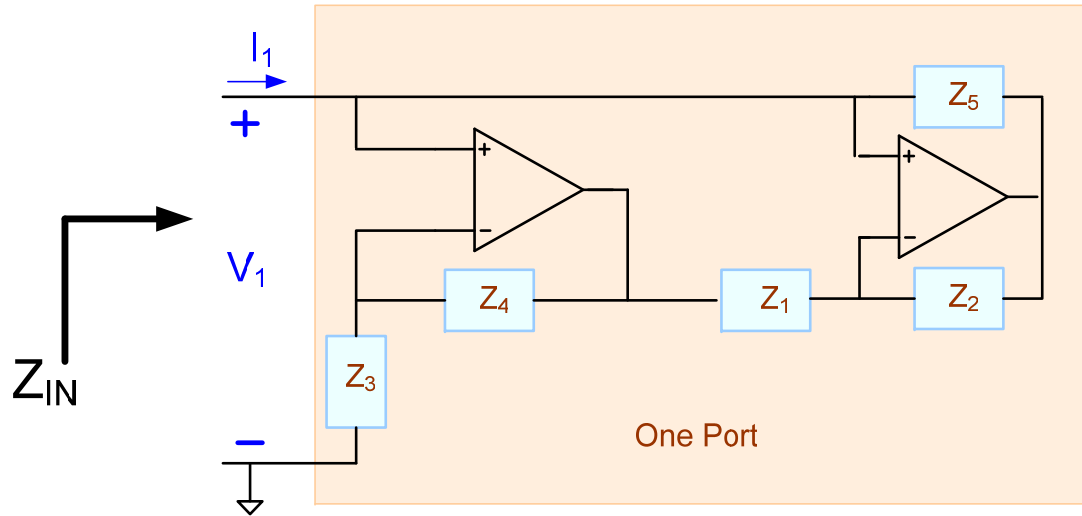

$$Z_{IN} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$

**This circuit is often called a Gyrator**

# Gyrator Analysis

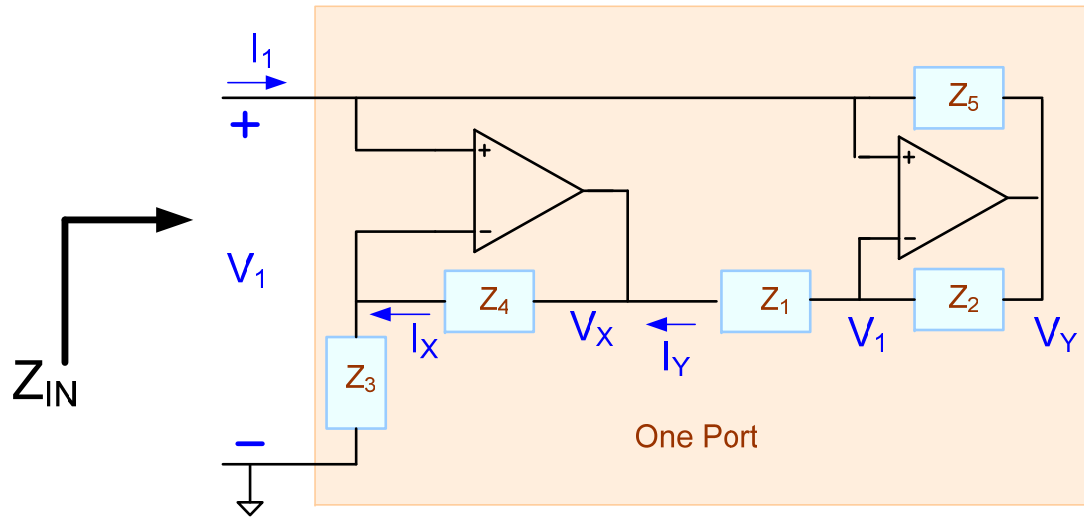

$$I_X = V_1 G_3$$

$$V_X = V_1 + V_1 G_3 / G_4 = V_1 \left( 1 + \frac{G_3}{G_4} \right)$$


$$I_Y = (V_1 - V_X) G_1 = V_1 \left( -\frac{G_3}{G_4} \right) G_1$$

$$V_Y = V_1 + I_Y / G_2 = V_1 \left( 1 - \frac{G_3}{G_4} \left( \frac{G_1}{G_2} \right) \right)$$

$$I_1 = (V_1 - V_Y) G_5 = V_1 \left( \frac{G_3}{G_4} \left( \frac{G_1}{G_2} \right) \right) G_5$$

$$Z_{IN} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$

# Gyrator Applications

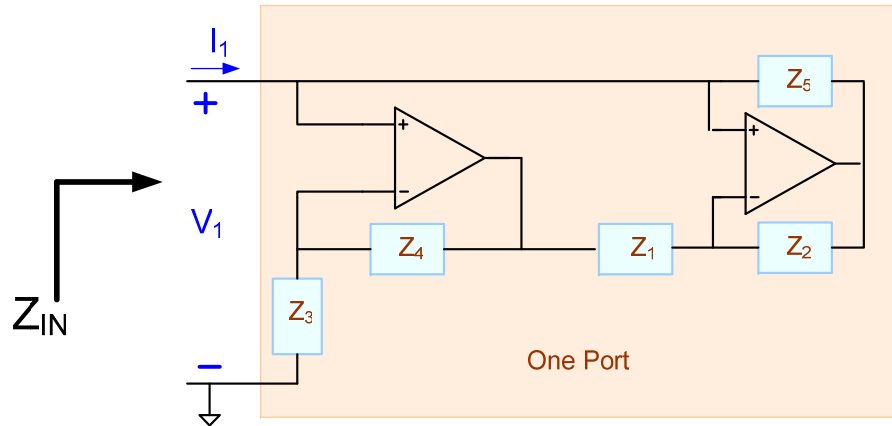

$$Z_{IN} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$

If  $Z_1=Z_3=Z_4=Z_5=R$  and  $Z_2=1/sC$        $Z_{IN} = (R^2C)s$       This is an inductor of value  $L=R^2C$


If  $Z_2=R_2$ ,  $Z_3=R_3$ ,  $Z_4=R_4$ ,  $Z_5=R_5$  and  $Z_1=1/sC$        $Z_{IN} = \frac{R_3 R_5}{s C R_2 R_4}$

This is a capacitor of value       $C_{EQ} = C \frac{R_2 R_4}{R_3 R_5}$       (can scale capacitance up or down)

If  $Z_2=Z_4=Z_5=R$  and  $Z_1=Z_3=1/sC$        $Z_{IN} = (R^3 C^2)s^2$       This is a "super" capacitor of value  $R^3 C^2$



# Impedance Converters

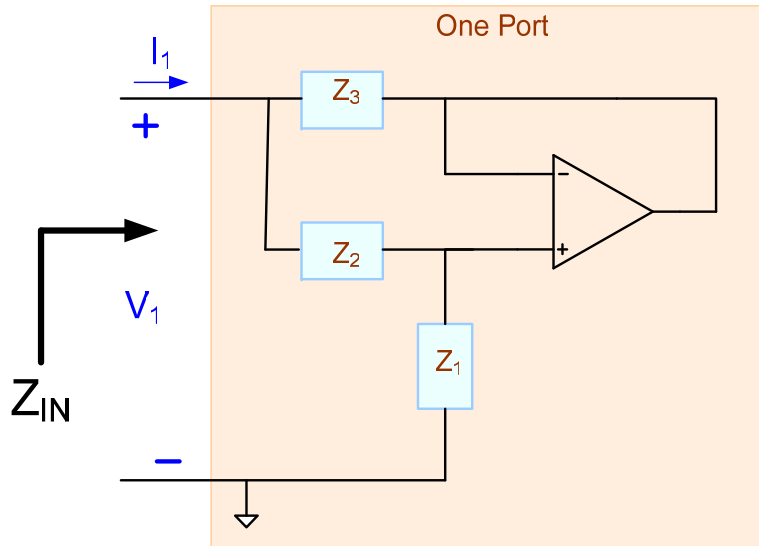


$$I_1 = \left( V_1 - \left( \frac{Z_1}{Z_1 + Z_2} \right) V_1 \right) G_3$$

$$Z_{IN} = Z_3 \left( 1 + \frac{Z_2}{Z_1} \right)$$

If  $Z_3 = R_3$ ,  $Z_2 = R_2$  and  $Z_1 = 1/sC$

$$Z_{IN} = R_3 + s(CR_2R_3)$$

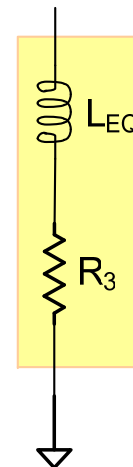

$$L_{EQ} = CR_2R_3$$

**End of Lecture 15**