

EE 230


Lecture 28

Nonlinear Circuits using Diodes

- Rectifiers
- Precision Rectifiers
- Nonlinear function generators

Quiz 18

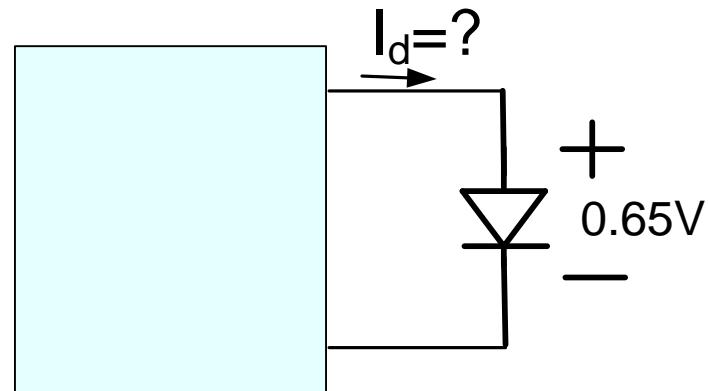If a diode has a value of $I_S=1E-14A$ and the diode voltage is $.65V$, what will be the diode current if operating at $T=300K$?



And the number is ?

1

3

8

5

4

2

6

9


7

And the number is ?

1 3 8
5 3 4
2 6 7
9

Quiz 18

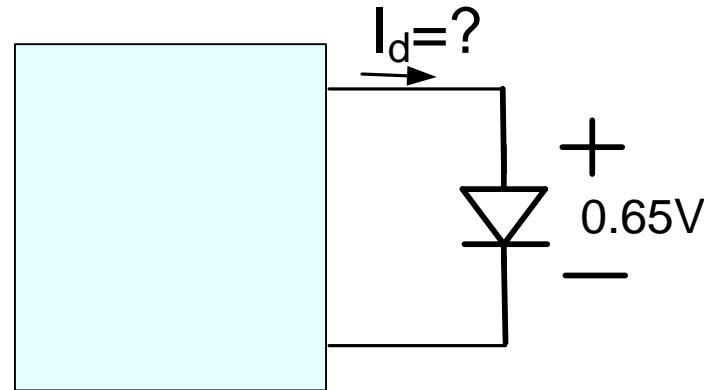If a diode has a value of $I_S=1E-14A$ and the diode voltage is $.65V$, what will be the diode current if operating at $T=300K$?



Solution:

$$I_d = I_s \left(e^{\frac{V_d}{V_t}} - 1 \right)$$

$$I_d = 1E-14 \left(e^{\frac{0.65}{300 \cdot 8.63E-5}} \right) = 1E-14 \cdot 8E10 = 800\mu A$$

Review from Last Time:


The Real Electronics World

Linear Circuits

Resistive Networks

Passive Filters
(RLC Networks)

Nonlinear Circuits

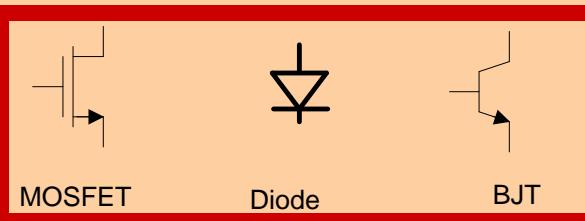

All Logic Circuits

Comparators

Nonlinear Amplifiers

Linearized Nonlinear Circuits
(small signal model)

Amplifiers
(Dependent Sources)

Sensor
Interfaces





Analog to Digital
Converters (ADC)

Digital to Analog
Converters (DAC)

Waveform
Generators

Review from Last Time:


The Diode

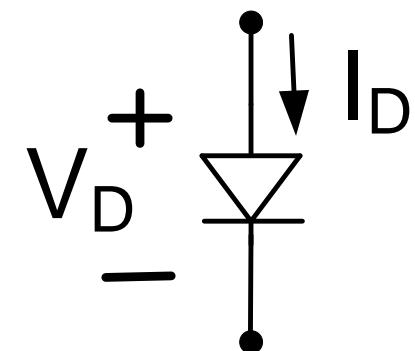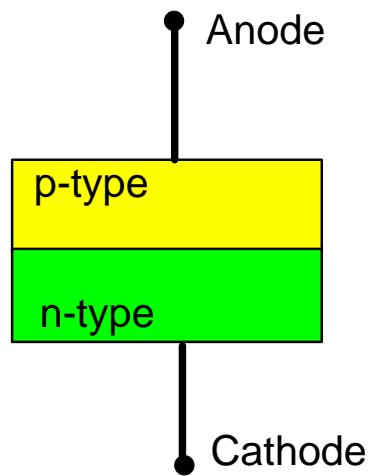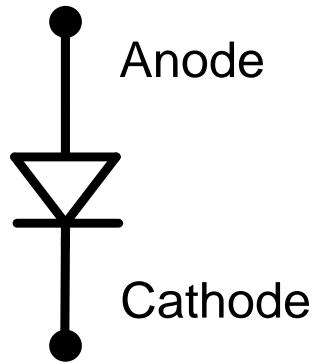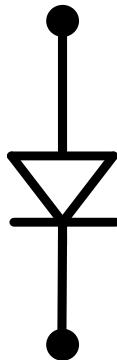


Review from Last Time:

Types of Diodes


pn junction diodes

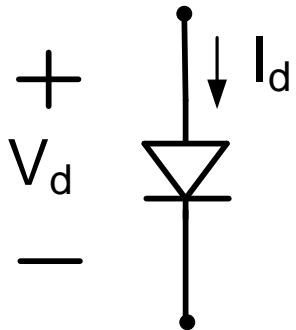


Signal or
Rectifier

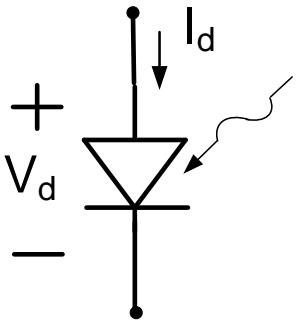


Pin or
Photo

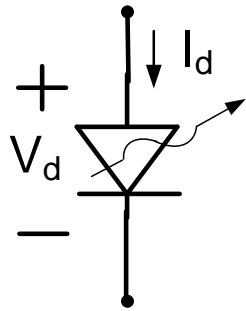


Light Emitting
LED
Laser Diode

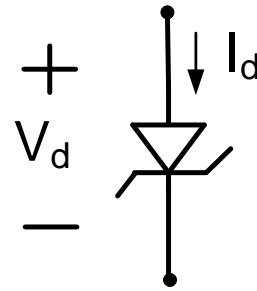




Zener

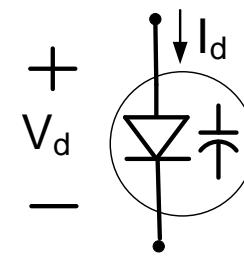

Varactor or
Varicap

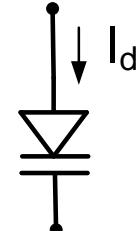


Metal-semiconductor junction diodes

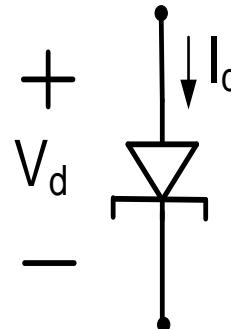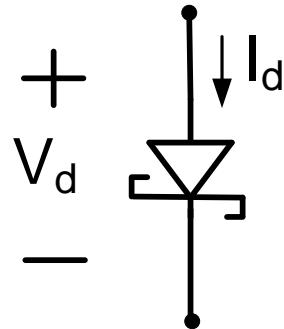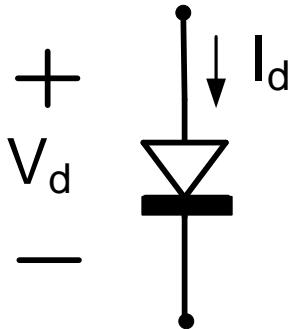

Schottky Barrier

Review from Last Time:

The Ideal Diode

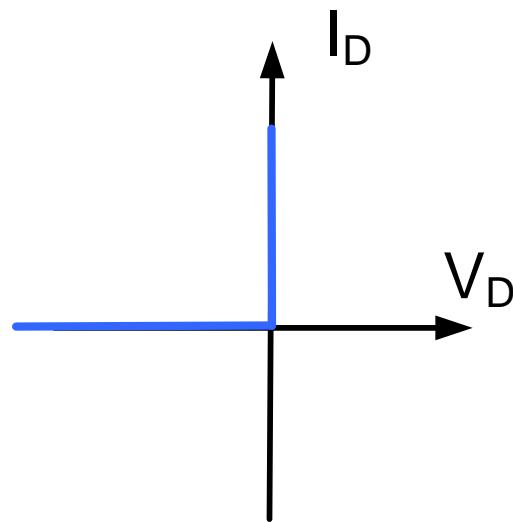

$$I_D = 0 \quad \text{if} \quad V_D \leq 0$$
$$V_D = 0 \quad \text{if} \quad I_D > 0$$


“OFF”

“ON”




“ON”

“OFF”

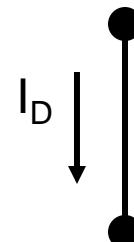

Valid for

$$I_D > 0$$

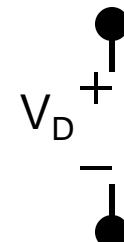


$$V_D \leq 0$$

Review from Last Time:

Diode equation (silicon pn junction diodes)
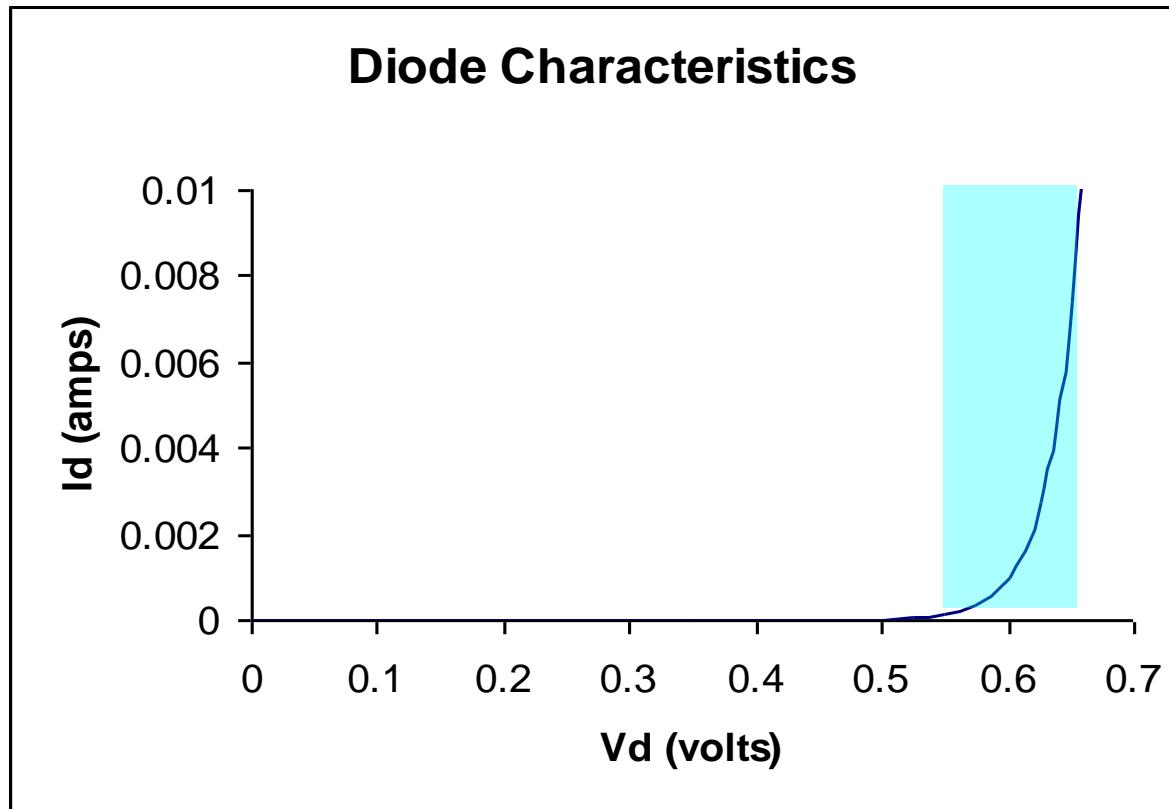
$$I_d = I_s \left(e^{\frac{V_d}{V_t}} - 1 \right)$$




Widely Used Piecewise Linear Model

Review from Last Time:

A more accurate approximation to the diode equation
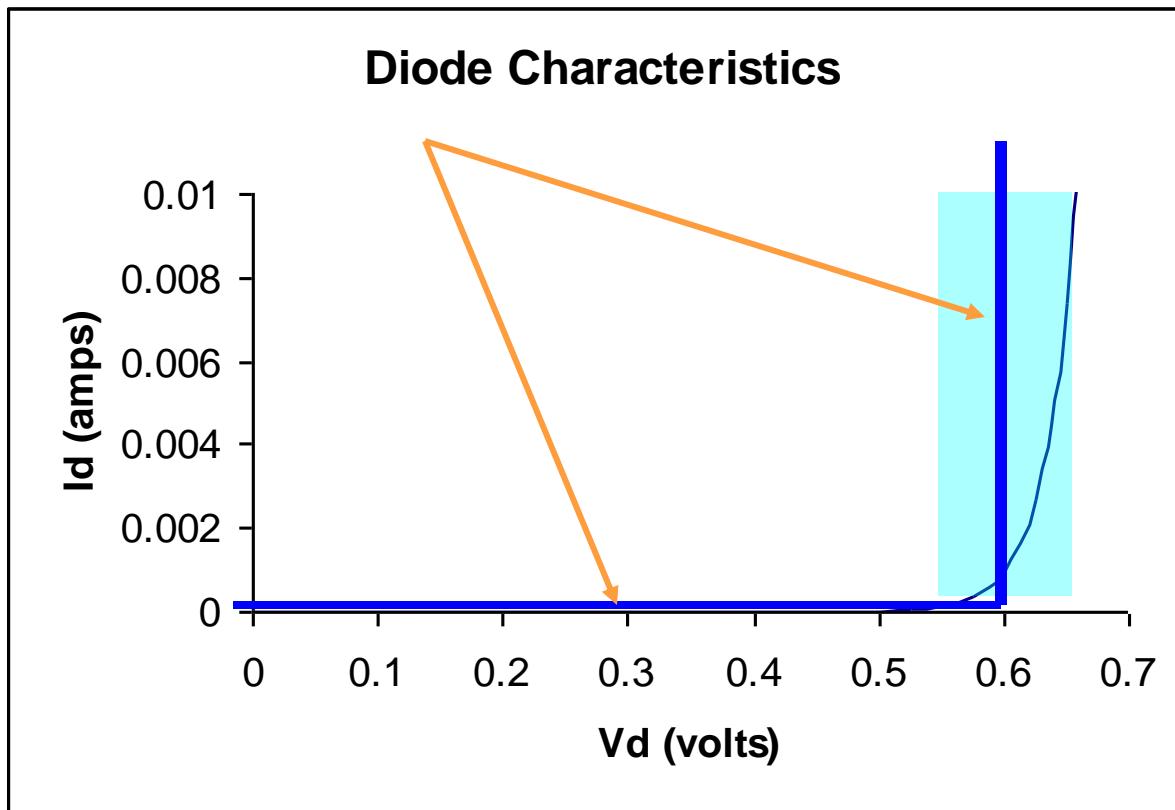
$$I_d = I_s \left(e^{\frac{V_d}{V_t}} - 1 \right)$$



More accurate pn junction
diode model:



$$\begin{array}{ll} I_d = 0 & V_d < 0.6V \\ V_d = 0.6V & I_d > 0 \end{array}$$

Review from Last Time:

A more accurate approximation to the diode equation




$$I_d = I_s \left(e^{\frac{V_d}{V_t}} - 1 \right)$$

Piecewise Linear Model



$$I_d = 0 \quad V_d < 0.6V$$

$$V_d = 0.6V \quad I_d > 0$$

Equivalent Circuit

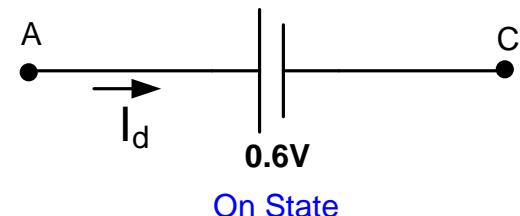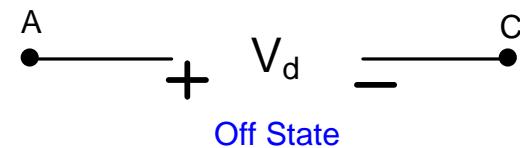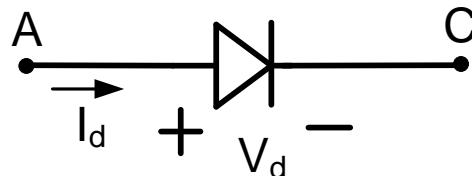


Review from Last Time:

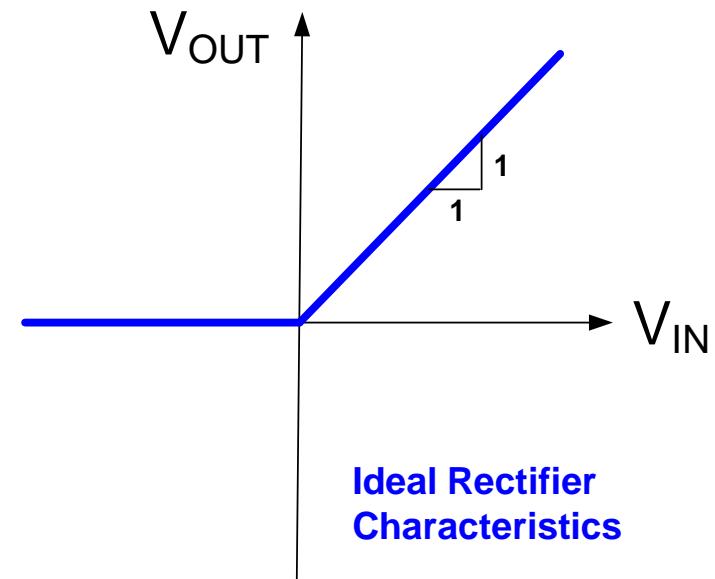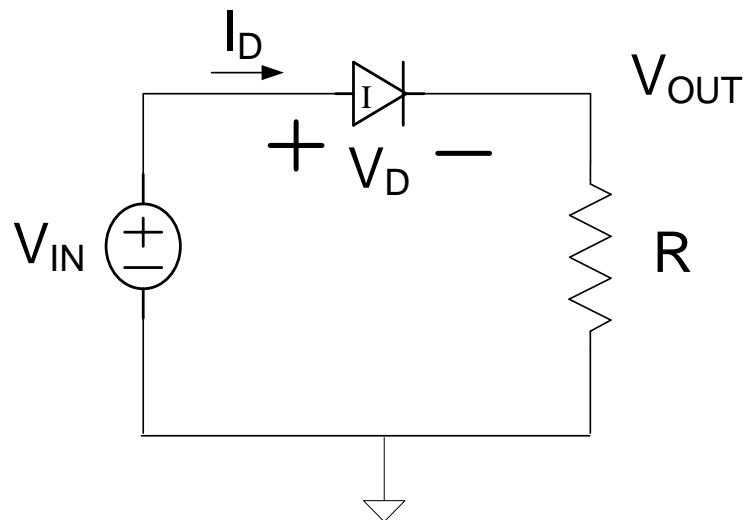


Diode rectifier circuit

If $V_{IN} = V_M \sin \omega t$

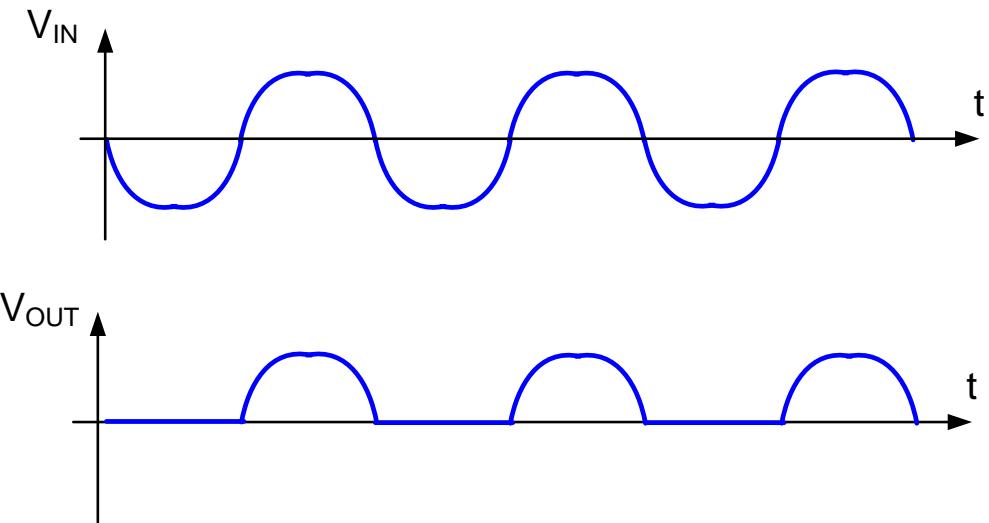

Serves as a rectifier – very useful function !

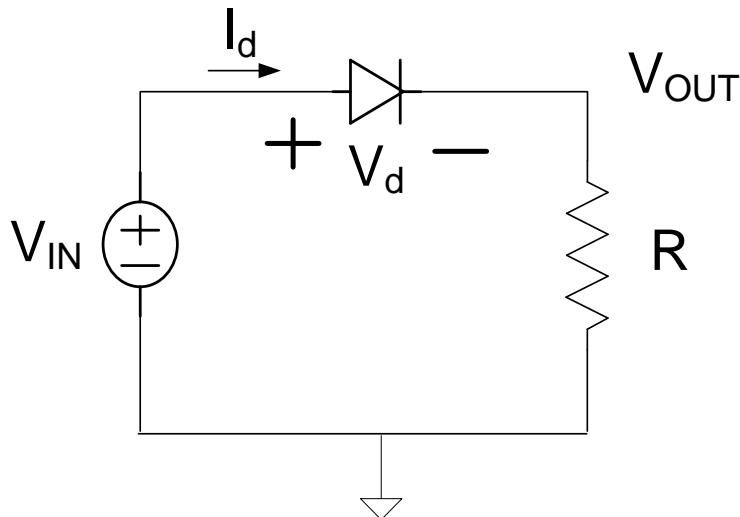Consider again the basic rectifier circuit



Analyze with piecewise linear model $I_d = 0$ $V_d \leq 0.6V$

$$V_d = 0.6V \quad I_d > 0$$

Case 1 $I_d = 0$


$$V_{OUT} = 0$$

valid for $V_d \leq 0.6V$


but $V_d = V_{IN}$

\therefore valid for

$$V_{IN} \leq 0.6V$$

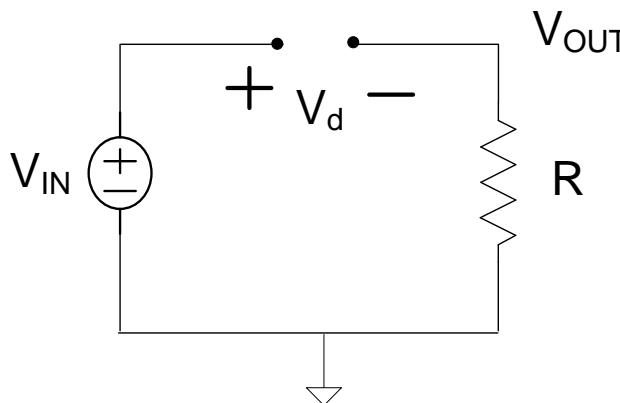

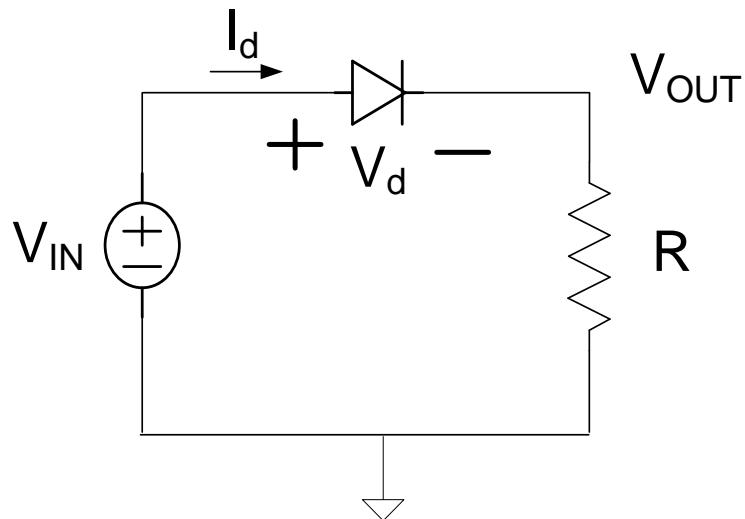Consider again the basic rectifier circuit



Analyze with piecewise linear model

$$\begin{array}{ll} I_d = 0 & V_d < 0.6V \\ V_d = 0.6V & I_d > 0 \end{array}$$


Case 2 $V_d = 0.6V$

$$V_{OUT} = V_{IN} - 0.6V$$


valid for $I_d > 0$

$$\text{but } I_d = \frac{V_{IN} - 0.6V}{R}$$

\therefore valid for $V_{IN} > 0.6V$

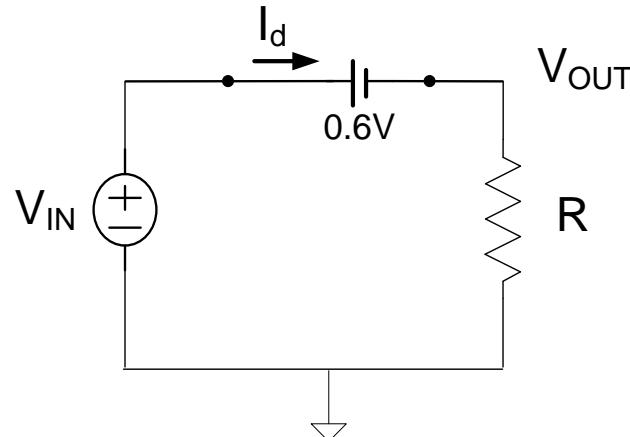

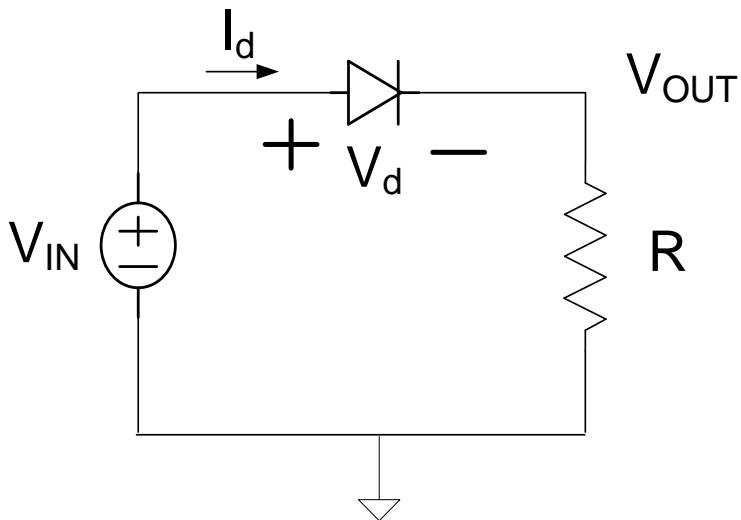Consider again the basic rectifier circuit




Analyze with piecewise linear model


$$\begin{array}{ll} I_d = 0 & V_d < 0.6V \\ V_d = 0.6V & I_d > 0 \end{array}$$

Solution summary:




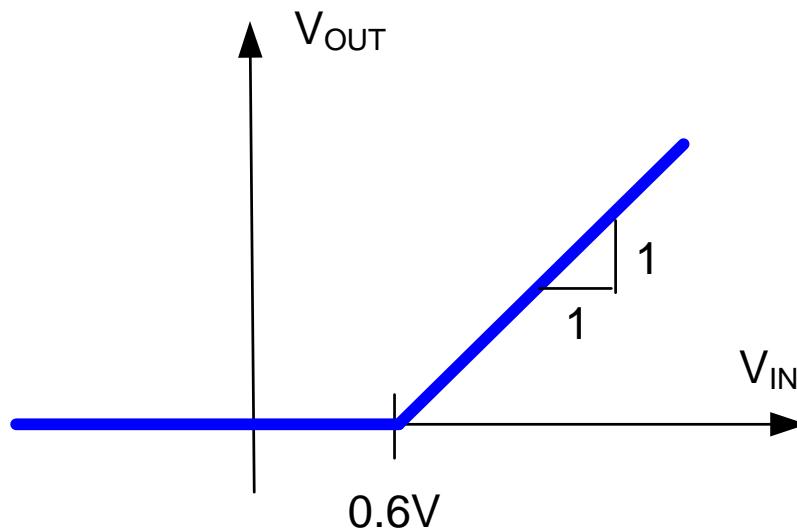
$$V_{OUT} = \begin{cases} 0 & V_{IN} \leq 0.6V \\ V_{IN} - 0.6V & V_{IN} > 0.6V \end{cases}$$



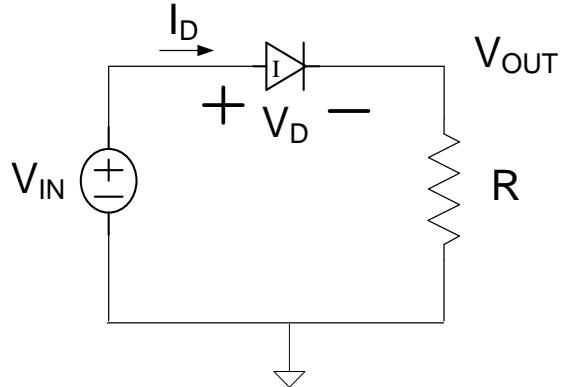
Performance Limitations of Diode Rectifier Circuit




Diode rectifier circuit

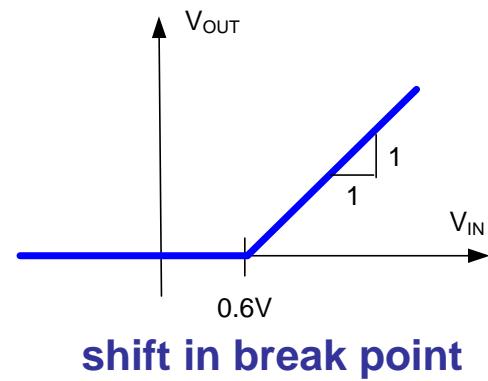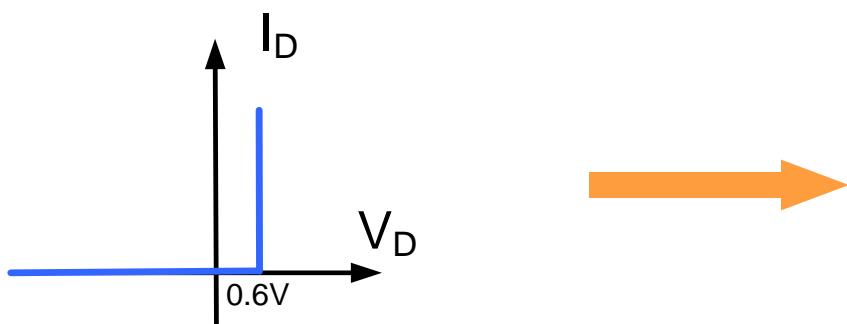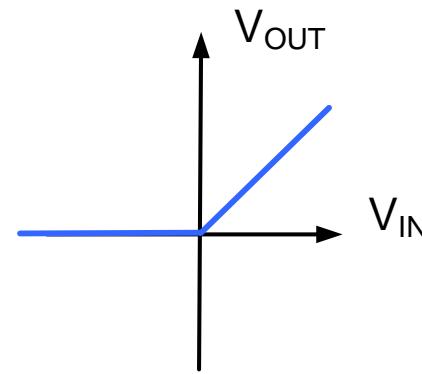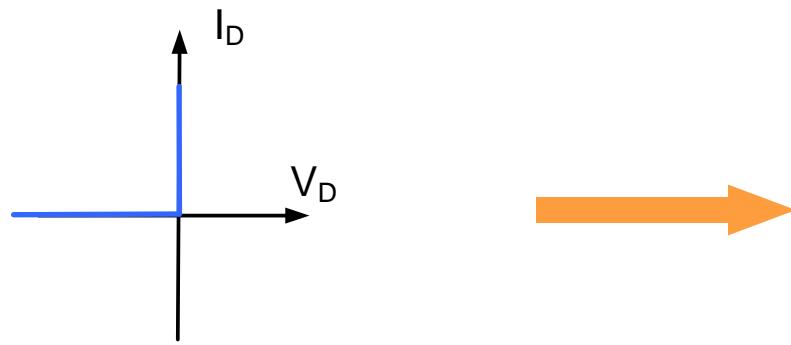

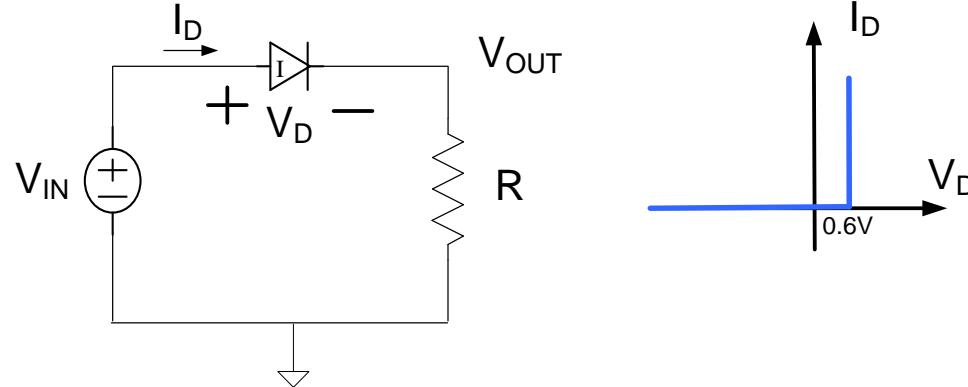Performance Limitations of Diode Rectifier Circuit




Diode rectifier circuit

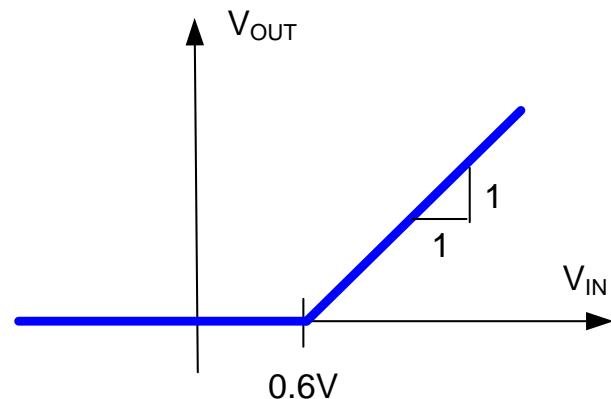

$$V_{OUT} = \begin{cases} 0 & V_{IN} \leq 0.6V \\ V_{IN} - 0.6V & V_{IN} > 0.6V \end{cases}$$

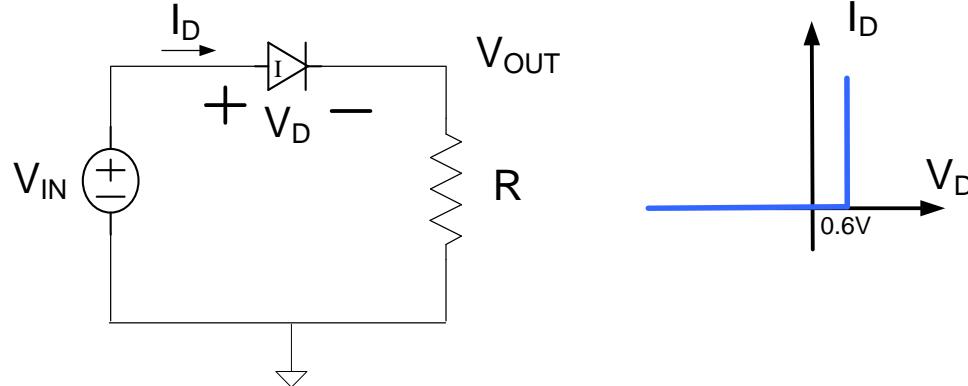Performance Limitations of Diode Rectifier Circuit





Diode rectifier circuit



$$V_{OUT} = \begin{cases} 0 & V_{IN} \leq 0.6V \\ V_{IN} - 0.6V & V_{IN} > 0.6V \end{cases}$$

Consider $V_{IN}=V_M \sin \omega t$ for $V_M=50V$, $V_M=1V$ and $V_M=0.5V$


Desired output:

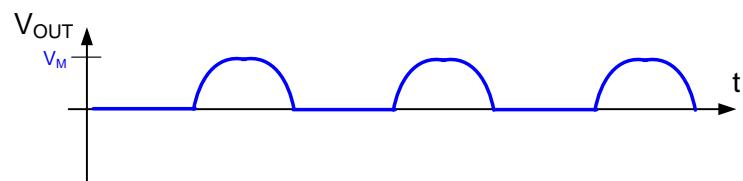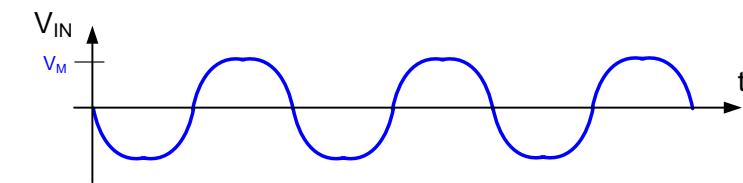

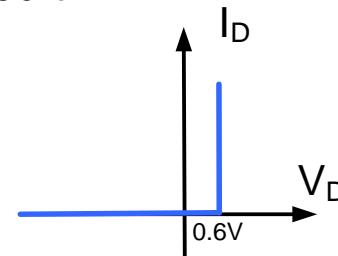
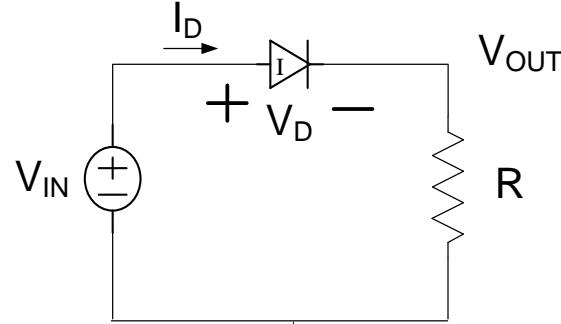
Performance Limitations of Diode Rectifier Circuit




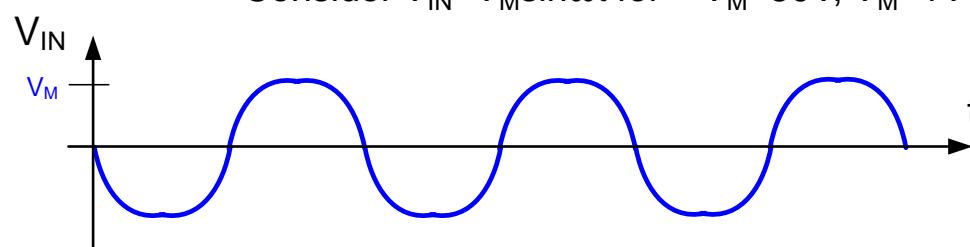
Consider $V_{IN}=V_M \sin \omega t$ for $V_M=50V$, $V_M=1V$ and $V_M=0.5V$




Desired output:

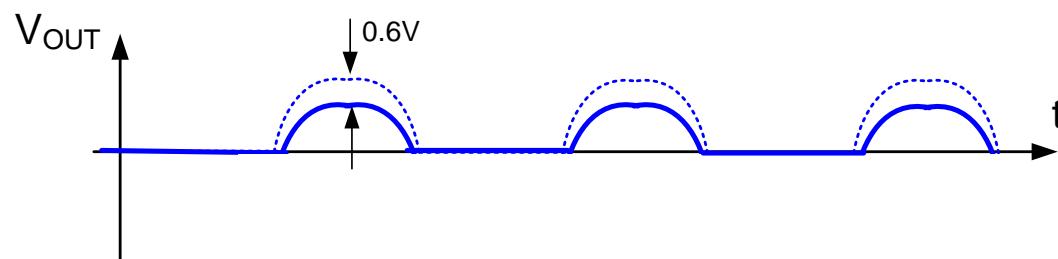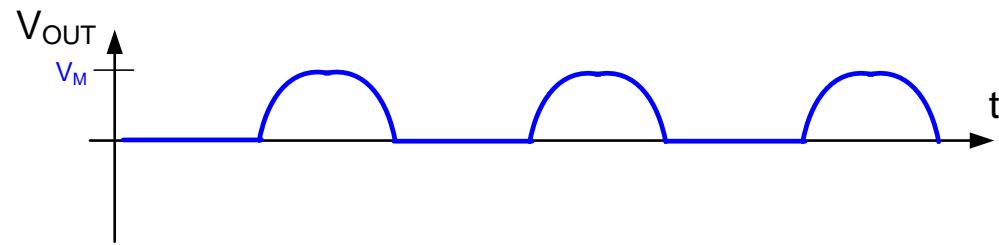

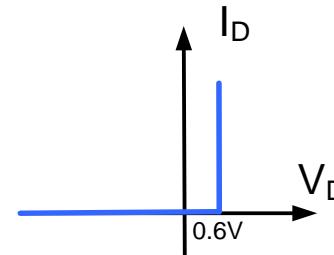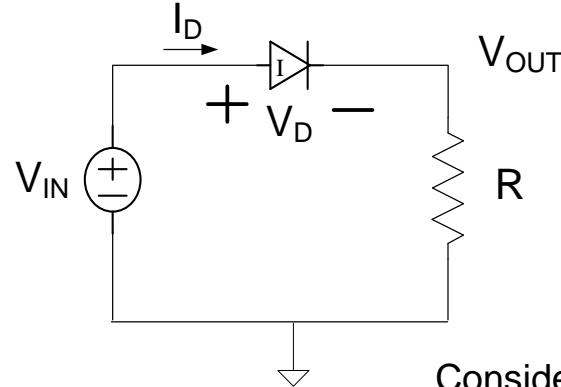Performance Limitations of Diode Rectifier Circuit




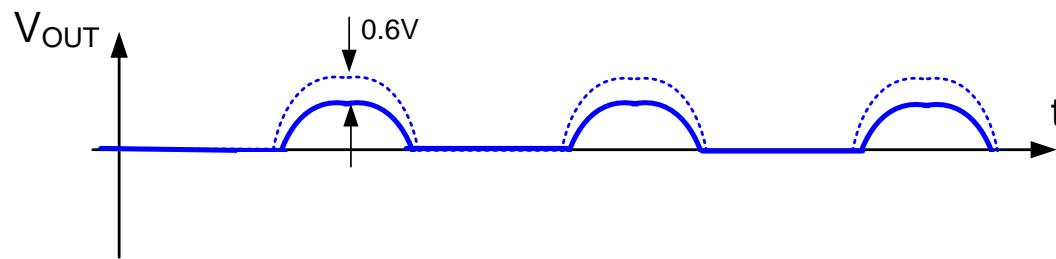Consider $V_{IN}=V_M \sin \omega t$ for $V_M=50V$, $V_M=1V$ and $V_M=0.5V$





If $V_M=50V$, the 0.6V drop causes very little degradation in performance

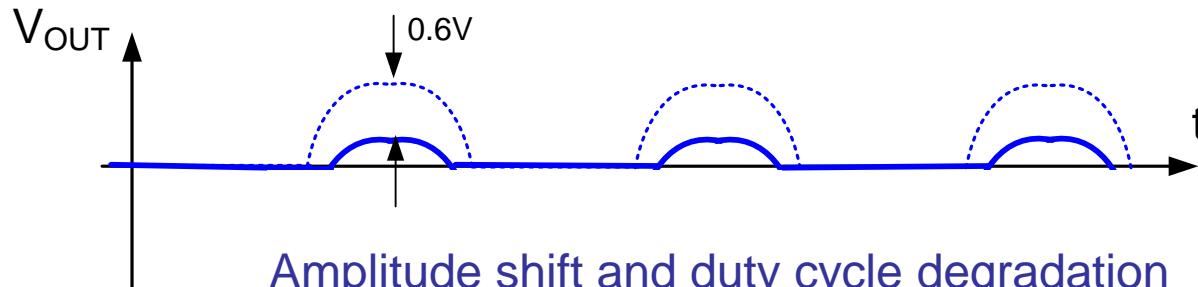
If $V_M=1V$, the 0.6V drop causes dramatic degradation in performance



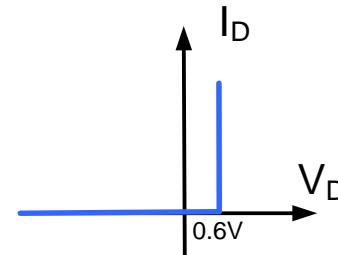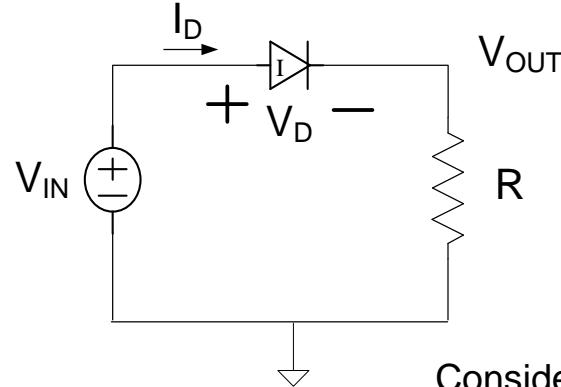
Performance Limitations of Diode Rectifier Circuit



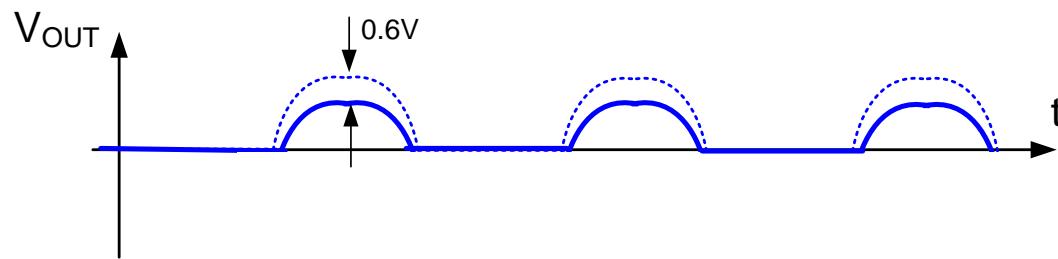Consider $V_{IN} = V_M \sin \omega t$ for $V_M = 50V$, $V_M = 1V$ and $V_M = 0.5V$





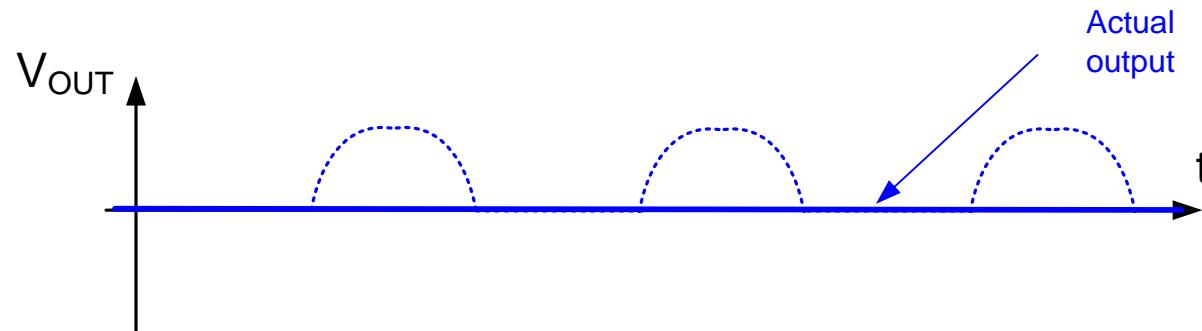If $V_M = 0.5V$, the 0.6V drop provides no output !



Precision Rectifier Circuit

(with nonideal diode)

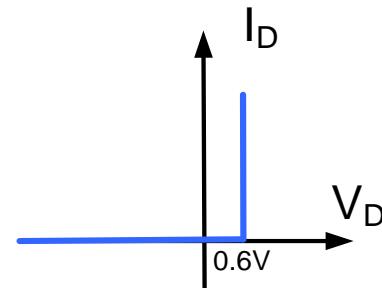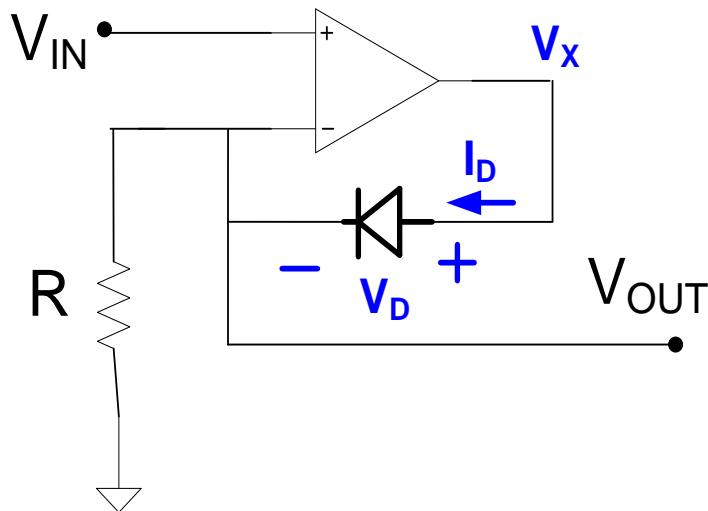

$$\begin{array}{ll} I_D = 0 & V_D < 0.6V \\ V_D = 0.6V & I_D > 0 \end{array}$$

Case 1 D_1 Conducting, Op Amp operating linearly

$$V_{OUT} = V_{IN}$$

Valid for $I_D > 0$ and

$$V_{SATL} < V_X < V_{SATH}$$

$$I_D = V_{IN}/R$$

$$V_X = V_{OUT} + 0.6V$$

$I_D > 0$ when $V_{IN} > 0$



and

$$V_{SATL} - 0.6 < V_{IN} < V_{SATH} - 0.6$$

$$0 < V_{IN} < V_{SATH} - 0.6$$

Precision Rectifier Circuit

(with nonideal diode)

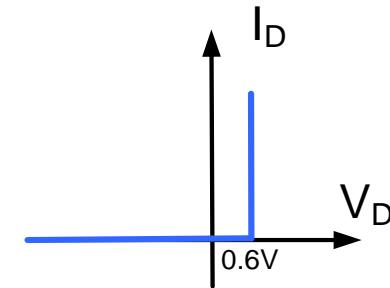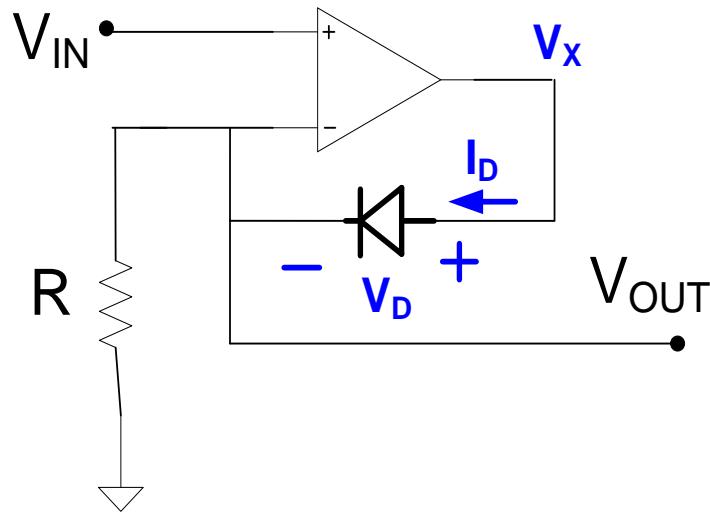


$$\begin{array}{ll} I_D = 0 & V_D < 0.6V \\ V_D = 0.6V & I_D > 0 \end{array}$$

Case 1 D₁ Conducting, Op Amp operating linearly



$$V_{OUT} = V_{IN}$$

$$0 < V_{IN} < V_{SATH} - 0.6$$

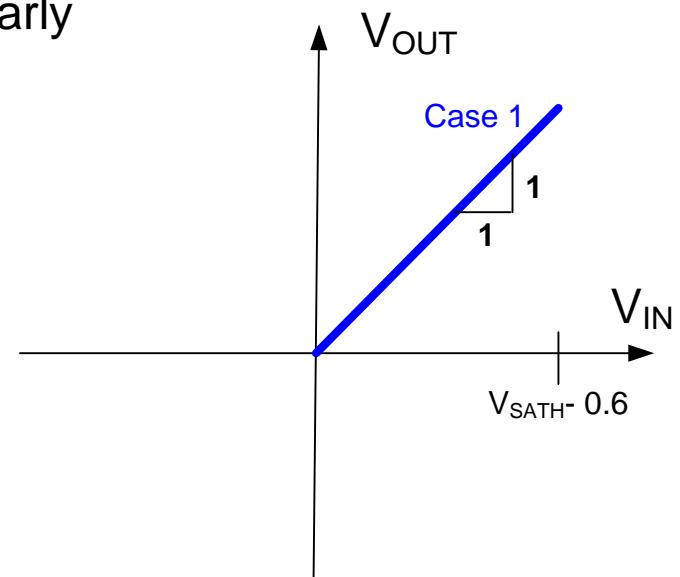

Precision Rectifier Circuit

(with nonideal diode)

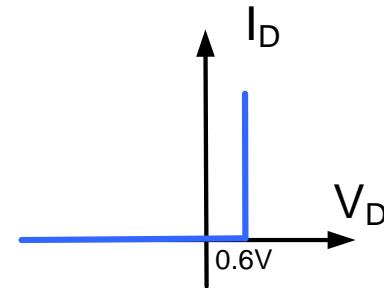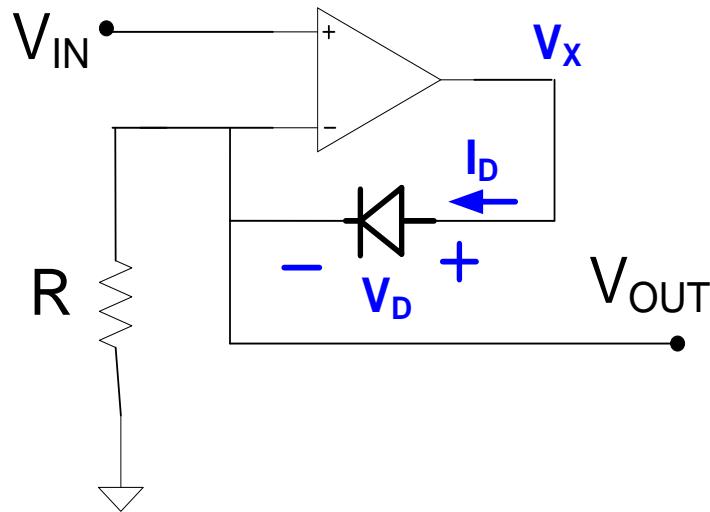

$$I_D = 0 \quad V_D < 0.6V$$

$$V_D = 0.6V \quad I_D > 0$$

Case 2 D_1 Not Conducting, Op Amp saturated low

$$V_{OUT} = 0 \quad (\text{since no current flowing through } R)$$

Valid for $V_D < 0.6V$

and

$V^+ < V^-$

$$V_X = V_{SATL}$$

$$V_{IN} < V_{OUT}$$

$$V_D = V_X - 0$$



$$V_{SATL} < 0.6V$$

and

$$V_{IN} < 0$$

Precision Rectifier Circuit

(with nonideal diode)

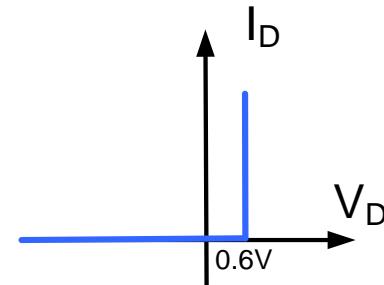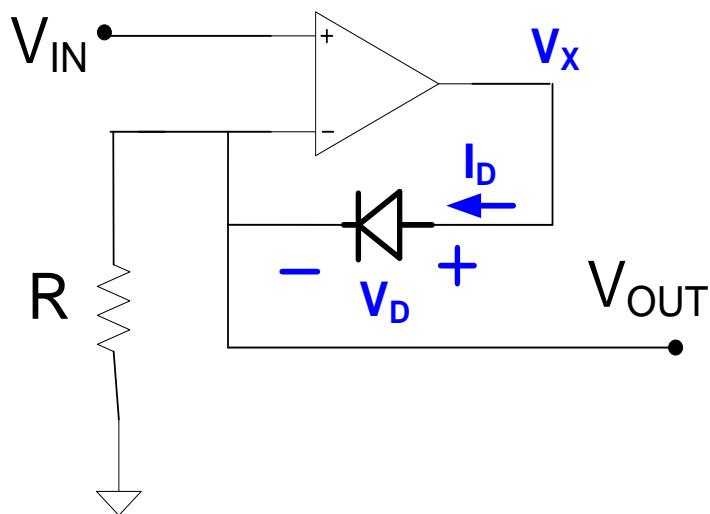



$$\begin{array}{ll} I_D = 0 & V_D < 0.6V \\ V_D = 0.6V & I_D > 0 \end{array}$$

Case 2 D_1 Not Conducting, Op Amp saturated low

$$V_{\text{OUT}} = 0$$



valid for

$$V_{\text{IN}} < 0$$

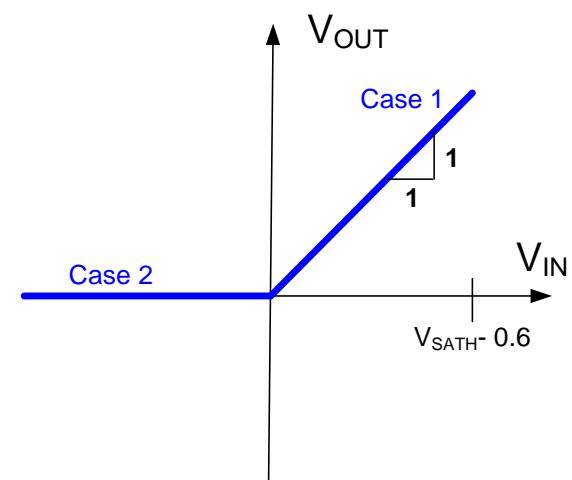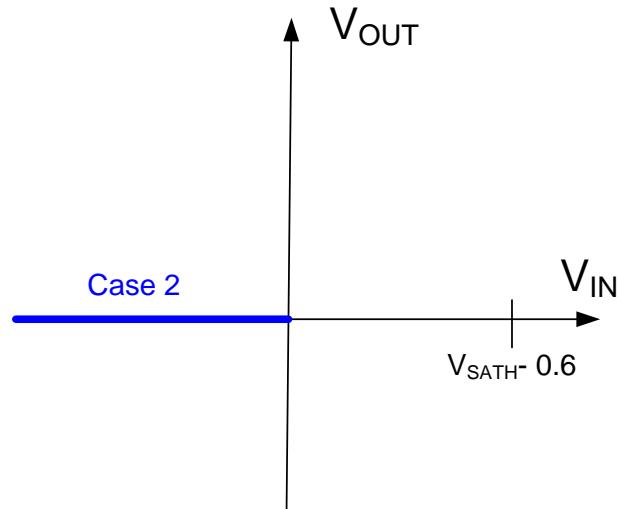


Precision Rectifier Circuit

(with nonideal diode)

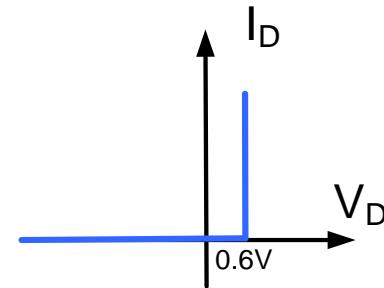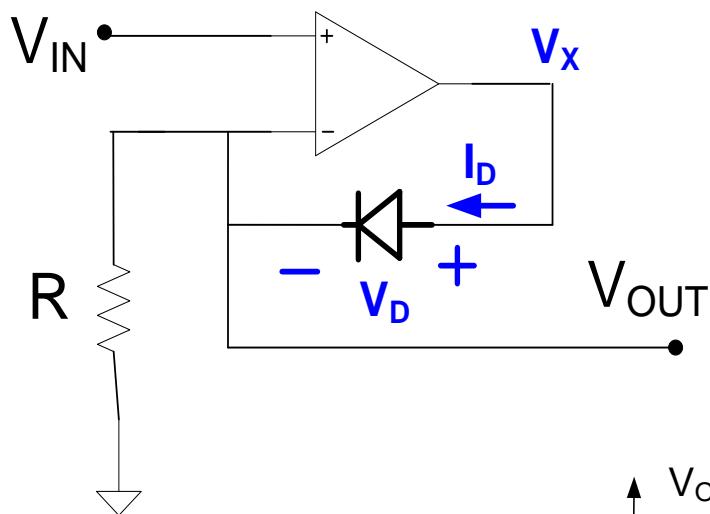
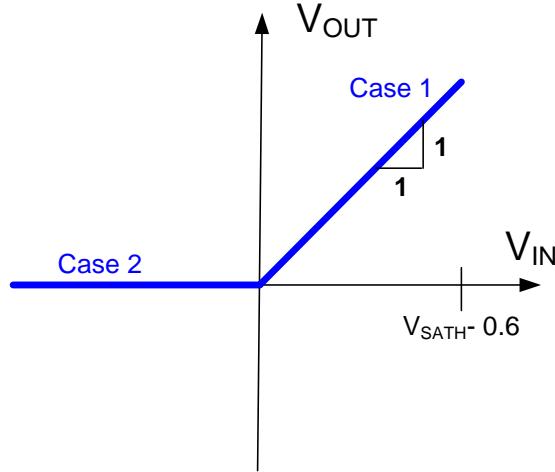
$$\begin{array}{ll} I_D = 0 & V_D < 0.6V \\ V_D = 0.6V & I_D > 0 \end{array}$$




This is the transfer characteristics of an ideal rectifier!




Can be used to rectify very small signals !

Need a buffer on V_{OUT} if any current is to be provided to a load !

Consider this circuit


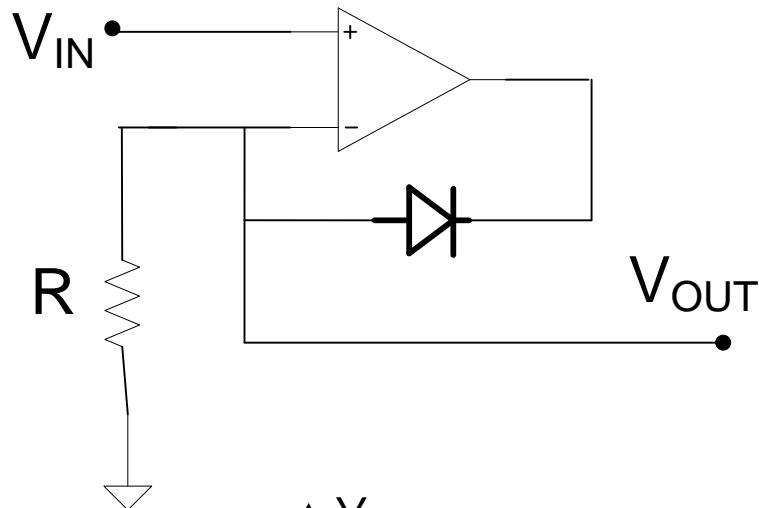


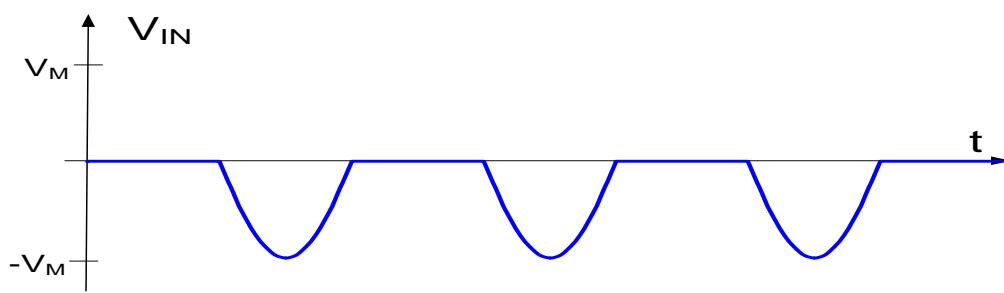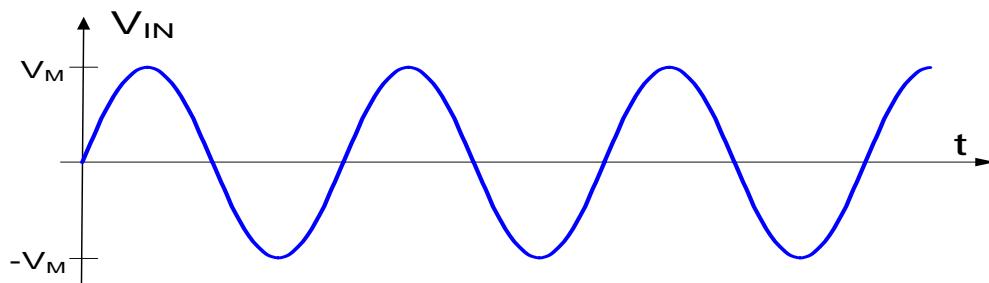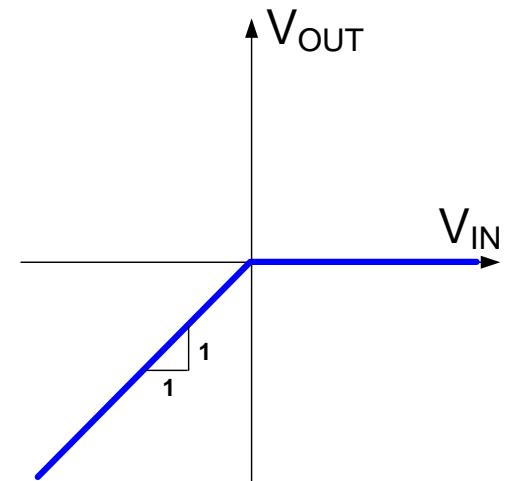Following an almost identical analysis, can show





This serves as a precision negative rectifier (not inverting rectifier)

Consider this circuit




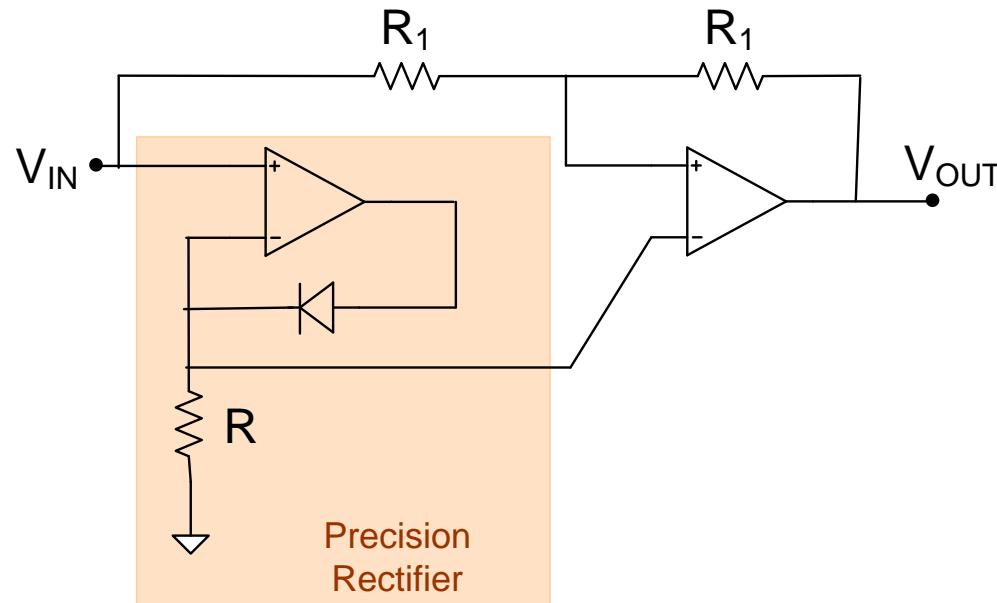
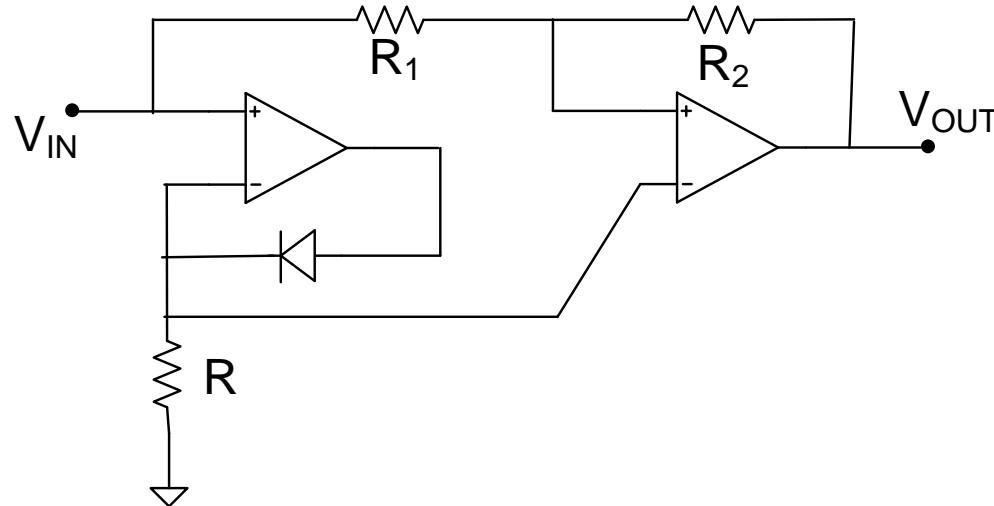


Consider this circuit

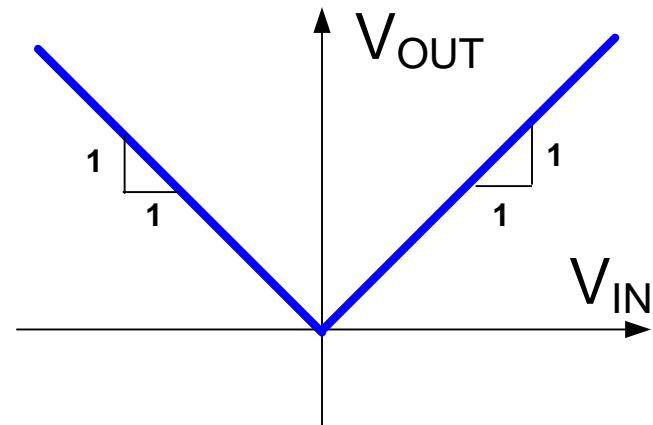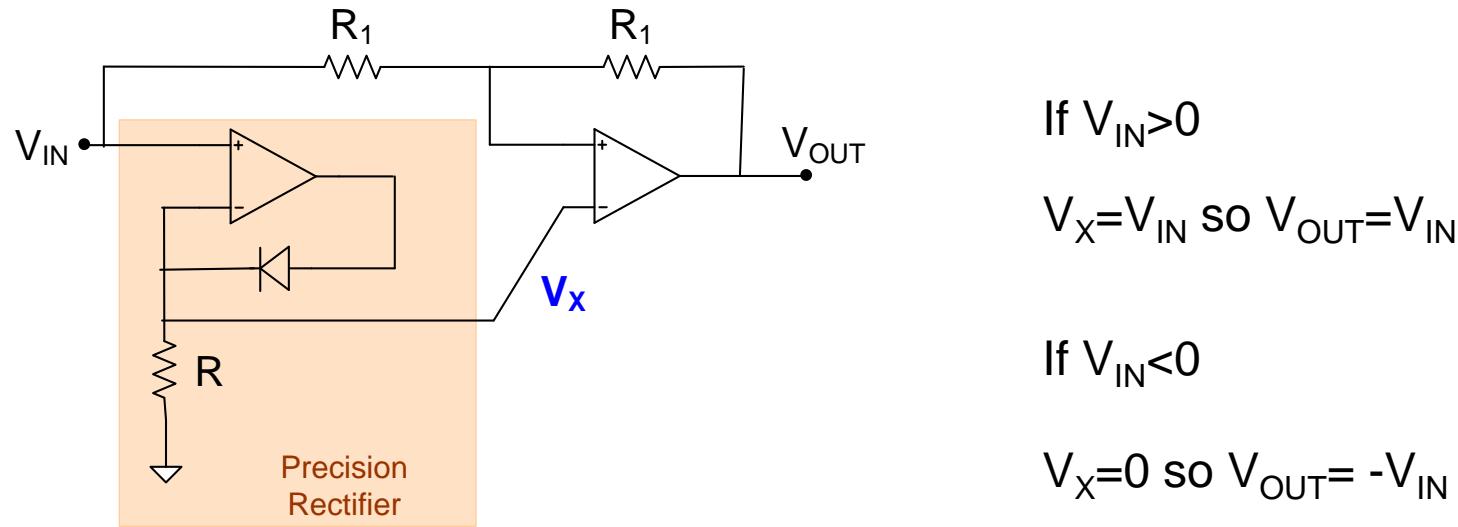


This is a precision full-wave rectifier
(rectifies positive signals, inverts and rectifies negative signals)

Precision Full-Wave Rectifier

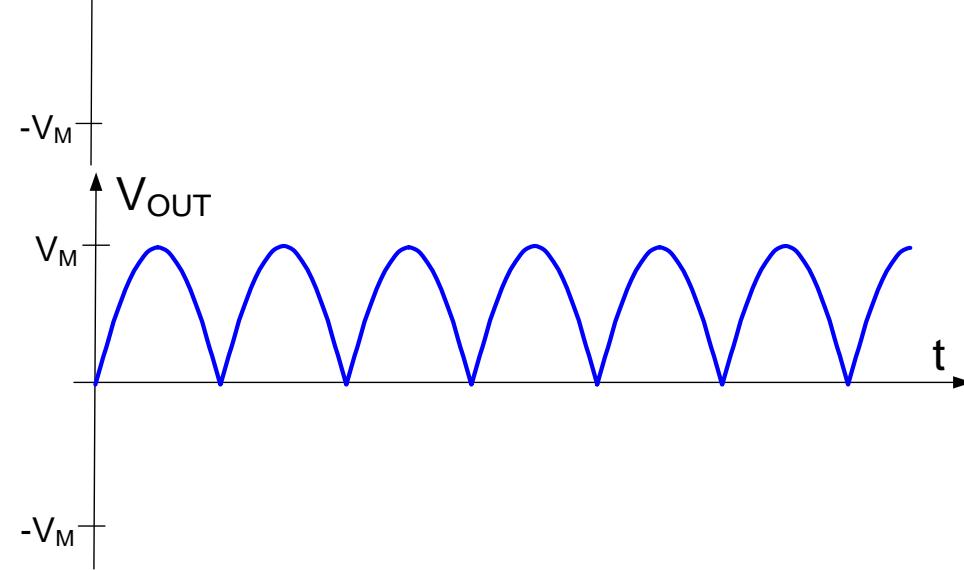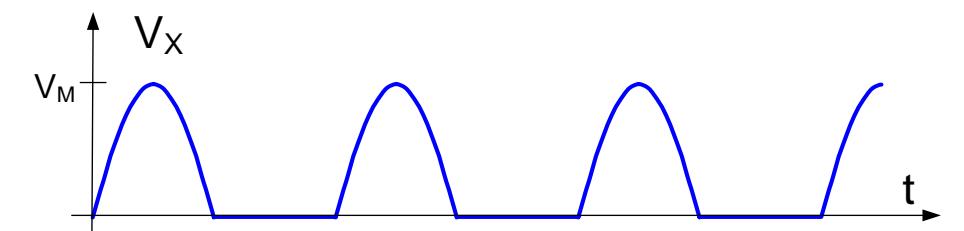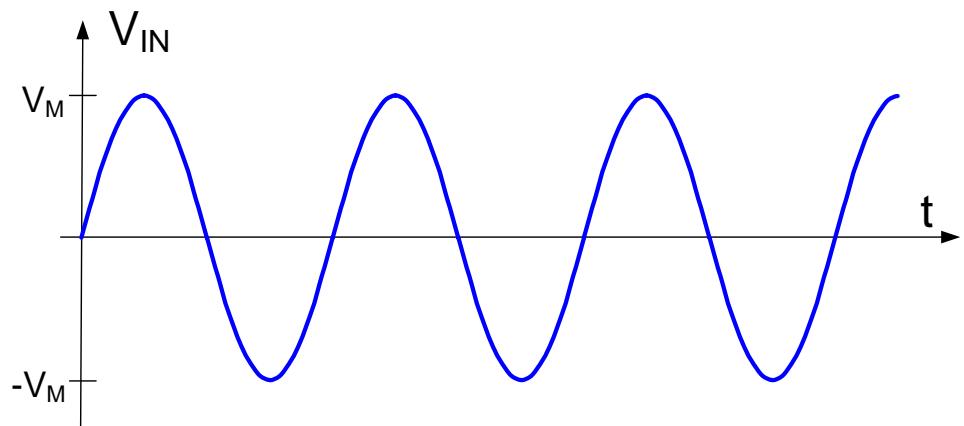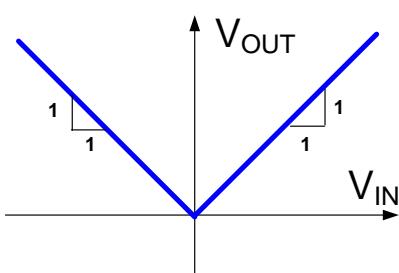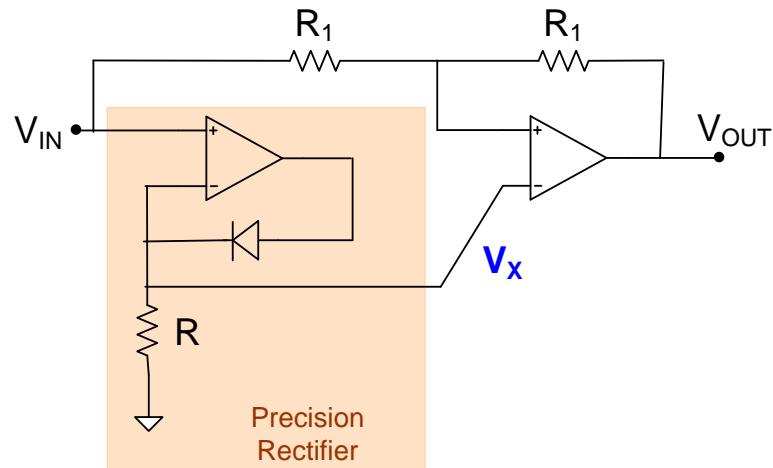


Consider this circuit

(assume diode is ideal)

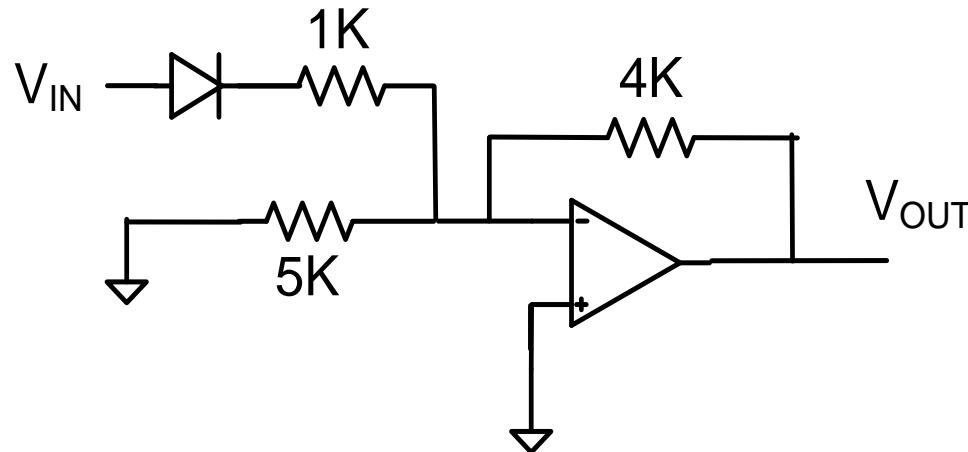

If diode is OFF, $V_{OUT}=0$


If diode is ON, $V_{OUT} = -10V_{IN}$

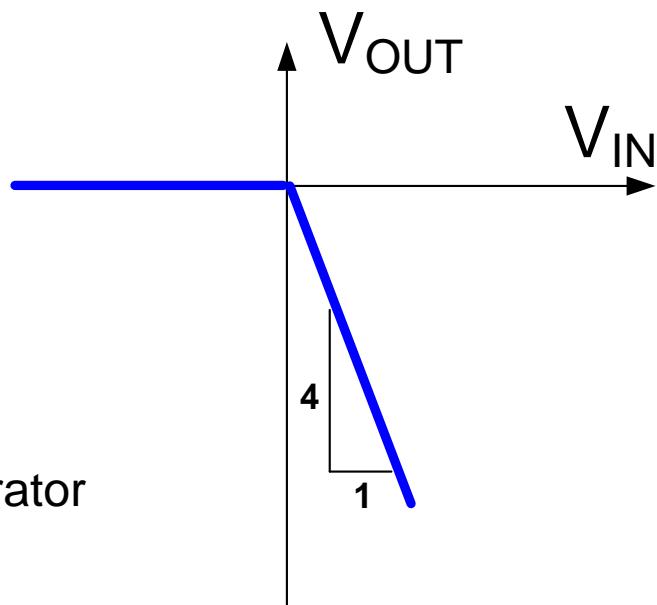

- Serves as a two-segment function generator
- But no control of the first slope

Consider this circuit

(assume diodes are ideal)

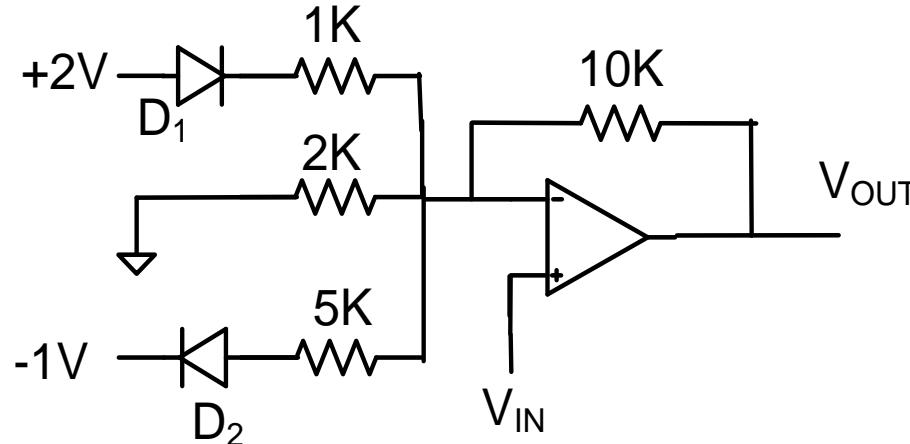

If $V_{IN} < -1V$, D₁ ON, D₂ OFF

$$V_{OUT} = V_{IN} \left(1 + \frac{10K}{1K/2K} \right) + 2 \left(-\frac{10K}{1K} \right)$$

$$V_{OUT} = V_{IN} \ 16 \ -20$$

If $2V > V_{IN} > -1V$, D₁ ON, D₂ ON

$$V_{OUT} = V_{IN} \left(1 + \frac{10K}{1K/2K/5K} \right) + 2 \left(-\frac{10K}{1K} \right) - 1V \left(-\frac{10K}{5K} \right)$$

$$V_{OUT} = V_{IN} \ 18 \ -18$$


If $V_{IN} > 2V$, D₁ OFF, D₂ ON

$$V_{OUT} = V_{IN} \left(1 + \frac{10K}{2K/5K} \right) + -1V \left(-\frac{10K}{5K} \right)$$


$$V_{OUT} = V_{IN} \ 8 \ +2$$

Consider this circuit

(assume diodes are ideal)

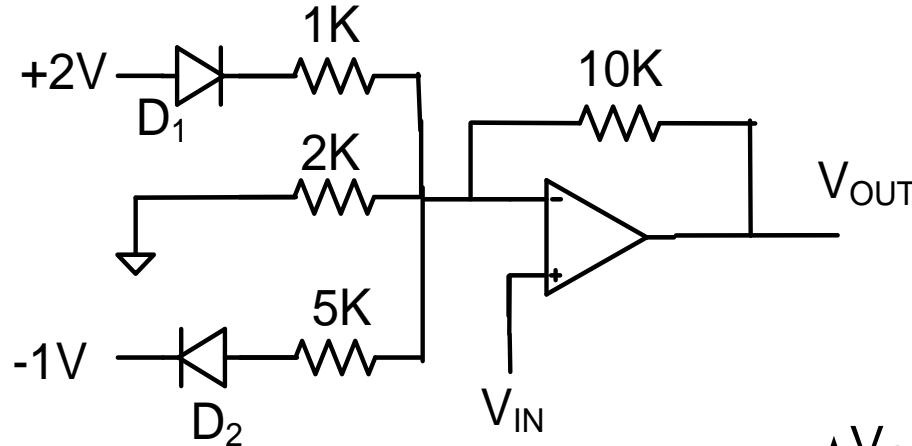

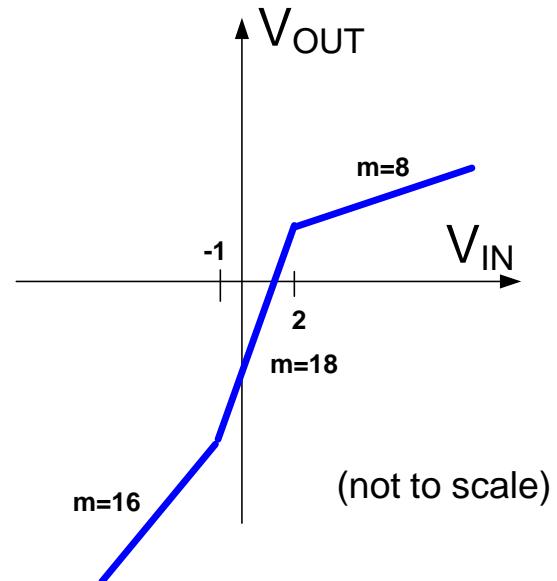
$$V_{\text{OUT}} = \begin{cases} 16V_{\text{IN}} - 20 & V_{\text{IN}} < -1 \\ 18V_{\text{IN}} - 18 & -1 < V_{\text{IN}} < 2 \\ 8V_{\text{IN}} + 2 & V_{\text{IN}} > 2 \end{cases}$$



This is a nonlinear function generator

Nonlinear Function Generator


(assume diodes are ideal)

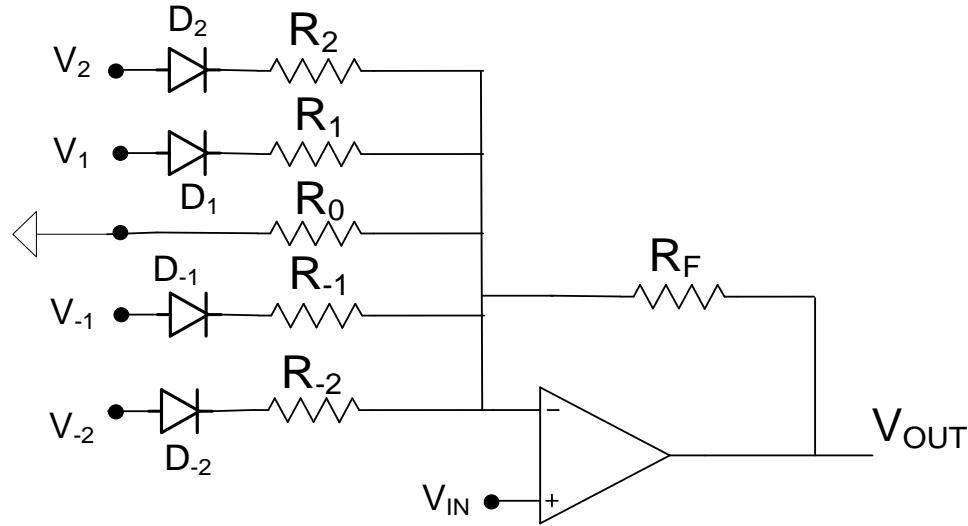

Assume $V_2 > V_1 > V_{-1} > V_{-2}$

- Provides a 5-segment nonlinear function generator
- Analysis straightforward but tedious
- Diode function generators like this can be used to convert a triangle wave to a very good sine wave
- Performance actually usually better with actual diodes since transition between regions is smoother


Generalized Nonlinear Function Generator

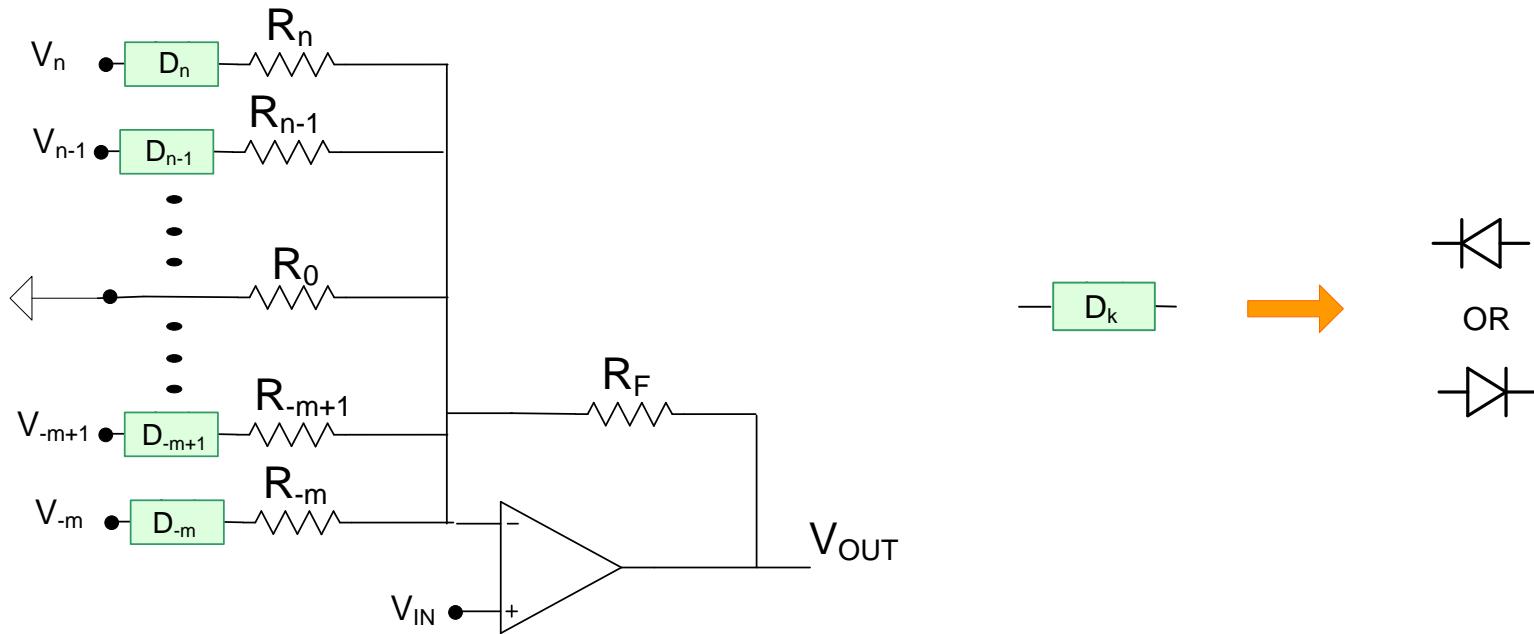

Assume $V_n > V_{n-1} > \dots > V_1 > 0 > V_{-1} > \dots > V_{-m}$

- Provides $m+n+1$ segment nonlinear function
- Slopes are always positive and greater than 1
- Can generate arbitrary nonlinear transfer characteristic
- Actually works better with nonideal diodes
- Can be extended to provide slopes less than 1
- Can be further extended to provide slopes of arbitrary sign and arbitrary magnitude

Generalized Nonlinear Function Generator

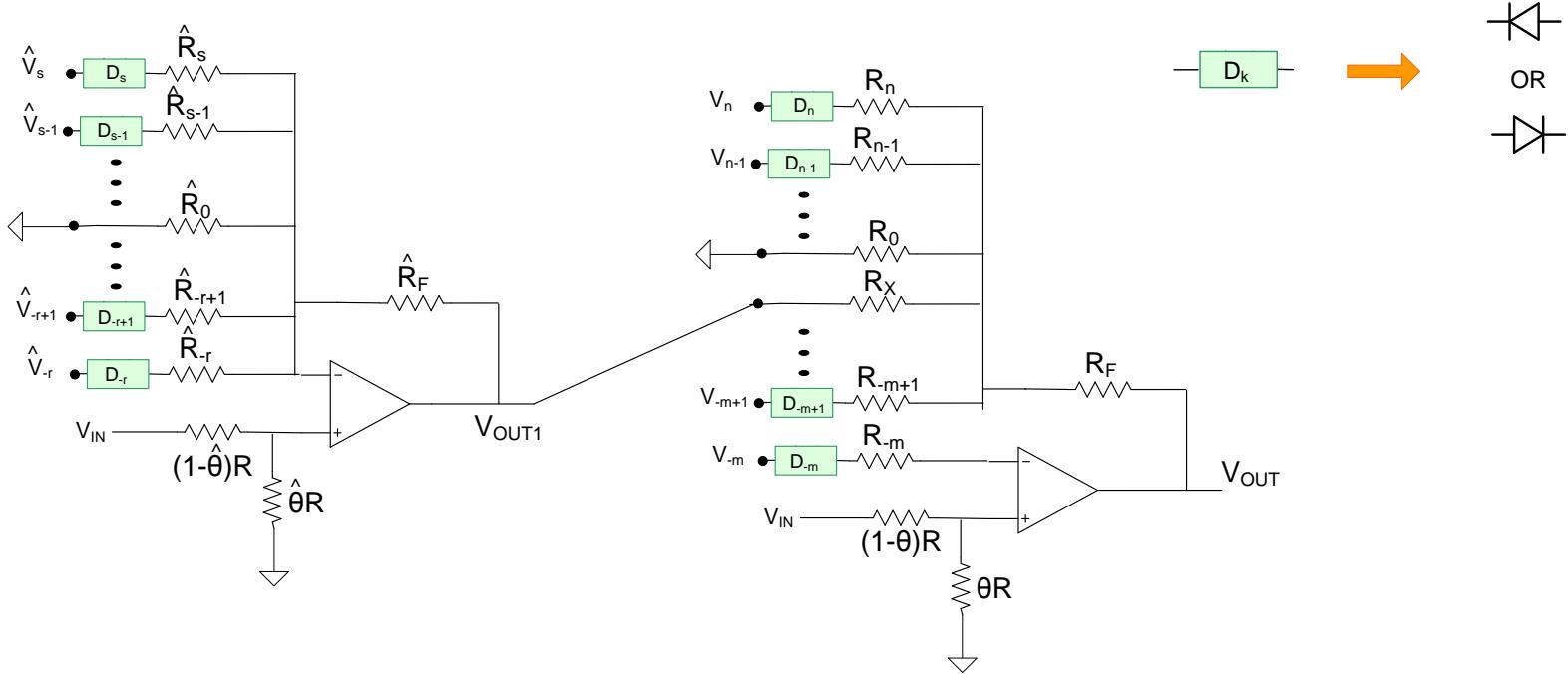

- Provides $m+n+r+s+2$ segment nonlinear function
- Slopes can be positive or negative of any magnitude
- Analysis and design tedious but straight forward

End of Lecture 28