

EE 230


Lecture 29

Nonlinear Circuits and Nonlinear Devices

- Diode
- BJT
- MOSFET

Quiz 19

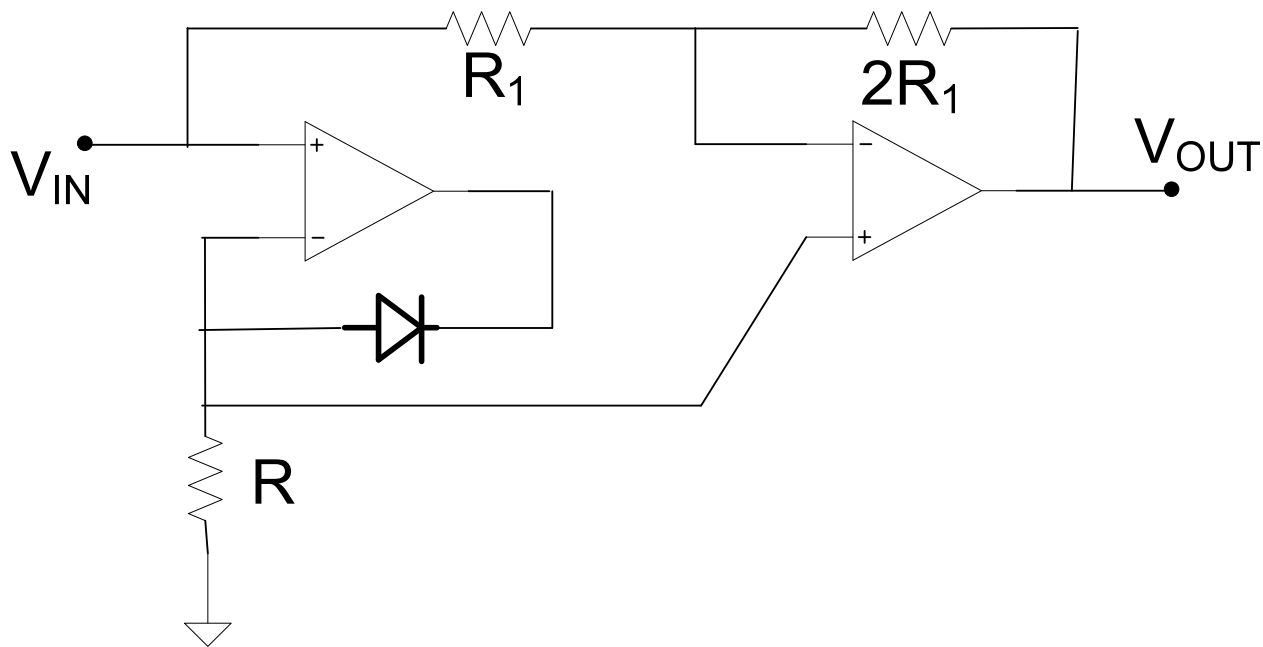Obtain the transfer characteristics of the following circuit and plot the output if $V_{IN} = -5\sin\omega t$. Assume the diode is ideal.



And the number is ?

1

3

8

5

4

2

6

9

7

And the number is ?

1

3

8

5

4

2

3


6

9

7

Quiz 19

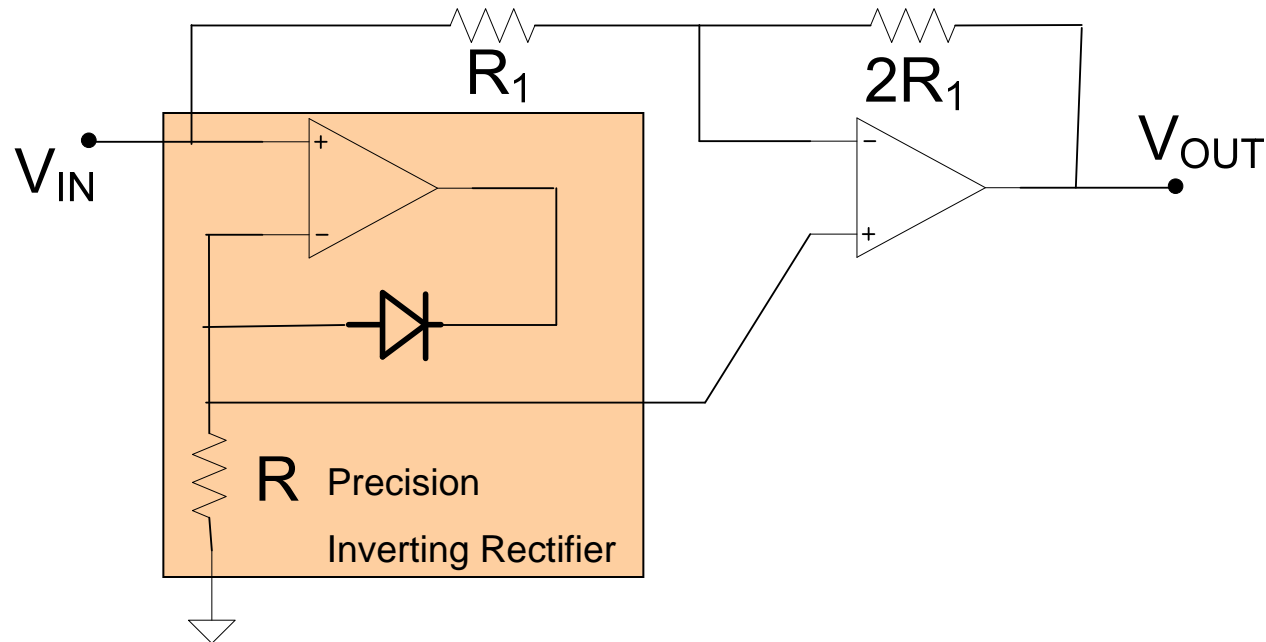Obtain the transfer characteristics of the following circuit and plot the output if $V_{IN}=5\sin\omega t$. Assume the diode is ideal.



Solution:

Observe D_1 is **ON** for $V_{IN} < 0$ and **OFF** for $V_{IN} > 0$

$$\therefore \text{ for } V_{IN} > 0, V_{OUT} = -2V_{IN}$$

$$\text{ for } V_{IN} \leq 0, V_{OUT} = (1+2)V_{IN} - 2V_{IN} = V_{IN}$$


Quiz 19

Obtain the transfer characteristics of the following circuit and plot the output if $V_{IN}=5\sin\omega t$. Assume the diode is ideal.

Solution:

$$\text{for } V_{IN} > 0, V_{OUT} = -2V_{IN}$$



$$\text{for } V_{IN} \leq 0, V_{OUT} = (1+2)V_{IN} - 2V_{IN} = V_{IN}$$

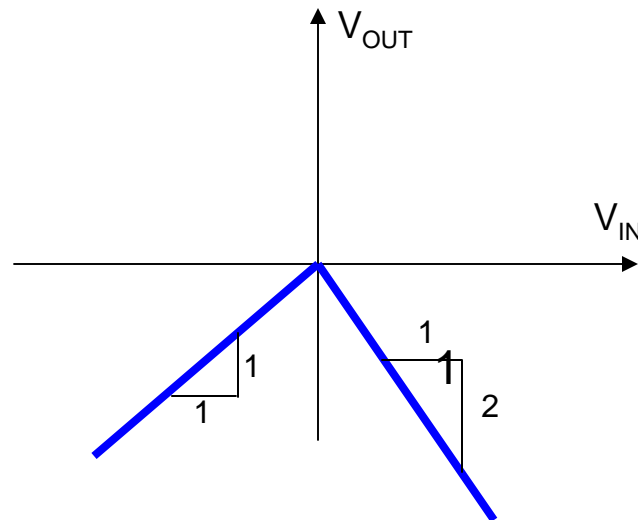

Quiz 19



Obtain the transfer characteristics of the following circuit and plot the output if $V_{IN} = -5\sin\omega t$. Assume the diode is ideal.

Solution:


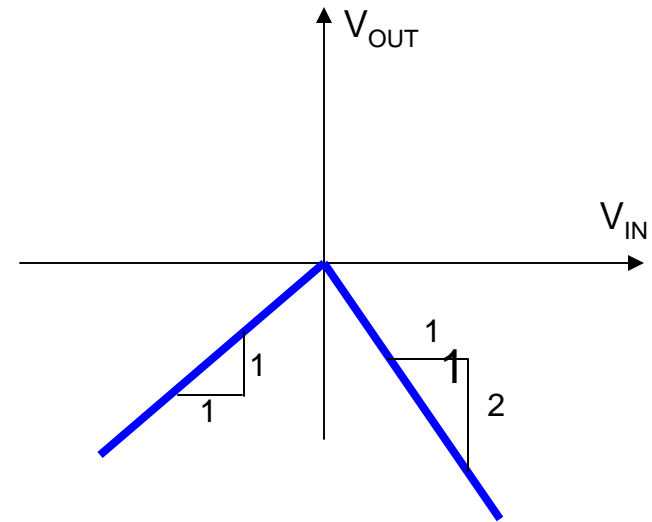
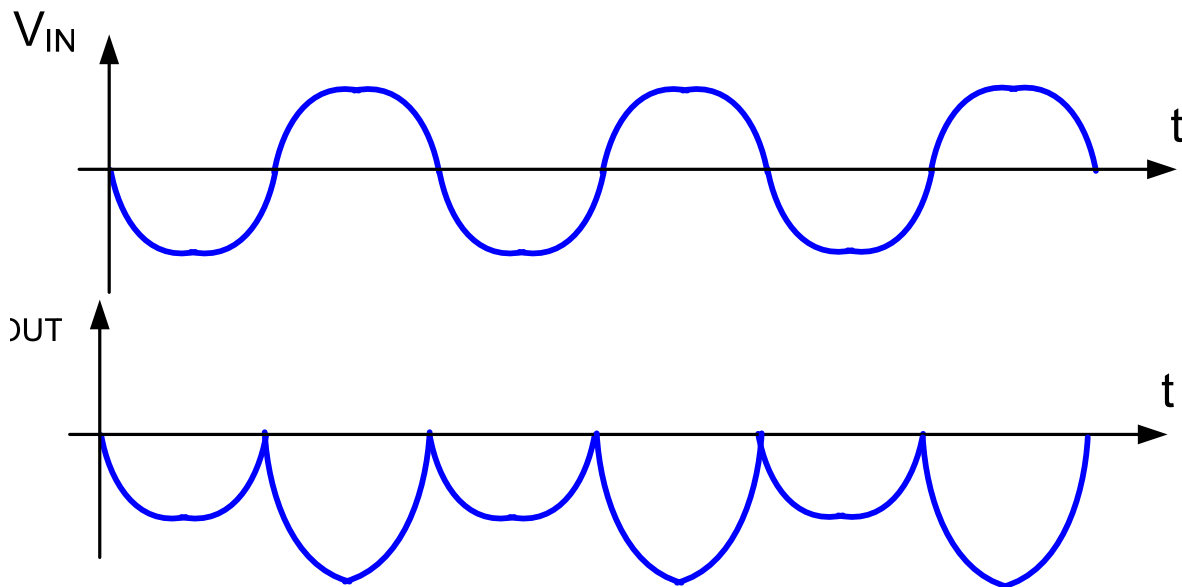


Review from Last Time:

Diode Rectifier Circuit

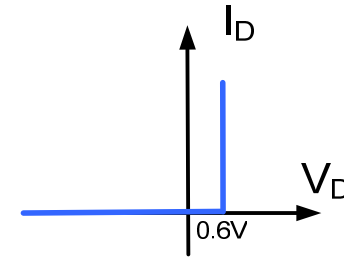
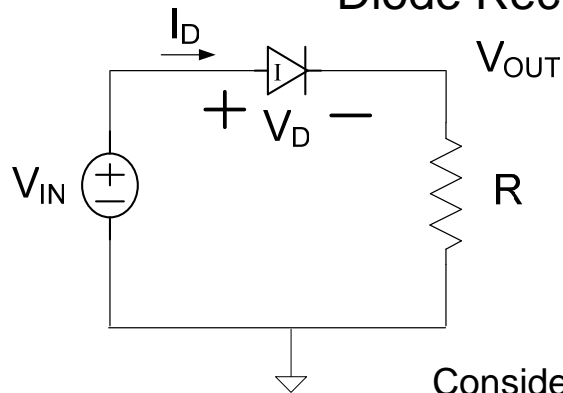


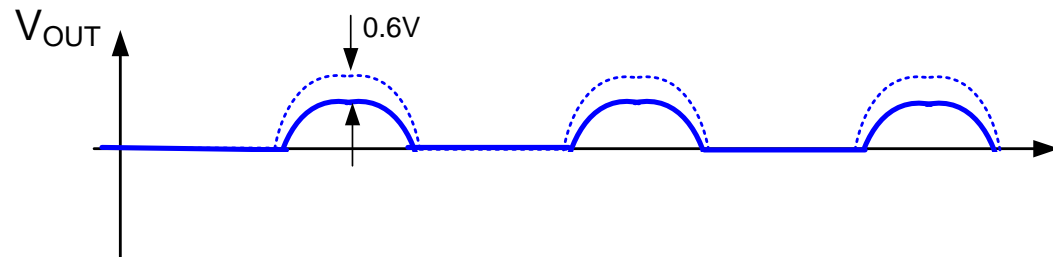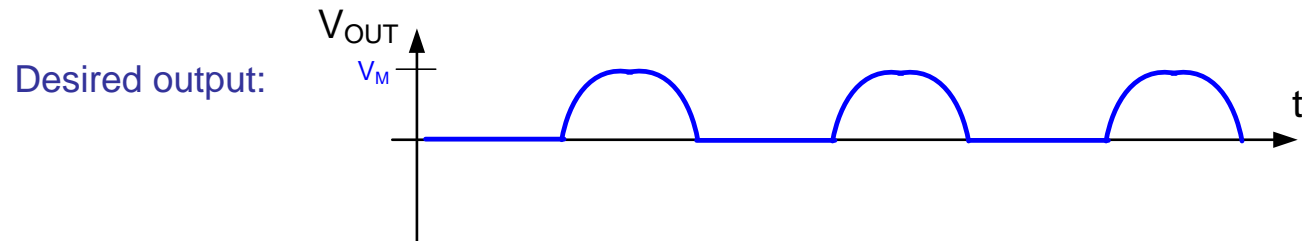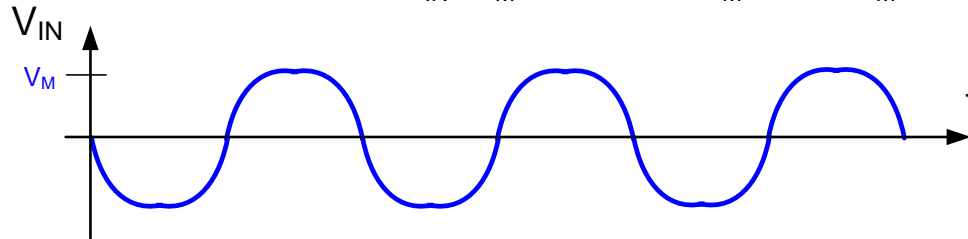Consider $V_{IN} = V_M \sin \omega t$ for $V_M = 50V$, $V_M = 1V$ and $V_M = 0.5V$



Review from Last Time:


Precision Rectifier Circuit

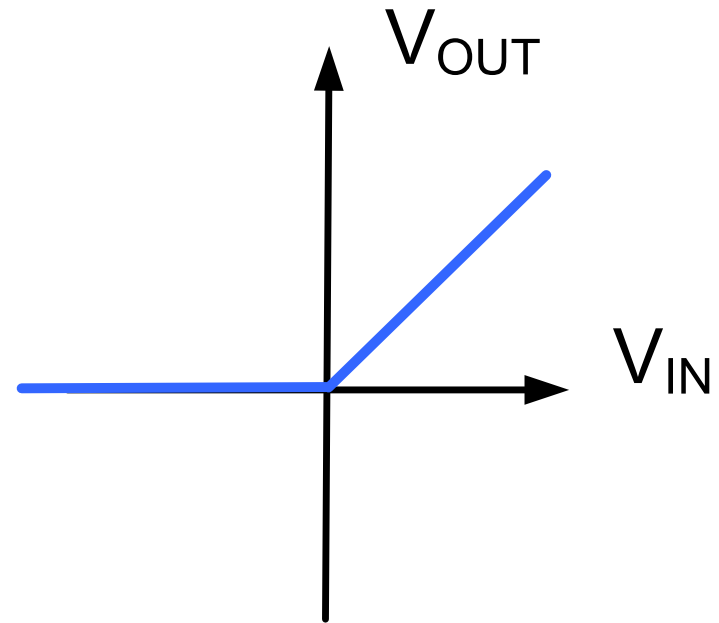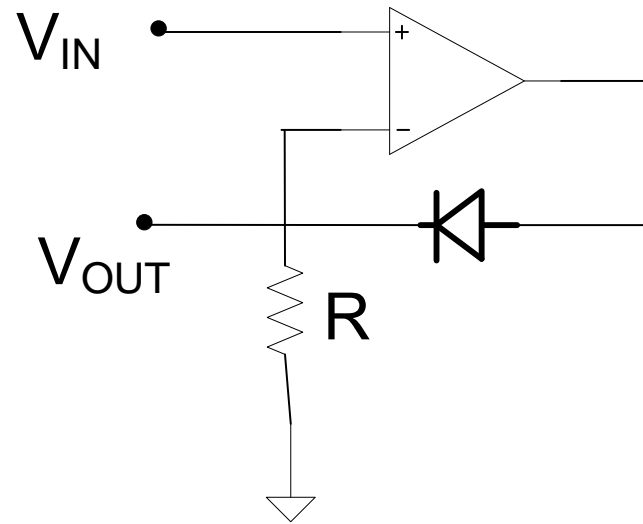

- Buffer may be needed on V_{OUT}
- SR of op amp limits speed of this circuit

Review from Last Time:


Precision Full-Wave Rectifier Circuit

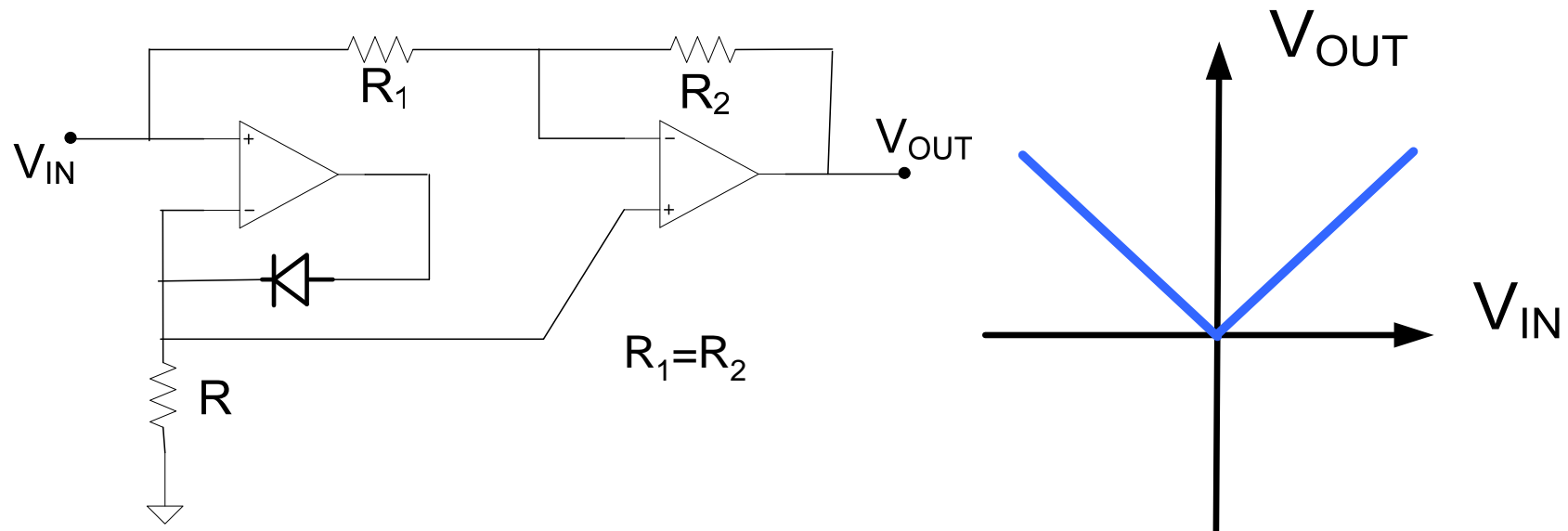

- SR on first op amp limits speed of this circuit


Review from Last Time:

Nonlinear Function Generation

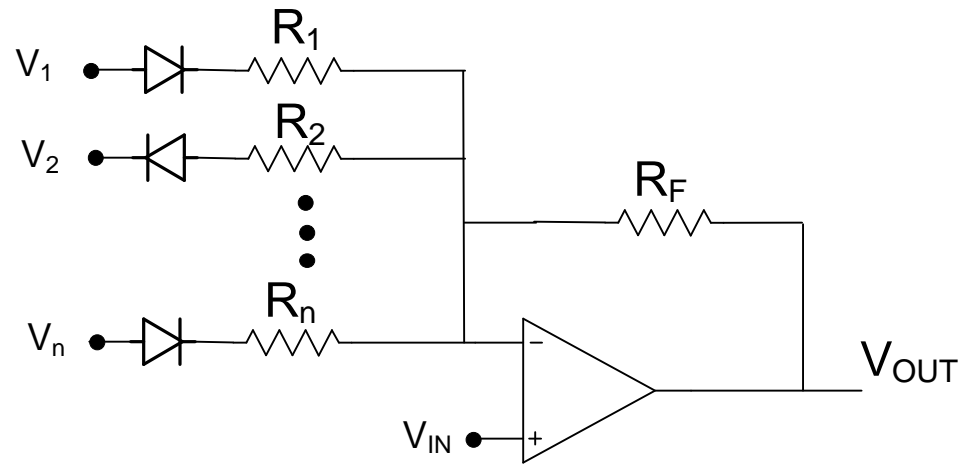


Variants of this approach can be used to generate arbitrary nonlinear functions

Diode Limitations

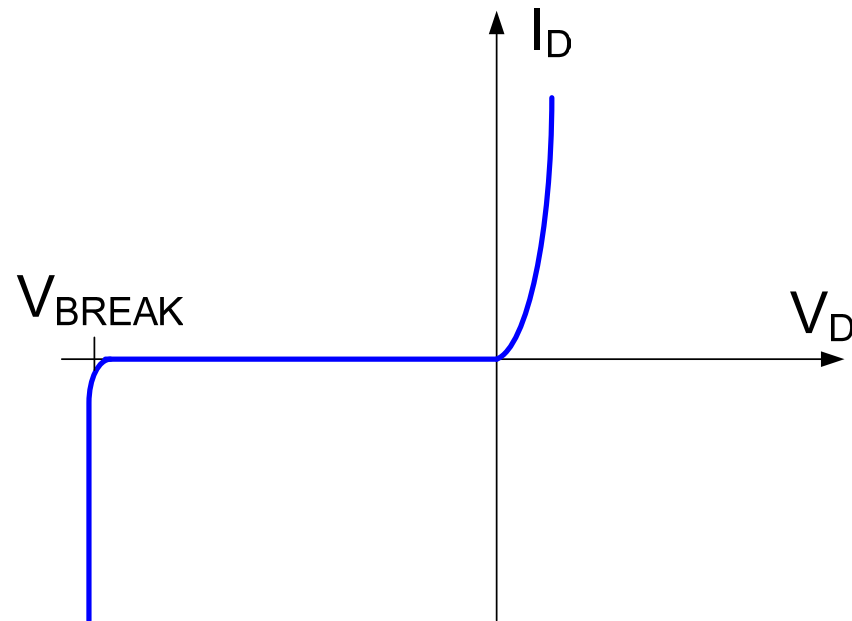


- All diodes will break down if too much reverse bias is applied
- V_{BREAK} can range from a few volts to over 1000V depending upon diode type
- Some are designed to work with modest breakdown voltages (zener diodes)
- Most are not and will be destroyed if allowed to breakdown due to excessive power dissipation


MOS Transistors

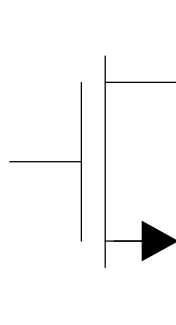

MOSFET

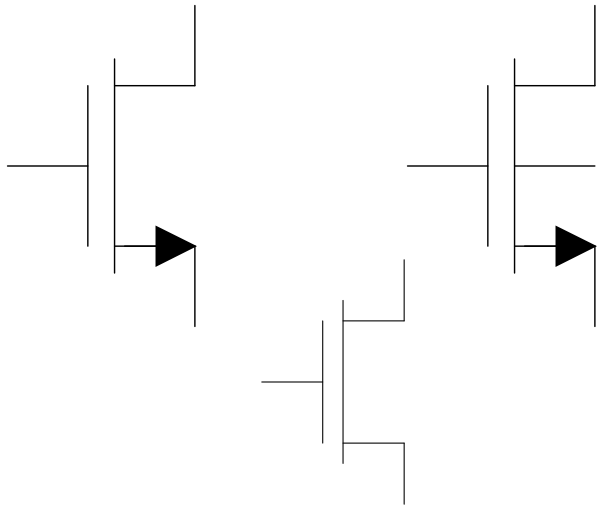


n-channel

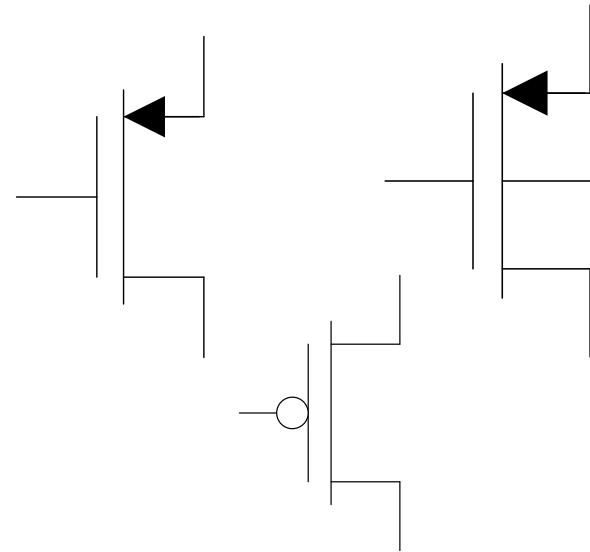


p-channel

MOS Transistors

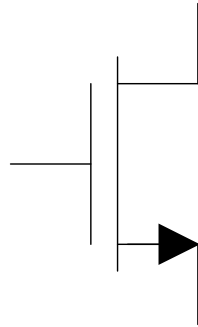



n-channel

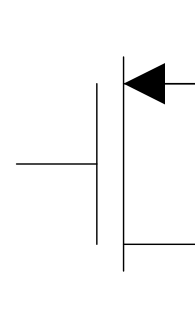

p-channel

- Operation very similar
- Model parameters differ modestly
- Direction of current flow differs


MOS Transistors

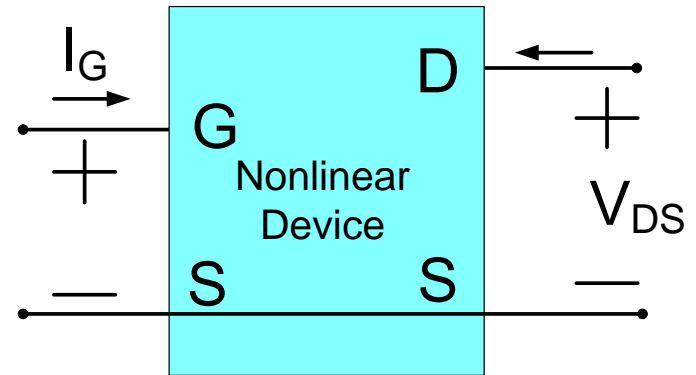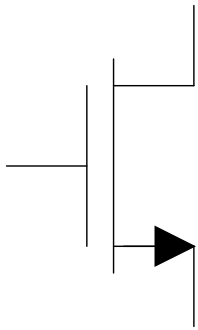

$$I_G = 0$$

$$I_D = \begin{cases} 0 & V_{GS} < 1V \\ 10^{-4} \left(V_{GS} - 1 - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} > 1V, \quad V_{DS} < V_{GS} - 1V \\ \frac{10^{-4}}{2} (V_{GS} - 1)^2 & V_{GS} > 1V, \quad V_{DS} > V_{GS} - 1V \end{cases}$$

MOS Transistors

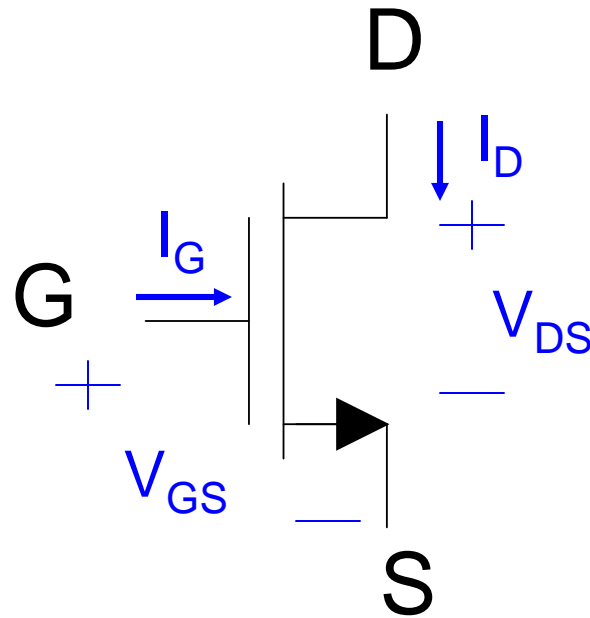

Model:

$$I_G = 0$$

$$I_D = f_1(V_{GS}, V_{DS})$$

the two-variable function f_1 is quite nonlinear

D: Drain
G: Gate
S: Source

End of Lecture 29