

EE 230


Lecture 30

Nonlinear Circuits and Nonlinear Devices

- Diode
- BJT
- MOSFET

Quiz 18

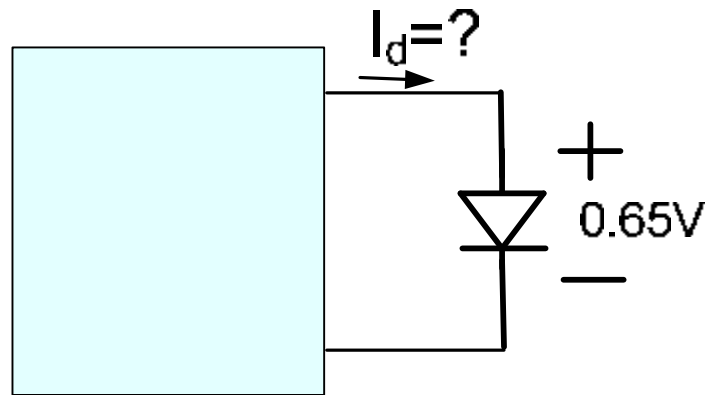If a diode has a value of $I_S=1E-14A$ and the diode voltage is .65V, what will be the diode current if operating at $T=300K$?



And the number is ?

1

3

8

5

4

2

6

9

7

And the number is ?

1

3

8

5

4

2

3


6

9

7

Quiz 18

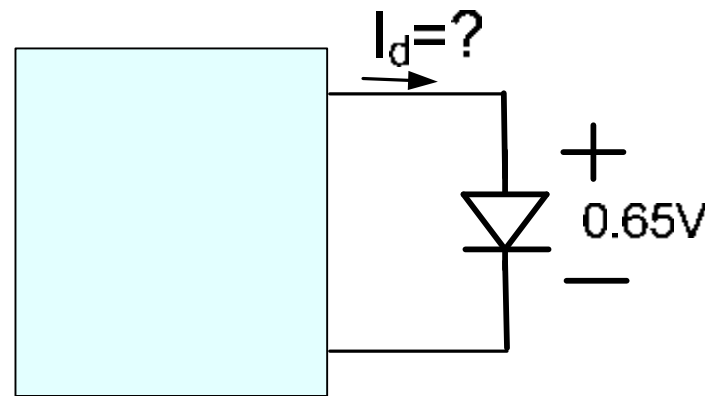If a diode has a value of $I_S=1E-14A$ and the diode voltage is .65V, what will be the diode current if operating at $T=300K$?





Solution:

$$I_d = I_S \left(e^{\frac{V_d}{V_t}} - 1 \right)$$

$$I_d = 1E-14 \left(e^{\frac{0.65}{300 \cdot 8.63E-5}} \right) = 1E-14 \cdot 8E10 = 800\mu A$$





Review from Last Time:

The Real Electronics World

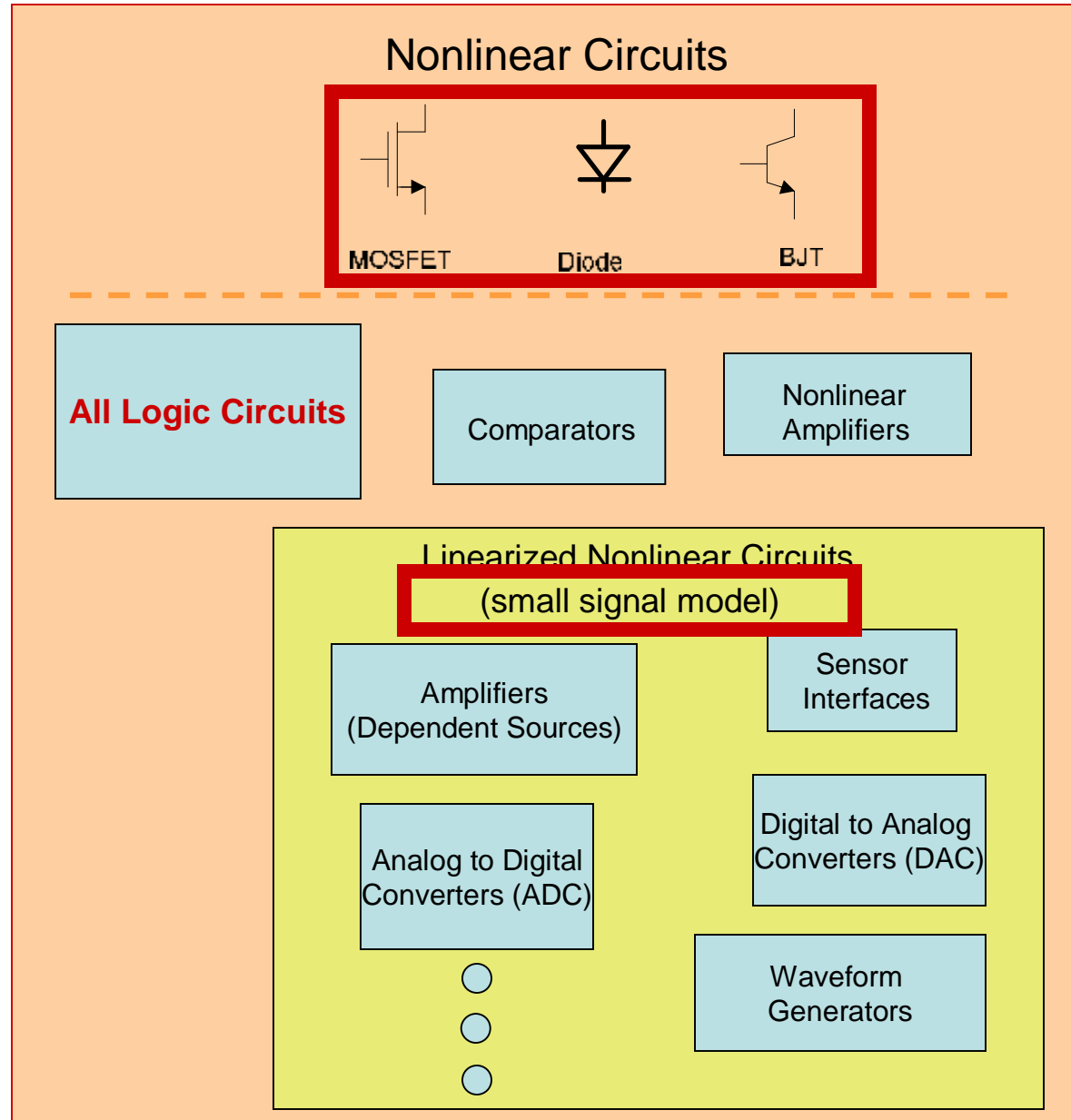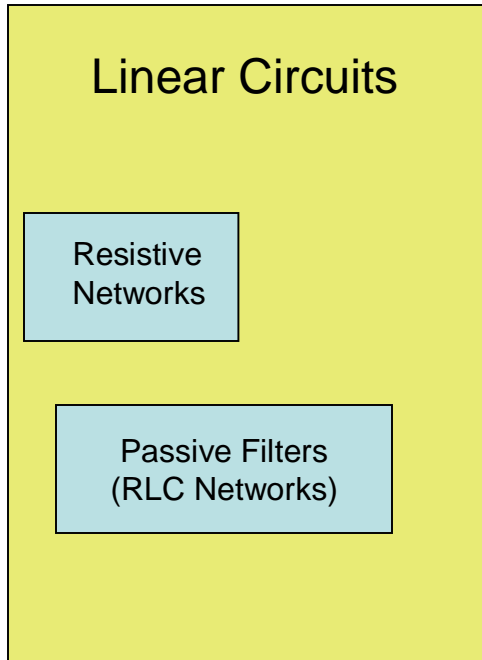

Review from Last Time:


The Diode

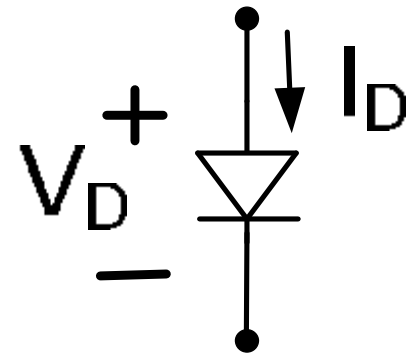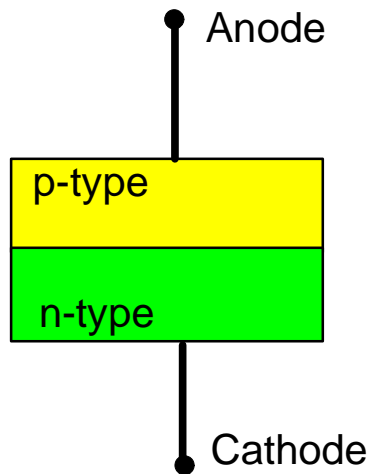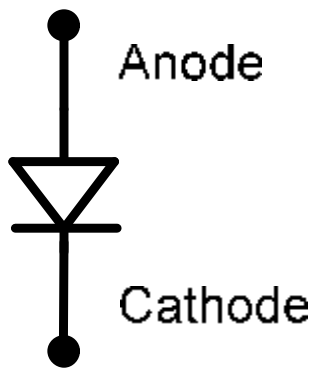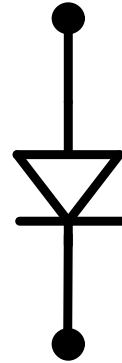


Review from Last Time:

Types of Diodes


pn junction diodes

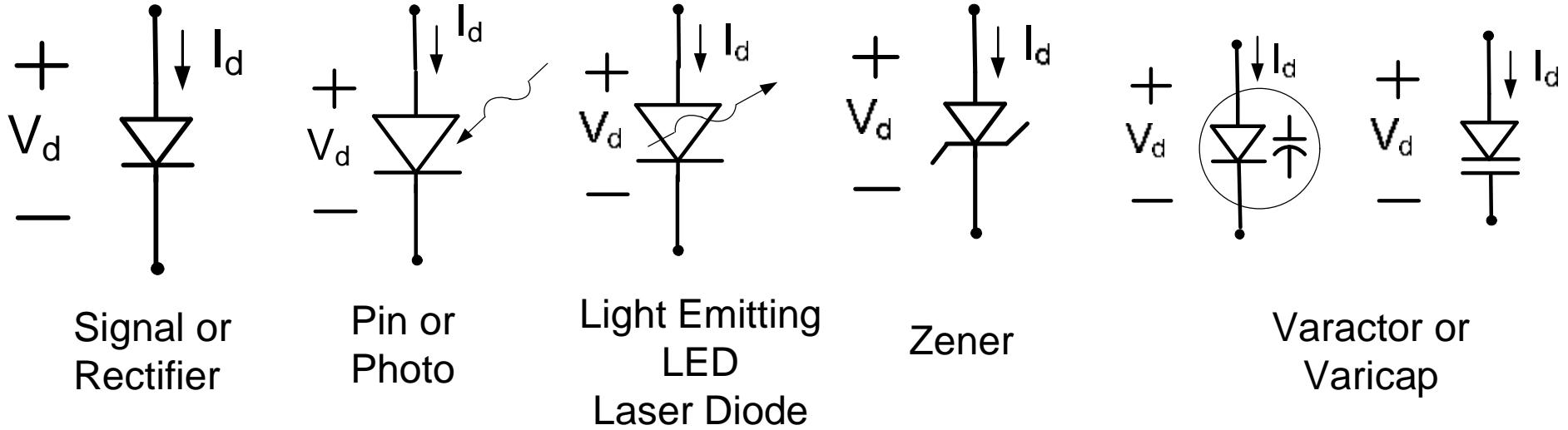

Metal-semiconductor junction diodes

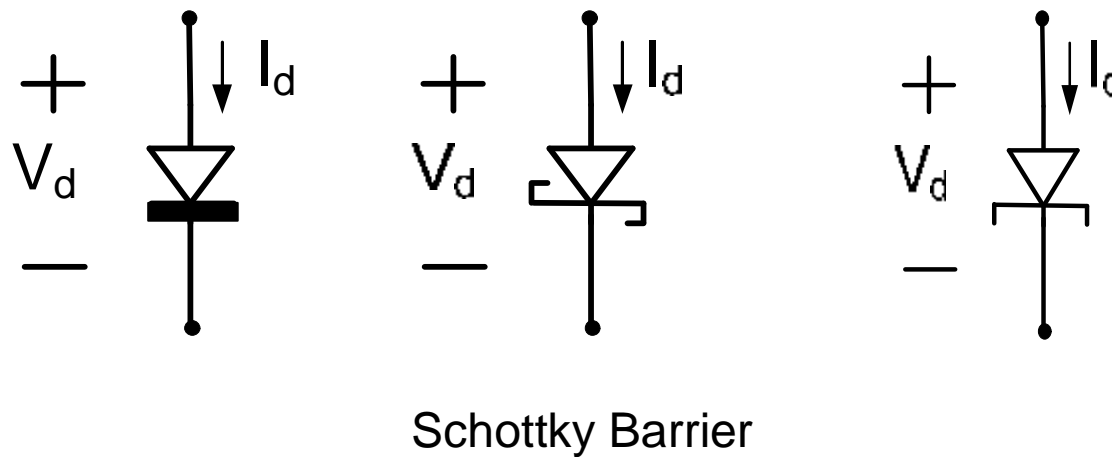

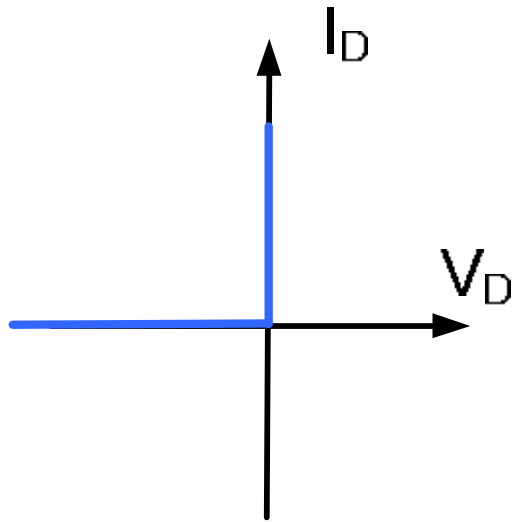
Review from Last Time: **The Ideal Diode**



$$I_D = 0 \quad \text{if} \quad V_D \leq 0 \quad \text{“OFF”}$$
$$V_D = 0 \quad \text{if} \quad I_D > 0 \quad \text{“ON”}$$




“ON”

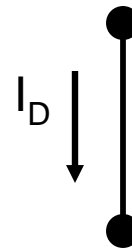

$$I_D > 0$$

“OFF”

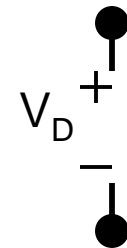


$$V_D \leq 0$$

Valid for

Review from Last Time:

Diode equation (silicon pn junction diodes)
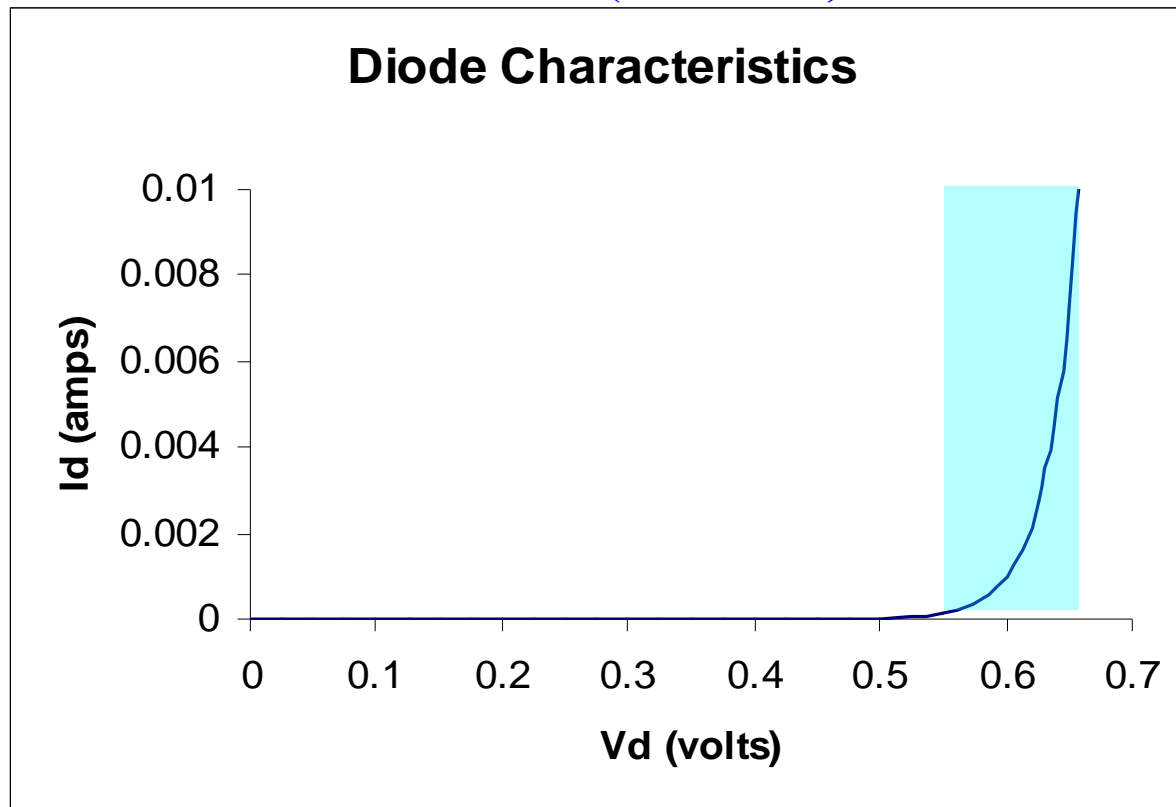
$$I_d = I_s \left(e^{\frac{V_d}{V_t}} - 1 \right)$$




Widely Used Piecewise Linear Model

Review from Last Time:

A more accurate approximation to the diode equation
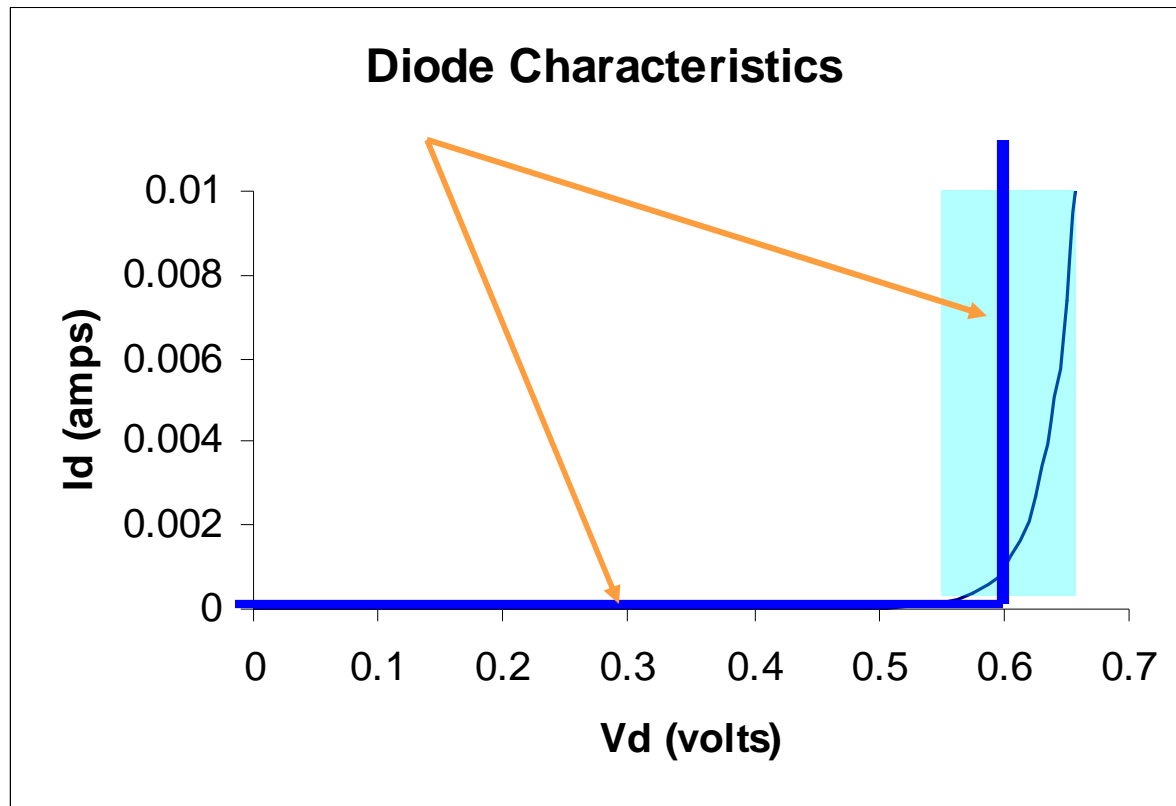
$$I_d = I_S \left(e^{\frac{V_d}{V_t}} - 1 \right)$$



More accurate pn junction
diode model:



$$\begin{array}{ll} I_d = 0 & V_d < 0.6V \\ V_d = 0.6V & I_d > 0 \end{array}$$

Review from Last Time:

A more accurate approximation to the diode equation




$$I_d = I_S \left(e^{\frac{V_d}{V_t}} - 1 \right)$$

Piecewise Linear Model


$$I_d = 0 \quad V_d < 0.6V$$

$$V_d = 0.6V \quad I_d > 0$$





Equivalent Circuit

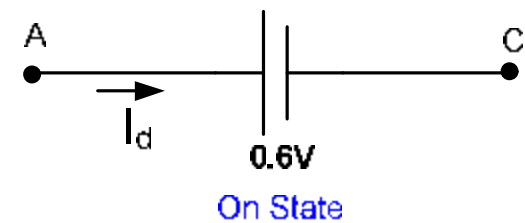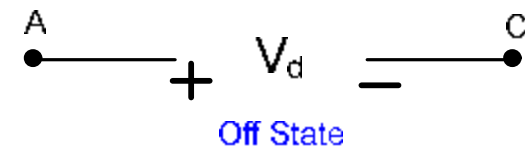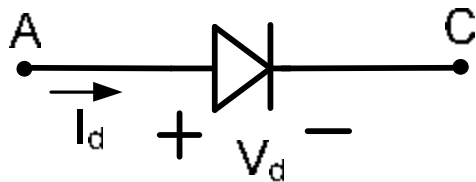

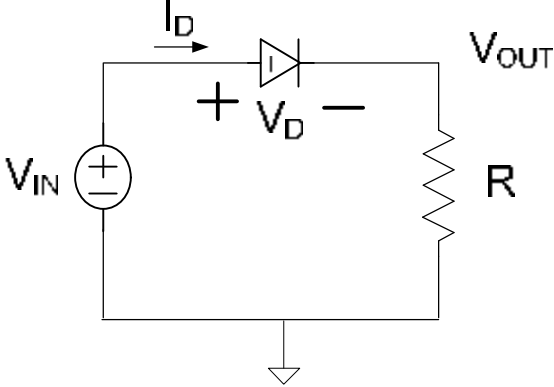Performance Limitations of Diode Rectifier Circuit




Diode rectifier circuit

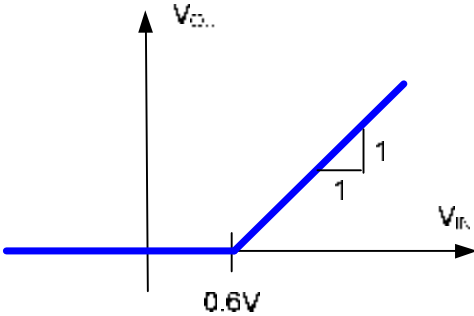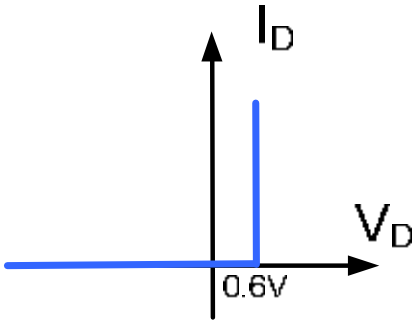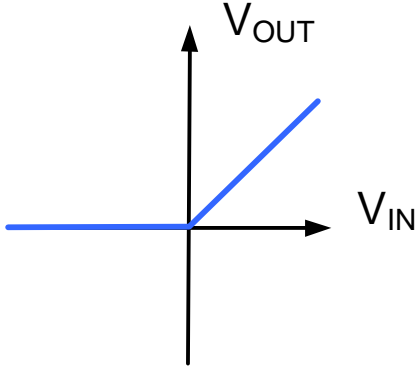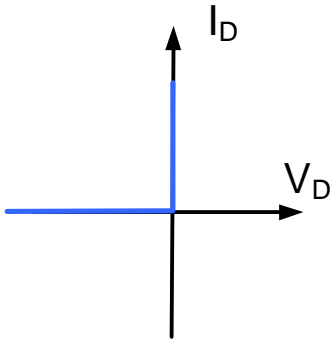


shift in break point


Review from Last Time:

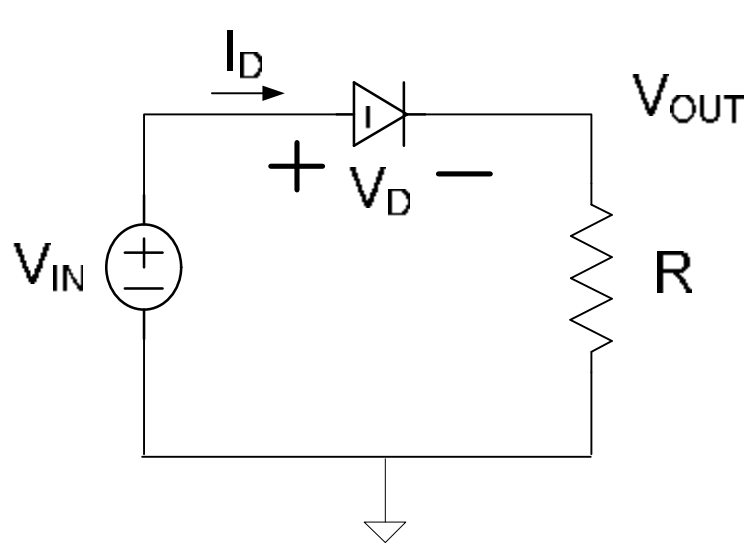

Diode rectifier circuit


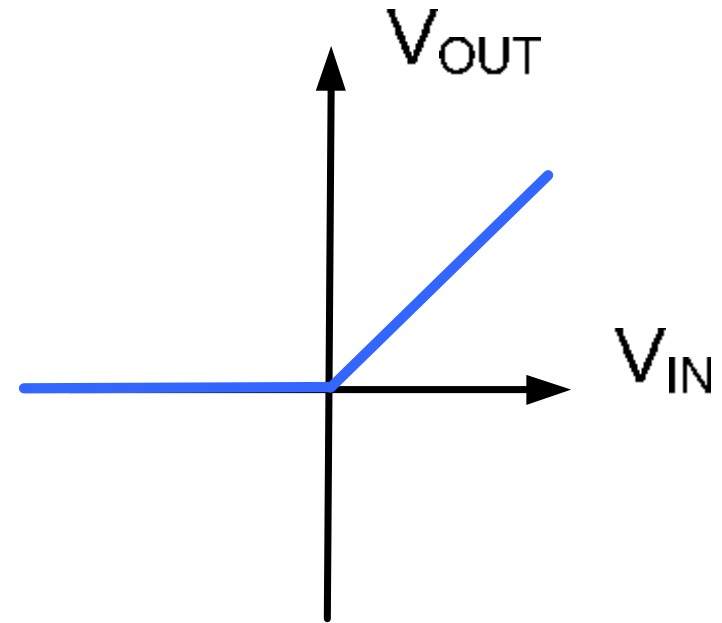


If $V_{IN} = V_M \sin \omega t$

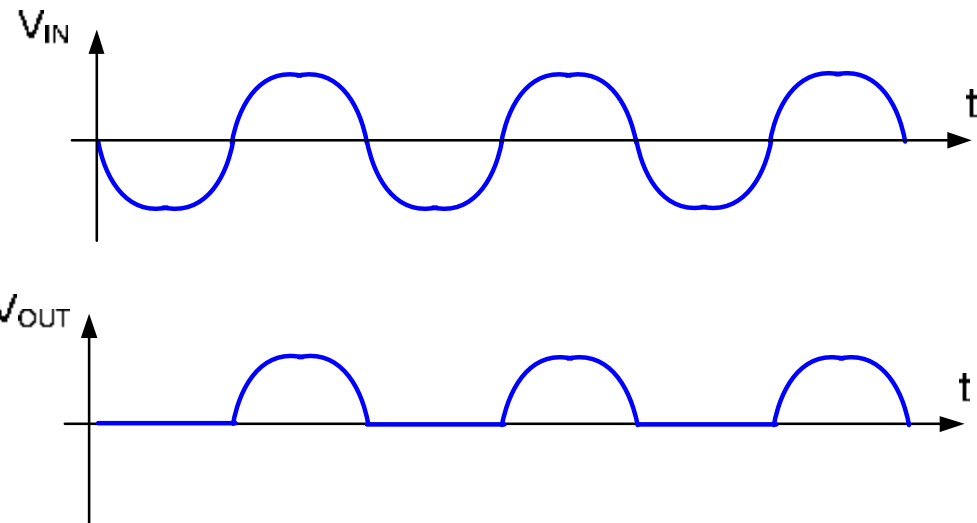


Serves as a rectifier – very useful function !

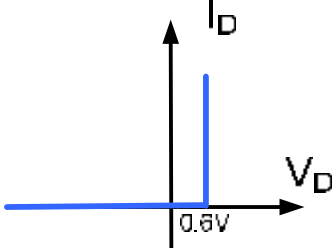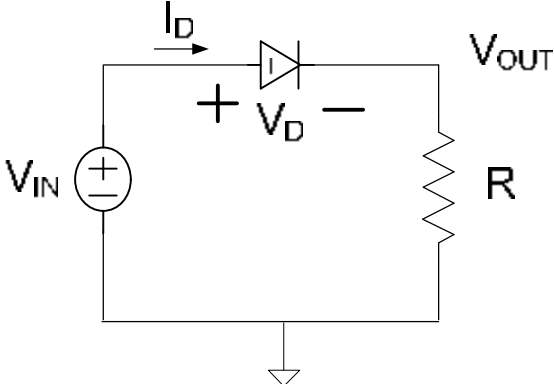Performance Limitations of Diode Rectifier Circuit




Diode rectifier circuit

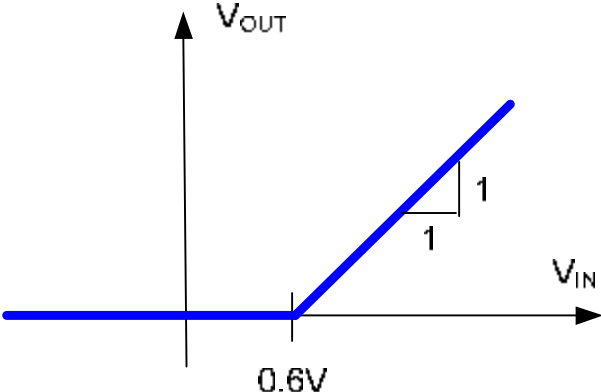

$$V_{OUT} = \begin{cases} 0 & V_{IN} \leq 0.6V \\ V_{IN} - 0.6V & V_{IN} > 0.6V \end{cases}$$

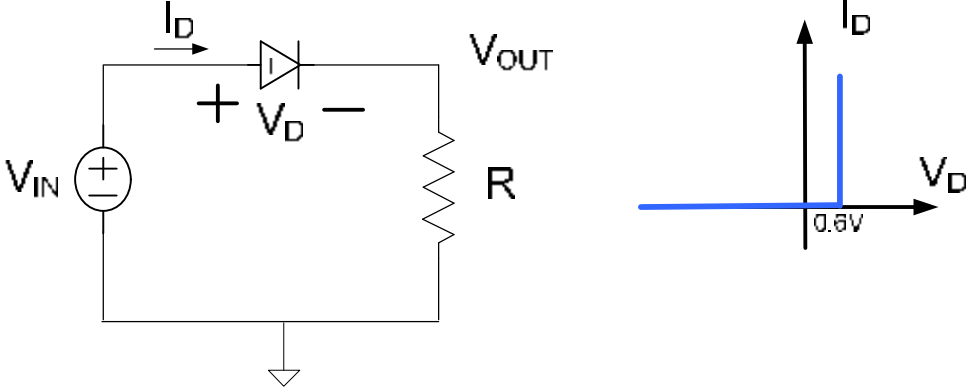Performance Limitations of Diode Rectifier Circuit




Diode rectifier circuit



$$V_{OUT} = \begin{cases} 0 & V_{IN} \leq 0.6V \\ V_{IN} - 0.6V & V_{IN} > 0.6V \end{cases}$$

Consider $V_{IN} = V_M \sin \omega t$ for $V_M = 50V$, $V_M = 1V$ and $V_M = 0.5V$




Desired output:

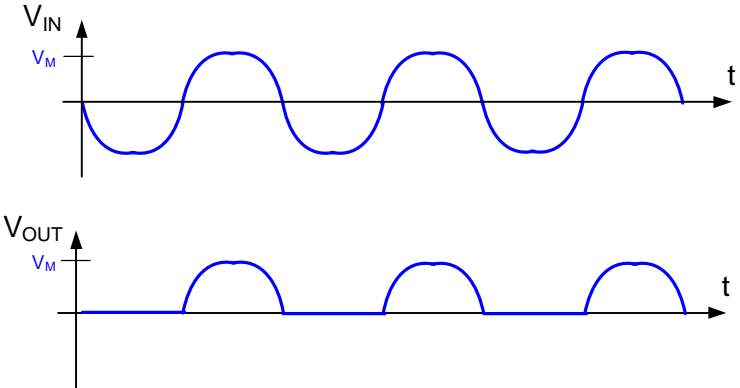

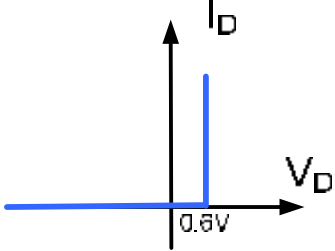
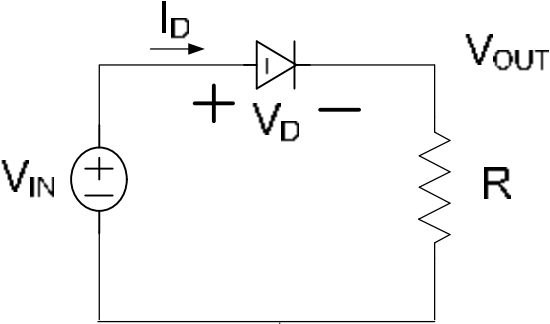
Performance Limitations of Diode Rectifier Circuit



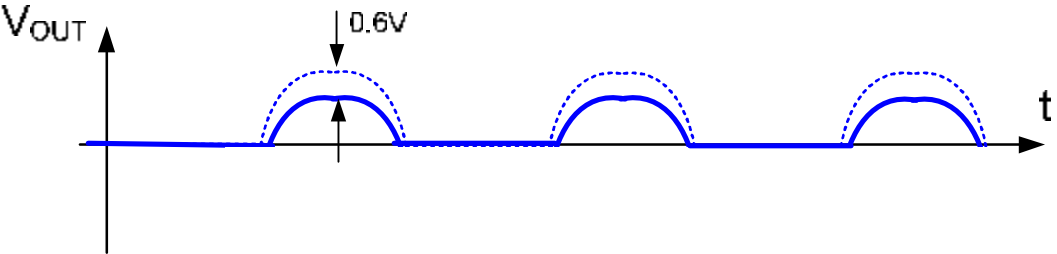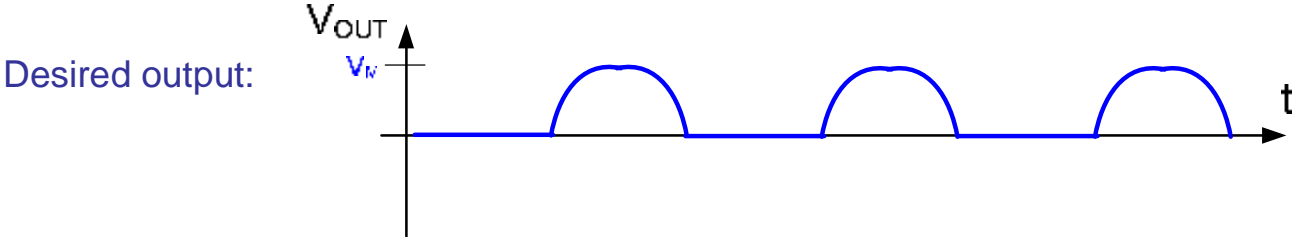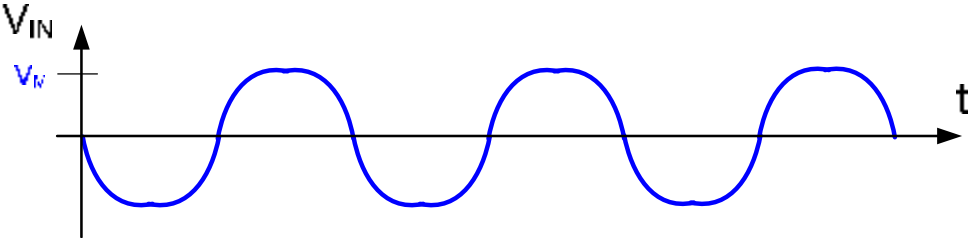
Consider $V_{IN} = V_M \sin \omega t$ for $V_M = 50V$, $V_M = 1V$ and $V_M = 0.5V$



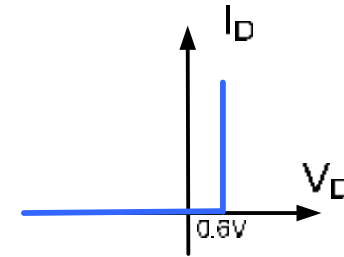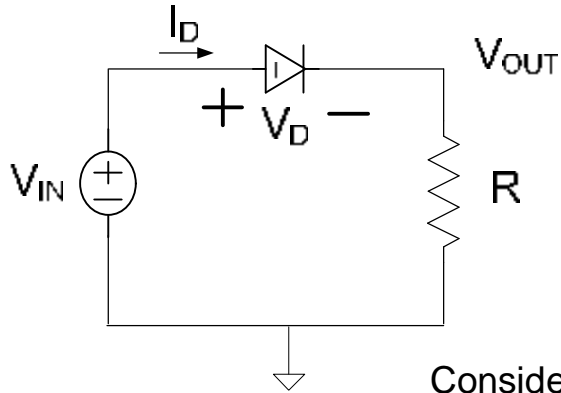Performance Limitations of Diode Rectifier Circuit




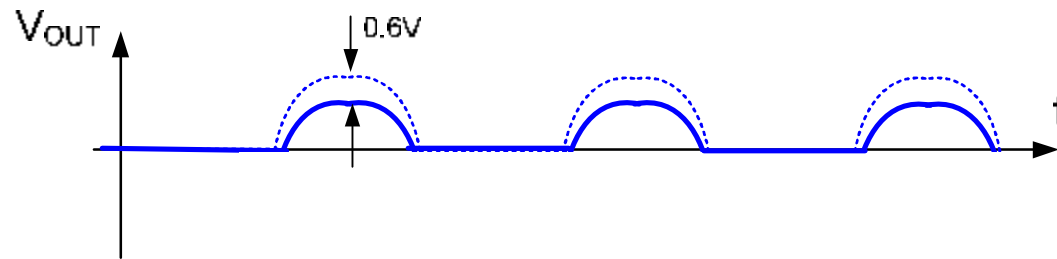Consider $V_{IN} = V_M \sin \omega t$ for $V_M = 50V$, $V_M = 1V$ and $V_M = 0.5V$





If $V_M = 50V$, the 0.6V drop causes very little degradation in performance

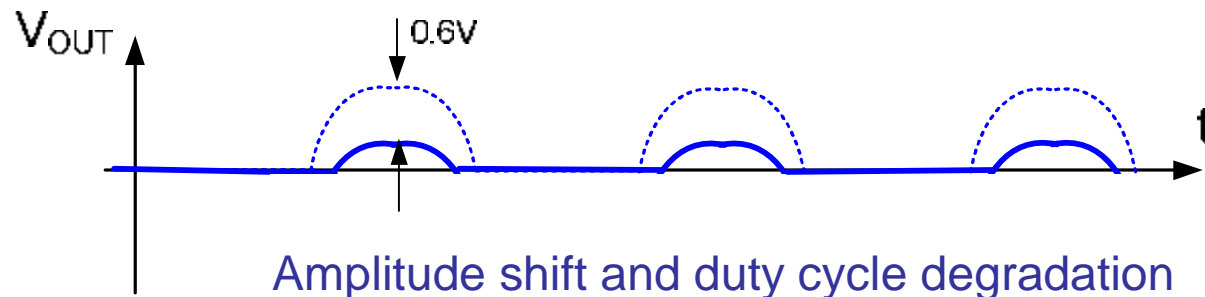
If $V_M = 1V$, the 0.6V drop causes dramatic degradation in performance



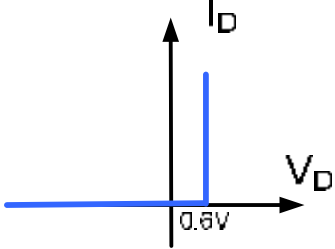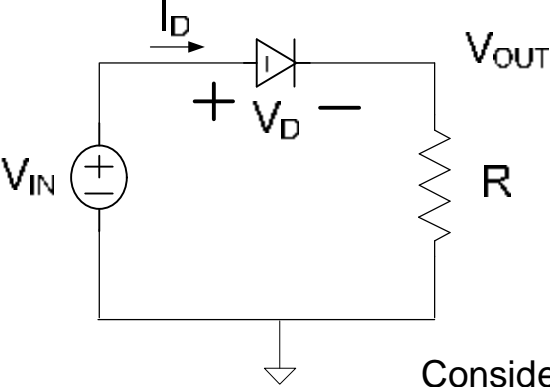
Performance Limitations of Diode Rectifier Circuit



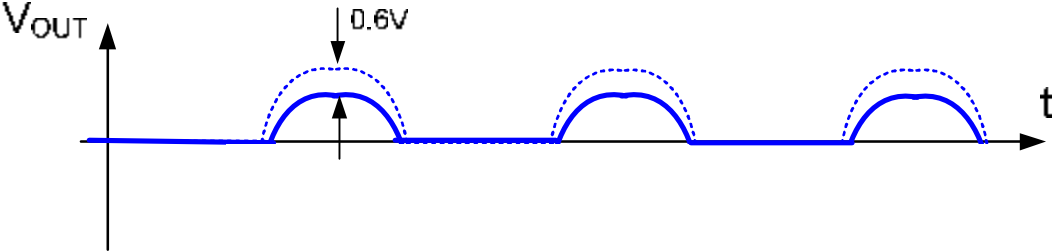
Consider $V_{IN} = V_M \sin \omega t$ for $V_M = 50V$, $V_M = 1V$ and $V_M = 0.5V$



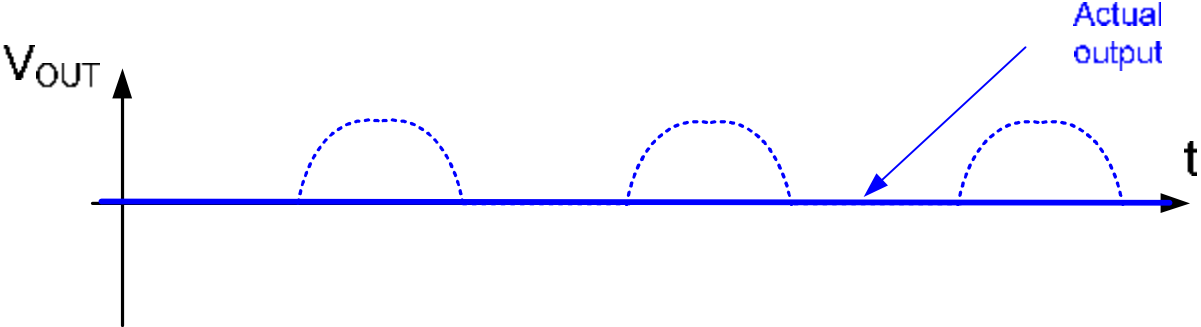If $V_M = 0.5V$, the 0.6V drop provides no output !



Precision Rectifier

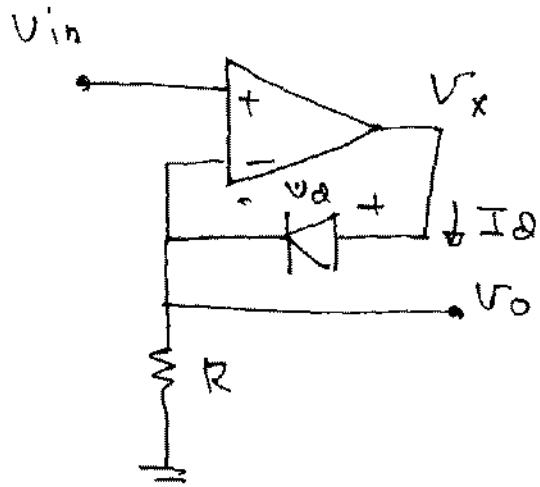

Case 1 D_1 conducting

$$V_x = V_i + 0.6V$$

$$V_o = V_i$$

Valid for $I_D > 0$

$$\frac{V_{in}}{R} > 0$$

$$V_{in} > 0$$


Case 2 D_1 cutoff

$$V_x = V_{ss}$$

$$V_o = 0$$



Valid for $v_D < 0$ + $V_{in} < V^-$

$$V_{ss} < 0 + V_{in} < 0$$

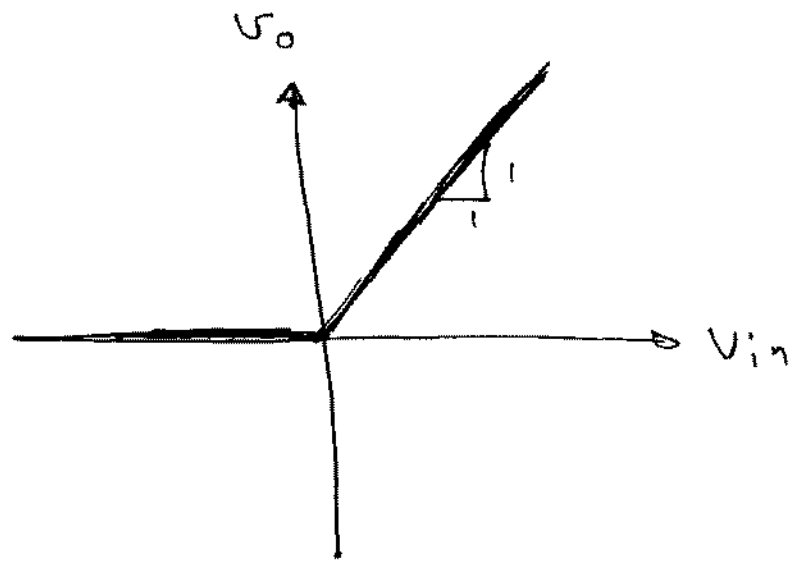



$$v_o = \begin{cases} v_{in} & v_{in} > 0 \\ 0 & v_{in} < 0 \end{cases}$$

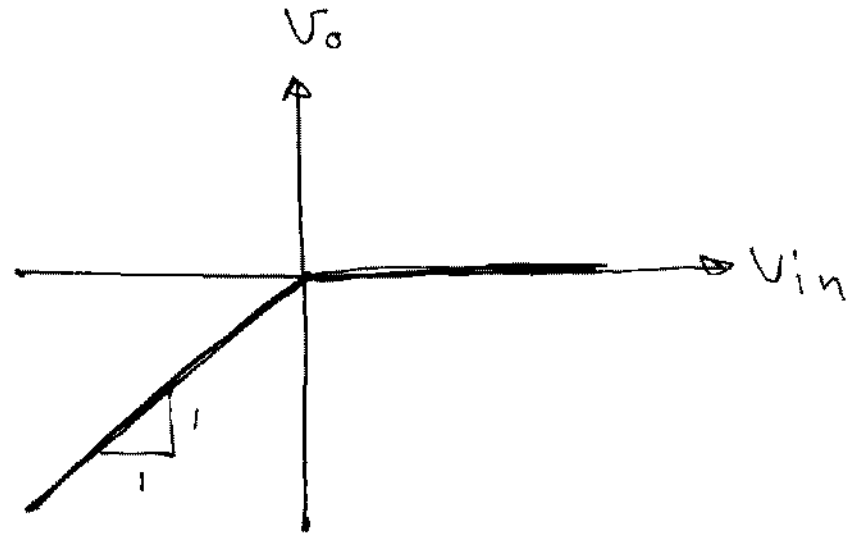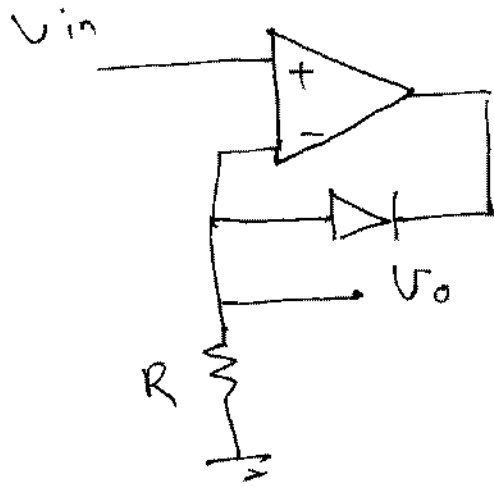This is termed precision rectifier because diode drop is not present in transfer characteristics



Precision Inverting Rectifier

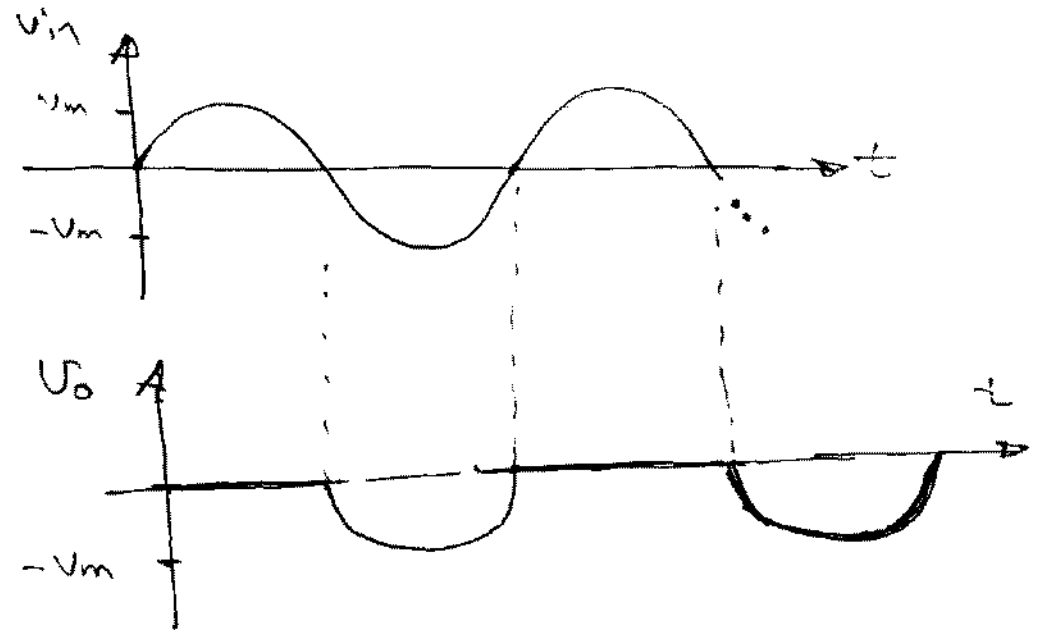

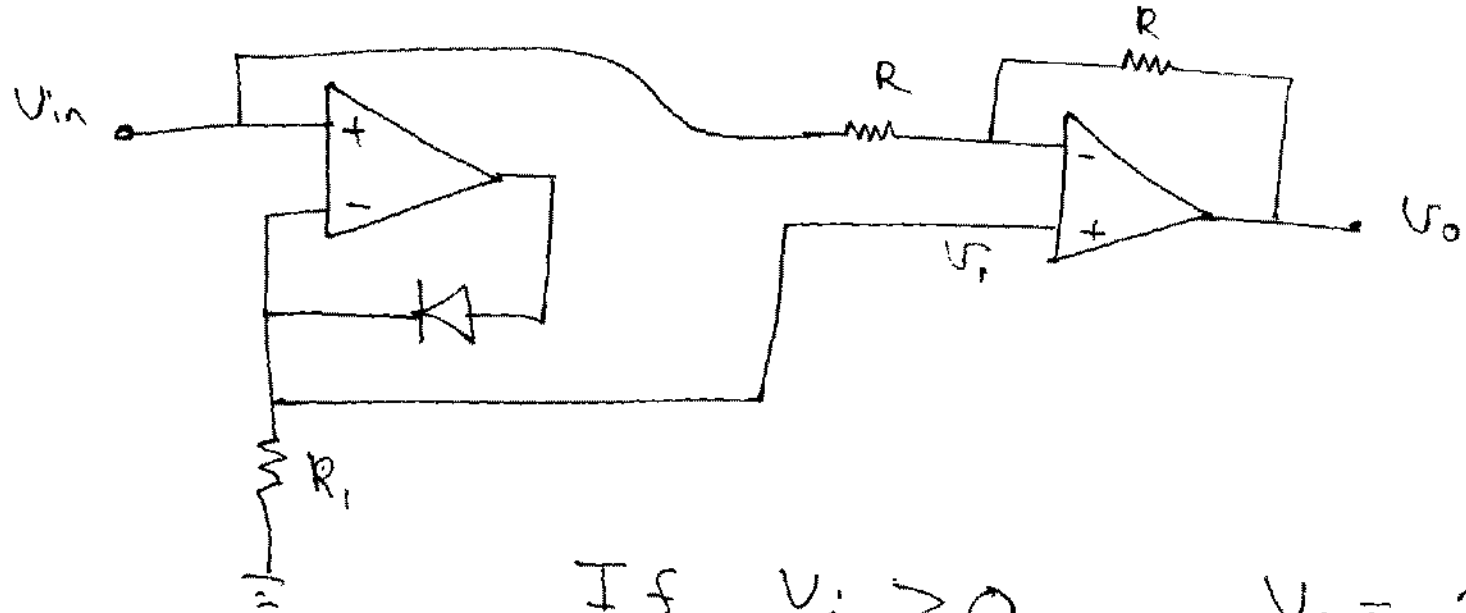


If $U_i > 0$

$$U_o = 2U_i - U_i$$


$$U_o = U_i$$

If $U_i < 0$

$$U_o = -U_i$$

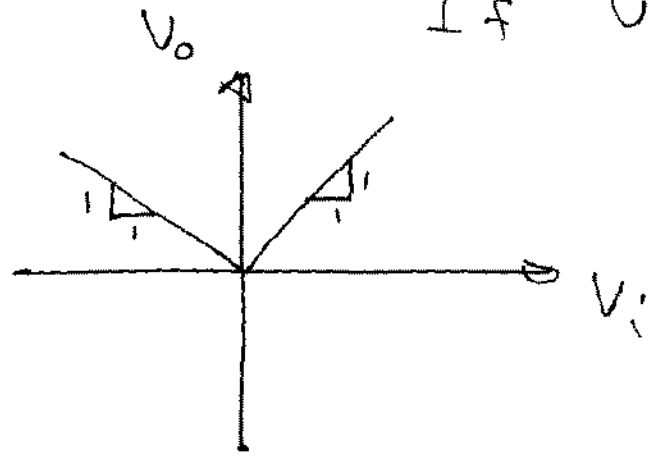

Precision Full-Wave Rectifier

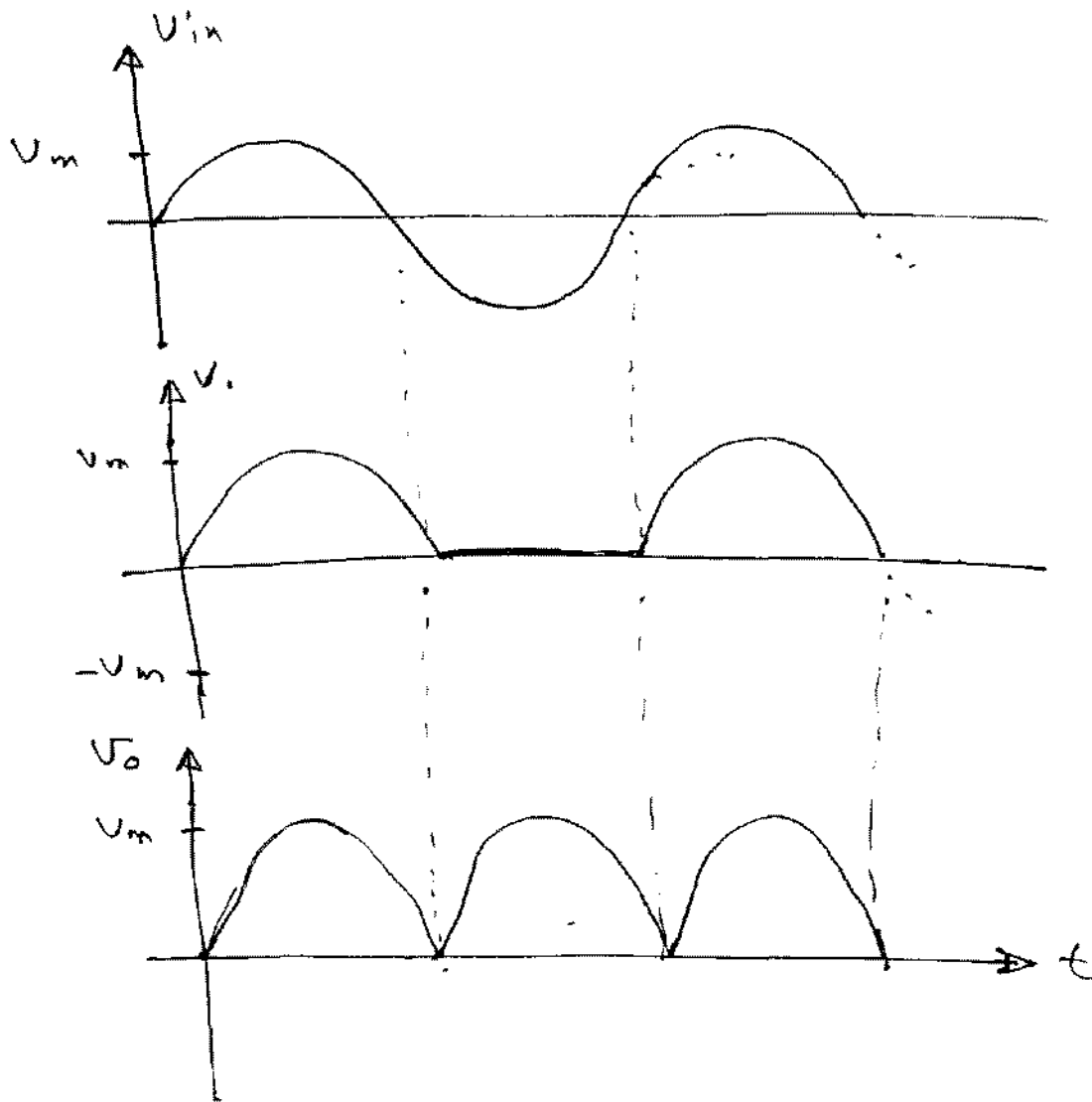

$$U_i = U_m \sin \omega t$$


$$U_i = \begin{cases} U_m \sin \omega t & U_i > 0 \\ 0 & U_i < 0 \end{cases}$$

$$U_o = 2U_i - U_i$$

$$U_o = \begin{cases} (2U_m - U_m) \sin \omega t & U_i > 0 \\ -U_m \sin \omega t & U_i < 0 \end{cases}$$

$$U_o = \begin{cases} U_m \sin \omega t & U_i > 0 \\ -U_m \sin \omega t & U_i < 0 \end{cases}$$

Nonlinear Function Generator.

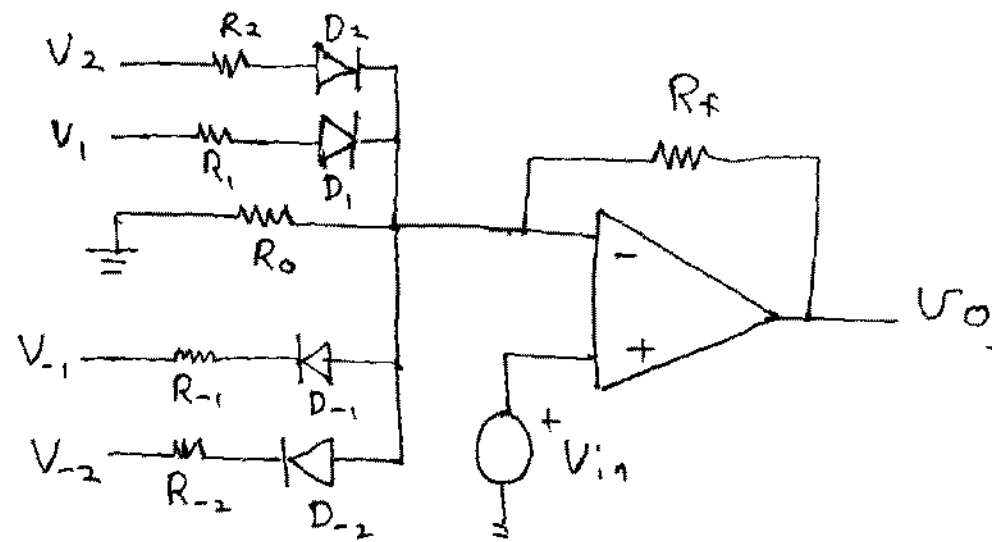

Assume ideal diodes (actually may work better with nonideal diodes)

$$V_2 > V_1 > 0 > V_{-1} > V_{-2}$$

For $V_i > V_2$, D_1 & D_2 off, D_{-1} , D_{-2} ON

$$\frac{V_o}{V_i} = 1 + \frac{R_f}{R_0 \parallel R_{-1} \parallel R_{-2}}$$

For $V_1 < V_i < V_2$ D_1 off, D_2, D_{-1}, D_{-2} ON

$$\frac{V_o}{V_i} = 1 + \frac{R_f}{R_0 \parallel R_2 \parallel R_{-1} \parallel R_{-2}}$$

For $V_{-1} < V_i < V_1$ D_1, D_2, D_{-1}, D_{-2} ON

$$\frac{V_o}{V_i} = 1 + \frac{R_f}{R_0 \parallel R_1 \parallel R_2 \parallel R_{-1} \parallel R_{-2}}$$

For $V_{-2} < V_i < V_{-1}$ D_{-1} off, D_1, D_2, D_{-2} ON

$$\frac{V_o}{V_i} = 1 + \frac{R_f}{R_0 \parallel R_1 \parallel R_2 \parallel R_{-2}}$$


For $V_i < V_{-2}$ D_1, D_2 ON

$$\frac{V_o}{V_i} = 1 + \frac{R_f}{R_0 \parallel R_1 \parallel R_2}$$

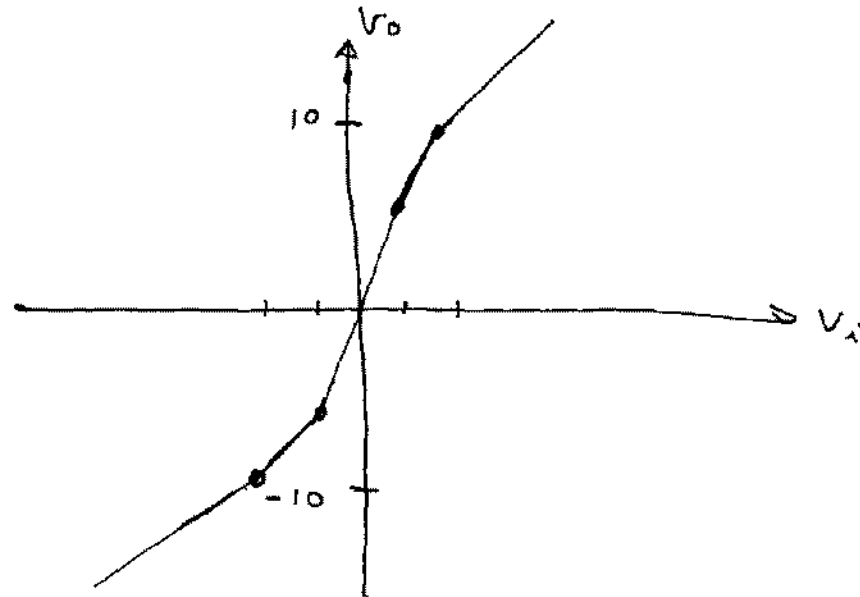
Example: $v_1 = 1V, v_2 = 2V, v_{-1} = -1V, v_{-2} = -2V$

$$R_0 = R_1 = R_2 = R_{-1} = R_{-2} = R_F$$

$$v_o = \begin{cases} 4v_i + 3 & 2 < v_i \\ 5v_i + 1 & 1 < v_i < 2 \\ 6v_i & -1 < v_i < 1 \\ 5v_i - 1 & -2 < v_i < -1 \\ 4v_i - 3 & v_i < -2 \end{cases}$$



Generalized Nonlinear Function Generator

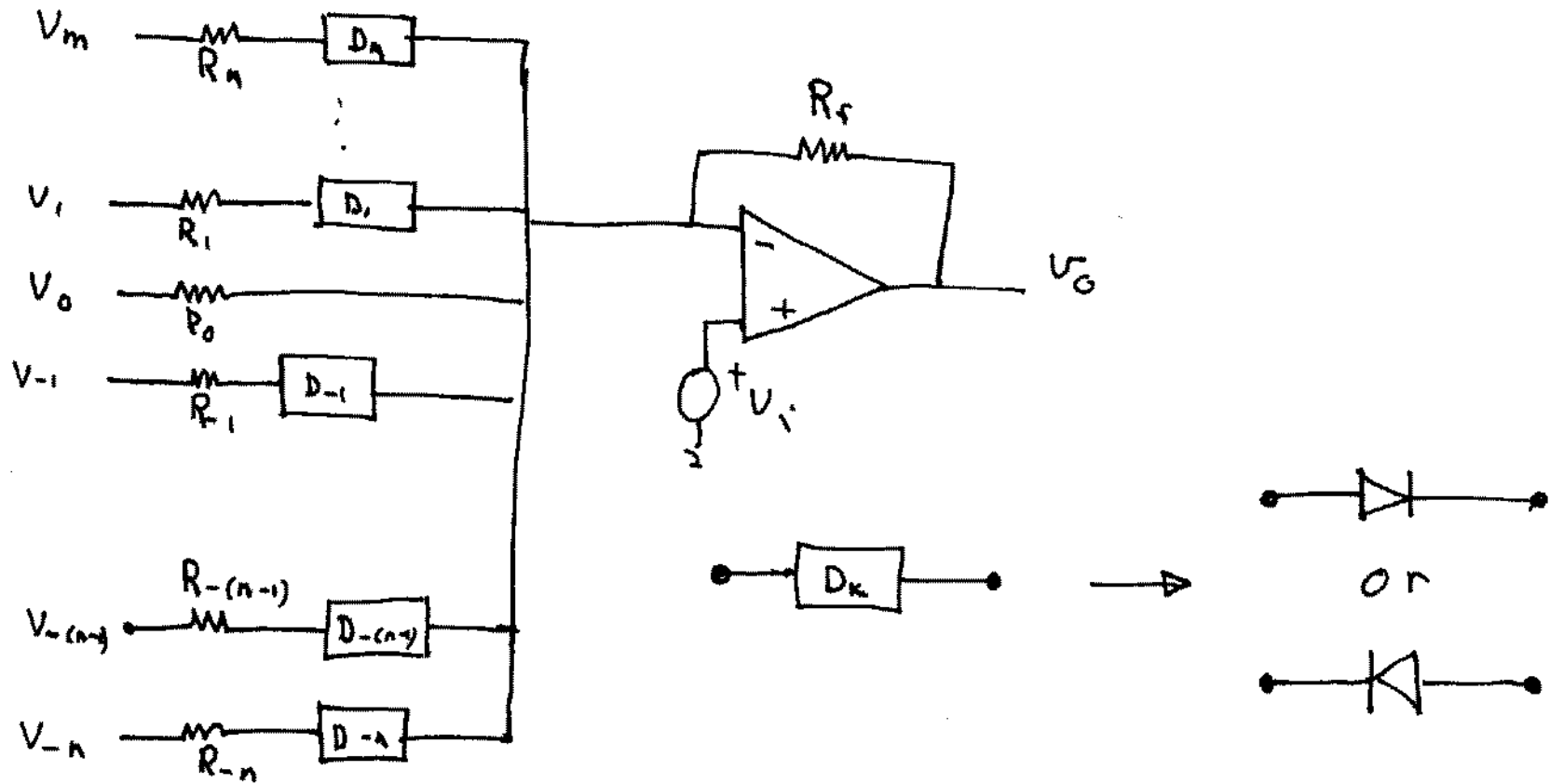

$$V_{-n} < V_{-(n-1)} < \dots < V_{-1} < V_0 < V_1 < \dots < V_m$$

Each diode can be oriented either to the left or to the right.

Slope of V_o vs V_i always positive and larger than 1

- This circuit can generate an arbitrary nonlinear transfer characteristic depending only upon how the diodes are oriented and how the voltages are selected.
- The slope of the transfer characteristic at a voltage V_i will depend upon which diodes are conducting and will be given

by

$$1 + \frac{R_f}{\quad}$$

(Parallel Combination
of Resistors for
branches with
conducting diodes)



A mathematical expression will now be given for U_0 . The notation is tedious. Define

the Boolean variable $b_k(v_i)$ for $-n \leq k < 0$ and $0 < k \leq m$ as

$$b_k(v_i) = \begin{cases} 1 & \text{if } V_i > V_k \text{ and diode}_k \text{ oriented} \\ & \text{or if } V_i < V_k \text{ and diode}_k \text{ oriented} \\ 0 & \text{if } V_i > V_k \text{ and diode}_k \text{ oriented} \\ & \text{or if } V_i < V_k \text{ and diode}_k \text{ oriented} \end{cases}$$

and define


$$b_0 = 1$$

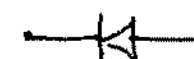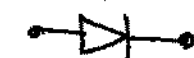


It follows from KCL by summing currents at the "-" terminal of the op amp that the output at a given v_i can be expressed as

$$V_o = V_i \left[1 + R_F \sum_{k=-n}^m \frac{b_k(V_i)}{R_k} \right] - \sum_{k=-n}^m V_k \left(\frac{R_F}{R_k} \right) b_k(V_i)$$

Example

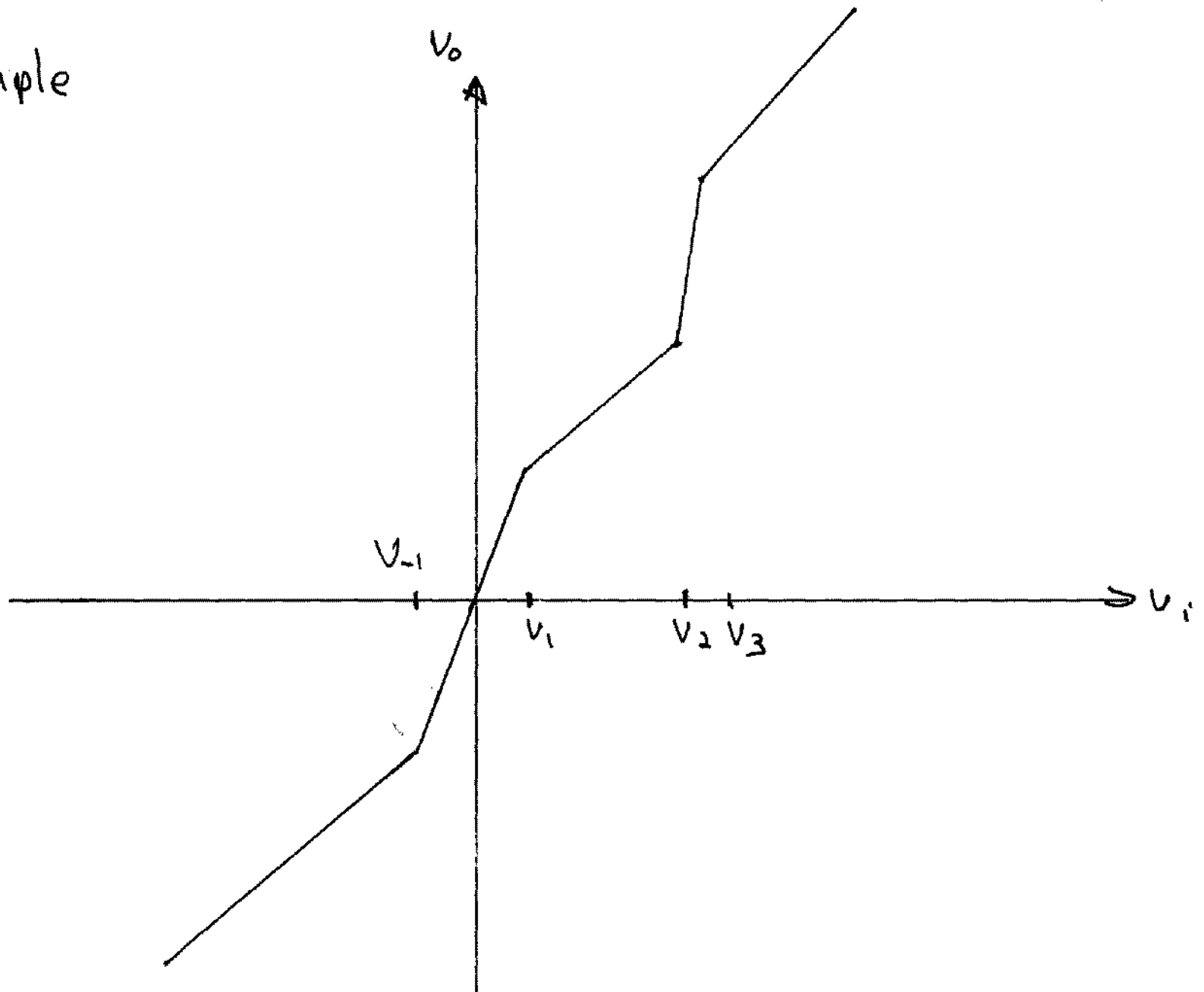

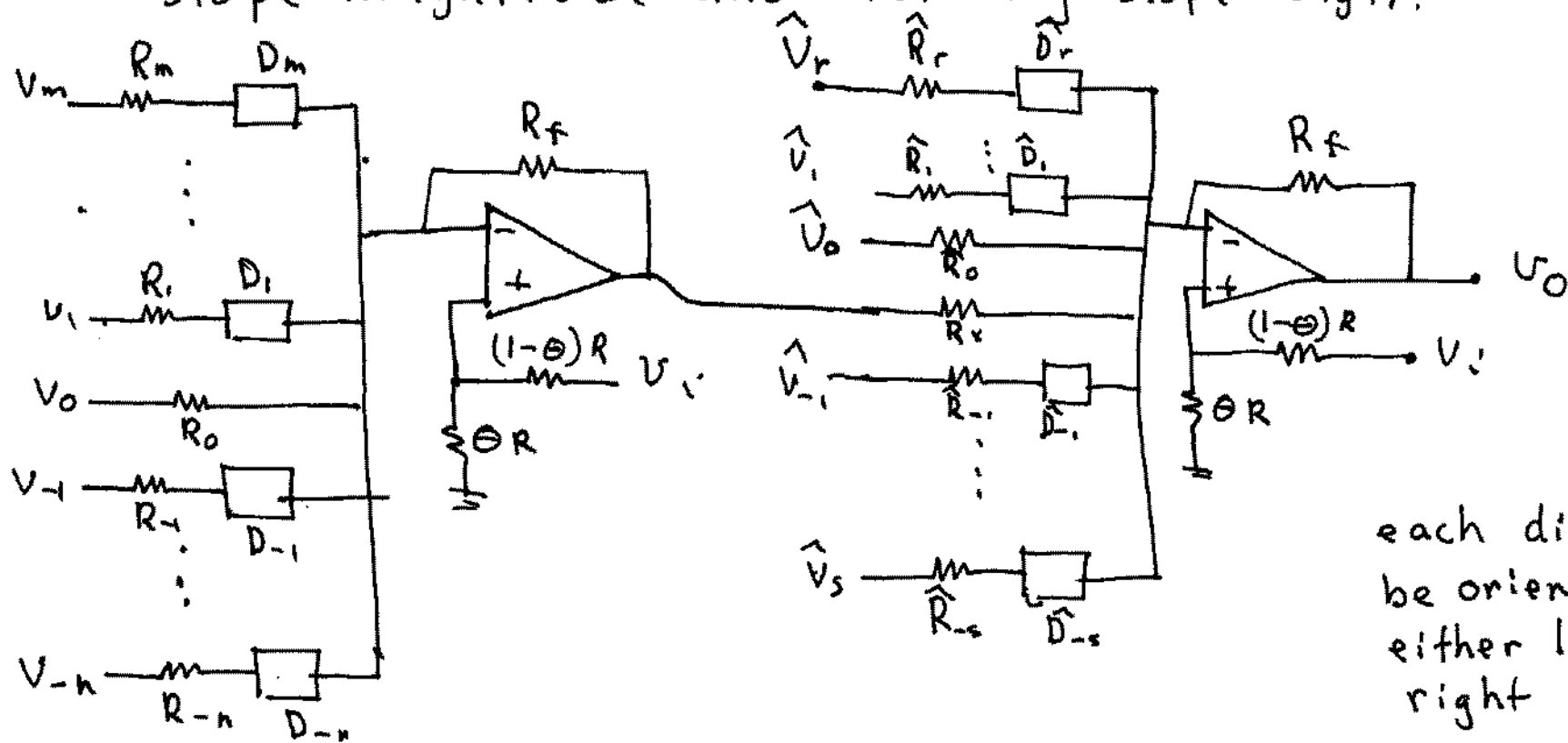Generalized Nonlinear Function Generator with arbitrary slope magnitude and arbitrary slope sign.



each diode can be oriented to either left or right

The formulation of an expression for V_o is quite tedious but operation and design is straight forward.

Example

