







# EE 230

## Lecture 34

Small Signal Models  
Small Signal Analysis

Review from Last Time:
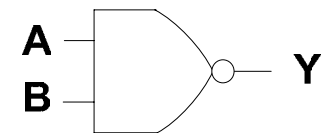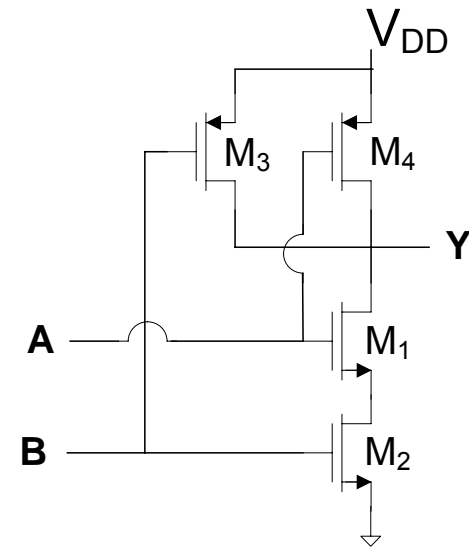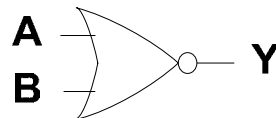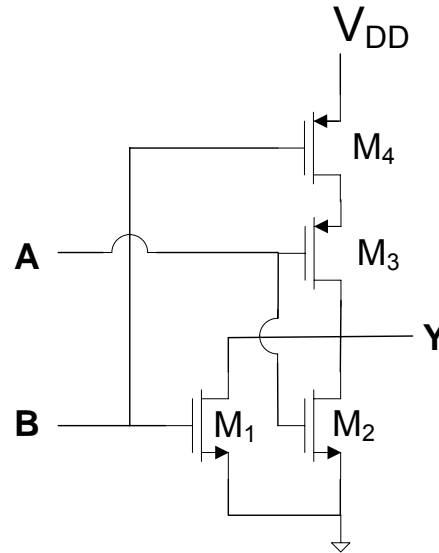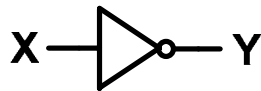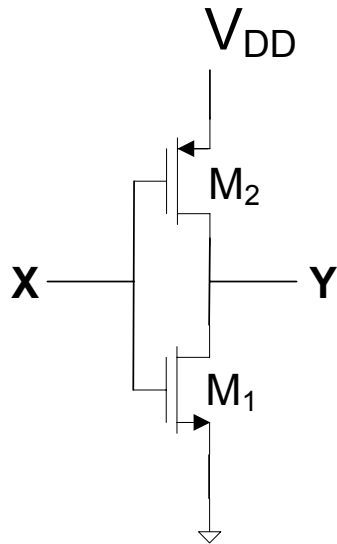
# MOS Transistor Applications (Digital Circuits)





- Termed CMOS Logic
- Widely used in industry today (millions of transistors in many ICs using this logic)
- Almost never used as discrete devices




Review from Last Time:

# Bipolar Transistor

npn

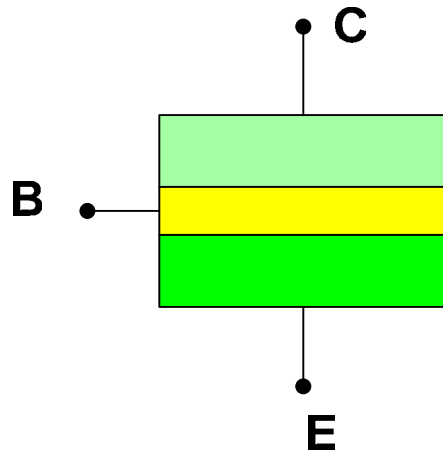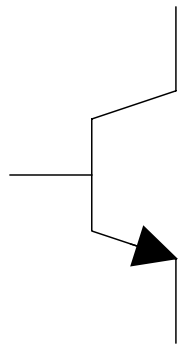


pnp

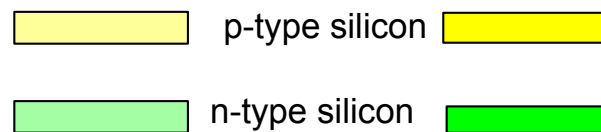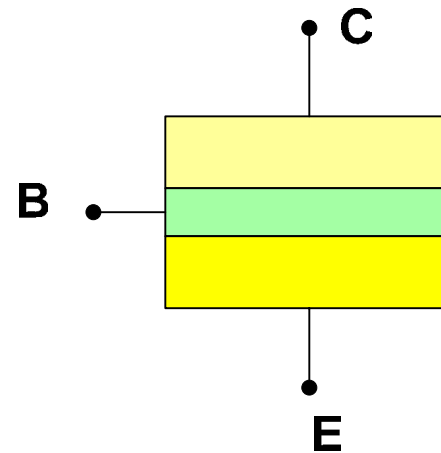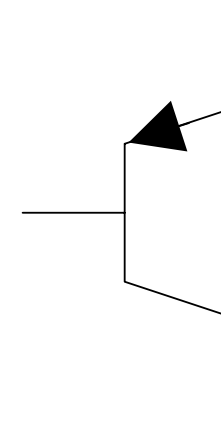


Review from Last Time:


# Bipolar and MOS Region Comparisons

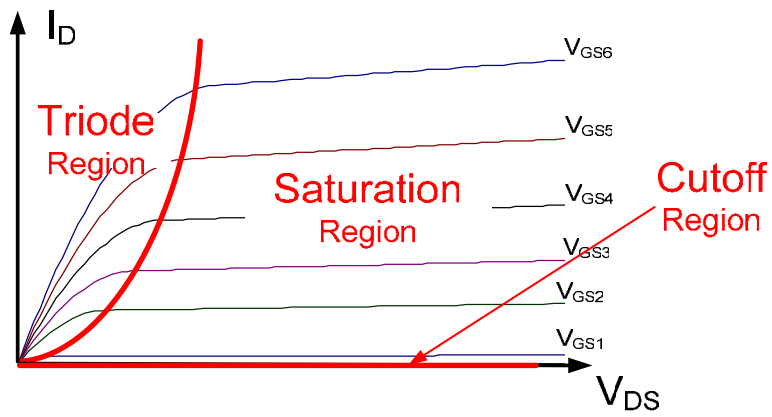

MOSFET

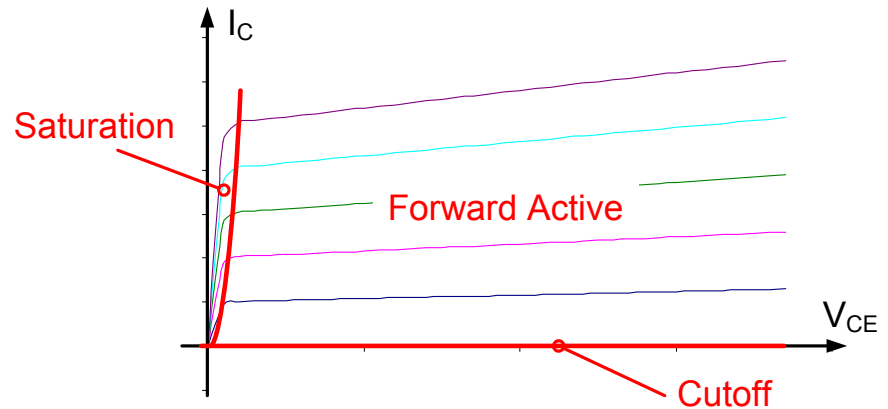

BJT

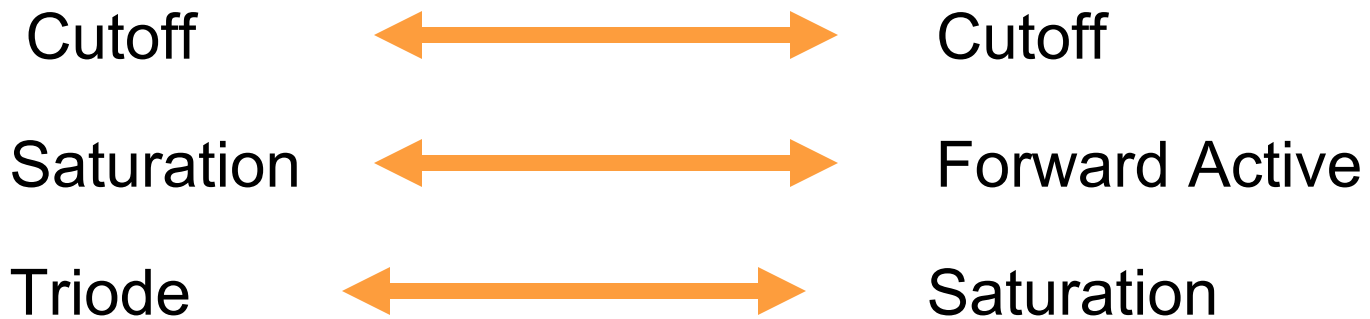

Review from Last Time:

# Bipolar Transistor

## Multi-Region Model

$$I_C = \beta I_B \left( 1 + \frac{V_{CE}}{V_{AF}} \right)$$

$$I_B = \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}}$$

$$V_t = \frac{kT}{q}$$

$$V_{BE} > 0.4V$$

$$V_{BC} < 0$$

Forward Active

$$V_{BE} = 0.7V$$
$$V_{CE} = 0.2V$$

$$I_C < \beta I_B$$

Saturation

$$I_C = I_B = 0$$


$$V_{BE} < 0$$

$$V_{BC} < 0$$

Cutoff

Review from Last Time:


# Small-Signal Principle

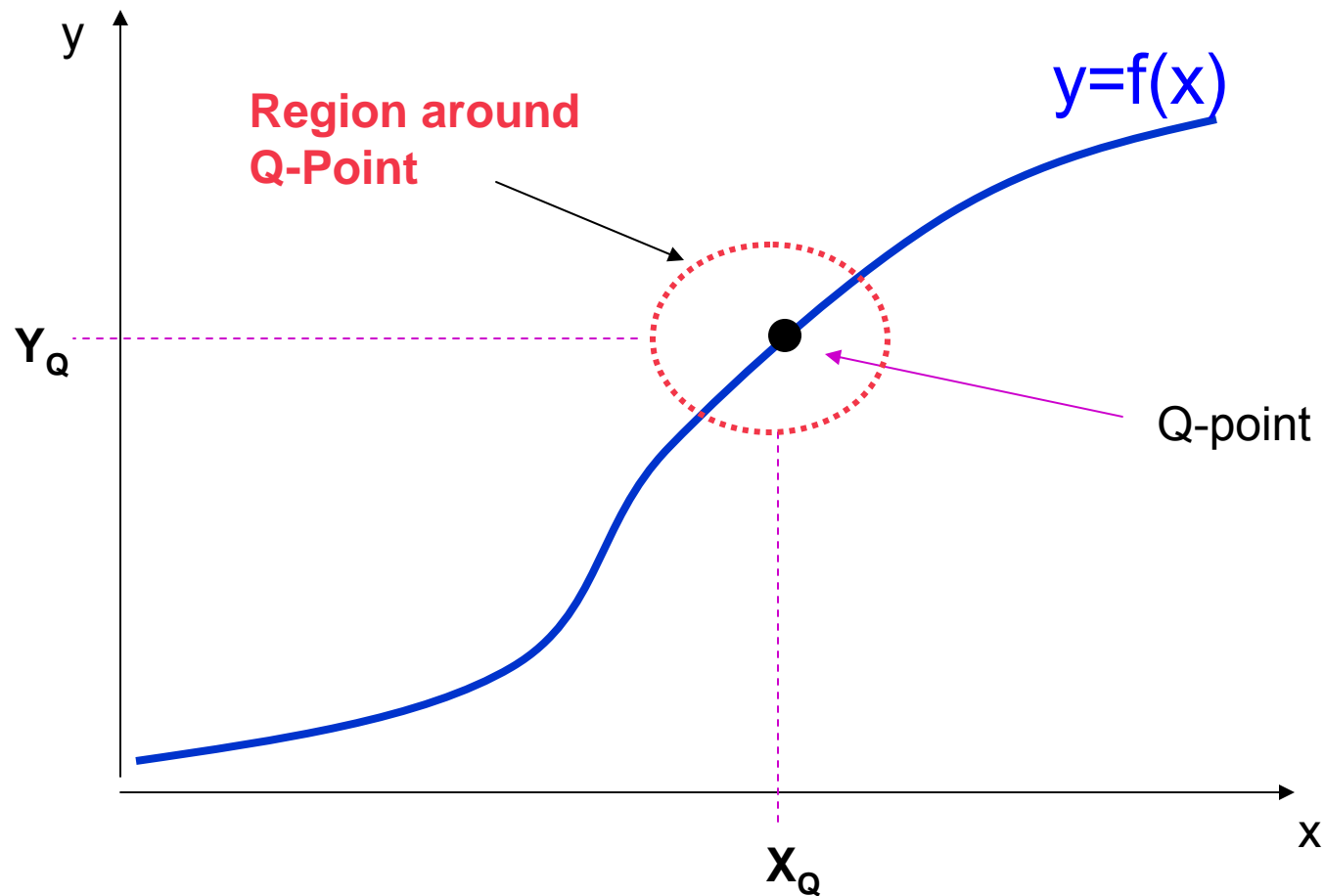

Relationship is nearly linear in a small enough region around Q-point  
Region of linearity is often quite large  
Linear relationship may be different for different Q-points

Review from Last Time:

# Small-Signal Principle

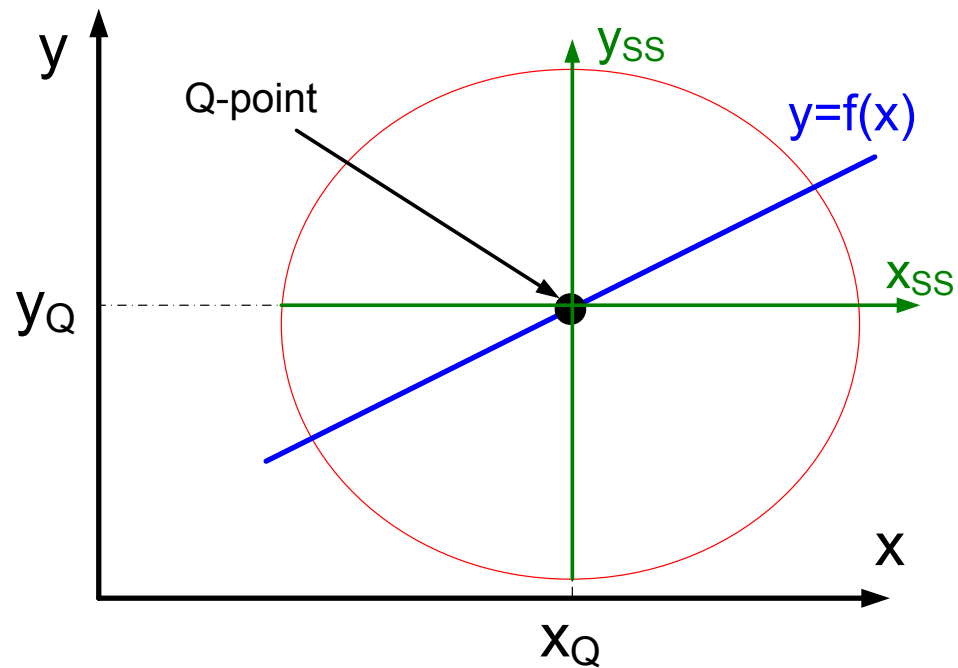


## Small-Signal Model:


$$y = f(x_Q) + \left. \frac{\partial f}{\partial x} \right|_{x=x_Q} (x - x_Q) \longleftrightarrow y_{ss} = \left. \frac{\partial f}{\partial x} \right|_{x=x_Q} x_{ss}$$

- *Mathematically, small signal model is simply Taylor's series expansion at the Q-point truncated after first-order terms*

# Small-Signal Principle

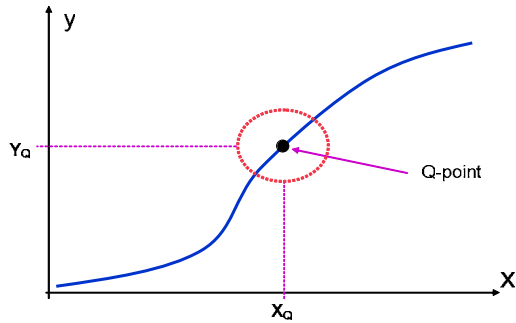


$$y_{ss} = \left. \frac{\partial f}{\partial x} \right|_{x=x_Q} x_{ss}$$

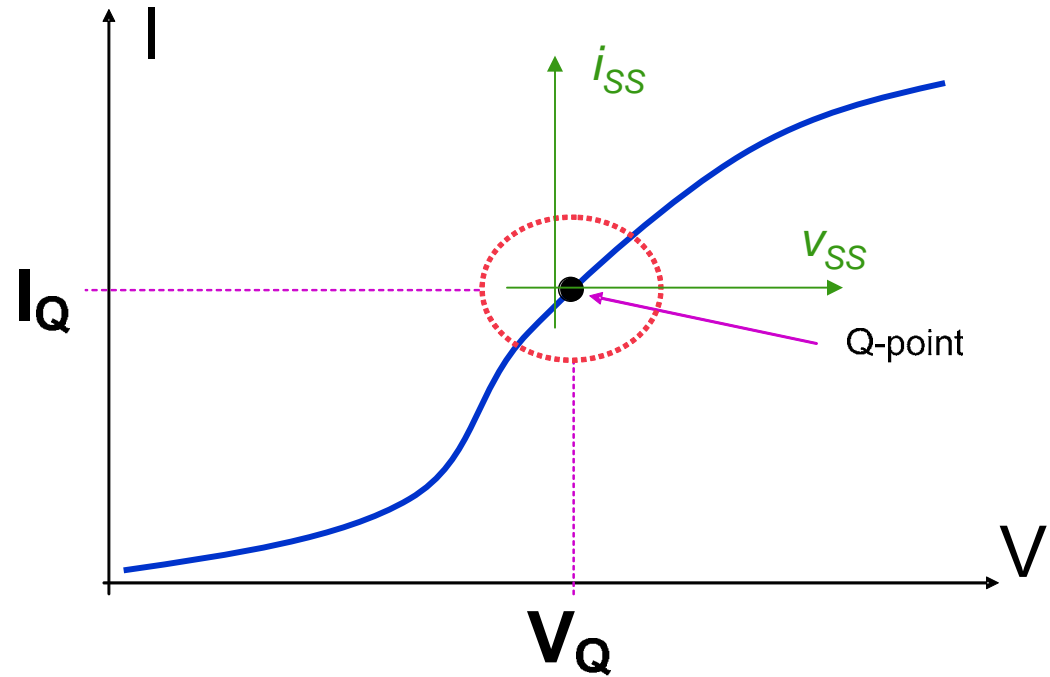

$$i_{ss} = \left. \frac{\partial I}{\partial V} \right|_{V=V_Q} v_{ss}$$



# Small-Signal Principle

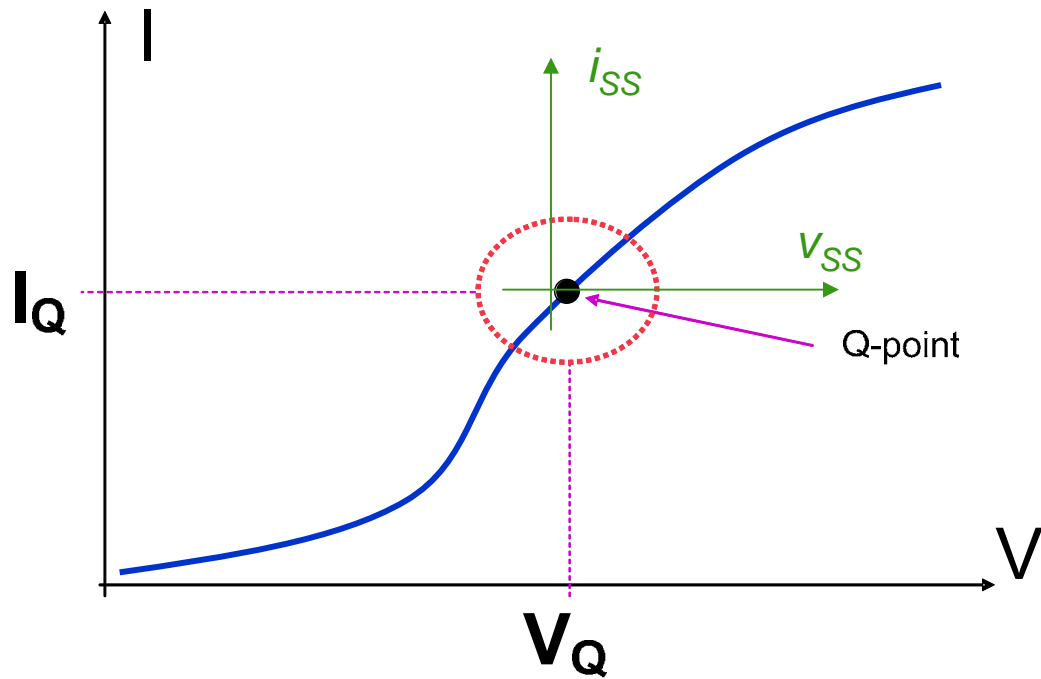

$$i_{ss} = \left. \frac{\partial I}{\partial V} \right|_{V=V_Q} v_{ss}$$


$$i_{ss} \stackrel{\text{def}}{=} i$$

$$v_{ss} \stackrel{\text{def}}{=} v$$

$$y \stackrel{\text{defn}}{=} \left. \frac{\partial I}{\partial V} \right|_{V=V_Q}$$

$$i = y v$$


# Small-Signal Principle

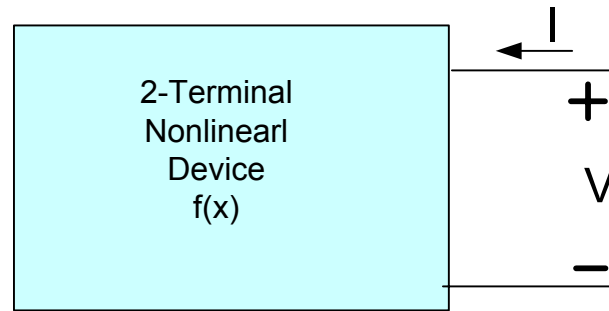

$$y = \left. \frac{\partial I}{\partial V} \right|_{V=V_Q}$$

$$i = y v$$

A Small Signal Equivalent Circuit

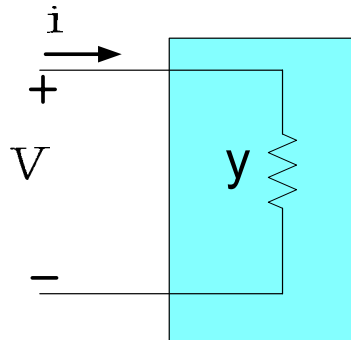

*The small-signal model of this 2-terminal electrical network is a resistor of value  $1/y$   
One small-signal parameter characterizes this one-port but it is dependent on Q-point*

Review from Last Time:

# Small-Signal Principle

Goal with small signal model is to predict performance of circuit or device in the vicinity of an operating point

Operating point is often termed Q-point

Will be extended to functions of two and three variables

# Small-signal Operation of Nonlinear Circuits

- Small-signal principles



## Example Circuit

- Small-Signal Models
- Small-Signal Analysis of Nonlinear Circuits
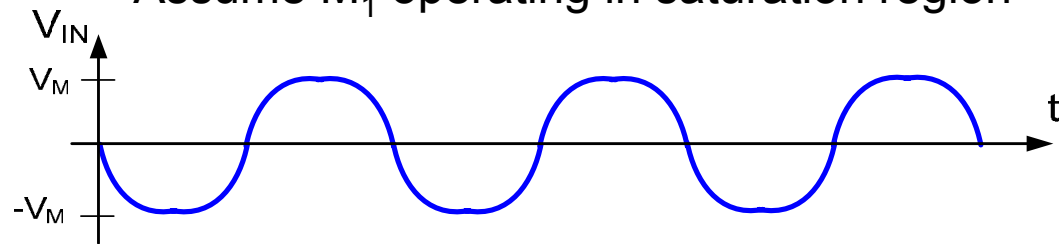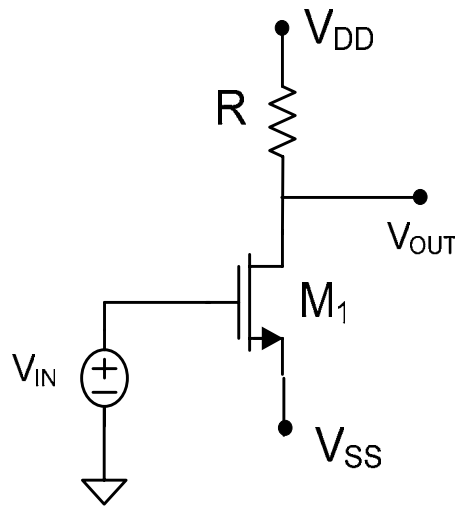
# Small signal analysis example

By selecting appropriate value of  $V_{SS}$ ,  $M_1$  will operate in the saturation region

Assume  $M_1$  operating in saturation region



$$V_{IN} = V_M \sin \omega t$$

$V_M$  is small


$$\left. \begin{aligned} V_{OUT} &= V_{DD} - I_D R \\ I_D &= \frac{\mu C_{OX} W}{2L} (V_{IN} - V_{SS} - V_T)^2 \end{aligned} \right\}$$

$$I_{DQ} = \frac{\mu C_{OX} W}{2L} (V_{SS} + V_T)^2$$

$$V_{OUT} = V_{DD} - \frac{\mu C_{OX} W}{2L} (V_{IN} - V_{SS} - V_T)^2 R$$

$$V_{OUT} = V_{DD} - \frac{\mu C_{OX} W}{2L} (V_M \sin \omega t - [V_{SS} + V_T])^2 R$$

# Small signal analysis example

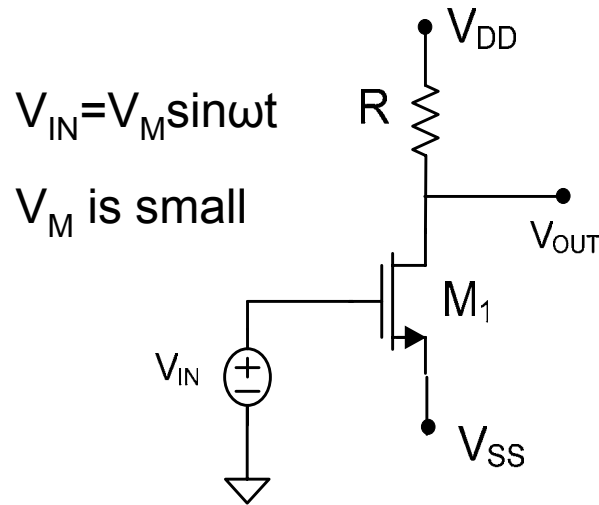

$$V_{OUT} = V_{DD} - \frac{\mu C_{OX} W}{2L} (V_M \sin \omega t - [V_{SS} + V_T])^2 R$$

$$V_{OUT} = V_{DD} - \frac{\mu C_{OX} W}{2L} [V_{SS} + V_T]^2 \left( 1 - \frac{V_M \sin \omega t}{[V_{SS} + V_T]} \right)^2 R$$


Recall that if  $x$  is small  $(1+x)^2 \cong 1+2x$

$$V_{OUT} = V_{DD} - \frac{\mu C_{OX} W}{2L} [V_{SS} + V_T]^2 \left( 1 - \frac{2V_M \sin \omega t}{[V_{SS} + V_T]} \right) R$$

$$V_{OUT} = \left\{ V_{DD} - \frac{\mu C_{OX} W}{2L} [V_{SS} + V_T]^2 R \right\} + \frac{\mu C_{OX} W}{2L} [V_{SS} + V_T]^2 \left( \frac{2V_M \sin \omega t}{[V_{SS} + V_T]} \right) R$$

$$V_{OUT} = \left\{ V_{DD} - \frac{\mu C_{OX} W}{2L} [V_{SS} + V_T]^2 R \right\} + \left\{ \frac{\mu C_{OX} W}{L} [V_{SS} + V_T] R \right\} V_M \sin \omega t$$

# Small signal analysis example

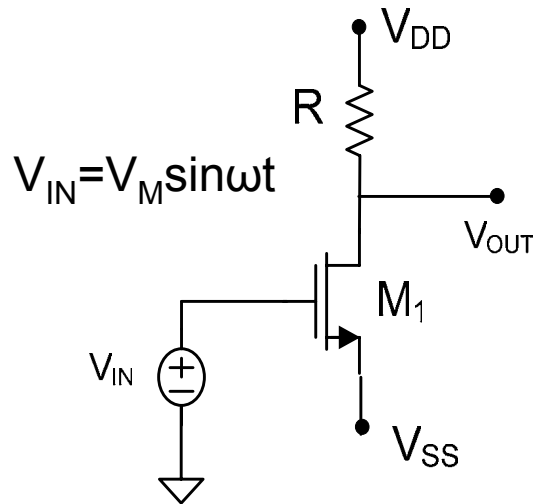


*By selecting appropriate value of  $V_{SS}$ ,  $M_1$  will operate in the saturation region*

Assume  $M_1$  operating in saturation region

$$V_{OUT} = \left\{ V_{DD} - \frac{\mu C_{OX} W}{2L} [V_{SS} + V_T]^2 R \right\} + \left\{ \frac{\mu C_{OX} W}{L} [V_{SS} + V_T] R \right\} V_M \sin \omega t$$

# Small signal analysis example

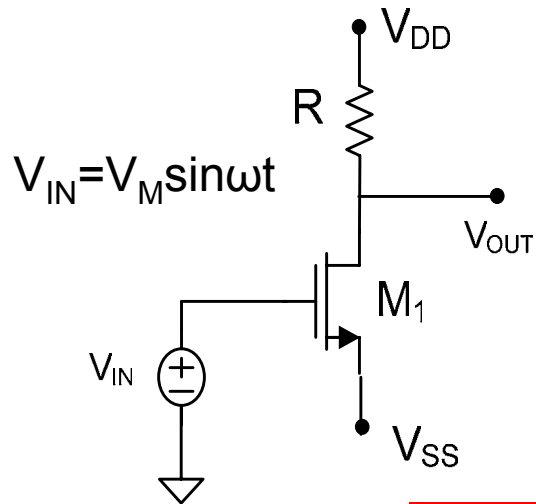

Assume  $M_1$  operating in saturation region

$$V_{OUT} = \left\{ V_{DD} - \frac{\mu C_{ox} W}{2L} [V_{SS} + V_T]^2 R \right\} + \left\{ \frac{\mu C_{ox} W}{L} [V_{SS} + V_T] R \right\} V_M \sin \omega t$$


*Quiescent Output*
*ss Voltage Gain*

$$A_v = \frac{\mu C_{ox} W}{L} [V_{SS} + V_T] R$$

*But – this expression gives little insight into how large the gain is !*



# Small signal analysis example

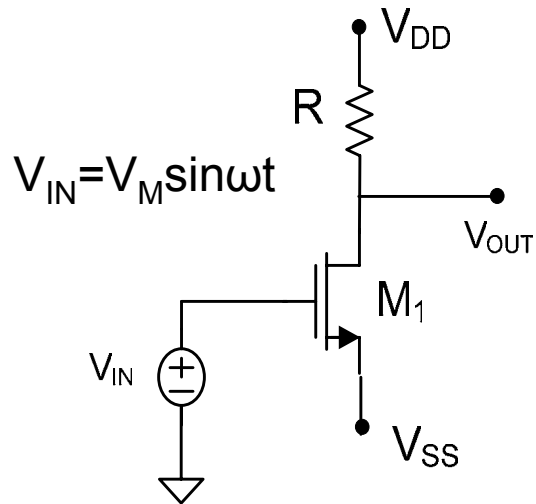

$$V_{OUT} = \left\{ V_{DD} - \frac{\mu C_{ox} W}{2L} [V_{SS} + V_T]^2 R \right\} + \left\{ \frac{\mu C_{ox} W}{L} [V_{SS} + V_T] R \right\} V_M \sin \omega t$$

$$A_v = \frac{\mu C_{ox} W}{L} [V_{SS} + V_T] R$$

But recall:


$$I_{DQ} = \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$

Thus, substituting from the expression for  $I_{DQ}$  we obtain

$$A_v = \frac{2I_{DQ} R}{[V_{SS} + V_T]}$$

Note this is negative since  $V_{SS} + V_T < 0$

# Small signal analysis example

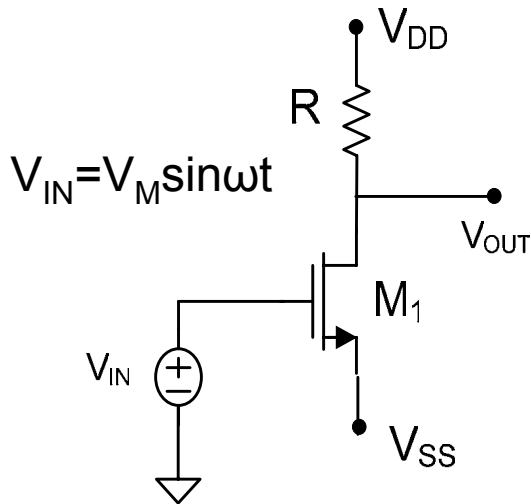

$$A_v = \frac{2I_{DQ} R}{[V_{SS} + V_T]}$$

*Observe the small signal voltage gain is twice the Quiescent voltage across  $R$  divided by  $V_{SS} + V_T$*

- This analysis which required linearization of a nonlinear output voltage is quite tedious.
- This approach becomes unwieldy for even slightly more complicated circuits
- A much easier approach based upon the development of small signal models will provide the same results, provide more insight into both analysis and design, and result in a dramatic reduction in computational requirements

# Small-signal Operation of Nonlinear Circuits

- Small-signal principles
- Example Circuit
- Small-Signal Models
- Small-Signal Analysis of Nonlinear Circuits

*Solution for the example was based upon solving the nonlinear circuit for  $V_{OUT}$  and then linearizing the solution by doing a Taylor's series expansion*

- Solution of nonlinear equations very involved with two or more nonlinear devices*
- Taylor's series linearization can get very tedious if multiple nonlinear devices are present*

**Standard Approach to small-signal analysis of nonlinear networks**

- 1. Solve nonlinear network*
- 2. Linearize solution*

**Alternative Approach to small-signal analysis of nonlinear networks**

- 1. Linearize nonlinear devices*
- 2. Replace all devices with small-signal equivalent*
- 3. Solve linear small-signal network*

## Alternative Approach to small-signal analysis of nonlinear networks

1. *Linearize nonlinear devices*
2. *Replace all devices with small-signal equivalent*
3. *Solve linear small-signal network*

- **Must only develop linearized model once for any nonlinear device**

*e.g. once for a MOSFET, once for a JFET, and once for a BJT*

*Linearized model for nonlinear device termed “small-signal model”*


*derivation of small-signal model for most nonlinear devices is less complicated than solving even one simple nonlinear circuit*

- **Solution of linear network much easier than solution of nonlinear network**


# Standard Approach to small-signal analysis of nonlinear networks

1. *Linearize nonlinear devices*
2. *Replace all devices with small-signal equivalent*
3. *Solve linear small-signal network*
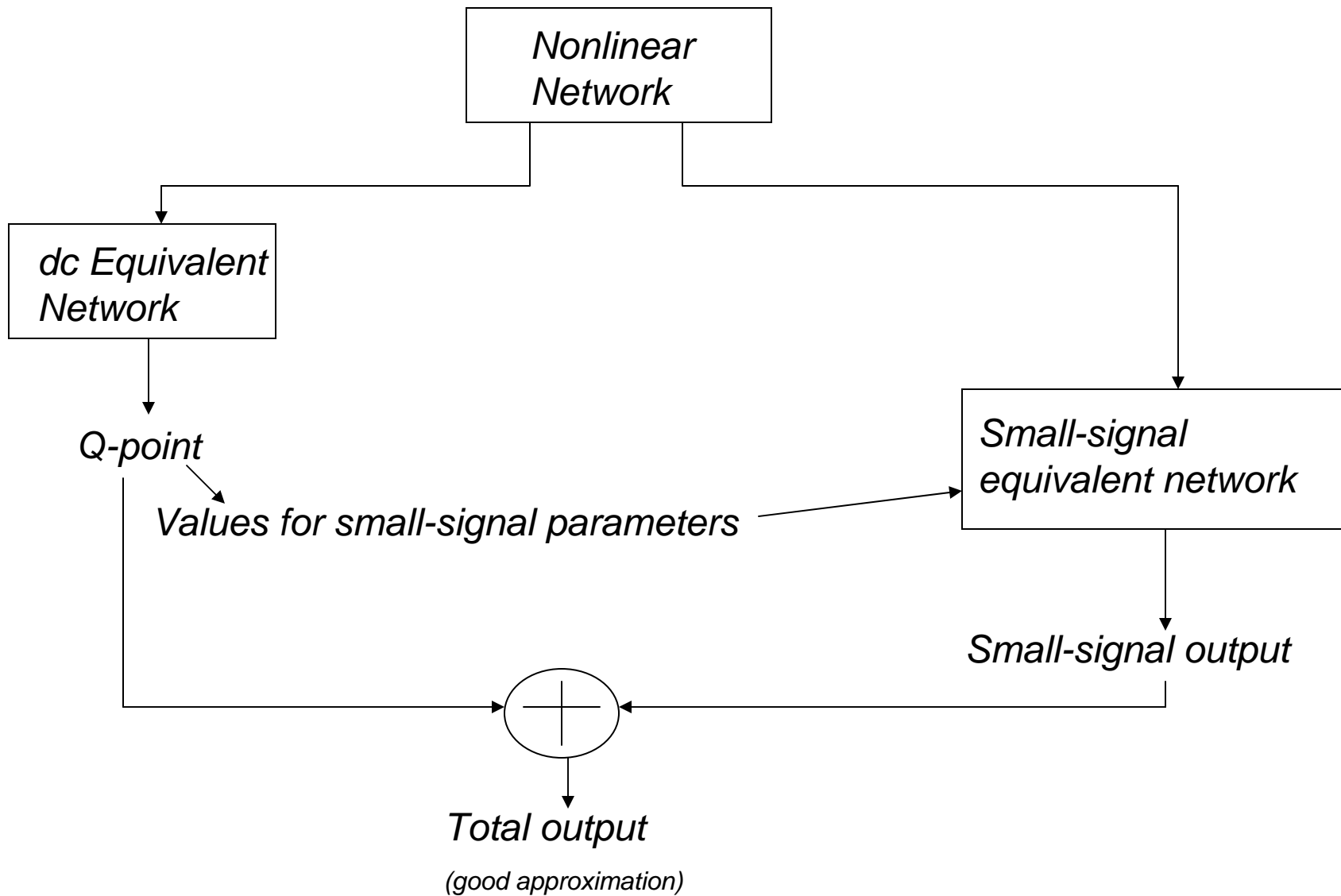
# Standard Approach to analysis of nonlinear networks





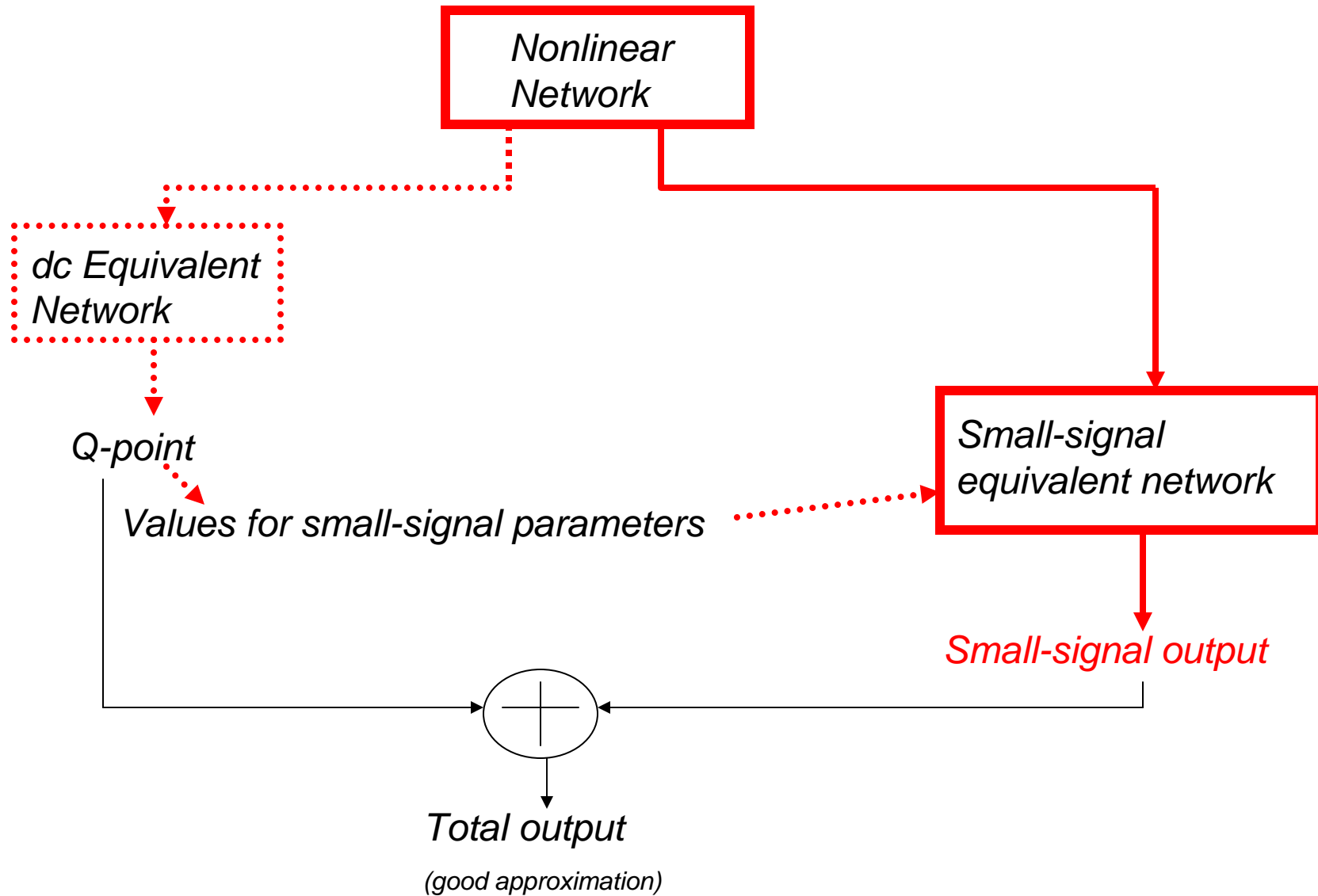
# Standard Approach to small-signal analysis of nonlinear networks







## *Linearized nonlinear devices*

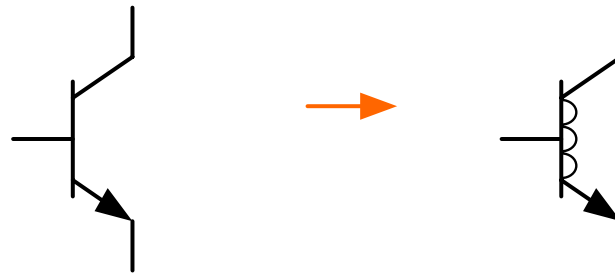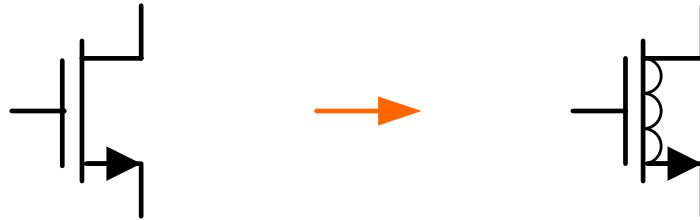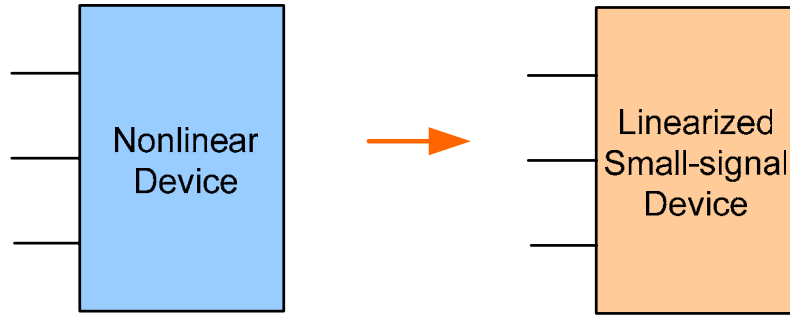

*Example:*

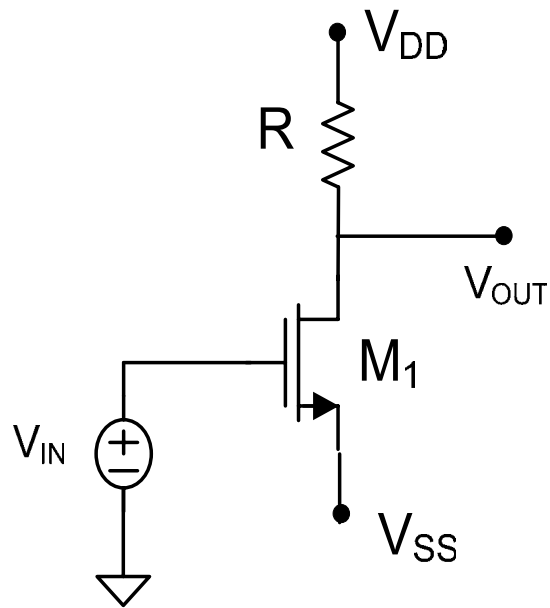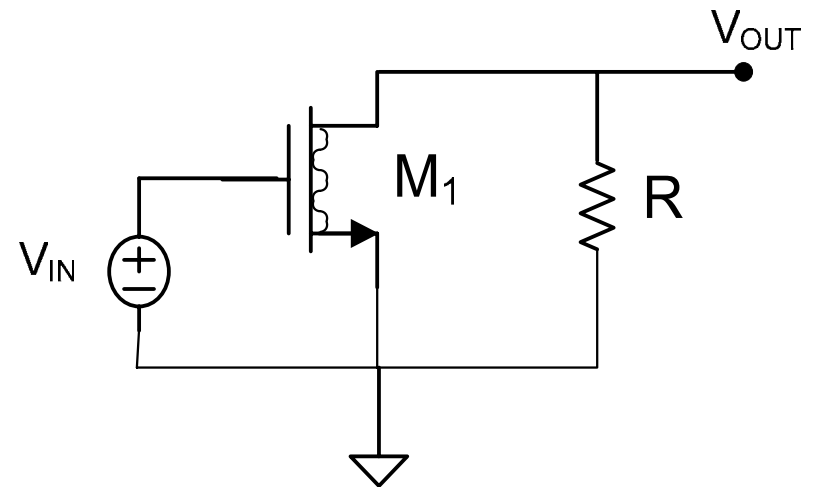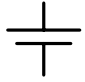

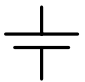














*Nonlinear network*




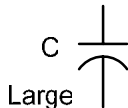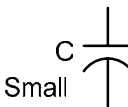
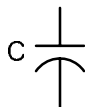

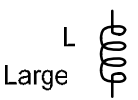













*Linearized small-signal network*


# Dc and small-signal equivalent elements

	Element	ss equivalent	dc equivalent
dc Voltage Source	$V_{DC}$ 		$V_{DC}$ 
ac Voltage Source	$V_{AC}$ 	$V_{AC}$ 	
dc Current Source	$I_{DC}$ 		$I_{DC}$ 
ac Current Source	$I_{AC}$ 	$I_{AC}$ 	
Resistor	$R$ 	$R$ 	$R$ 
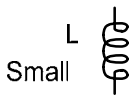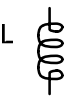
# Dc and small-signal equivalent elements

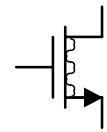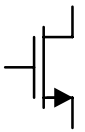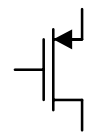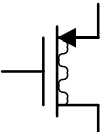
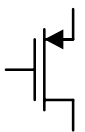
	Element	ss equivalent	dc equivalent
Capacitors	<p>C</p> <p>Large</p> 		
	<p>C</p> <p>Small</p> 	<p>C</p> 	
Inductors	<p>L</p> <p>Large</p> 		
	<p>L</p> <p>Small</p> 	<p>L</p> 	
MOS Transistors			 <p>Simplified</p>
			 <p>Simplified</p>
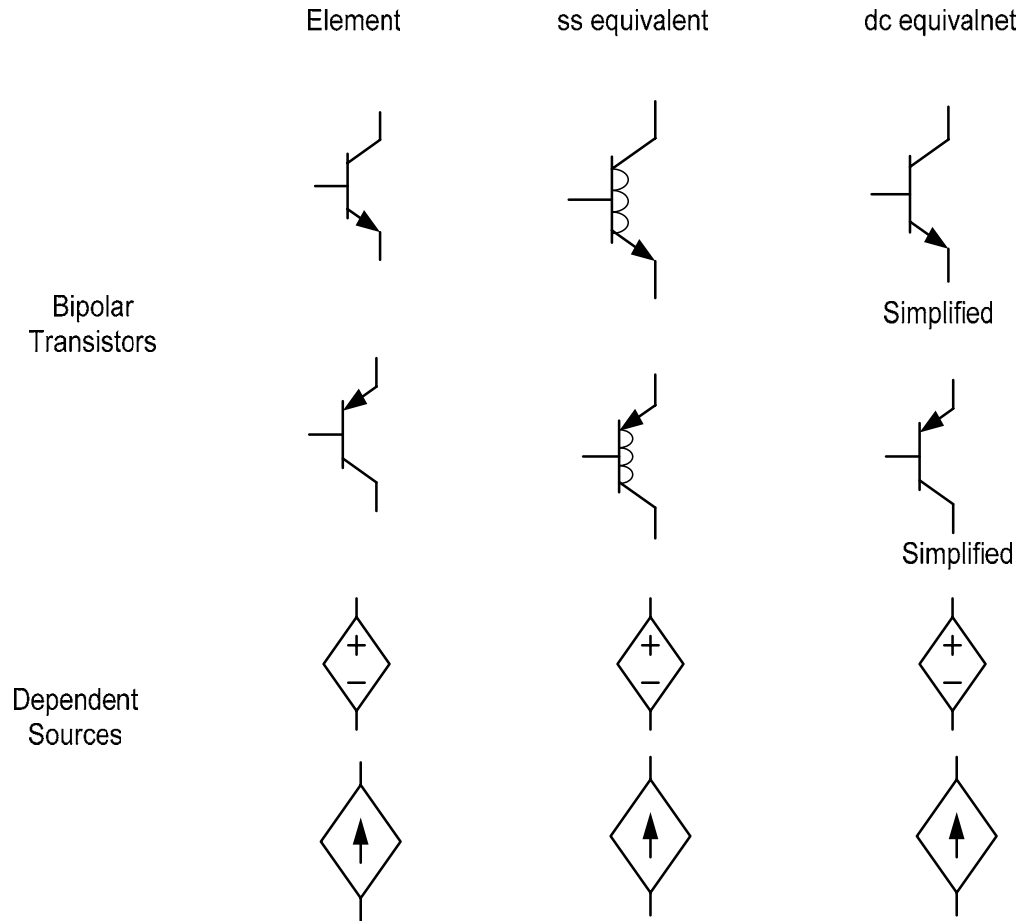
# Dc and small-signal equivalent elements




How is the small-signal equivalent circuit obtained from the nonlinear circuit?

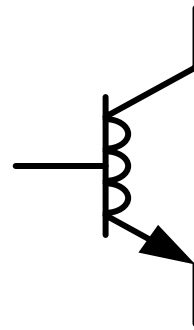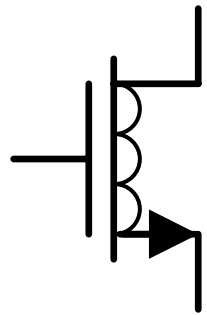*What is the small-signal equivalent of the MOSFET and BJT ?*



# Small-Signal Model

Consider 4-terminal network

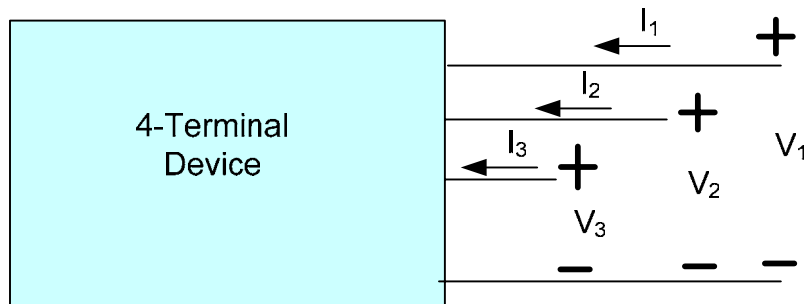

$$\left. \begin{aligned} I_1 &= f_1(V_1, V_2, V_3) \\ I_2 &= f_2(V_1, V_2, V_3) \\ I_3 &= f_3(V_1, V_2, V_3) \end{aligned} \right\}$$

Define

$$i_1 = I_1 - I_{1Q}$$

$$i_2 = I_2 - I_{2Q}$$

$$i_3 = I_3 - I_{3Q}$$

$$u_1 = V_1 - V_{1Q}$$


$$u_2 = V_2 - V_{2Q}$$

$$u_3 = V_3 - V_{3Q}$$

Small signal model is that which represents the relationship between the small signal voltages and the small signal currents

# Small-Signal Model

Consider 4-terminal network

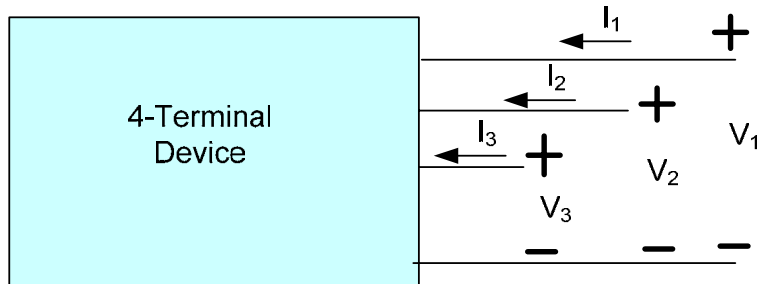

$$\left. \begin{aligned} \dot{i}_1 &= g_1(v_1, v_2, v_3) \\ \dot{i}_2 &= g_2(v_1, v_2, v_3) \\ \dot{i}_3 &= g_3(v_1, v_2, v_3) \end{aligned} \right\}$$

Small signal model is that which represents the relationship between the small signal voltages and the small signal currents

For small signals, this relationship should be linear

Can be thought of as a change in coordinate systems from the large signal coordinate system to the small-signal coordinate system



# Recall for a function of one variable

$$y = f(x)$$

Taylor's Series Expansion about the point  $x_0$

$$y = f(x) = f(x)|_{x=x_0} + \left. \frac{\partial f}{\partial x} \right|_{x=x_0} (x - x_0) + \left. \frac{\partial^2 f}{\partial x^2} \right|_{x=x_0} \frac{1}{2!} (x - x_0)^2 + \dots$$

If  $x - x_0$  is small

$$y \cong f(x)|_{x=x_0} + \left. \frac{\partial f}{\partial x} \right|_{x=x_0} (x - x_0)$$

$$y \cong y_0 + \left. \frac{\partial f}{\partial x} \right|_{x=x_0} (x - x_0)$$

# Recall for a function of one variable

$$y = f(x)$$

If  $x - x_0$  is small

$$y \cong y_0 + \left. \frac{\partial f}{\partial x} \right|_{x=x_0} (x - x_0)$$

$$y - y_0 = \left. \frac{\partial f}{\partial x} \right|_{x=x_0} (x - x_0)$$

If we define the small signal variables as

$$\boldsymbol{y} = y - y_0$$

$$\boldsymbol{x} = x - x_0$$

# Recall for a function of one variable

$$y = f(x)$$

If  $x-x_0$  is small

$$y - y_0 = \left. \frac{\partial f}{\partial x} \right|_{x=x_0} (x - x_0)$$

If we define the small signal variables as

$$\mathbf{y} = y - y_0$$


$$\mathbf{x} = x - x_0$$

Then

$$\mathbf{y} = \left. \frac{\partial f}{\partial x} \right|_{x=x_0} \mathbf{x}$$

This relationship is linear !

## Consider 4-terminal network

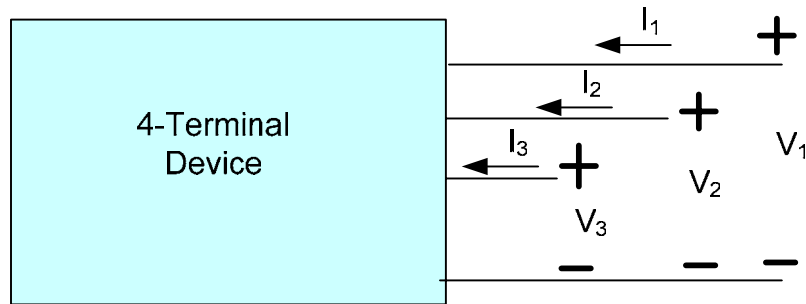

$$\left. \begin{aligned} \mathbf{I}_1 &= \mathbf{f}_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3) \\ \mathbf{I}_2 &= \mathbf{f}_2(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3) \\ \mathbf{I}_3 &= \mathbf{f}_3(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3) \end{aligned} \right\}$$

Nonlinear network characterized by 3 functions each functions of 3 variables

Consider now 3 functions each functions of 3 variables

$$\left. \begin{aligned} \mathbf{l}_1 &= \mathbf{f}_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3) \\ \mathbf{l}_2 &= \mathbf{f}_2(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3) \\ \mathbf{l}_3 &= \mathbf{f}_3(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3) \end{aligned} \right\}$$

Define

$$\bar{\mathbf{V}}_Q = \begin{bmatrix} \mathbf{V}_{1Q} \\ \mathbf{V}_{2Q} \\ \mathbf{V}_{3Q} \end{bmatrix}$$

Consider now 3 functions each functions of 3 variables

$$\left. \begin{aligned} \mathbf{I}_1 &= \mathbf{f}_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3) \\ \mathbf{I}_2 &= \mathbf{f}_2(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3) \\ \mathbf{I}_3 &= \mathbf{f}_3(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3) \end{aligned} \right\}$$

Define

$$\bar{\mathbf{V}}_Q = \begin{bmatrix} \mathbf{V}_{1Q} \\ \mathbf{V}_{2Q} \\ \mathbf{V}_{3Q} \end{bmatrix}$$

$$\mathbf{I}_1 = \mathbf{f}_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3) \cong \mathbf{f}_1(\mathbf{V}_{1Q}, \mathbf{V}_{2Q}, \mathbf{V}_{3Q}) + \left. \frac{\partial \mathbf{f}_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_1} \right|_{\bar{\mathbf{V}}=\bar{\mathbf{V}}_Q} (\mathbf{V}_1 - \mathbf{V}_{1Q}) + \left. \frac{\partial \mathbf{f}_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_2} \right|_{\bar{\mathbf{V}}=\bar{\mathbf{V}}_Q} (\mathbf{V}_2 - \mathbf{V}_{2Q}) + \left. \frac{\partial \mathbf{f}_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_3} \right|_{\bar{\mathbf{V}}=\bar{\mathbf{V}}_Q} (\mathbf{V}_3 - \mathbf{V}_{3Q})$$

$$\mathbf{I}_1 - \mathbf{I}_{1Q} = \left. \frac{\partial \mathbf{f}_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_1} \right|_{\bar{\mathbf{V}}=\bar{\mathbf{V}}_Q} (\mathbf{V}_1 - \mathbf{V}_{1Q}) + \left. \frac{\partial \mathbf{f}_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_2} \right|_{\bar{\mathbf{V}}=\bar{\mathbf{V}}_Q} (\mathbf{V}_2 - \mathbf{V}_{2Q}) + \left. \frac{\partial \mathbf{f}_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_3} \right|_{\bar{\mathbf{V}}=\bar{\mathbf{V}}_Q} (\mathbf{V}_3 - \mathbf{V}_{3Q})$$

Consider now 3 functions each functions of 3 variables

$$I_1 - I_{1Q} = \left. \frac{\partial f_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_1} \right|_{\bar{\mathbf{v}} = \bar{\mathbf{v}}_Q} (\mathbf{V}_1 - \mathbf{V}_{1Q}) + \left. \frac{\partial f_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_2} \right|_{\bar{\mathbf{v}} = \bar{\mathbf{v}}_Q} (\mathbf{V}_2 - \mathbf{V}_{2Q}) + \left. \frac{\partial f_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_3} \right|_{\bar{\mathbf{v}} = \bar{\mathbf{v}}_Q} (\mathbf{V}_3 - \mathbf{V}_{3Q})$$

$$y_{11} = \left. \frac{\partial f_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_1} \right|_{\bar{\mathbf{v}} = \bar{\mathbf{v}}_Q}$$

$$y_{12} = \left. \frac{\partial f_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_2} \right|_{\bar{\mathbf{v}} = \bar{\mathbf{v}}_Q}$$

$$y_{13} = \left. \frac{\partial f_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_3} \right|_{\bar{\mathbf{v}} = \bar{\mathbf{v}}_Q}$$

$$\dot{i}_1 = I_1 - I_{1Q}$$

$$\dot{i}_2 = I_2 - I_{2Q}$$

$$\dot{i}_3 = I_3 - I_{3Q}$$

$$u_1 = \mathbf{V}_1 - \mathbf{V}_{1Q}$$

$$u_2 = \mathbf{V}_2 - \mathbf{V}_{2Q}$$

$$u_3 = \mathbf{V}_3 - \mathbf{V}_{3Q}$$

Consider now 3 functions each functions of 3 variables

$$I_1 - I_{1Q} = \left. \frac{\partial f_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_1} \right|_{\bar{\mathbf{v}} = \bar{\mathbf{v}}_Q} (\mathbf{V}_1 - \mathbf{V}_{1Q}) + \left. \frac{\partial f_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_2} \right|_{\bar{\mathbf{v}} = \bar{\mathbf{v}}_Q} (\mathbf{V}_2 - \mathbf{V}_{2Q}) + \left. \frac{\partial f_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_3} \right|_{\bar{\mathbf{v}} = \bar{\mathbf{v}}_Q} (\mathbf{V}_3 - \mathbf{V}_{3Q})$$

$$\mathbf{i}_1 = y_{11} \mathbf{u}_1 + y_{12} \mathbf{u}_2 + y_{13} \mathbf{u}_3$$

This is now a linear relationship between the small signal electrical variables



Consider now 3 functions each functions of 3 variables

$$\dot{i}_1 = y_{11}u_1 + y_{12}u_2 + y_{13}u_3$$

Lets now extend this to  $I_2$  and  $I_3$

Define 
$$y_{ij} = \left. \frac{\partial f_i(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_j} \right|_{\bar{\mathbf{v}} = \bar{\mathbf{v}}_Q}$$


$$\dot{i}_1 = y_{11}u_1 + y_{12}u_2 + y_{13}u_3$$

$$\dot{i}_2 = y_{21}u_1 + y_{22}u_2 + y_{23}u_3$$

$$\dot{i}_3 = y_{31}u_1 + y_{32}u_2 + y_{33}u_3$$

This is a small-signal model of a 4-terminal network and it is linear  
9 small-signal parameters characterize the linear 4-terminal network  
Small-signal model parameters dependent upon Q-point !

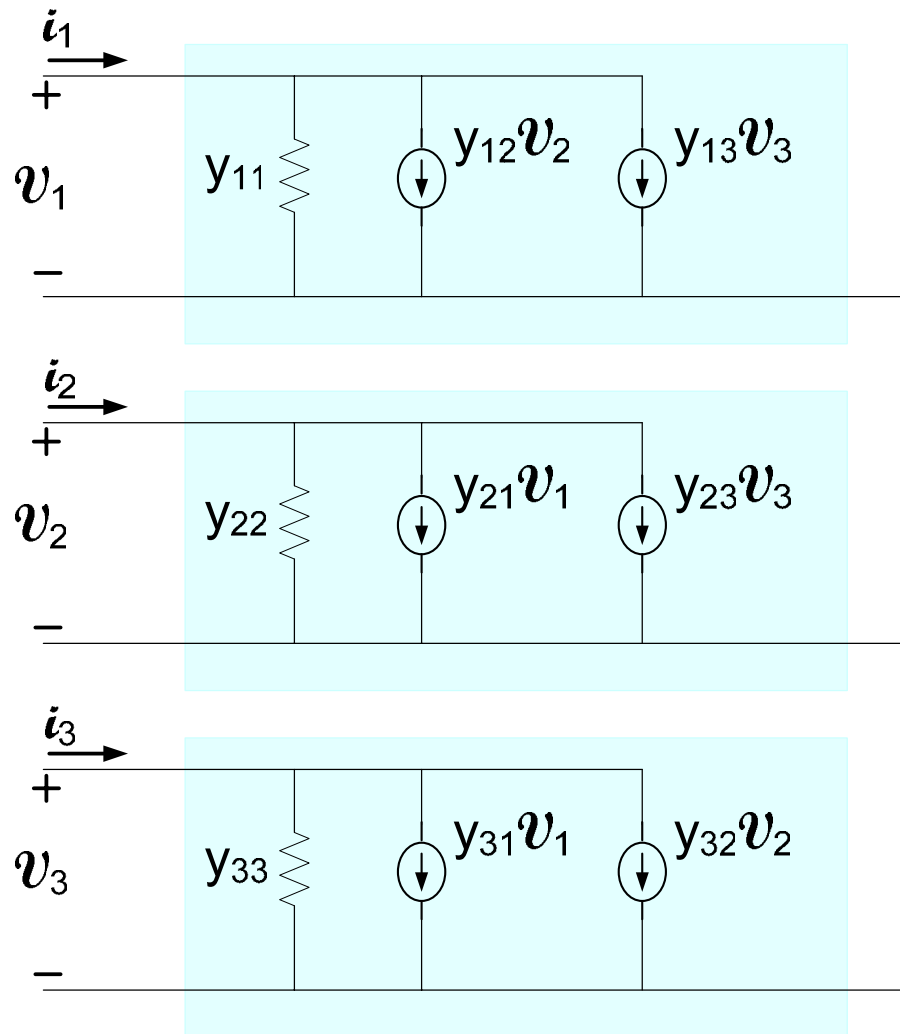
## A small-signal equivalent circuit of a 4-terminal nonlinear network



$$y_{ij} = \left. \frac{\partial f_i(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_j} \right|_{\bar{\mathbf{V}} = \bar{\mathbf{V}}_Q}$$

Equivalent circuit is not unique
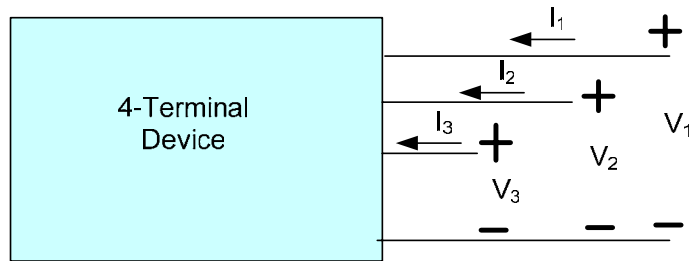
## 4-terminal small-signal network summary




$$\left. \begin{aligned} \mathbf{I}_1 &= \mathbf{f}_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3) \\ \mathbf{I}_2 &= \mathbf{f}_2(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3) \\ \mathbf{I}_3 &= \mathbf{f}_3(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3) \end{aligned} \right\}$$

### Small signal model:


$$\begin{aligned} \mathbf{i}_1 &= y_{11} \mathbf{u}_1 + y_{12} \mathbf{u}_2 + y_{13} \mathbf{u}_3 \\ \mathbf{i}_2 &= y_{21} \mathbf{u}_1 + y_{22} \mathbf{u}_2 + y_{23} \mathbf{u}_3 \\ \mathbf{i}_3 &= y_{31} \mathbf{u}_1 + y_{32} \mathbf{u}_2 + y_{33} \mathbf{u}_3 \end{aligned}$$

$$\mathbf{y}_{ij} = \left. \frac{\partial \mathbf{f}_i(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_j} \right|_{\bar{\mathbf{V}} = \bar{\mathbf{V}}_Q}$$

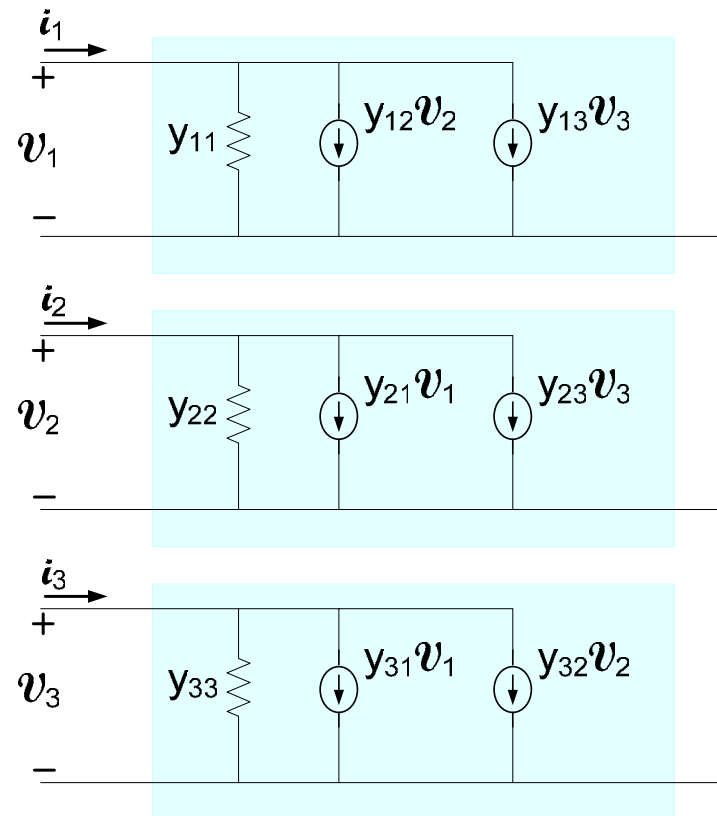

Consider 3-terminal network

# Small-Signal Model

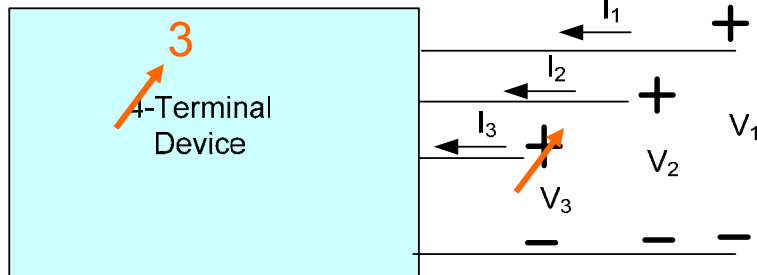

$$\left. \begin{aligned} \dot{i}_1 &= g_1(v_1, v_2, v_3) \\ \dot{i}_2 &= g_2(v_1, v_2, v_3) \\ \dot{i}_3 &= g_3(v_1, v_2, v_3) \end{aligned} \right\}$$

$$\dot{i}_1 = y_{11}v_1 + y_{12}v_2 + y_{13}v_3$$


$$\dot{i}_2 = y_{21}v_1 + y_{22}v_2 + y_{23}v_3$$

$$\dot{i}_3 = y_{31}v_1 + y_{32}v_2 + y_{33}v_3$$

$$y_{ij} = \left. \frac{\partial f_i(v_1, v_2, v_3)}{\partial v_j} \right|_{\bar{v} = \bar{v}_0}$$

Consider 3-terminal network

# Small-Signal Model

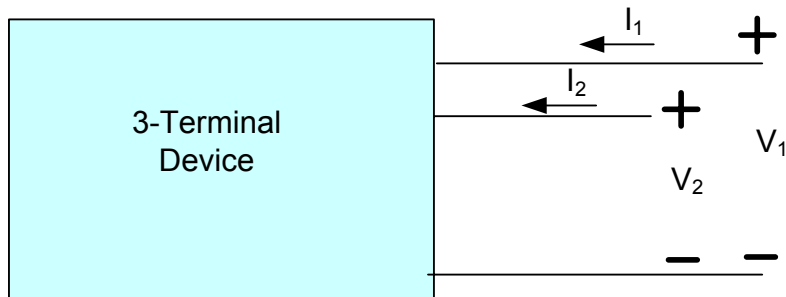

$$\left. \begin{aligned} I_1 &= f_1(V_1, V_2) \\ I_2 &= f_2(V_1, V_2) \end{aligned} \right\}$$

Define

$$i_1 = I_1 - I_{1Q}$$

$$u_1 = V_1 - V_{1Q}$$


$$i_2 = I_2 - I_{2Q}$$

$$u_2 = V_2 - V_{2Q}$$

Small signal model is that which represents the relationship between the small signal voltages and the small signal currents

Consider 3-terminal network

# Small-Signal Model

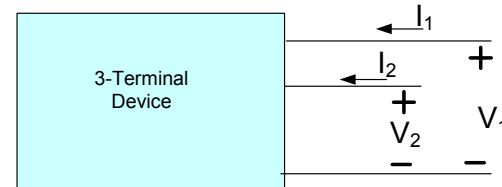


$$\begin{aligned} i_1 &= y_{11} v_1 + y_{12} v_2 \\ i_2 &= y_{21} v_1 + y_{22} v_2 \end{aligned}$$

$$y_{ij} = \left. \frac{\partial f_i(\mathbf{V}_1, \mathbf{V}_2)}{\partial V_j} \right|_{\bar{\mathbf{v}} = \bar{\mathbf{v}}_Q}$$


$$\bar{\mathbf{v}} = \begin{pmatrix} V_{1Q} \\ V_{2Q} \end{pmatrix}$$

A Small Signal Equivalent Circuit

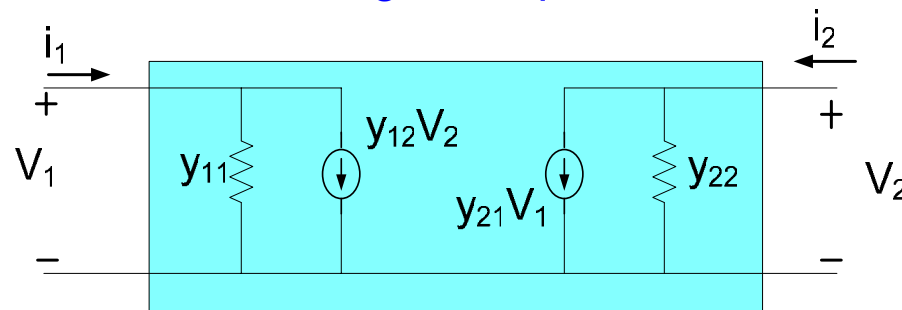

*4 small-signal parameters characterize this 3-terminal (two-port) linear network*  
*Small signal parameters dependent upon Q-point*
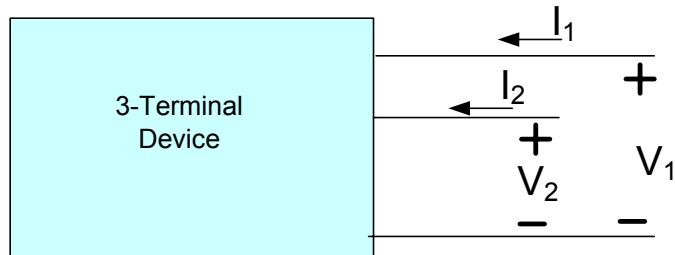
### 3-terminal small-signal network summary




$$\left. \begin{aligned} \mathbf{I}_1 &= \mathbf{f}_1(\mathbf{V}_1, \mathbf{V}_2) \\ \mathbf{I}_2 &= \mathbf{f}_2(\mathbf{V}_1, \mathbf{V}_2) \end{aligned} \right\}$$

### Small signal model:


$$\begin{aligned} \mathbf{i}_1 &= y_{11} \mathbf{v}_1 + y_{12} \mathbf{v}_2 \\ \mathbf{i}_2 &= y_{21} \mathbf{v}_1 + y_{22} \mathbf{v}_2 \end{aligned}$$

$$\mathbf{y}_{ij} = \left. \frac{\partial \mathbf{f}_i(\mathbf{V}_1, \mathbf{V}_2)}{\partial \mathbf{V}_j} \right|_{\bar{\mathbf{v}} = \bar{\mathbf{v}}_q}$$

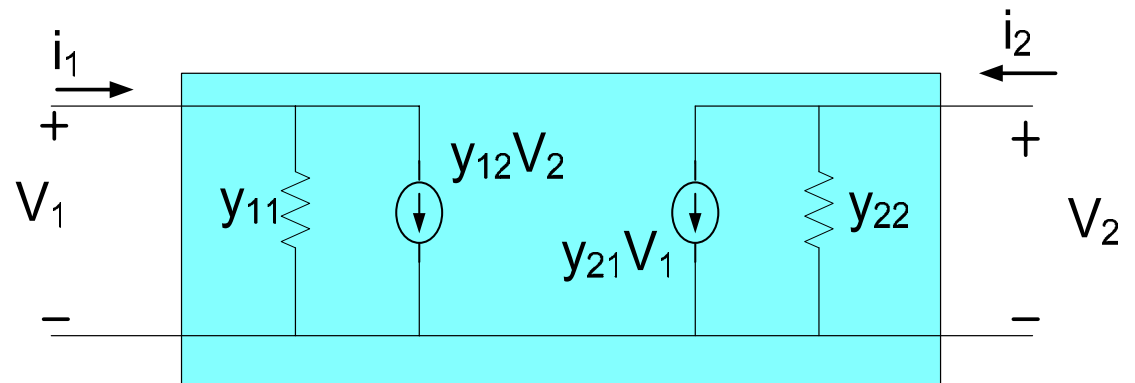

Consider 2-terminal network

# Small-Signal Model

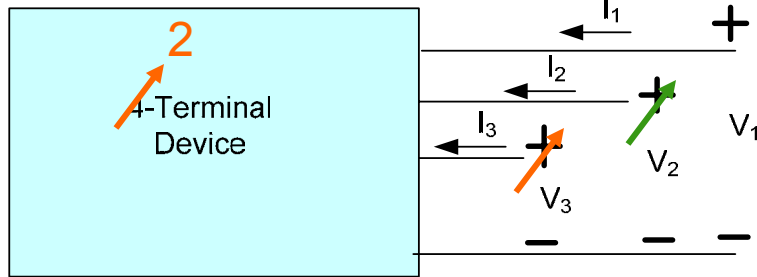

$$\left. \begin{aligned} \dot{i}_1 &= g_1(v_1, v_2, v_3) \\ \dot{i}_2 &= g_2(v_1, v_2, v_3) \\ \dot{i}_3 &= g_3(v_1, v_2, v_3) \end{aligned} \right\}$$

$$\dot{i}_1 = y_{11}v_1 + y_{12}v_2 + y_{13}v_3$$

$$\dot{i}_2 = y_{21}v_1 + y_{22}v_2 + y_{23}v_3$$


$$\dot{i}_3 = y_{31}v_1 + y_{32}v_2 + y_{33}v_3$$

$$y_{ij} = \left. \frac{\partial f_i(v_1, v_2, v_3)}{\partial v_j} \right|_{\bar{v} = \bar{v}_0}$$



Consider 2-terminal network

# Small-Signal Model

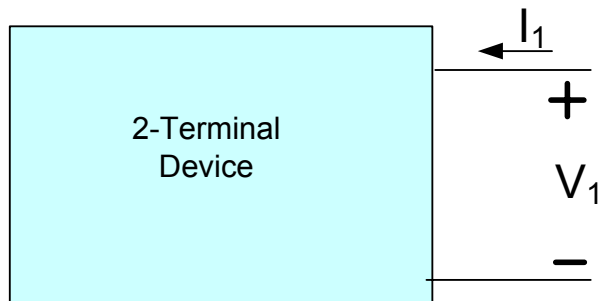

$$I_1 = f_1(V_1)$$

Define


$$i_1 = I_1 - I_{1Q}$$

$$v_1 = V_1 - V_{1Q}$$

Small signal model is that which represents the relationship between the small signal voltages and the small signal currents

Consider 2-terminal network


# Small-Signal Model

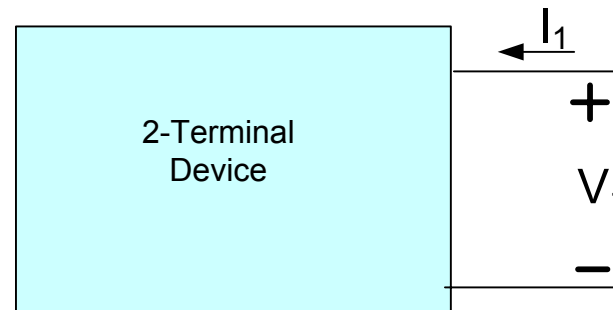


$$\mathbf{i}_1 = y_{11} \mathbf{v}_1$$

$$y_{11} = \left. \frac{\partial f_1(V_1)}{\partial V_1} \right|_{\bar{V} = \bar{V}_Q} \quad \bar{V} = V_{1Q}$$


A Small Signal Equivalent Circuit

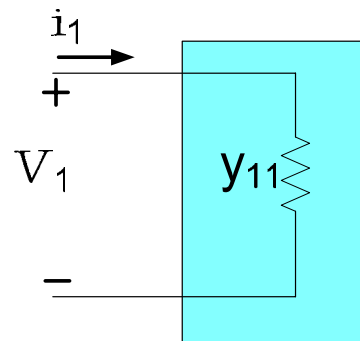

# Small Signal Model of MOSFET

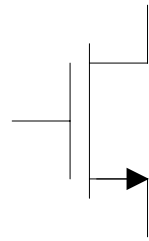

*3-terminal device*

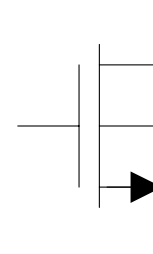


*4-terminal device*

*MOSFET is actually a 4-terminal device but for many applications acceptable predictions of performance can be obtained by treating it as a 3-terminal device by neglecting the bulk terminal*

*In this course, we have been treating it as a 3-terminal device and in this lecture will develop the small-signal model by treating it as a 3-terminal device*


# Small Signal Model of MOSFET

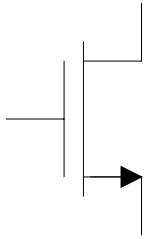

Large Signal Model

$$I_G = 0$$

3-terminal device

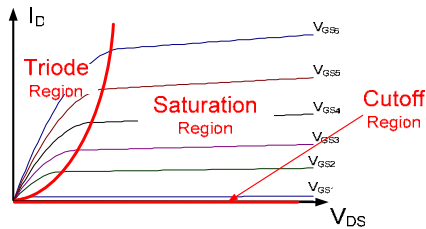

$$I_D = \begin{cases} 0 & V_{GS} \leq V_T \\ \mu C_{OX} \frac{W}{L} \left( V_{GS} - V_T - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} \geq V_T, V_{DS} < V_{GS} - V_T \\ \mu C_{OX} \frac{W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) & V_{GS} \geq V_T, V_{DS} \geq V_{GS} - V_T \end{cases}$$

*MOSFET is usually operated in saturation region in linear applications where a small-signal model is needed so will develop the small-signal model in the saturation region*

# Small Signal Model of MOSFET

$$I_1 = f_1(V_1, V_2) \quad \longleftrightarrow \quad I_G = 0$$

$$I_2 = f_2(V_1, V_2) \quad \longleftrightarrow \quad I_D = \mu C_{\text{ox}} \frac{W}{2L} (V_{\text{GS}} - V_{\text{T}})^2 (1 + \lambda V_{\text{DS}})$$

*Small-signal model:*

$$y_{ij} = \left. \frac{\partial f_i(V_1, V_2)}{\partial V_j} \right|_{\bar{V}=\bar{V}_Q}$$

$$y_{11} = \left. \frac{\partial I_G}{\partial V_{\text{GS}}} \right|_{\bar{V}=\bar{V}_Q}$$

$$y_{12} = \left. \frac{\partial I_G}{\partial V_{\text{DS}}} \right|_{\bar{V}=\bar{V}_Q}$$

$$y_{21} = \left. \frac{\partial I_D}{\partial V_{\text{GS}}} \right|_{\bar{V}=\bar{V}_Q}$$

$$y_{22} = \left. \frac{\partial I_D}{\partial V_{\text{DS}}} \right|_{\bar{V}=\bar{V}_Q}$$

# Small Signal Model of MOSFET

$$I_1 = f_1(V_1, V_2) \quad \longleftrightarrow \quad I_G = 0$$

$$I_2 = f_2(V_1, V_2) \quad \longleftrightarrow \quad I_D = \mu C_{\text{ox}} \frac{W}{2L} (V_{\text{GS}} - V_{\text{T}})^2 (1 + \lambda V_{\text{DS}})$$

*Small-signal model:*

$$y_{11} = \left. \frac{\partial I_G}{\partial V_{\text{GS}}} \right|_{\bar{V}=\bar{V}_Q} = 0$$


$$y_{12} = \left. \frac{\partial I_G}{\partial V_{\text{DS}}} \right|_{\bar{V}=\bar{V}_Q} = 0$$

$$y_{21} = \left. \frac{\partial I_D}{\partial V_{\text{GS}}} \right|_{\bar{V}=\bar{V}_Q} = 2\mu C_{\text{ox}} \frac{W}{2L} (V_{\text{GS}} - V_{\text{T}})^1 (1 + \lambda V_{\text{DS}}) \Big|_{\bar{V}=\bar{V}_Q} = \mu C_{\text{ox}} \frac{W}{L} (V_{\text{GSQ}} - V_{\text{T}}) (1 + \lambda V_{\text{DSQ}})$$

$$y_{21} \cong \mu C_{\text{ox}} \frac{W}{L} (V_{\text{GSQ}} - V_{\text{T}})$$


$$y_{22} = \left. \frac{\partial I_D}{\partial V_{\text{DS}}} \right|_{\bar{V}=\bar{V}_Q} = \mu C_{\text{ox}} \frac{W}{2L} (V_{\text{GS}} - V_{\text{T}})^2 \lambda \Big|_{\bar{V}=\bar{V}_Q} \cong \lambda I_{\text{DQ}}$$

# Small Signal Model of MOSFET

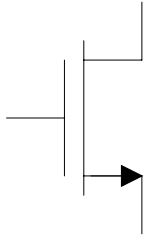

$$I_G = 0$$
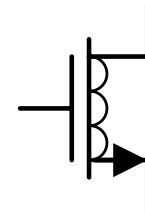
$$I_D = \mu C_{OX} \frac{W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$




$$y_{12} = 0$$

$$y_{11} = 0$$


$$y_{21} \cong \mu C_{OX} \frac{W}{L} (V_{GSQ} - V_T)$$

$$y_{22} \cong \lambda I_{DQ}$$
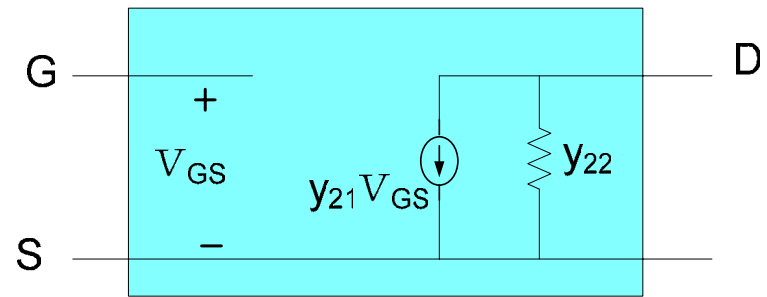
$$\begin{aligned} i_G &= y_{11} v_{GS} + y_{12} v_{DS} \\ i_D &= y_{21} v_{GS} + y_{22} v_{DS} \end{aligned}$$





# Small Signal Model of MOSFET

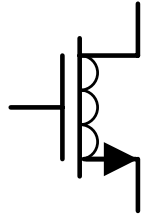

by convention,  $y_{21} = g_m$ ,  $y_{22} = g_o$

$$\therefore y_{21} \cong g_m = \mu C_{\text{ox}} \frac{W}{L} (V_{\text{GSQ}} - V_T)$$
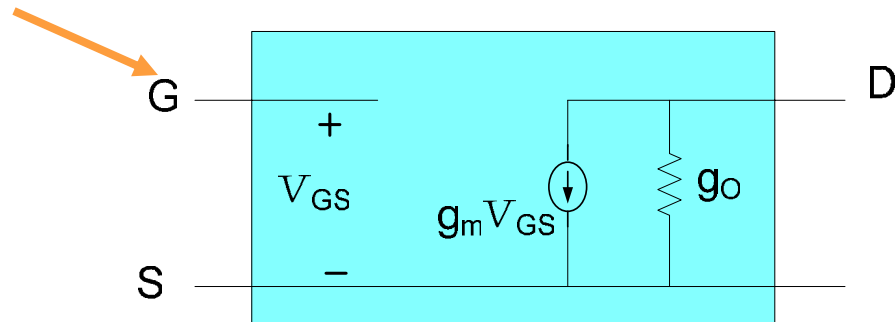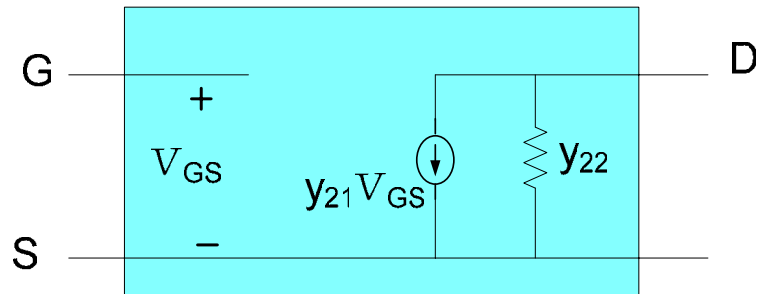
$$y_{22} = g_o \cong \lambda I_{\text{DQ}}$$




$$i_G = 0$$

$$i_D = g_m v_{GS} + g_o v_{DS}$$




# Small Signal Model of MOSFET

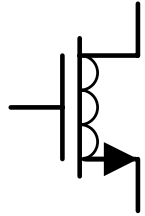

$$g_m = \mu C_{\text{ox}} \frac{W}{L} (V_{\text{GSQ}} - V_T)$$

$$g_o \cong \lambda I_{\text{DQ}}$$

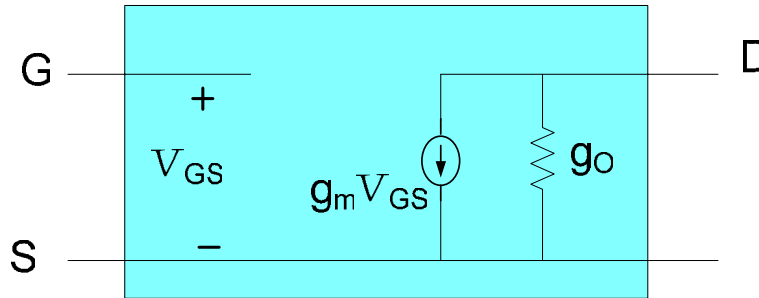

*Alternate equivalent expressions:*

$$I_{\text{DQ}} = \mu C_{\text{ox}} \frac{W}{2L} (V_{\text{GSQ}} - V_T)^2 (1 + \lambda V_{\text{DSQ}}) \cong \mu C_{\text{ox}} \frac{W}{2L} (V_{\text{GSQ}} - V_T)^2$$

$$g_m = \mu C_{\text{ox}} \frac{W}{L} (V_{\text{GSQ}} - V_T)$$

$$g_m = \sqrt{2\mu C_{\text{ox}} \frac{W}{L}} \cdot \sqrt{I_{\text{DQ}}}$$

$$g_m = \frac{2I_{\text{DQ}}}{V_{\text{GSQ}} - V_T}$$