


# EE 230

## Lecture 34

Small Signal Models  
Small Signal Analysis
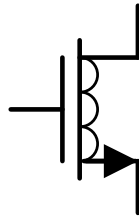
# Quiz 34

Determine the small-signal Model for a MOSFET with  $W=10\mu$ ,  $L=1\mu$  if operating with a quiescent gate-source voltage of 3V and a quiescent drain-source voltage of 8V. Assume  $\mu C_{ox}=100E-4A/V^2$ ,  $V_T=1V$ , and  $\lambda=0$ .



And the number is ?

1

3

8

5

4

?

2


6

9


7
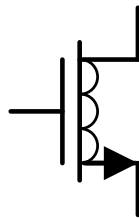
# Quiz 34

Determine the small-signal Model for a MOSFET with  $W=10\mu$ ,  $L=1\mu$  if operating with a quiescent gate-source voltage of 3V and a quiescent drain-source voltage of 8V. Assume  $\mu C_{OX}=100E-4A/V^2$ ,  $V_T=1V$ , and  $\lambda=0$ .



*Solution:*

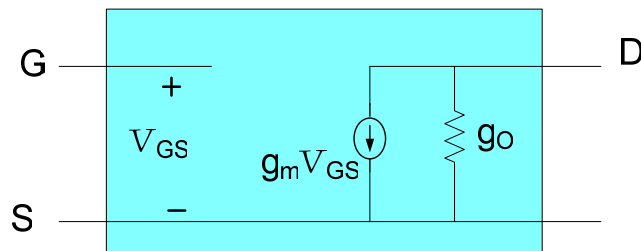

$$g_m = \mu C_{OX} \frac{W}{L} (V_{GSQ} - V_T)$$

$$g_o = \lambda I_{DQ}$$

$$g_m = 10^{-4} \frac{10}{1} (3 - 1) = 2E-3$$

$$g_o = 0$$

# Small-signal Operation of Nonlinear Circuits

- Small-signal principles
- Example Circuit
- Small-Signal Models
- Small-Signal Analysis of Nonlinear Circuits

## Review from Last Time:

*Solution for the example was based upon solving the nonlinear circuit for  $V_{OUT}$  and then linearizing the solution by doing a Taylor's series expansion*

- Solution of nonlinear equations very involved with two or more nonlinear devices*
- Taylor's series linearization can get very tedious if multiple nonlinear devices are present*

### **Standard Approach to small-signal analysis of nonlinear networks**

- 1. Solve nonlinear network*
- 2. Linearize solution*

### **Alternative Approach to small-signal analysis of nonlinear networks**

- 1. Linearize nonlinear devices*
- 2. Replace all devices with small-signal equivalent*
- 3. Solve linear small-signal network*

Review from Last Time:

## Alternative Approach to small-signal analysis of nonlinear networks

1. *Linearize nonlinear devices*
2. *Replace all devices with small-signal equivalent*
3. *Solve linear small-signal network*

- **Must only develop linearized model once for any nonlinear device**

*e.g. once for a MOSFET, once for a JFET, and once for a BJT*




*Linearized model for nonlinear device termed “small-signal model”*

*derivation of small-signal model for most nonlinear devices is less complicated than solving even one simple nonlinear circuit*

- **Solution of linear network much easier than solution of nonlinear network**

## Review from Last Time:




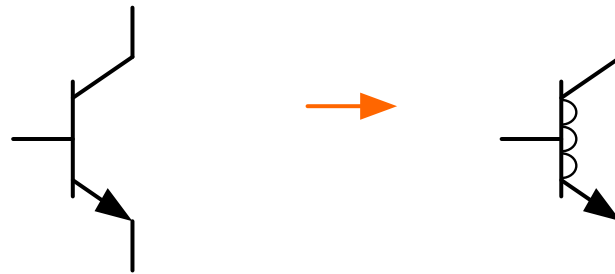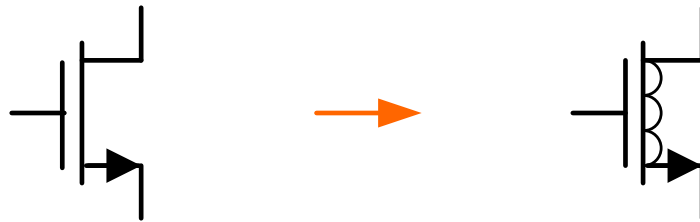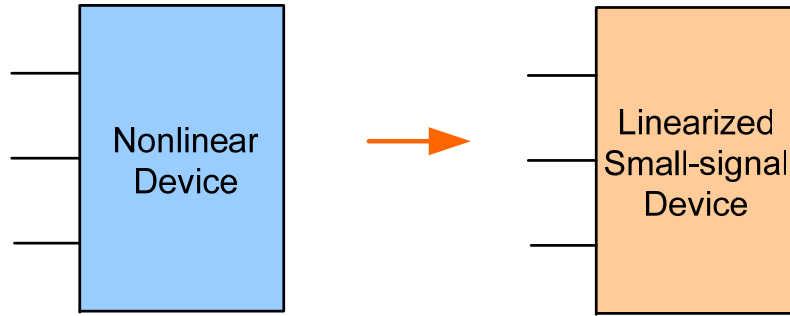







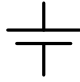



### *Linearized nonlinear devices*








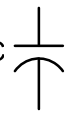
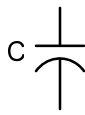





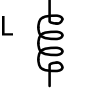

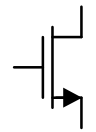
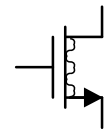
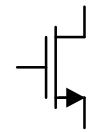
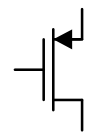
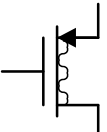
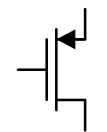
## Review from Last Time:

### Dc and small-signal equivalent elements

	Element	ss equivalent	dc equivalent
dc Voltage Source	$V_{DC}$ 		$V_{DC}$ 
ac Voltage Source	$V_{AC}$ 	$V_{AC}$ 	
dc Current Source	$I_{DC}$ 		$I_{DC}$ 
ac Current Source	$I_{AC}$ 	$I_{AC}$ 	
Resistor	$R$ 	$R$ 	$R$ 


# Review from Last Time:

## Dc and small-signal equivalent elements

	Element	ss equivalent	dc equivalent
Capacitors	<p>C</p> <p>Large</p> 		
	<p>C</p> <p>Small</p> 	<p>C</p> 	
Inductors	<p>L</p> <p>Large</p> 		
	<p>L</p> <p>Small</p> 	<p>L</p> 	
MOS Transistors			 <p>Simplified</p>
			 <p>Simplified</p>

# Review from Last Time:


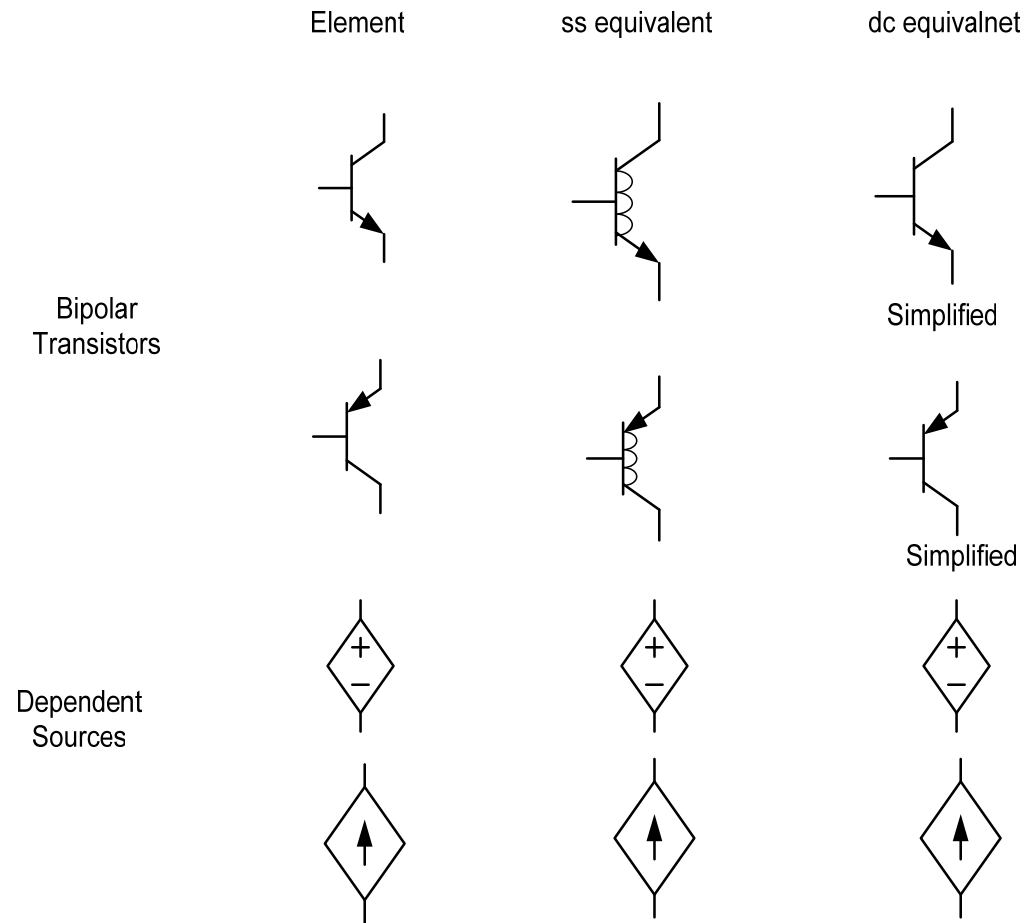
## Dc and small-signal equivalent elements



Review from Last Time:


How is the small-signal equivalent circuit obtained from the nonlinear circuit?

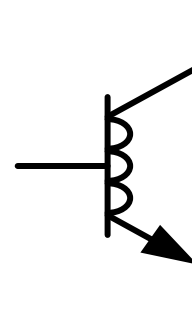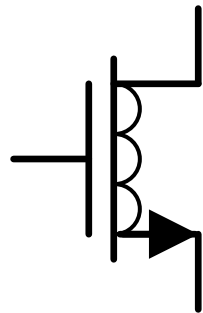*What is the small-signal equivalent of the MOSFET and BJT ?*



Review from Last Time:

4-terminal small-signal network summary

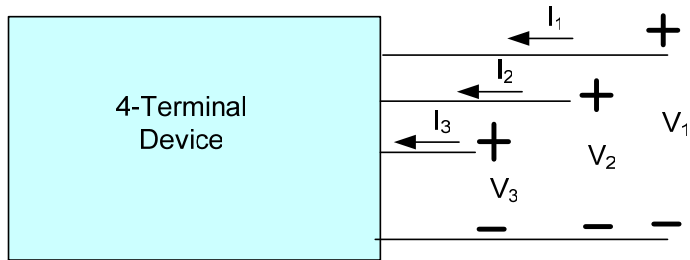


$$\left. \begin{aligned} I_1 &= f_1(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3) \\ I_2 &= f_2(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3) \\ I_3 &= f_3(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3) \end{aligned} \right\}$$

Small signal model:


$$\begin{aligned} i_1 &= y_{11} u_1 + y_{12} u_2 + y_{13} u_3 \\ i_2 &= y_{21} u_1 + y_{22} u_2 + y_{23} u_3 \\ i_3 &= y_{31} u_1 + y_{32} u_2 + y_{33} u_3 \end{aligned}$$

$$y_{ij} = \left. \frac{\partial f_i(\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3)}{\partial \mathbf{V}_j} \right|_{\bar{\mathbf{V}} = \bar{\mathbf{V}}_Q}$$

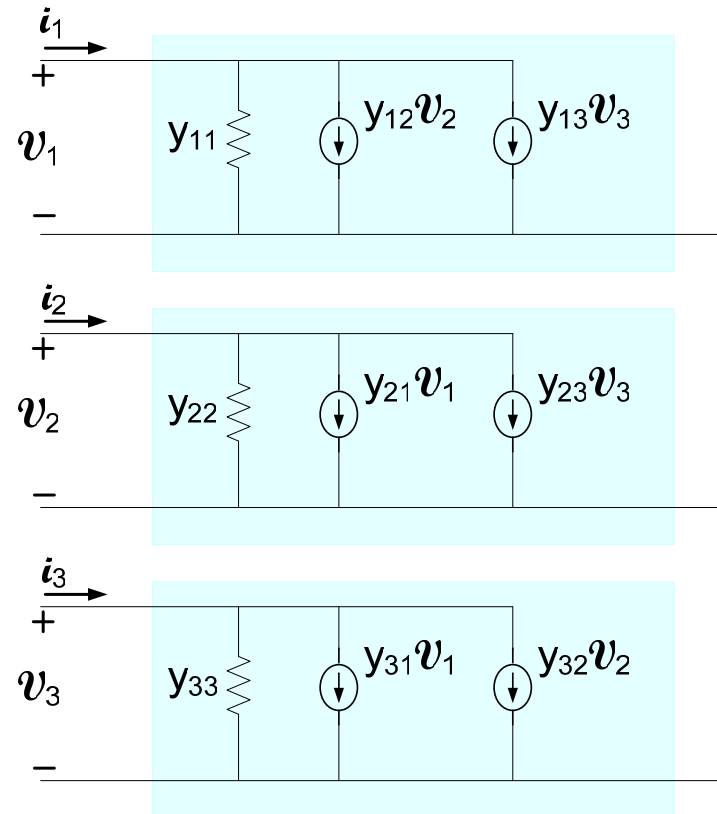

Review from Last Time:
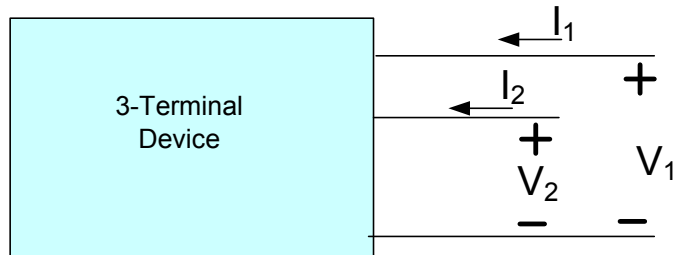
### 3-terminal small-signal network summary




$$\left. \begin{aligned} \mathbf{I}_1 &= \mathbf{f}_1(\mathbf{V}_1, \mathbf{V}_2) \\ \mathbf{I}_2 &= \mathbf{f}_2(\mathbf{V}_1, \mathbf{V}_2) \end{aligned} \right\}$$

### Small signal model:


$$\begin{aligned} \mathbf{i}_1 &= y_{11} \mathbf{v}_1 + y_{12} \mathbf{v}_2 \\ \mathbf{i}_2 &= y_{21} \mathbf{v}_1 + y_{22} \mathbf{v}_2 \end{aligned}$$

$$\mathbf{y}_{ij} = \left. \frac{\partial \mathbf{f}_i(\mathbf{V}_1, \mathbf{V}_2)}{\partial \mathbf{V}_j} \right|_{\bar{\mathbf{v}} = \bar{\mathbf{v}}_Q}$$

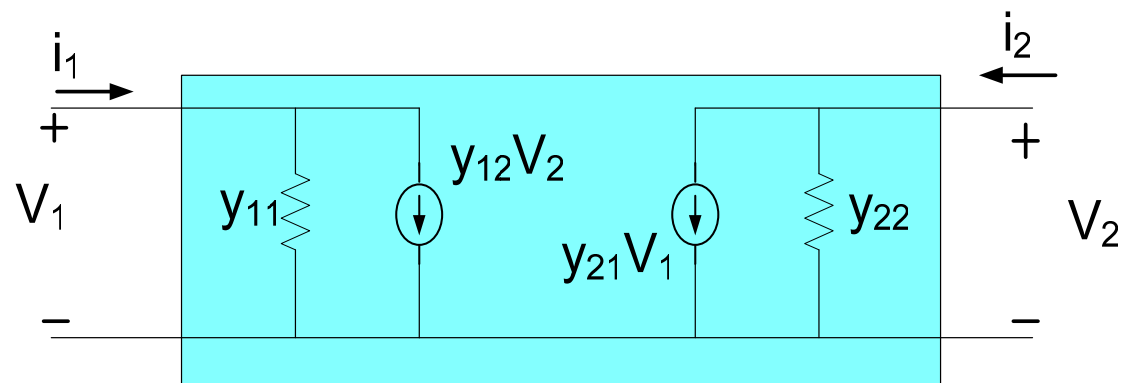

Review from Last Time:  
2-terminal network summary


# Small-Signal Model

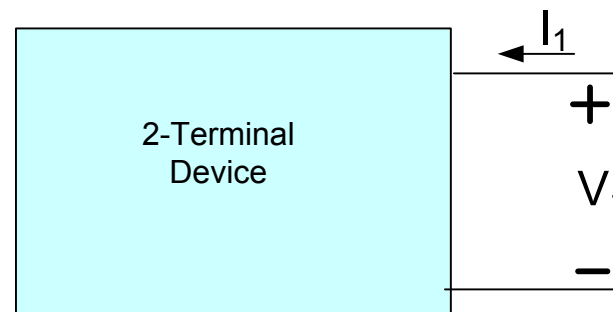

$$\mathbf{i}_1 = y_{11} \mathbf{v}_1$$


$$y_{11} = \left. \frac{\partial f_1(V_1)}{\partial V_1} \right|_{\bar{V} = \bar{V}_Q} \quad \bar{V} = V_{1Q}$$

## A Small Signal Equivalent Circuit

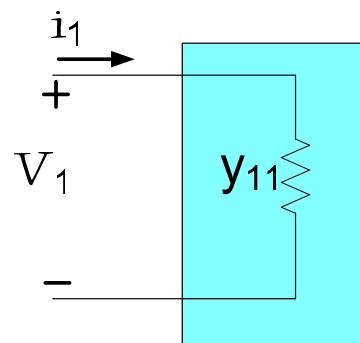

Review from Last Time:


# Small Signal Model of MOSFET

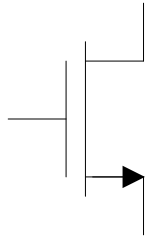

Large Signal Model

$$I_G = 0$$

3-terminal device

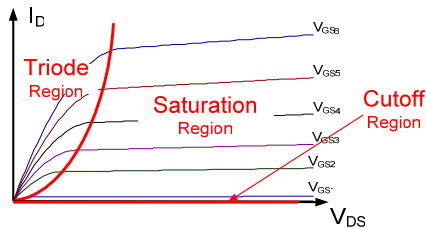


$$I_D = \begin{cases} 0 & V_{GS} \leq V_T \\ \mu C_{OX} \frac{W}{L} \left( V_{GS} - V_T - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} \geq V_T, V_{DS} < V_{GS} - V_T \\ \mu C_{OX} \frac{W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) & V_{GS} \geq V_T, V_{DS} \geq V_{GS} - V_T \end{cases}$$

*MOSFET is usually operated in saturation region in linear applications where a small-signal model is needed so will develop the small-signal model in the saturation region*



Review from Last Time:



# Small Signal Model of MOSFET

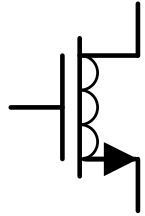

by convention,  $y_{21} = g_m$ ,  $y_{22} = g_o$

$$y_{21} \cong g_m = \mu C_{\text{ox}} \frac{W}{L} (V_{\text{GSQ}} - V_T)$$

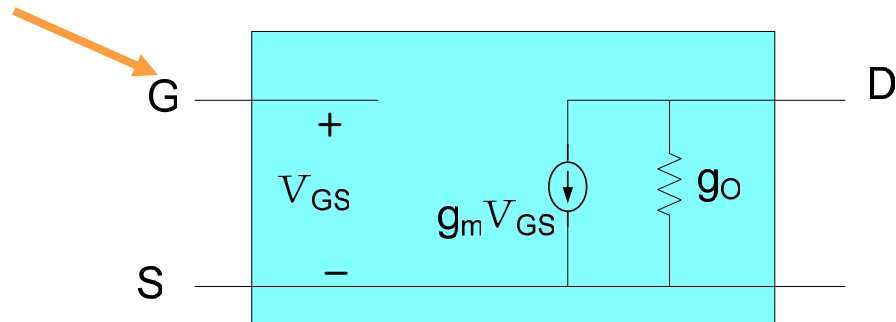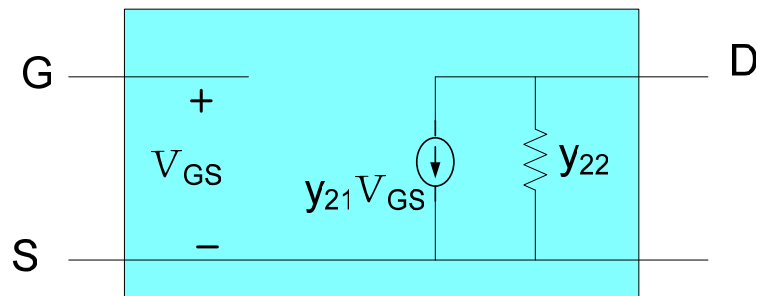
$$y_{22} = g_o \cong \lambda I_{\text{DQ}}$$



$$\begin{aligned} i_G &= 0 \\ i_D &= g_m v_{GS} + g_o v_{DS} \end{aligned}$$


Review from Last Time:

# Small Signal Model of MOSFET

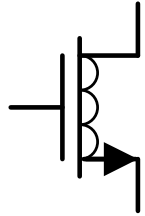

$$g_m = \mu C_{\text{ox}} \frac{W}{L} (V_{\text{GSQ}} - V_T)$$

$$g_o \cong \lambda I_{\text{DQ}}$$

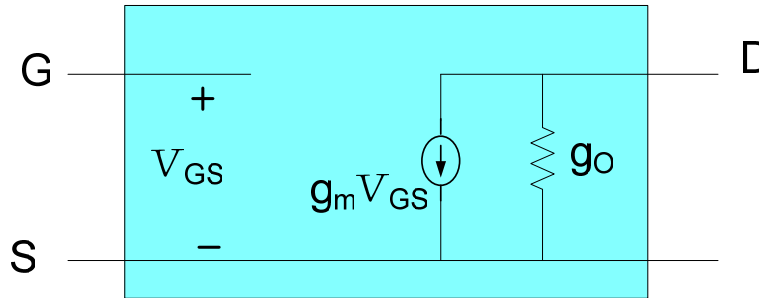

*Alternate equivalent expressions:*

$$I_{\text{DQ}} = \mu C_{\text{ox}} \frac{W}{2L} (V_{\text{GSQ}} - V_T)^2 (1 + \lambda V_{\text{DSQ}}) \cong \mu C_{\text{ox}} \frac{W}{2L} (V_{\text{GSQ}} - V_T)^2$$


$$g_m = \mu C_{\text{ox}} \frac{W}{L} (V_{\text{GSQ}} - V_T)$$

$$g_m = \sqrt{2\mu C_{\text{ox}} \frac{W}{L}} \cdot \sqrt{I_{\text{DQ}}}$$

$$g_m = \frac{2I_{\text{DQ}}}{V_{\text{GSQ}} - V_T}$$

Review from Last Time:

## Small signal analysis example

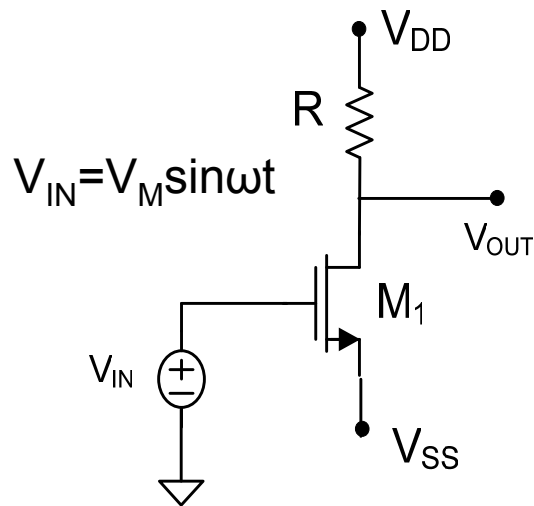

$$A_v = \frac{2I_{DQ} R}{[V_{SS} + V_T]}$$



*Observe the small signal voltage gain is twice the Quiescent voltage across  $R$  divided by  $V_{SS} + V_T$*

- This analysis which required linearization of a nonlinear output voltage is quite tedious.
- This approach becomes unwieldy for even slightly more complicated circuits
- A much easier approach based upon the development of small signal models will provide the same results, provide more insight into both analysis and design, and result in a dramatic reduction in computational requirements

# Small Signal-Large Signal Model of MOSFET in Saturation Region


## Summary
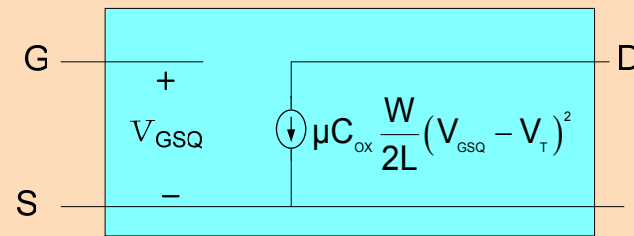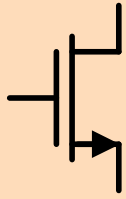
### Large Signal Model for Q-Point Calculations




### Small Signal Model

#### Basic Model

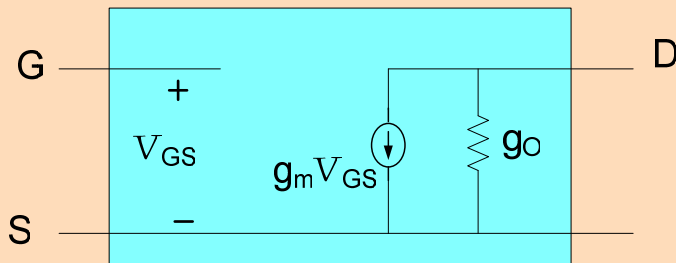


$$g_m = \mu C_{ox} \frac{W}{L} (V_{GSQ} - V_T)$$

$$g_o \cong \lambda I_{DQ}$$

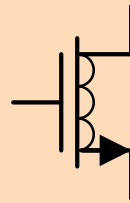


#### Simplified

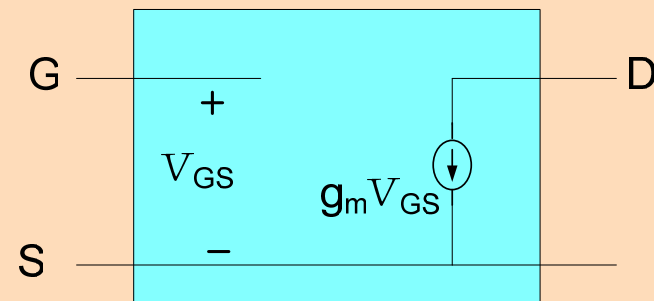

$$g_m = \mu C_{ox} \frac{W}{L} (V_{GSQ} - V_T)$$

Consider again:


## Small signal analysis example

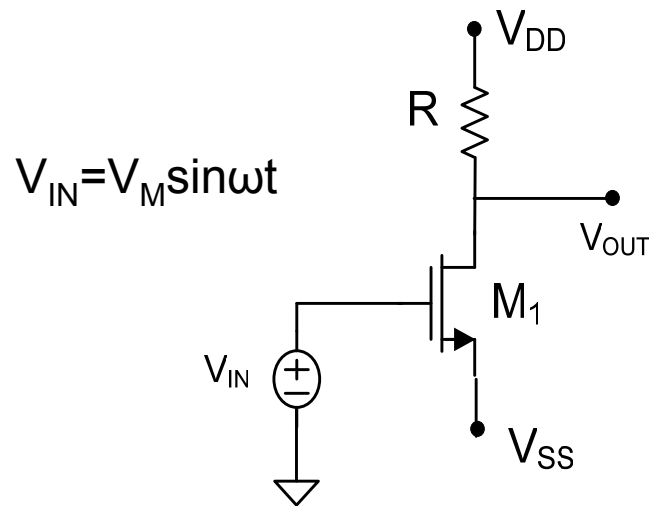

$$A_v = \frac{2I_{DQ} R}{[V_{SS} + V_T]}$$


Derived for  $\lambda=0$  (i.e.  $g_0=0$ )
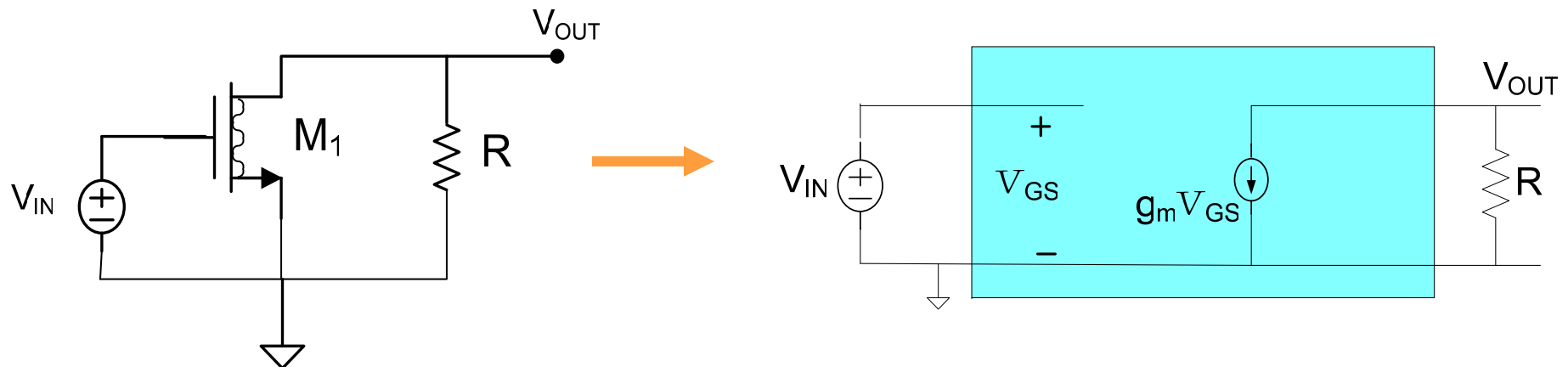
$$I_{DQ} = \mu C_{OX} \frac{W}{2L} (V_{GSQ} - V_T)^2$$




Consider again:


## Small signal analysis example

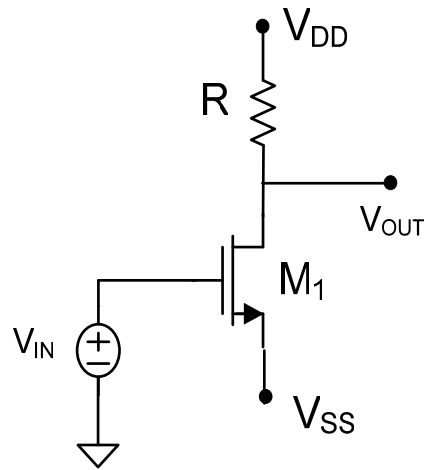
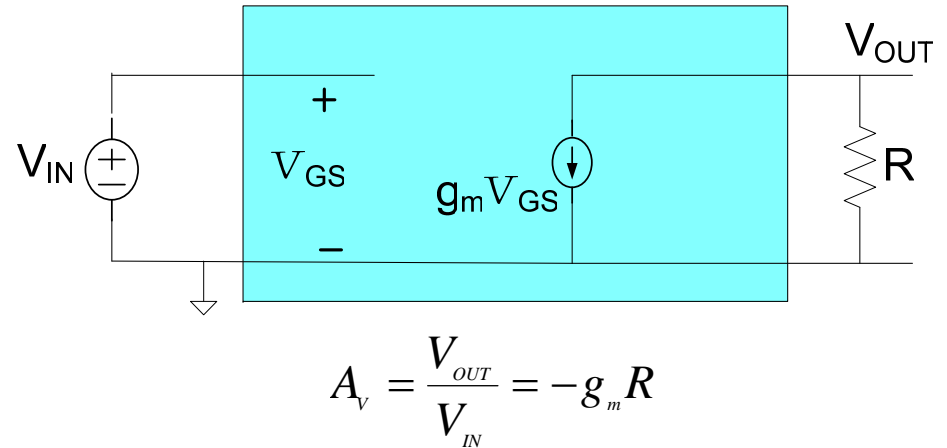
$$A_v = \frac{2I_{DQ} R}{[V_{SS} + V_T]}$$



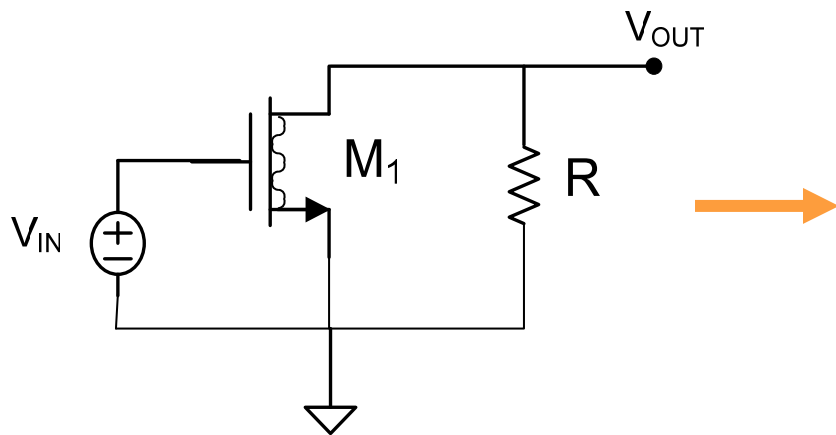*The gain expressions appear to be different !*



but


$$g_m = \frac{2I_{DQ}}{V_{GSQ} - V_T} \quad V_{GSQ} = -V_{SS}$$

thus


$$A_v = \frac{2I_{DQ} R}{[V_{SS} + V_T]}$$

Consider again:

## Small signal analysis example

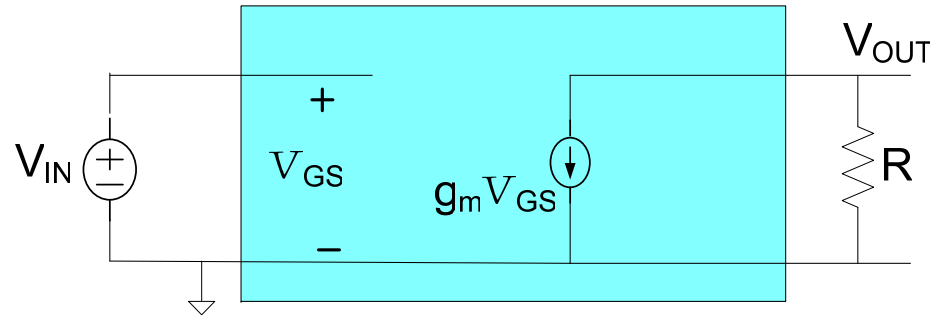
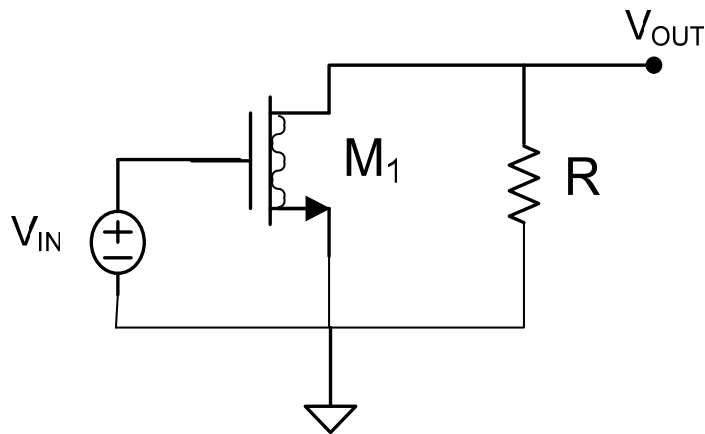
$$A_v = \frac{V_{OUT}}{V_{IN}} = -g_m R$$



$$A_v = \frac{2I_{DQ} R}{[V_{SS} + V_T]}$$


Same expression as derived before

More accurate gain can be obtained if  $\lambda$  effects are included and does not significantly increase complexity of small signal analysis

# Small Signal Model of BJT



*3-terminal device*

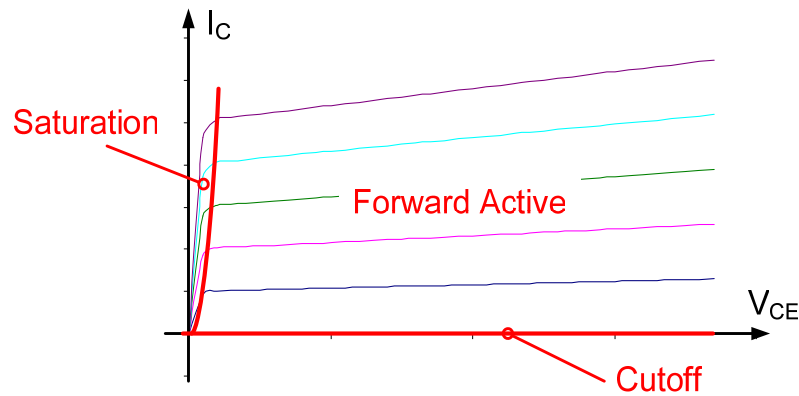

*Forward Active Model:*

$$I_C = J_S A_E e^{\frac{V_{BE}}{V_t}} \left( 1 + \frac{V_{CE}}{V_{AF}} \right)$$
$$I_B = \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}}$$

*Usually operated in Forward Active Region  
when small-signal model is needed*



# Small Signal Model of BJT

$$I_1 = f_1(V_1, V_2) \quad \longleftrightarrow \quad I_B = \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}}$$

$$I_2 = f_2(V_1, V_2) \quad \longleftrightarrow \quad I_C = J_S A_E e^{\frac{V_{BE}}{V_t}} \left( 1 + \frac{V_{CE}}{V_{AF}} \right)$$

*Small-signal model:*

$$y_{ij} = \left. \frac{\partial f_i(V_1, V_2)}{\partial V_j} \right|_{\bar{V}=\bar{V}_Q}$$

$$y_{11} = g_\pi = \left. \frac{\partial I_B}{\partial V_{BE}} \right|_{\bar{V}=\bar{V}_Q}$$

$$y_{12} = \left. \frac{\partial I_B}{\partial V_{CE}} \right|_{\bar{V}=\bar{V}_Q}$$

$$y_{21} = g_m = \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{\bar{V}=\bar{V}_Q}$$

$$y_{22} = g_o = \left. \frac{\partial I_C}{\partial V_{CE}} \right|_{\bar{V}=\bar{V}_Q}$$

# Small Signal Model of BJT

$$I_B = \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}}$$

$$I_C = J_S A_E e^{\frac{V_{BE}}{V_t}} \left( 1 + \frac{V_{CE}}{V_{AF}} \right)$$

*Small-signal model:*


$$g_\pi = \left. \frac{\partial I_B}{\partial V_{BE}} \right|_{\bar{V}=\bar{V}_Q} = \frac{1}{V_t} \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}} \bigg|_{\bar{V}=\bar{V}_Q} = \frac{I_{BQ}}{V_t} \approx \frac{I_{CQ}}{\beta V_t}$$

$$y_{12} = \left. \frac{\partial I_B}{\partial V_{CE}} \right|_{\bar{V}=\bar{V}_Q} = 0$$

$$y_{21} = g_m = \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{\bar{V}=\bar{V}_Q} = \frac{1}{V_t} J_S A_E e^{\frac{V_{BE}}{V_t}} \left( 1 + \frac{V_{CE}}{V_{AF}} \right) \bigg|_{\bar{V}=\bar{V}_Q} = \frac{I_{CQ}}{V_t}$$

$$y_{22} = g_o = \left. \frac{\partial I_C}{\partial V_{CE}} \right|_{\bar{V}=\bar{V}_Q} = \frac{J_S A_E e^{\frac{V_{BE}}{V_t}}}{V_{AF}} \bigg|_{\bar{V}=\bar{V}_Q} \approx \frac{I_{CQ}}{V_{AF}}$$

# Small Signal Model of BJT

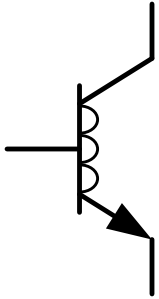

$$\begin{aligned} i_B &= y_{11} v_{BE} + y_{12} v_{CE} \\ i_C &= y_{21} v_{BE} + y_{22} v_{CE} \end{aligned}$$




$$\begin{aligned} i_B &= g_\pi v_{BE} \\ i_C &= g_m v_{BE} + g_o v_{CE} \end{aligned}$$

$$g_\pi = \frac{I_{CQ}}{\beta V_t}$$



$$g_m = \frac{I_{CQ}}{V_t}$$

$$g_o = \frac{I_{CQ}}{V_{AF}}$$

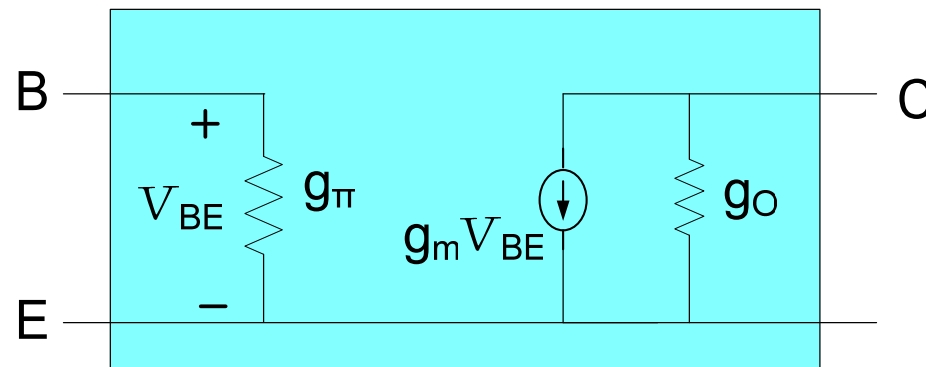

$g_o$  can often be neglected !


# Alternate Small Signal Model of BJT

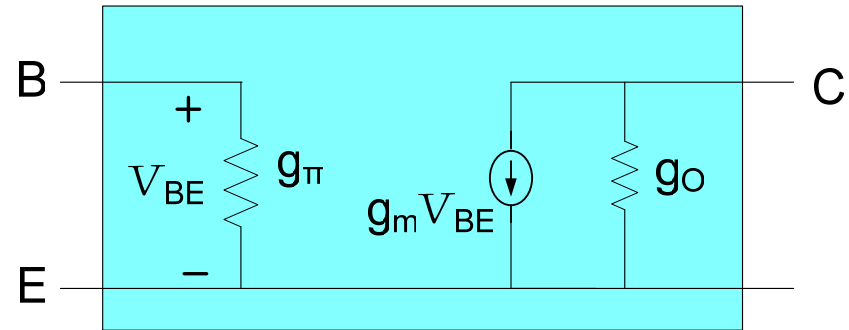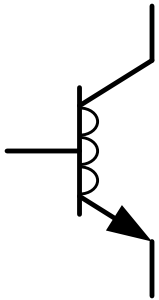

$$g_{\pi} = \frac{I_{CQ}}{\beta V_t} \quad g_m = \frac{I_{CQ}}{V_t} \quad g_o = \frac{I_{CQ}}{V_{AF}}$$


Observe:  $g_m V_{BE} = g_m \frac{I_B}{g_{\pi}} = \beta I_B$

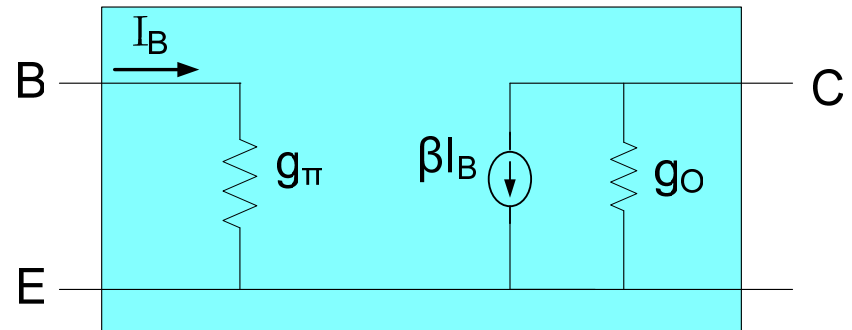*Alternate Equivalent Small-signal Model*



$$g_{\pi} = \frac{I_{CQ}}{\beta V_t} \quad g_o = \frac{I_{CQ}}{V_{AF}}$$
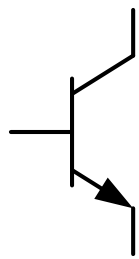
# Large Signal Model of BJT in Forward Active Region for Q-point Calculations



$$I_B = \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}}$$

$$I_C = J_S A_E e^{\frac{V_{BE}}{V_t}} \left( 1 + \frac{V_{CE}}{V_{AF}} \right)$$




$$I_B = \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}}$$

$$I_C = \beta I_B$$

But when operating in Forward Active Region,  $V_{BE}$  will be around 0.6V


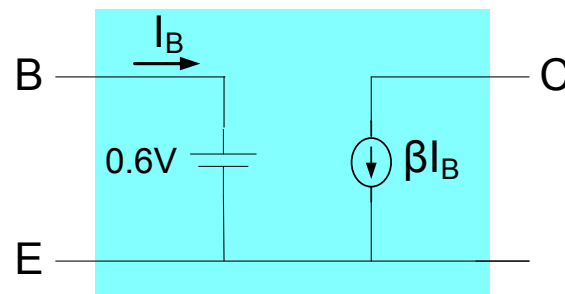
In most applications, the following model is adequate for Q-point calculations



# Small Signal-Large Signal Model of BJT in Forward Active Region


## Summary
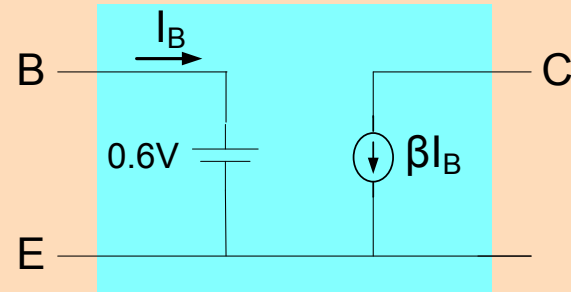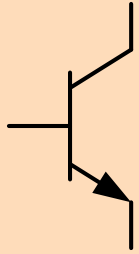
### Large Signal Model for Q-Point Calculations




### Small Signal Model

#### Basic Model

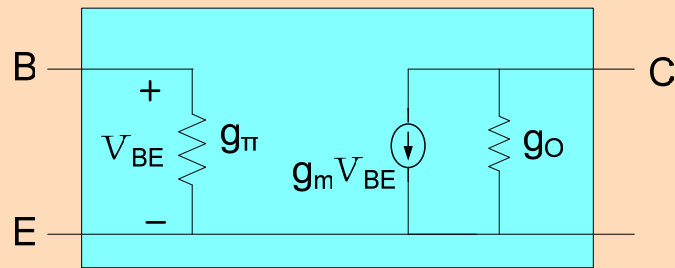

$$g_{\pi} = \frac{I_{CQ}}{\beta V_t} \quad g_m = \frac{I_{CQ}}{V_t} \quad g_o = \frac{I_{CQ}}{V_{AF}}$$

#### Simplified

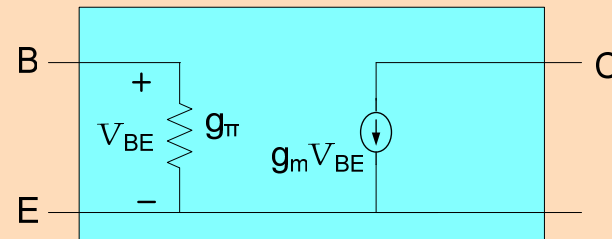

$$g_{\pi} = \frac{I_{CQ}}{\beta V_t} \quad g_m = \frac{I_{CQ}}{V_t}$$

# Small-signal Operation of Nonlinear Circuits

- Small-signal principles
  - Example Circuit
  - Small-Signal Models
- Small-Signal Analysis of Nonlinear Circuits


Recall:

## **Standard Approach to small-signal analysis of nonlinear networks**

- 1. Linearize nonlinear devices**  
*(have small-signal model for key devices!)*
- 2. Replace all devices with small-signal equivalent**
- 3. Solve linear small-signal network**




Example:

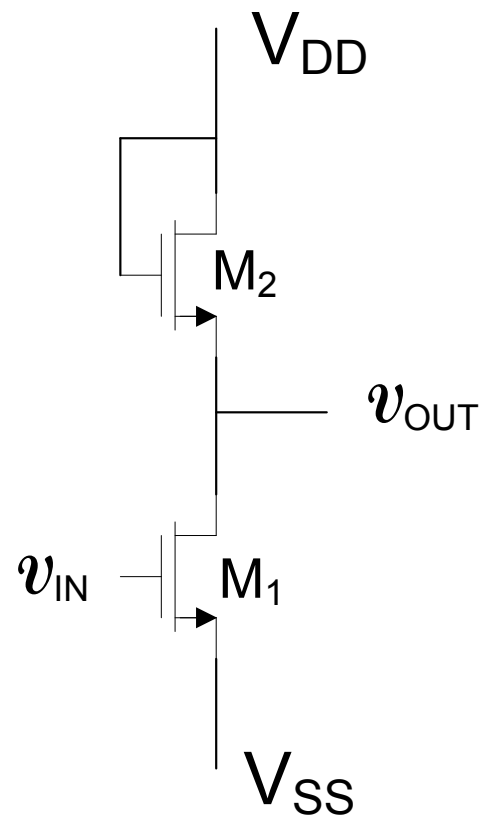




Determine the small signal voltage gain  $A_V = v_{OUT}/v_{IN}$ . Assume  $M_1$  and  $M_2$  are operating in the saturation region and that  $\lambda=0$

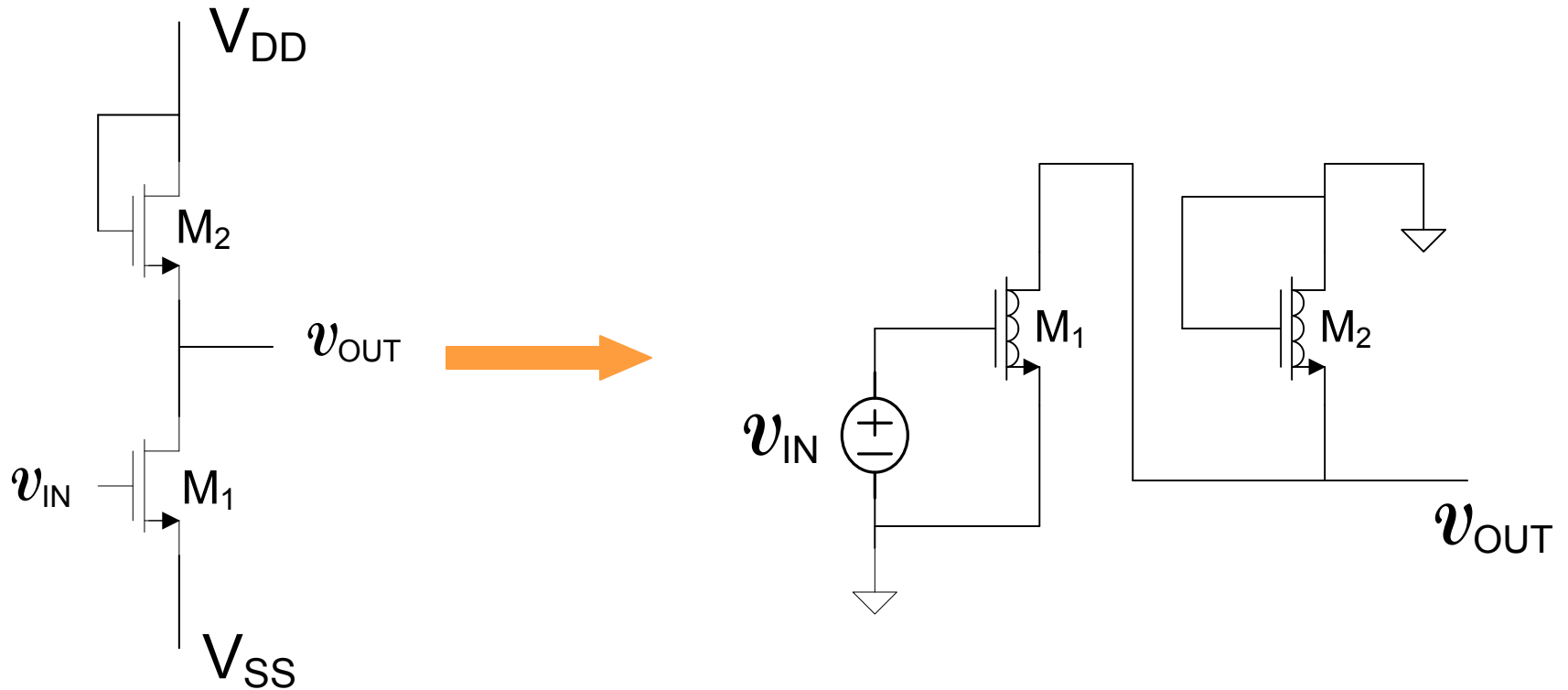**Example:** Determine the small signal voltage gain  $A_V = v_{OUT}/v_{IN}$ . Assume  $M_1$  and  $M_2$  are operating in the saturation region and that  $\lambda=0$





*Small-signal circuit*

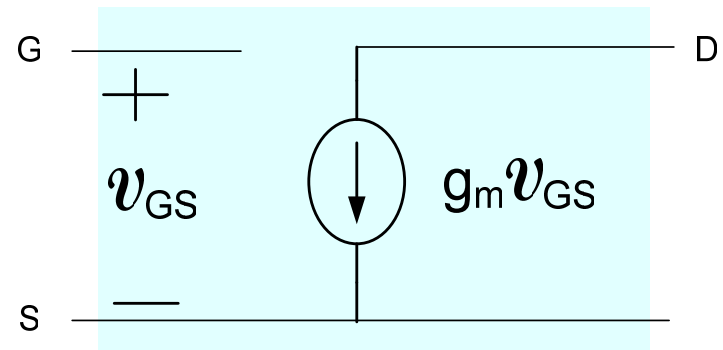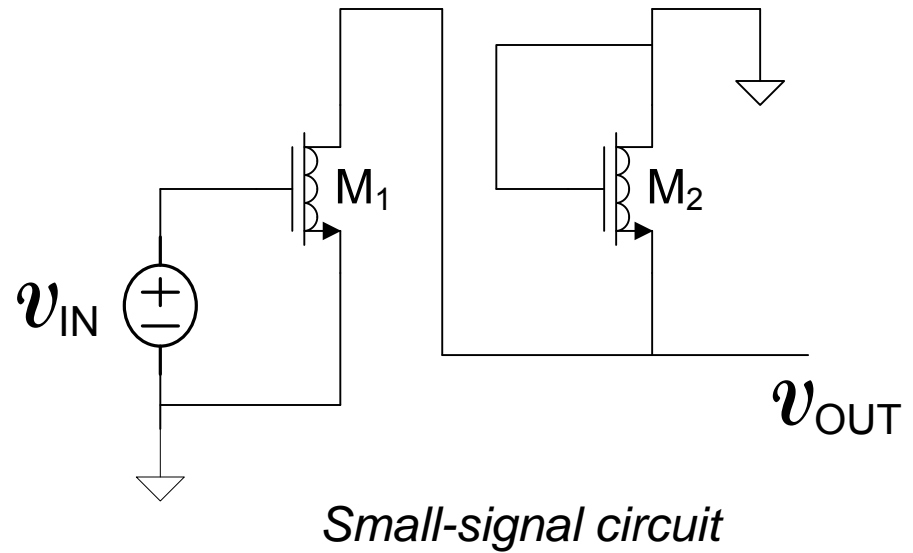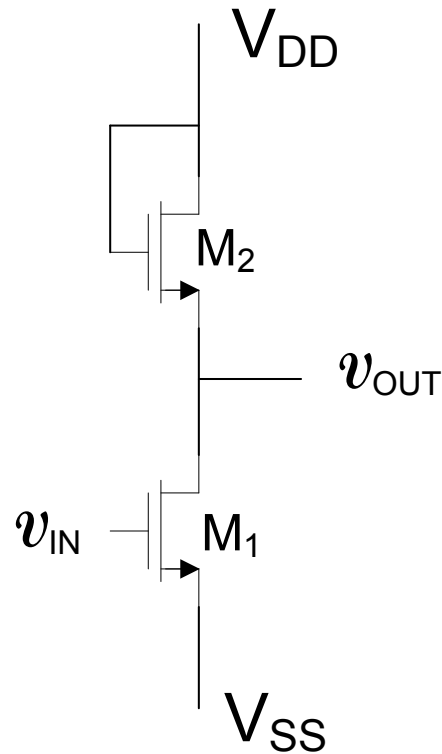**Example:** Determine the small signal voltage gain  $A_V = v_{OUT}/v_{IN}$ . Assume  $M_1$  and  $M_2$  are operating in the saturation region and that  $\lambda=0$




*Small-signal MOSFET model for  $\lambda=0$*

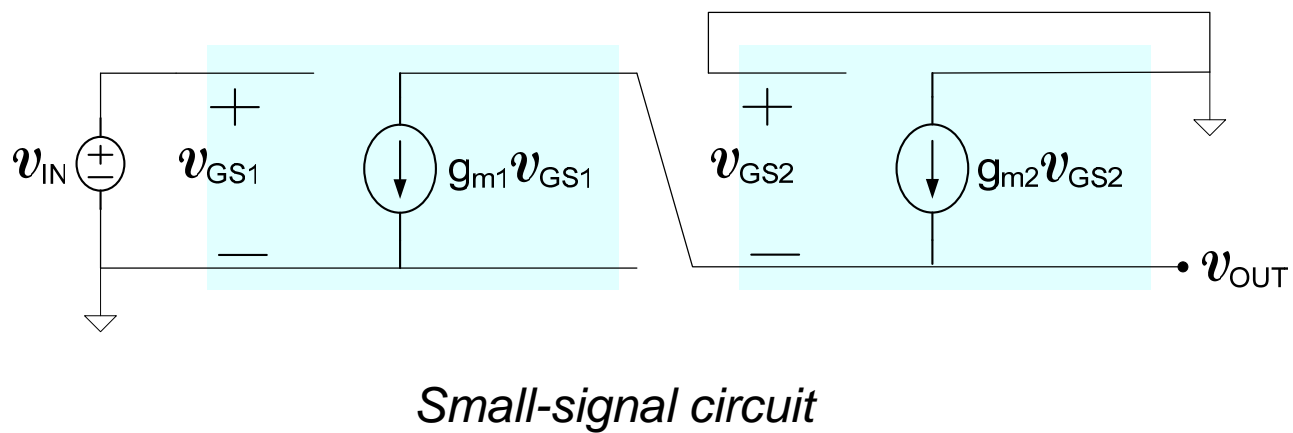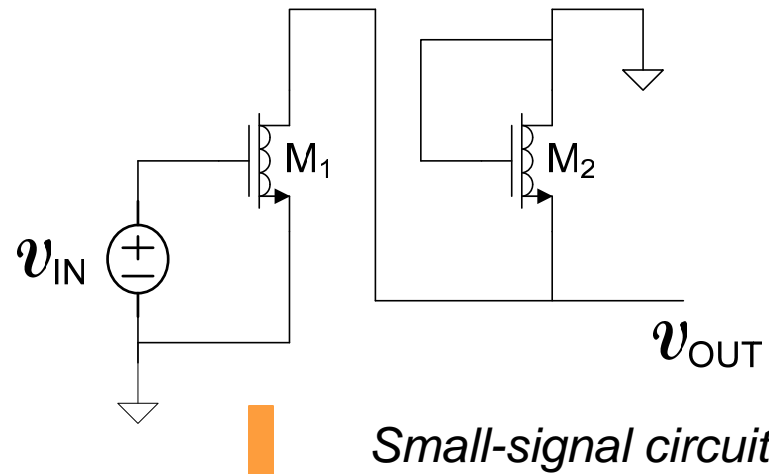Example: Determine the small signal voltage gain  $A_V = v_{OUT}/v_{IN}$ . Assume  $M_1$  and  $M_2$  are operating in the saturation region and that  $\lambda=0$



Example:

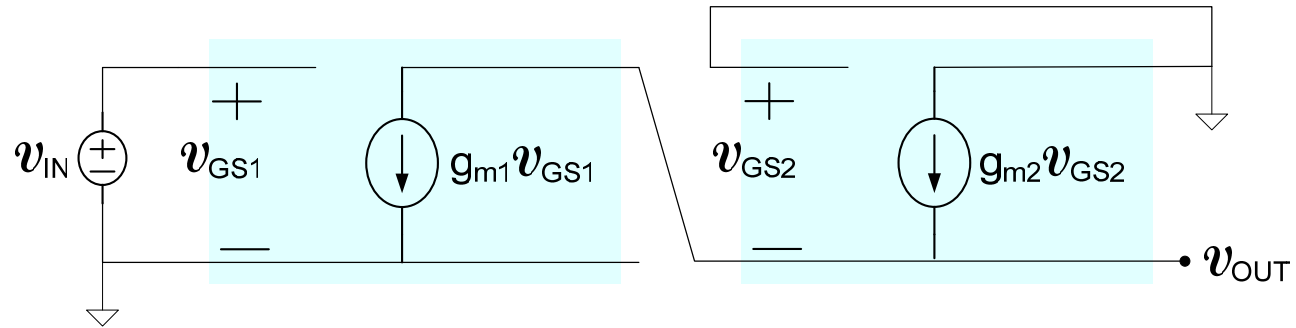

*Small-signal circuit*

*Analysis:*

*By KCL*

$$g_{m1} v_{GS1} = g_{m2} v_{GS2}$$

*but*


$$v_{GS1} = v_{IN}$$

$$-v_{GS2} = v_{OUT}$$

*thus:*

$$A_V = \frac{v_{OUT}}{v_{IN}} = -\frac{g_{m1}}{g_{m2}}$$

Example:

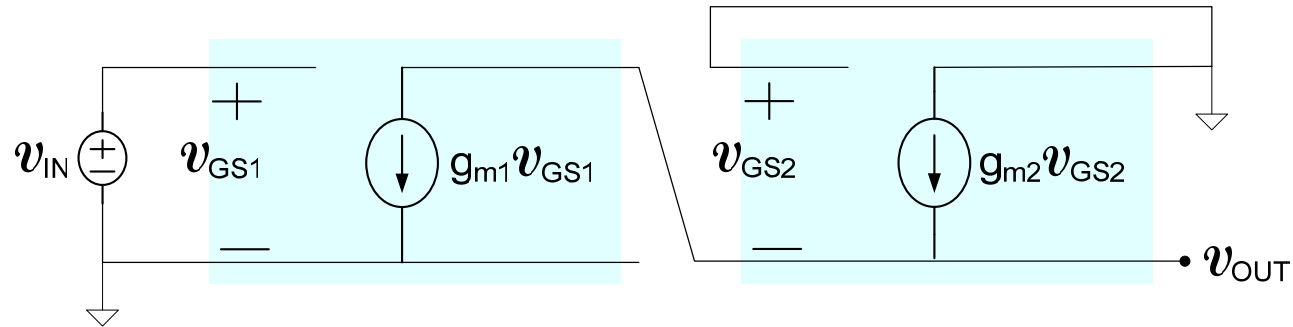


*Analysis:* *Small-signal circuit*

$$A_V = \frac{v_{OUT}}{v_{IN}} = -\frac{g_{m1}}{g_{m2}}$$

*Recall:*  $g_m = -\sqrt{2I_D \mu C_{ox}} \sqrt{\frac{W_1}{L_1}}$

$$A_V = -\frac{\sqrt{2I_D \mu C_{ox} \frac{W_1}{L_1}}}{\sqrt{2I_D \mu C_{ox} \frac{W_2}{L_2}}} = -\sqrt{\frac{W_1}{W_2}} \sqrt{\frac{L_2}{L_1}}$$

Example:

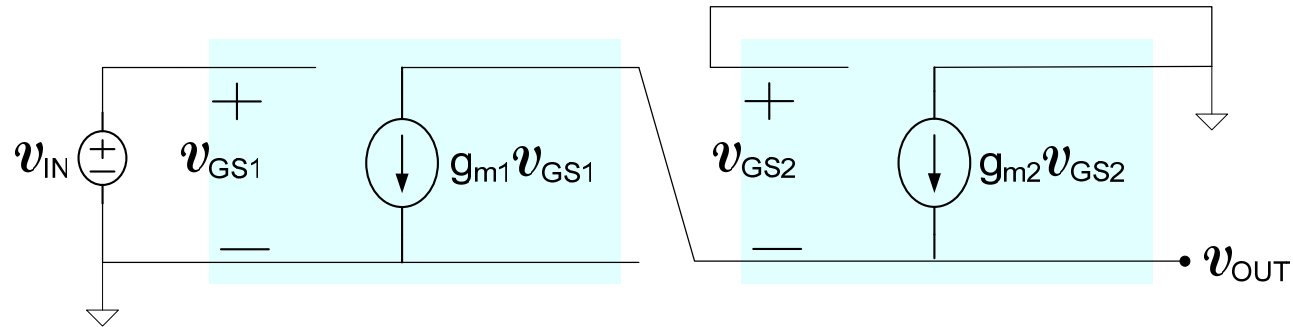

*Small-signal circuit*

*Analysis:*

$$A_V = \frac{v_{OUT}}{v_{IN}} = -\frac{g_{m1}}{g_{m2}}$$

$$A_V = -\sqrt{\frac{W_1}{W_2}} \sqrt{\frac{L_2}{L_1}}$$

*If  $L_1=L_2$ , obtain*

$$A_V = -\sqrt{\frac{W_1}{W_2}} \sqrt{\frac{L_2}{L_1}} = -\sqrt{\frac{W_1}{W_2}}$$

*The width and length ratios can be accurately set when designed in a standard CMOS process*

**End of Lecture 34**