

EE 230

Lecture 36


Data Converters

Review from Last Time:

Small Signal Model of BJT



3-terminal device

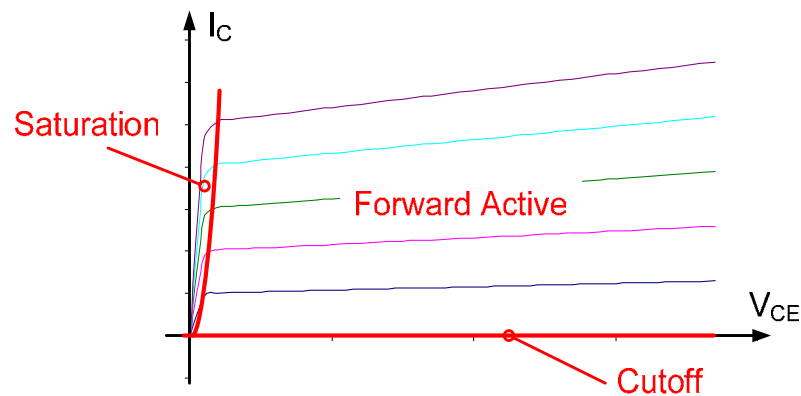

Forward Active Model:


$$I_C = J_S A_E e^{\frac{V_{BE}}{V_t}} \left(1 + \frac{V_{CE}}{V_{AF}} \right)$$

$$I_B = \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}}$$

*Usually operated in Forward Active Region
when small-signal model is needed*

Review from Last Time:

Small Signal Model of BJT

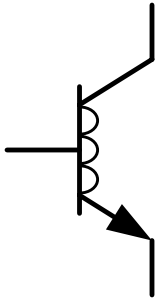

$$\begin{aligned} i_B &= g_\pi v_{BE} \\ i_C &= g_m v_{BE} + g_o v_{CE} \end{aligned}$$



$$g_\pi = \frac{I_{CQ}}{\beta V_t} \quad g_m = \frac{I_{CQ}}{V_t} \quad g_o = \frac{I_{CQ}}{V_{AF}}$$

Observe

$$g_m v_{BE} = g_m \left[\frac{i_b}{g_\pi} \right] = \left[\frac{g_m}{g_\pi} \right] i_b$$

$$\frac{g_m}{g_\pi} = \frac{I_{CQ} / V_t}{I_{CQ} / \beta V_t} = \beta$$

$$\therefore g_m v_{BE} = \beta i_b$$

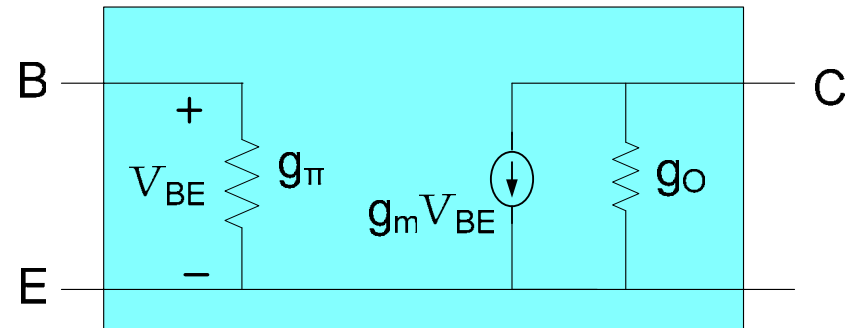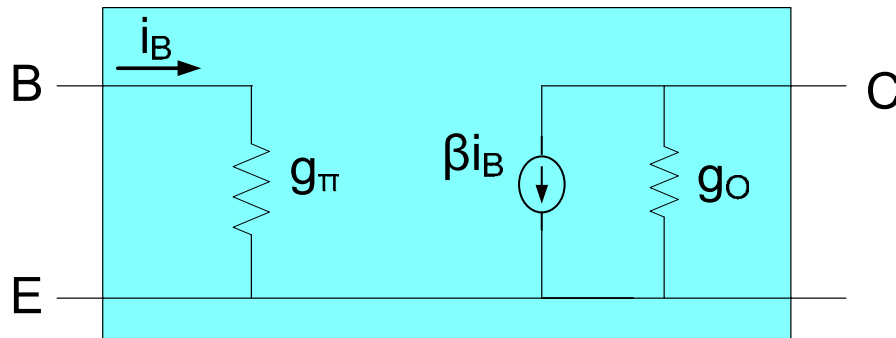

Alternate equivalent small-signal models of the BJT

Review from Last Time:


Recall:

Alternative Approach to small-signal analysis of nonlinear networks


- 1. Linearize nonlinear devices**
(have small-signal model for key devices!)
- 2. Replace all devices with small-signal equivalent**
- 3. Solve linear small-signal network**

Data Converters

Standard Symbols:

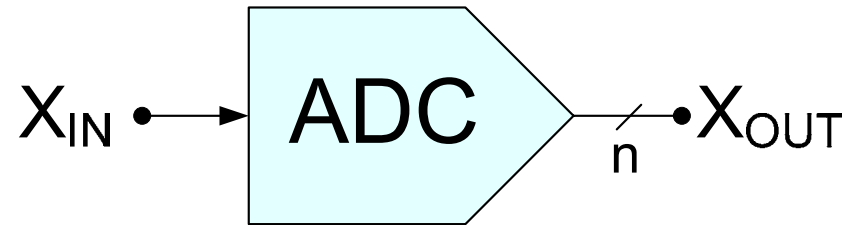


Analog to Digital Converter

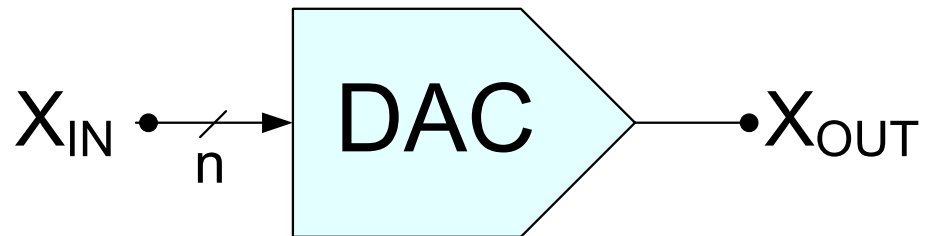

Digital to Analog Converter

Data Converters

Other Symbols:

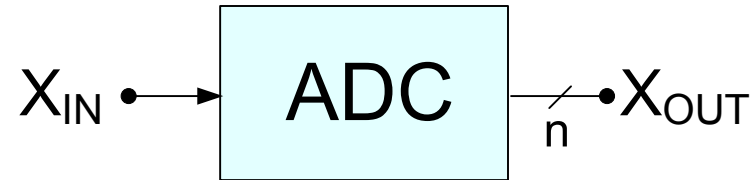

Analog to Digital Converter



Digital to Analog Converter

Data Converters




	X_{IN}	X_{OUT}
ADC	Analog	Digital
DAC	Digital	Analog

Analog variables: Voltage, Current, time, charge, occasionally other physical variables



Digital variables: Usually represented in binary form but other forms occasionally used (e.g. gray, Thermometer code)

Data Converters

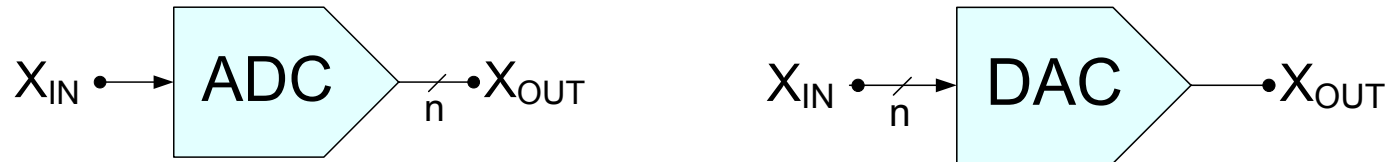

Applications: Dominantly the interfaces between the continuous-time Continuous-amplitude physical environment and a digital system such as a computer, microprocessor, microcontroller, or finite state machine

Data Converters

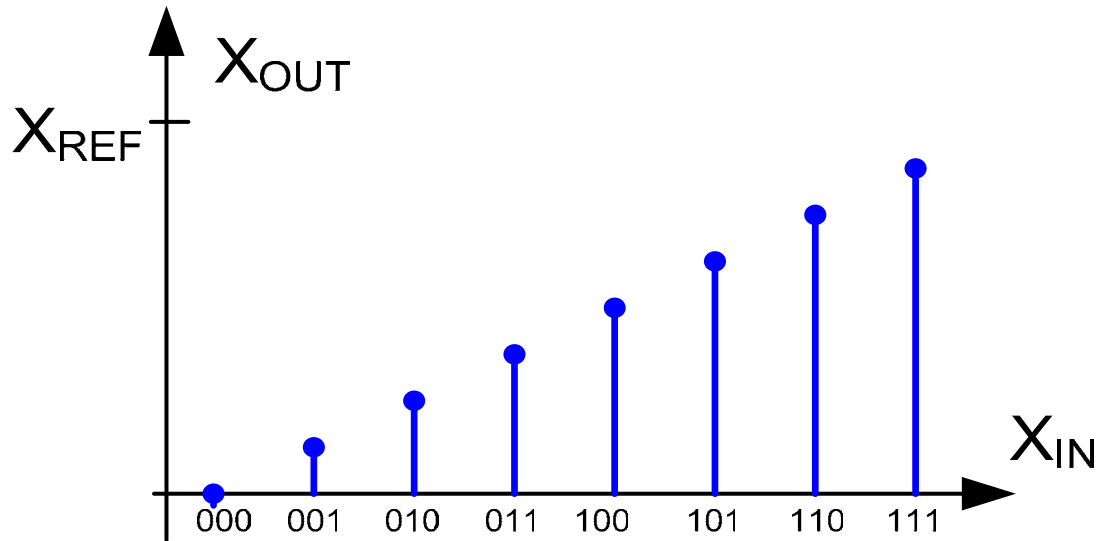
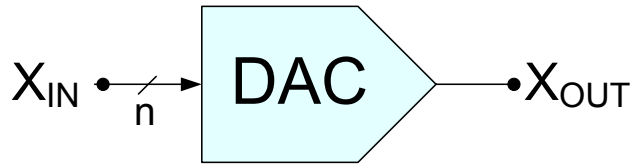


B: $[b_1 b_2 \dots b_n]$

An ideal DAC

(Some specific shifted versions of this DAC would also be termed an ideal DAC)

Data Converters

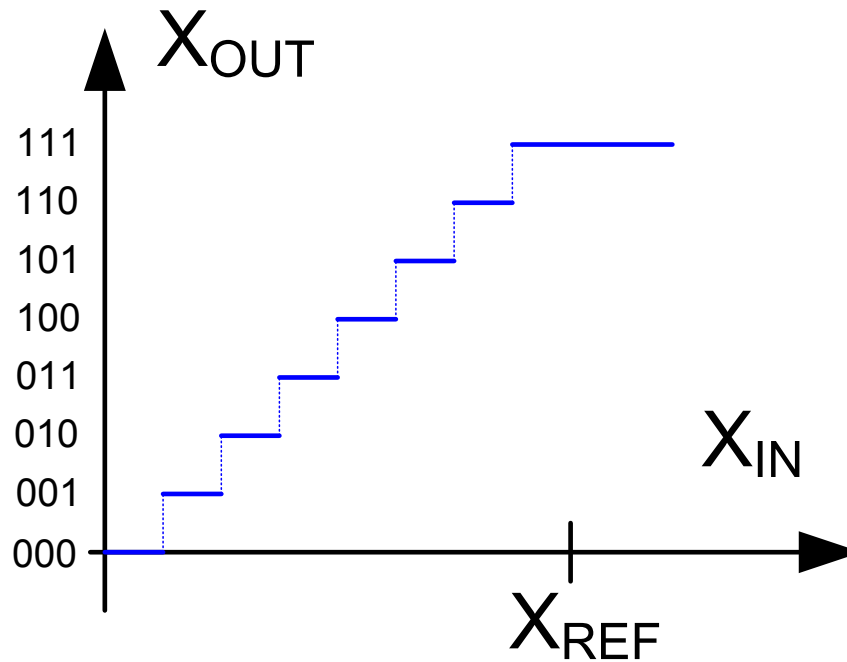
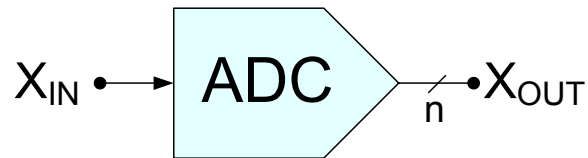


B: $[b_1 b_2 \dots b_n]$

An ideal ADC

(Some specific shifted versions of this ADC would also be termed an ideal ADC)

Data Converters

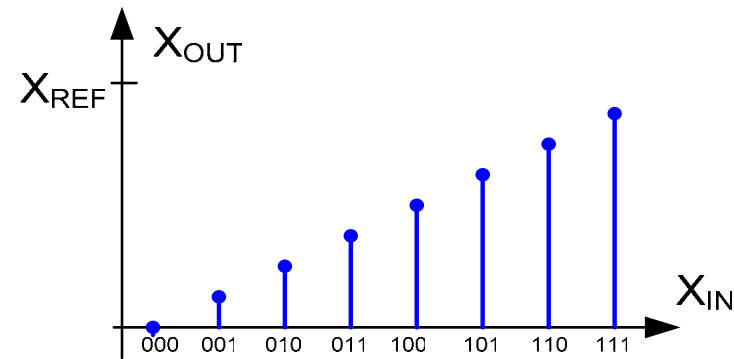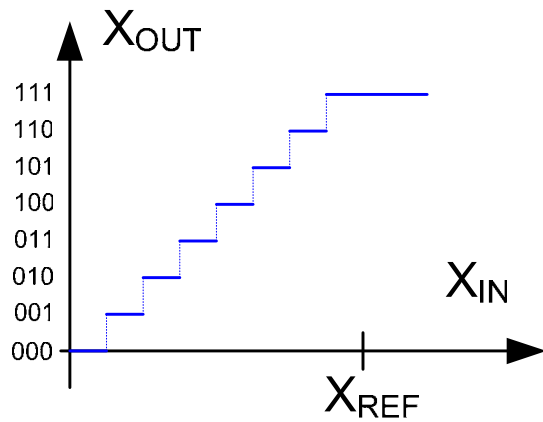

Terminology:

B: $[b_1 b_2 \dots b_n]$

b_1 : Most Significant Bit (MSB)



b_n : Least Significant Bit (LSB)

Resolution: Defines number of distinct levels for DAC or Boolean outputs for ADC. If there are N distinct levels, resolution generally defined as $n = \log_2 N$ thus, $N = 2^n$

X_{REF} : specifies the full-scale range of the data converter. Input range for ADC or output range for DAC is usually

$$X_{REF} \left(\frac{2^n - 1}{2^n} \right) \stackrel{n \text{ large}}{\approx} X_{REF}$$

Data Converters

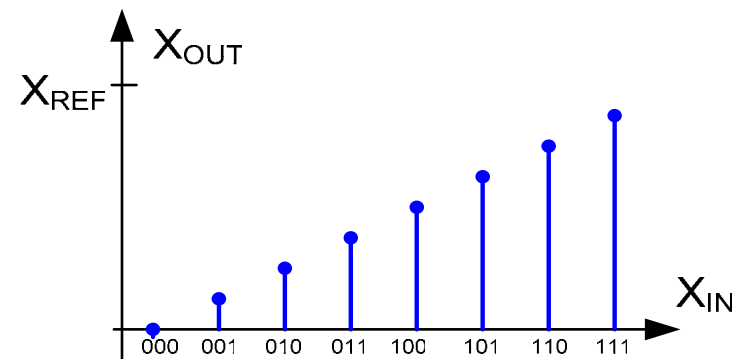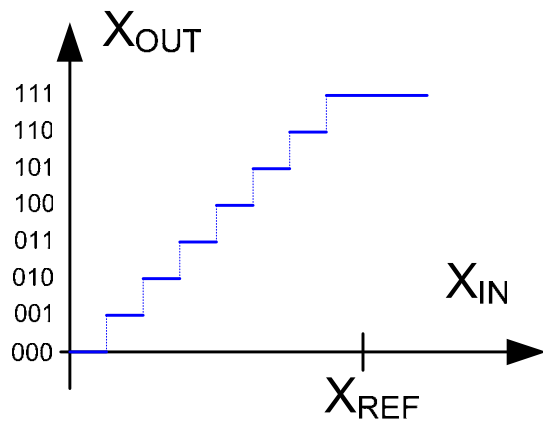

Terminology:

LSB (or X_{LSB}) : Analog change (in input to ADC or output of DAC) corresponding to one LSB digital change

$$X_{\text{LSB}} = \frac{X_{\text{REF}}}{2^n}$$

Transition Points (for ADC): values of X_{IN} where output changes by 1 LSB (an n-bit ADC has N-1 transition points partitioning input into N distinct intervals)

Decimal Equivalent: Decimal equivalent of **B**: $[b_1 b_2 \dots b_n]$



$$D(\mathbf{B}) = \left(\frac{b_1}{2} + \frac{b_2}{4} + \dots + \frac{b_n}{2^n} \right) \quad \longrightarrow \quad D(\mathbf{B}) = \sum_{k=1}^n \frac{b_k}{2^k}$$

Number of levels for different resolution

n	N	
1	2^1	2
2	2^2	4
3	2^3	8
4	2^4	16
5	2^5	32
6	2^6	64
7	2^7	128
8	2^8	256
9	2^9	512

n	N	
10	2^{10}	1024
11	2^{11}	2048
12	2^{12}	4096
13	2^{13}	8192
14	2^{14}	16384
15	2^{15}	32768
16	2^{16}	65536
20	2^{20}	1,048,576
24	2^{24}	16,772,216

Data Converters

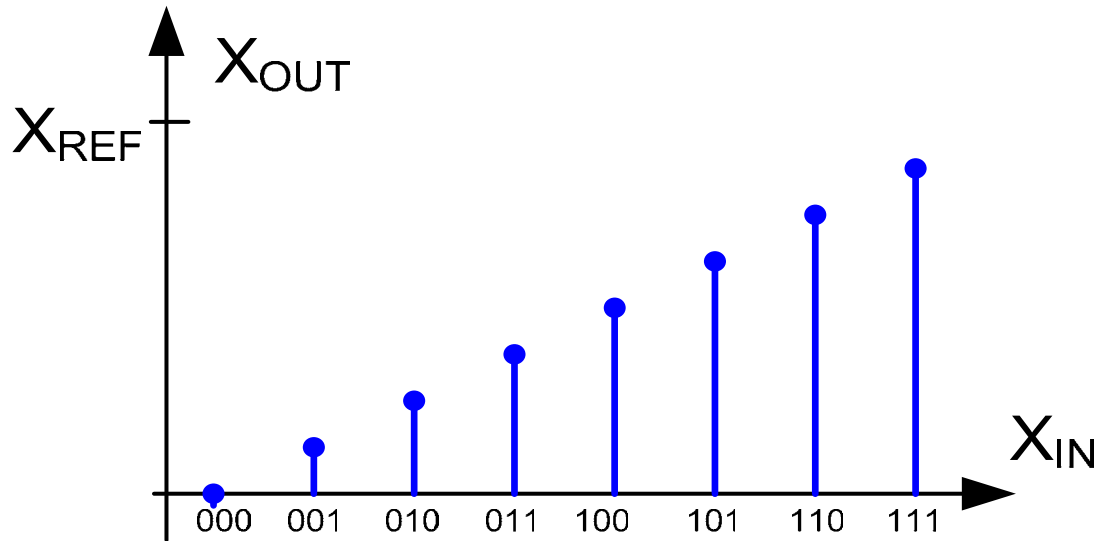
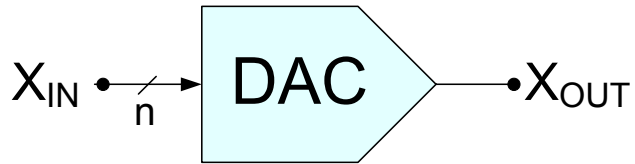


B: $[b_1 b_2 \dots b_n]$

An ideal DAC

$$X_{OUT} = X_{REF} D(X_{IN}) = X_{REF} \sum_{k=1}^n \frac{b_k}{2^k}$$

Data Converters

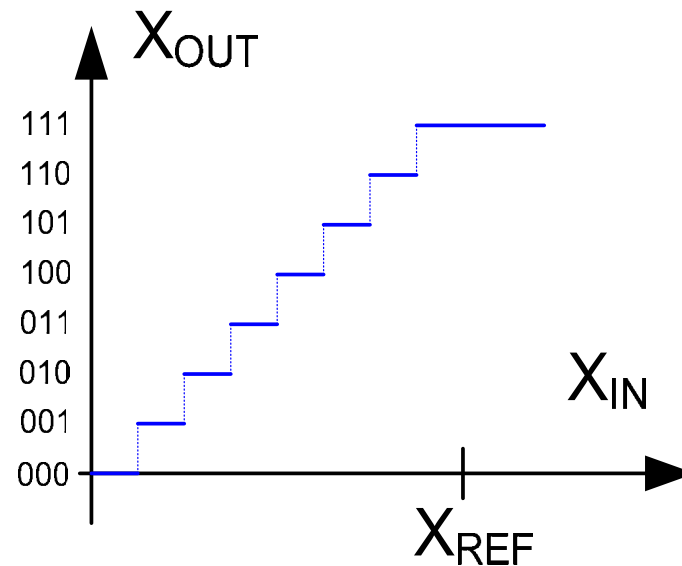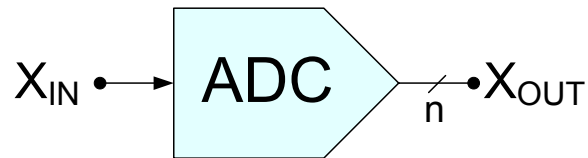

B: $[b_1 b_2 \dots b_n]$

An ideal ADC

$$X_{\text{OUT}} = B$$

$$X_{\text{REF}} D(B) < X_{\text{IN}} < X_{\text{REF}} D(B) + X_{\text{LSB}}$$

Example

Determine V_{LSB} for a 16-bit ADC if X_{REF} is a voltage of 1V.

$$X_{\text{LSB}} = \frac{1\text{V}}{2^{16}} = 15.25\mu\text{V}$$

Observe X_{LSB} is very small and for a 16-bit ADC, must resolve an input signal to $\pm X_{\text{LSB}}/2 = \pm 7.5\mu\text{V}$

Example

Determine the number of bits of resolution, n , required in an ADC if it is to be used in a DMM that has accuracy corresponding to m decimal digits

Resolution of an m -digit DMM is $V_{REF}/10^m$

Thus equating the resolution of an ADC represented in binary form to that of the DMM, we obtain the expression

$$\frac{V_{REF}}{2^n} = \frac{V_{REF}}{10^m}$$

It thus follows that $m = n \log_{10} 2$

Solving for n , we obtain $n = \frac{m}{\log_{10} 2}$

If $m=6$, $n=20$

If $m=7$, $n=23+$

If $V_{REF}=1V$, $V_{LSB}=0.95\mu V$

If $V_{REF}=1V$, $V_{LSB}=112nV$

Very high resolution is required in applications such as this!

Data Converters

Discrete implementations of data converters are seldom used

- Not cost effective
- Too large
- Vary difficult to maintain acceptable accuracies of components

Integrated data converters usually have voltage or current as input or output variables

- If conversion of other physical units is required, a transducer precedes or follows a voltage or current data converter